

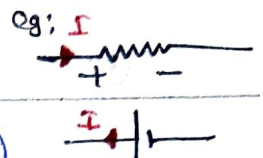


Basic concepts of Network

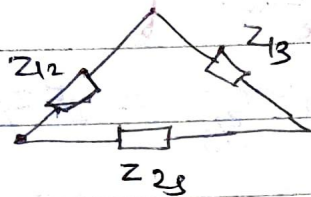- (i) If current enters +ve terminal $P = \text{absorbed}$
 If current leaves +ve terminal $P = \text{delivered}$



(i) Y to Δ conversion

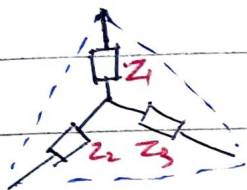


$$Z_{12} = \frac{Z_1 Z_2 + Z_2 Z_3 + Z_1 Z_3}{Z_3}$$

Samne wali Khidki me



(ii) Δ to Y conversion

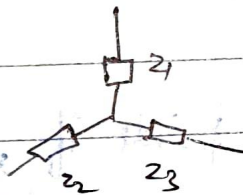




$$Z_1 = \frac{Z_{12} Z_{13}}{Z_{12} + Z_{23} + Z_{13}}$$

Adosi Padosi




* Note in both (i) & (ii) N^o contains $\Omega \times \Omega$ { Z^2 terms }

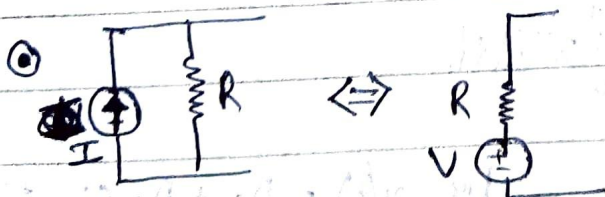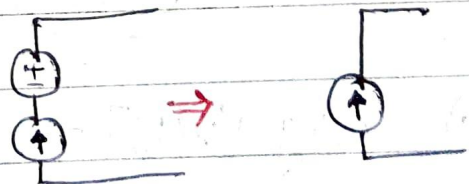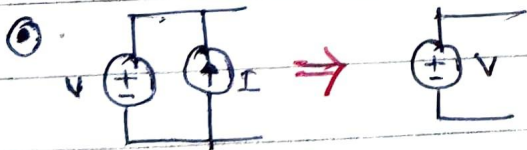STAR $\xrightarrow[\text{C} \times 3]{\text{R} \times 3}$ DELTA $\xrightarrow[\text{C} \times 3]{\text{R} / 3}$ STAR




where $V = IR$
 $I = V/R$

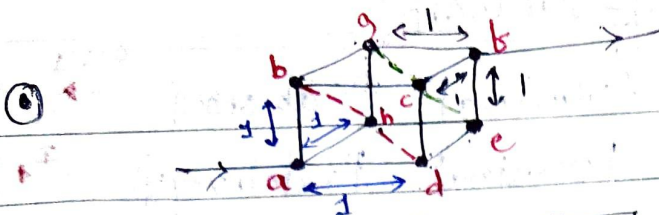
* Source transformation is not valid for controlling variable branch but it is valid for dependent source




equipotential pnts

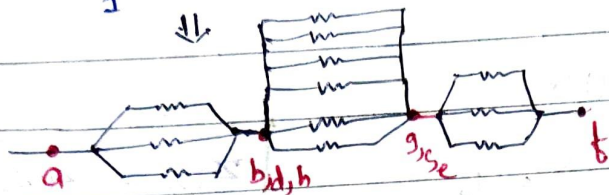

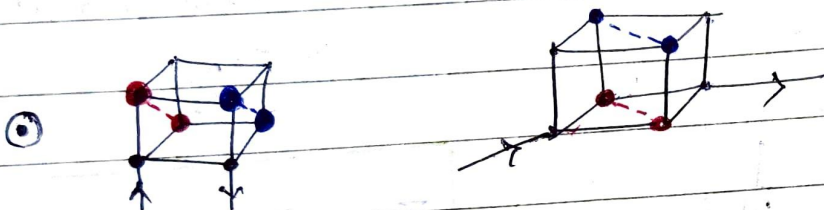
$$\frac{Z}{3} + \frac{Z}{6} + \frac{Z}{3} = \frac{5Z}{6}$$



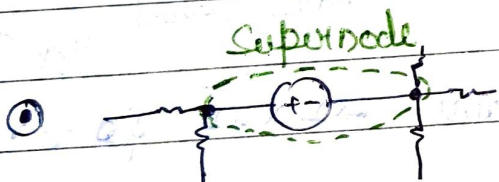Note: b & h are equipot. points if $\left[\begin{array}{l} \text{distance } ab = ah \\ \text{distance } fb = fh \end{array} \right]$



Supernode = KCL + KVL + Ohm's law

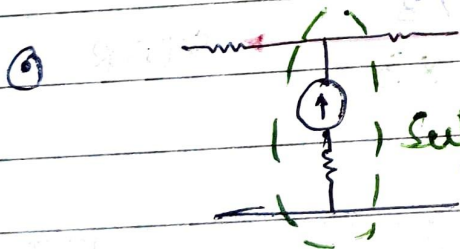

Supermesh = KVL + Ohm's law + KCL

⑤

$$\text{Avg}[x(t)] = \frac{1}{T} \int_0^T x(t) dt$$

$$\text{RMS}[x(t)] = \sqrt{\frac{1}{T} \int_0^T x^2(t) dt}$$

$$\text{RMS} = \sqrt{D_c^2 + \left(\frac{A_c}{\sqrt{2}}\right)^2}$$

for $x(t) = D_c + A_c \sin \omega t$

Two port N/W

* for 'n' variable, 'r' port N/W, No. of possible parameters are nC_r

eg: 4 variable 2port $\Rightarrow {}^4C_2 = 6$ Parameters $[Z, Y, g, h, T, T']$

(i) Z-parameter [O.C. parameter]

$$V_1 = Z_{11} I_1 + Z_{12} I_2$$

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} \quad Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2$$

and so on.

Z_{11}/Z_{22} : Driving point i/p or o/p impedance when o/p or i/p is o.c.

Z_{12} or Z_{21} : Transfer i/p or o/p impedance when i/p or o/p is o.c.

(ii) Y-parameter [S.C. para]

$$I_1 = Y_{11} V_1 + Y_{12} V_2$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2$$

(iii) h-parameter [hybrid para]

$$V_1 = h_{11} I_1 + h_{12} V_2$$

$$I_2 = h_{21} I_1 + h_{22} V_2$$

$$[h] = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} h_i & h_r \\ h_f & h_o \end{bmatrix}$$

(2-1)

h_i : input impedance h_r = reverse V/g gain = V_1/V_2

h_f : forward current gain = I_2/I_1 h_o = o/p admittance

(iv) g-parameter

$$I_1 = g_{11} V_1 + g_{12} I_2$$

$$V_2 = g_{21} V_1 + g_{22} I_2$$

Note: $z_{11} \neq \frac{1}{y_{11}}$ [$\because$ S.C. $\neq$ O.C.]

(v) ABCD / X^{min} parameters

$$V_1 = AV_2 - BI_2$$

$$I_1 = CV_2 - DI_2$$

(vi) T^{-1} parameters

$$V_2 = aV_1 - bI_1$$

$$I_2 = cV_1 - dI_1$$

To remember

$X_{11} \ X_{12}$ $\rightarrow$ Reciprocity

$X_{21} \ X_{22}$ $\rightarrow$ Symmetry

Koi bhi parameter ko (z, y, h, T, T⁻¹)

Agar X_{12} & X_{21} ka unit same h to $X_{21} = X_{12}$

Agar same ni h to $|X| = 1$ (reciprocity condⁿ)

Agar X_{12} , X_{22} ka unit same h to $X_{12} = X_{22}$ (Symmetry condⁿ)

Conditions for reciprocity & Symmetry

	Reciprocity	Symmetry
Z-para	$Z_{12} = Z_{21}$	$Z_{11} = Z_{22}$
Y-para	$Y_{12} = Y_{21}$	$Y_{11} = Y_{22}$
h-para	$h_{12} = -h_{21}$	$\Delta h = 1$
g-para	$g_{12} = -g_{21}$	$\Delta g = 1$
T-para	$\Delta T = 1$	$A = D$
T^{-1} - para	$\Delta T^{-1} = 1$	$a = d$

Inter conversion :

(i) $[Z] = [Y]^{-1}$ or $[Z]^{-1} = [Y]$

(ii) $[g] = [h]^{-1}$ or $[g]^{-1} = [h]$

(iii) $[T] = [T^{-1}]^{-1}$ or $[T]^{-1} = [T^{-1}]$


(iv) $h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{1}{y_{11}}$ $h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} = \frac{y_{21}}{y_{11}}$

$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} = \frac{Z_{12}}{Z_{22}}$ $h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{Z_{22}}$

$$[h] = \begin{bmatrix} 1/y_{11} & z_{12}/z_{22} \\ y_{21}/y_{11} & 1/z_{22} \end{bmatrix}$$



Standard Networks

(i) T N/W

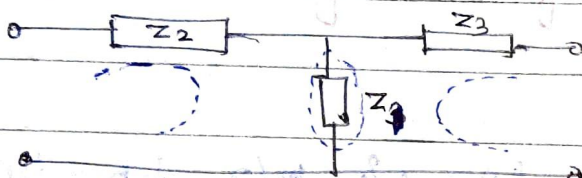


$$[Z] = \begin{bmatrix} Z_1 + Z_2 & Z_1 \\ Z_1 & Z_1 + Z_3 \end{bmatrix}$$

(ii) Lattice N/W

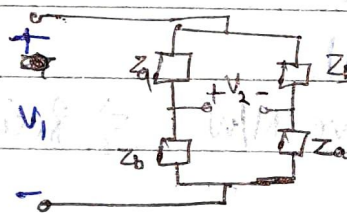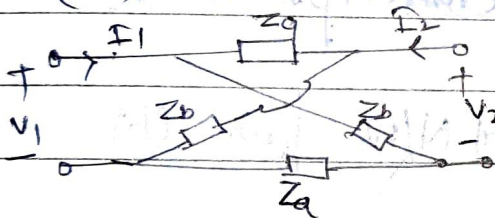


$$[Z] = \begin{bmatrix} \frac{Z_a + Z_b}{2} & \frac{Z_b - Z_a}{2} \\ \frac{Z_c - Z_d}{2} & \frac{Z_c + Z_d}{2} \end{bmatrix}$$

(iii) π - N/W

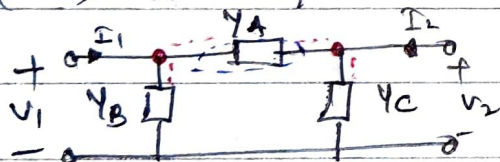
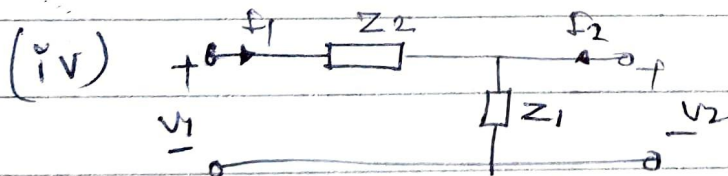
$$[Y] = \begin{bmatrix} Y_A + Y_B & -Y_A \\ -Y_A & Y_A + Y_C \end{bmatrix}$$



↓ Special case

$$[T] = \begin{bmatrix} 1 + \frac{Z_2}{Z_1} & Z_2 \\ \frac{1}{Z_1} & 1 \end{bmatrix}$$




$$\begin{bmatrix} 1 & Z \\ 0 & 1 \end{bmatrix}$$



$$\begin{bmatrix} 1 & 0 \\ Y & 1 \end{bmatrix}$$

(vi) Transformer :

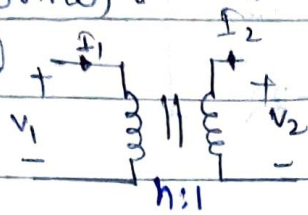

$$\frac{V_1}{V_2} = n, \quad \frac{I_2}{I_1} = -n$$

$$[h] = \begin{bmatrix} 0 & n \\ -n & 0 \end{bmatrix}$$

$$[T] = \begin{bmatrix} n & 0 \\ 0 & 1/n \end{bmatrix}$$

* (Z-para & Y-para) doesn't exist for Transformer

** Key point :


~~**~~ (1) All complex N/w {R, L, C} w/o dependent source are reciprocal N/w

(2) Dependent source N/w are non-reciprocal & asymmetrical

(3) Passive N/w $\Rightarrow$ Reciprocal N/w from (1)


Interconnection of 2-port N/W

(i) Series connection

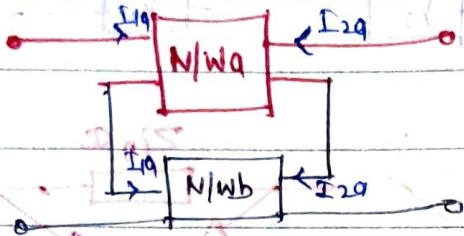


$$[Z]_{\text{total}} = [Z]_{N/wa} + [Z]_{N/wb}$$

(ii) Parallel connection

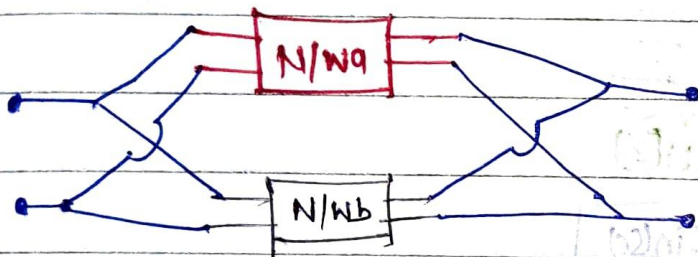

$$[Y]_{\text{total}} = [Y]_{N/wa} + [Y]_{N/wb}$$

(iii) Series-parallel connection

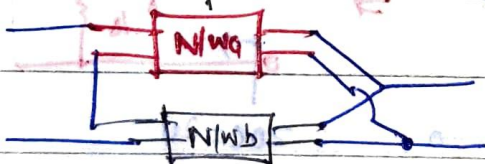

$$[h]_{\text{total}} = [h]_a + [h]_b$$

(iv) Parallel-series connection


$$[g]_{\text{total}} = [g]_a + [g]_b$$

(v) Cascade




$$[T] = [T_a] \times [T_b]$$

① Bartlett's Bisection Theorem

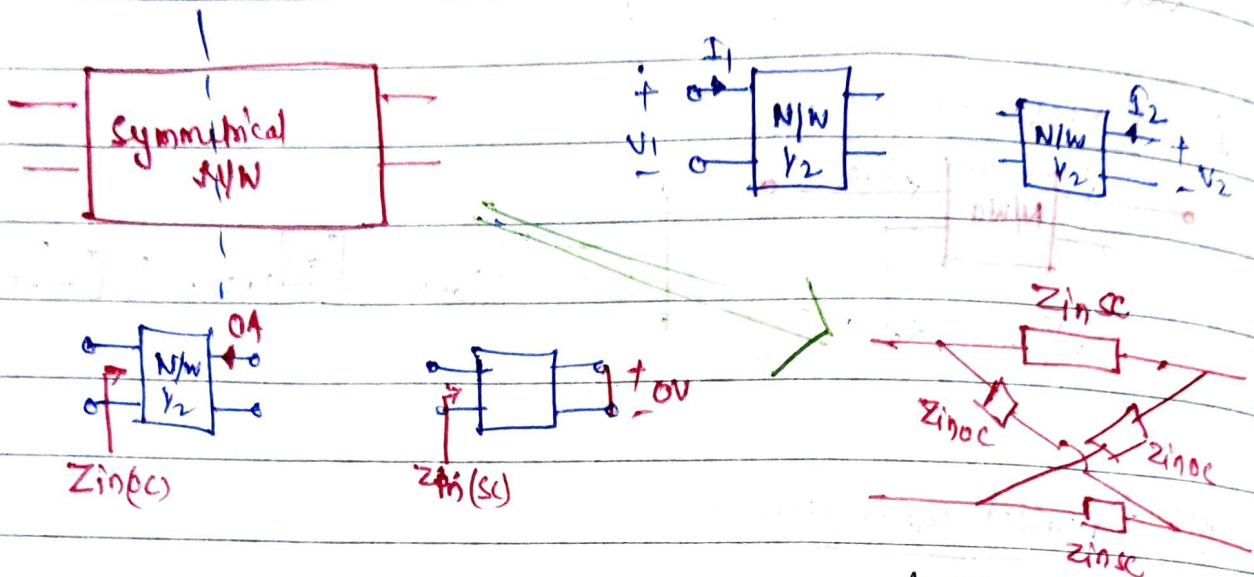


Characteristic or Image Impedance = $\sqrt{\frac{\Delta Z}{\det[Z]}}$
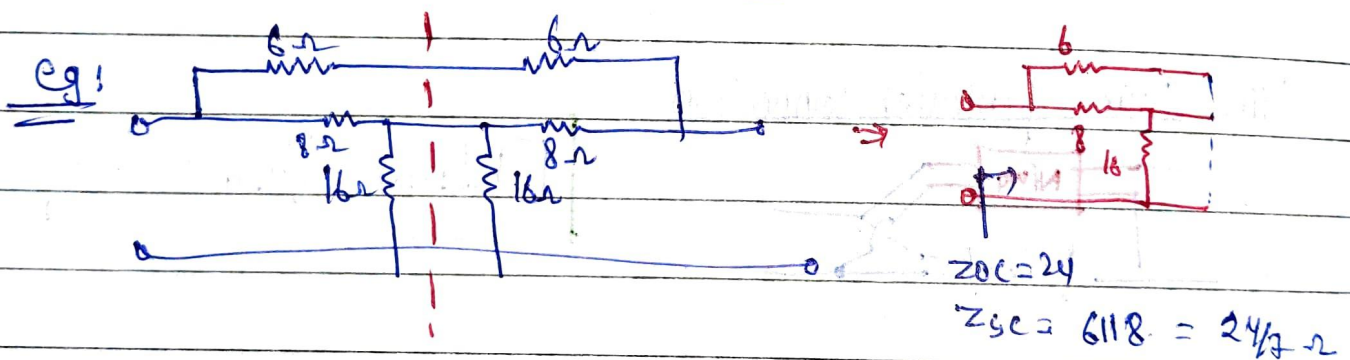
$$\Delta Z = Z_{in(oc)} \times Z_{in(sc)}$$




Gyration

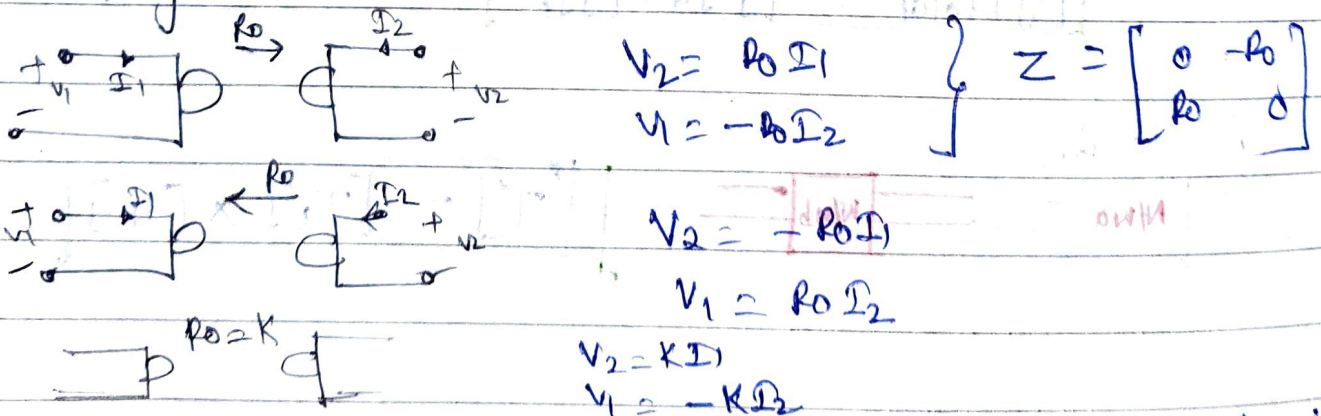

* Gyration is Nonreciprocal device, known as impedance inversion device

Transient & steady state response

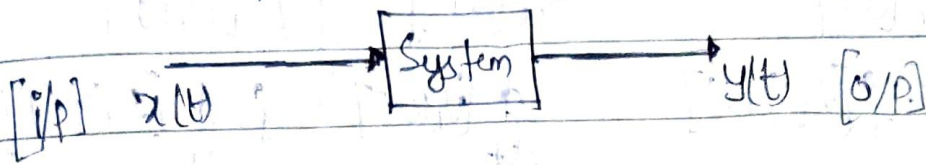

① $e = 2.718$; $e^{-1} = 0.368$; $1 - e^{-1} = 0.632$

② $y(t) = y(\infty) + \{y[0] - y[\infty]\} e^{-t/\tau}$ ← Not valid for 2nd order eqⁿ i.e. more than 1 L or C
 $y(t)$ can be $I_L(t)$, $V_L(t)$, $I_R(t)$, $V_R(t)$ etc.

③ for finite time switching

$$I_L(t) = I_L(\infty) + [I_L(0^+) - I_L(\infty)] e^{-\frac{(t-t_0)}{\tau}}$$
 Same for $V_L(t)$, $I_R(t)$, $V_R(t)$

④ $\tau = \frac{L_{eq}}{R_{th}}$ Henry = sec

⑤ * Laplace Xform is valid everywhere

* Transient eqⁿ is valid only for 1st order N/W

⑥ $I_L[0^+] = I_L[0^-]$;
 Calculate $V_L[0^+]$ from ckt by replacing $\frac{I[0^+]}{L}$ by $\oplus$ $I[0^+]$
 $\frac{d(I[0^+])}{dt} = \frac{V_L[0^+]}{L}$

KVL eg: $-V + I_L(t) R + V_L(t)$
 diff. $R \frac{dI_L(t)}{dt} + \frac{dV_L(t)}{dt} = 0$

Put $t=0$
 & solve

$\frac{dV_L(0^+)}{dt} = -\frac{RV}{L}$

$\frac{d(V_L(t))}{dt} = L \frac{d^2 I(t)}{dt^2}$

$\frac{d^2 I(0^+)}{dt^2} = \frac{1}{L} \frac{dV_L(0^+)}{dt}$

$$\rightarrow I_L[0^-] = I_L[0^+]$$

$$V_L[0^+] = f[I_L(0^+)]$$

$$\rightarrow \frac{d}{dt} [I_L(0^+)] = f[V_L(0^+)]$$

$$\frac{d}{dt} [V_L(0^+)] = f \frac{d}{dt} [I_L(0^+)]$$

$$\rightarrow \frac{d^2}{dt^2} [I_L(0^+)] = f \frac{d}{dt} [V_L(0^+)]$$


from KVL

put $V_L = L \frac{dI_L}{dt}$

* for impulse and step response go by Laplace

NETWORK THEOREMS

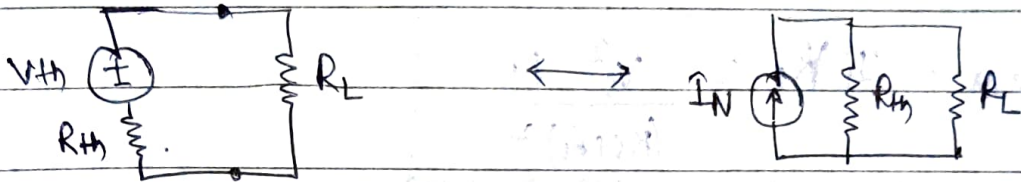① $R_{eq} = R_{th} = \frac{V_{OC}}{I_{SC}} = \frac{V_{th}}{I_N}$




$R_{th} = R_N$, $V_{th} = I_N R_N$

② Maximum Power transfer theorem

- In case of fixed load, we choose min. value of R_s for max. P_{Lmax} .
- This theorem gives at most 50% η .

Case: 1 $Z_s = R_s$, $Z_L = R_L$

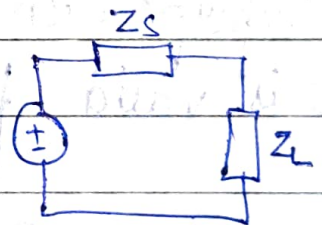

condⁿ $R_L = R_s$ $P_{Lmax} = \frac{V_s^2}{4R_s}$

$P_{del} = \frac{V_s^2}{2R_s}$ at M.P.T.

Case: 2 $Z_s = R_s + jX_s$, $Z_L = R_L + jX_L$

condⁿ, $R_L = \sqrt{R_s^2 + (X_s + X_L)^2}$

$P_{L(max)} = I_L^2 R_L = \frac{V_s^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$

Case 3: $Z_s = R_s + jX_s$, $Z_L = R_L + jX_L$

condⁿ $\boxed{X_s = -X_L}$

$$\boxed{P_{L\max} = I_L^2 R_L = \frac{V_s^2 R_L}{(R_s + R_L)^2}}$$

Case 4: $Z_s = R_s + jX_s$, $Z_L = R_L + jX_L$

condn : $\boxed{Z_L = Z_s^*}$

$$\boxed{P_{L\max} = I_L^2 R_L = \frac{V_s^2}{4R_s}}$$

⊙ Superposition theorem

It is valid for dependent as well as independent ~~new~~

→ $I_o = I_1 + I_2 + I_3 + \dots + I_n$

→ $V_o = V_1 + V_2 + V_3 + \dots + V_n$

→ $P_o = (\sqrt{P_1} + \sqrt{P_2} + \sqrt{P_3} + \dots + \sqrt{P_n})^2$

→ Depending upon direction of both currents

$P_{\max} = (\sqrt{P_1} + \sqrt{P_2})^2$

$P_{\min} = (\sqrt{P_1} - \sqrt{P_2})^2$



{ when I_1, I_2 are in same dirⁿ }

⊙ Reciprocity theorem

→ Not valid for dependent source N/W

① Millman's Theorem

(1)

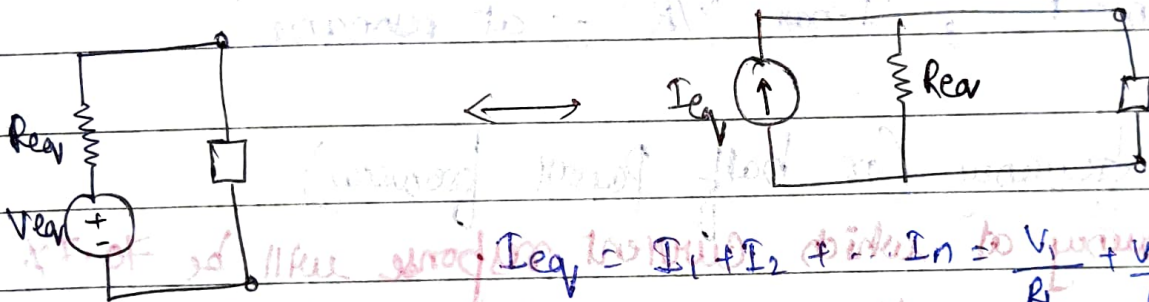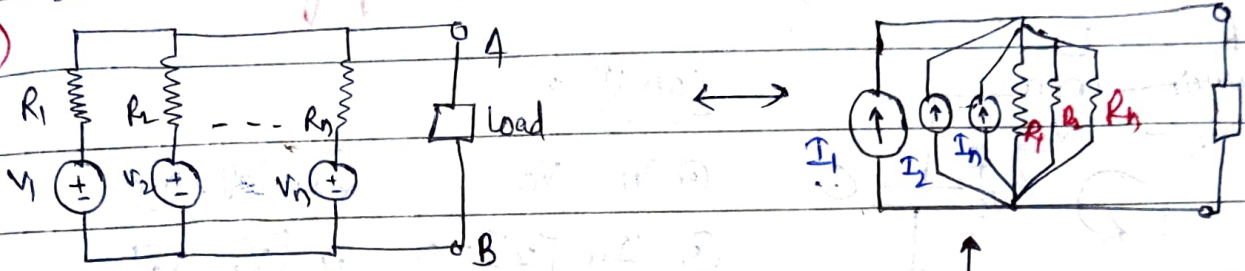


$$I_{eq} = I_1 + I_2 + \dots + I_n = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n}$$

$$R_{eq} = (R_1 \parallel R_2 \parallel R_3 \dots \parallel R_n)$$

$$V_{eq} = I_{eq} R_{eq}$$

(2)

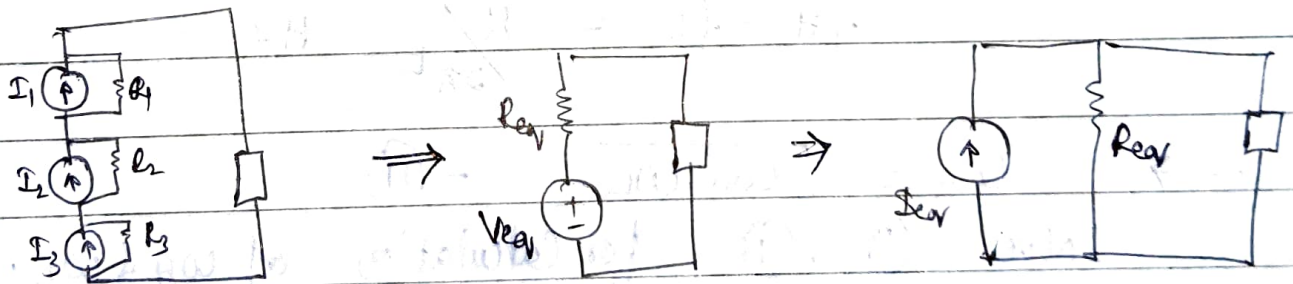


$$V_{eq} = I_1 R_1 + I_2 R_2 + I_3 R_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$I_{eq} = \frac{V_{eq}}{R_{eq}}$$

Resonance

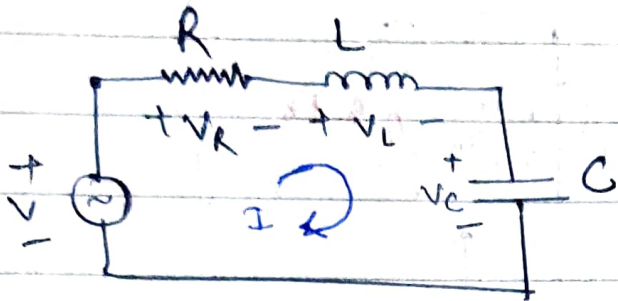(i) Series RLC resonance ckt (V/g Amplifier ckt)



Condⁿ :

① $V_L = V_C$

$\{ \text{Im}[Z] = 0 \}$

② $\text{Im}[Z] = 0 \Rightarrow \boxed{X_L = X_C}$

$\omega_0 = \frac{1}{\sqrt{LC}} \text{ rad/s}$

③ $(Z_{\min} = R, I_{\max} = V/R) \rightarrow \text{at resonance}$

④ 3dB frequency (or half power frequency)

frequency at which current response will be 70.7% or $1/\sqrt{2}$ times the maximum value is referred as 3dB frequency.

$\rightarrow BW = \omega_H - \omega_L = R/L \text{ rad/s} \quad \text{--- (i)}$

$= f_H - f_L = \frac{R}{2\pi L} \text{ Hz} \quad \text{--- (ii)}$

$\rightarrow \omega_0 = \sqrt{\omega_H \omega_L} \quad \text{--- (iii)}$

Solve ① & ③ for calculation of ω_H & ω_L .

$\rightarrow Q = 2\pi \frac{\text{Energy stored}}{\text{R dissipated energy}} = 2\pi \times \frac{\text{Energy stored}}{\text{R dissipated energy}}$

$\rightarrow Q = \frac{\omega L}{R}$

$\rightarrow Q = \frac{1}{R} \sqrt{\frac{L}{C}} \text{ at resonance}$
 $= \frac{\omega_0}{BW}$

$\left\{ \begin{array}{l} \text{To remember } Z_0 = \sqrt{\frac{L}{C}} \Omega \\ \frac{1}{R} \times \sqrt{\frac{L}{C}} = \frac{1}{R} \times Z_0 = \text{unitless} \end{array} \right\}$

for series RLC
**

$$V_L = jQV$$

$$= QV \angle 90^\circ$$

$$V_C = -jQV$$

$$= QV \angle -90^\circ$$

for parallel RLC
**


$$I_L = -jQI$$

$$= QI \angle -90^\circ$$

$$I_C = jQI$$

$$= QI \angle 90^\circ$$

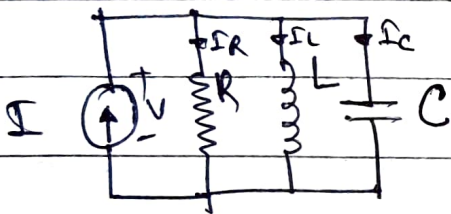(ii) Parallel RLC resonance ckt. (Current Amplifier ckt)



$$Y = \frac{I}{V} = \frac{1}{R} + j \left(\frac{1}{X_C} - \frac{1}{X_L} \right)$$

$= 0$ at resonance

At resonance:

$$\left. \begin{aligned} V_{\max} &= IR \\ Y_{\min} &= 1/R \\ Z_{\max} &= R \end{aligned} \right\}$$

$$\rightarrow BW = \omega_H - \omega_L = \frac{1}{RC} \text{ rad/s}$$

$$= f_H - f_L = \frac{1}{2\pi RC} \text{ Hz}$$

$$\rightarrow \omega_0 = \sqrt{\omega_H \omega_L}$$

$$\rightarrow Q_{\text{parallel}} = R \sqrt{\frac{C}{L}} = \frac{1}{Q_{\text{series}}}$$


$$\rightarrow Q = \frac{\omega_0}{BW} \text{ for both series \& parallel}$$

Graph theory

① Rank of graph, $R = n - 1$

$\{ n = \text{No. of nodes} \}$

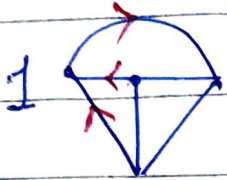② Degree of Node = No. of incoming branches
 $\downarrow$
 $\sum \text{degree of each node} = \text{No. of branches}$




$D[F] = 2$

③ If all Node-pair contains single branch b/w them $\Rightarrow$ Complete graph



Complete

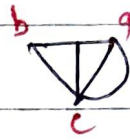

Branch $ab = \text{Absent}$
 2 Branches at ac

Incomplete

④ Connected graph means it doesn't contain any free node $\Rightarrow$




eg 1


connected graph

($\because$ no free node)

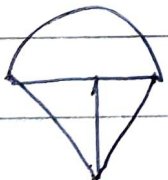Tree: Subgraph which connects all nodes w/o forming any closed loop.



graph

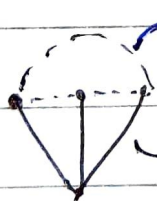

Twigs = $n - 1$

Links = $b - n + 1$

* No. of tree of a Complete graph = $n^{(n-2)}$

* Min. no. of edges in a complete graph = nC_2

No. of node pair voltages = nC_2

Complex Power

Note: $\rightarrow$ Avoid Laplace Xform in $\dots$ calculations
~~in case of~~ in case of sinusoidal input only, as it
refers to sinusoidal steady state analysis.

So, if solved by Laplace we will get an
exponentially decreasing term say for eg: e^{-st}

eg: $i(t) = e^{-st} + \sin st$

$\uparrow$
($=0$) at steady state

So, $i(t) = \sin st$ is final answer.

$$\frac{dy}{dx} = \sin t$$

$\frac{dy}{dx}$

$$y = -\cos t + C$$