

Q.1 – Q.20 Carry One Mark Each.

1. The rank of the matrix

$$\begin{bmatrix} 1 & 1 & 1 \\ 1 & -1 & 0 \\ 1 & 1 & 1 \end{bmatrix} \text{ is:}$$

- (A) 0
- (B) 1
- (C) 2
- (D) 3

2. $\nabla \times \nabla \times P$, where P is a vector, is equal to

- (A) $P \times \nabla \times P - \nabla^2 P$
- (B) $\nabla^2 P + \nabla (\nabla \cdot P)$
- (C) $\nabla^2 P + \nabla \times P$
- (D) $\nabla (\nabla \cdot P) - \nabla^2 P$

3. $\iint (\nabla \times P) \cdot ds$, where P is a vector, is equal to

- (A) $\oint P \cdot dl$
- (B) $\oint \nabla \times \nabla \times P \cdot dl$
- (C) $\oint \nabla \times P \cdot dl$
- (D) $\iiint \nabla \cdot P dv$

4. A probability density function is of the form

$$p(x) = Ke^{-\alpha|x|}, x \in (-\infty, \infty).$$

The value of K is

- (A) 0.5
- (B) 1
- (C) 0.5α
- (D) α

5. A solution for the differential equation

$$\dot{x}(t) + 2x(t) = \delta(t)$$

with initial condition $x(0-) = 0$ is:

- (A) $e^{-2t}u(t)$
- (B) $e^{2t}u(t)$
- (C) $e^{-t}u(t)$
- (D) $e^t u(t)$
6. A low-pass filter having a frequency response $H(j\omega) = A(\omega)e^{j\phi(\omega)}$ does not produce any phase distortion if
- (A) $A(\omega) = C\omega^2, \phi(\omega) = k\omega^3$
- (B) $A(\omega) = C\omega^2, \phi(\omega) = k\omega$
- (C) $A(\omega) = C\omega, \phi(\omega) = k\omega^2$
- (D) $A(\omega) = C, \phi(\omega) = k\omega^{-1}$
7. The values of voltage (V_D) across a tunnel-diode corresponding to peak and valley currents are V_p and V_v respectively. The range of tunnel-diode voltage V_D for which the slope of its $I - V_D$ characteristics is negative would be
- (A) $V_D < 0$
- (B) $0 \leq V_D < V_p$
- (C) $V_p \leq V_D < V_v$
- (D) $V_D \geq V_v$
8. The concentration of minority carriers in an extrinsic semiconductor under equilibrium is:
- (A) directly proportional to the doping concentration
- (B) inversely proportional to the doping concentration
- (C) directly proportional to the intrinsic concentration
- (D) inversely proportional to the intrinsic concentration
9. Under low level injection assumption, the injected minority carrier current for an extrinsic semiconductor is essentially the
- (A) diffusion current
- (B) drift current
- (C) recombination current
- (D) induced current

10. The phenomenon known as "Early Effect" in a bipolar transistor refers to a reduction of the effective base-width caused by
- (A) electron-hole recombination at the base
 - (B) the reverse biasing of the base-collector junction
 - (C) the forward biasing of emitter-base junction
 - (D) the early removal of stored base charge during saturation-to-cutoff switching.
11. The input impedance (Z_i) and the output impedance (Z_o) of an ideal trans-conductance (voltage controlled current source) amplifier are
- (A) $Z_i = 0, Z_o = 0$
 - (B) $Z_i = 0, Z_o = \infty$
 - (C) $Z_i = \infty, Z_o = 0$
 - (D) $Z_i = \infty, Z_o = \infty$
12. An n-channel depletion MOSFET has following two points on its $I_D - V_{GS}$ curve:
- (i) $V_{GS} = 0$ at $I_D = 12mA$ and
 - (ii) $V_{GS} = -6$ Volts at $I_D = 0$
- Which of the following Q-points will give the highest trans-conductance gain for small signals?
- (A) $V_{GS} = -6$ Volts
 - (B) $V_{GS} = -3$ Volts
 - (C) $V_{GS} = 0$ Volts
 - (D) $V_{GS} = 3$ Volts
13. The number of product terms in the minimized sum-of-product expression obtained through the following K-map is (where "d" denotes don't care states)

1	0	0	1
0	d	0	0
0	0	d	1
1	0	0	1

- (A) 2
- (B) 3
- (C) 4
- (D) 5

14. Let $x(t) \leftrightarrow X(j\omega)$ be Fourier Transform pair. The Fourier Transform of the signal $x(5t - 3)$ in terms of $X(j\omega)$ is given as

(A) $\frac{1}{5} e^{-\frac{j3\omega}{5}} X\left(\frac{j\omega}{5}\right)$

(B) $\frac{1}{5} e^{\frac{j3\omega}{5}} X\left(\frac{j\omega}{5}\right)$

(C) $\frac{1}{5} e^{-j3\omega} X\left(\frac{j\omega}{5}\right)$

(D) $\frac{1}{5} e^{j3\omega} X\left(\frac{j\omega}{5}\right)$

15. The Dirac delta function $\delta(t)$ is defined as

(A) $\delta(t) = \begin{cases} 1 & t = 0 \\ 0 & \text{otherwise} \end{cases}$

(B) $\delta(t) = \begin{cases} \infty & t = 0 \\ 0 & \text{otherwise} \end{cases}$

(C) $\delta(t) = \begin{cases} 1 & t = 0 \\ 0 & \text{otherwise} \end{cases}$ and $\int_{-\infty}^{\infty} \delta(t) dt = 1$

(D) $\delta(t) = \begin{cases} \infty & t = 0 \\ 0 & \text{otherwise} \end{cases}$ and $\int_{-\infty}^{\infty} \delta(t) dt = 1$

16. If the region of convergence of $x_1[n] + x_2[n]$ is $\frac{1}{3} < |z| < \frac{2}{3}$, then the region of convergence of $x_1[n] - x_2[n]$ includes

(A) $\frac{1}{3} < |z| < 3$

(B) $\frac{2}{3} < |z| < 3$

(C) $\frac{3}{2} < |z| < 3$

(D) $\frac{1}{3} < |z| < \frac{2}{3}$


17. The open-loop transfer function of a unity-gain feedback control system is given by

$$G(s) = \frac{K}{(s+1)(s+2)}.$$

The gain margin of the system in dB is given by

- (A) 0
- (B) 1
- (C) 20
- (D) ∞

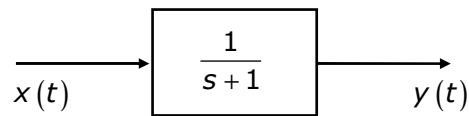18. In the system shown below, $x(t) = (\sin t)u(t)$. In steady-state, the response $y(t)$ will be:



- (A) $\frac{1}{\sqrt{2}} \sin\left(t - \frac{\pi}{4}\right)$
 - (B) $\frac{1}{\sqrt{2}} \sin\left(t + \frac{\pi}{4}\right)$
 - (C) $\frac{1}{\sqrt{2}} e^{-t} \sin t$
 - (D) $\sin t - \cos t$
19. The electric field of an electromagnetic wave propagating in the positive z-direction is given by

$$E = \hat{a}_x \sin(\omega t - \beta z) + \hat{a}_y \sin\left(\omega t - \beta z + \frac{\pi}{2}\right).$$

The wave is

- (A) linearly polarized in the z-direction
 - (B) elliptically polarized
 - (C) left-hand circularly polarized
 - (D) right-hand circularly polarized
20. A transmission line is feeding 1 Watt of power to a horn antenna having a gain of 10 dB. The antenna is matched to the transmission line. The total power radiated by the horn antenna into the free-space is:
- (A) 10 Watts

- (B) 1 Watt
- (C) 0.1 Watt
- (D) 0.01 Watt

21. The eigenvalues and the corresponding eigenvectors of a 2×2 matrix are given by

Eigenvalue

Eigenvector

$$\lambda_1 = 8$$

$$v_1 = \begin{bmatrix} 1 \\ 1 \end{bmatrix}$$

$$\lambda_2 = 4$$

$$v_2 = \begin{bmatrix} 1 \\ -1 \end{bmatrix}$$

The matrix is:

- (A) $\begin{bmatrix} 6 & 2 \\ 2 & 6 \end{bmatrix}$
 - (B) $\begin{bmatrix} 4 & 6 \\ 6 & 4 \end{bmatrix}$
 - (C) $\begin{bmatrix} 2 & 4 \\ 4 & 2 \end{bmatrix}$
 - (D) $\begin{bmatrix} 4 & 8 \\ 8 & 4 \end{bmatrix}$
22. For the function of a complex variable $W = \ln Z$ (where, $W = u + jv$ and $Z = x + jy$), the $u = \text{constant}$ lines get mapped in Z -plane as
- (A) set of radial straight lines
 - (B) set of concentric circles
 - (C) set of confocal hyperbolas
 - (D) set of confocal ellipses

23. The value of the contour integral $\oint_{|z-j|=2} \frac{1}{z^2 + 4} dz$ in positive sense is

- (A) $\frac{j\pi}{2}$
- (B) $\frac{-\pi}{2}$
- (C) $\frac{-j\pi}{2}$

(D) $\frac{\pi}{2}$

24. The integral $\int_0^{\pi} \sin^3 \theta \, d\theta$ is given by

(A) $\frac{1}{2}$

(B) $\frac{2}{3}$

(C) $\frac{4}{3}$

(D) $\frac{8}{3}$

25. Three companies, X, Y and Z supply computers to a university. The percentage of computers supplied by them and the probability of those being defective are tabulated below.

Company	% of computers supplied	Probability of being defective
X	60%	0.01
Y	30%	0.02
Z	10%	0,03

Given that a computer is defective, the probability that it was supplied by Y is:

(A) 0.1

(B) 0.2

(C) 0.3

(D) 0.4

26. For the matrix $\begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix}$ the eigenvalue corresponding to the eigenvector $\begin{bmatrix} 101 \\ 101 \end{bmatrix}$ is:

(A) 2

(B) 4

(C) 6

(D) 8

27. For the differential equation $\frac{d^2 y}{dx^2} + k^2 y = 0$ the boundary conditions are

(i) $y = 0$ for $x = 0$ and

(ii) $y = 0$ for $x = a$

The form of non-zero solutions of y (where m varies over all integers) are

(A) $y = \sum_m A_m \sin \frac{m\pi x}{a}$

(B) $y = \sum_m A_m \cos \frac{m\pi x}{a}$

(C) $y = \sum_m A_m x^{\frac{m\pi}{a}}$

(D) $y = \sum_m A_m e^{\frac{m\pi x}{a}}$

28. Consider the function $f(t)$ having Laplace transform

$$F(s) = \frac{\omega_0}{s^2 + \omega_0^2} \quad \text{Re}[s] > 0$$

The final value of $f(t)$ would be:

(A) 0

(B) 1

(C) $-1 \leq f(\infty) \leq 1$

(D) ∞

29. As x is increased from $-\infty$ to ∞ , the function

$$f(x) = \frac{e^x}{1 + e^x}$$

(A) monotonically increases

(B) monotonically decreases

(C) increases to a maximum value and then decreases

(D) decreases to a minimum value and then increases

30. A two port network is represented by ABCD parameters given by


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

If port-2 is terminated by R_L , the input impedance seen at port-1 is given by


(A) $\frac{A + BR_L}{C + DR_L}$

- (B) $\frac{AR_L + C}{BR_L + D}$
- (C) $\frac{DR_L + A}{BR_L + C}$
- (D) $\frac{B + AR_L}{D + CR_L}$

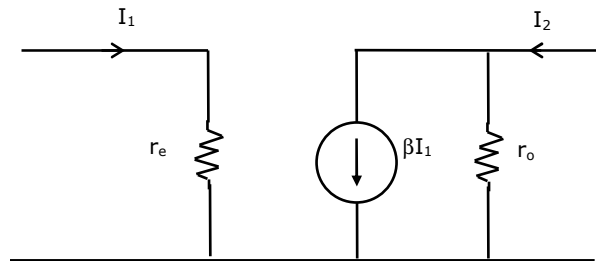31. In the two port network shown in the figure below, z_{12} and z_{21} are, respectively




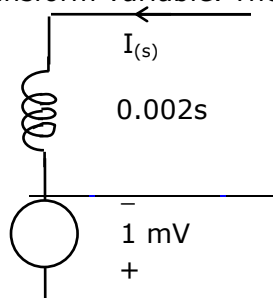- (A) r_c and βr_o
- (B) 0 and $-\beta r_o$
- (C) 0 and βr_o
- (D) r_c and $-\beta r_o$
32. The first and the last critical frequencies (singularities) of a driving point impedance function of a passive network having two kinds of elements, are a pole and a zero respectively. The above property will be satisfied by
- (A) RL network only
- (B) RC network only
- (C) LC network only
- (D) RC as well as RL networks
33. A 2mH inductor with some initial current can be represented as shown below, where s is the Laplace Transform variable. The value of initial current is:



- (A) 0.5 A
- (B) 2.0 A
- (C) 1.0 A
- (D) 0.0 A

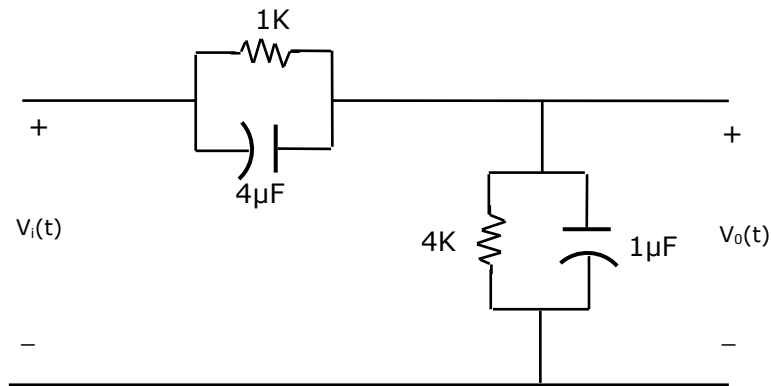34. In the figure shown below, assume that all the capacitors are initially uncharged. If $v_i(t) = 10u(t)$ Volts, $v_o(t)$ is given by



- (A) $8e^{-0.004t}$ Volts
 - (B) $8(1 - e^{-0.004t})$ Volts
 - (C) $8u(t)$ Volts
 - (D) 8 Volts
35. Consider two transfer functions


$$G_1(s) = \frac{1}{s^2 + as + b} \text{ and } G_2(s) = \frac{s}{s^2 + as + b}.$$

The 3-dB bandwidths of their frequency responses are, respectively


- (A) $\sqrt{a^2 - 4b}, \sqrt{a^2 + 4b}$
- (B) $\sqrt{a^2 + 4b}, \sqrt{a^2 - 4b}$

- (C) $\sqrt{a^2 - 4b}, \sqrt{a^2 - 4b}$
 (D) $\sqrt{a^2 + 4b}, \sqrt{a^2 + 4b}$

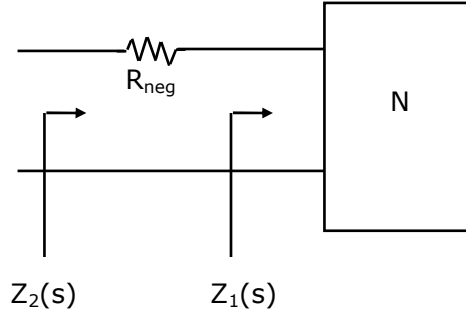36. A negative resistance R_{neg} is connected to a passive network N having driving point impedance $Z_1(s)$ as shown below. For $Z_2(s)$ to be positive real,



- (A) $|R_{neg}| \leq \text{Re } Z_1(j\omega), \forall \omega$
 (B) $|R_{neg}| \leq |Z_1(j\omega)|, \forall \omega$
 (C) $|R_{neg}| \leq \text{Im } Z_1(j\omega), \forall \omega$
 (D) $|R_{neg}| \leq \angle Z_1(j\omega), \forall \omega$
37. In the circuit shown below, the switch was connected to position 1 at $t < 0$ and at $t = 0$, it is changed to position 2. Assume that the diode has zero voltage drop and a storage time t_s . For $0 < t \leq t_s$, v_R is given by (all in Volts)

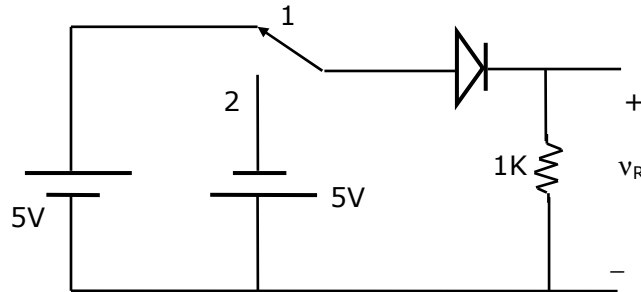

- (A) $v_R = -5$
 (B) $v_R = +5$
 (C) $0 \leq v_R < 5$

(D) $-5 < v_R < 0$

38. The majority carriers in an n-type semiconductor have an average drift velocity \mathbf{v} in a direction perpendicular to a uniform magnetic field \mathbf{B} . the electric field \mathbf{E} induced due to Hall effect acts in the direction

- (A) $\mathbf{v} \times \mathbf{B}$
 (B) $\mathbf{B} \times \mathbf{v}$
 (C) along \mathbf{v}
 (D) opposite to \mathbf{v}

39. Find the correct match between Group 1 and Group 2:

Group 1	Group 2
(E) Varactor diode	(1) Voltage reference
(F) PIN diode	(2) High frequency switch
(G) Zener diode	(3) Tuned circuits
(H) Schottky diode	(4) Current controlled attenuator

- (A) E - 4 F - 2 G - 1 H - 3
 (B) E - 2 F - 4 G - 1 H - 3
 (C) E - 3 F - 4 G - 1 H - 2
 (D) E - 1 F - 3 G - 2 H - 4

40. A heavily doped n -type semiconductor has the following data:

Hole-electron mobility ratio : 0.4


Doping concentration : 4.2×10^8 atoms/m³

Intrinsic concentration : 1.5×10^4 atoms/m³

The ratio of conductance of the n -type semiconductor to that of the intrinsic semiconductor of same material and at the same temperature is given by

- (A) 0.00005
 (B) 2,000
 (C) 10,000
 (D) 20,000


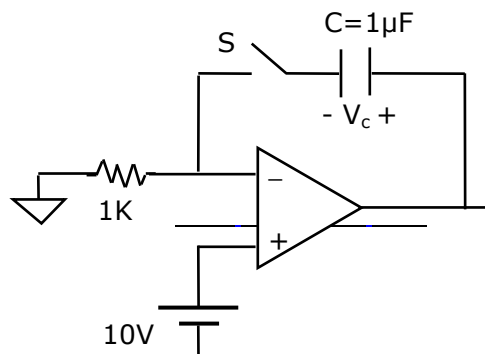
41. For the circuit shown in the following figure, the capacitor C is initially uncharged. At $t = 0$, the switch S is closed. The voltage V_C across the capacitor at $t = 1$ millisecond is:



In the figure shown above, the OP-AMP is supplied with $\pm 15\text{V}$ and the ground has been shown by the symbol ∇ .

- (A) 0 Volt
- (B) 6.3 Volts
- (C) 9.45 Volts
- (D) 10 Volts

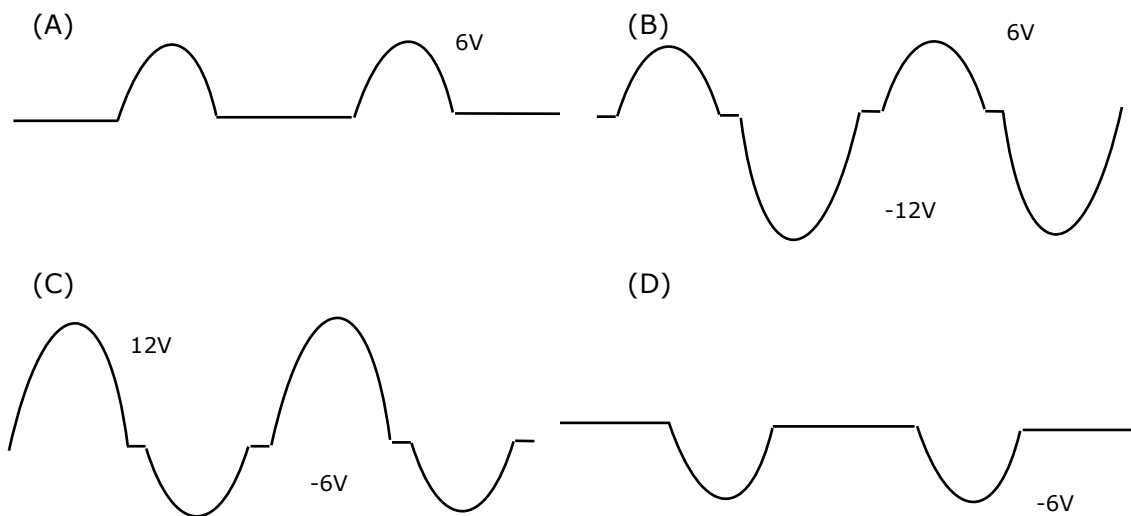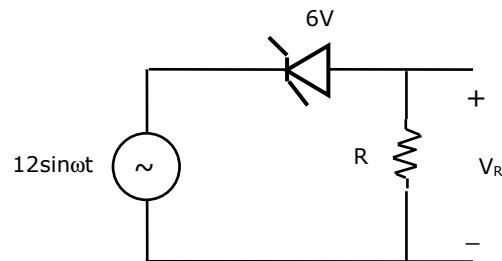42. For the circuit shown below, assume that the zener diode is ideal with a breakdown voltage of 6 Volts. The waveform observed across R is:



43. A new Binary Coded Pentary (BCP) number system is proposed in which every digit of a base-5 number is represented by its corresponding 3-bit binary code. For example, the base-5 number 24 will be represented by its BCP code 010100. In this numbering system, the BCP code 100010011001 corresponds to the following number in base-5 system
- (A) 423
(B) 1324
(C) 2201
(D) 4231
44. An I/O peripheral device shown in figure (b) below is to be interfaced to an 8085 microprocessor. To select the I/O device in the I/O address range D4 H – D7 H, its chip-select (\overline{CS}) should be connected to the output of the decoder shown in figure (a) below:

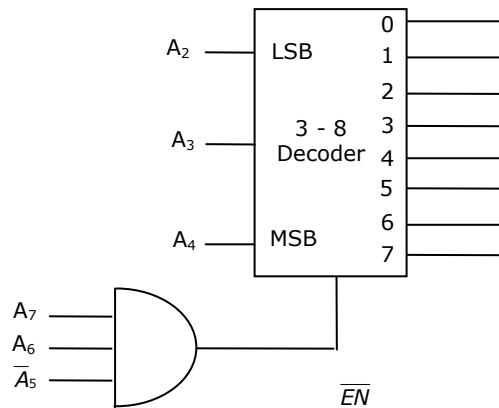


Fig. (a)


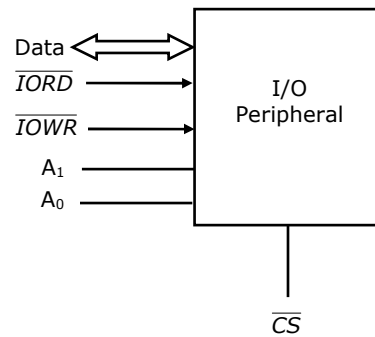


Fig. (b)

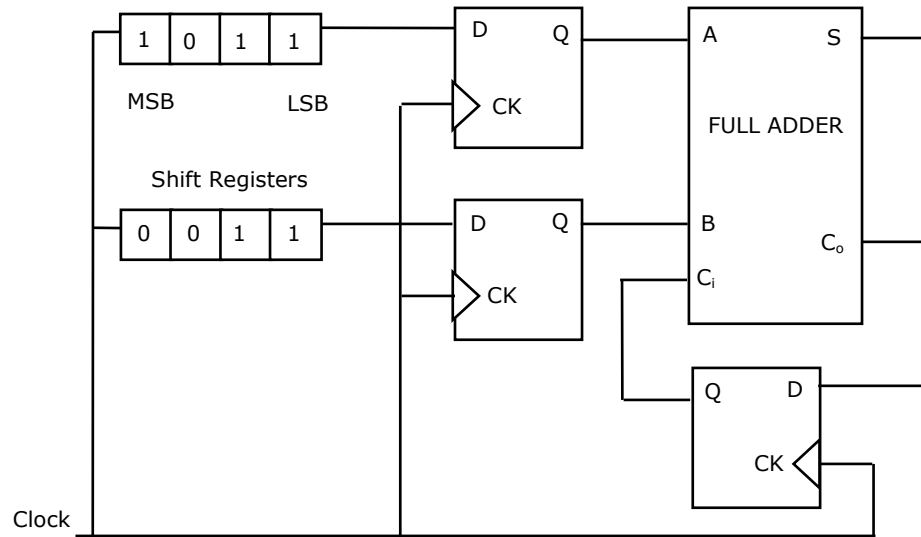
- (A) output 7
(B) output 5
(C) output 2
(D) output 0
45. For the circuit shown in figure below, two 4-bit parallel-in serial-out shift registers loaded with the data shown are used to feed the data to a full adder. Initially, all

the flip-flops are in clear state. After applying two clock pulses, the outputs of the full-adder should be




- (A) $S = 0 \quad C_0 = 0$
- (B) $S = 0 \quad C_0 = 1$
- (C) $S = 1 \quad C_0 = 0$
- (D) $S = 1 \quad C_0 = 1$

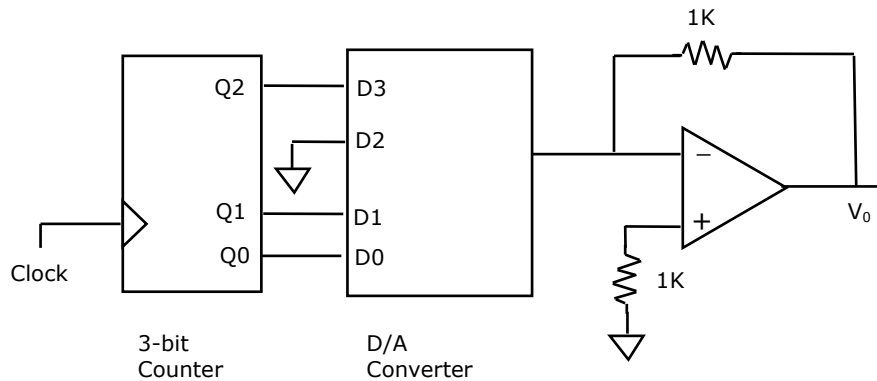
46. A 4-bit D/A converter is connected to a free-running 3-bit UP counter, as shown in the following figure. Which of the following waveforms will be observed at V_0 ?



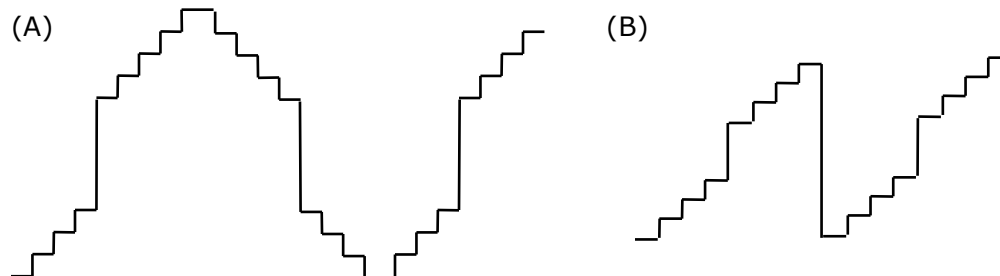
In the figure shown above, the ground has been shown by the symbol ∇



(C)

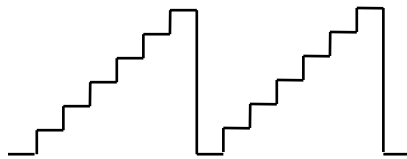


(D)

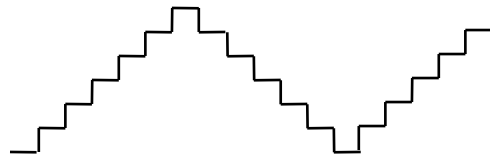

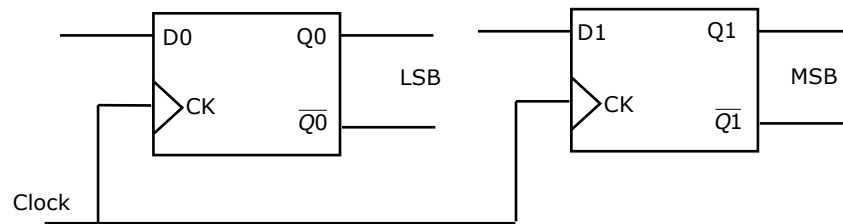47. Two D-flip-flops, as shown below, are to be connected as a synchronous counter that goes through the following Q_1Q_0 sequence

$00 \rightarrow 01 \rightarrow 11 \rightarrow 10 \rightarrow 00 \rightarrow \dots$

The inputs D_0 and D_1 respectively should be connected as




- (A) \bar{Q}_1 and Q_0
(B) \bar{Q}_0 and Q_1
(C) \bar{Q}_1Q_0 and \bar{Q}_1Q_0
(D) $\bar{Q}_1\bar{Q}_0$ and Q_1Q_0
48. Following is the segment of a 8085 assembly language program:

```
LXI SP, EFFF H
CALL 3000 H
:
:
3000 H : LXI H, 3CF4 H
        PUSH PSW
        SPHL
        POP PSW
        RET
```


On completion of RET execution, the contents of SP is:

- (A) 3CFO H
- (B) 3CF8 H
- (C) 3FFD H
- (D) EFFF H

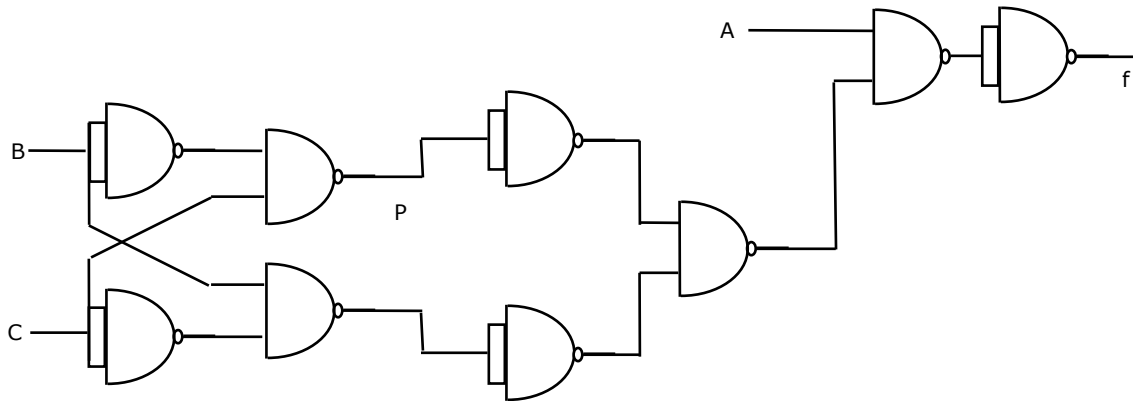49. The point P in the following figure is stuck-at-1. The output f will be



- (A) \overline{ABC}
- (B) \overline{A}
- (C) ABC
- (D) A

50. A signal $m(t)$ with bandwidth 500 Hz is first multiplied by a signal $g(t)$ where

$$g(t) = \sum_{k=-\infty}^{\infty} (-1)^k \delta(t - 0.5 \times 10^{-4} k)$$

The resulting signal is then passed through an ideal lowpass filter with bandwidth 1 kHz. The output of the lowpass filter would be:

- (A) $\delta(t)$
- (B) $m(t)$
- (C) 0
- (D) $m(t)\delta(t)$


51. The minimum sampling frequency (in samples/sec) required to reconstruct the following signal from its samples without distortion.

$$x(t) = 5 \left(\frac{\sin 2\pi 1000t}{\pi t} \right)^3 + 7 \left(\frac{\sin 2\pi 1000t}{\pi t} \right)^2 \text{ would be:}$$

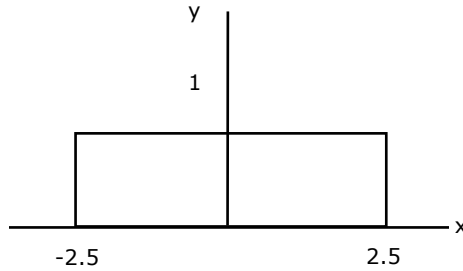- (A) 2×10^3
 (B) 4×10^3
 (C) 6×10^3
 (D) 8×10^3
52. A uniformly distributed random variable X with probability density function

$$f_x(x) = \frac{1}{10}(u(x+5) - u(x-5))$$

Where $u(\cdot)$ is the unit step function is passed through a transformation given in the figure below. The probability density function of the transformed random variable Y would be



- (A) $f_Y(y) = \frac{1}{5}(u(y+2.5) - u(y-2.5))$
 (B) $f_Y(y) = 0.5\delta(y) + 0.5\delta(y-1)$
 (C) $f_Y(y) = 0.25\delta(y+2.5) + 0.25\delta(y-2.5) + 0.5\delta(y)$
 (D) $f_Y(y) = 0.25\delta(y+2.5) + 0.25\delta(y-2.5) + \frac{1}{10}(u(y+2.5) - u(y-2.5))$
53. A system with input $x[n]$ and output $y[n]$ is given as $y[n] = \left(\sin \frac{5}{6} \pi n \right) x(n)$. The system is:
- (A) linear, stable and invertible
 (B) non-linear, stable and non-invertible

- (C) linear, stable and non-invertible
- (D) linear, unstable and invertible


54. The unit-step response of a system starting from rest is given by

$$c(t) = 1 - e^{-2t} \text{ for } t \geq 0$$

The transfer function of the system is:

- (A) $\frac{1}{1+2s}$
 - (B) $\frac{2}{2+s}$
 - (C) $\frac{1}{2+s}$
 - (D) $\frac{2s}{1+2s}$
55. The Nyquist plot of $G(j\omega)H(j\omega)$ for a closed loop control system, passes through $(-1, j0)$ point in the GH plane. The gain margin of the system in dB is equal to
- (A) infinite
 - (B) greater than zero
 - (C) less than zero
 - (D) zero

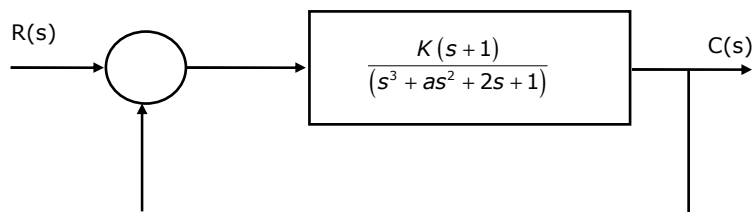56. The positive values of "K" and "a" so that the system shown in the figure below oscillates at a frequency of 2 rad/sec respectively are



- (A) 1, 0.75
- (B) 2, 0.75
- (C) 1, 1

(D) 2, 2

57. The unit impulse response of a system is:

$$h(t) = e^{-t}, \quad t \geq 0$$

For this system, the steady-state value of the output for unit step input is equal to

- (A) -1
- (B) 0
- (C) 1
- (D) ∞

58. The transfer function of a phase-lead compensator is given by

$$G_c(s) = \frac{1 + 3Ts}{1 + Ts} \quad \text{where } T > 0$$

The maximum phase-shift provided by such a compensator is:

- (A) $\frac{\pi}{2}$
- (B) $\frac{\pi}{3}$
- (C) $\frac{\pi}{4}$
- (D) $\frac{\pi}{6}$

59. A linear system is described by the following state equation

$$\dot{X}(t) = AX(t) + BU(t), \quad A = \begin{bmatrix} 0 & 1 \\ -1 & 0 \end{bmatrix}$$

The state-transition matrix of the system is:

- (A) $\begin{bmatrix} \cos t & \sin t \\ -\sin t & \cos t \end{bmatrix}$
- (B) $\begin{bmatrix} -\cos t & \sin t \\ -\sin t & -\cos t \end{bmatrix}$
- (C) $\begin{bmatrix} -\cos t & -\sin t \\ -\sin t & \cos t \end{bmatrix}$
- (D) $\begin{bmatrix} \cos t & -\sin t \\ \cos t & \sin t \end{bmatrix}$


60. The minimum step-size required for a Delta-Modulator operating at 32 K samples/sec to track the signal (here $u(t)$ is the unit-step function)

$$x(t) = 125t(u(t) - u(t-1)) + (250 - 125t)(u(t-1) - u(t-2))$$

So that slope-overload is avoided, would be


- (A) 2^{-10}
(B) 2^{-8}
(C) 2^{-6}
(D) 2^{-4}
61. A zero-mean white Gaussian noise is passed through an ideal lowpass filter of bandwidth 10 kHz. The output is then uniformly sampled with sampling period $t_s = 0.03$ msec. The samples so obtained would be
(A) correlated
(B) statistically independent
(C) uncorrelated
(D) orthogonal
62. A source generates three symbols with probabilities 0.25, 0.25, 0.50 at a rate of 3000 symbols per second. Assuming independent generation of symbols, the most efficient source encoder would have average bit rate as
(A) 6000 bits/sec
(B) 4500 bits/sec
(C) 3000 bits/sec
(D) 1500 bits/sec
63. The diagonal clipping in Amplitude Demodulation (using envelope detector) can be avoided if RC time-constant of the envelope detector satisfies the following condition, (here W is message bandwidth and ω_c is carrier frequency both in rad/sec)
(A) $RC < \frac{1}{W}$
(B) $RC > \frac{1}{W}$
(C) $RC < \frac{1}{\omega_c}$
(D) $RC > \frac{1}{\omega_c}$

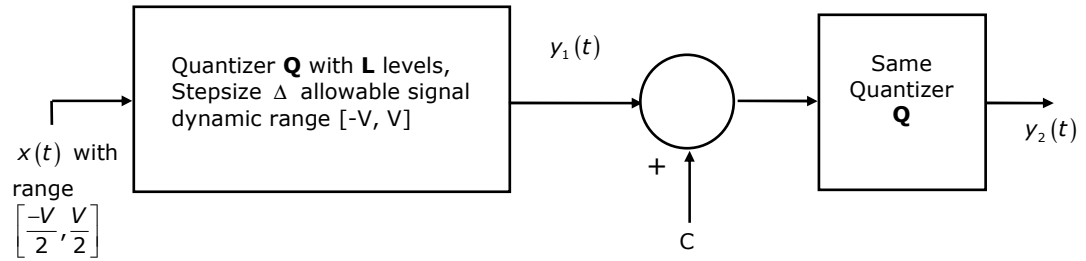64. In the following figure the minimum value of the constant "C", which is to be added to $y_1(t)$ such that $y_1(t)$ and $y_2(t)$ are different, is



- (A) Δ
- (B) $\frac{\Delta}{2}$
- (C) $\frac{\Delta^2}{12}$
- (D) $\frac{\Delta}{L}$
65. A message signal with bandwidth 10 kHz is Lower-Side Band SSB modulated with carrier frequency $f_{c1} = 10^6$ Hz. The resulting signal is then passed through a Narrow-Band Frequency Modulator with carrier frequency $f_{c2} = 10^9$ Hz. The bandwidth of the output would be:
- (A) 4×10^4 Hz
- (B) 2×10^6 Hz
- (C) 2×10^9 Hz
- (D) 2×10^{10} Hz
66. A medium of relative permittivity $\epsilon_{r2} = 2$ forms an interface with free-space. A point source of electromagnetic energy is located in the medium at a depth of 1 meter from the interface. Due to the total internal reflection, the transmitted beam has a circular cross-section over the interface. The area of the beam cross-section at the interface is given by
- (A) $2\pi m^2$
- (B) $\pi^2 m^2$
- (C) $\frac{\pi}{2} m^2$
- (D) πm^2

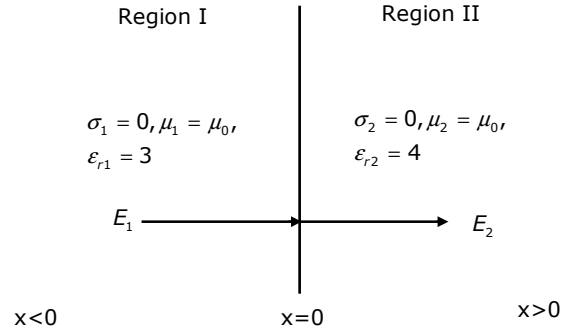67. A medium is divided into regions I and II about $x = 0$ plane, as shown in the figure below. An electromagnetic wave with electric field $E_1 = 4\hat{a}_x + 3\hat{a}_y + 5\hat{a}_z$ is incident normally on the interface from region-I. The electric field E_2 in region-II at the interface is:



- (A) $E_2 = E_1$
 (B) $4\hat{a}_x + 0.75\hat{a}_y - 1.25\hat{a}_z$
 (C) $3\hat{a}_x + 3\hat{a}_y + 5\hat{a}_z$
 (D) $-3\hat{a}_x + 3\hat{a}_y + 5\hat{a}_z$
68. When a plane wave traveling in free-space is incident normally on a medium having $\epsilon_r = 4.0$, the fraction of power transmitted into the medium is given by
- (A) $\frac{8}{9}$
 (B) $\frac{1}{2}$
 (C) $\frac{1}{3}$
 (D) $\frac{5}{6}$
69. A rectangular waveguide having TE_{10} mode as dominant mode is having a cutoff frequency of 18-GHz for the TE_{30} mode. The inner broad-wall dimension of the rectangular waveguide is:
- (A) $\frac{5}{3}$ cms
 (B) 5 cms
 (C) $\frac{5}{2}$ cms
 (D) 10 cms

70. A mast antenna consisting of a 50 meter long vertical conductor operates over a perfectly conducting ground plane. It is base-fed at a frequency of 600 kHz. The radiation resistance of the antenna in Ohms is:

- (A) $\frac{2\pi^2}{5}$
 (B) $\frac{\pi^2}{5}$
 (C) $\frac{4\pi^2}{5}$
 (D) $20\pi^2$


Common Data Questions:

Common Data for Questions 71, 72, 73:

In the transistor amplifier circuit shown in the figure below, the transistor has the following parameters:

$$\beta_{DC} = 60, V_{BE} = 0.7V, h_{ie} \rightarrow \infty, h_{fe} \rightarrow \infty$$

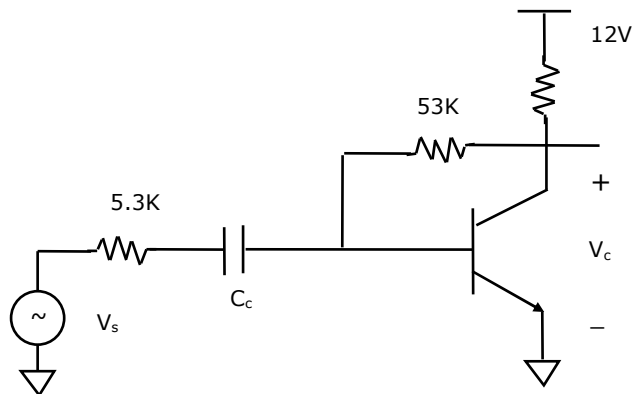The capacitance C_c can be assumed to be infinite.



In the figure above, the ground has been shown by the symbol ∇

71. Under the DC conditions, the collector-to-emitter voltage drop is:
 (A) 4.8 Volts
 (B) 5.3 Volts
 (C) 6.0 Volts
 (D) 6.6 Volts
72. If β_{DC} is increased by 10%, the collector-to-emitter voltage drop

- (A) increases by less than or equal to 10%
- (B) decreases by less than or equal to 10%
- (C) increases by more than 10%
- (D) decreases by more than 10%

73. The small-signal gain of the amplifier v_c/v_s is:
- (A) -10
 - (B) -5.3
 - (C) 5.3
 - (D) 10

Common Data for Questions 74, 75:


Let $g(t) = p(t) * p(t)$, where $*$ denotes convolution and $p(t) = u(t) - u(t-1)$ with $u(t)$ being the unit step function

74. The impulse response of filter matched to the signal $s(t) = g(t) - \delta(t-2) * g(t)$ is given as:
- (A) $s(1-t)$
 - (B) $-s(1-t)$
 - (C) $-s(t)$
 - (D) $s(t)$
75. An Amplitude Modulated signal is given as
- $$x_{AM}(t) = 100(p(t) + 0.5g(t)) \cos \omega_c t$$
- in the interval $0 \leq t \leq 1$. One set of possible values of the modulating signal and modulation index would be
- (A) $t, 0.5$
 - (B) $t, 1.0$
 - (C) $t, 2.0$
 - (D) $t^2, 0.5$

Linked Answer Questions: Q.76 to Q.85 Carry Two Marks Each.

Statement for Linked Answer Questions 76 & 77:

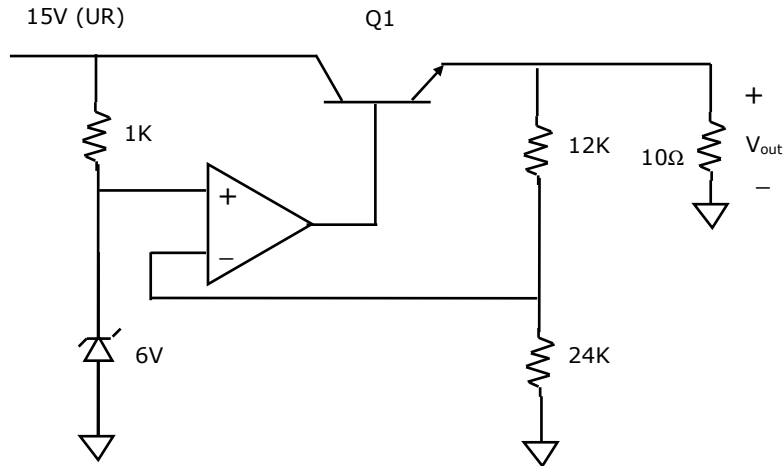A regulated power supply, shown in figure below, has an unregulated input (UR) of 15 Volts and generates a regulated output V_{out} . Use the component values shown in the figure.



In the figure above, the ground has been shown by the symbol ∇

76. The power dissipation across the transistor Q1 shown in the figure is:
 - (A) 4.8 Watts
 - (B) 5.0 Watts
 - (C) 5.4 Watts
 - (D) 6.0 Watts
77. If the unregulated voltage increases by 20%, the power dissipation across the transistor Q1
 - (A) increases by 20%
 - (B) increases by 50%
 - (C) remains unchanged
 - (D) decreases by 20%

Statement for Linked Answer Questions 78 & 79:

The following two questions refer to wide sense stationary stochastic processes

78. It is desired to generate a stochastic process (as voltage process) with power spectral density

$$S(\omega) = \frac{16}{16 + \omega^2}$$

By driving a Linear-Time-Invariant system by zero mean white noise (as voltage process) with power spectral density being constant equal to 1. The system which can perform the desired task could be:

- (A) first order lowpass R-L filter
- (B) first order highpass R-C filter
- (C) tuned L-C filter
- (D) series R-L-C filter

79. The parameters of the system obtained in Q.78 would be
- (A) first order R-L lowpass filter would have $R = 4\Omega$ $L = 4H$
 - (B) first order R-C highpass filter would have $R = 4\Omega$ $C = 0.25F$
 - (C) tuned L-C filter would have $L = 4H$ $C = 4F$
 - (D) series R-L-C lowpass filter would have $R = 1\Omega$, $L = 4H$, $C = 4F$

Statement for Linked Answer Questions 80 & 81:


Consider the following Amplitude Modulated (AM) signal, where $f_m < B$:

$$x_{AM}(t) = 10(1 + 0.5 \sin 2\pi f_m t) \cos 2\pi f_c t$$

80. The average side band power for the AM signal given above is:
- (A) 25
 - (B) 12.5
 - (C) 6.25
 - (D) 3.125

81. The AM signal gets added to a noise with Power Spectral Density $S_n(f)$ given in the figure below. The ratio of average sideband power to mean noise power would be:

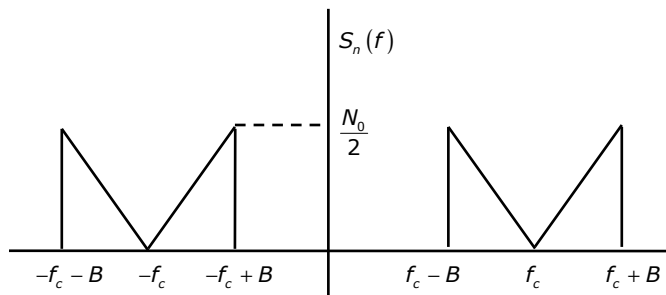- (A) $\frac{25}{8N_0B}$
- (B) $\frac{25}{4N_0B}$
- (C) $\frac{25}{2N_0B}$
- (D) $\frac{25}{N_0B}$



Statement for Linked Answer Questions 82 & 83:

Consider a unity-gain feedback control system whose open-loop transfer function is:

$$G(s) = \frac{as + 1}{s^2}$$

82. The value of "a" so that the system has a phase margin equal to $\frac{\pi}{4}$ is approximately equal to
- (A) 2.40
 - (B) 1.40
 - (C) 0.84
 - (D) 0.74
83. With the value of "a" set for a phase-margin of $\frac{\pi}{4}$, the value of unit-impulse response of the open-loop system at $t = 1$ second is equal to
- (A) 3.40
 - (B) 2.40
 - (C) 1.84
 - (D) 1.74

Statement for Linked Answer Questions 84 & 85:

A 30-Volts battery with zero source resistance is connected to a coaxial line of characteristic impedance of 50 Ohms at $t = 0$ second terminated in an unknown resistive load. The line length is that it takes 400 μ s for an electromagnetic wave to travel from source end to load end and vice-versa. At $t = 400\mu$ s, the voltage at the load end is found to be 40 Volts.

84. The load resistance is
- (A) 25 Ohms
 - (B) 50 Ohms
 - (C) 75 Ohms
 - (D) 100 Ohms
85. The steady-state current through the load resistance is:
- (A) 1.2 Amps
 - (B) 0.3 Amps
 - (C) 0.6 Amps
 - (D) 0.4 Amps