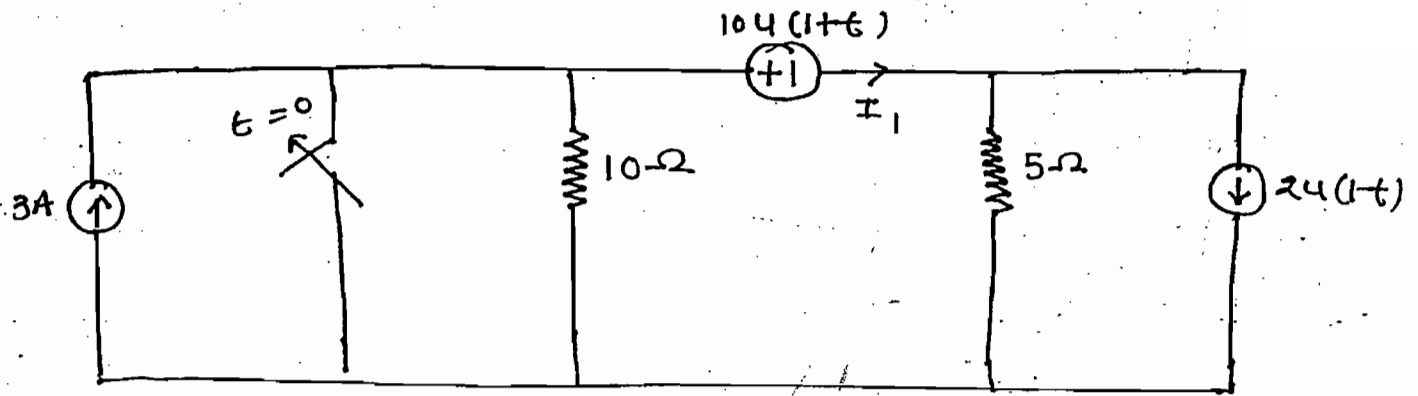


Lecture -11

Ques:- Find I_1 at $t = -2$ seconds:




Soln:-

$$DC \rightarrow -\infty \text{ to } \infty$$



$$u(t) \rightarrow 0 \text{ to } \infty$$

$$u(-t) \rightarrow -\infty \text{ to } 0$$

$$u(1+t)$$

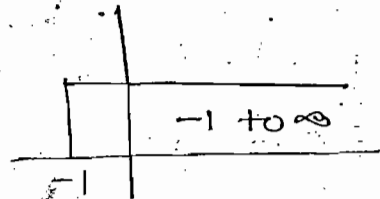


$$u(1-t)$$

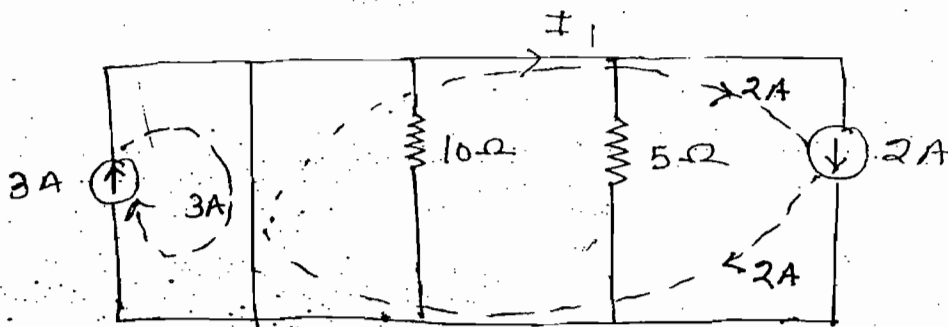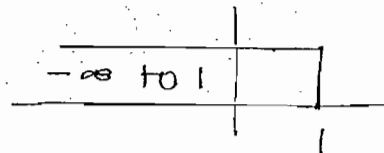

$$I_1 = 2A$$


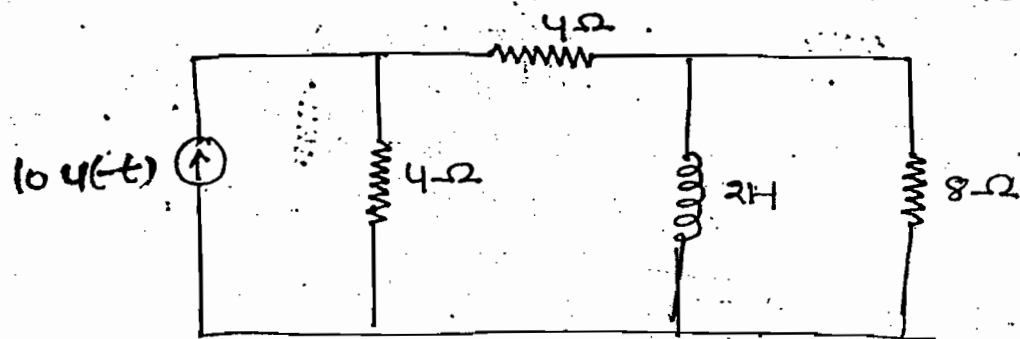
Ques:- Find current response in the inductor for $t > 0$




Soln:-

$$t = 0^-$$
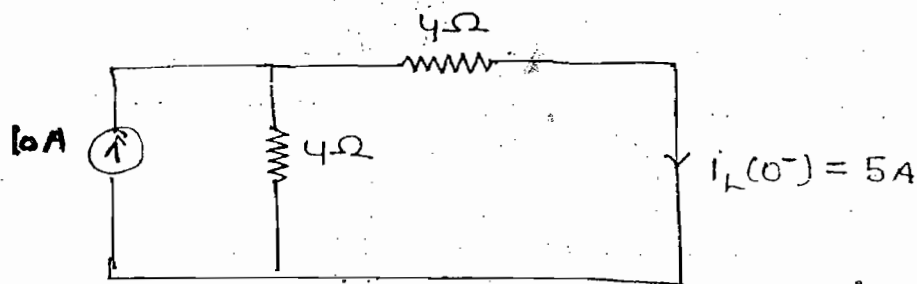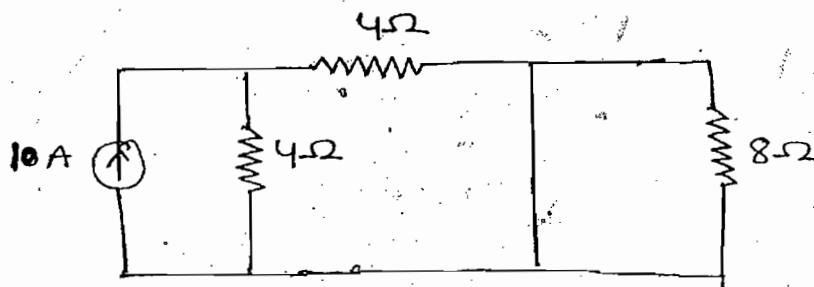
$$u(t) \rightarrow -\infty \text{ to } 0$$




$$t > 0$$

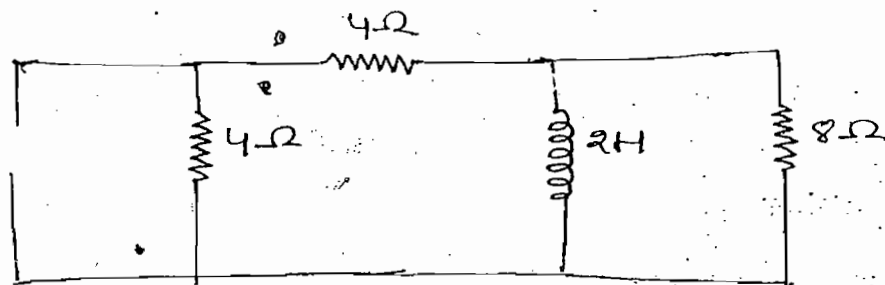


$$i(t) = I_0 e^{-R_L t}$$

$$i(t) = 5 e^{-2t}, \text{ Ans}$$

$$I_0 = i_L(0) = 5A$$

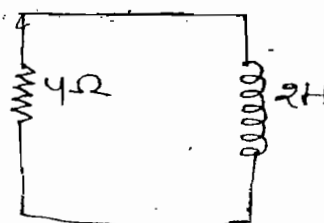

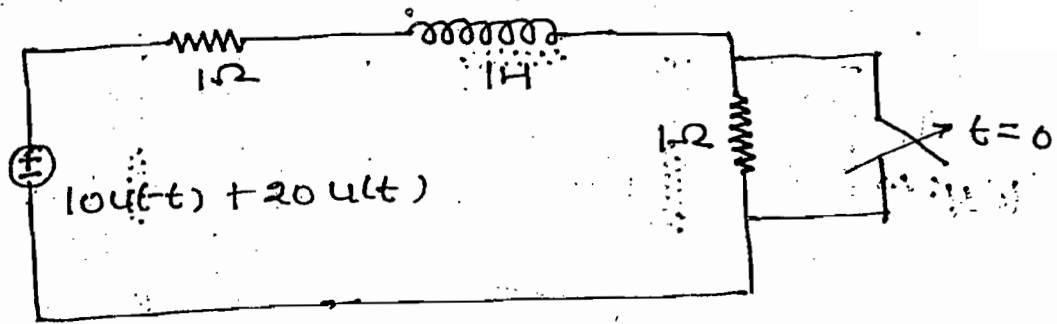
ques:- Find current in the inductor for $t > 0$




soln:- $i(t) = [i(0^+) - i(\infty)] e^{-\frac{R}{L}t} + i(\infty)$

$t = 0^-$

$i(0^+) = i(0^-) = 10A$

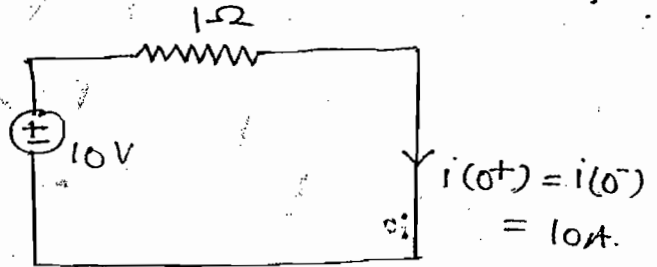

$t = \infty$

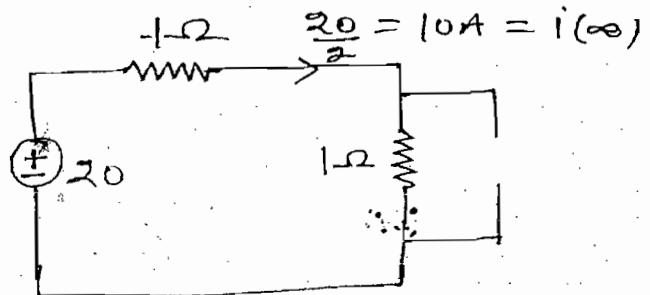

$i(t) = [10 - 10] e^{-R/L t} + 10 = 10 \text{ Ans.}$

TWO PORT NETWORK

→ A pair of terminals at which signal may enter or leave from the N/w is called as port.



Port


A pair of terminals

Single Port


eg:- Motor

→ When the N/w is having one pair of terminals then the N/w is called as single port N/w

eg:- Motor, Generator

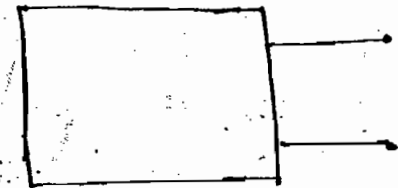

eg:- Generator

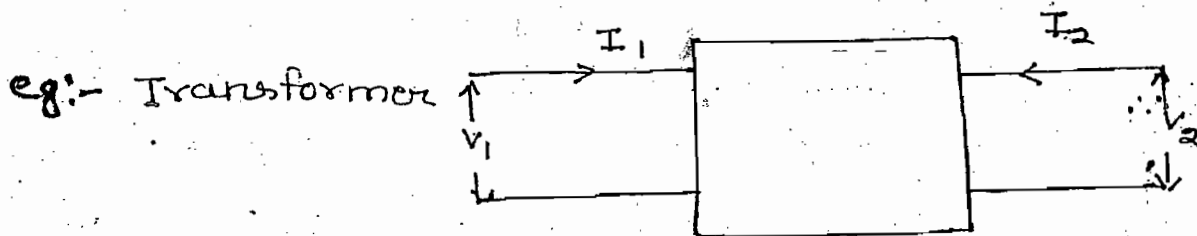

eg:- Transformer

Classification of Parameters:-

- (i) z - Parameter (O.C Parameter)
- (ii) Y - Parameter (S.C Parameter)
- (iii) h - Parameter (Hybrid Parameter)
- (iv) g - Parameter (Inverse hybrid Parameter)
- (v) ABCD - Parameter (Transmission line parameter)
- (vi) abcd - Parameter (Inverse transmission line parameter)

(i) Z-Parameter :-

$$V_1 = Z_{11}I_1 + Z_{12}I_2 \quad \text{---(I)} \rightarrow \text{KVL}$$

$$V_2 = Z_{21}I_1 + Z_{22}I_2 \quad \text{---(II)} \rightarrow \text{KVL}$$

$V_1, V_2 \rightarrow$ Dependent Variables


Source $\rightarrow I_1, I_2 \rightarrow$ Independent Variables

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0}$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0}$$

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0}$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

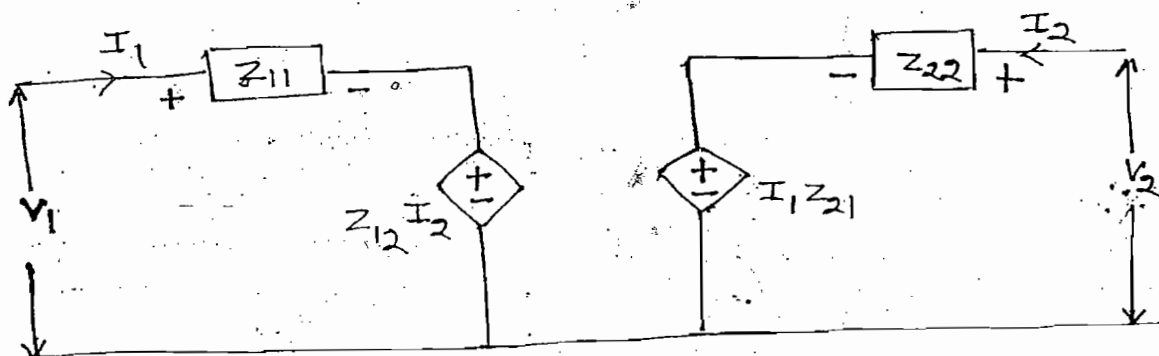

Z_{11} = Open ckt i/p impedance / Driving point i/p impedance

Z_{21} = Forward transfer impedance

Z_{12} = Reverse transfer impedance

Z_{22} = Open ckt o/p impedance / Driving point o/p impedance

(ii) Y-Parameter :-

$$I_1 = Y_{11}V_1 + Y_{12}V_2 \quad \text{---(I)} \rightarrow \text{KCL}$$

$$I_2 = Y_{21}V_1 + Y_{22}V_2 \quad \text{---(II)} \rightarrow \text{KCL}$$

$I_1, I_2 \rightarrow$ Dependent Variables


$V_1, V_2 \rightarrow$ Independent Variables
(source)

$$Y_{11} = \left. \frac{I_1}{V_1} \right|_{V_2=0}$$

$$Y_{12} = \left. \frac{I_1}{V_2} \right|_{V_1=0}$$

$$Y_{21} = \left. \frac{I_2}{V_1} \right|_{V_2=0}$$

$$Y_{22} = \left. \frac{I_2}{V_2} \right|_{V_1=0}$$

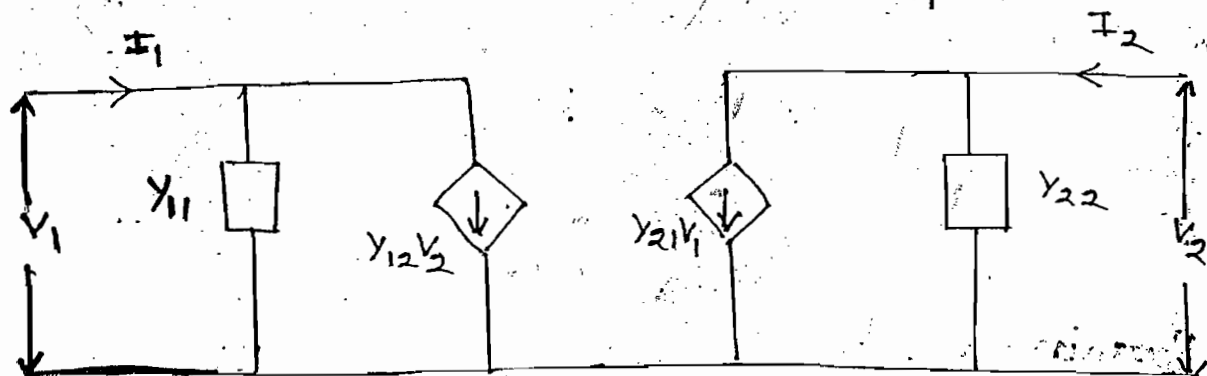

Y_{11} = S.C i/p admittance / Driving point i/p admittance

Y_{21} = forward transfer admittance

Y_{12} = Reverse transfer admittance

Y_{22} = S.C o/p admittance / Driving point o/p admittance

h-Parameter:-

$$V_1 = h_{11}I_1 + h_{12}V_2 \quad \text{--- (I) } \rightarrow \text{KVL}$$

$$I_2 = h_{21}I_1 + h_{22}V_2 \quad \text{--- (II) } \rightarrow \text{KCL}$$

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0} \quad \left(h_{11} \neq Z_{11} \quad , \quad h_{11} = \frac{1}{Y_{11}} \right)$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \left(h_{21} = \frac{Y_{21}}{Y_{11}} = \frac{I_2/V_1}{I_1/V_1} \right)$$


(unitless)

$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0} \quad \left(h_{12} = \frac{Z_{12}}{Z_{22}} \right)$$

↓
Unitless

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} \quad \left(h_{22} \neq Y_{22}, \quad h_{22} = \frac{1}{Z_{22}} \right)$$

↓
(mho)

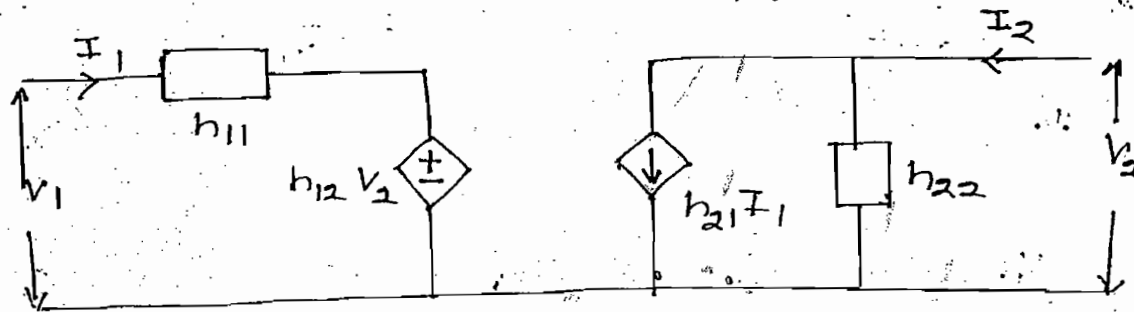

g-Parameters:-

$$I_1 = g_{11}V_1 + g_{12}I_2 \quad \text{--- (I)}$$

$$V_2 = g_{21}V_1 + g_{22}I_2 \quad \text{--- (II)}$$

$$g_{11} = \left. \frac{I_1}{V_1} \right|_{I_2=0}$$

↓
mho

$$\left(g_{11} \neq Y_{11}, \quad g_{11} = \frac{1}{Z_{11}} \right)$$

$$g_{21} = \left. \frac{V_2}{V_1} \right|_{I_2=0}$$

↓
Unitless

$$\left(g_{21} = \frac{Z_{21}}{Z_{11}} \right)$$

$$g_{12} = \left. \frac{I_1}{I_2} \right|_{V_1=0}$$

↓
(Unitless)


$$\left(g_{12} = \frac{Y_{12}}{Y_{22}} \right)$$

$$g_{22} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

↓
Ω

$$\left(g_{22} \neq Z_{22}, \quad g_{22} = \frac{1}{Y_{22}} \right)$$


(mho)

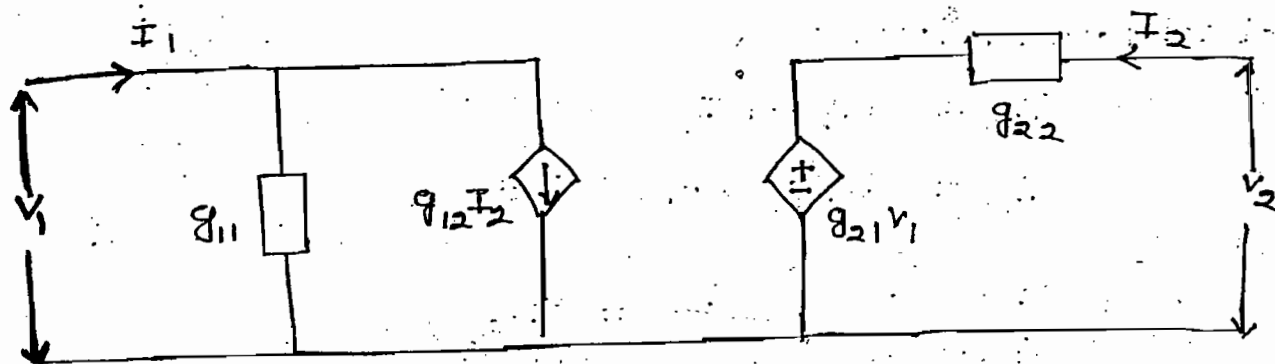

ABCS Parameters:-

$$V_1 = AV_2 - BI_2 \quad \text{--- (I)}$$
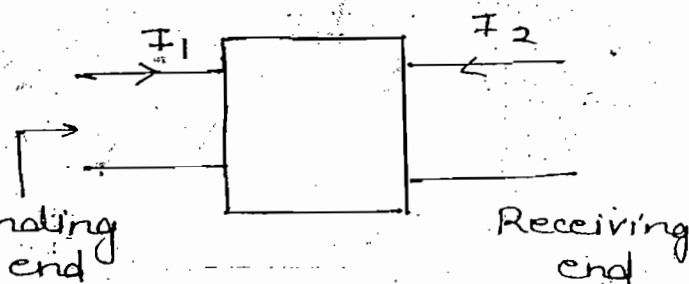
$$I_1 = CV_2 - DI_2 \quad \text{--- (II)}$$



$$A = \left. \frac{V_1}{V_2} \right|_{I_2=0} \quad \left(A = \frac{Z_{11}}{Z_{21}} \right)$$

Unitless

$$C = \left. \frac{I_1}{V_2} \right|_{I_2=0} \quad \left(C = \frac{1}{Z_{21}} \right)$$

mho

$$B = \left. -\frac{V_1}{I_2} \right|_{V_2=0} \quad \left(B = -\frac{1}{Y_{21}} \right)$$

Ω

$$D = \left. -\frac{I_1}{I_2} \right|_{V_2=0} \quad \left(D = -\frac{Y_{11}}{Y_{21}} \right)$$

Unitless

By using eq. (I) & (II) it is not possible to develop ckt since both equations are developed w.r.t i/p

abcd Parameter:-

$$V_2 = aV_1 - bI_1 \quad \text{--- (I)}$$

$$I_2 = cV_1 - dI_1 \quad \text{--- (II)}$$

$$a = \left. \frac{V_2}{V_1} \right|_{I_1=0} \quad \left(a = \frac{Z_{22}}{Z_{12}} \right)$$

Unitless

$$c = \left. \frac{I_2}{V_1} \right|_{I_1=0} \quad \left(c = \frac{1}{Z_{12}} \right)$$


mho

$$b = \left. \frac{-V_2}{I_1} \right|_{V_1=0} \quad \left(b = -\frac{1}{Y_{12}} \right)$$


Ω

$$d = \left. -\frac{I_2}{I_1} \right|_{V_1=0} \quad \left(d = -\frac{Y_{22}}{Y_{12}} \right)$$


No units

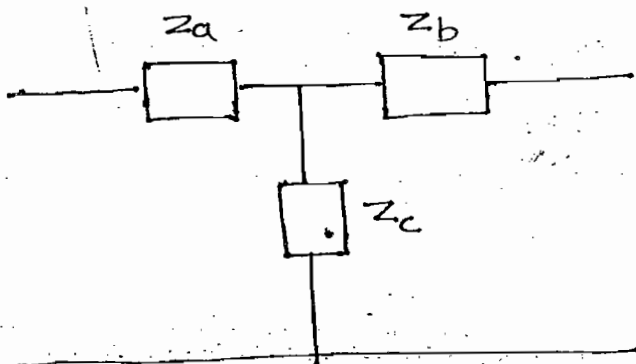


→ Unsymmetrical T-N/w

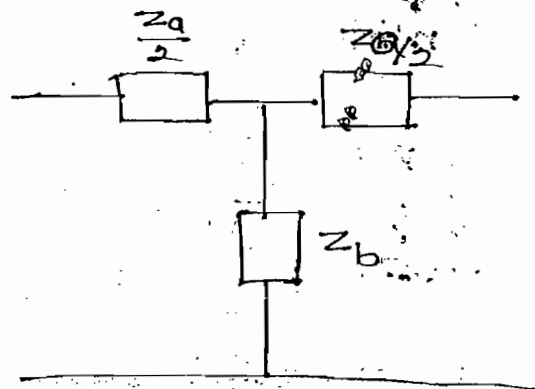


→ Symmetrical T-N/w

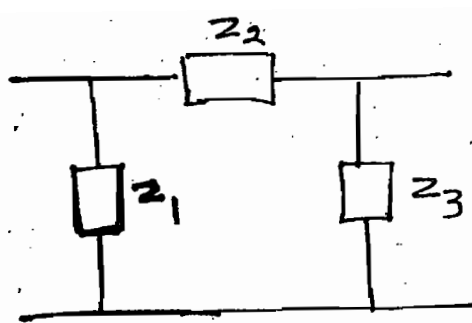

→ Unsymmetrical
T N/w

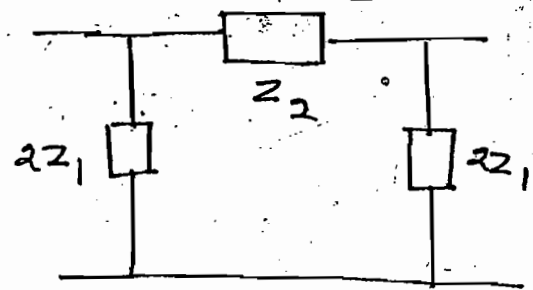

→ Symmetrical - T N/w

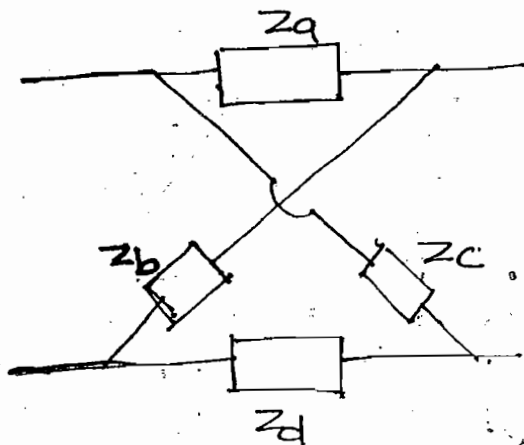

$Z_a = Z_c$
 $Z_b = Z_d$ } Symmetrical
Lattice
N/w

$Z_a \neq Z_c$
 $Z_b \neq Z_d$ } Unsymmetrical
Lattice N/w

**

Symmetrical	Reciprocal
$Z_{11} = Z_{22}$	$Z_{12} = Z_{21}$
$Y_{11} = Y_{22}$	$Y_{12} = Y_{21}$
$h_{11}h_{22} - h_{12}h_{21} = 1$	$h_{12} = -h_{21}$
$A = D$	$AD - BC = 1$


Z-Parameter → Use T-N/w

$$V_1 = (Z_a + Z_b)I_1 + Z_b I_2 \quad \text{--- (I)}$$

$$V_1 = Z_{11} I_1 + Z_{12} I_2 \quad \text{--- (II)}$$

$$Z_{11} = Z_a + Z_b$$

$$Z_{12} = Z_b$$

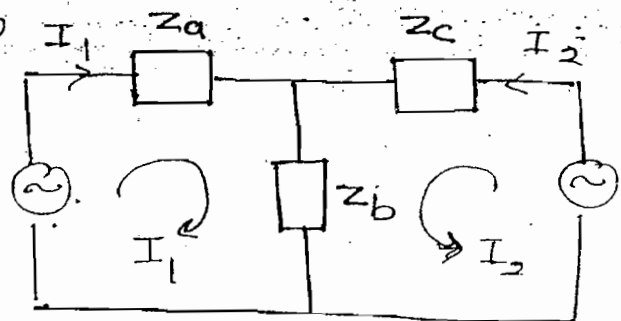

$$V_2 = Z_b I_1 + (Z_b + Z_c) I_2 \quad \text{--- (III)}$$

$$V_2 = Z_{21} I_1 + Z_{22} I_2 \quad \text{--- (IV)}$$

$$Z_{21} = Z_b \quad \& \quad Z_{22} = Z_b + Z_c$$

$$Z_{11} = Z_a + Z_b$$

$$Z_{11} = Z_a + Z_{12}$$

$$Z_a = Z_{11} - Z_{12}$$

$$Z_c = Z_{22} - Z_{12}$$

$$Z_b = Z_{12} = Z_{21}$$

For Y-Parameter $\rightarrow$ Convert complex N/w into Π -N/w

$$I_1 = V_1 Y_a + (V_1 - V_2) Y_b$$

$$I_1 = (Y_a + Y_b) V_1 - Y_b V_2 \quad \text{--- (I)}$$

$$I_1 = Y_{11} V_1 + Y_{12} V_2 \quad \text{--- (II)}$$

$$Y_{11} = Y_a + Y_b$$

$$Y_{12} = -Y_b$$

$$I_2 = V_2 Y_c + (V_2 - V_1) Y_b$$

$$\Rightarrow I_2 = -V_1 Y_b + (Y_b + Y_c) V_2 \quad \text{--- (III)}$$

$$I_2 = Y_{21} V_1 + Y_{22} V_2 \quad \text{--- (IV)}$$


$$Y_{21} = -Y_b \quad \& \quad Y_{22} = Y_b + Y_c$$

**

$$Y_a = Y_{11} + Y_{12}$$

$$Y_c = Y_{22} + Y_{12}$$

$$Y_b = -Y_{12} = -Y_{21}$$

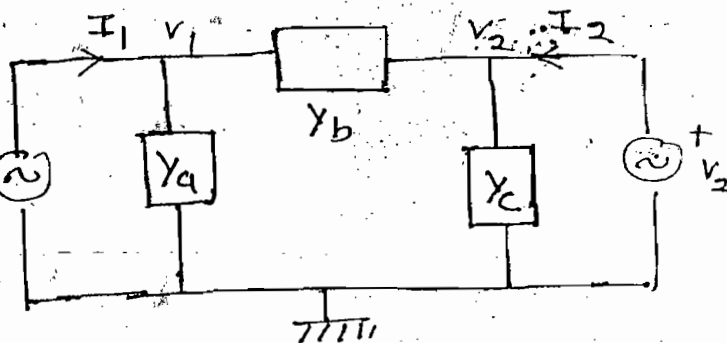

$$Z_a = Z_d, Z_b = Z_c$$


→ Symmetrical lattice N/w

$$Z_{11} = Z_{22} = \frac{Z_b + Z_a}{2}$$

$$Z_{12} = Z_{21} = \frac{Z_b - Z_a}{2}$$

$$Z_b = Z_{11} + Z_{12}$$

$$Z_a = Z_{11} - Z_{12}$$

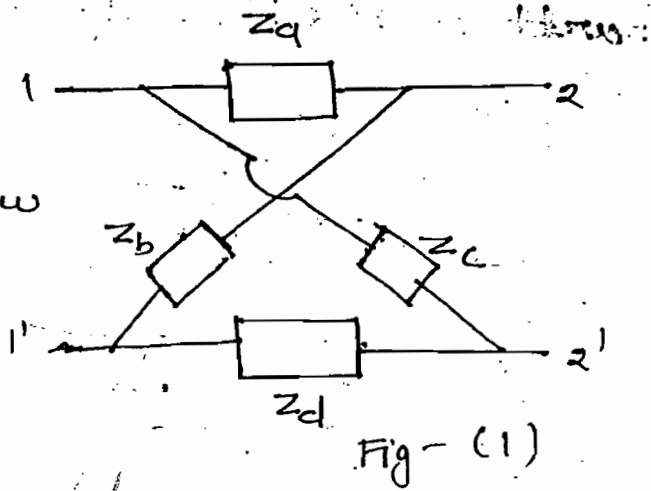


$$Y_a = Y_d, Y_b = Y_c$$

→ Symmetrical lattice N/w

$$Y_{11} = Y_{22} = \frac{Y_b + Y_a}{2}$$
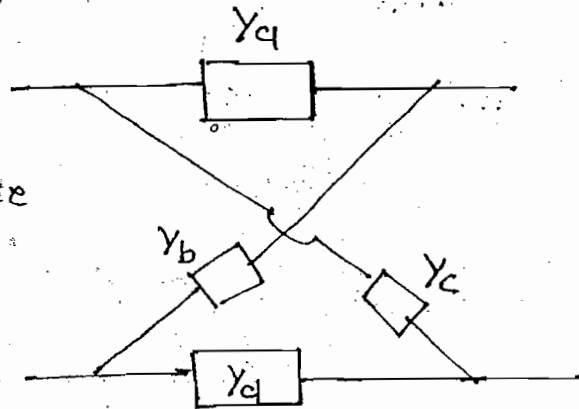
$$Y_{12} = Y_{21} = \frac{Y_b - Y_a}{2}$$




$$Y_b = Y_{11} + Y_{12}$$

$$Y_a = Y_{11} - Y_{12}$$


→ Fig-(1) & (ii) are same.

Fig-(ii)

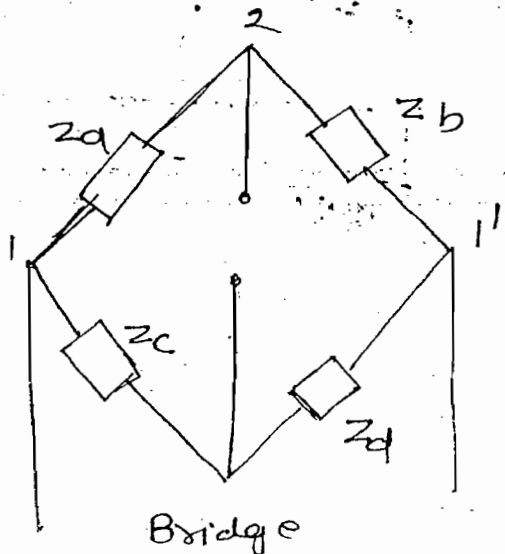

Bartlett's Bi-section theorem:-



eg:- Filter

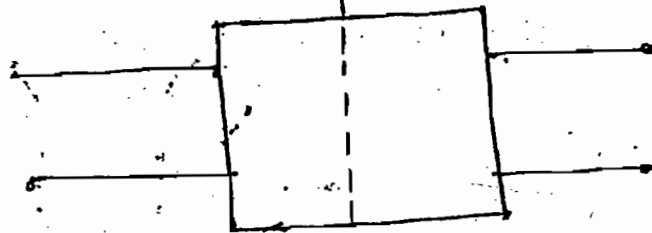



Symmetrical

$$Z_{11} = Z_{22} = \frac{Z_{OCH} + Z_{SCH}}{2}$$
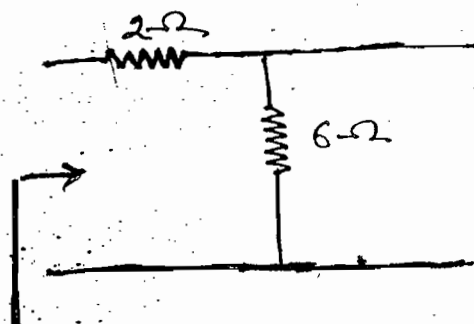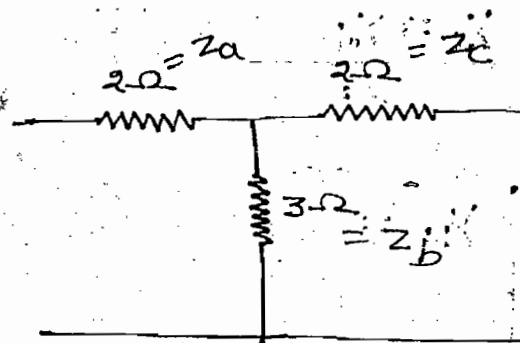
$$Z_{12} = Z_{21} = \frac{Z_{OCH} - Z_{SCH}}{2}$$



$$Z_{OCH} = 2 + 6 = 8$$

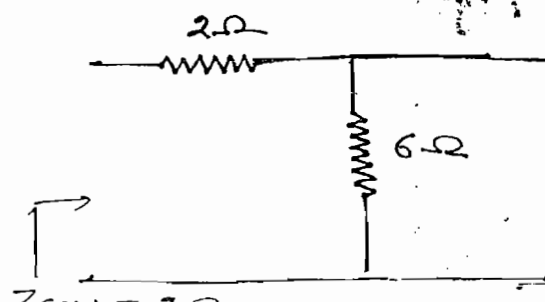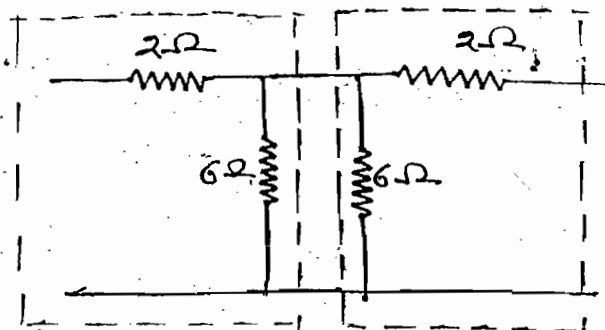

$$Z_{11} = Z_{22} = \frac{Z_{OCH} + Z_{SCH}}{2} = \frac{8+2}{2} = 5$$

$$Z_{12} = Z_{21} = \frac{Z_{OCH} - Z_{SCH}}{2} = \frac{8-2}{2} = 3$$


Alternate Way:-

$$Z_{11} = Z_a + Z_b = 5$$


$$Z_{22} = Z_b + Z_c = 5$$

$$Z_{12} = Z_{21} = Z_b = 3$$

Series combination:-

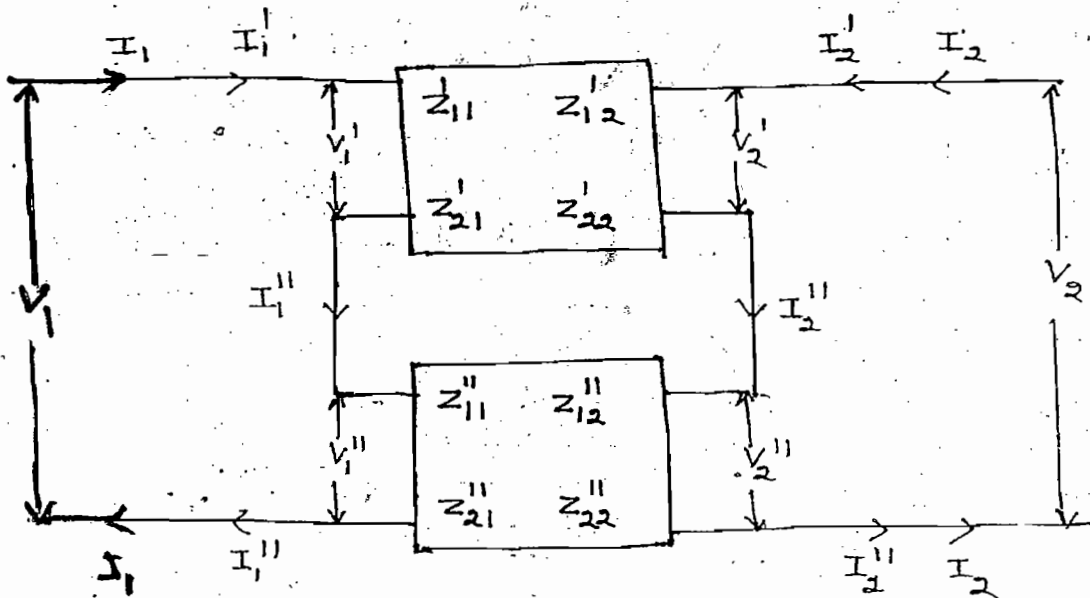

Parallel combination:-

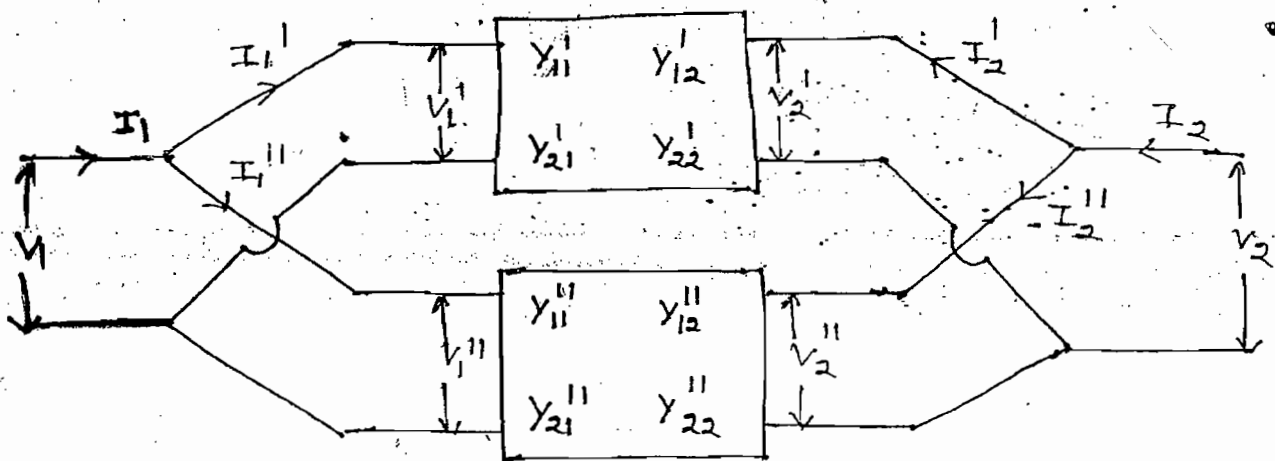

For series combination:-

$$V_1 = V_1' + V_1''$$

$$V_2 = V_2' + V_2''$$

$$I_1 = I_1' = I_1''$$

$$I_2 = I_2' = I_2''$$

$$\begin{bmatrix} z_{11} & z_{12} \\ z_{21} & z_{22} \end{bmatrix} = \begin{bmatrix} z_{11}' & z_{12}' \\ z_{21}' & z_{22}' \end{bmatrix} + \begin{bmatrix} z_{11}'' & z_{12}'' \\ z_{21}'' & z_{22}'' \end{bmatrix}$$

For Parallel combination:-


$$V_1 = V_1' = V_1''$$

$$V_2 = V_2' = V_2''$$

$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$
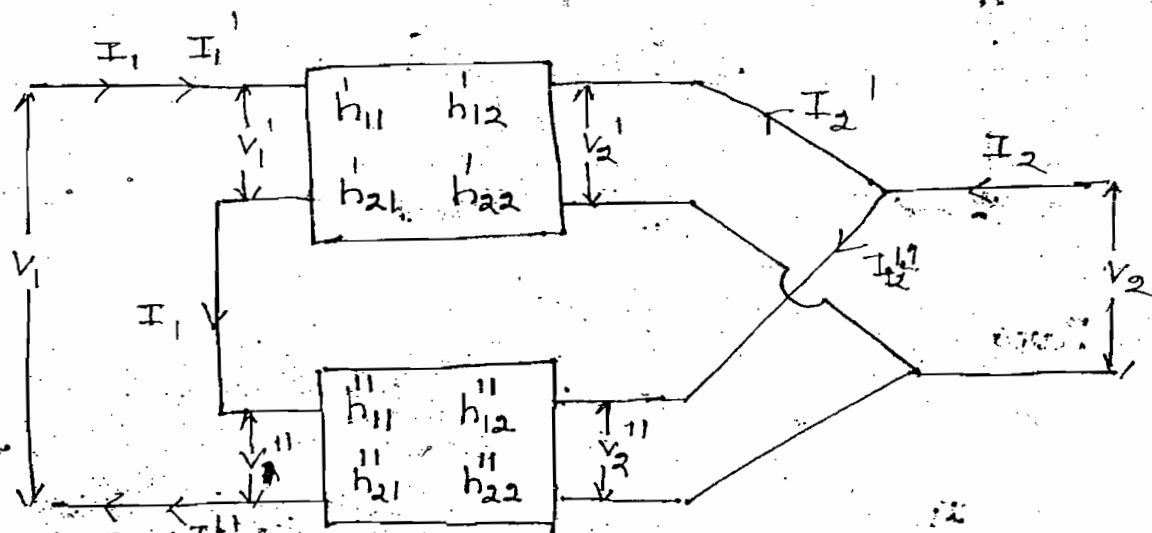
$$\begin{bmatrix} y_{11} & y_{12} \\ y_{21} & y_{22} \end{bmatrix} = \begin{bmatrix} y_{11}' & y_{12}' \\ y_{21}' & y_{22}' \end{bmatrix} + \begin{bmatrix} y_{11}'' & y_{12}'' \\ y_{21}'' & y_{22}'' \end{bmatrix}$$



$$V_1 = V_1' = V_1''$$


$$V_2 = V_2' = V_2''$$

$$I_1 = I_1' + I_1''$$

$$I_2 = I_2' + I_2''$$

$$\begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} = \begin{bmatrix} h_{11}' & h_{12}' \\ h_{21}' & h_{22}' \end{bmatrix} + \begin{bmatrix} h_{11}'' & h_{12}'' \\ h_{21}'' & h_{22}'' \end{bmatrix}$$

Cascade or Tardum Connection:-

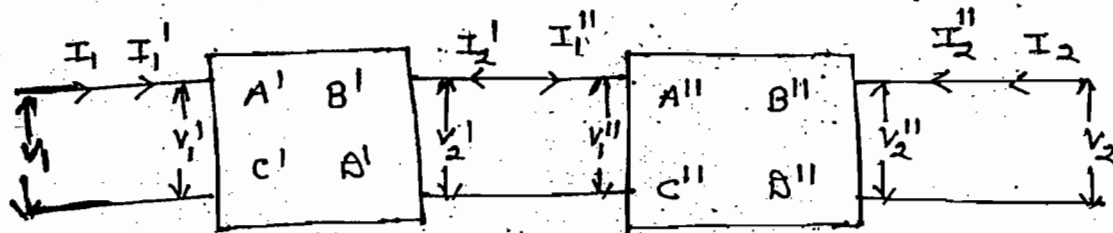

$$\begin{matrix} V_1 = V_1' \\ I_1 = I_1' \end{matrix}$$


$$\begin{matrix} V_2' = V_1'' \\ I_1'' = -I_2' \end{matrix}$$

$$\begin{matrix} V_2 = V_2'' \\ I_2 = I_2'' \end{matrix}$$

$$\begin{bmatrix} A & B \\ C & D \end{bmatrix} = \begin{bmatrix} A' & B' \\ C' & D' \end{bmatrix} \begin{bmatrix} A'' & B'' \\ C'' & D'' \end{bmatrix}$$

Ques:- Find $Z, Y, ABCD$ parameters of the N/w shown:-

Ideal t/f

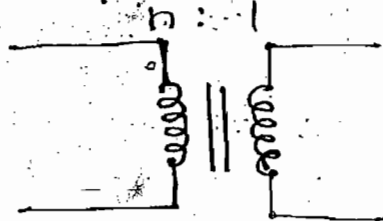

Soln:-

$$A = \frac{V_1}{V_2} = n$$

$$B = -\frac{I_1}{I_2} = +\frac{1}{n}$$

-ve is due to current direction

$$\frac{I_2}{I_1} = \frac{V_1}{V_2} = \frac{N_1}{N_2} = \frac{n}{1}$$


Note:-

In ideal t/f it is not possible to find impedance and admittance values since self and mutual inductance of ideal transformer are ∞

Ques:- Find O.C & S.C impedance w.r.t

(i) 1-1'

(ii) 2-2'

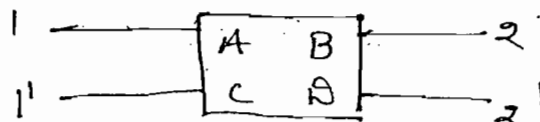

Soln:- (1) 1-1':-

$$Z_{i/p} = \frac{V_1}{I_1} = \frac{AV_2 - BI_2}{CV_2 - BI_2}$$

$$(Z_{i/p})_{o.c} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = \frac{A}{C} \Omega$$

$$(Z_{i/p})_{s.c} = \left. \frac{V_1}{I_1} \right|_{V_2=0} = \frac{B}{A} \Omega$$

(ii) 2-2':-

$$(Z_{o/p})_{o.c} = \left. \frac{V_2}{I_2} \right|_{I_1=0}$$

$$I_1 = CV_2 - BI_2 = 0$$

$$\Rightarrow \frac{V_2}{I_2} = \frac{B}{C}$$

$$(Z_{o/p})_{o.c} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = \frac{B}{C} \Omega$$

$$(Z_{o/p})_{s.c} = \left. \frac{V_2}{I_2} \right|_{V_1=0}$$

$$V_1 = AV_2 - BI_2$$

$$\Rightarrow 0 = AV_2 - BI_2$$


$$\Rightarrow \frac{V_2}{I_2} = \frac{B}{A}$$

$$(Z_{o/p})_{s.c} = \frac{B}{A} \Omega, \text{ Ans}$$

$$B = - \frac{V_1}{I_2} \bigg|_{V_2=0} \Rightarrow \frac{2s+1}{s^2} = \frac{2V-(1)}{2V-(1)}$$

$$\Rightarrow \boxed{Z(s) = \frac{1}{s}} \quad \text{Ans}$$

ques:- Find B and A of the circuit shown

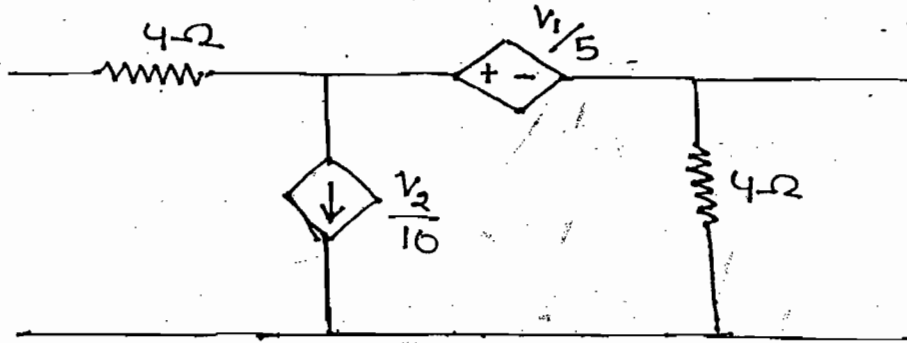


Soln:-

$$B = - \frac{V_1}{I_2} \bigg|_{V_2=0}$$

$$A = - \frac{I_1}{I_2} \bigg|_{V_2=0}$$

$$= - \frac{-(-I_2)}{I_2} = 1$$

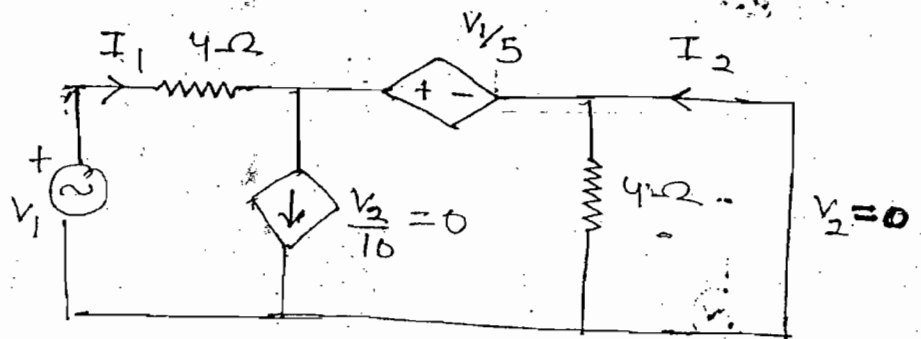

$$I_1 = -I_2$$

$$I_1 = \frac{V_1 - \frac{V_1}{5}}{4}$$

$$-I_2 = \frac{4V_1/5}{4}$$

$$\Rightarrow \boxed{B = - \frac{V_1}{I_2} = 5} \quad \text{Ans}$$