

Theorems

When given N/W having more no. of nodes then Nodal Analysis makes more no. of nodal eqns. If the N/W is having more meshes then mesh Analysis is required more meshing.

$\Rightarrow$ more complexity will present.
For Analysis of large N/W the nodal & mesh Analysis is difficult since complexity.


By using some special Techniques we can reduce the Complexity of Calculations. Thevenin's & Norton's Theorems make the large N/W into a single N/W having voltage source in series with resistance like with Norton's also.

When the N/W is having (or) solving more no. of nodes & meshes the response in any one of the branches can be easily obtained by using theorems.


Superposition theorem:-

In any linear bidirectional ckt having more than one independent source the response in any one of the branches is equal to the algebraic sum of responses caused by individual sources, while the rest of the sources are replaced by its internal resistances.

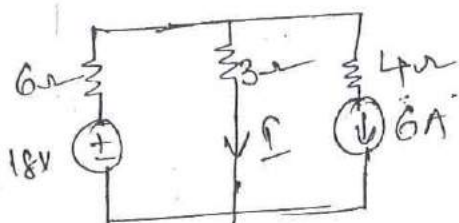(Pb) find the value of 'I' by using Superposition Theorem.




Sol:-

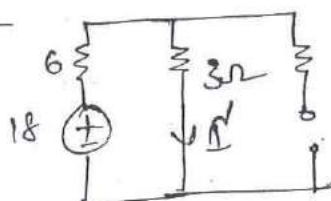


$$I' = \frac{18}{3} = 6A$$

(Pb)

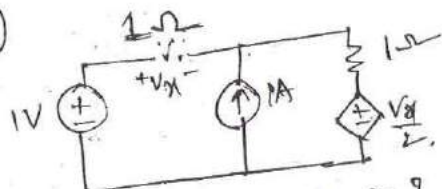

find V_x by S.P.T?

Sol:-

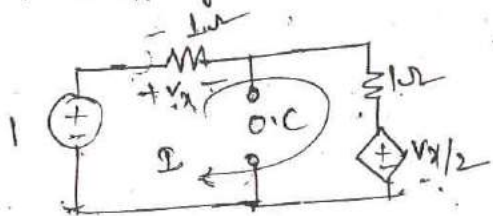


$$-1 + I + I + \frac{I}{2} = 0$$

$$\Rightarrow \frac{5I}{2} = 1$$

$$I = \frac{2}{5} A$$

$$\Rightarrow V_x = \frac{2}{5} V$$

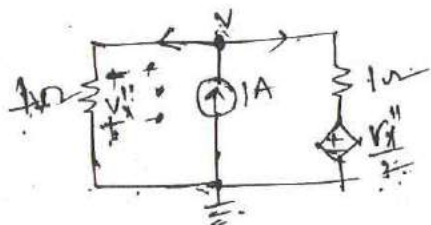

$$\frac{V-0}{1} + \frac{V - \frac{V_x}{2}}{1} = 1 \rightarrow (1)$$

$$V_x = -1 \cdot \left(\frac{V}{1}\right) = V \rightarrow (2)$$

$$\Rightarrow V_x + \left(V - \frac{V_x}{2}\right) = 1 \Rightarrow -2V_x + V_x = 2$$

$$V_x = -\frac{2}{1} \text{ Volts}$$

$$\therefore V_x = V_x' + V_x''$$

$$= \frac{2}{5} + \left(-\frac{2}{1}\right) = \frac{2-10}{5} = -\frac{8}{5}$$

$$V_x = -\frac{8}{5} V$$


$$= -\frac{1.6}{1.25} V$$

NOTE:- While applying Superposition Theorem is replaced by neither open circuit nor short ckt. And it remains same as the original ckt.


$$\Rightarrow V_x'' = -\frac{2}{1} \text{ Volts} \Rightarrow \text{which is -ve}$$

Since in the first ckt $+V_x$ in second ckt $-V_x$

Pb

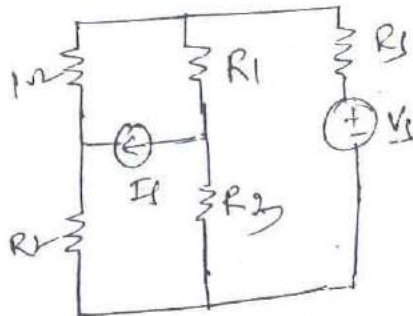

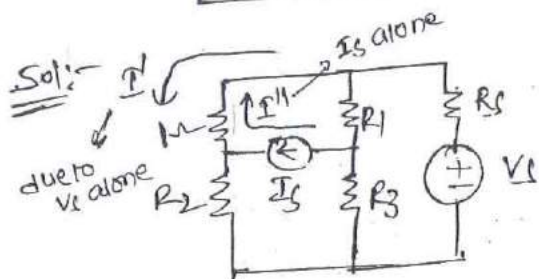In the ckt shown power dissipation in the 1Ω res is $576W$ when voltage source is acting alone. & power dissipation in the 1Ω resistor is $1W$ when current source is acting alone. find total power dissipation in the 1Ω resistor?



$$P^I = I'^2 R \Rightarrow I' = \sqrt{\frac{P_1}{R}}$$

$$P^II = I''^2 R \Rightarrow I'' = \sqrt{\frac{P_2}{R}}$$

$$I = \pm I' \pm I''$$

$$= \pm \sqrt{\frac{P_1}{R}} \pm \sqrt{\frac{P_2}{R}}$$

$$\therefore P = I^2 R$$

$$= \left(\pm \sqrt{\frac{P_1}{R}} \pm \sqrt{\frac{P_2}{R}} \right)^2 \cdot R$$

$$P = \left(\pm \sqrt{P_1} \pm \sqrt{P_2} \right)^2 \dots$$

→ General Expression for power

$$\therefore P = (\sqrt{576} - \sqrt{1})^2 = 529 \dots$$


Pb

In the ckt shown if the source voltage is incremented by 10%, find variation of the power in the R_4 resistor?

Sol:-

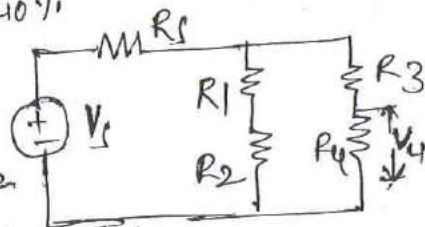- (a) 10% (b) 15% (c) 21% (d) 40%

Since all the elements are linear. If excitation is changed by 'k' factor then response of each element changes with respect to all the elements by factor of 'k'.




$$P_4 = \frac{V_4^2}{R_4}$$

$$P_4' = \frac{(1.1 V_4)^2}{R_4} = 1.21 \frac{V_4^2}{R_4}$$

$$\Rightarrow P_4' = 1.21 P_4 \dots$$

NOTE:- when the N/w is having linear bidirectional elements based on the Homogeneity Principle if excitation is multiply with constant 'k' response of each element also multiply with constant 'k'.

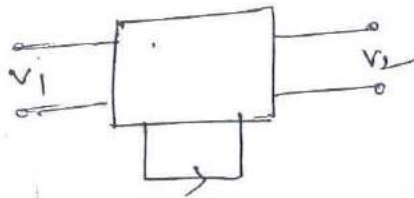(Pb) find the value of 'I' when $V_1 = -15V$ & $V_2 = 10V$.



V_1	V_2	I
0	2V	3A
3V	0	-2A

Sol:-

$V_1 = 3V ; I = -2A$
 when $V_1 = -15V \Rightarrow I = 10A$



$V_2 = 2V ; I = 3A$
 when $V_2 = 10V ; I = 15A$

Based on S.P.T

$I = I' + I'' = 10 + 15 = 25 A$


[Note:- when excitation $\uparrow$ k times $\Rightarrow$ response $\uparrow$ k times]

Thevenin's Theorem :-

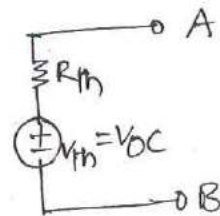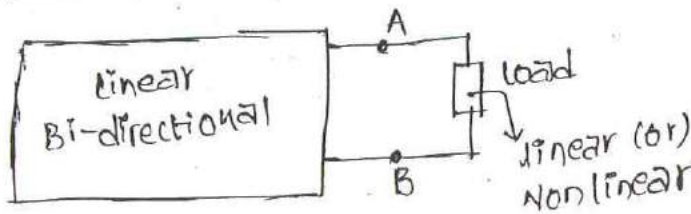

DC

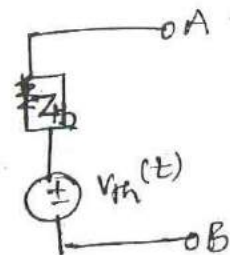
Any linear bidirectional circuit having more number of passive elements, it can be replaced by single equivalent circuit consisting of equivalent voltage source (V_{th}) in series with equivalent resistance (R_{th}).




AC

find I_{a2} by using Thevenin's Theorem?

(Pb)

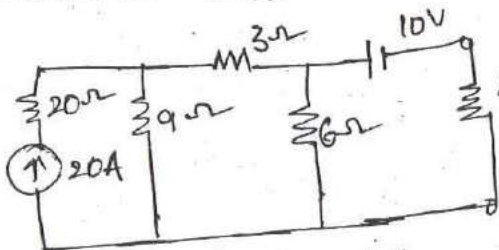


Sol:-

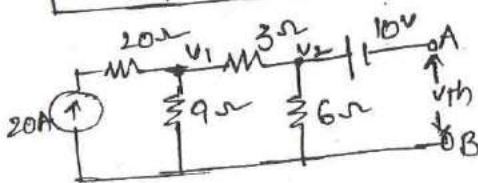

$\frac{V_1}{9} + \frac{V_1 - V_2}{3} = 20 \rightarrow (1)$


Rth:-

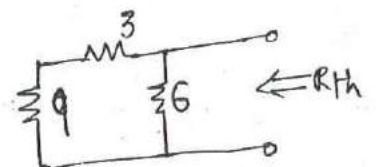


$R_{th} = 3 \parallel 6$
 $= \frac{12 \times 6}{18}$
 $= 4 \Omega$

$$\frac{v_2 - v_1}{3} + \frac{v_2}{6} = 0 \quad \text{--- (2)}$$


(Pb)

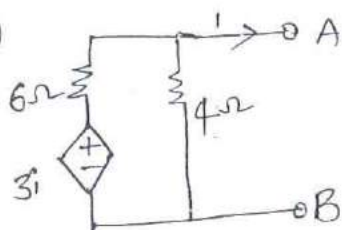find V_{th} & R_{th} w.r.t. to A & B?

sol:-

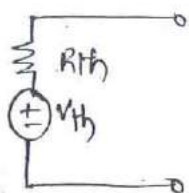


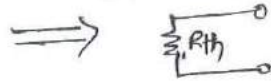Here V_{th} is independent source. but in the given ckt there is no independent source. $\therefore V_{th} = 0$



While finding R_{th} in the above ckt dependent source is replaced by neither open circuit nor short ckt. And it remains same as the original ckt.

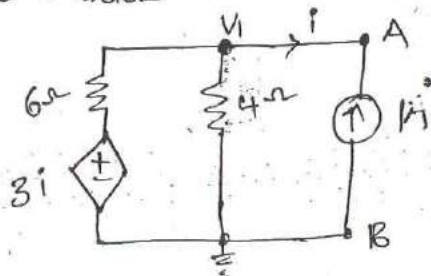Assume voltage source (or) current source b/w A & B with any magnitude. Now, select a current source with 1A.



$$R_{th} = R_{AB} = \frac{V_{AB}}{I_{AB}} = \frac{V_{AB}}{1A}$$

Nodal Analysis $\rightarrow \frac{V_1 - 3i}{6} + \frac{V_1}{4} = 1 \rightarrow (1)$


but $i = -1A$

$$(1) \Rightarrow \frac{V_1 + 3}{6} + \frac{V_1}{4} = 1 \Rightarrow V_1 = 1.2$$

voltage across $4\Omega = \left(\frac{V_1}{4}\right) 4$


$$= V_1 = 1.2V$$
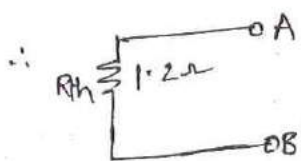
$$\therefore R_{th} = \frac{1.2}{1} = 1.2\Omega$$



$\Leftarrow$ thevenin's eqn ckt.

Note:- let current source = 100A

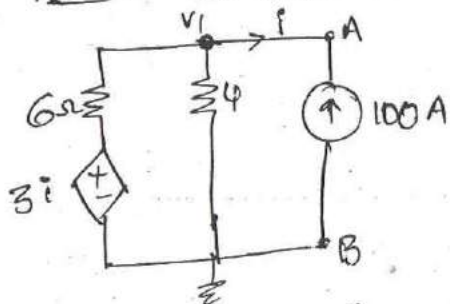


$$\frac{V_1 + 3}{6} + \frac{V_1}{4} = 100 \Rightarrow V_1 = 120$$

$$\therefore R_{th} = \frac{120}{100} = 1.2\Omega$$

When even $I \uparrow \Rightarrow V \uparrow$ proportionally. Since the N/W is linear N/W. Always $\frac{V_{AB}}{I_{AB}}$ ratio is constant.

Note :-

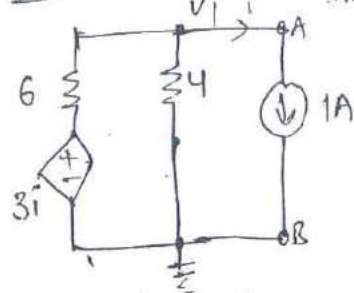


$$\begin{aligned} \frac{V_1 - 3i}{6} + \frac{V_1}{4} + 1 &= 0 \\ \Rightarrow \frac{V_1}{4} &= -1.2V \\ R_{th} &= \frac{V_{AB}}{I_{AB}} \\ &= \frac{1.2}{1} \\ &= 1.2\Omega \end{aligned}$$

Note :-

Whenever elements are connected in parallel current source is taken since calculation is simple.

Whenever " " series voltage source " " .


Note :-

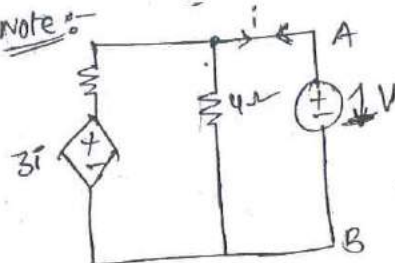

$$\frac{V_{AB}}{I_{AB}} = \frac{1}{1} = 1.2\Omega$$

Note :- we can take any source b/w A & B, but finally $R_{th} = \text{constant} = 1.2\Omega$

(Pb) Find R_{th} w.r.to A & B?

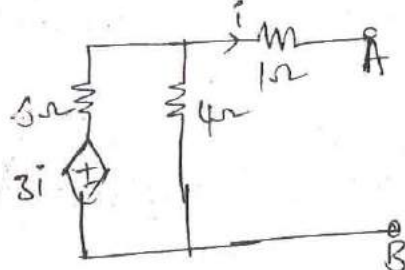


Sol:-

$$\therefore I_s = -i = 5/11 A$$

$$R_{AB} = \frac{V_{AB}}{I_s} = ?$$
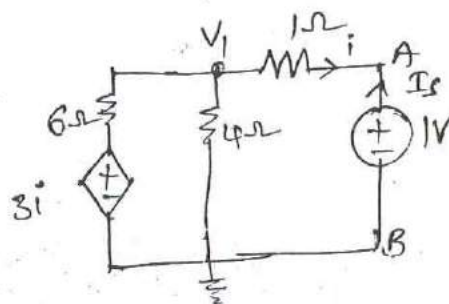
$$V_{AB} = 1V \quad \therefore R_{AB} = \frac{1}{5/11} = \frac{11}{5} = 2.2\Omega$$




$$\frac{V_1 - 3i}{6} + \frac{V_1}{4} + \frac{V_1 - 1}{1} = 0 \rightarrow (1)$$

$$\text{From (1) \& (2)} \Rightarrow V_1 = 6/11 \dots$$

$$i = \frac{V_1 - 1}{1} \rightarrow (2)$$


$$i = \frac{6}{11} - 1 = -\frac{5}{11} A$$

EC
IES
2012

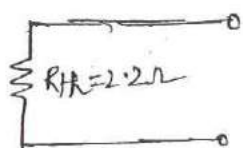

(Pb)

Find openckt voltage w.r.to A & B

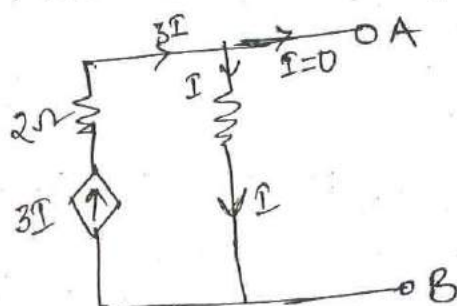


- (a) 0
- (b) 3
- (c) 4V
- (d) NONE

KCL Not Satisfied.


NOTE:- In the above N/w it is not possible to find open circuit voltage since it is not satisfying KCL.

(Pb)

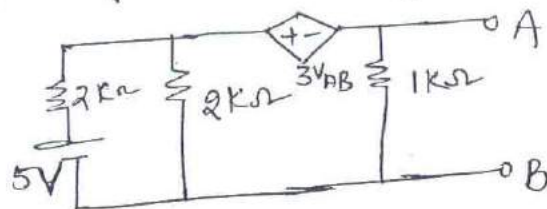

find V_{th} & R_{th} w.r.t. to A & B?

Sol:-

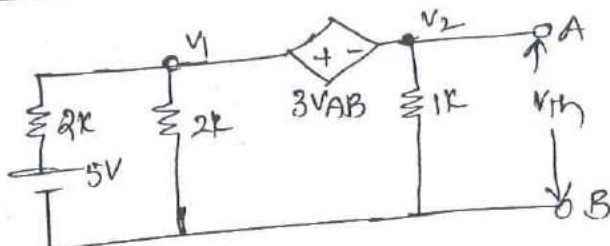

$$\frac{V_1 - 5}{2k} + \frac{V_1}{2k} + V_1 \times \frac{V_2}{1k} = 0 \quad \text{--- (1)}$$

$$V_1 - V_2 = 3V_{AB}$$

$$\text{but } V_2 = V_{AB} \Rightarrow V_1 = 4V_{AB}$$


$$\text{from (1)} \Rightarrow \frac{4V_{AB} - 5}{2k} + \frac{4V_{AB}}{2k} + \frac{V_{AB}}{1k} = 0$$

$$4V_{AB} + 4V_{AB} + 2V_{AB} = 5$$

$$10V_{AB} = 5$$

$$V_{AB} = \frac{1}{2} \text{ Volts}$$

NOW

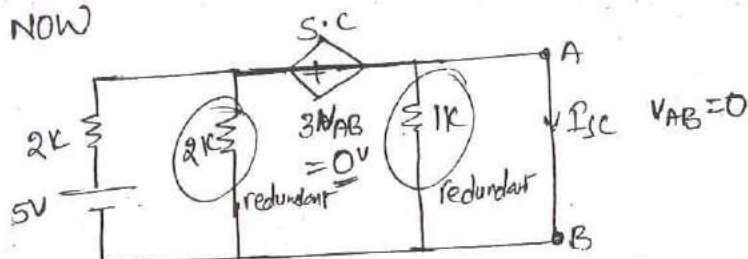


$$I_{sc} = \frac{5}{2k} = 2.5 \text{ mA}$$

$$\therefore R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{1}{2} \div 2.5$$

$$= \frac{1}{5} \text{ mA}$$


$$= 0.2 \text{ k}\Omega$$

$\therefore$ thevenin's circuit is

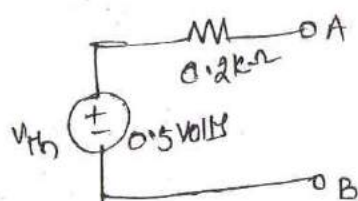


While finding R_{th} make all independent voltage sources replaced with their internal res.

(Q.2) Short voltage source

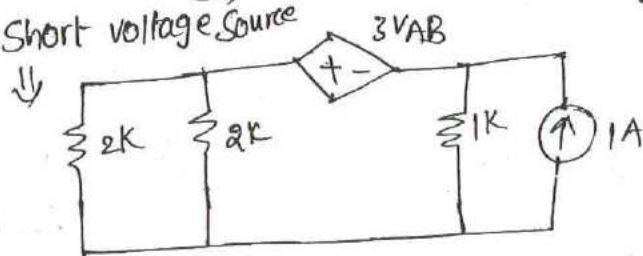
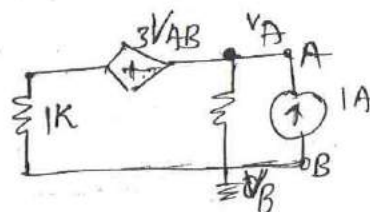
$$R_{th} = \frac{V_{AB}}{I_S} = \frac{200}{1A} = 200 \Omega$$




$$\frac{V_A + 3V_{AB}}{1 \times 10^3} + \frac{V_A}{1 \times 10^3} = 1$$


$$\Rightarrow V_{AB} = 200 \text{ Volts}$$

NORTON'S THEOREM:-

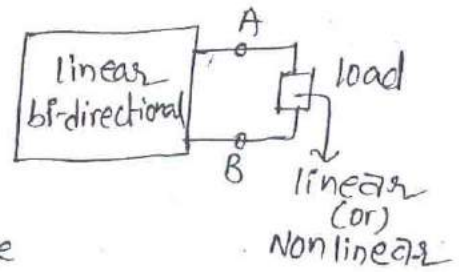
Any linear bidirectional circuit having more No. of Active & passive elements, it can be replaced by single circuit consisting of eqn current source $[I_N]$ in parallel with eqn resistance (R_N) .



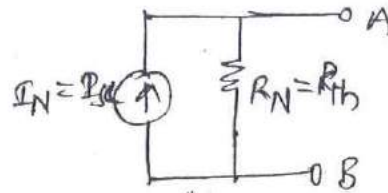(Pb) find Current in the 1Ω resistor by using Norton's Theorem?




DC

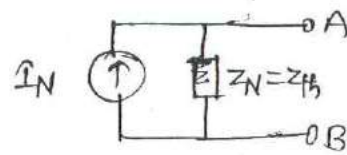

AC

Sol:-

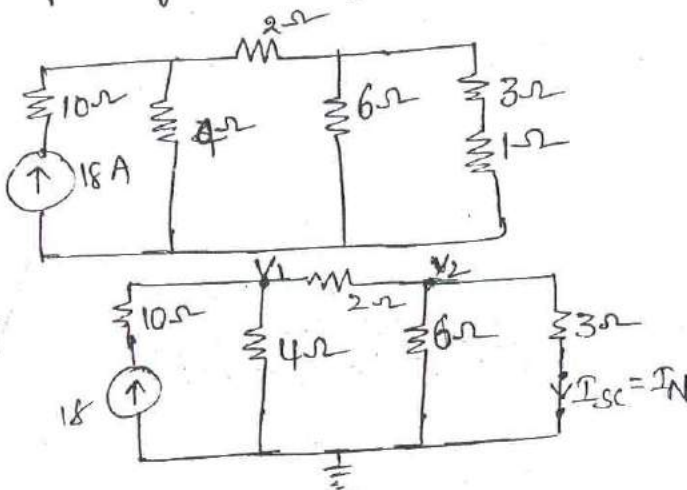

$$\frac{V_1}{4} + \frac{V_1 - V_2}{2} = 18 \rightarrow (1)$$

$$\frac{V_2 - V_1}{2} + \frac{V_2}{6} + \frac{V_2}{3} = 0 \rightarrow (2)$$


$$\therefore I_{sc} = \frac{V_2}{3} = \frac{18}{3} = 6A$$

from (1) & (2)


$$V_1 = 18V$$

$$V_2 = 18V$$


By reduction technique

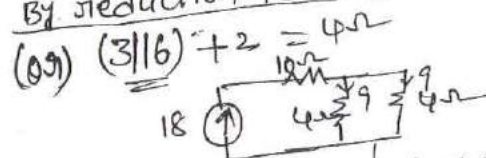

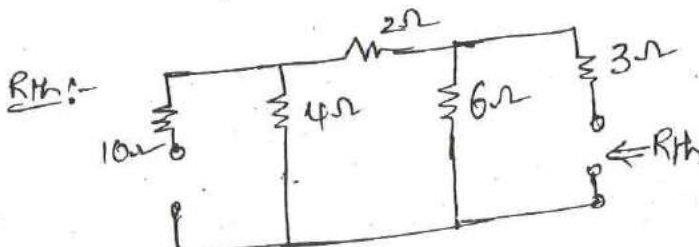Note:- Replace the load resistor by short ckt & find short ckt current.


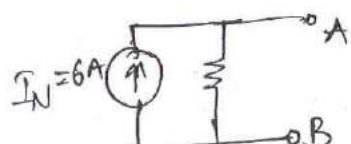
$$R_{Th} = (6 \parallel 3) + 2 = 6\Omega$$




$$\therefore I_{3\Omega} = \frac{6 \times 6}{6+3}$$

$$= 6A$$

$$I_N = 6A$$


Pb

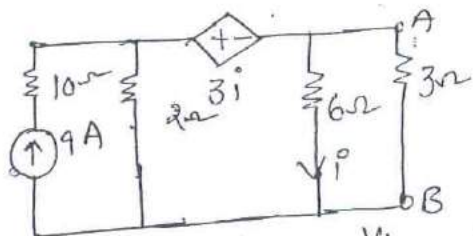

find short ckt current w.r. to A & B?

Sol:-

R_{th}

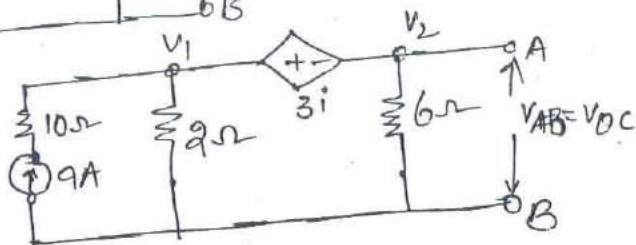

$$\frac{V_1}{2} + \frac{V_2}{6} = 9 \rightarrow (1)$$

$$V_1 - V_2 = 3i$$

$$V_1 - V_2 = 3\left(\frac{V_2}{6}\right)$$

$$V_1 = V_2\left(1 + \frac{1}{2}\right)$$

$$V_1 = \frac{3}{2}V_2 \rightarrow (2)$$

.....

from (1) $\Rightarrow \frac{3V_2}{2} + \frac{V_2}{6} = 9$


$$\frac{3}{4}V_2 + \frac{V_2}{6} = 9$$

$$\frac{9V_2 + 2V_2}{12} = 9$$

$$11V_2 = 108$$

$$V_2 = \frac{108}{11} = V_{oc}$$


.....

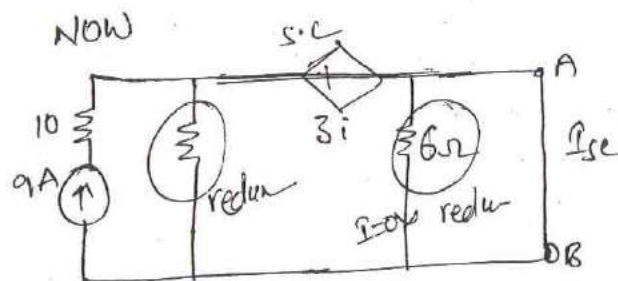

$$I_{sc} = \frac{9}{10} \cdot 9A = \dots$$


$$\therefore R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{108/11}{9/10} = \frac{12}{11} \Omega$$

.....

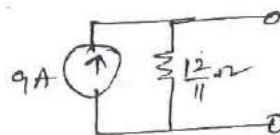


Pb

find V_{oc} & I_{sc} ?

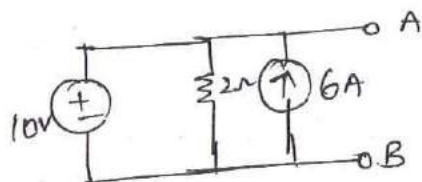


Sol:-

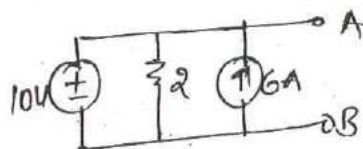

$$V_{AB} = 10V = V_{oc}$$


.....

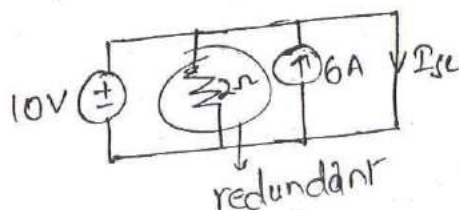

KVL Not satisfied.


Note:- In the above N/W it is not possible to find short-circuit current, since it is not satisfying KVL.

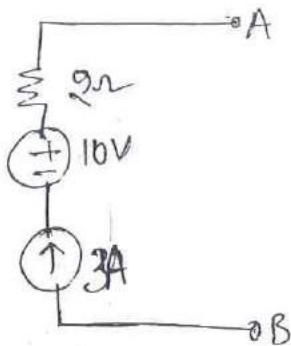(Pb) find V_{oc} & I_{sc} w.r.t. to A & B.




Sol:- $I_{sc} = 3A$

$V_{oc} = ?$

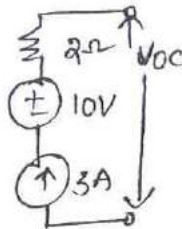


KVL can't be applied, since current source exists
(or)

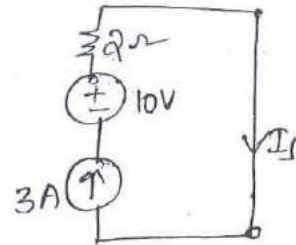$\frac{I}{I} = \frac{3A}{3A}$, $\frac{I}{I} = \frac{0}{0}$ not satisfying KCL.




Note:- In the above ckt it is not possible to find open-circuit voltage since it is not satisfying KCL.

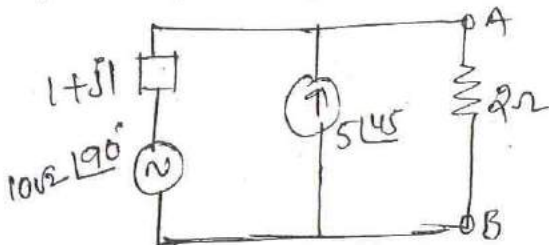(Pb) Find short-circuit current w.r.t. to A & B.



Sol:-

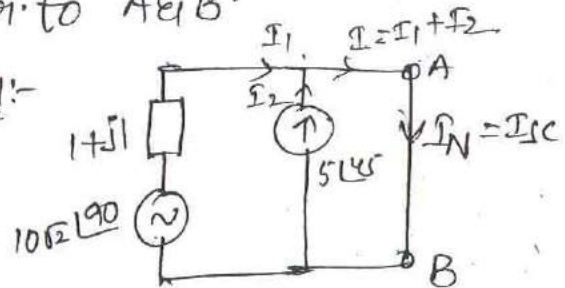

$I_1 = \frac{10\angle 190^\circ}{1+j1} = 10\angle 45^\circ$

$I_2 = 5\angle 45^\circ$

$\therefore I = I_1 + I_2$
 $= 10\angle 45^\circ + 5\angle 45^\circ$
 $= 15\angle 45^\circ A$

(Pb) Find current in the 4 ohm resistor by using the following data.

V	60V	0
I	0	10A


Sol:-

$V_{oc} = 60$

$I_{sc} = 10A$

$\frac{V_{oc}}{I_{sc}} = 6\Omega = R_{th}$

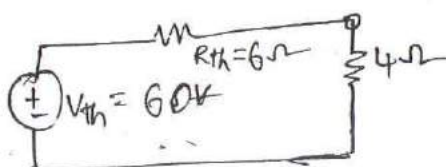
→ (based on Source Transformation theorem we can write this)



$I_{4\Omega} = \frac{60}{10} = 6A = 6A$

Reciprocity :-

Case i:-

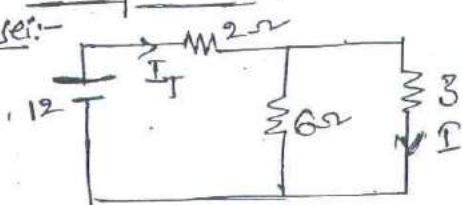

$$I = I_T \cdot \frac{6}{6+3}$$


$$I_T = \frac{12}{R_{eq}}$$

$$R_{eq} = (3 \parallel 6) + 2 = 4 \Omega$$

$$\Rightarrow I_T = \frac{12}{4} = 3A \quad \therefore I = 3 \times \frac{6}{9} = 2A \dots$$

$$\frac{I_2}{V_1} = \frac{\text{Response}}{\text{Excitation}} = \frac{2}{12} = \frac{1}{6} \dots$$

Case (ii):-

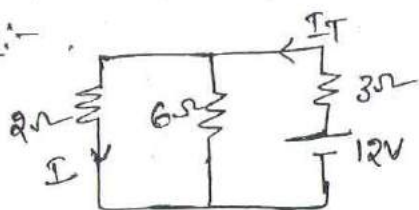

$$R_{eq} = (2 \parallel 6) + 3 = \frac{2 \times 6}{8} + 3 = \frac{9}{2}$$

$$I_T = \frac{12}{9/2}$$

$$I_{2\Omega} = I_T \cdot \frac{6}{6+2} = \left(\frac{12 \times 2}{9} \right) \times \frac{6}{8} = 2A$$

$$= 2A \dots$$

$$\therefore \frac{I_1}{V_2} = \frac{\text{Response}}{\text{Excitation}} = \frac{2}{12} = \frac{1}{6} \dots$$


$$\frac{I_2}{V_1} = \frac{I_1}{V_2}$$

$$\Rightarrow \boxed{\frac{V_2}{I_1} = \frac{V_1}{I_2}} \dots$$

In the above N/W after interchanging response & excitation the ratio of response to excitation is constant. Hence given N/W satisfy the reciprocity. [Linear N/W].

(Pb)

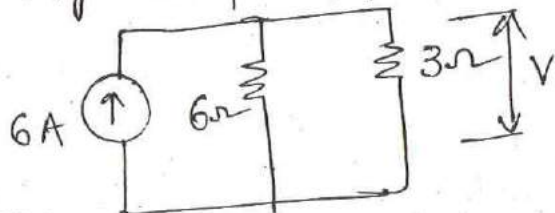verify Reciprocity Theorem of the CKT shown.



Sol:-

$$V = ?$$


$$I_{3\Omega} = 6 \times \frac{6}{9}$$

$$= 4A$$

$$V = 4 \times 3 = 12V$$

$$\frac{\text{Response}}{\text{excitation}} = \frac{12}{6} = 2 \dots$$

Case (ii)

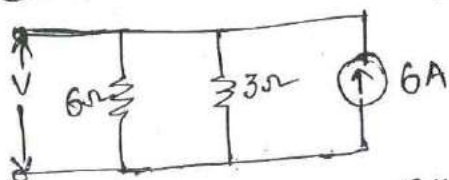

$$I_{6\Omega} = 6 \times \frac{3}{6+3} = 2A$$

$$V = 6 \times 2 = 12V$$


$$\therefore \frac{\text{Response}}{\text{excitation}} = \frac{12}{6} = 2$$

(Pb) Verify Reciprocity Theorem of the ckt shown?




Sol:-
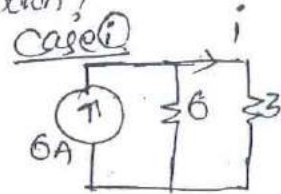
$$i_{3\Omega} = 6 \times \frac{6}{6+3} = 4A$$



Case (ii):

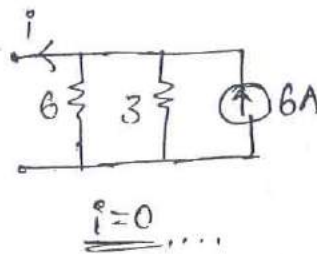

$$\frac{R_{EL}}{E_{XC}} = \frac{4}{6} = \frac{2}{3}$$

$$\frac{R_{EL}}{E_{XC}} = \frac{0}{6} = 0$$

Not Satisfies

Note:-

for first pbm

$$1) \frac{R_{EL}}{E_{XC}} = \frac{i}{V_S} \rightarrow \text{mho}$$

for second pbm

$$2) \frac{R_{EL}}{E_{XC}} = \frac{V}{I_S} \rightarrow \Omega$$

for 3rd pbm

$$3) \frac{R_{EL}}{E_{XC}} = \frac{i}{I_S} \rightarrow \text{No unit}$$

$$4) \frac{R_{EL}}{E_{XC}} = \frac{V}{V_S} \rightarrow \text{No unit}$$

(Only for first two cases we can apply the Reciprocity theorem. for last two cases Reciprocity theorem not applicable.)



Note:-

* To apply the Reciprocity Theorem unit of Response to Excitation should be either mho (or) ohms.

* While applying Reciprocity Theorem ckt should consists of only one independent source.

* When the N/w is having any dependent sources Reciprocity theorem can not be applied.

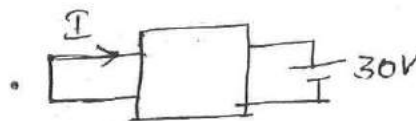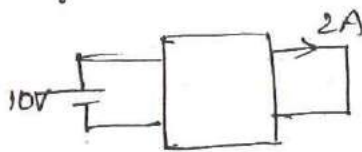(Pb) When given N/w satisfy the Reciprocity find the value of I?



Sol:-

According to Reciprocity theorem Ratio of Response to Excitation is constant. so

Ckt 1:-

$$\frac{2}{10} = \frac{1}{5}$$

for Ckt 2:-

$$\frac{I}{30} = \frac{1}{5} \Rightarrow I = 6A$$


Now come to direction

$$I = -6A$$

direction is


Since Actually the

Qb

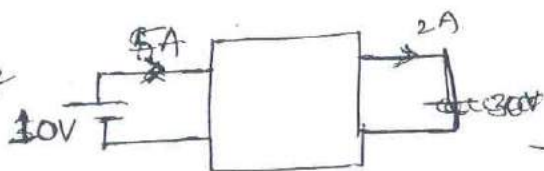


When Given N/w satisfy the Reciprocity find out I?

Sol:-

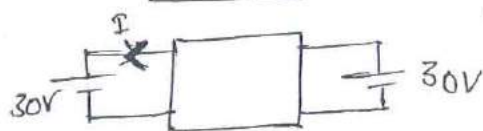

$$\frac{\text{Response}}{\text{excitation}} = \frac{2}{10}$$

case (i):-

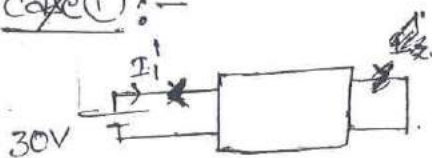

$$\frac{\text{Response}}{\text{excitation}} = -\frac{I_1}{30} = \frac{5}{10}$$

$$\Rightarrow I_1 = -15 \dots$$

case (ii):-





$$\frac{\text{Response}}{\text{excitation}} = \frac{I_1}{30} = \frac{2}{10}$$

$$\Rightarrow I_1 = 6 \dots$$

$$\therefore I = I_1 + I_1' = 6 - 15 = -9 \dots$$

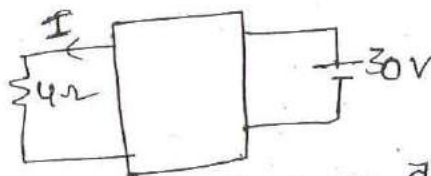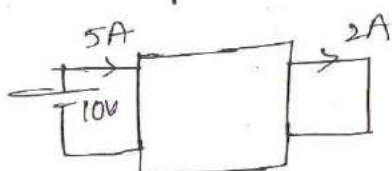This is done by Superposition theorem & Reciprocity theorem. When Given N/w satisfy the Reciprocity find I?



Sol:-

To find out I, load resistor is s.c. so here we are using Norton's & Reciprocity theorems.

case (i):-




$$\frac{I_{sc}}{30} = \frac{2}{10}$$


$$\Rightarrow I_{sc} = 6A$$


case (ii):-

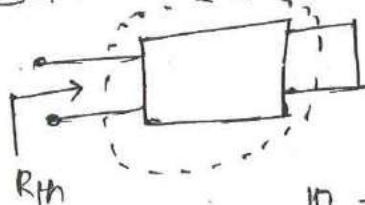When ever physical connections are same $\Rightarrow$ circuit elements are same.



$$R_{th} = \frac{10}{5} = 2 \Omega$$



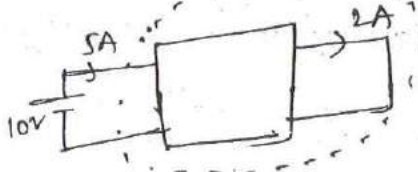


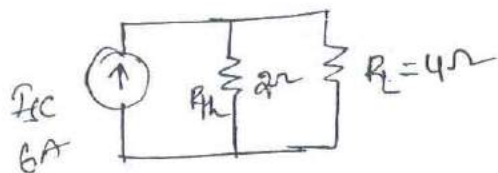

$$\therefore I_{4\Omega} = 6 \times \frac{2}{6} = 2A$$

(Pb) When given N/w satisfy the Reciprocity find the value of I ?

Sol:- case (i):-

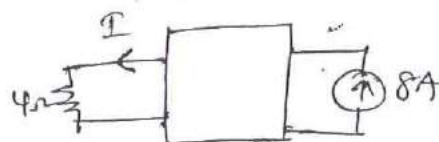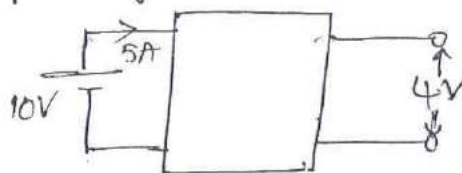
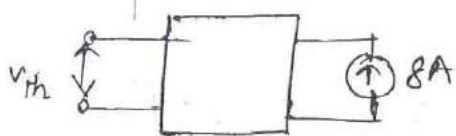


$$\frac{\text{Response}}{\text{Excitation}} = \frac{V_{th}}{8} = \frac{4}{5}$$

case from original N/w the excitation is 10V. Response is 4V. So Reciprocity Theorem not satisfied. The second N/w excitation is 8A. so we are taking 5A as Excitation since in the problem they given Reciprocity Theorem is satisfied.


$$\Rightarrow V_{th} = \frac{32}{5} \text{ volts}$$

case (ii):-

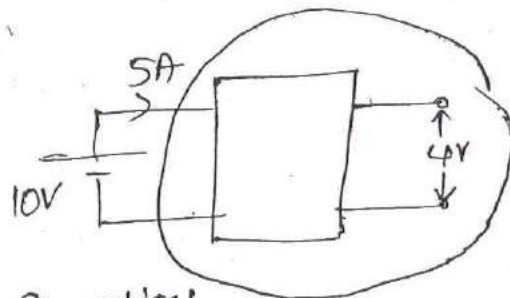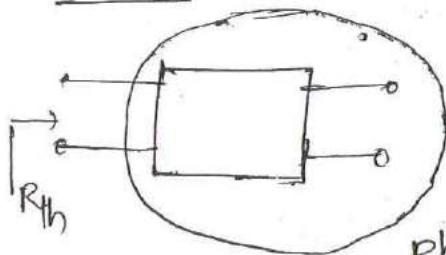

Physical Connections are same.

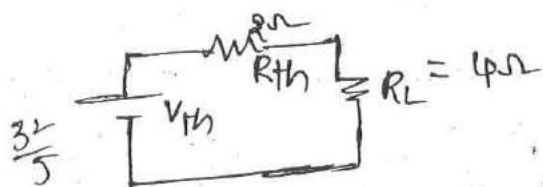
$$\text{so } R_{th} = \frac{10}{5} = 2\Omega \dots$$



$$I_{R_L} = \frac{(32/5)}{6}$$

$$= \frac{32}{30} = \frac{16}{15} A \dots$$

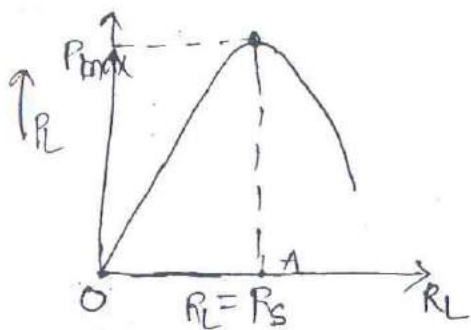Note: Here we are using Reciprocity & Thevenin's Theorem.



corresponds to OA portion $\rightarrow R_S > R_L$

$$\eta < 50\%$$

exactly at $R_S = R_L \rightarrow R_S$

$$\eta = 50\%$$

corresponds to $R_L > R_S$ portion

$$\eta > 50\%$$

Q1:-

$$\eta = \frac{R_L}{R_S + R_L}$$

$$R_S = 10, R_L = 12\Omega$$

$$\Rightarrow \eta = \frac{12}{12+10} \times 100$$


$$= \frac{12}{22} \times 100$$

$$\eta = 54.5\%$$


Note:-

So generally while designing any machine we are choosing R_S as low as possible so that η will be high.

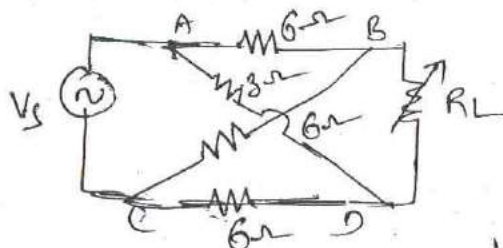(Pb) In the ckt shown at what value of R_L the power delivered from source to load is max.



Sol:-

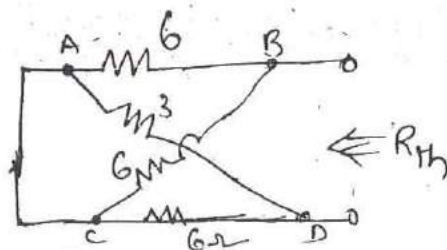


$$= (6 \parallel 3) + (6 \parallel 8)$$

$$= 2 + 3$$

$$= 5\Omega$$

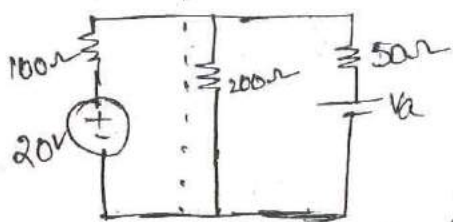(Pb) In the ckt shown at value of V_L power delivered from source to load is max?



$$(a) 7.5V$$


$$(b) 10V$$

$$(c) 15V$$


$$(d) 20V$$

Sol:-

Now that ckt will become as

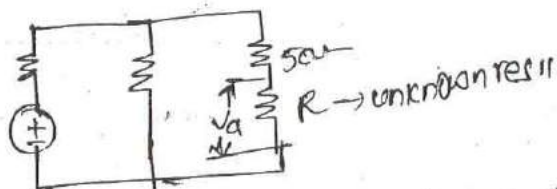
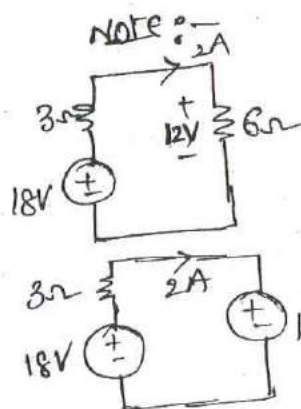
$$P_{load} = \frac{200(50+R)}{200+50+R}$$



So resⁿ is replaced by a voltage source with that resⁿ

$$I = \frac{18-12}{3} = \frac{6}{3} = 2A$$


$(R_{eq})_{load} = R_s = 100\Omega \rightarrow$ for max power transfer.

$$I_T = \frac{20}{R_s + (R_{eq})_{load}}$$


$$I_T = \frac{20}{100+100} = \frac{1}{10} A \dots$$

$$\therefore (R_{eq})_{load} = \frac{200(50+R)}{250+R}$$

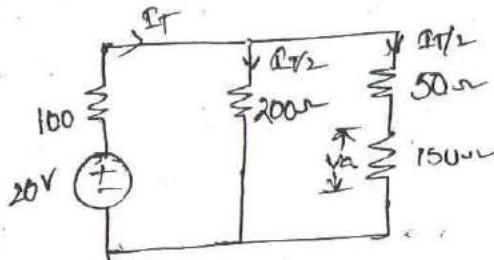
$$100 = \frac{(R+50)200}{250+R} \Rightarrow \boxed{R=150\Omega}$$


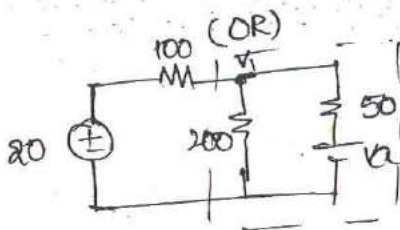
$$V_A = \left(\frac{1}{2 \times 10}\right) \times 150 = \frac{15}{2} = 7.5V \dots$$



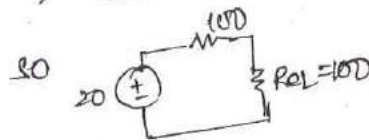for P_{max} ; load R_{eq} must be $\geq 100\Omega$



$$I_{load(200\Omega)} = 0.05A$$

$$I_{(50\Omega+R_A)} = 0.05A$$

$$200 \times 0.05 = 10V$$

$$\text{so } V_1 = 10V$$


$$\frac{V_1 - V_A}{50} = 0.05$$

$$\frac{10 - V_A}{50} = 0.05 \Rightarrow V_A = 7.5$$

(Pb)

IE
Gate
2008

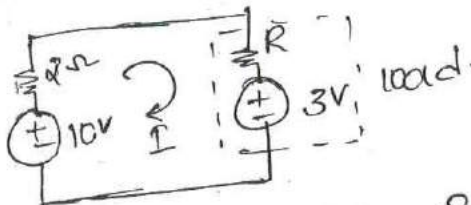In the ckt shown for what value of 'R' Power deliver from source to load is Max?



for max power transfer


$$R_{eq, load} = 2\Omega \dots$$

you have to more concentrate on this.

$$\text{so } I = \frac{10}{2+2} = 2.5A$$

$$-10 + 2(2.5) + R(2.5) + 3 = 0$$
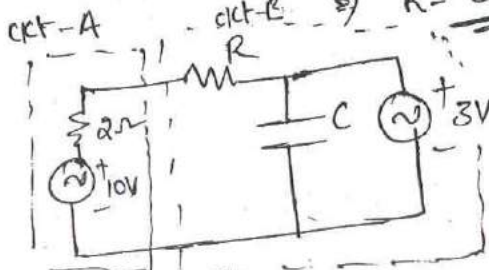
$$\text{ckt-B} \Rightarrow R = 0.8\Omega$$





In the figure shown at what value of 'R' Power delivered from ckt 'A' to ckt 'B' is max?

Gate 2012
EE
2012

(Pb)

Sol:-

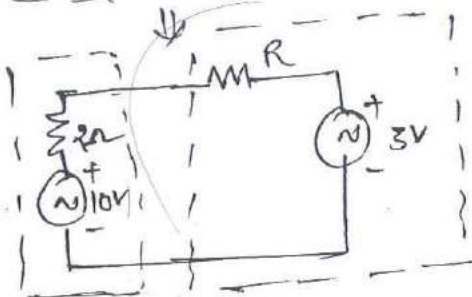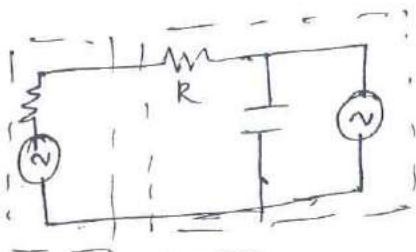


Ans:- $R = 0.8\Omega$...

load $R_{eq} = 2\Omega \Rightarrow I = \frac{10}{4} = 2.5A$

$\Rightarrow -10 + 2(2.5) + R(2.5) + 3 = 0$
 $\Rightarrow R = 0.8\Omega$...

Maximum Power Transfer Theorem :- (AC)

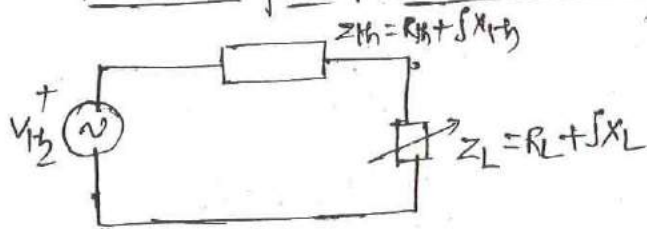

$i = \frac{V_{th}}{(R_L + R_{th}) + j(X_L + X_{th})}$

$I = \frac{V_{th}}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$

$P_L = i^2 R_L$

$= \frac{V_{th}^2 \cdot R_L}{[(R_L + R_{th})^2 + (X_L + X_{th})^2]} \rightarrow (1)$

Case (i) :-

Both R_L & X_L are variable :-

1. Differentiate eqn (1) w.r.to R_L & equated to zero.
2. Differentiate eqn (1) w.r.to X_L & equated to zero.




with result of 1st diffⁿ & 2nd diffⁿ, we obtain a condn

$R_L + jX_L = R_{th} - jX_{th}$

$Z_L = Z_{th}^*$

By substituting this into eqn (1) we get

note:-

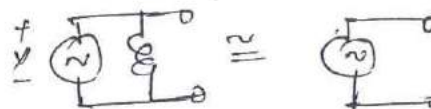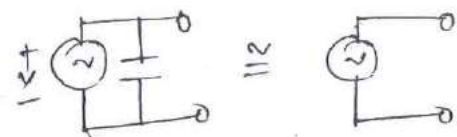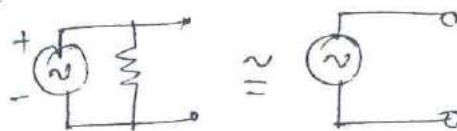

when ever any element is connected across ideal voltage source, the element doesn't produce any effect. so we can eliminate.

while finding load current

$$P_{max} = \frac{V_{th}^2}{4R_L}$$

$$\eta = 50\%$$

case (ii) :-

Only R_L is variable (X_L is constant) :-

* Differentiate eqn (1) w.r. to R_L & equated to zero.

$$R_L = \sqrt{R_{th}^2 + (X_L + X_{th})^2}$$

(or)

$$R_L = Z_{th} + jX_L = R_{th} + j(X_L + X_{th})$$

$$R_L > R_{th}$$

$$\begin{aligned} \eta &= 50\% \\ \eta &> 50\% \\ \eta &< 50\% \end{aligned}$$

let check it?

$$\therefore \eta > 50\%$$

$$R_L = 10 \Omega$$

$$R_{th} = 8 \Omega$$

$$\Rightarrow \eta = \frac{10}{10 + 8}$$

$$= \frac{10}{18} > 50\%$$

valid for both AC & DC.

$$\text{Note: } \eta = \frac{R_L}{R_L + R_s} \times 100$$

Since in efficiency calculation only Active Power is considered. There is no reactive component.

case (iii) :-

load impedance is only Resistive :- ($X_L = 0$)

$$P_L = \frac{V_{th}^2 R_L}{(R_L + R_{th})^2 + X_{th}^2} \rightarrow (2)$$

Differentiate eqn (2) w.r. to R_L & equated to zero.

$$R_L = |Z_{th}|$$

(or)

$$R_L = \sqrt{R_{th}^2 + X_{th}^2}$$

$$\left\{ \begin{aligned} \eta &= 50\% \\ \eta &> 50\% \\ \eta &< 50\% \end{aligned} \right\} \text{ let's check it}$$

so

$$\eta > 50\%$$


Always R_L is greater.

$$R_L = 10$$

$$R_{th} = 8$$

$$\Rightarrow \eta > 50\%$$

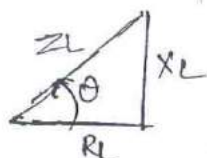Case (iv) :- $Z_L = R_L + jX_L$...
 load impedance angle = $\tan^{-1}(\frac{X_L}{R_L}) = \text{constant}$
 Both R_L & X_L are variable, but load impedance angle is constant.



$$R_L = Z_L \cos \theta$$

$$X_L = Z_L \sin \theta$$


$$P_L = \frac{V_{th}^2 R_L}{(R_L + R_{th})^2 + (X_L + X_{th})^2}$$

$$= \frac{V_{th}^2 Z_L \cos \theta_L}{(Z_L \cos \theta_L + R_{th})^2 + (Z_L \sin \theta_L + X_{th})^2} \quad \text{--- (3)}$$

Here Z_L only variable, $\theta_L = \text{constant}$ already we are discuss.
 Differentiate eqn (3) w.r.t to Z_L & equated to zero.

$Z_L = Z_{th}$

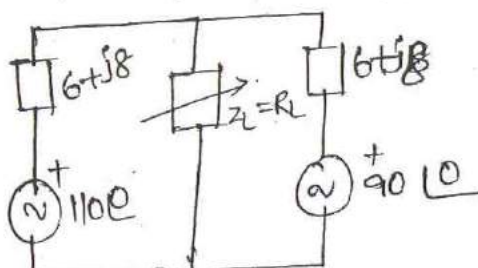
(Pb) Find max power dissipation in the load impedance.



Sol:-

note:-

$R_L = |Z_{th}|$

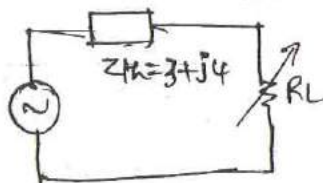

$$R_L = \sqrt{R_{th}^2 + X_{th}^2}$$


$$= \sqrt{9+16}$$

$$= \underline{\underline{5\Omega}}$$

$$Z_{th} = \frac{6+j8}{2}$$

$$= \underline{\underline{3+j4}}$$

Thevenin's circuit:-

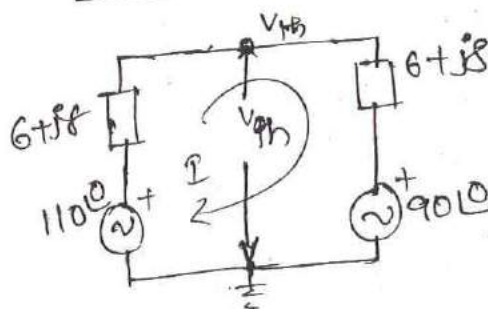

$$\frac{V_{th} - 110}{6+j8} + \frac{V_{th} - 90}{6+j8} = 0$$

$$\Rightarrow \underline{\underline{V_{th} = 100 \angle 0^\circ}}$$

$$Z_{th} = (6+j8) \parallel (6+j8)$$

$$\frac{6+j8}{2} \Leftarrow \frac{(6+j8)(6+j8)}{12+j16+12+j16}$$



$$= \underline{\underline{3+j4}}$$

$$I_1 = \frac{100 \angle 0}{3 + j4 + 5} = \frac{100 \angle 0}{\sqrt{8^2 + 4^2}}$$

$$P_L = (I_1^2) R_L$$

$$= 625 \text{ W} \dots$$

Millman's Theorem :-

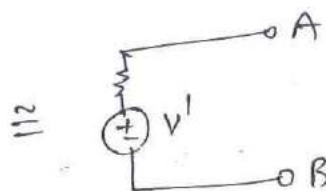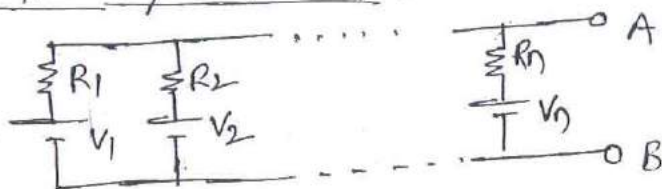

$R' = R_{th}$ → Procedure of R' & R_{th} is same, i.e. all sources are deactivate.

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$


$$\Rightarrow R' = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

$$\Rightarrow R' = \frac{1}{G_1 + G_2 + \dots + G_n}$$

Now

$$V' = I' R'$$

$$V_{OC} = I_{SC} R_{th}$$

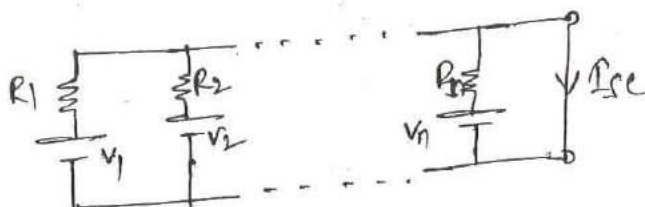



$$I_{SC} = I' = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n}$$

$$I_{SC} = V_1 G_1 + V_2 G_2 + \dots + V_n G_n$$

$$\therefore V' = \frac{\frac{V_1}{R_1} + \frac{V_2}{R_2} + \dots + \frac{V_n}{R_n}}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$

$$V = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

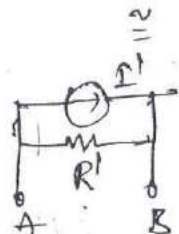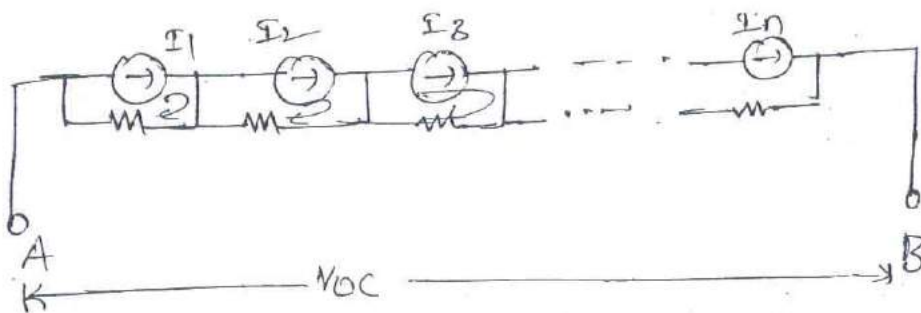that means In millman's theorem also indirectly we are concentrate on thevenin's & Norton's.



$R' = R_{th} \rightarrow$ deactivate all current sources i.e. open all current sources

$$R' = R_1 + R_2 + \dots + R_n$$


$$I' = \frac{V'}{R'}$$

$$I_{sc} = \frac{V_{OC}}{R_{th}}$$


$$V_{OC} = I_1 R_1 + I_2 R_2 + \dots + I_n R_n$$

$$\therefore I' = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + R_3 + \dots + R_n}$$

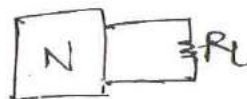(Pb) When a complex N/w of 'N' is connected to load resistor, power diss in the resistor is 'P' watts.



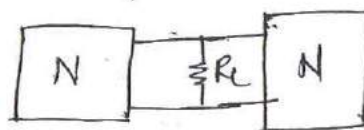
When two identical complex N/w of 'N' are connected to same load resistor find power diss in the load resistor.



- (a) P (b) 2P (c) 4P (d) P (or) 4P


Sol:- Any complex N/w can be write by using Thevenin's (or) Norton's theorem.

Now by using Thevenin's

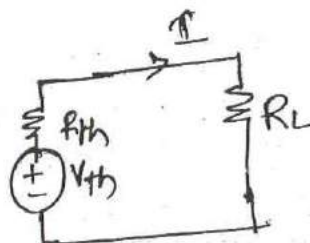


$$I = \frac{V_{th}}{R_{th} + R_L}$$

$$P = I^2 R_L = \left(\frac{V_{th}}{R_{th} + R_L} \right)^2 R_L \rightarrow (1)$$

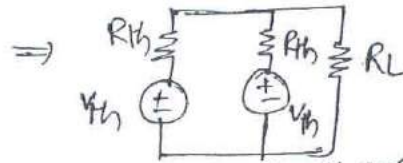

$$V' = \frac{\frac{V_{th}}{R_{th}} + \frac{V_{th}}{R_{th}}}{\frac{1}{R_{th}} + \frac{1}{R_{th}}} \quad \dots = \frac{\frac{V_{th}}{R_{th}} [1+1]}{\frac{1}{R_{th}} [1+1]} = V_{th} \quad \dots$$
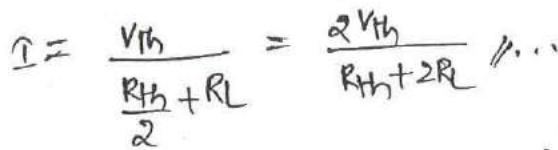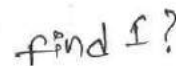
$$R_1 = \frac{1}{\frac{1}{R_{th}} + \frac{1}{R_{th}}} = \frac{R_{th}}{2}$$




$$P = I^2 R = \left(\frac{2 V_{Th}}{R_{Th} + 2R_L} \right)^2 R \rightarrow \textcircled{E}$$

$EV(1) \neq EV(2)$, so option a X
 $2EV(1) \neq EV(2)$, " " b X
 $EV(2) \neq 4EV(1)$, so Ans is (d) ✓



Sol:-

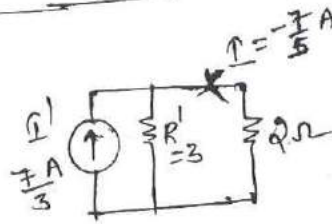

$$① \Rightarrow \left(\frac{-7}{3} \right) \times \frac{3}{3+2}$$

$$I = -\frac{7}{5} \text{ A} //$$

$$\Delta = \frac{(6)(1) - (2)(1) + (3)(1)}{1+1+1}$$

$$= \frac{7}{3} \text{ l.u.}$$

$$R' = R_1 + R_2 + R_3 = 1 + 1 + 1 = 3$$

Tellegen's Theorem :-
Tellegen's Theorem ~~can~~ applied states that algebraic sum of powers in any circuit at any instant is equal to zero.
- Unidirectional, bidirectional, time variant &


(linear, Nonlinear, unidirectional, bidirectional, time variant & time invariant elements).

$$\sum_{k=1}^n V_k i_k = 0$$

Mathematical expression for Tellegen's theorem

$$\sum_{k=1}^n V_k i_k = 0$$

(P6) verify Tellegen's Theorem?

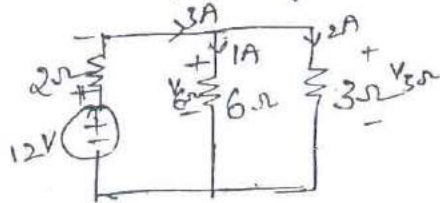

sol:-

$$I_T = \frac{12}{4} = 3A$$

$$I_{6\Omega} = \frac{3 \times 3}{9} = 1A$$

$$I_{3\Omega} = 2A$$

$$P_{\text{deliver}} = 36W$$

$$P_{\text{absorb}} = 36W$$


Hence Tellegen's Theorem is Verified.

$$\begin{aligned} P_{2\Omega} &= (3)^2 \times 2 = 18W \text{ (absorb)} \\ P_{6\Omega} &= (1)^2 \times 6 = 6W \text{ (absorb)} \\ P_{3\Omega} &= (2)^2 \times 3 = 12W \text{ (absorb)} \\ P_{12V} &= (12)(3) = 36W \text{ (deliver)} \end{aligned}$$


NOTE:- For verification of the Tellegen's Theorem KVL & KCL eqns are used.

*NOTE:- Tellegen's Theorem works based on the Principle of Law of Conservation of Energy.

Compensation Theorem:-

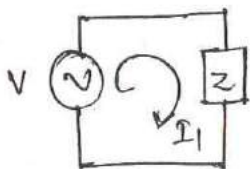

$$I = \frac{V}{Z}$$

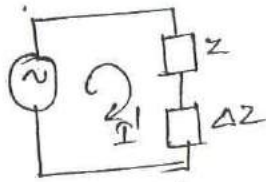

$$I' = \frac{V}{Z + \Delta Z}$$

Change in current $\Rightarrow \Delta I = I - I'$

$\downarrow$ CW $\downarrow$ CW $\downarrow$ CW
 $\leftarrow$ so $\leftarrow$ so $\leftarrow$ so

let $Z = 3 + j4$

(i) $\Delta Z = j2$

$(Z + \Delta Z) \uparrow \Rightarrow I' \downarrow$

(ii) $\Delta Z = -j3$

$\therefore (Z + \Delta Z) \downarrow \Rightarrow I' \uparrow$

where

$$\begin{aligned} I &> I' \\ I &< I' \end{aligned}$$

Let's check.

so I & I' relation depends on change in impedance.


$$\text{so } \Delta I = |I - I'|$$

The compensation emf circulates the current in ACW.

$$\Delta I = \frac{I \Delta Z}{Z + \Delta Z}$$

since actually from I & I' , ΔI CW, but here ACW, so -ve sign is taken.


modified ckt:-

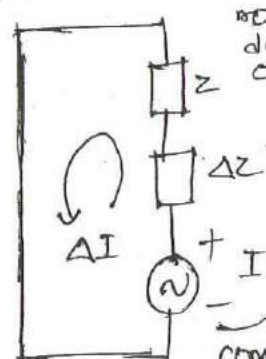

To draw the modified ckt deactivate all original sources

compensation emf (or) opposing emf


17b

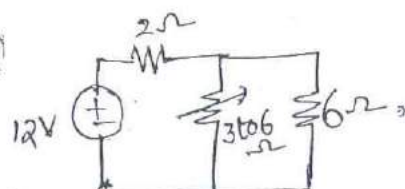

find change in Current in the 2Ω & 6Ω resistor when Resistance in the variable branch is changed from 3 to 6Ω .

Sol:-

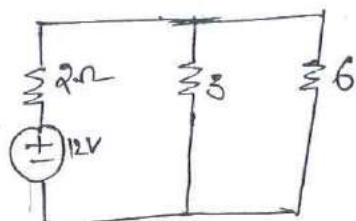
step(1):- find Original Current circulating in the variable branch.



$$I_T = \frac{12}{R_{eq}} = \frac{12}{4} = 3A \dots$$

$$I_{3\Omega} = \frac{3 \times 6}{3+6} = 2A //$$

step(2):- find compensation EMF.

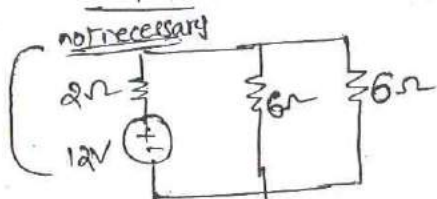


$$I' = \frac{12}{R_{eq}} = \frac{12}{(6||6)+2} = \frac{12}{5} = 2.4A$$

Now compensation emf = $I(\Delta Z) = (2)(6-3) = 6V \dots$

Step(3):- develop modified circuit.

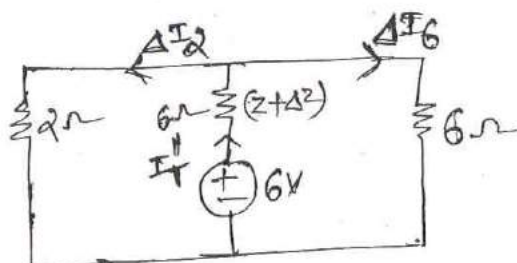While developing modified ckt deactivate all the original sources & connect the compensation emf in series to variable branch.



$$R_{eq} = (6||2) + 6 = \frac{12}{8} + 6$$

$$I_T' = \frac{6}{R_{eq}}$$

$$\Delta I_2 = I_T' \cdot \frac{6}{6+2}$$

$$= \frac{6}{R_{eq}} \times \frac{6}{6+2}$$

$$= \frac{6}{(\frac{12}{8}+6)} \times \frac{6}{8}$$

$$= \frac{36}{12+48} = \frac{36}{60} = \frac{6}{10} = 0.6$$

$$\Delta I_2 = I_T' \cdot \frac{2}{2+6}$$


$$= \frac{6}{(\frac{12}{8}+6)} \cdot \frac{2}{8}$$

$$= 0.2A$$


$$I_T' = 0.8A$$

NOTE:- In the bridge circuits to obtain Null deflection in the Galvanometer Compensation Theorem is used.

Substitution Theorem:-

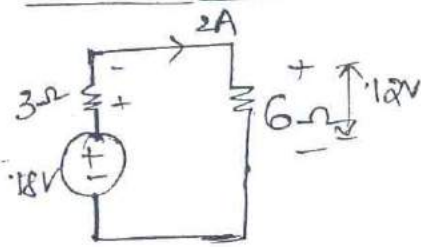


⇒

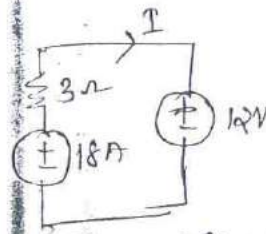


$$I = \frac{18-12}{3} = 2A$$

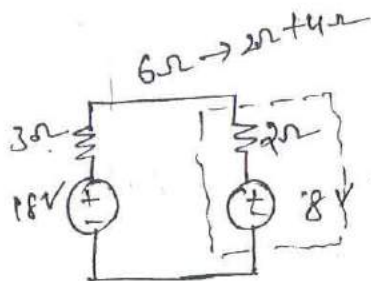6Ω resistor is replaced by eqⁿ voltage (drop) & vice versa.



$$I = \frac{18-8}{6} = 2A$$

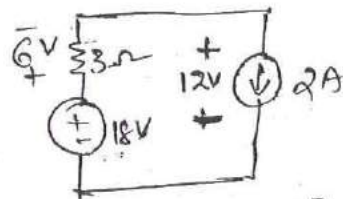


resistance is replaced by eqⁿ current source

Workbook

Page 3

Q:1

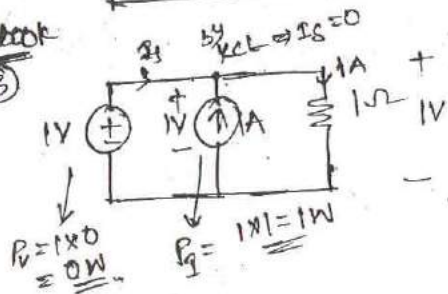

$$P_R = I^2 R = 1^2 \times 1 = 1W$$


Ans: - b

Q:2

$$C_{eq} = \frac{0.1}{2} + \frac{0.1}{2} = 0.1 F$$

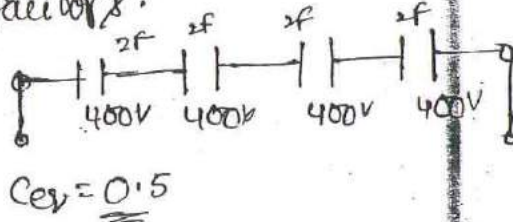Q:3:-

each capacitor rating, 2μF & 400V
for getting 1600V we require 4 series
Capacitors.




$$C_{eq} = 0.5$$

Ans: (a)

12 capacitors required.

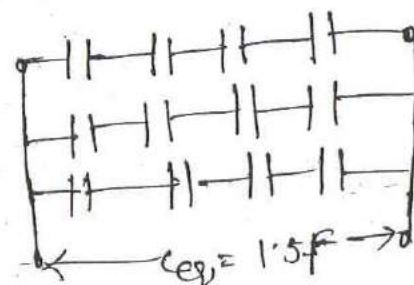for getting 1.5 F we connect
3 parallel connection.



$$C_{eq} = 1.5 F$$


$$V = 1600V$$

Q:4


$$v = 4I - 9$$

$$-2I = 4I - 9$$

$$\Rightarrow I = 1.5 \text{ A}$$

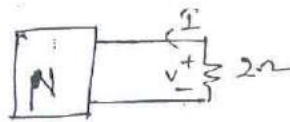


Q:5:-

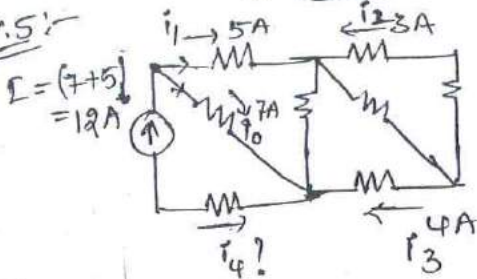

$$i_4 = -1.2 \text{ A}$$


Q:6

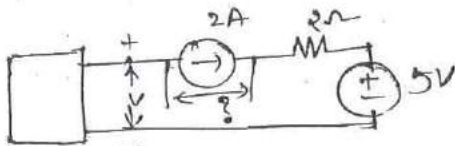

In this ckt voltage across current source is unknown. Hence by it is not possible to find out v .

One eqn, Two unknowns, $\therefore$ not possible.
 v & $v_{\text{current source}}$

Q:7

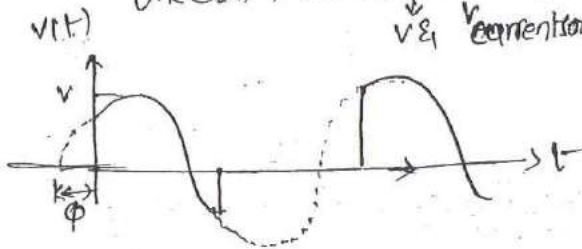

$$\text{sol: } V_{\text{avg}} = \frac{1}{2\pi} \left[\int_0^\pi V_m \sin(\omega t + \phi) d\omega t + \int_\pi^{2\pi} 0 d\omega t \right]$$

$$= \frac{1}{2\pi} V_m \left[\int_0^\pi \sin(\omega t + \phi) d\omega t \right]$$

$$= \frac{V_m \cos \phi}{\pi} \dots$$

Q:8

$$i^2 R = 18 \text{ W} \rightarrow (1)$$

$$\frac{v^2}{R} = 4.5 \rightarrow (2)$$

since $v = I$ $\rightarrow$ given in p.w.m

$$\frac{i^2}{R} = 4.5 \rightarrow (3)$$

from (1) & (3) $\Rightarrow$

$$i^2 R = 18 \text{ W}$$

$$(4.5R)R = 18 \text{ W}$$

$$R^2 = \frac{18}{4.5}$$

$$\Rightarrow R = \sqrt{4} = 2 \Omega$$

$$\therefore i^2 = (4.5)(2)$$

$$= 9$$


$$i = \sqrt{9} = 3 \text{ A}$$

Q:9

$$\frac{P_{dc}}{P_{ac}} = \frac{I_{avg}^2 R}{I_{rms}^2 R}$$

$$= \frac{\left(\frac{2I_m}{\pi} \right)^2}{\left(\frac{I_m}{\sqrt{2}} \right)^2} = 8/\pi^2$$

Q:10

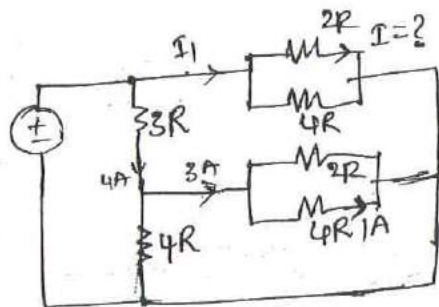

$$I_{2R} = 2 \text{ A}$$

$$I_T = 3 \text{ A}$$

$$I \cdot \left(\frac{4}{\left(\frac{4 \times 2}{4+2} \right) + 4} \right) = 3$$

$$\Rightarrow I = \frac{3 \times 16}{4 \times 8} = 4 \text{ A}$$

$$I \left(\frac{2 \times 4}{2+4} \right) = 4$$

$$\left(\frac{8}{6} \right) + 9$$

$$I = \frac{(4) \left(\frac{8+18}{6} \right)}{\left(\frac{8}{6} \right)}$$

$$= \frac{4(26)12}{8 \cancel{6}}$$

$$I = 13A$$

$$P_1 = (13A) \times 4$$

$$I_1 = 13 - 4 = 9A$$

$$\therefore P_{2R} = 9 - 1 = 8A \dots$$


Q:112

$$I = \sqrt{(12)^2 + (16)^2}$$

$$= \sqrt{144 + 256}$$

$$= 20A$$


Q:113

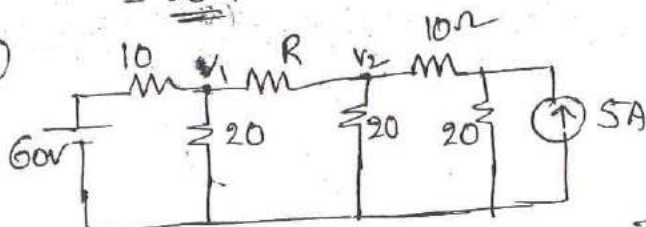

sol:-

$$V_1 = 40 \text{ when } R = 10 \Omega$$
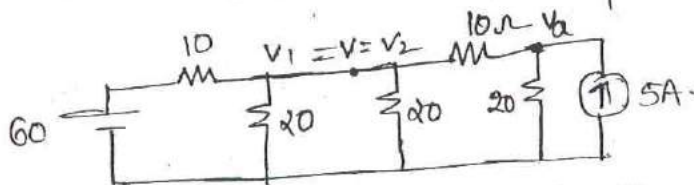
$$\text{when } R = 0 \Rightarrow V_2 = ?$$




$$\frac{V-60}{10} + \frac{V}{20} + \frac{V}{20} + \frac{V-V_a}{10} = 0$$

$$\frac{V_a}{20} + \frac{V_a - V}{10} = 5$$

$$\frac{V_a}{20} + \frac{V_a}{10} - \frac{V}{10} = 5$$

$$\frac{V_a}{10} = 5$$

$$V_a = 50V$$

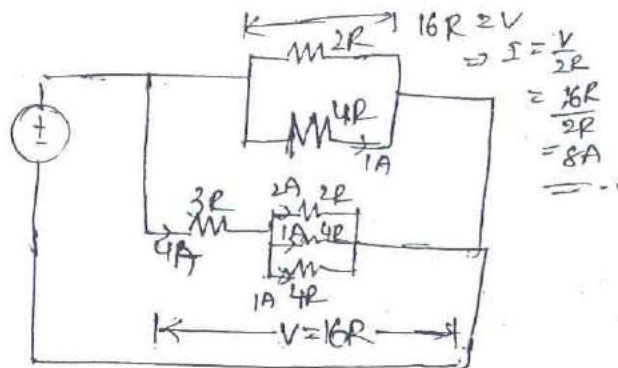

Q:111

sol:-

$$R = 10 \Omega; |X_L| = 20 \Omega, |X_C| = 20 \Omega$$

$$V_{rms} = 200V$$


$$Z = R + j(X_L - X_C) = R + j(20 - 20) = R$$


$$Z = R = 10 \Omega$$

$$I = \frac{V}{Z} = \frac{V}{R} = \frac{200}{10} = 20A$$

$$V_C = -jX_C$$

$$= (20)(20) \angle -90^\circ$$

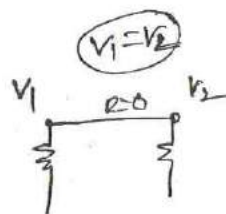

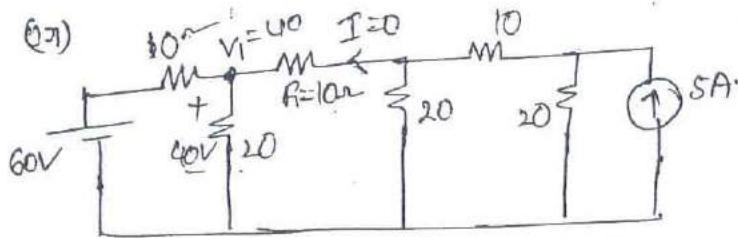

for first loop:- $-60 + 10I + 40 = 0$


$\Rightarrow I = 2A$

so $R = 10\Omega$ (or) 0Ω (or) 100Ω any value, $I = 0$.

so $V = 40V$...

Q: 14)

sol:-

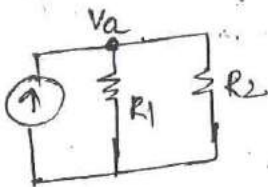

$I = \frac{V_a}{R_1} + \frac{V_a}{R_2}$


$I = \frac{2V_a}{2R_1} + \frac{2V_a}{2R_2}$ should be double.

Q: 16)

$i_L = e^{at} + e^{bt}$

$v = L \frac{di_L}{dt} \Rightarrow v = a e^{at} + b e^{bt}$

Q: 17)

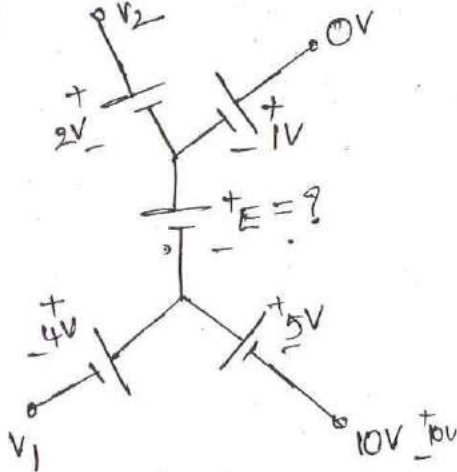

find $E = ?$

sol:-


$-v_1 - 4 + 5 + 10 = 0$

$\Rightarrow v_1 = 11V$

$0 + 1 + E + 5 + 10 = 0$

$E = -16V$

Q: 18)

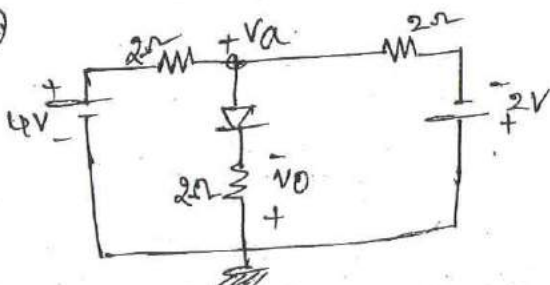


$v_o = ?$

sol:-

$\frac{v_a - 4}{2} + \frac{v_a}{2} + \frac{v_a + 2}{2} = 0 \Rightarrow v_a = \frac{2}{3}$


$\therefore v_o = -v_a = -\frac{2}{3}$

Q: 19

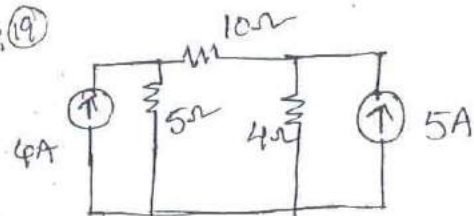

Find P_{dk} in 5Ω ?


Sol:-

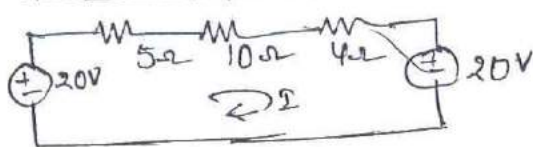

$$I = \frac{+20 - 20}{4 + 10 + 5} = 0 \text{ A} \dots$$

from this we can say $I_{5\Omega} = 0$
 $\Rightarrow P = 0$

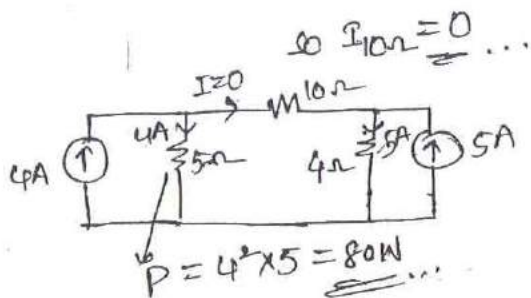But this analysis is wrong.
 Source Transformation theorem is obtained only for R_L , not for R_{int} .



$$P = 4^2 \times 5 = 80 \text{ W} \dots$$

By using source transformation response is obtained in the load resistor, but not in the internal resistor.

Q: 20

Sol:-

$$\begin{aligned} -24 + 1i - 2V_b + 3i + 4i &= 0 \\ -24 + 1i - 2(3i) + 3i + 4i &= 0 \Rightarrow i = 4 \text{ A} \dots \end{aligned}$$

$$\Rightarrow V_b = 12 \text{ V}$$

Q: 21

Sol:-

$$V_{6\Omega} = 50 \times \frac{6}{13} ; V_{7\Omega} = 50 \times \frac{7}{13}$$

$$\therefore V_R = \frac{50 \times 7}{13} \quad \therefore 4 \text{ A} = \frac{12.5 \times 50 \times 7/13}{R} \Rightarrow R = 3.5 \Omega$$

Q: 22

When impedances of equal values transformed from Δ to Y , impedance decreased by 3 times.

Q: 23


Ans: d

Q: 24

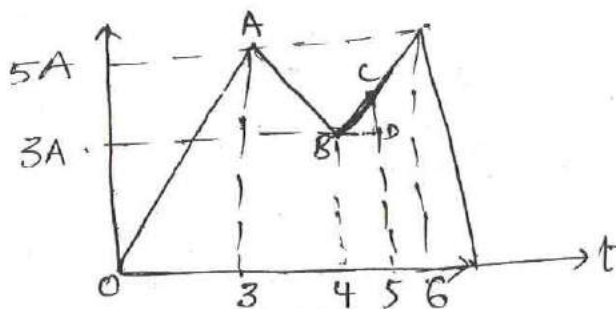Q: 25

$$\frac{dq}{dt} = i$$

$$\Rightarrow q = \int_0^{5\mu s} i \, dt$$



$$0 \text{ to } 3\mu s :- \frac{1}{2} ab = \frac{1}{2} (3) (5) = 7.5 \mu C$$

$$3 \text{ to } 4\mu s :- \text{shape is trapezoidal, so}$$

$$= \frac{1}{2} (5 + 3) \times 1 = 4 \mu C$$


$$4 \text{ to } 6\mu s :-$$

$$= \frac{1}{2} (1 \times 1) + (1 \times 3)$$


$$= 0.5 + 3 = 3.5 \dots$$

$$\begin{aligned} \text{Total charge:} \\ 7.5 + 4 + 3.5 \\ = 15 \mu C \dots \end{aligned}$$


Q: 26

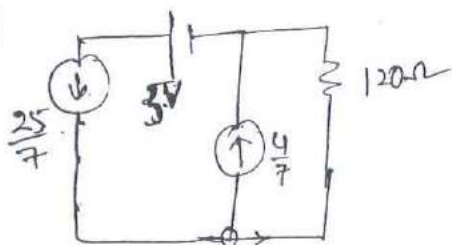
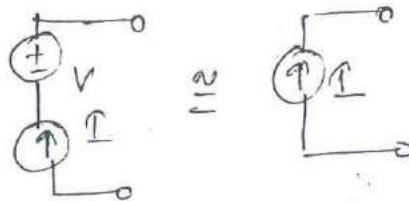
$$\frac{25}{7} - \frac{4}{7} = \frac{21}{7} = 3A$$



Q: 28

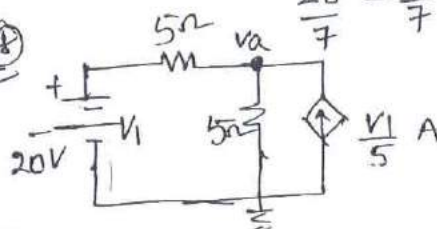

$$P = V_a \times \left(\frac{V_1}{5}\right) = 20 \times 4 = 80W \text{ delivered}$$


Sol:-

$$\frac{V_a - 20}{5} + \frac{V_a}{5} = \frac{V_1}{5}$$

Since $V_1 = 20$ $\Rightarrow V_a = 20V$

$$\frac{V_1}{5} = 4$$

Q: 29

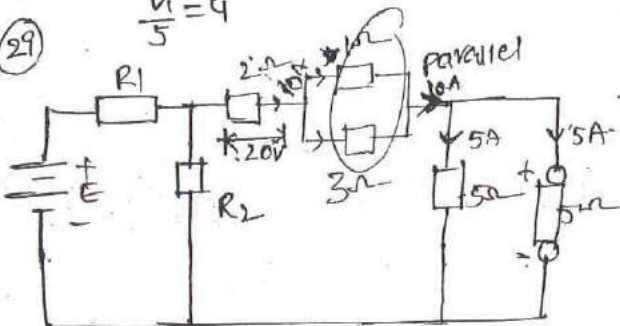

Sol:-


$$V_{20V} = 20V$$

$$V_x \cdot \frac{9}{9+2} = 20V$$

$$\Rightarrow V_x = \frac{20 \cdot 11}{9} = V_{R2}$$


Now $V_{9\Omega} = \frac{20 \cdot 11}{9} \cdot (9)$

Q: 30

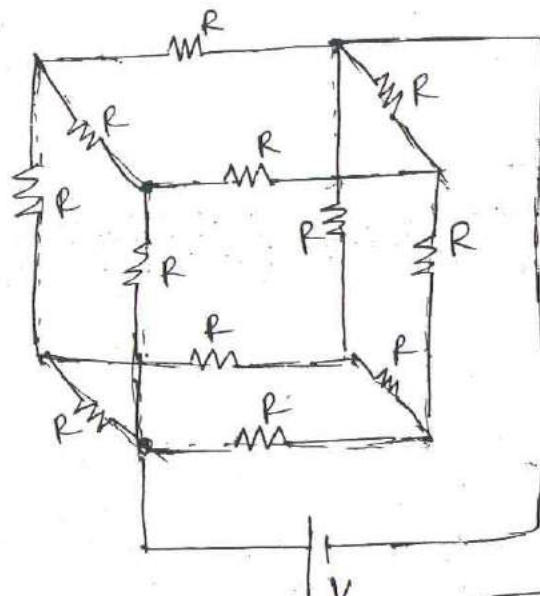



$$R_{eq} = \frac{5}{6} R \quad L_{eq} = \frac{5}{6} L \quad C_{eq} = \frac{6}{5} C$$

Q: 32

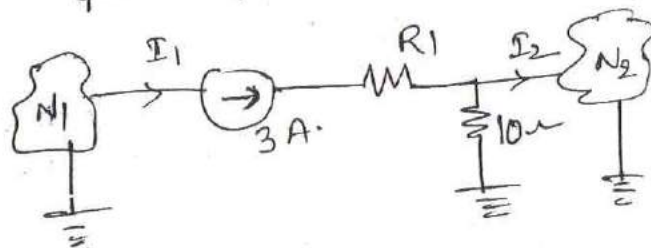

for any value of R $I_2 = 2A$


Q: 33

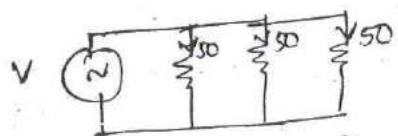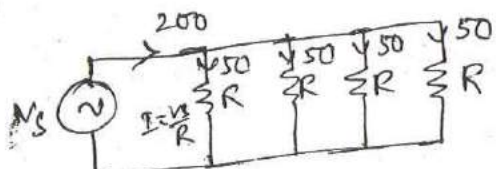

$I_{branch} = \text{remains unaffected}$

Why don't we current source here?
reason:- our system source is voltage source not current source. so always we are taking voltage source. * current source is taken if will change

Q: 34

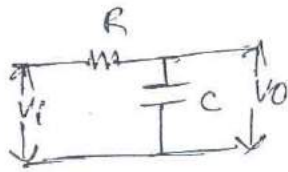

sol:

$$V_i(t) = \sqrt{2} \sin 1000t$$

$$RC = 1 \text{ ms}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{1}{RCs+1}$$

$$= \frac{1}{(1 \times 10^{-3})s + 1}$$

$$V_o(s) = V_i(s) \cdot \frac{1}{10^{-3}s + 1}$$

$$= V_i(s) \cdot \frac{1}{10^{-3}j(1000) + 1}$$


$$= V_i(s) \cdot \frac{1}{1+j1}$$

$$= V_i(s) \cdot \frac{1}{\sqrt{2}} \angle -45^\circ$$

$$V_o(t) = \frac{1}{\sqrt{2}} \sin(1000t - 45^\circ)$$

$$= \sin(1000t - 45^\circ)$$

Q: 35

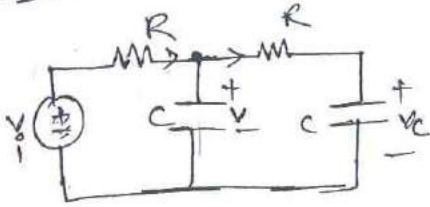


$$V_i = V + V_R \rightarrow (1)$$

$$V = V_R + V_C \rightarrow (2)$$

$$V = iR + V_C$$

$$V = RC \cdot \frac{dV_C}{dt} + V_C$$

Q: 36


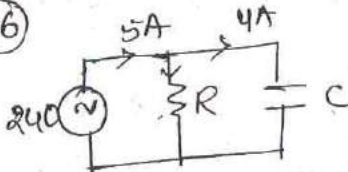


$$5 = \sqrt{I_R^2 + I_C^2}$$

$$I_R = 3A$$


$$\therefore I_R = \frac{240}{R} \Rightarrow R = \frac{240}{3} = 80 \Omega$$

Q: 40

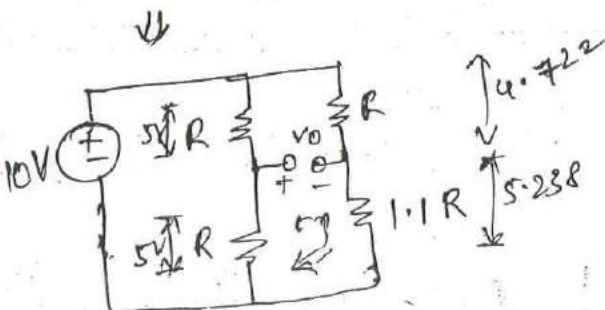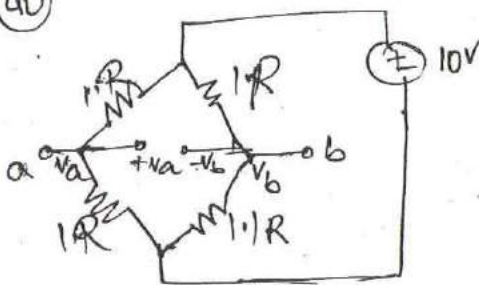

Q: 37

bridge balance when $R_L = 2\Omega$

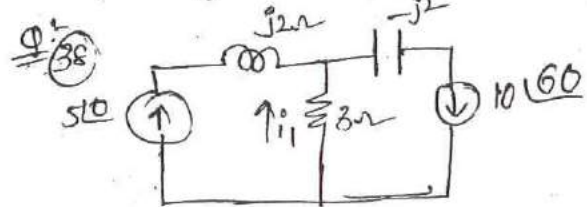

$$I_1 + 50 = 10/60$$

$$\Rightarrow I_1 = 10/60 - 50$$


$$= 10 \angle 90^\circ + j0 \sin 60^\circ - 50$$

$$= \frac{10\sqrt{3}}{2} \angle 90^\circ$$

$$-5 + V_o + 5 \cdot 238 = 0$$


$$\Rightarrow V_o = -0.238 \text{ V}$$

Q 41

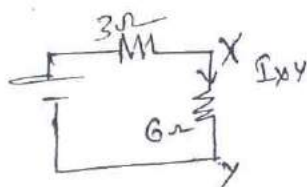

$$I_{xy} = \frac{18}{6+3} = 2A$$

$$V_{xy} = 6 \times 2 = 12V$$

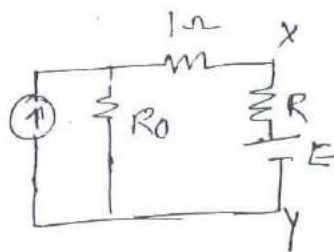

$$V_{xy} = RI_{xy} + E$$

$$12 = 2R + E$$

① $E = 2V, R = 5\Omega$
satisfies the condition

② $E = 4V, R = 4\Omega$

③ $E = 6V, R = 3\Omega$

④ $E = 10V, R = 1\Omega$

Ans: (C)

Q 42



$$e_1(t) = \sqrt{3} \cos(\omega t + 30^\circ)$$

$$e_2(t) = \sqrt{3} \sin(\omega t + 60^\circ)$$

Sol:-

$$e_1(t) = \sqrt{3} \cos(\omega t + 30^\circ)$$

$$e_2(t) = \sqrt{3} \cos(\omega t + 60^\circ - 90^\circ)$$

$$\frac{v_1 - e_1(t)}{1} + \frac{v_1 - e_2(t)}{1} + \frac{v_1}{1} = 0$$

$$\Rightarrow v_1 = \frac{e_1 + e_2}{3} = \frac{\sqrt{3}}{3} [\cos(\omega t + 30^\circ) + \cos(\omega t - 30^\circ)]$$


$$= \frac{1}{\sqrt{3}} \left[\cos \omega t \cdot \left(\frac{\sqrt{3}}{2}\right) + \sin \omega t \cdot \left(\frac{1}{2}\right) + \cos \omega t \cdot \left(\frac{\sqrt{3}}{2}\right) + \sin \omega t \cdot \left(\frac{1}{2}\right) \right]$$

$$= \frac{1}{\sqrt{3}} \left[\frac{\sqrt{3}}{2} \cos \omega t \right] = \cos \omega t \text{ volts}$$

Q 43

By using Superposition theorem

Q: (44)

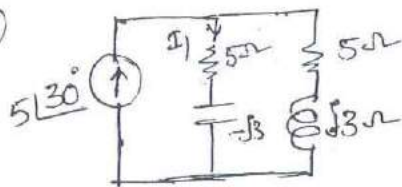


Sol:-

$$I_1 = 5\angle 30^\circ \left[\frac{(5+j3)}{5-j3+5+j3} \right]$$

$$= \frac{1}{2} 130 \left[\frac{5+j3}{5} \right]$$

$$= \frac{1}{2} 130 \left[\frac{1}{2} \right] \left[\frac{1}{2} + j\frac{3}{2} \right] (5+j3)$$

Q: (45)

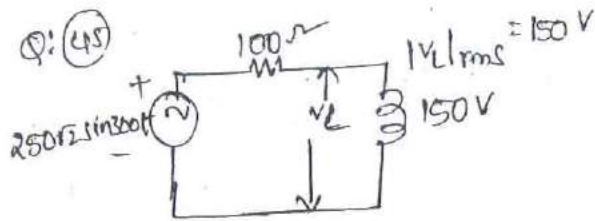

Sol:-

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\frac{250}{\sqrt{2}} = \sqrt{V_R^2 + (150)^2}$$

$$V_R = 200V$$


$$I = \frac{V_R}{R} = \frac{200}{100} = 2A$$

$$V_L = I X_L \Rightarrow 150 = 2(\omega L)$$


$$150 = 2(300L)$$

$$L = \frac{1}{6} = 0.167 H$$

Q: (46)

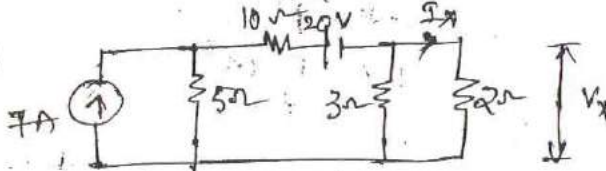

Q: (47)

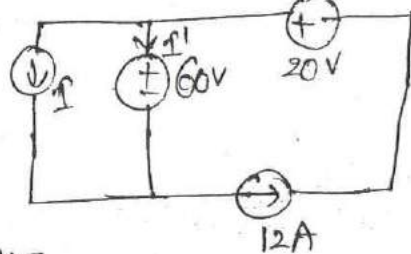


Sol:-

$$I + I' = 12$$

$$I = 12 - I'$$

Q: (48)

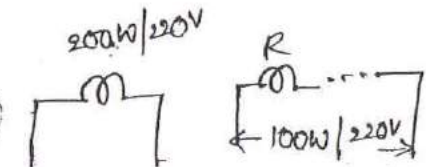

$$R = \frac{V^2}{P}$$

$$R = \frac{(220)^2}{200}$$


$$= 242 \Omega$$

$$R_{eq} = \frac{V_{eq}^2}{P_{eq}}$$


$$= \frac{(220)^2}{100}$$

$$= 484 \Omega$$

Q: (49)

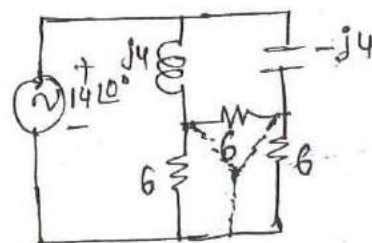

Sol:-

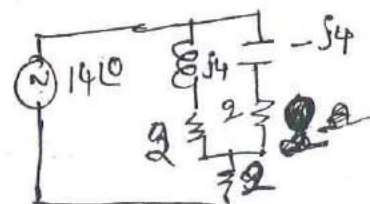


$$I = ?$$

$$Z_{eq} = 2 + \frac{(2+j4)(2-j4)}{(2+j4) + (2-j4)}$$

$$Z_{eq} = 7\Omega$$

$$I = \frac{14\angle 0}{7\angle 0} = 2\angle 0 \text{ A}$$

Q.51

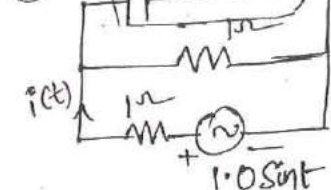

Sol:-


$$\begin{aligned} Z_1 &= j(X_L - X_C) \\ &= j(\omega L - \frac{1}{\omega C}) \\ &= j(1 - 1) \\ &= 0 \end{aligned}$$

i.e. short


$$i = \frac{V}{R_{eq}} = \frac{1}{\sqrt{2}} \text{ A}$$

$$= \frac{1}{\sqrt{2}}$$

Q.53

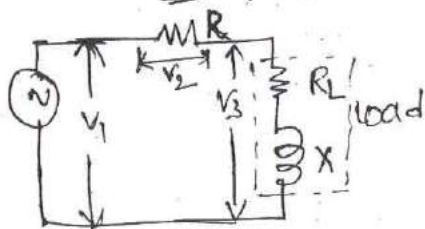

Sol:-

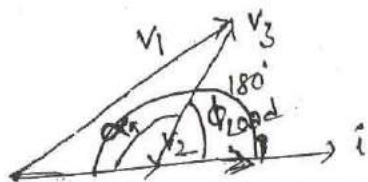

$$V_1 = \sqrt{V_2^2 + V_3^2 + 2V_2V_3 \cos \alpha}$$


$$220 = \sqrt{122^2 + 136^2 + 2(122)(136) \cos \alpha}$$

$$\alpha = 116.91^\circ$$

$$\phi_{load} = 180 - 116.91 = 63.08^\circ$$


$$\cos(63.08) = 0.45$$

Prob 5

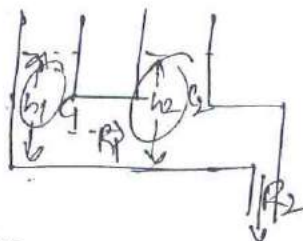


Ans:- (d)

Sol:-

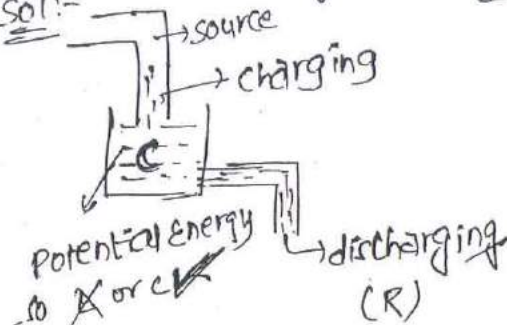

Q.52

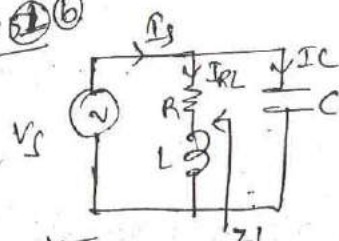

Sol:-

$$Z_1 = (R + j\omega L)$$

$$Z_1 = \frac{V_S}{I_{RL}} = \frac{10}{\sqrt{2} \angle -\pi/4}$$

$$= \frac{1}{\sqrt{2}} \angle \pi/4$$

$$= \frac{1}{\sqrt{2}} \left[\frac{1}{\sqrt{2}} + j\frac{1}{\sqrt{2}} \right]$$

$$= \frac{1}{2} + j\frac{1}{2} = R + jX_L$$

$$R = \frac{1}{2} \Omega \quad X_L = \frac{1}{2} \Omega$$


$$I_{RL} = \sqrt{2} \angle -\pi/4$$

$$\therefore P = I_{RL}^2 \cdot R = (\sqrt{2})^2 \cdot \frac{1}{2} = 1 \text{ W}$$



$V_{3\phi L} = V_3 \cos \phi_L + j V_3 \sin \phi_L$

Active compn $\rightarrow R_L$

Reactive component $\rightarrow jX_L$

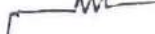
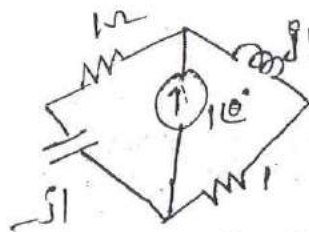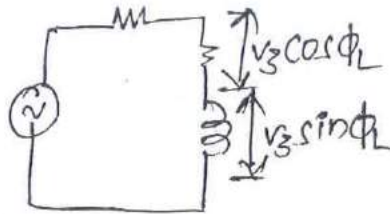
$$\begin{aligned} \text{Power} &= \frac{\left(\frac{V_3 \cos \phi_L}{5}\right)^2}{R_L} \\ &= \frac{\left[\frac{136 \times \cos(63.04^\circ)}{5}\right]^2}{5} \\ &= \frac{(136 \times 0.47)^2}{5} = 750 \text{ W} \end{aligned}$$



$$I_L = \frac{(10)(1-j1)}{(1+j1)(1-j1)}$$

$$\mathcal{I}_L = \frac{1-j}{1+j} = \frac{1-j}{2} //$$


$$= \frac{(1+j1)(1-j1)}{2(1+j1)}$$

$$= \frac{2}{x(1+j1)}$$

$$\underline{\underline{I_L = \left(\frac{1}{1+j1} \right) A}}$$

Current is same in entering = leaving
so voltage sources O.C.
(or) bridge balance. so diagonal
elements are O.C....

Q:1:-

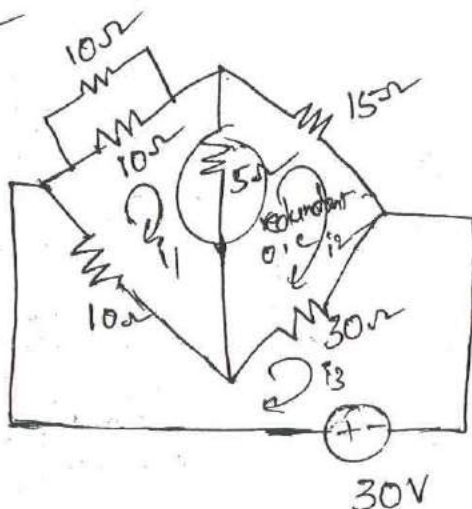


Sol:- $z_1 z_4 = z_2 z_3$

so 52 branch redundant.

$$\underline{\underline{I_{5R} = 0}} \dots$$

for conventional plbm we go for mesh-Analysis for obtaining i_{R_2} .

Q.2

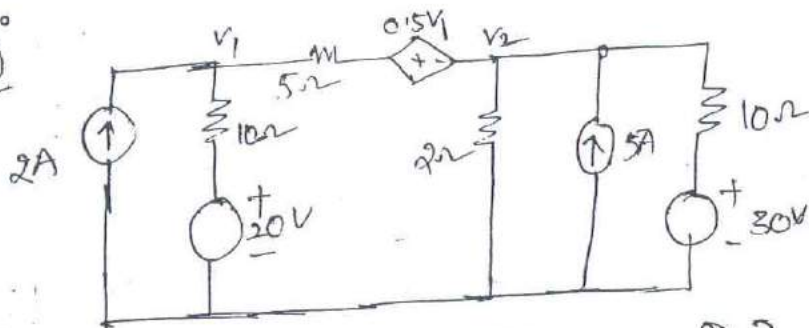

Sol:-


$$\frac{V_1 - 20}{10} + \frac{V_1 - V_2 - 0.5V_1}{5} = 2 \rightarrow (1) \quad \left. \begin{array}{l} \text{from (1) \& (2)} \\ V_1 = \\ V_2 = \end{array} \right\}$$

$$\frac{V_2 - V_1 + 0.5V_1 + \frac{V_2}{2}}{5} + \frac{V_2 - 30}{10} = 5 \rightarrow (2)$$

Page No: 24

Q.1

Sol:-

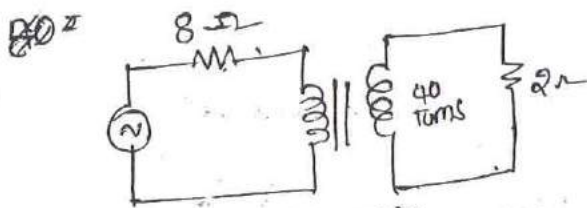

$R_1 = R_2 / k^2$

$$8 = (2) \left(\frac{N_1}{N_2} \right)^2$$

$$4 = \left(\frac{N_1}{40} \right)^2 \quad (00)$$

$$N_1^2 = (40)^2 \cdot 4$$

$N_1 = 80$

$$I_1^2 R_1' = I_2^2 \cdot R$$


$$R_1' = \left(\frac{I_2}{I_1} \right)^2 \cdot R$$

$$R_1' = \left(\frac{N_1}{N_2} \right)^2 \cdot R$$

$$8 = \left(\frac{N_1}{40} \right)^2 \cdot (2)$$

$$\Rightarrow N_1 = 80$$



Q.2:-

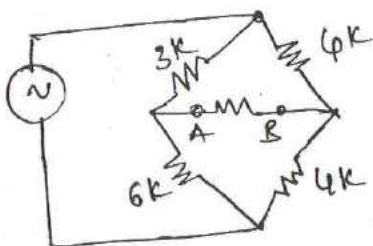

$$R_{th} = (3 \parallel 6) + (4 \parallel 4)$$

$$= \frac{3 \times 6}{3+6} + 2$$

$$= 4 \Omega \dots$$

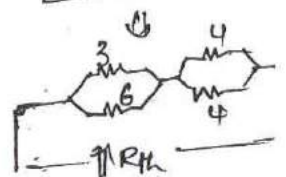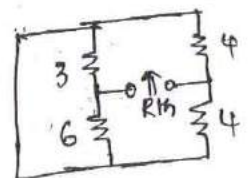

Q.3

1st statement $\rightarrow$ valid
2nd " $\rightarrow$ valid } but both are independent statements

Ans: (B)

Q.4

Req in both cases is same since 'I' same. so


$$\left[\frac{1}{32R} + \frac{1}{16R} + \frac{1}{8R} \right] = \left[\frac{1}{4R} + \frac{1}{2R} + \frac{1}{R} \right] + R_0$$

$$\Rightarrow R_0 = 4R$$


Q5

By using S.P.T:-

Case (i)

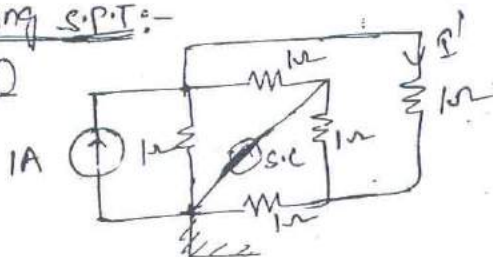


$$\Rightarrow I = 0$$

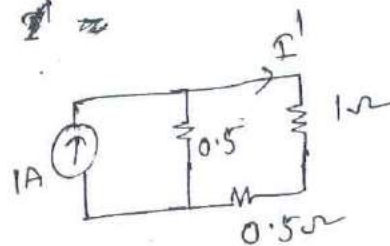

$$I' = 1 \times \frac{0.5}{0.5 + 0.5} = 0.25 \dots$$


Case (ii):-

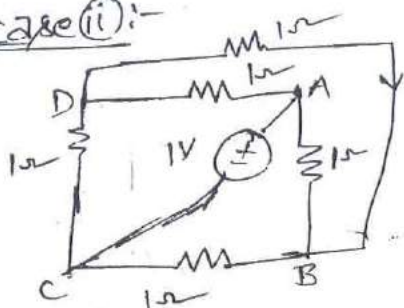

Since bridge balance.

$$\therefore I = I' + I'' = 0 + 0.25 = 0.25 A \dots$$

Q6:-

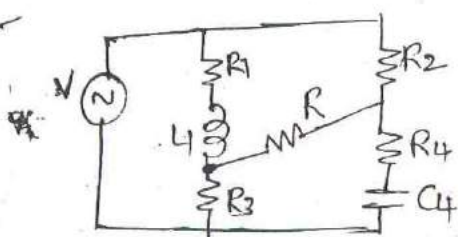

given $I_R = 0$

so bridge is balanced.

$$(R_1 + j\omega L_1) (R_4 - \frac{j}{\omega C_4}) = R_2 R_3$$

$$\Rightarrow j\omega L_1 R_4 - \frac{j R_1}{\omega C_4} \text{ is the imaginary part.}$$


so compare both sides imaginary parts

$$\Rightarrow \omega L_1 R_4 - \frac{R_1}{\omega C_4} = 0$$

$$\omega L_1 R_4 = \frac{R_1}{\omega C_4}$$

$$\Rightarrow \frac{\omega L_1}{R_1} = \frac{1}{R_4 \omega C_4}$$

Q7

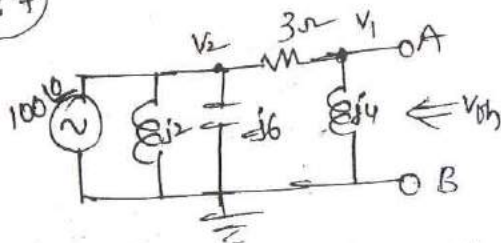

$$\frac{V_1 - V_2}{3} + \frac{V_1}{j4} = 0 \dots$$

$$\frac{100 \angle 0}{j2} + \frac{100 \angle 0}{(-j6)} + \frac{100 \angle 0}{3} - \frac{V_{th}}{j4} = 0$$

$$\Rightarrow V_{th} = \dots$$

By voltage divider rule.

$$V_{th} = 100 \angle 0 \cdot \frac{(j4)}{3 + j4} = 916 (3 - j4)$$


Q.8) $P = (\pm \sqrt{P_1} \pm \sqrt{P_2} \pm \sqrt{P_3})^2$
 $P_{max} = (\sqrt{18} + \sqrt{50} + \sqrt{98})^2$
 $= 450W$

for min power
 you have to
 take like
 +ve. subtract
 from max
 power.



$P_{min} = (\sqrt{98} - \sqrt{50} - \sqrt{18})^2$
 $= 2W$

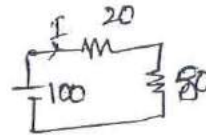Q.9) $V_{OC} = 100V$
 $I_{SC} = 5A$
 $R_L = 80\Omega$


$\frac{V_{OC}}{I_{SC}} = R_{Th} = \frac{100}{5} = 20\Omega$



$\frac{100}{80+20} = 1.00A$

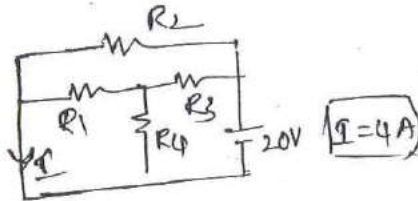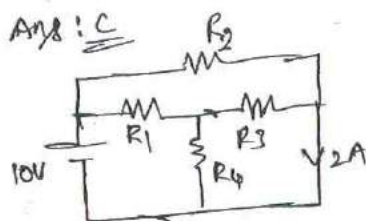

Q.12) Ans: C

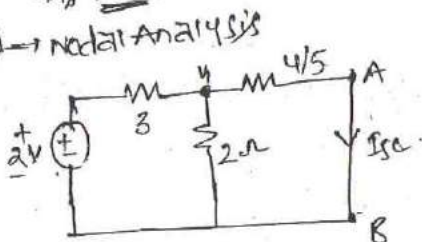

$\frac{V-2}{3} + \frac{V_1}{2} + \frac{V_1}{4/5} = 0$

$\Rightarrow \frac{V_1}{3} - \frac{2}{3} + \frac{V_1}{2} + \frac{5V_1}{4} = 0$

$\Rightarrow V_1 = \dots$

$\frac{V_1}{4/5} = I_{SC} = \dots$


$R_{eq} = \frac{4}{5} + (2||3)$

$I_{SC} = (I)$

$\therefore I_{SC} = \frac{(2)(2)}{5} / 4/5$
 $= 1A \dots$

$V_{Th} = \frac{(2)(2)}{5}$


Ans (d)

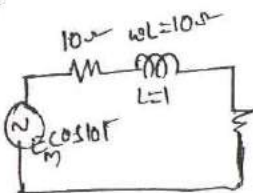

$R_L = |Z_{Th}| = \sqrt{10^2 + 1^2} = 14.14\Omega$

Q.17) Sol: $P_{max} = \frac{(12)^2}{4 \times 2} = \frac{3 \times 12 \times 12}{4 \times 2} = 18W$


Q.20) $\frac{V_{OC}}{I_{SC}} = ?$

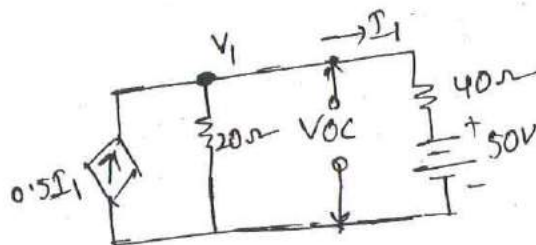

$\frac{V_1 - 50}{40} + \frac{V_1}{20} = 0.5I_1$

but $I_1 = \frac{V_1 - 50}{40}$

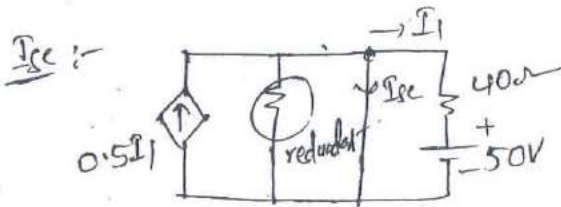Q.18) (b)
 Q.19) $V = \frac{(10)(\frac{1}{6}) + (10)(\frac{1}{4})}{\frac{1}{6} + \frac{1}{4}}$
 $= 7V$
 $R' = \frac{1}{\frac{1}{6} + \frac{1}{4}} = 2.4\Omega$
 $\Rightarrow (0.5 \frac{V_1 - 50}{40}) + \frac{V_1}{20} = 0.5(\frac{V_1 - 50}{40})$
 $(\frac{V_1 - 50}{40}) 0.5 + \frac{V_1}{20} = 0$
 $\Rightarrow V_1 = \dots = V_{OC}$




$$0.5I_1 = I_{sc} + I_1$$

$$\Rightarrow I_{sc} = -I_1$$

$$I_1 = \frac{50}{40} = 1.25A \Rightarrow I_{sc} = -1.25A$$


$$\frac{V_{OC}}{I_{sc}} = R_{th}$$

(or)

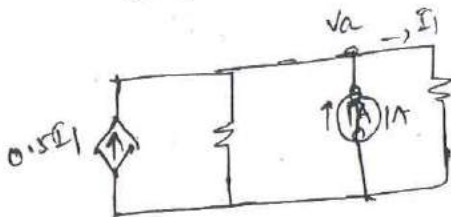

Q.21
Q.22

Ans: - C

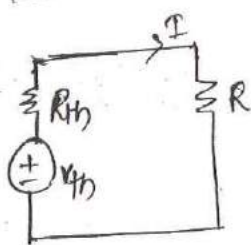

$$I = \frac{V_{th}}{R_{th} + R} \rightarrow (1)$$

from given data

$$R=0 \Rightarrow I = \frac{V_{th}}{0 + R_{th}} \rightarrow (1)$$


$$R=2 \Rightarrow I = \frac{V_{th}}{1 + R_{th}} = 1.5 \rightarrow (2)$$

from (1) & (2)

$$V_{th} = 6V; R_{th} = 2\Omega$$

$$I = \frac{V_{th}}{R_{th} + 1} = \frac{6}{3} = 2A$$

Q.23

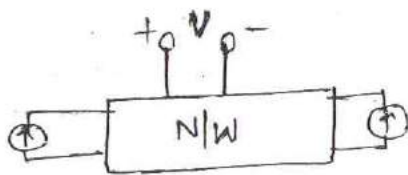

Case (i)

$$I_1 = -8, I_2 = 4$$

$$V = 0$$

$$-8K_1 + 4K_2 = 0 \rightarrow (1)$$

from (1) & (2)

$$K_1 = 2.5, K_2 = 5$$

Case (ii) $I_1 = 8, I_2 = 12$

$$V = 80$$

$$8K_1 + 12K_2 = 80 \rightarrow (2)$$

$$I_1 = I_2 = 10$$

$$V = ?$$


$$10K_1 + 10K_2 = V$$

$$\Rightarrow V = 75V$$

Q.24 C

Q.25 C

Q: 26

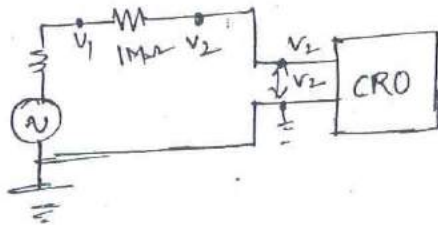

$V_1 = 5V$
 $V_2 = 3V$

$I = \frac{V_1 - V_2}{1M} = \frac{5-3}{1M} = 2\mu A$

voltage across CRO = V_2

$\Rightarrow R = \frac{3}{2} = 1.5M\Omega$

Q: 27

a)

Q: 28

d)

Q: 29

$I_L = \frac{10}{1+1} = 5A$

$I_L = I_C \left(\frac{R_C}{R_C + 1} \right)$

$5 = \frac{I_C R_C}{R_C + 1}$


Q: 30

Tellegen's Theorem

Q: 31

Ans: c

Q: 32

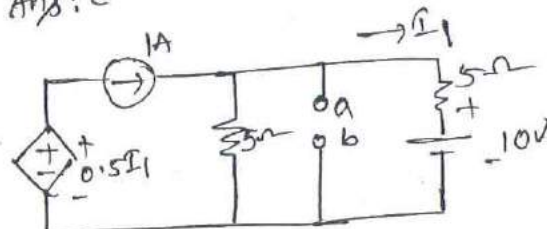


$1 = \frac{V_{th}}{5} + \frac{V_{th} - 10}{5} \Rightarrow V_{th} = 7.5V$

Ans: (b)

Q: 33


Ans: (b)

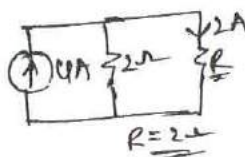

Q: 34

Ans: b

Q: 35

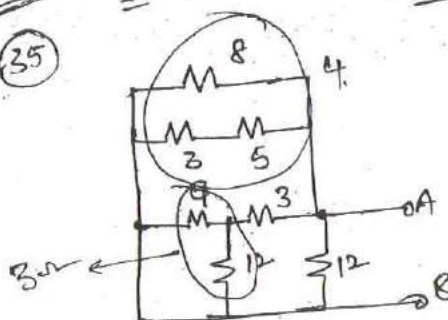

$\Rightarrow R_{th} = 2\Omega$


Q: 36

Ans: (d)

Q: 37

Ans: (d)

Q: 38

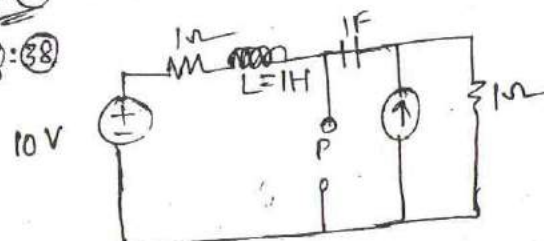

Since $de \rightarrow f \rightarrow$

$V_{AB} \rightarrow$
 $C \rightarrow D$

$\Rightarrow Z_{th} = (1 + sL) // (1 + \frac{1}{s})$
 $= \frac{(1+s)(1+\frac{1}{s})}{(1+s) + (\frac{1}{s} + 1)} = 1$

Ans: (a)

Q: 39

case (i)

$E = E_1, I = 0 \rightarrow V = 5 = V_{OC}$

case (ii):


$E = 0, I = 1A; V = 5$

all the sources are deactivated. w.r.to second side V & I both are known

$\Rightarrow R_{th} = \frac{V}{I} = 5\Omega$


case (iii):

$E = E_1, I \rightarrow 5\Omega$

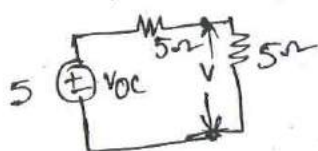

$V = 2.5V$

Q: 40

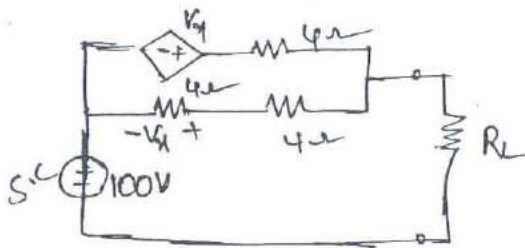

$$\frac{V_A - V_x}{4} + \frac{V_A}{8} = 1 \quad \text{--- (1)}$$


Since $V_A = \frac{V_x}{2}$

$\Rightarrow$ (1) $\Rightarrow V_A = 4V$


$V_{AB} = V_A - V_B = 4 - 0 = 4V$

$R_{th} = \frac{V_{AB}}{I_s} = \frac{4}{1} = 4\Omega$

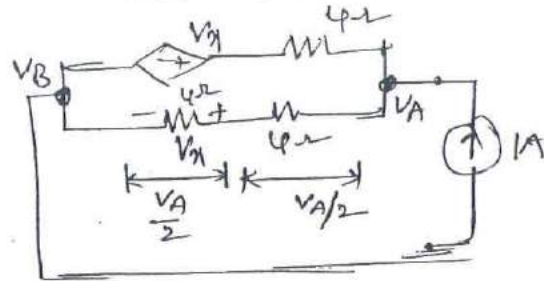$\Rightarrow$ Write R_L branch 1 & branch 2 are parallel. So take current source with 1A




(C9) By substitution theorem

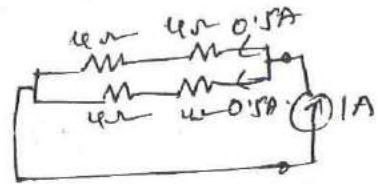

$\Rightarrow V_{AB} = 4V$
 $I_s = 1A$
 $R_{th} = \frac{4}{1} = 4\Omega$

Q: 41

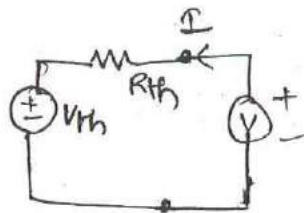

from given data

$I = 0.2V - 2$

$V = \frac{I}{0.2} + \frac{2}{0.2}$
 $= 10 + 5I$


$I = \frac{V - V_{th}}{R_{th}}$

$IR_{th} = V - V_{th}$
 $V = V_{th} + IR_{th} \quad \text{--- (1)}$

from (1) & (2)
 $R_{th} = 5\Omega$
 $V_{th} = 10V$

Q: 42 Ans: (C)


Q: 43

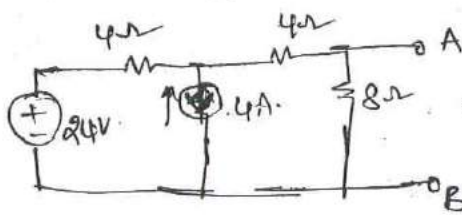

$R_{th} = 4\Omega$

$I_N = 5A$ Ans: (A)

Q: 44

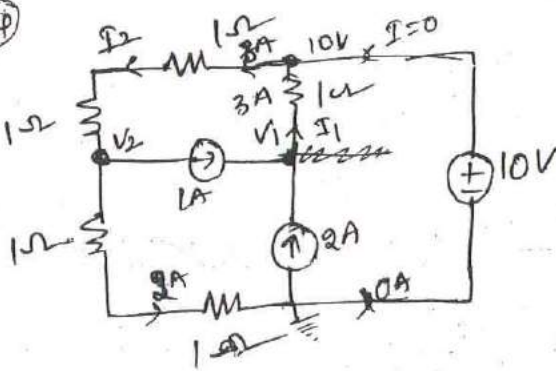

Ans: (a)

$\frac{V_1 - 10}{1} = 2 + 1$

$V_1 = 13V$


$\therefore I_1 = \frac{13 - 10}{1} = 3A$

$\frac{V_2 - 10}{2\Omega} + \frac{V_2}{2} = 0$

$V_2 [1] = 4V \Rightarrow V_2 = 4V$

$I_2 = \frac{10 - 4}{2} = 3A$

Q:45

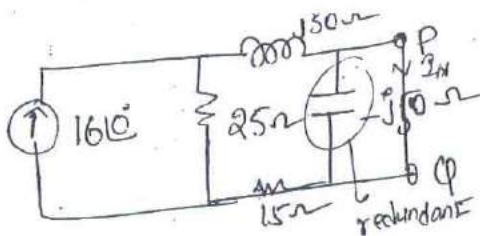

$$I_N = 16 \angle [25]$$

$$= \frac{16 \angle [25]}{25 + 15 + j30}$$

$$= \frac{16 \angle [25]}{(40)^2 + (30)^2}$$



$$= \frac{16 \angle [25]}{100 \angle [25]}$$

$$= 6.4 - j4.8 \quad \text{Ans (a)}$$

Q:46

Ans: (a)

Q:47

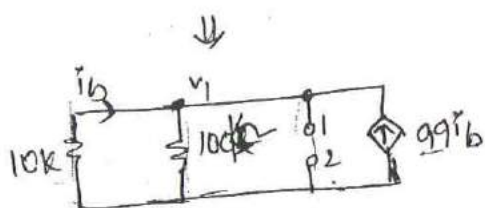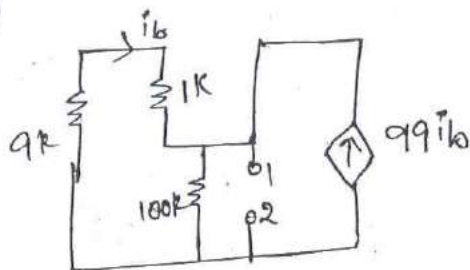

$$R_{th} = \frac{V_{oc}}{I_{sc}} \quad V_{oc} \Rightarrow ?$$

$$\frac{V_1}{10k} + \frac{V_1}{100k} = 99i_b$$

$$= 99 \left[\frac{-V_1}{100k} \right]$$

$$\frac{V_1}{10} + \frac{V_1}{100}$$

$$V_1 [1.1] = -V_1 [99]$$

$$V_1 = \frac{1}{100.1} = 0.001 V = V_{oc}$$

$$I_{sc} = 99i_b + i_b = 100i_b$$

$$\therefore \frac{V_{oc}}{I_{sc}} = \frac{\frac{1}{100.1}}{\frac{100i_b}{100k}} = \frac{99 \times 100k}{100} = 9k\Omega$$

Conventional:-


Q:2 $V_{th} = \frac{108}{31} \text{ volts} ; R_{th} = \frac{96}{31} \Omega$

Q:3) $V_{th} = 5\sqrt{2} \sin 100t$
 $Z_{th} = (5 - j100)k\Omega$
 $i = 0.049 \text{ mA}$

Q:4) $V_{th} = 72.11 \angle 3.18$
 $Z_{th} = 3.77 \angle 68.8$
 $i_L(t) = 11.2 \angle -30.11$
 $P_L = 505.8$

Q:6) $V_{th} = 1.83 \angle 46.02$
 $Z_{th} = 8.28 \angle -69.2$
 $I_N = 0.219 \angle 115.25$

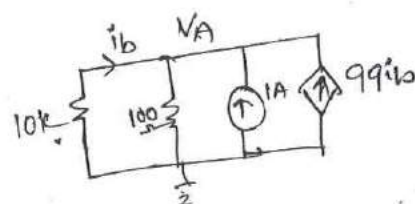Q:7) $V_{th} = 0$
 $R_{th} = \frac{5 + 2k}{3}$



Same problem 100kΩ is replaced by 100Ω.

$$\frac{V_1}{10} + \frac{V_1}{0.1k} = 99i_b + i_b$$

$$\Rightarrow V_{th} = 99i_b$$

$$i_b = \frac{-V_A}{10 \times 10^3}$$

$$V_A = 50$$

$$\therefore R_{th} = \frac{V_{AB}}{I_{sc}} = \frac{50}{1} = 50\Omega$$

Q5
sol:-

$$V = 10 \sin(2\pi \times 10^6 t)$$

$$R_{int} = 1 \Omega$$


ii) $P_{max} = ?$

$$P_{max} = \frac{V_r^2}{4R_L}$$


$$R_L = R_S = 1 \Omega$$

i) $P_{max} = \frac{V_r^2}{4R_L}$

for max power the load res = 0.

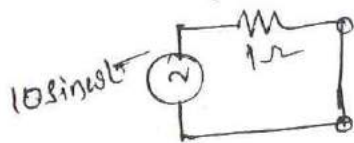


$$P = \frac{(10/2)^2}{4(1)} = 50W$$

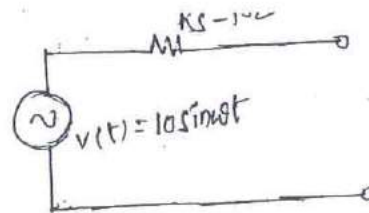

$$\Rightarrow P_{max} = \frac{(10/2)^2}{4(1)} = \frac{100}{8} = 12.5W$$


iii)

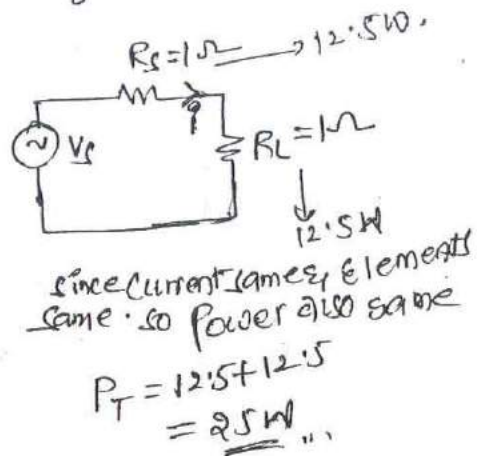

since current same & elements same. so power also same


$$P_T = 12.5 + 12.5 = 25W$$

Proof of Thevenin's Theorem:-

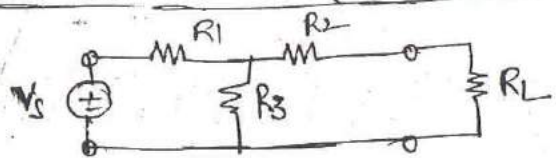


Case i) :- (V_{th})

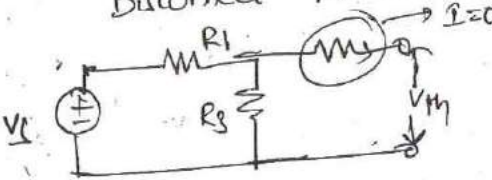Disconnect the load resistor and find the voltage across load resistor.




$$V_{th} = V_S \cdot \frac{R_3}{R_1 + R_3} \rightarrow 1$$

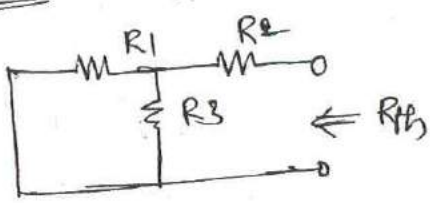Case ii) :- Deactivate all independent sources.



$$R_{th} = (R_1 || R_3) + R_2 = \frac{R_1 R_3}{R_1 + R_3} + R_2$$

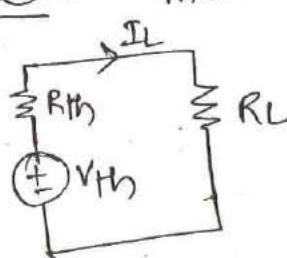Case iii) :- develop Thevenin's equivalent circuit. sh




$$I_L = \frac{V_{th}}{R_{th} + R_L} \rightarrow 3$$

Substitute eq 1 & eq 2 in eq 3, we can get

a new equation
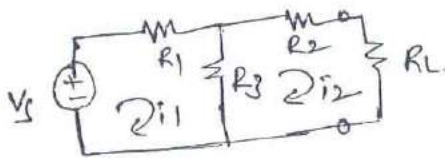
$$I_L = \frac{V_S R_3}{R_1 R_3 + R_3 R_2 + R_3 R_1 + R_3 R_2} \rightarrow 4$$



$$V_S = (R_1 + R_3)I_1 - R_3 I_2 \quad \text{--- (5)}$$

$$0 = (I_2 - I_1)R_3 + R_2 I_2 + R_L I_2 \quad \text{--- (6)}$$

Subst (7) in (5), we get

$$\text{From (6)} \Rightarrow I_1 = \frac{(R_2 + R_L + R_3) I_2}{R_3} \quad \text{--- (7)}$$


$$\text{from (5)} \Rightarrow V_S = \left[(R_1 + R_3) \frac{(R_2 + R_L + R_3)}{R_3} - R_3 \right] I_2 \quad \text{--- (8)}$$

$$\Rightarrow I_2 = \frac{V_S (R_3)}{R_2 R_1 + R_2 R_3 + R_3 R_1 + R_3 R_L} \quad \text{--- (8)}$$

from the above calculation it is concluded that load current of eqn (4) & eqn (8) are equal. Hence Thevenin's theorem is Proved.

Page no (48)

Q:1

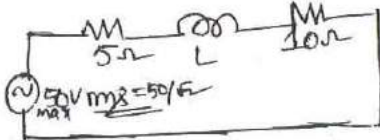

$$I^2 R_L = P \Rightarrow 10 = I^2 \cdot R$$

$$\Rightarrow I = \sqrt{\frac{10}{5}} = \sqrt{2} \text{ A}$$

$$Z = \frac{V}{I} = \frac{50/\sqrt{2}}{\sqrt{2}} = 25 \Omega$$

$$\text{Eqv Resistance} = 15 \Omega$$

$$\therefore \text{P.F} = \frac{R}{Z} = \frac{15}{25} = \frac{3}{5} = 0.6$$

Q:2

Sol:

$$v = 200 \sin(2000t + 50^\circ)$$

$$i = 4 \cos(2000t + 13^\circ)$$

$$\Rightarrow v = 200 \sin(2000t - 40^\circ)$$

'i' is lead by v. so R & C.

Ans (d)

R & C.

RLC $\rightarrow (X_C > X_L)$

(09)

$$v = 200 \sin(2000t + 50^\circ)$$

$$i = 4 \sin(2000t + (13.2 + 90))$$

Q:3

$$X_L = 1000 \Omega$$

$$X_C = 1000 \Omega$$

$$R = 0.1 \Omega$$

$$f_0 = 10 \text{ MHz}$$

$$\text{B.W} = \frac{R}{2\pi L} = f_2 - f_1 \text{ \& also known that}$$

$$Q = \frac{f_0}{f_2 - f_1} \Rightarrow f_2 - f_1 = \frac{f_0}{Q}$$


$$\text{Now } Q = \frac{X_L}{R} = \frac{1000}{0.1}$$

$$Q = 10^4$$

$$\therefore f_2 - f_1 = \frac{10 \times 10^6}{10^4} = 1000$$

$$= 1 \text{ kHz}$$

Q:4

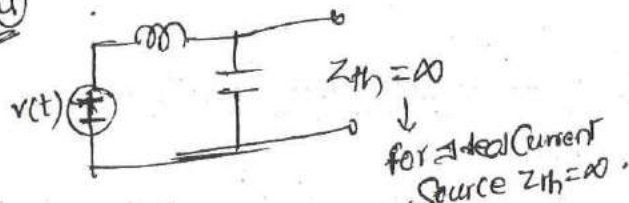

(09)

by s.c the source, it will form a tank circuit

$$Z_{pf} = \infty$$

$$\omega_c = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{16 \times 1}} = 4 \text{ rad/sec}$$

Q: In the ckt shown at what value of R_1 & R_2 circuit resonant for all frequencies.

Sol:



$$B_L = B_C$$

$$\frac{X_L}{R_1^2 + X_L^2} = \frac{X_C}{R_2^2 + X_C^2}$$

$$\frac{\omega L}{R_1^2 + (\omega L)^2} = \frac{(1/\omega C)}{R_2^2 + (1/\omega C)^2}$$

$$\frac{1}{\frac{R_1^2 + \omega L}{\omega L}} = \frac{1}{\frac{R_2^2 + 1/\omega C}{R_2^2 \cdot \omega C + 1/\omega C}}$$

To satisfy $B_L = B_C$ coefficients of ω should become.

$$\omega \Rightarrow L = R_2^2 C$$

$$\text{Coeff} \Rightarrow \boxed{R_2^2 = \frac{L}{C}}$$

$$\frac{1}{\omega} \Rightarrow \frac{R_1^2}{L} = \frac{1}{C}$$

$$\text{Coeff} \Rightarrow \boxed{R_1^2 = \frac{L}{C}}$$

$$\therefore \boxed{R_1^2 = R_2^2 = \frac{L}{C}}$$

Q: 5

$$R_1^2 = R_2^2 = \frac{L}{C}$$

$$\Rightarrow 16 = \frac{1}{C} \Rightarrow \underline{\underline{C = 1/16 \text{ F}}}$$


$$\text{Q: 6} \quad \boxed{X_L = X_C}$$

$$2\pi f L = \frac{1}{2\pi f C}$$

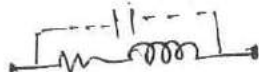Q: 7 Statement $\rightarrow$ valid

Self resonant is possible at high freq, but real time applications $f = 50 \text{ Hz}$ (low).

wherever inductor
capacitor present
self res is present



Ans (b)

Note:- For the inductor is present at high frequency, & there is a possibility to get self resonance at high frequency. But in the real time system inductor is operated at normal frequency (low frequency).

Q. 10

$$Y(s) = \frac{s^2 + 0.5s + 100}{5s}$$

→ for calculation simple eqn for parallel we go for Y'

$$Y(s) = \frac{s}{5} + \frac{0.1}{s} + \frac{20}{s}$$

$$B.C = \frac{1}{X_c} = \left(\frac{1}{sC}\right) = sC$$


$$\therefore \boxed{C = \frac{1}{5}}$$

$$B.L = \frac{1}{sL}$$

$$\boxed{L = \frac{1}{20}}$$

$$\boxed{R = \frac{1}{0.1} = 10}$$

Q. 10

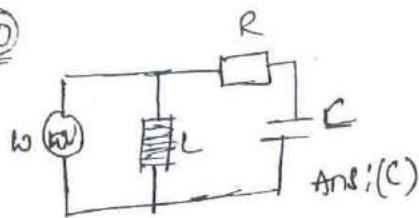

- (1) Find eqn impedance
- (2) Equate imaginary part to zero.

Q. 11

B. (a)

$$H(s) = \frac{10^6}{s^2 + 20s + 10^6} = \frac{V_o(s)}{V_i(s)}$$

Voltage ratio means indirectly series RLC. Since voltage division is possible in series only.

$$(D^2 + \frac{R}{L}D + \frac{1}{LC})I = 0$$

$$\left(\frac{R}{L}\right) = 20; \left(\frac{1}{LC}\right) = 10^6$$

$$B.W = 20$$

$$\omega_2 - \omega_1 = 20$$

$$\Rightarrow Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{1000}{20} = 50 \dots$$

Q. 13

soln

$$R = 20\Omega$$

$$I = i \angle -45^\circ$$

$$V_L = 2V_C$$

$$\cancel{X_L} = 2\cancel{X_C}$$

$$\Rightarrow X_C = \frac{X_L}{2} \quad \text{--- (1)}$$

$$\phi = \tan^{-1}\left(\frac{X_L - X_C}{R}\right)$$

$$I = \frac{X_L - X_C}{R} \Rightarrow X_L - X_C = 20\Omega$$

$$X_L - X_C = 20$$

$$X_L - \frac{X_L}{2} = 20$$

$$\boxed{X_C = 20\Omega}$$

$$\boxed{X_L = 40\Omega}$$