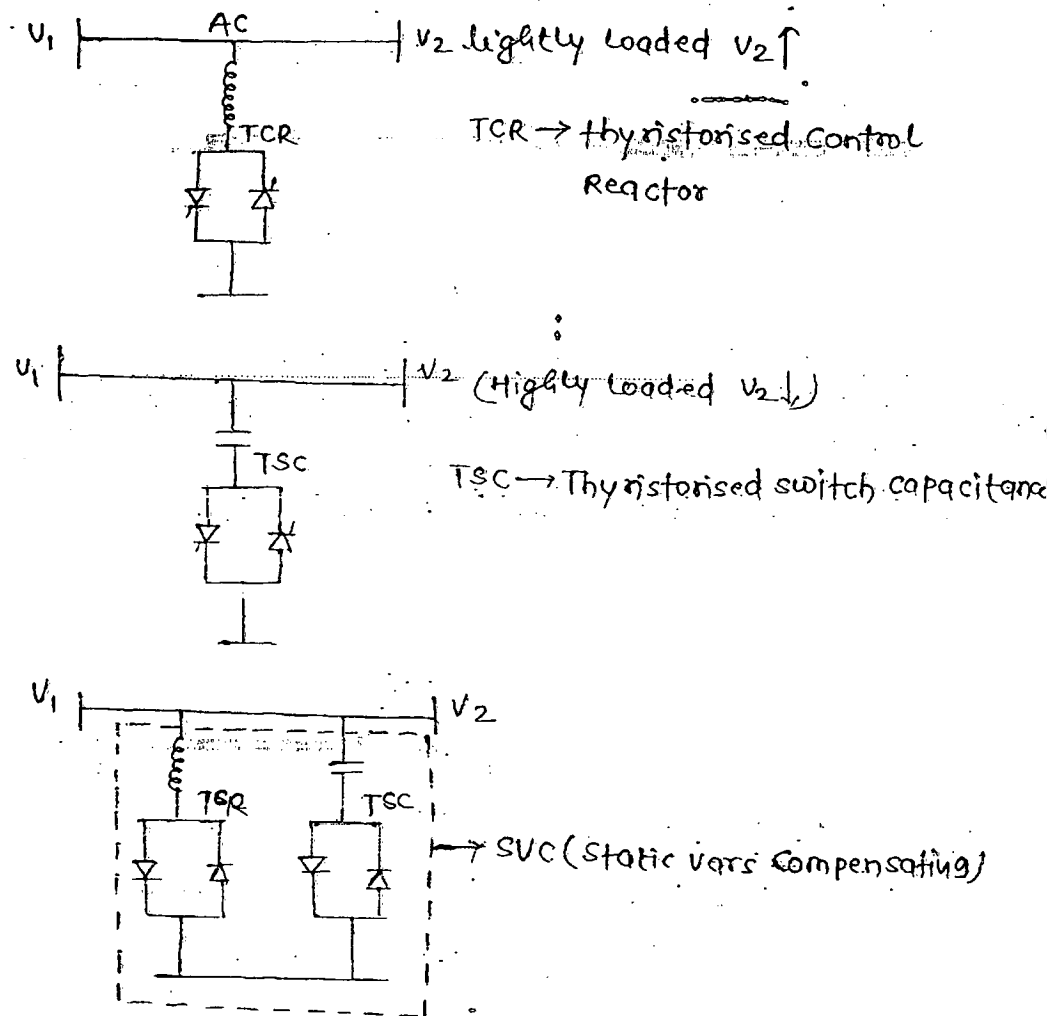


HVDC


* We can transmit the power by using EHVAC (or) HVDC.

Features of AC lines:-


- (1) The power flow magnitude & dirⁿ can't be quickly & easily control.
- (2) The transient stability limit is lesser in the AC line when compared with dc line.
- (3) The other prob. associated with AC lines are skin effect, corona losses, radio & TV interference b/n the comm. lines & power lines.



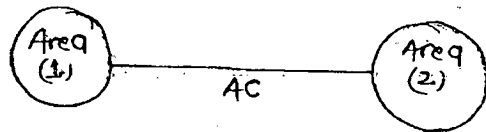- (4) Intermediate substation are installed in the ac line to compensate the reactive power automatically as per the requirement of the line.



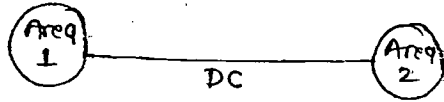Synchronous tie [Frequencies must be same]



Asynchronous tie [freq. need not be same].

(5) The sys. disturbance in one of area results in power swings.

If the power swings are unstable then it may lead to cascading of tripping the alternators & this results in large scale blackouts.

(6) With ac interconnection the freq. disturbance in one area is transferred to other area.

(7) If multiple no. of areas is interconnected by ac line then the fault level of the system increases.

8

* HVDC → It is economical to Xmit bulk power over long distance.


Advantages →

- (1) The power flow magnitude & dirn can be quickly & easily controlled.
- (2) The transient stability limit is improved in the dc line.
- (3) There is no skin effect prob. in the dc line.
- (4) The other prob. likes corona losses, radio & tv interference is very much reduced in the dc lines.
- (5) HVDC is used for underground & submarine cables even for short distance (because dc cables will not charge continuously)
- (6) HVDC can utilise earth for its return path.
- (7) The power xⁿ capacity of a bipolar HVDC line is almost same as that of 3φ single ckt ac line.
- (8) We can interconnect 2 independant areas at different freq. because it is an asynchronous type.
- (9) With dc interconnection the freq. disturbance in one area can't be Xferred to other area.

(10) If multiple no. of areas are interconnected with dc line then the fault level of the sys. will not be substantially increased.

Types of HVDC →

(1) Bipolar HVDC →

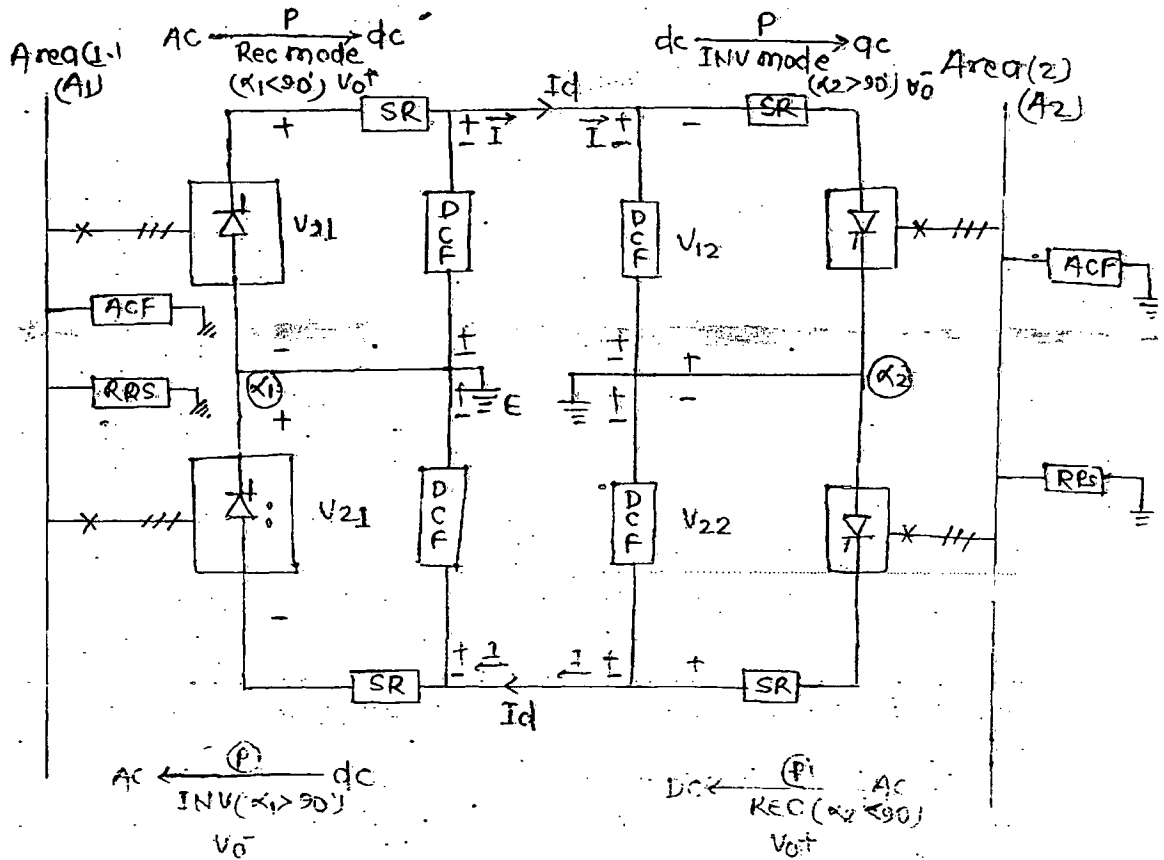

SR → Smoothing Reactor

DCF → DC Filter

ACF → AC Filter


RPS → Reactive power source (To compensate the required Power for converter operation)

$\{ \pm \text{Ref} \}$

$\{ \pm \text{Actual } (A_1 \rightarrow A_2) \}$



$\{ \pm \text{Actual } (A_1 \leftarrow A_2) \}$


(2) Monopolar HVDC →

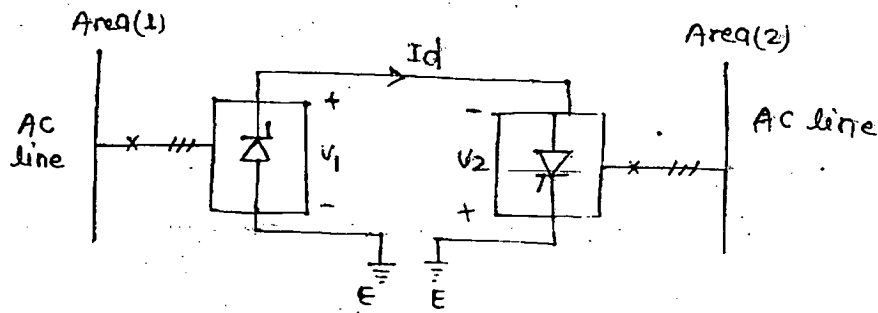

* In order to reduce the harmonics the 6 pulse conf is replaced by the 12 pulse conf.

12 pulse Converter →

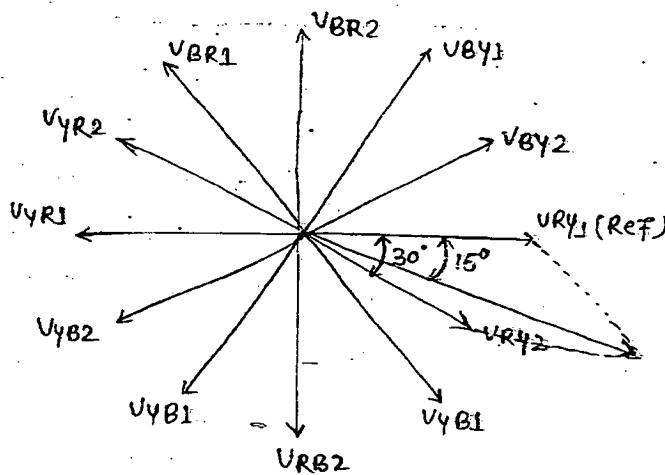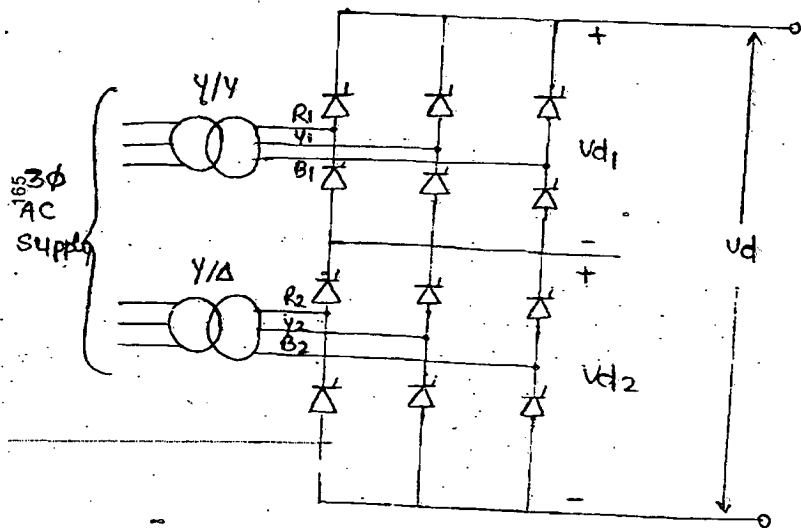

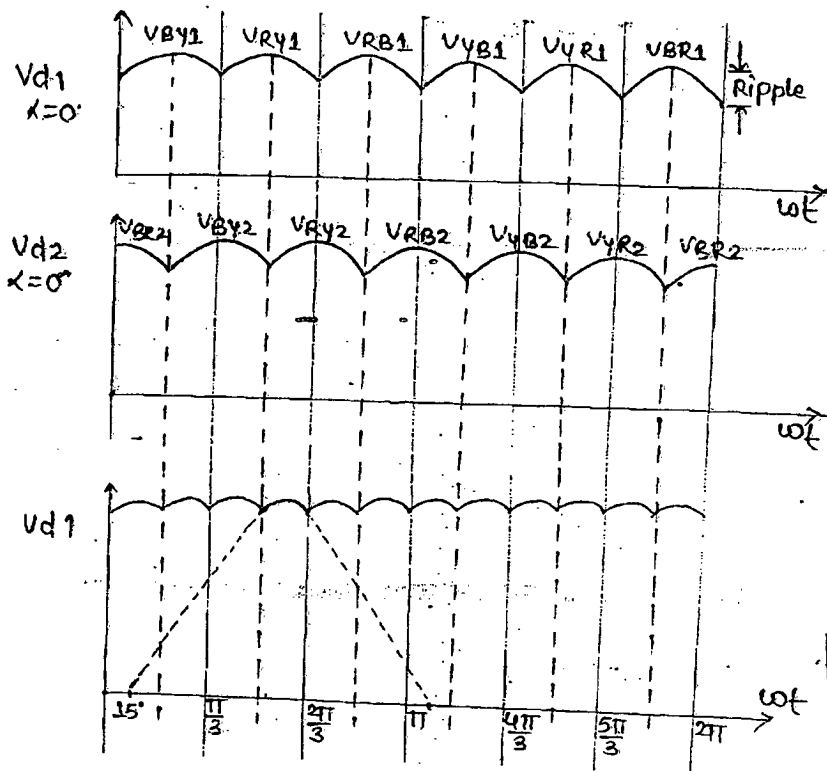

$$V_{RY1} = V_m \sin \omega t$$

$$V_{RY2} = V_m \sin(\omega t - 30^\circ)$$

$$V_d = V_{RY1} + V_{RY2}$$

$$V_d = V_m [\sin \omega t + \sin(\omega t - 30^\circ)]$$

$$= V_m \cdot 2 \sin(\omega t - 15^\circ) \cos 15^\circ$$

$$V_d = 1.93 V_m \sin(\omega t - 15^\circ)$$

Harmonics On AC side →

Harmonics on AC side of m pulse $\text{conv}^r(I_s) \rightarrow m k \pm 1$

Harmonics on AC side of 2 pulse $\text{conv}^r(I_s) \rightarrow 2k \pm 1 = 3, 5, 7, 9, \dots$

6 pulse $\text{conv}^r(I_s) \rightarrow 6k \pm 1 = 5, 7, 11, 13, \dots$

12 pulse $\text{conv}^r(I_s) \rightarrow 12k \pm 1 = 11, 13, 23, 25, \dots$

Harmonics on dc side →

Harmonics on dc side of m puls $\text{conv}^r(V_o) = m k$

2 pulse $\text{conv}^r(V_o) = 2k$

6 pulse $\text{conv}^r(V_o) = 6k$

12 pulse $\text{conv}^r(V_o) = 12k$

$\frac{11}{57}$ $\frac{V}{f}$ control of IM

$$N_s = \frac{120f}{P} = \frac{120 \times 50}{2} = 3000 \text{ rpm}$$

$$\therefore s = \frac{N_s - N_r}{N_s} = \frac{3000 - 2850}{3000} = 0.05$$

11500 for 40 Hz

$$N_s = \frac{120f}{p} = \frac{120 \times 40}{2} = 2400$$

$$\frac{1}{2} s_r = \frac{N_s - N_r}{N_s}$$

$$\frac{0.05}{2} = \frac{2400 - N_r}{2400}$$

$$N_r = 2340 \text{ rpm}$$

14
58

$$V_o = E_b + I_o R_a \rightarrow \text{Neglected}$$

$$\frac{3V_{m1}}{\pi} \cos \alpha = 220$$

$$\frac{3 \times 440/\sqrt{2} \cos \alpha}{\pi} = 220$$

$$PF = \frac{3}{\pi} \cos \alpha = \frac{1}{\sqrt{2}}$$

$$\cos \alpha = 0.354$$

$$\frac{3}{\pi} \cos \alpha = 0.354$$

$$E_b \propto N$$

It half the rated speed

$$\frac{N}{2} \propto \frac{E}{2} \propto \frac{440}{2} = 220$$

167

15
58

$$\alpha \downarrow, V_o \uparrow, \omega \uparrow$$

16
58

$$\text{Regenerated Power} = V_o \cdot I_o$$

$$= V_s (1 - \alpha) I_o$$

$$= 600 (1 - 0.7) 100$$

$$= 18 \text{ kW}$$

Because Regenerative braking is done only in Boost con.
Hence $V_o = V_s$.

Inverter Question

(1/49)

$$2d = 120^\circ$$

$$d = 60^\circ$$

$$V_{on} = \frac{2\sqrt{2}}{\pi} \sin nd \cdot V_s$$

$$V_{ol} = \frac{2\sqrt{2}}{\pi} \sin d \cdot V_s$$

$$= \frac{2\sqrt{2}}{\pi} \cdot 1 \cdot \sin d$$

$$= 0.78V$$


(4/49)

$$\frac{V_{o3}}{(V_{ol})_{max}} = \frac{2\sqrt{2} V_s \sin 3d}{3\pi}$$

$$= \frac{\frac{2\sqrt{2}}{\pi} V_s}{3} \sin 3d = 19.6V$$

(11/50)

$$V_{12} = V_1 - V_2$$

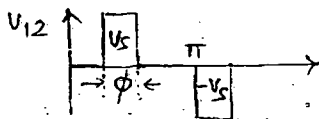

$$V_{12} = V_s \left(\frac{\phi}{\pi} \right)^{1/2}$$

(13/51)

$$D \rightarrow \phi = \tan^{-1} \frac{X_C - X_L}{R}$$

$$= \tan^{-1} \left(\frac{X_C - 0}{0} \right) = 90^\circ$$

$$\omega t = \pi/2 \text{ rad}$$

$$t = \pi/2\omega \text{ rad} = \frac{1}{4f} \text{ sec}$$

$$t = 5 \text{ ms}$$

(5/49)


$$g = \frac{2\sqrt{2} \sin nd}{\sqrt{(2d) \cdot \pi}} \quad 2d = 150 = \frac{5\pi}{6} \text{ rad}$$

$$d = 75^\circ$$

$$g = \frac{2\sqrt{2} \sin 75^\circ}{\sqrt{\frac{5\pi}{6} \cdot \pi}} \quad g = 0.95$$

$$THD = 31.8\%$$

(7/50)

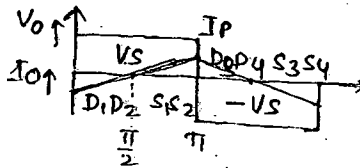

$$\pi/2 \text{ to } \pi; S_1, S_2 \rightarrow \text{ON}, V_o = V_s$$

$$\frac{dI_o}{dt} = V_s; \int_0^{\pi/2} dI_o = \frac{V_s}{\omega L} \int_0^{\pi/2} d(\omega t)$$

$$I_p = \frac{V_s}{\omega L} \cdot \frac{\pi}{2} = \frac{V_s}{4fL} = 10A$$

(12/50)

$$|Z_n| = X_{Ln} = n\omega L$$

$$V_{on} = \kappa_n \cdot V_{ol} \quad (\kappa_n < 1)$$

$$I_{on} = \frac{V_{on}}{|Z_n|} = \frac{\kappa_n V_{ol}}{n \cdot \omega L} = \frac{\kappa_n}{n} I_{ol}$$

conv. (1.) $\rightarrow$

$$(1.) RLC; \omega t_c = \phi = \tan^{-1} \frac{X_C - X_L}{R}; \omega = \frac{2\pi}{T} = \frac{2\pi}{0.2 \times 10^{-3}}$$

$$\tan(\omega t_c) = \frac{X_C - X_L}{R}$$

$$t_c = (SE) t_d = 2.42 \times 10^{-6} = 2.4 \times 10^{-6}$$

$$\tan \left[\frac{2\pi}{0.2 \times 10^{-3}} \times 2.4 \times 10^{-6} \right] = \frac{X_C - 12}{3}$$

$$X_C = 14.7 \Omega, \frac{1}{\omega C} = 14.7$$

$$C = 2.15 \mu F$$