

# 6

## Two-Port Networks




### Multiple Choice Questions

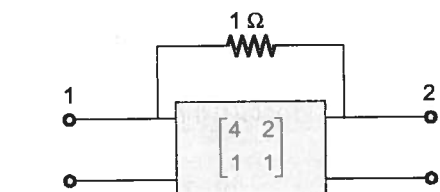Q.1 The Y parameters of a four-terminal block are

$$\begin{bmatrix} 4 & 2 \\ 1 & 1 \end{bmatrix}$$

A single element of 1 ohm is connected across as shown in the given figure. The new Y parameters will be



- (a)  $\begin{bmatrix} 5 & 1 \\ 0 & 2 \end{bmatrix}$  (b)  $\begin{bmatrix} 4 & 3 \\ 2 & 2 \end{bmatrix}$   
 (c)  $\begin{bmatrix} 3 & 2 \\ 1 & 2 \end{bmatrix}$  (d)  $\begin{bmatrix} 4 & 2 \\ 1 & 1 \end{bmatrix}$

[ESE-1994]

Q.2 With the usual notation, a two-port resistive network satisfies the condition


$$A = D = \frac{3}{2}B = \frac{4}{3}C$$

The  $Z_{11}$  of the network is

- (a) 5/3 (b) 4/3  
 (c) 2/3 (d) 1/3

[ESE-1995]

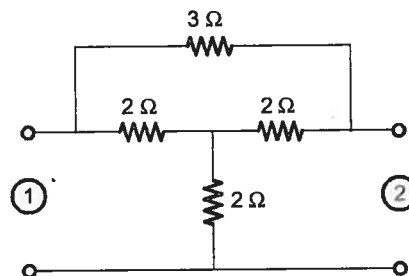Q.3 The  $Y_{21}$  parameter of the network shown in the given figure will be



- (a)  $\frac{1}{6}$  mho (b)  $-\frac{1}{6}$  mho  
 (c)  $\frac{1}{3}$  mho (d)  $-\frac{1}{2}$  mho

[ESE-1996]

Q.4 The short-circuit admittance matrix of a two-port network is


$$\begin{bmatrix} 0 & -1/2 \\ 1/2 & 0 \end{bmatrix}$$

The two-port network is

- (a) non-reciprocal and passive  
 (b) non-reciprocal and active  
 (c) reciprocal and passive  
 (d) reciprocal and active

[GATE-1998]

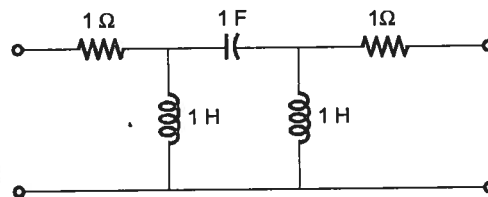
Q.5 Driving-point impedance of the network shown in the figure is



- (a)  $\frac{s^3 + 2s^2 + s + 1}{2s^2 + 1}$  (b)  $\frac{s^3 + s^2 + s + 1}{s^2 + 1}$   
 (c)  $\frac{2s^2 + 1}{s^3 + 2s^2 + s + 1}$  (d)  $\frac{s^3 + 2s^2 + s + 1}{s^2 + 1}$

[ESE-1999]

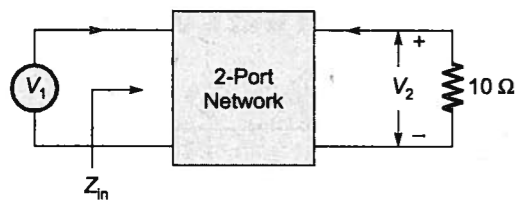- Q.6** If the transmission parameters of the above network are  $A = C = 1$ ,  $B = 2$  and  $D = 3$ , then the value of  $Z_{in}$  is



- (a)  $\frac{12}{13} \Omega$  (b)  $\frac{13}{12} \Omega$   
(c)  $\frac{8}{7} \Omega$  (d)  $4 \Omega$

[ESE-2000]

- Q.7** The impedance matrices of two, two-port networks are given by


$$\begin{bmatrix} 3 & 2 \\ 2 & 3 \end{bmatrix} \text{ and } \begin{bmatrix} 15 & 5 \\ 5 & 25 \end{bmatrix}$$

If these two networks are connected in series, the impedance matrix of the resulting two-port network will be

- (a)  $\begin{bmatrix} 3 & 5 \\ 2 & 25 \end{bmatrix}$  (b)  $\begin{bmatrix} 18 & 7 \\ 7 & 28 \end{bmatrix}$   
(c)  $\begin{bmatrix} 15 & 2 \\ 5 & 3 \end{bmatrix}$  (d) indeterminate

[ESE-2000]

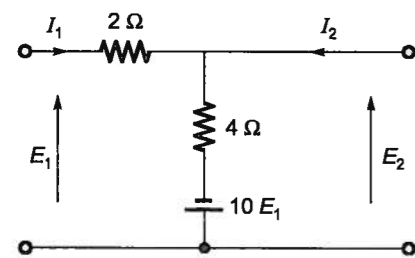
- Q.8** The  $z$  parameters  $z_{11}$  and  $z_{21}$  for the 2-port network in the figure are



- (a)  $z_{11} = \frac{-6}{11} \Omega$ ;  $z_{21} = \frac{16}{11} \Omega$   
(b)  $z_{11} = \frac{6}{11} \Omega$ ;  $z_{21} = \frac{4}{11} \Omega$   
(c)  $z_{11} = \frac{6}{11} \Omega$ ;  $z_{21} = \frac{-16}{11} \Omega$   
(d)  $z_{11} = \frac{4}{11} \Omega$ ;  $z_{21} = \frac{4}{11} \Omega$

[GATE-2001]

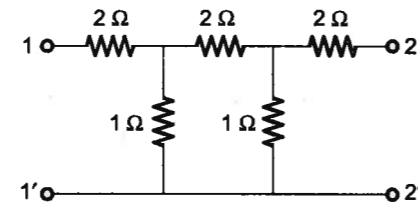- Q.9** The impedance parameters  $z_{11}$  and  $z_{12}$  of the two-port network in the figure are



- (a)  $z_{11} = 2.75 \Omega$  and  $z_{12} = 0.25 \Omega$   
(b)  $z_{11} = 3 \Omega$  and  $z_{12} = 0.5 \Omega$   
(c)  $z_{11} = 3 \Omega$  and  $z_{12} = 0.25 \Omega$   
(d)  $z_{11} = 2.25 \Omega$  and  $z_{12} = 0.5 \Omega$

[GATE-2001]


- Q.10** The driving point impedance  $Z(s) = \frac{s+2}{s+3}$ . The

system is initially at rest. For a voltage signal of unit step, the current  $i(t)$  through the impedance  $Z$  is given by

- (a)  $2 - e^{-t}$  (b)  $3/2 - 1/2 e^{-3t}$   
(c)  $3/2 - 1/2 e^{-2t}$  (d)  $3 - 2 e^{-2t}$

[ESE-2001]

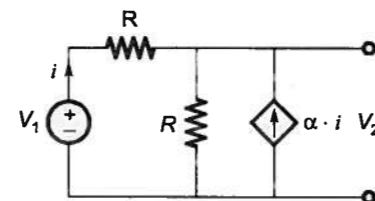- Q.11** Consider the circuit as shown below which has a current-dependent current source. The value  $V_2/V_1$  is




- (a) 1 (b) 2  
(c)  $\frac{1+\alpha}{2+\alpha}$  (d)  $\frac{\alpha}{2+\alpha}$

[ESE-2003]

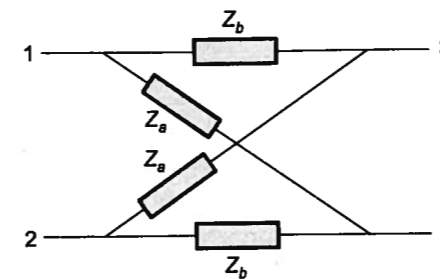- Q.12** For the lattice circuit shown in the figure,  $Z_a = j2 \Omega$  and  $Z_b = 2 \Omega$ . The values of the open circuit

impedance parameters  $Z = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$  are




- (a)  $\begin{bmatrix} 1-j & 1+j \\ 1+j & 1+j \end{bmatrix}$  (b)  $\begin{bmatrix} 1-j & 1+j \\ -1+j & 1-j \end{bmatrix}$   
(c)  $\begin{bmatrix} 1+j & 1+j \\ 1+j & 1-j \end{bmatrix}$  (d)  $\begin{bmatrix} 1+j & -1+j \\ -1+j & 1+j \end{bmatrix}$

[GATE-2003]

- Q.13** The input voltage  $V_1$  and current  $I_1$  for linear passive network is given by  $V_1 = AV_2 - BI_2$  and  $I_1 = CV_2 - DI_2$

Now consider the following network:

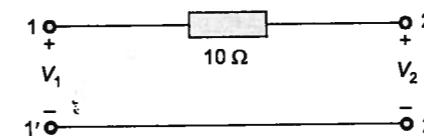

Which one of the following is the transfer matrix

$\begin{bmatrix} A & B \\ C & D \end{bmatrix}$  of the network shown above?

- (a)  $\begin{bmatrix} 1 & 0 \\ 0 & 10 \end{bmatrix}$  (b)  $\begin{bmatrix} 1 & 10 \\ 0 & 1 \end{bmatrix}$   
(c)  $\begin{bmatrix} 0 & 1 \\ 10 & 0 \end{bmatrix}$  (d)  $\begin{bmatrix} 0 & 10 \\ 1 & 0 \end{bmatrix}$


[ESE-2004]

- Q.14** For an ideal step-down ( $n:1$ ) transformer, which one of the following is the ABCD parameter matrix?

- (a)  $\begin{bmatrix} n & 1 \\ 1 & n \end{bmatrix}$  (b)  $\begin{bmatrix} n & 0 \\ 0 & n \end{bmatrix}$   
(c)  $\begin{bmatrix} n & 0 \\ 0 & 1/n \end{bmatrix}$  (d)  $\begin{bmatrix} n & 1/n \\ 1/n & 1 \end{bmatrix}$

[ESE-2004]

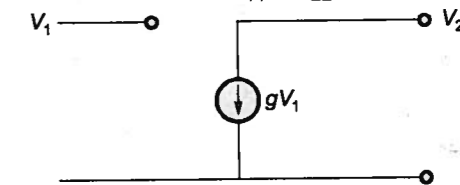- Q.15** The 2-port network shown in the circuit given below is connected in parallel with another 2-port network which has  $y_{11} = y_{22} = -Y$ ,  $-y_{12} = -y_{21} = Y$ .



The  $y$ -parameters of the composite network will satisfy which one of the following?

- (a)  $y_{11} = Y + g$  (b)  $y_{12} = -Y + g$   
(c)  $y_{21} = -Y + g$  (d)  $y_{22} = Y + g$

[ESE-2004]

- Q.16** In the case of ABCD parameters, if all the impedances in the network are doubled, then

- (a) A and D remain unchanged, C is halved and B is doubled  
(b) A, B, C and D are doubled  
(c) A and B are doubled, C and D are unchanged  
(d) A and D are unchanged, C is doubled and B is halved


[ESE-2010]

- Q.17** The  $h_{11}$  and  $h_{22}$  of a standard  $T$ -network with series impedances  $2 \Omega$  and  $7 \Omega$ , and shunt branch impedance of  $3 \Omega$  are

- (a)  $5 \Omega$  and  $10 \text{ mho}$  respectively  
(b)  $10 \Omega$  and  $5 \text{ mho}$  respectively  
(c)  $4.1 \Omega$  and  $0.1 \text{ mho}$  respectively  
(d)  $10 \Omega$  and  $0.2 \text{ mho}$  respectively

[ESE-2012]

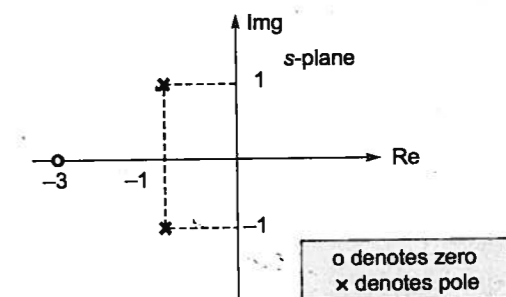- Q.18** The driving-point impedance  $Z(s)$  of a network has the pole-zero locations are shown in the figure. If  $Z(0) = 3$ , then  $Z(s)$  is




- (a)  $\frac{3(s-3)}{s^2+2s+3}$  (b)  $\frac{2(s+3)}{s^2+2s+2}$   
 (c)  $\frac{3(s-3)}{s^2-2s-2}$  (d)  $\frac{2(s-3)}{s^2-2s-3}$

[GATE-2003]

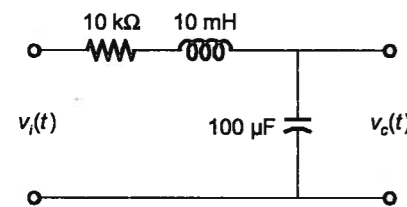Q.19 For the circuit shown in the figure, the initial conditions are zero. Its transfer function


$$H(s) = \frac{V_o(s)}{V_i(s)} \text{ is}$$



- (a)  $\frac{1}{s^2+10^6s+10^6}$  (b)  $\frac{10^6}{s^2+10^3s+10^6}$   
 (c)  $\frac{10^3}{s^2+10^3s+10^6}$  (d)  $\frac{10^6}{s^2+10^6s+10^6}$

[GATE-2004]

Q.20 For the network shown below.

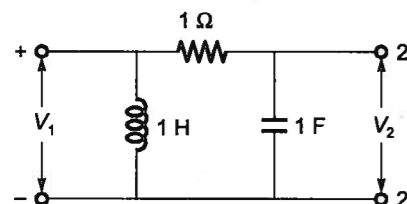

Match List-I (y-parameter) with List-II (Value) and select the correct answer using the code given below the lists:


- | List-I               | List-II      |
|----------------------|--------------|
| A. $y_{11}$          | 1. $s+1$     |
| B. $y_{12}$          | 2. $-1$      |
| C. $y_{22} + y_{21}$ | 3. $1 + 1/s$ |
| D. $y_{22}$          | 4. $s$       |

Codes:

- |     | A | B | C | D |
|-----|---|---|---|---|
| (a) | 3 | 2 | 4 | 1 |
| (b) | 1 | 4 | 2 | 3 |
| (c) | 3 | 4 | 2 | 1 |
| (d) | 1 | 2 | 4 | 3 |

[ESE-2005]

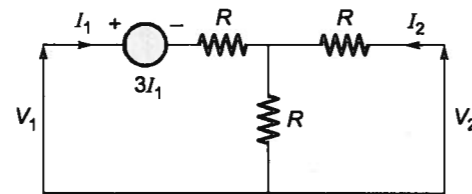Q.21 Which one of the following is correct? The circuit shown in the figure below.



- (a) is reciprocal but not symmetrical  
 (b) is not reciprocal but symmetrical  
 (c) is both reciprocal and symmetrical  
 (d) is neither reciprocal nor symmetrical

[ESE-2007]

Q.22 A two-terminal network consists of a coil having inductance  $L$  and resistance  $R$  shunted by a capacitance  $C$ . The poles and zeros of the driving-point impedance function  $Z(\omega)$  are


located as poles at  $-\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$  and zero at  $-1$ .

If  $Z(0) = 1$ , the values of  $R$ ,  $L$  and  $C$  are

- (a)  $1 \Omega$ ,  $1 \text{ H}$  and  $1 \mu\text{F}$   
 (b)  $1 \Omega$ ,  $1 \text{ H}$  and  $1 \text{ F}$   
 (c)  $1 \Omega$ ,  $1 \mu\text{H}$  and  $1 \text{ F}$   
 (d)  $1 \text{ k}\Omega$ ,  $1 \text{ H}$  and  $1 \text{ F}$

[ESE-2012]

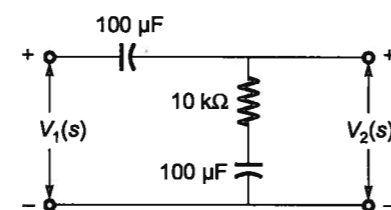Q.23 The transfer function  $\frac{V_2(s)}{V_1(s)}$  of the circuit shown below is



- (a)  $\frac{0.5s+1}{s+1}$  (b)  $\frac{3s+6}{s+2}$   
 (c)  $\frac{s+2}{s+1}$  (d)  $\frac{s+1}{s+2}$

[GATE-2013]

Q.24 Two 2-port networks with transmission matrices


$$T_A = \begin{bmatrix} 1 & 2 \\ 0.1 & 4 \end{bmatrix} \text{ and } T_B = \begin{bmatrix} 2 & 4 \\ 0.5 & 3 \end{bmatrix}$$

are connected in cascade. Which is the transmission matrix of the combination?

- (a)  $\begin{bmatrix} 3 & 10 \\ 2.2 & 12.4 \end{bmatrix}$  (b)  $\begin{bmatrix} 3 & 6 \\ 0.2 & 12.4 \end{bmatrix}$   
 (c)  $\begin{bmatrix} 1 & 10 \\ 2.0 & 12.0 \end{bmatrix}$  (d)  $\begin{bmatrix} 3 & 10 \\ 12.4 & 2.2 \end{bmatrix}$

[ESE-2006]

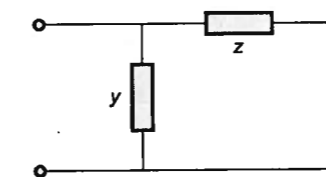
Q.25 Which one of the following is the transmission matrix for the network shown in the figure given below?



- (a)  $\begin{bmatrix} 1 & 1+yz \\ y & z \end{bmatrix}$  (b)  $\begin{bmatrix} 1+yz & z \\ y & 1 \end{bmatrix}$   
 (c)  $\begin{bmatrix} 1 & z \\ y & 1+yz \end{bmatrix}$  (d)  $\begin{bmatrix} 1 & 1+yz \\ z & y \end{bmatrix}$

[ESE-2006]

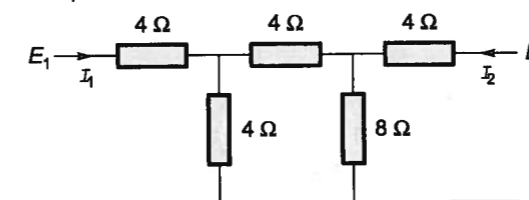
Q.26 What is the value of the parameter  $h_{12}$  for the 2-port network shown in the figure given below?



- (a) 0.125 (b) 0.167  
 (c) 0.250 (d) 0.625

[ESE-2006]

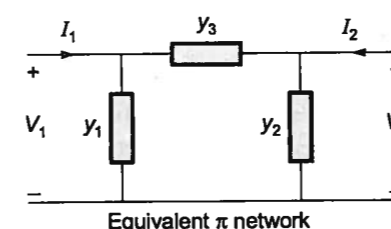Q.27 The currents  $I_1$  and  $I_2$  at the output of 2-port network can be written as



$$I_1 = 5V_1 - V_2$$

$$I_2 = -V_1 + V_2$$


Which one of the following gives the parameters of an equivalent  $\pi$  network shown above?

- (a)  $y_1 = 4 \text{ }\Omega$ ,  $y_2 = 0$ ,  $y_3 = 1 \text{ }\Omega$   
 (b)  $y_1 = 4 \text{ }\Omega$ ,  $y_2 = 4 \text{ }\Omega$ ,  $y_3 = 1 \text{ }\Omega$   
 (c)  $y_1 = 1 \text{ }\Omega$ ,  $y_2 = 1 \text{ }\Omega$ ,  $y_3 = 1 \text{ }\Omega$   
 (d)  $y_1 = 4 \text{ }\Omega$ ,  $y_2 = 0$ ,  $y_3 = 2 \text{ }\Omega$

[ESE-2006]

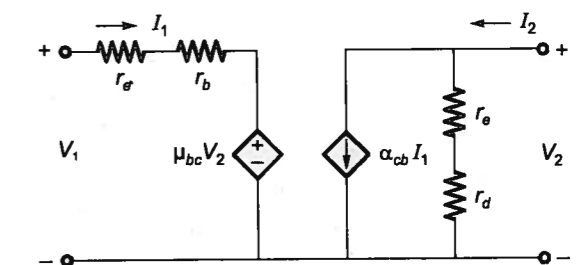Q.28 Consider the two port transistor circuit as given below:

Match List-I (Hybrid Parameter) with List-II (Circuit Element) and select the correct answer using the code given below in the lists:



List-I

List-II

- |             |                          |
|-------------|--------------------------|
| A. $h_{11}$ | 1. $\frac{1}{r_e + r_d}$ |
| B. $h_{12}$ | 2. $r_b + r_e$           |
| C. $h_{21}$ | 3. $\mu_{bc}$            |
| D. $h_{22}$ | 4. $\alpha_{cb}$         |

Codes:

- |     | A | B | C | D |
|-----|---|---|---|---|
| (a) | 2 | 1 | 4 | 3 |
| (b) | 4 | 3 | 2 | 1 |
| (c) | 2 | 3 | 4 | 1 |
| (d) | 4 | 1 | 2 | 3 |

[ESE-2006]

Q.29 A two-port network is represented by ABCD parameters given by


$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} A & B \\ C & D \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

If port-2 is terminated by  $R_L$ , the input impedance seen at port-1 is given by

- (a)  $\frac{A + BR_L}{C + DR_L}$  (b)  $\frac{AR_L + C}{BR_L + D}$   
 (c)  $\frac{DR_L + A}{BR_L + C}$  (d)  $\frac{B + AR_L}{D + CR_L}$

[GATE-2006]

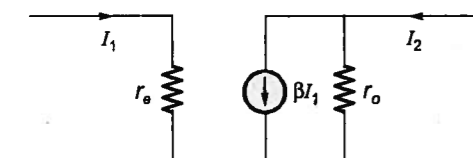**Q.30** In the two port network shown in the figure below,  $Z_{12}$  and  $Z_{21}$  are, respectively



- (a)  $r_e$  and  $\beta r_o$  (b) 0 and  $-\beta r_o$   
(c) 0 and  $\beta r_o$  (d)  $r_e$  and  $-\beta r_o$


[GATE-2006]

**Q.31** For determining the network functions of a two-port network, it is required to consider that

- (a) all initial conditions remain same  
(b) all initial conditions are zero  
(c) part of initial conditions are equal to zero  
(d) initial conditions vary depending on nature of network

[ESE-2009]

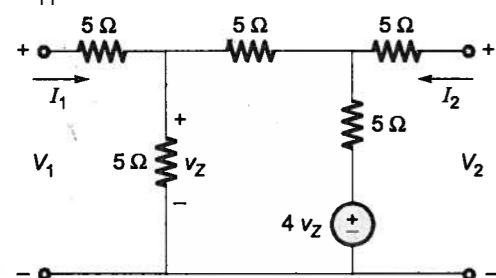
**Q.32** With reference to the below network the value of  $Z_{11}$  will be



- (a) -3 (b) 3  
(c) -1 (d) -5

[ESE-2009]

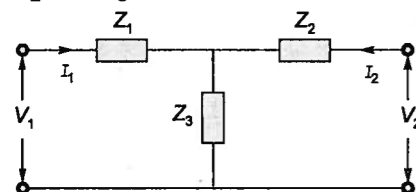
**Q.33** If the Z-parameters for the T-network as shown below are  $z_{11} = 40 \Omega$ ,  $z_{22} = 50 \Omega$  and  $z_{12} = z_{21} = 30 \Omega$ , then what are the values of  $z_1$ ,  $z_2$  and  $z_3$ ?



- (a) 10  $\Omega$ , 20  $\Omega$  and 30  $\Omega$   
(b) 20  $\Omega$ , 30  $\Omega$  and 20  $\Omega$   
(c) 30  $\Omega$ , 40  $\Omega$  and 10  $\Omega$   
(d) 40  $\Omega$ , 50  $\Omega$  and 10  $\Omega$

[ESE-2009]

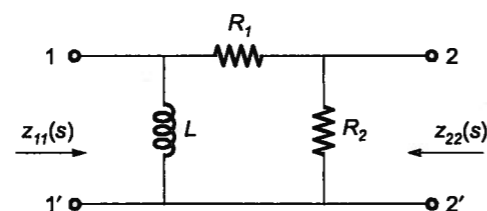
**Q.34** For the circuit shown below, the natural frequencies at port 2 are given by  $s + 2 = 0$  and  $s + 5 = 0$ , without knowing which refers to open-circuit and which to short-circuit. Then the impedances  $Z_{11}$  and  $Z_{22}$  are given respectively by



- (a)  $K_1 \frac{s+5}{s+2}$ ,  $K_2 \frac{s+2}{s+5}$   
(b)  $K_1 \frac{s+2}{s+5}$ ,  $K_2 \frac{s+5}{s+2}$   
(c)  $K_1 \frac{s}{s+5}$ ,  $K_2 \frac{s+2}{s+5}$   
(d)  $K_1 \frac{s+2}{s+5}$ ,  $K_2 \frac{s+2}{s+5}$

[ESE-2010]

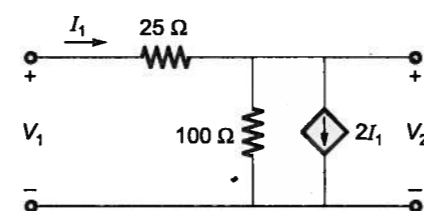
**Q.35** The Y-parameters of the network shown below are



- (a)  $\begin{bmatrix} -0.04 & 0.04 \\ -0.04 & 0.03 \end{bmatrix}$  (b)  $\begin{bmatrix} 0.04 & -0.04 \\ 0.04 & -0.03 \end{bmatrix}$   
(c)  $\begin{bmatrix} 0.04 & -0.03 \\ -0.04 & 0.03 \end{bmatrix}$  (d)  $\begin{bmatrix} -0.04 & 0.04 \\ 0.04 & 0.03 \end{bmatrix}$

[ESE-2010]

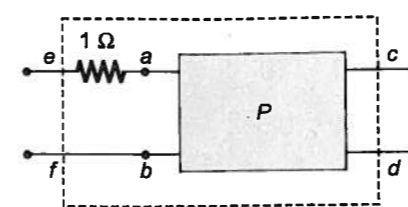**Q.36** The two-port network  $P$  shown in the figure has port 1 and 2, denoted by terminals (a, b) and (c, d), respectively. It has an impedance matrix  $Z$  with parameters denoted by  $z_{ij}$ . A 1  $\Omega$  resistor is connected in series with the network at port 1 as shown in the figure. The impedance matrix of the modified two-port network (shown as a dashed box) is




- (a)  $\begin{bmatrix} z_{11}+1 & z_{12}+1 \\ z_{21} & z_{22}+1 \end{bmatrix}$  (b)  $\begin{bmatrix} z_{11}+1 & z_{12} \\ z_{21} & z_{22}+1 \end{bmatrix}$   
(c)  $\begin{bmatrix} z_{11}+1 & z_{12} \\ z_{21} & z_{22} \end{bmatrix}$  (d)  $\begin{bmatrix} z_{11}+1 & z_{12} \\ z_{21}+1 & z_{22} \end{bmatrix}$

[GATE-2010]

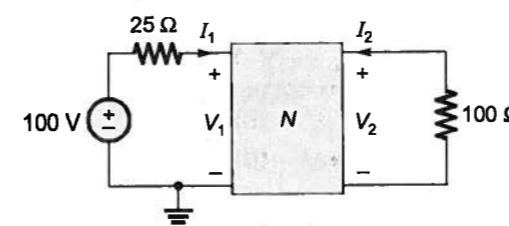**Q.37** In the circuit shown below, the network  $N$  is described by the following y matrix:

$$Y = \begin{bmatrix} 0.1S & -0.01S \\ 0.01S & 0.1S \end{bmatrix}. \text{ The voltage gain } \frac{V_2}{V_1} \text{ is}$$



- (a) 1/90 (b) -1/90  
(c) -1/99 (d) -1/11

[GATE-2011]

**Q.38** A 2-port network is represented by the following equations:


$$V_1 = 60 I_1 + 20 I_2 \\ V_2 = 20 I_1 + 40 I_2$$

The ABCD parameters of the above network would be

- (a)  $\begin{bmatrix} 2 & \frac{1}{20} \\ 3 & 100 \end{bmatrix}$  (b)  $\begin{bmatrix} 100 & 3 \\ 2 & \frac{1}{20} \end{bmatrix}$   
(c)  $\begin{bmatrix} 100 & 20 \\ 6 & 3 \end{bmatrix}$  (d)  $\begin{bmatrix} 3 & 100 \\ \frac{1}{20} & 2 \end{bmatrix}$

[ESE-2013]

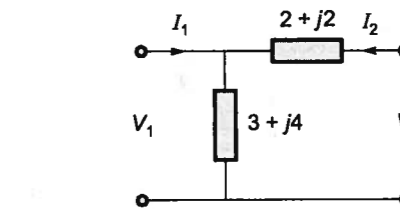
**Q.39** The Z-parameter matrix of the two-port network as shown below is



- (a)  $\begin{bmatrix} 3+j4 & 2+j2 \\ 2+j2 & 5+j6 \end{bmatrix}$  (b)  $\begin{bmatrix} 3+j4 & 3+j4 \\ 3+j4 & 5+j6 \end{bmatrix}$   
(c)  $\begin{bmatrix} 2+j2 & 3+j4 \\ 2+j2 & 5+j6 \end{bmatrix}$  (d)  $\begin{bmatrix} 3+j4 & 2+j2 \\ 1+j2 & 3+j4 \end{bmatrix}$

[ESE-2013]

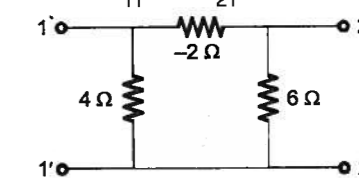
**Q.40** For the two port network as shown below, the parameters  $h_{11}$  and  $h_{21}$  are



- (a) 1  $\Omega$  and 2  $\Omega$  (b) 2  $\Omega$  and 1  
(c) 1 and  $\frac{1}{2} \Omega$  (d)  $\frac{1}{2} \Omega$  and 1

[ESE-2013]

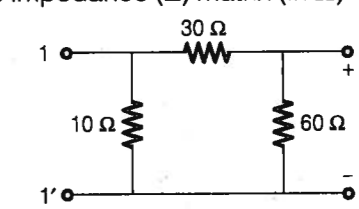
**Q.41** For the two-port network shown in the figure, the impedance ( $Z$ ) matrix (in  $\Omega$ ) is



- (a)  $\begin{bmatrix} 6 & 24 \\ 42 & 9 \end{bmatrix}$  (b)  $\begin{bmatrix} 9 & 8 \\ 8 & 24 \end{bmatrix}$   
(c)  $\begin{bmatrix} 9 & 6 \\ 6 & 24 \end{bmatrix}$  (d)  $\begin{bmatrix} 42 & 6 \\ 6 & 60 \end{bmatrix}$

[GATE-2014]

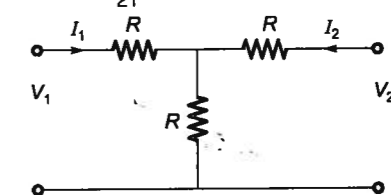**Q.42** A 2-port network is shown in figure. The parameter  $h_{21}$  for this network can be given by




- (a) -1/2 (b) +1/2  
(c) -3/2 (d) +3/2


[ESE-2015]

# **Numerical Data Type Questions**

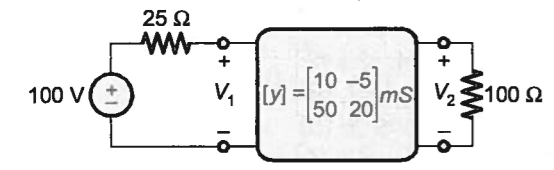
Q.43 For the circuit shown below the voltage  $V_1$  is \_\_ Volts.



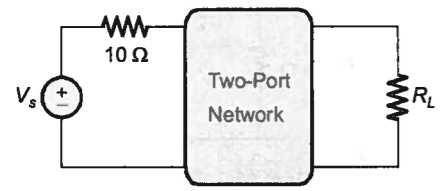Q.44 The two-port network in the following circuit has z-parameters  $z_{11} = 40\Omega$ ,  $z_{12} = 60\Omega$ ,  $z_{21} = 80\Omega$  and  $z_{22} = 120\Omega$ . If  $V_s = 60\text{V}$ , then maximum power delivered to the load  $R_L$  will be \_\_\_\_ watts.




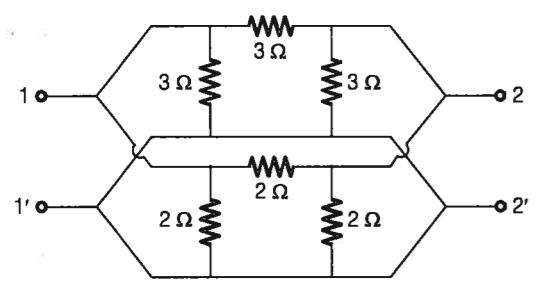Q.45 In the h-parameter model of the 2-port network given in the figure shown, the value of  $h_{22}$  (in S) is \_\_\_\_.



[GATE-2014]

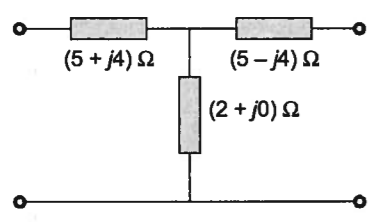Q.46 The ABCD parameters of the following 2-port network are




- (a)  $\begin{bmatrix} 3.5 + j2 & 20.5 \\ 20.5 & 3.5 - j2 \end{bmatrix}$
- (b)  $\begin{bmatrix} 3.5 + j2 & 0.5 \\ 0.5 & 3.5 - j2 \end{bmatrix}$

- (c)  $\begin{bmatrix} 10 & 2 + j0 \\ 2 + j0 & 10 \end{bmatrix}$
- (d)  $\begin{bmatrix} 7 + j4 & 0.5 \\ 30.5 & 7 - j4 \end{bmatrix}$

[GATE-2015]

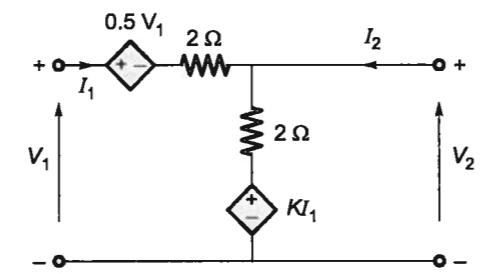
## **Try Yourself**

T1. When given network satisfy the reciprocity. Find the value of 'K'




- (a) 2
- (b) -2
- (c) 1
- (d) -1


T2. Find  $Z_{22}$

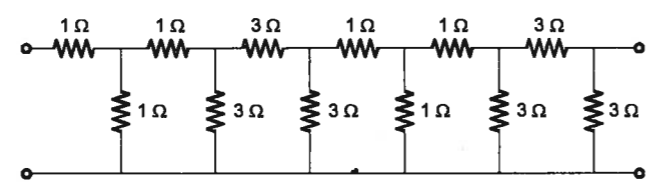

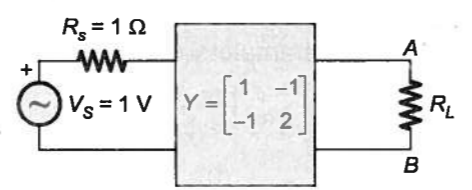
T3. Find  $I_{sc}$  with respect to A and B



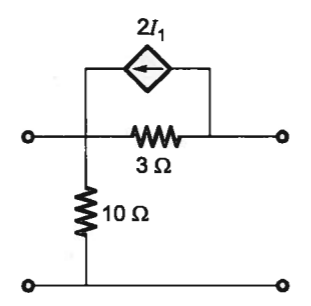T4. Find Z-parameters of the circuit shown



T5. Find the two-port shown

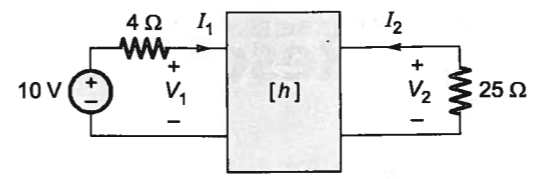


$$[h] = \begin{bmatrix} 16\Omega & 3 \\ -2 & 0.01s \end{bmatrix}$$


Find

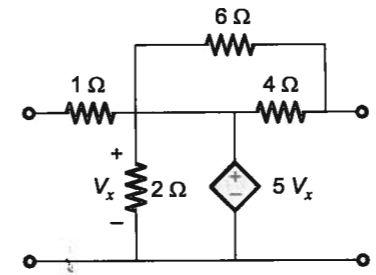- (a)  $\frac{V_2}{V_1}$
- (b)  $\frac{I_2}{I_1}$
- (c)  $\frac{I_1}{V_1}$
- (d)  $\frac{V_2}{I_1}$

T6. Find ABCD parameters of the network shown




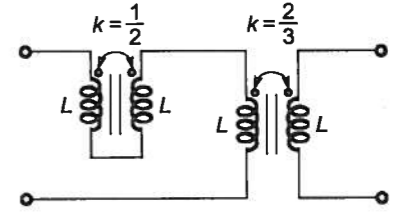T7. In the following circuit the z-parameters for  $L = 3\text{H}$  are



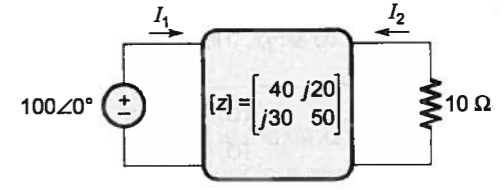- (a)  $\begin{bmatrix} 7.5s & 2s \\ 2s & 3s \end{bmatrix}$
- (b)  $\begin{bmatrix} 7.5s & -2s \\ -2s & 3s \end{bmatrix}$
- (c)  $\begin{bmatrix} 6s & 2s \\ 2s & 3s \end{bmatrix}$
- (d)  $\begin{bmatrix} 2s & 3s \\ 6s & 2s \end{bmatrix}$

T8. In the given two port network what are the values of current  $I_1$  and  $I_2$ ?



- (a)  $2\angle 0^\circ\text{A}, 1\angle 90^\circ\text{A}$
- (b)  $2\angle 0^\circ\text{A}, 1\angle 0^\circ\text{A}$
- (c)  $2\angle 0^\circ\text{A}, 1\angle -90^\circ\text{A}$
- (d)  $2\angle -90^\circ\text{A}, 1\angle -90^\circ\text{A}$

