

# Physics

## (Chapter - 3) (Current Electricity)

### (Class - XII)

#### EXERCISES

##### Question 3.1:

The storage battery of a car has an emf of 12 V. If the internal resistance of the battery is  $0.4\Omega$ , what is the maximum current that can be drawn from the battery?

##### Answer 3.1:

Emf of the battery,  $E = 12\text{ V}$

Internal resistance of the battery,  $r = 0.4\Omega$

Maximum current drawn from the battery =  $I$

According to Ohm's law,  $E = Ir \Rightarrow I = \frac{E}{r} = \frac{12}{0.4} = 30\text{A}$

The maximum current drawn from the given battery is 30 A.

##### Question 3.2:

A battery of emf 10 V and internal resistance  $3\Omega$  is connected to a resistor. If the current in the circuit is 0.5 A, what is the resistance of the resistor? What is the terminal voltage of the battery when the circuit is closed?

##### Answer 3.2:

Emf of the battery,  $E = 10\text{ V}$  and Internal resistance of the battery,  $r = 3\Omega$

Current in the circuit,  $I = 0.5\text{ A}$

Resistance of the resistor =  $R$

The relation for current using Ohm's law is,

$$I = \frac{E}{R + r} \Rightarrow R + r = \frac{E}{I} = \frac{10}{0.5} = 20\Omega$$

$$\therefore R = 20 - 3 = 17\Omega$$

Terminal voltage of the resistor =  $V$

According to Ohm's law,  $V = IR = 0.5 \times 17 = 8.5\text{ V}$

Therefore, the resistance of the resistor is  $17\Omega$  and the terminal voltage is 8.5 V.

##### Question 3.3:

At room temperature ( $27.0^\circ\text{C}$ ) the resistance of a heating element is  $100\Omega$ . What is the temperature of the element if the resistance is found to be  $117\Omega$ , given that the temperature coefficient of the material of the resistor is  $1.70 \times 10^{-4}^\circ\text{C}^{-1}$ .

##### Answer 3.3:

Room temperature,  $T = 27^\circ\text{C}$

Resistance of the heating element at  $T$ ,  $R = 100\Omega$

Let  $T_1$  is the increased temperature of the filament.

Resistance of the heating element at  $T_1$ ,  $R_1 = 117\Omega$

Temperature co-efficient of the material of the filament,  $\alpha = 1.70 \times 10^{-4}^\circ\text{C}^{-1}$

$\alpha$  is given by relation,

$$\alpha = \frac{R_1 - R}{R(T_1 - T)} \Rightarrow T_1 - T = \frac{R_1 - R}{R\alpha} \Rightarrow T_1 - 27 = \frac{117 - 100}{100(1.7 \times 10^{-4})} \Rightarrow T_1 - 27 = 1000$$

$$\Rightarrow T_1 = 1027^\circ\text{C}$$

Therefore, at  $1027^\circ\text{C}$ , the resistance of the element is  $117\Omega$ .



**Question 3.4:**

A negligibly small current is passed through a wire of length 15 m and uniform cross section  $6.0 \times 10^{-7} \text{ m}^2$ , and its resistance is measured to be  $5.0 \Omega$ . What is the resistivity of the material at the temperature of the experiment?

**Answer 3.4:**

Length of the wire,  $l = 15 \text{ m}$

Area of cross-section of the wire,  $a = 6.0 \times 10^{-7} \text{ m}^2$ , Resistance of the material of the wire,  $R = 5.0 \Omega$

Resistivity of the material of the wire =  $\rho$ , Resistance is related with the resistivity as

$$R = \rho \frac{l}{A} \Rightarrow \rho = \frac{RA}{l} = \frac{5 \times 6 \times 10^{-7}}{15}$$

$$= 2 \times 10^{-7} \Omega \text{ m}$$

Therefore, the resistivity of the material is  $2 \times 10^{-7} \Omega \text{ m}$ .

**Question 3.5:**

A silver wire has a resistance of  $2.1 \Omega$  at  $27.5^\circ \text{C}$ , and a resistance of  $2.7 \Omega$  at  $100^\circ \text{C}$ . Determine the temperature coefficient of resistivity of silver.

**Answer 3.5:**

Temperature,  $T_1 = 27.5^\circ \text{C}$

Resistance of the silver wire at  $T_1$ ,  $R_1 = 2.1 \Omega$

Temperature,  $T_2 = 100^\circ \text{C}$

Resistance of the silver wire at  $T_2$ ,  $R_2 = 2.7 \Omega$

Temperature coefficient of silver =  $\alpha$

It is related with temperature and resistance as

$$\alpha = \frac{R_2 - R_1}{R_1 (T_2 - T_1)} = \frac{2.7 - 2.1}{2.1 (100 - 27.5)} = 0.0039^\circ \text{C}^{-1}$$

Therefore, the temperature coefficient of silver is  $0.0039^\circ \text{C}^{-1}$ .

**Question 3.6:**

A heating element using nichrome connected to a 230 V supply draws an initial current of 3.2 A which settles after a few seconds to a steady value of 2.8 A. What is the steady temperature of the heating element if the room temperature is  $27.0^\circ \text{C}$ ? Temperature coefficient of resistance of nichrome averaged over the temperature range involved is  $1.70 \times 10^{-4}^\circ \text{C}^{-1}$ .

**Answer 3.6:**

Supply voltage,  $V = 230 \text{ V}$  and Initial current drawn,  $I_1 = 3.2 \text{ A}$

Initial resistance =  $R_1$ , which is given by the relation,

$$R_1 = \frac{V}{I_1} = \frac{230}{3.2} = 71.87 \Omega$$

Steady state value of the current,  $I_2 = 2.8 \text{ A}$

Resistance at the steady state =  $R_2$ , which is given as

$$R_2 = \frac{V}{I_2} = \frac{230}{2.8} = 82.14 \Omega$$

Temperature co-efficient of nichrome,  $\alpha = 1.70 \times 10^{-4}^\circ \text{C}^{-1}$

Initial temperature of nichrome,  $T_1 = 27.0^\circ \text{C}$



Study state temperature reached by nichrome =  $T_2$

$T_2$  can be obtained by the relation for  $\alpha$ ,  $T_1 = 1027^\circ\text{C}$

$$\alpha = \frac{R_2 - R_1}{R_1 (T_2 - T_1)} \Rightarrow T_2 - 27^\circ\text{C} = \frac{82.14 - 71.87}{71.87 - 1.7 \times 10^{-4}} = 840.5$$

$$T_2 = 840.5 + 27 = 867.5^\circ\text{C}$$

Therefore, the steady temperature of the heating element is  $867.5^\circ\text{C}$

### Question 3.7:

Determine the current in each branch of the network shown in Figure.

#### Answer 3.7:

Current flowing through various branches of the circuit is represented in the given figure.

$I_1$  = Current flowing through the outer circuit


$I_2$  = Current flowing through branch AB

$I_3$  = Current flowing through branch AD

$I_2 - I_4$  = Current flowing through branch BC

$I_3 + I_4$  = Current flowing through branch CD

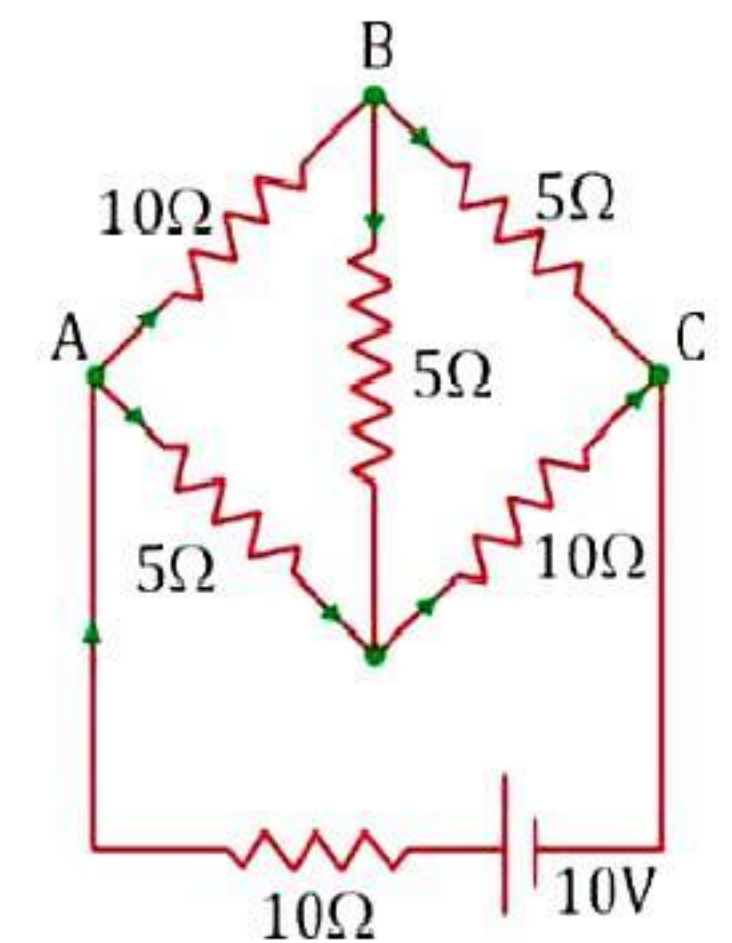$I_4$  = Current flowing through branch BD



For the closed circuit ABDA, potential is zero i.e.,

$$10I_2 + 5I_4 - 5I_3 = 0$$

$$2I_2 + I_4 - I_3 = 0$$

$$I_3 = 2I_2 + I_4 \quad \dots (1)$$

For the closed circuit BCDB, potential is zero i.e.,

$$5(I_2 - I_4) - 10(I_3 + I_4) - 5I_4 = 0$$

$$5I_2 + 5I_4 - 10I_3 - 10I_4 - 5I_4 = 0$$

$$5I_2 - 10I_3 - 20I_4 = 0$$

$$I_2 = 2I_3 + 4I_4 \quad \dots (2)$$

For the closed circuit ABCFEA, potential is zero i.e.,

$$-10 + 10(I_1) + 10(I_2) + 5(I_2 - I_4) = 0$$

$$10 = 15I_2 + 10I_1 - 5I_4$$

$$3I_2 + 2I_1 - I_4 = 2 \quad \dots (3)$$

From equations (1) and (2), we obtain

$$I_3 = 2(2I_3 + 4I_4) + I_4$$

$$I_3 = 4I_3 + 8I_4 + I_4$$

$$-3I_3 = 9I_4$$

$$-3I_4 = +I_3 \quad \dots (4)$$

Putting equation (4) in equation (1), we obtain


$$I_3 = 2I_2 + I_4$$

$$-4I_4 = 2I_2$$

$$I_2 = -2I_4 \quad \dots (5)$$

It is evident from the given figure that,

$$I_1 = I_3 + I_2 \quad \dots (6)$$

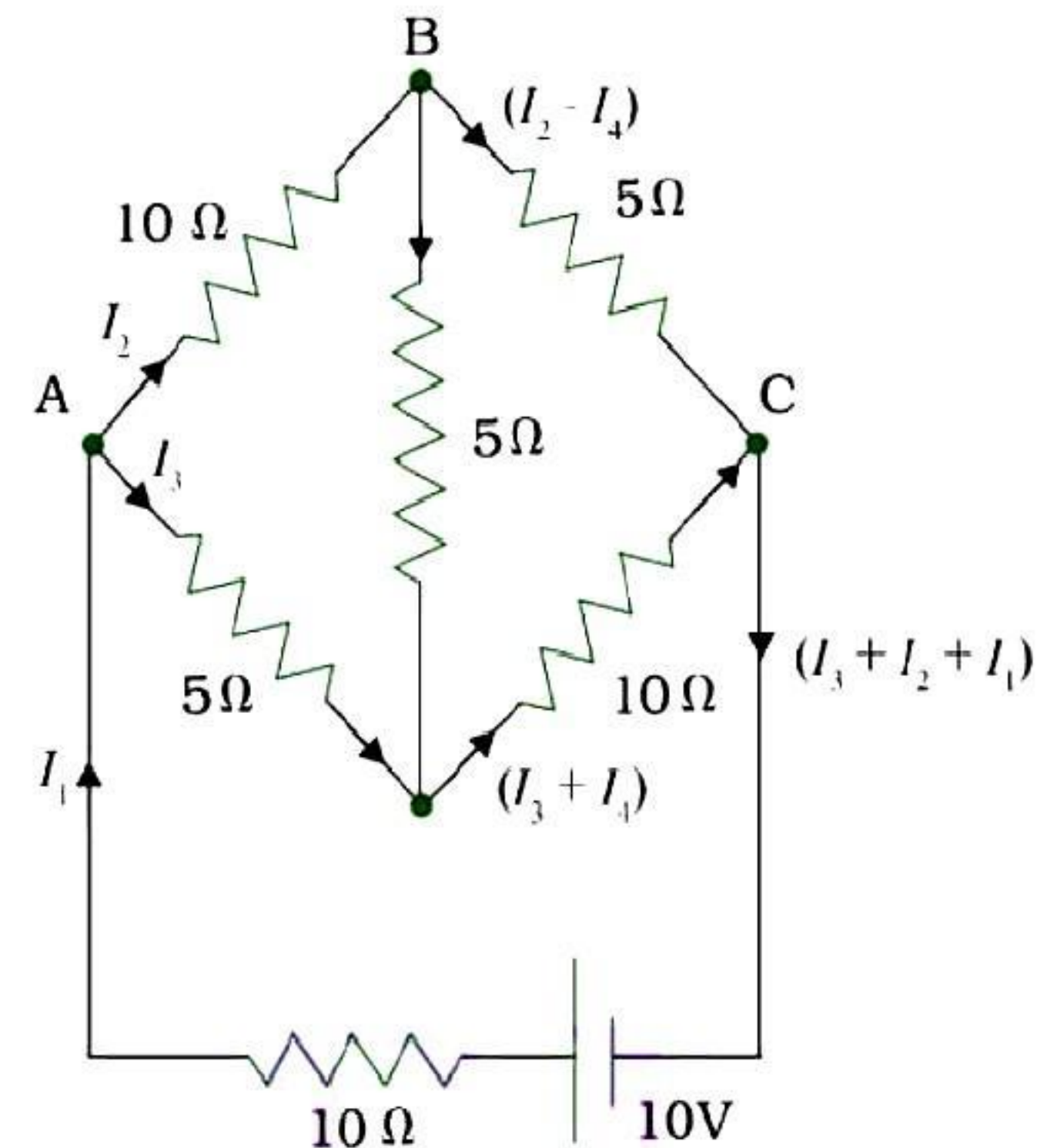



Putting equation (6) in equation (1), we have

$$3I_2 + 2(I_3 + I_2) - I_4 = 2$$

$$5I_2 + 2I_3 - I_4 = 2 \quad \dots (7)$$

Putting equations (4) and (5) in equation (7), we have

$$5(-2I_4) + 2(-3I_4) - I_4 = 2 \Rightarrow -10I_4 - 6I_4 - I_4 = 2 \Rightarrow 17I_4 = -2$$

$$I_4 = -\frac{2}{17} A$$

Equation (4) reduces to

$$I_3 = -3I_4 = -3\left(-\frac{2}{17}\right) = \frac{6}{17} A$$

$$I_2 = -2I_4 = -2\left(-\frac{2}{17}\right) = \frac{4}{17} A$$

$$I_2 - I_4 = \frac{4}{17} - \left(-\frac{2}{17}\right) = \frac{6}{17} A$$

$$I_3 + I_4 = \frac{6}{17} + \left(-\frac{2}{17}\right) = \frac{4}{17} A$$

$$I_1 = I_3 + I_2 = \frac{6}{17} + \frac{4}{17} = \frac{10}{17} A$$

Therefore, the current in branch in AB =  $I_2 = \frac{4}{17} A$

The current in branch in BC =  $I_2 - I_4 = \frac{6}{17} A$

In branch CD =  $I_3 + I_4 = \frac{4}{17} A$                       In branch AD =  $I_3 = \frac{6}{17} A$

In branch BD =  $I_4 = -\frac{2}{17} A$                       Total current =  $I_1 = \frac{10}{17} A$

### Question 3.8:

A storage battery of emf 8.0 V and internal resistance 0.5  $\Omega$  is being charged by a 120 V dc supply using a series resistor of 15.5  $\Omega$ . What is the terminal voltage of the battery during charging? What is the purpose of having a series resistor in the charging circuit?

#### Answer 3.8:

Emf of the storage battery,  $E = 8.0 V$  and Internal resistance of the battery,  $r = 0.5 \Omega$

DC supply voltage,  $V = 120 V$  and Resistance of the resistor,  $R = 15.5 \Omega$

Effective voltage in the circuit =  $V^1$

$R$  is connected to the storage battery in series. Hence, it can be written as  $V^1 = V - E$

$$V^1 = 120 - 8 = 112 V$$

Current flowing in the circuit =  $I$ , which is given by the relation,

$$I = \frac{V^1}{R + r} = \frac{112}{15.5 + 0.5} = \frac{112}{16} = 7 A$$

Voltage across resistor  $R$  given by the product,  $IR = 7 \times 15.5 = 108.5 V$

DC supply voltage = Terminal voltage of battery + Voltage drop across  $R$

Terminal voltage of battery =  $120 - 108.5 = 11.5 V$

A series resistor in a charging circuit limits the current drawn from the external source.

The current will be extremely high in its absence. This is very dangerous.



**Question 3.9:**

The number density of free electrons in a copper conductor estimated in Example 3.1 is  $8.5 \times 10^{28} \text{ m}^{-3}$ . How long does an electron take to drift from one end of a wire 3.0 m long to its other end? The area of cross-section of the wire is  $2.0 \times 10^{-6} \text{ m}^2$  and it is carrying a current of 3.0 A.

**Answer 3.9:**

Number density of free electrons in a copper conductor,  $n = 8.5 \times 10^{28} \text{ m}^{-3}$

Length of the copper wire,  $l = 3.0 \text{ m}$

Area of cross-section of the wire,  $A = 2.0 \times 10^{-6} \text{ m}^2$

Current carried by the wire,  $I = 3.0 \text{ A}$ , which is given by the relation,  $I = nAeV_d$

Where,  $e$  = Electric charge =  $1.6 \times 10^{-19} \text{ C}$

$V_d$  = Drift Velocity

$$= \frac{\text{Length of the wire } (l)}{\text{Time taken to cover } l \text{ (t)}}$$

$$I = n A e \frac{l}{t}$$

$$I = \frac{n A e l}{t}$$

$$= \frac{3 \times 8.5 \times 10^{28} \times 2 \times 10^{-6} \times 1.6 \times 10^{-19}}{3.0}$$

$$= 2.7 \times 10^4 \text{ s}$$

Therefore, the time taken by an electron to drift from one end of the wire to the other is  $2.7 \times 10^4 \text{ s}$ .