

SMPS

Here the transistor operates in the switch mode in very high freq. (Cut off region is used for off state & saturation region is used for on state).

At such an high freq. we can reduce the size of filter as well as X_{mer} .

* Here we use ferrite core for high freq. X_{mer} used in SMPS.

* With the availability of high speed device like power MOSFET SMPS is popularly used in now a days.

* SMPS is highly efficient & compact in size.


* In linear power supply the transistor operates in the active region & therefore it is not efficient power supply & it occupy more space & weight (because we use 50 Hz X_{mer} in linear power supply)

* Types of SMPS →

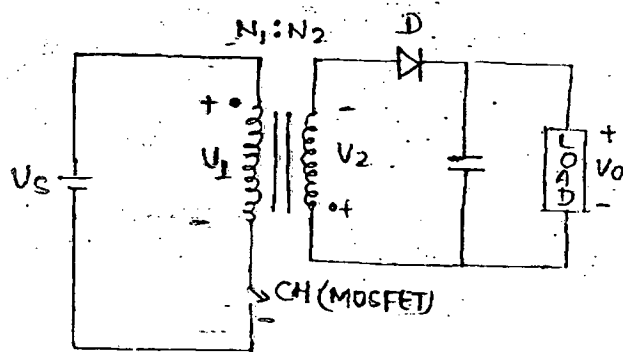(1) Flyback Converter → * It is derived from Buck-Boost Converter.

* It is also known as isolated Buck-Boost Converter.

* Here in place of the inductor we use X_{mer} here because both store magnetic energy.



mode (1) → $0 \leq t \leq T_{on}$

CH → ON

X_{mer} stores energy in the form of magnetic field

$$V_1 = V_s$$

$$V_2 = \frac{N_2}{N_1} V_1$$

$$V_2 = \frac{N_2}{N_1} V_s$$


mode (2) → $T_{on} \leq t \leq T$

CH → OFF, D → ON

$$V_2 = -V_o$$

$$V_1 = \frac{N_1}{N_2} V_2$$

$$V_1 = -\frac{V_o}{\frac{N_1}{N_2}}$$

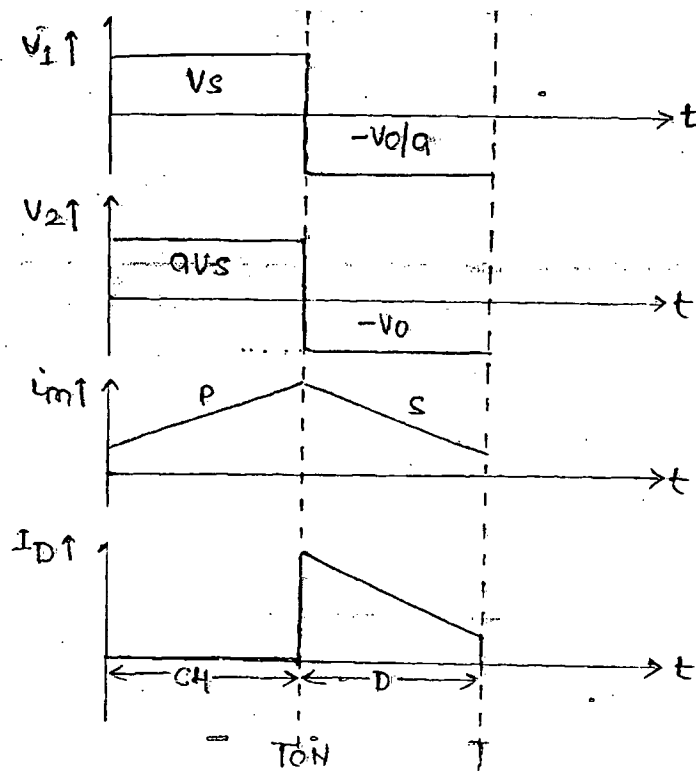

$$V_o = q \cdot \frac{\alpha V_s}{(1-\alpha)}$$


The peak forward blocking voltage of CH switch = $V_s + \frac{V_o}{q}$

Note:- The o/p voltage of front end rectifier without voltage doubling = V_m

V_m (Peak value of ac i/p Vol.)

o/p voltage of front end rectifier with voltage doubling = $2V_m$

35/59

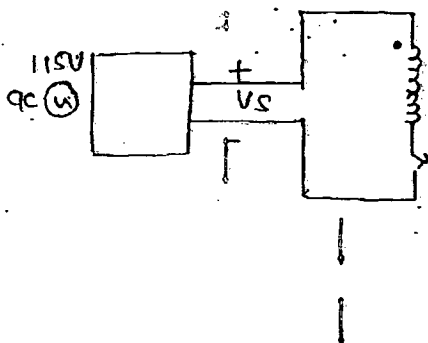

$$V_s = 115\sqrt{2} \text{ (Peak)}$$

$$V_o = q \cdot \frac{\alpha V_s}{1-\alpha}$$

$$35 = \frac{q \times 0.3 \times 115\sqrt{2}}{(1-0.3)}$$


$$q = 0.5$$

$$\text{Forward blocking Vol.} = V_s + \frac{V_o}{q} = 115\sqrt{2} + \frac{35}{0.5} = 232 \text{ V}$$

Forward converter → * It is derived from Buck Conf.

Case (1) → Ideal Xmer;

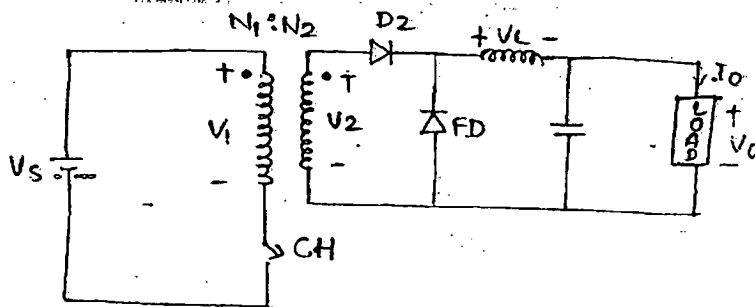- $I_m = 0$
- No Losses
- No leakage inductance



Mode (1) → $0 \leq t \leq T_{ON}$

CH → ON
 $V_1 = V_s$, $V_2 = \frac{N_2}{N_1} V_1$


$V_2 = q \cdot V_s$

17. Applying KVL;

$-V_2 + V_L + V_o = 0$

$V_L = V_2 - V_o$

$V_L = qV_s - V_o$

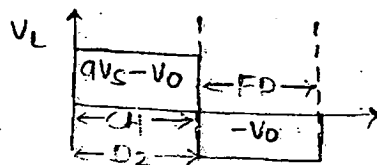

Mode (2) → $T_{ON} \leq t \leq T$

CH → OFF, D2 → OFF

FD → ON

$+V_L + V_o = 0$

$V_L = -V_o$

$(V_L)_{avg} = 0$

$(qV_s - V_o) T_{ON} - V_o T_{OFF} = 0$


$qV_s T_{ON} = V_o T$

$V_o = q \cdot \frac{T_{ON}}{T} \cdot V_s$

$V_o = q \cdot V_s$


Qqse(2) → For non-ideal X_{mer}

→ $I_m \neq 0$

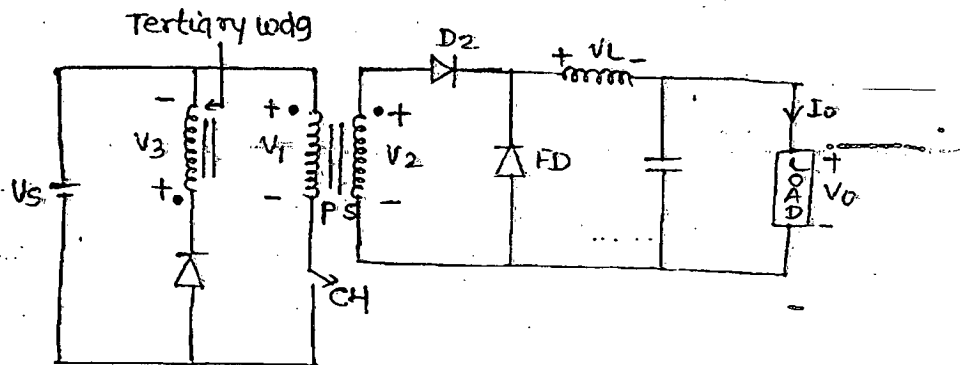

* Tertiary wdg is used to provide a path to magnetising current when the CH switch becomes off.

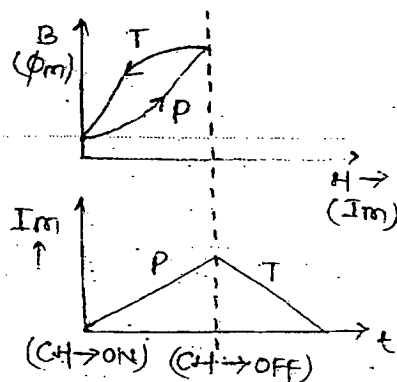* Here X_{mer} magnetises through 1° wdg & demagnetises through 3° wdg.



* In Flyback & Forward Converters the X_{mer} is excited only in one dirⁿ.

It is called unidirectional core excitation.

③ Push-Pull Converter → * In this con^r the X_{mer} core is excited bi-directionally.

Therefore it is called bidirectional core excitation.

Fig is que (5/59)

$$V_o = 2.9 \alpha V_s$$


$$V_o = 2 \cdot \frac{N_2}{N_1} \cdot \frac{T_{ON}}{T_{ON} + T_{OFF}} \cdot V_s$$

Chopper Question

1/52

0 to Ton

$$V_{dc} = 60V$$

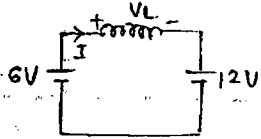

KVL →

$$-60 + V_L + 12 = 0$$

$$V_L = 48$$

$$L \frac{dI}{dt} = 48$$

$$\int_{I_{min}}^{I_{max}} dI = \frac{48}{L} \int_0^{T_{on}} dt$$

$$\Delta I = \frac{48}{L} T_{on} = 0.48A$$

2/52

$$I_0 = \frac{\alpha V_s}{R} = \frac{0.8 \times 100}{10} = 8A$$

$$(I_D)_{avg} = I_0 \left(\frac{T_{off}}{T} \right) = I_0 (1 - \alpha) = 8(1 - 0.8) = 1.6A$$

3/52

$$(t_{on})_{min} = \frac{2V_s}{R} = \frac{2 \times 100}{250} = 0.8s \quad \pi\sqrt{LC} = 140\mu s$$

4/52

$$(V_o)_{min} = V_s \frac{(T_{on})_{eff}}{T} = 47.5V$$

5/52

$$(I_m)_{max} = I_0 + V_s \sqrt{\frac{C}{L}} = 12A, (I_A)_{max} = I_0 = 10A$$

Conventional question →

(a) (i) $(T_{on})_{eff} = T_{on} + 2t_{cm}$
 $= 1075\mu s$

(ii) $t_{cm} = \frac{CV_s}{I_0} = 137.5\mu s$

(b) $(I_m)_{max} = I_0 + V_s \sqrt{\frac{C}{L}} : (I_A)_{max} = I_0$

(c) $t_{CA} = \frac{\pi}{2} \sqrt{LC} = 49\mu s$ & $t_{cm} = \frac{CV_s}{I_0}$


(d) $2t_{cm} = 275\mu s$

(e)

$$V_c = \frac{V_s}{t_{cm}} t - V_s$$

$$= \frac{220}{137.5} (150) - 220$$

$$V_c = 20V$$

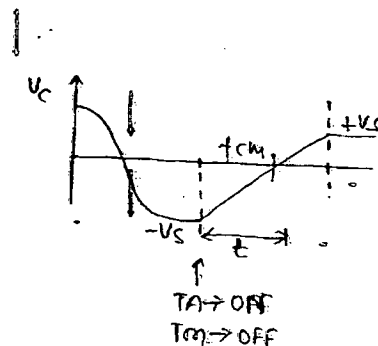


$$(8.) T_{ON} = T_Q \ln \left[1 + m(e^{T/\tau_Q} - 1) \right]$$

$$(10.) t_{min} \leq t \leq t_{max}$$

$$\pi\sqrt{LC} \leq t \leq \frac{3\pi}{2}\sqrt{LC}$$

$$50\mu s \leq t \leq 75\mu s$$

$$(11) I_0 + I_p \sin \omega t$$

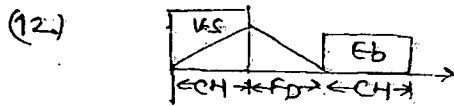

$$V_0 = \frac{V_{sf} t_r + E_b t_r}{t_r + t_f + t_o}$$

$$(13.) I_{m\lambda} = I_0 + \frac{\lambda I_c}{2}$$

$$= 5 + \frac{1.6}{2}$$

$$= 5.8A$$

1- ϕ Half wave Rectifier

Rectifier Load	V_o	V_{or}	t_c	I_o	Other
R	$\frac{V_m}{2\pi} (1 + \cos \alpha)$	$\frac{V_m}{2\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$	$\frac{\pi}{\omega}$	$(I_s)_{avg} = \frac{V_m}{2\pi R} (1 + \cos \alpha)$	$I_{sr} = I_{or} = \frac{V_{or}}{R}$ $V_{sr} = \frac{V_m}{\sqrt{2}}$
R-L	$\frac{V_m}{2\pi} (\cos \alpha - \cos \beta)$	$\frac{V_m}{2\sqrt{\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$	$\frac{2\pi - \beta}{\omega}$	$I_o = \frac{V_m \sin(\omega t - \phi) + K e^{-\frac{R}{L}t}}{ Z }$	$K = \frac{-V_m \sin(\alpha - \phi)}{ Z } e^{-\frac{R}{L}\alpha}$
R-L + F.D.	$\frac{V_m}{2\pi} (1 + \cos \alpha)$	$\frac{V_m}{2\sqrt{\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$	$\frac{\pi}{\omega}$		$PF = \frac{P_o}{V_{sr} I_{sr}}$
RE	$(V_o)_{avg} = \frac{1}{2\pi} \left[V_m (\cos \alpha - \cos \beta) + E (2\pi + \alpha - \beta) \right]$		$\frac{\pi + 2\theta_1}{\omega}$	$\frac{1}{2\pi R} \left[V_m (\cos \alpha - \cos \beta) - E (\theta_2 - \alpha) \right]$	(1) $PF = \frac{I_{or}^2 R + E I_o}{V_{sr} I_{sr}}$ (2) $I_{or} = \left[\frac{1}{2\pi} \int_{\alpha}^{\theta_2} \left(\frac{V_m \sin \omega t - E}{R} \right)^2 dt \right]^{1/2}$ (3) PIV of thy. $= V_m + E$ $\theta_1 = \sin^{-1} \left(\frac{E}{V_m} \right)$ $\theta_2 = \pi - \theta_1$

1-φ Fully Controlled Con^r

Rectifier load	V_o	V_{or}	t_c	Other
R load	$\frac{V_m}{\pi}(1+\cos\alpha)$	$\frac{V_m}{\sqrt{2}\pi} \left[(\pi-\alpha) + \frac{1}{2}\sin 2\alpha \right]^{1/2}$	$\frac{\pi}{\omega}$	(1) $PF = \frac{1}{\sqrt{2}} \left[(\pi-\alpha) + \frac{1}{2}\sin 2\alpha \right]^{1/2}$ (2) Mid pt. Rect PIV = $2V_m$ Bridge PIV = V_m
RL (discontinuous)	$\frac{V_m}{\pi}(\cos\alpha - \cos\beta)$	$\frac{V_m}{\sqrt{2}\pi} \left[(\beta-\alpha) + \frac{1}{2}(\sin 2\alpha - \sin 2\beta) \right]^{1/2}$	$\frac{2\pi-\beta}{\omega}$	
RL (continuous)	$\frac{2V_m}{\pi} \cos\alpha$	$\frac{V_m}{\sqrt{2}\pi} \left[\pi + \frac{\pi}{2} \right]^{1/2} = \frac{V_m}{\sqrt{2}} = V_{sr}$	$\frac{\pi-\alpha}{\omega}$	(1) $I_{sr} = I_o$ High inductive load (2) Cond ⁿ angle of thy. = π rad's
RE	$\frac{1}{\pi} [V_m(\cos\alpha - \cos\theta_2) + E(\pi + \alpha - \theta_2)]$		$\frac{\pi + 2\theta_1}{\omega}$	(1) $I_{avg} = \frac{I_o}{2}$, $(I_r)_{rms} = \frac{I_o}{\sqrt{2}}$ (2) $I_o = \frac{1}{\pi R} [V_m(\cos\alpha - \cos\theta_2) - E(\theta_2 - \alpha)]$ (2) $V_o = \frac{V_m \sin \omega t - E}{R}$
RE continuous	$\frac{2V_m}{\pi} \cos\alpha$	$PF = \frac{2\sqrt{2}}{\pi} \cos\alpha$, $THD = 0.4634$ $P = \frac{2V_m}{\pi} I_o \cos\alpha = V_o I_o$		$I_{SR} = I_o$ $I_{SI} = \frac{2\sqrt{2}}{\pi} I_o$, $PDF = \cos\alpha$
RE discontinuous	$\frac{1}{\pi} [V_m(\cos\alpha - \cos\beta) + E_b(\pi + \alpha - \beta)]$	$P = \frac{2V_m}{\pi} I_o \cos\alpha$ $Q = V_o I_o + \omega n \alpha$ $FF = \frac{\pi}{2\sqrt{2}} \cdot \frac{1}{\cos\alpha}$		$I_{SI} = \frac{2\sqrt{2}}{\pi} I_o$, $PDF = \cos\alpha$ $g = \frac{2\sqrt{2}}{\pi}$, $I_{SN} = \frac{2\sqrt{2} I_o}{\pi}$

1 ϕ semi-converter

$$* V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$* V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right]^{1/2}$$

Condⁿ angle of each thy = $\pi - \alpha$

$$* (I_T)_{avg} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)$$

$$* (I_T)_{RMS} = I_o \left(\frac{\pi - \alpha}{2\pi} \right)^{1/2}$$

Condⁿ angle of FD = α

$$* (I_{FD})_{avg} = I_o \left(\frac{\alpha}{\pi} \right)$$

$$* (I_{FD})_{RMS} = I_o \left(\frac{\alpha}{\pi} \right)^{1/2}$$

$$* I_{sr} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$

with dc motor
(RLE load)

Discontinuous Condⁿ:-

(1.) $\beta < \pi$;

$$* V_o = \frac{1}{\pi} \left[(\cos \alpha - \cos \beta) V_m + E_b (\pi + \alpha - \beta) \right]$$

(2.) $\beta > \pi$;

$$* V_o = \frac{1}{\pi} \left[V_m (1 + \cos \alpha) + E_b (\pi + \alpha - \beta) \right]$$

Continuous Condⁿ $\rightarrow$

$$* V_o = \frac{V_m}{\pi} (1 + \cos \alpha)$$

$$* I_{sr} = I_o \left(\frac{\pi - \alpha}{\pi} \right)^{1/2}$$

$$* I_{SN} = \frac{2\sqrt{2}}{\pi} I_o \cos \frac{\alpha}{2}$$

$$* |S_1| = \frac{2\sqrt{2}}{\pi} I_o \cos \frac{\alpha}{2}$$

$$* FPF = \cos \frac{\alpha}{2}$$

$$* g = \frac{2\sqrt{2} \cos \alpha/2}{\sqrt{(\pi - \alpha)\pi}}$$

$$* pf = \frac{\sqrt{2} (1 + \cos \alpha)}{\sqrt{\pi (\pi - \alpha)}}$$

$$* THD = \left[\frac{\pi (\pi - \alpha)}{8 \cos^2 \alpha/2} - 1 \right]^{1/2}$$

$$* P = V_{sr} I_{sr} \cos \alpha/2$$

$$* Q = V_o I_o \tan \frac{\alpha}{2}$$

spec: 1 ϕ -full converter

$$i_s = \frac{4I_0}{\pi} \sin(n\omega t + \phi_n)$$

$$I_{s1} = \frac{2\sqrt{2}}{\pi} I_0$$

$$\text{PDF} = \cos \alpha$$

$$g = \frac{2\sqrt{2}}{\pi}$$

$$\text{PF} = \frac{2\sqrt{2}}{\pi} \cos \alpha$$

$$\text{THD} = 48.94\%$$

1 ϕ semi-converter

$$\frac{4I_0}{\pi} \sin \frac{n\pi}{2} \sin(n\omega t + \phi_n)$$

$$\frac{2\sqrt{2}}{\pi} I_0 \cos \frac{\alpha}{2}$$

$$\cos \frac{\alpha}{2}$$

$$\frac{2\sqrt{2} \cos \alpha/2}{\sqrt{\pi(\pi-\alpha)}}$$

$$\frac{2\sqrt{2}(1+\cos \alpha)}{\sqrt{\pi(\pi-\alpha)}}$$

$$\left[\frac{\pi(\pi-\alpha)}{8 \cos^2 \frac{\alpha}{2}} \right]^{1/2}$$

3 ϕ full con π

$$\frac{4I_0}{\pi} \sin \frac{n\pi}{2} \sin(n\omega t + \phi_n)$$

$$\frac{2\sqrt{2} I_0 \sin \frac{\pi}{3}}{\pi} = \frac{\sqrt{6}}{\pi} I_0$$

$$\cos \alpha$$

$$\frac{3}{\pi}$$

$$\frac{3}{\pi} \cos \alpha$$

$$31\%$$

Specific: Current Commutated Chopper (class B)

$(I_{Tm})_{peak}$	I_o
$(I_{TA})_{peak}$	$I_p = V_s \sqrt{\frac{C}{L}}$
* Cond'n time of the TA	$\pi \sqrt{LC}$
* t_{cm}	$\frac{V_{RC}}{I_o}$
* ^{total} Time req. to turn off T_m after T_A is ON	$t_1 + t_2 = \pi \sqrt{LC} + \sqrt{LC} \sin^{-1} \left(\frac{I_o}{I_p} \right)$
* $(T_m)_{min} =$	
$t_{min}(\min)$ time req. to turn off the T_m after T_A ON	$\pi \sqrt{LC}$
* t_{max}	$\frac{3\pi}{2} \sqrt{LC}$
* Reverse Vol.	$V_R = V_s \cos \left[\sin^{-1} \left(\frac{I_o}{I_p} \right) \right]$
* $(T_{ON})_{min}$	
* PIV of F_D	
* PIV of T_m	
* t_{CA}	
* commutation interval	
* $(T_{ON})_{eff}$	
* V_o	
* $(V_o)_{min}$	

Voltage Commutated Chopper (Class D)

$I_o + I_p = I_{ot} \sqrt{\frac{C}{L}}$	
I_o	
$2t_{cm}$	
$\frac{V_{SC}}{I_o}$	$R \ln 2$ (with R load)
$\pi \sqrt{LC}$	
$2V_s$	
V_s	
$\frac{\pi}{2} \sqrt{LC}$	
$2t_{cm}$	
$T_{ON} + 2t_{cm}$	
$V_s \frac{(T_{ON})_{eff}}{T}$	
$V_s (\pi \sqrt{LC} + 2t_{cm}) \neq$	