

Lecture - 4



ques:- Find RMS value of following waveforms

$$(1) \quad V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} v^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (V_m \sin \omega t)^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} V_m^2 \left(\frac{1 - \cos 2\omega t}{2} \right) dt}$$

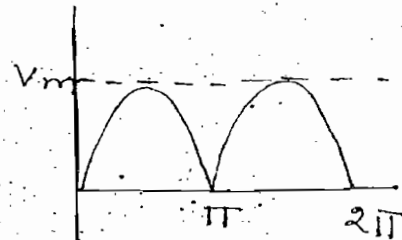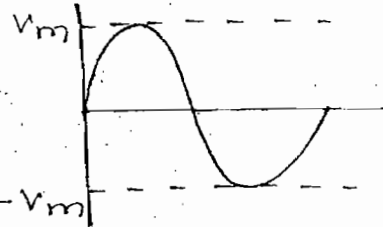
$$\Rightarrow \boxed{V_{RMS} = \frac{V_m}{\sqrt{2}}}$$



(11)


$$\boxed{V_{RMS} = \frac{V_m}{\sqrt{2}}}$$

→ $V_{RMS} = \frac{V_m}{2}$

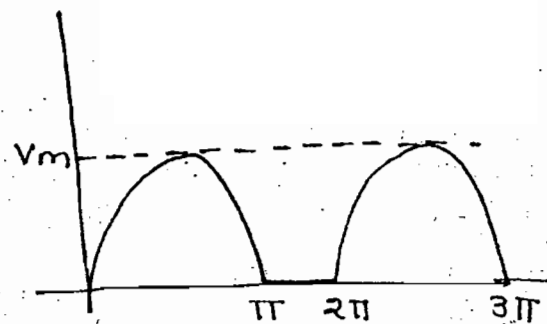


→ $V_{RMS} = \frac{V_m}{\sqrt{2}}$
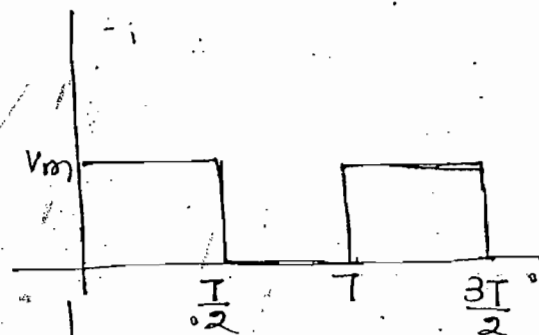
$$V_{RMS} = \sqrt{\frac{1}{T} \left[\int_0^{T/2} V_m^2 dt + \int_{T/2}^T 0 dt \right]}$$



→ Note: $V_{RMS} = \frac{V_m}{\sqrt{2}}$

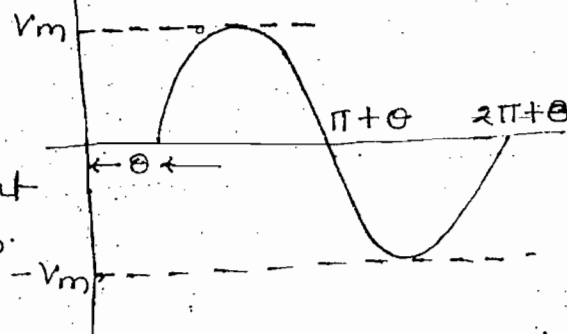
RMS value is independent on the ^{position of} starting of waveform. But it depends on the shape of waveform.




→ $V_{RMS} = \frac{V_m}{\sqrt{3}}$

$0 < t < T \quad y = mx$

$\Rightarrow V = \frac{V_m}{T} t$

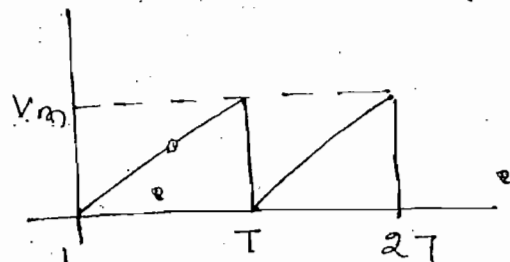


→ $V_{RMS} = V_m$

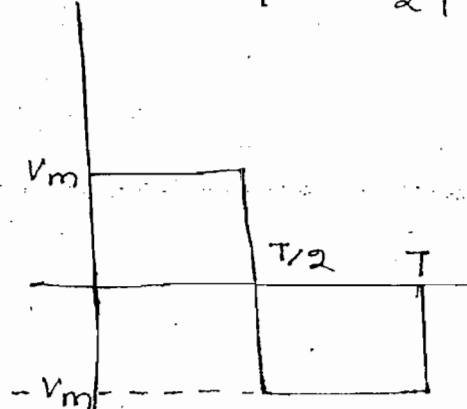

$$\rightarrow V_{RMS} = \sqrt{\frac{1}{T} \int_0^T V^2 dt}$$

$$V_{RMS} = \sqrt{\frac{1}{T} \int_0^T \left(\frac{V_m}{T} t\right)^2 dt}$$
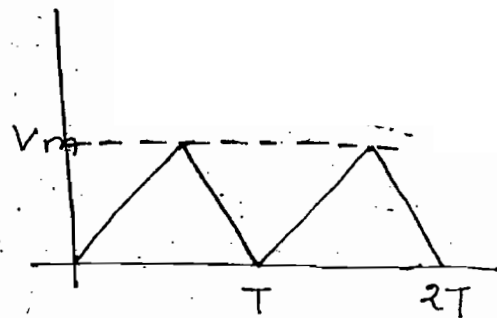
$$\Rightarrow \boxed{V_{RMS} = \frac{V_m}{\sqrt{3}}}$$




$$\rightarrow 0 < t < 2$$

$$y = mx$$

$$m = \frac{y_2 - y_1}{x_2 - x_1} = \frac{10 - 0}{2 - 0}$$

$$= 5$$

$$V = 5t$$

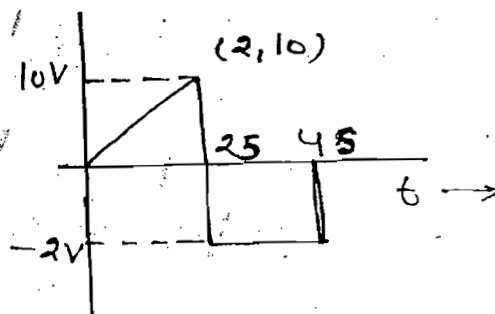


$$V_{RMS} = \sqrt{\frac{1}{4} \left[\int_0^2 (5t)^2 dt + \int_2^4 (-2)^2 dt \right]}$$

$$\Rightarrow V_{RMS} = \sqrt{\frac{1}{4} \left[25 \left(\frac{t^3}{3} \right)_0^2 + (4t)_2^4 \right]}$$

$$\Rightarrow V_{RMS} = 4$$

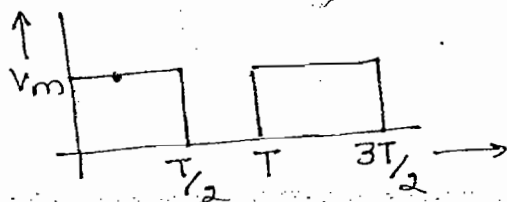ques:- Find power dissipation in the resistor for the given voltage waveform



$$(a) P_{av} = \frac{P_{peak}}{\sqrt{2}}$$

$$(b) P_{av} = \frac{P_{peak}}{2}$$

$$(c) P_{av} = P_{peak}$$

$$(d) P_{av} = \frac{P_{peak}}{\sqrt{3}}$$

Soln:- B. $P_{peak} = \frac{V_m^2}{R}$

$$P_{av} = \frac{V_{RMS}^2}{R} = \frac{(V_m/\sqrt{2})^2}{R} = \frac{V_m^2}{2R} = \frac{P_{peak}}{2}$$

Note:-

$$\rightarrow P_{RMS} = \frac{V_{RMS}^2}{R}$$

**

$$\rightarrow \frac{P_{DC}}{P_{AC}} = \frac{I_{av}^2 R}{I_{RMS}^2 R}$$

ques:- Find RMS value for the following function

$$V(t) = 3 + \sin 3t + \cos t$$

Soln:-


$$V_{RMS} = \sqrt{V_{RMS_1}^2 + V_{RMS_2}^2 + V_{RMS_3}^2 + \dots + V_{RMS_n}^2}$$

[Used when different wave are present]

$$\Rightarrow V_{RMS} = \sqrt{(3)^2 + \left(\frac{1}{\sqrt{2}}\right)^2 + \left(\frac{1}{\sqrt{2}}\right)^2}$$


$$\Rightarrow \boxed{V_{RMS} = \sqrt{10}}$$

Average Value:-

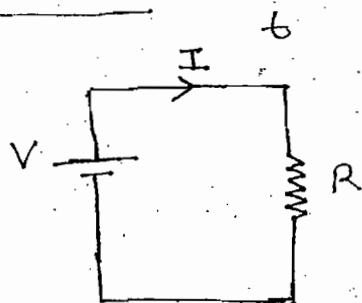

$$I = \frac{V}{R}$$

$$Q = It \rightarrow DC$$

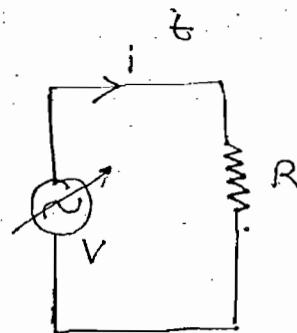

$$i = \frac{V}{R}$$




$$Q = it \rightarrow AC$$

$$\boxed{Q_{AC} = Q_{DC}}$$

→ Average value is defined based on charge transfer in the circuit

→ The voltage at which charge transfer in AC circuit is equal to charge transfer in DC circuit is called as V_{avg} provided both AC and DC circuit having equal value of resistance and operated for same time.

Symmetrical Wave :-

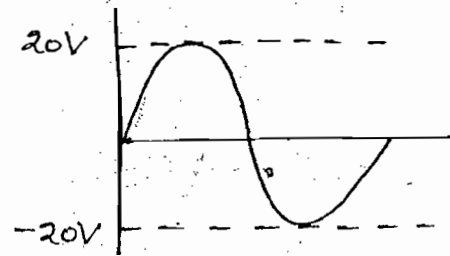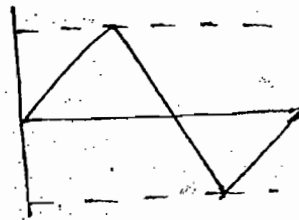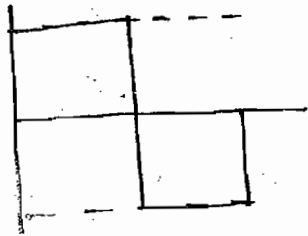

$$\text{Form factor} = \frac{V_{RMS}}{V_{av}}$$

→ Avg. Value for complete symmetrical wave = 0


→ Hence we can find Average value only for half cycles for symmetrical waveform

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V dt$$

[For current and voltage waveform]

Unsymmetrical Wave :-

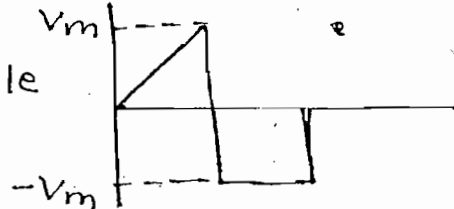→ Finding average value of unsymmetrical wave angle of complete cycle is considered




$$V_{av} = \frac{1}{2\pi} \left[\int_0^{\pi} V dt + \int_{\pi}^{2\pi} V dt \right]$$

ques:- Find Avg. value of following waveforms


$$\rightarrow V_{av} = \frac{1}{\pi} \int_0^{\pi} V \, d\omega t$$

$$V_{av} = \frac{1}{\pi} \int_0^{\pi} V_m \sin \omega t \, d\omega t$$

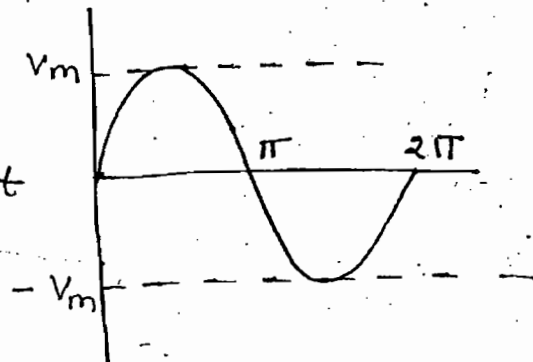
$$\Rightarrow \boxed{V_{av} = \frac{2V_m}{\pi}}$$




$$\rightarrow V_{av} = \frac{V_m}{2}$$

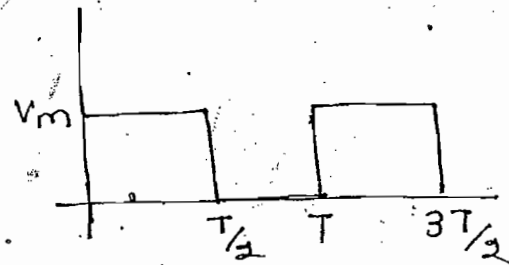

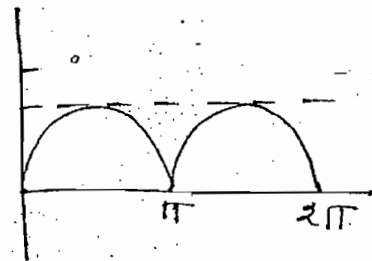
$$\rightarrow V_{av} = \frac{2V_m}{\pi}$$



$$\rightarrow V_{av} = \frac{V_m}{\pi}$$

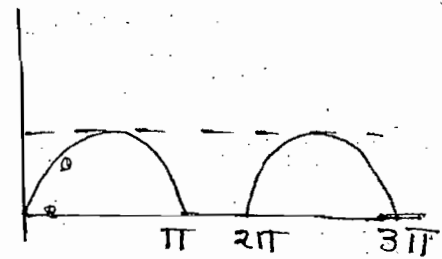


$$\rightarrow V_{RMS} = V_{av} = V_m$$

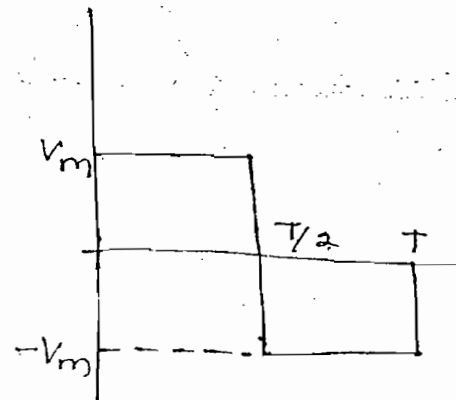


$$\rightarrow V_{av} = \frac{1}{4} \left[\int_0^2 10 dt + \int_2^4 20 dt \right] = 15 \text{ V}$$


$$V_{av} = 15$$

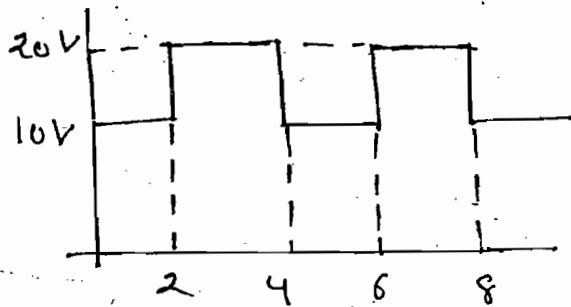


$$\rightarrow V_{av} = \frac{V_m}{2}$$

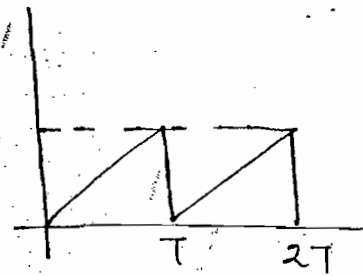

$$\rightarrow V_{av} = \frac{V_m}{2}$$

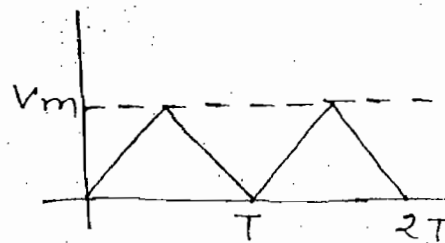

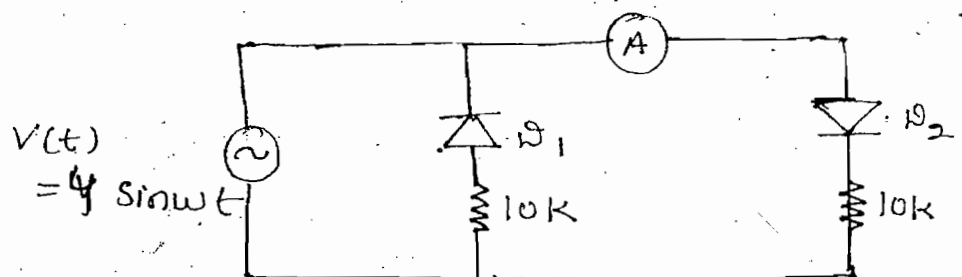Ques - When the circuit is having ideal diodes and avg. value of indicating ammeter. Find reading of ammeter.



Soln - $V_{av} = \frac{V_m}{\pi} = \frac{4}{\pi}$

$$I_{av} = \frac{V_{av}}{10 \times 10^3} = \frac{4/\pi}{10 \times 10^3}$$

$$\Rightarrow I_{av} = \frac{0.4}{\pi} \text{ mA}$$

Note:-

Form factor = $\frac{V_{RMS}}{V_{av}} = \frac{V_m/\sqrt{2}}{2V_m/\pi} = 1.11$ → For sine wave




Peak factor = $\frac{V_m}{V_{RMS}} = \frac{V_m}{V_m/\sqrt{2}} = \sqrt{2}$

Power System:-

11 kV, 33 kV, 66 kV, 132 kV, 220 kV] → basis of form factor

→ To justify above shape of waveform form factor and peak factor concepts are introduced

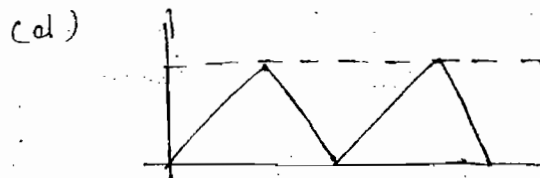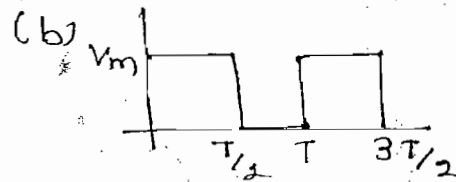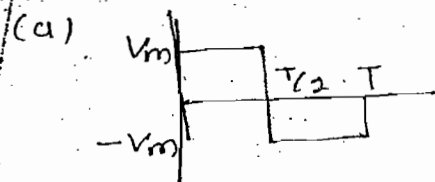Ques:- Which of the following waveforms have form factor = peak factor?



Soln:- (a) $V_{RMS} = V_{av} = V_m$
Form factor = 1
Peak factor = 1

(b) $V_{RMS} = \frac{V_m}{\sqrt{2}}$, $V_{av} = \frac{V_m}{2}$
Form factor = $\frac{V_{RMS}}{V_{av}} = \sqrt{2}$
Peak factor = $\frac{V_m}{V_{RMS}} = \sqrt{2}$

(c) $V_{RMS} = V_m = V_{av}$
 $= V$
Form factor = 1
Peak factor = 1

(d) $V_{rms} = \frac{V_m}{\sqrt{3}}$
 $V_{av} = V_m/2$
Form factor = $2/\sqrt{3}$
Peak factor = $\sqrt{3}$

AC Source Across Resistor!-

$$i(t) = \frac{V(t)}{R}$$

$$i(t) = \frac{V_m \sin \omega t}{R}$$

$$\Rightarrow \boxed{i(t) = I_m \sin \omega t}$$

$$P(t) = V(t) i(t)$$

$$P(t) = V_m \sin \omega t I_m \sin \omega t$$

$$\boxed{P(t) = \frac{V_m I_m}{2} (1 - \cos 2\omega t)}$$

$$P_{av} = \frac{1}{2\pi} \int_0^{2\pi} P(t) d\omega t$$

$$\Rightarrow \boxed{P_{av} = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}} = V_{RMS} I_{RMS}}$$

eg!- $f = 50 \text{ Hz or C/sec}$

$$\Rightarrow f_p = 100 \text{ Hz} \quad (\text{Power of frequency})$$

→ When voltage or current completes one cycle then power completes two cycle.


AC source across Inductor!-

$$V = L \frac{di}{dt}$$



$$\therefore V(t) = L \frac{d}{dt} (I_m \sin \omega t)$$

$$V(t) = \omega L I_m \cos \omega t \quad (X_L = \omega L)$$

$$V(t) = V_m \sin (\omega t + 90)$$

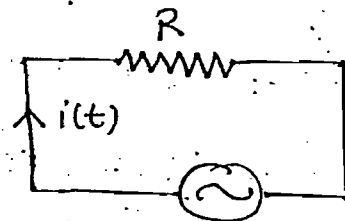

$$V(t) = V_m \sin \omega t$$

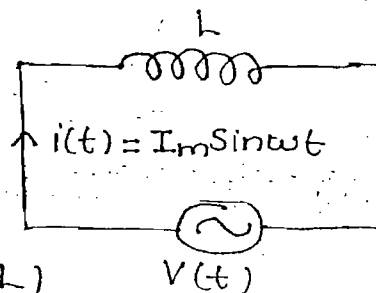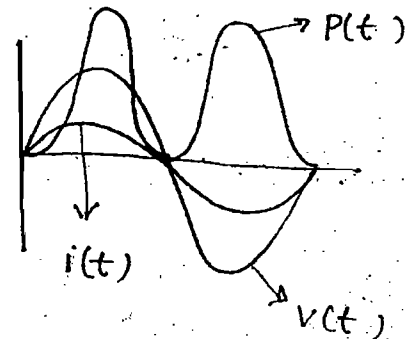

$$\begin{aligned}
 P &= I^2 R = VI \cos \theta \\
 Q_L &= X^2 I = VI \sin \theta \\
 S &= I^2 Z = VI^* \rightarrow \text{conjugate}
 \end{aligned}$$

eg:- $V = 10 \angle 40^\circ$

$$S = Vi$$

$$\Rightarrow S = 10 \angle 40 \quad 5 \angle 15$$

$$\Rightarrow S = 50 \angle 55$$

Wrong


$$i = 5 \angle 15^\circ$$

$$S = Vi^*$$

$$\Rightarrow S = 10 \angle 40 \quad 5 \angle -15$$

$$\Rightarrow S = 50 \angle 25$$

Correct

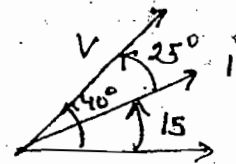



R-C Series Circuit:-

By KVL

$$V = V_R \angle 0^\circ + V_C \angle -90^\circ$$


$$\Rightarrow IZ = IR - jIX_C$$

$$\Rightarrow \boxed{Z = R - jX_C}$$

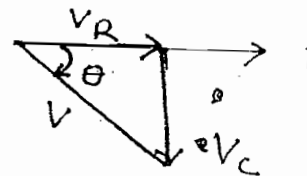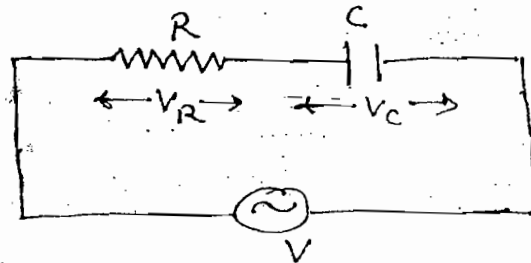


$$\boxed{V = \sqrt{V_R^2 + V_C^2}}$$
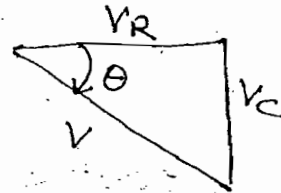
$$\boxed{\theta = \tan^{-1} \left(\frac{-V_C}{V_R} \right)}$$



$$\boxed{Z = \sqrt{R^2 + X_C^2}}$$
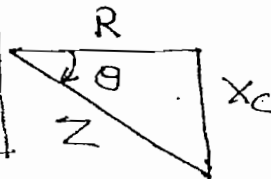
$$\boxed{\theta = \tan^{-1} \left(\frac{-X_C}{R} \right)}$$



$$S = \sqrt{P^2 + Q^2}$$

$$\theta = \tan^{-1}\left(\frac{-Q_c}{P}\right)$$

$$I^2 R = P$$


$$I^2 Z = S$$

$$Q_c = I^2 X_c$$

Power Factor :-

$$\text{Power Factor} = \cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S} \rightarrow \text{leading}$$

Ques:- Find voltage across inductor

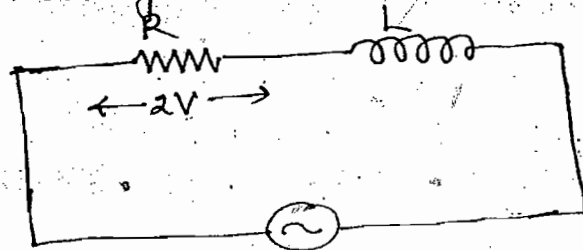

20V (RMS)

Soln:-


$$V_m = 10$$

$$V_{RMS} = \frac{10}{\sqrt{2}} = V$$

$$V = \sqrt{V_R^2 + V_L^2}$$

$$\Rightarrow \frac{10}{\sqrt{2}} = \sqrt{2^2 + V_L^2}$$
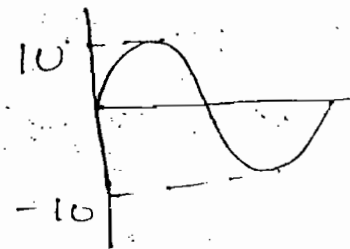
$$\Rightarrow V_L = \sqrt{46} \text{ V}$$



Ques:- Find circuit element for given voltage and current equations



$$V(t) = 9 \sin(t + 45^\circ)$$

$$i(t) = 3 \sin(t - 45^\circ)$$

Soln:-

$$X_L = \frac{V}{i}$$

$$X_L = \frac{9/\sqrt{2}}{3/\sqrt{2}}$$

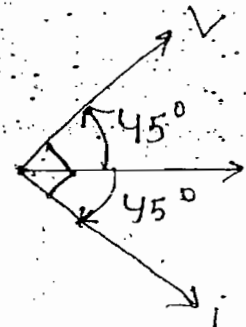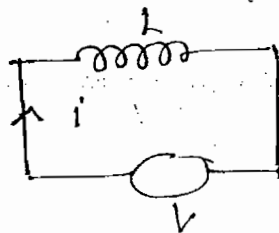

$$\Rightarrow X_L = 3 = \omega L \Rightarrow L = 3 \quad (\because \omega = 1)$$

Ques:- Find circuit element for given voltage and current equations

$$V(t) = 9 \sin(t + 30^\circ)$$

$$i(t) = 3 \sin(2t + 60^\circ)$$

Note:-

By using above equations it is not possible to design the network since frequency of voltage and current are unequal.

Ques:- Find active power, reactive power and apparent power by using following equations:-

$$V(t) = 9 \sin(t + 30^\circ)$$

$$i(t) = 3 \sin(t + 60^\circ)$$

Soln:-

$$P = VI \cos \theta$$

$$\Rightarrow P = \frac{9}{\sqrt{2}} \cdot \frac{3}{\sqrt{2}} \cos 30^\circ$$

$$\Rightarrow P = 27 \times \frac{\sqrt{3}}{2}$$

→ R-C circuit (I leading)

$$Q_c = VI \sin \theta$$

$$\Rightarrow Q_c = \frac{9}{\sqrt{2}} \frac{3}{\sqrt{2}} \sin 30^\circ$$

$$\Rightarrow Q_c = \frac{27}{4}$$


$$S = \sqrt{P^2 + Q_c^2} =$$

Alternate Way:-

$$Z = V/I$$

$$Z = \frac{9/\sqrt{2}}{3/\sqrt{2}}$$

$$Z = 3$$

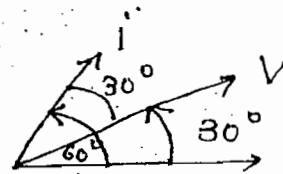

$$\cos \theta = \frac{R}{Z}$$

$$\Rightarrow \cos 30^\circ = R/3 \Rightarrow R = 3 \cos 30^\circ$$

$$X_c = \sqrt{Z^2 - R^2}$$


$$P = I^2 R = (3/\sqrt{2})^2 R$$

$$Q_c = I^2 X_c = (3/\sqrt{2})^2 X_c$$

Ques:- Find ammeter reading and power factor of the ckt shown

$$V_1(t) = 10 \sin t$$

$$V_2(t) = 10\sqrt{5} \sin 2t$$

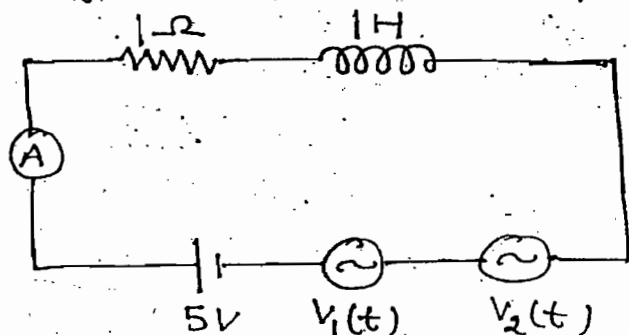

Soln:- When multiple sources are present then at one time only one source is activated.

For V_1 $X_{L1} = \omega_1 L = 1$

$$Z_1 = \sqrt{R^2 + X_{L1}^2} = \sqrt{1^2 + 1^2} = \sqrt{2}$$

$$i_1 = \frac{V_1}{Z_1} = \frac{10/\sqrt{2}}{\sqrt{2}} = 5$$

For V_2 $X_{L2} = \omega_2 L = 2$

$$Z_2 = \sqrt{1^2 + 2^2} = \sqrt{5}$$

$$i_2 = \frac{V_2}{Z_2} = \frac{10\sqrt{5}/\sqrt{2}}{\sqrt{5}} = \frac{10}{\sqrt{2}}$$

For V_3 $\omega C \rightarrow \omega = 0$

$$i_3 = \frac{V_3}{R} = \frac{5}{1} \Rightarrow i_3 = 5$$


When same frequency are present then directly add them. But above question different frequency are present. Hence use general formula: $i = \sqrt{i_1^2 + i_2^2 + i_3^2} = 10A$ Ans

For power factor use power triangle not impedance triangle (same reason)

$$P.F = \cos \theta = P/S \Rightarrow \cos \theta = i^2 R / V_i = \frac{iR}{V}$$

$$V = \sqrt{V_1^2 + V_2^2 + V_3^2} = \sqrt{\left(\frac{10}{\sqrt{2}}\right)^2 + \left(\frac{10\sqrt{5}}{\sqrt{2}}\right)^2 + 5^2} = 6.55$$

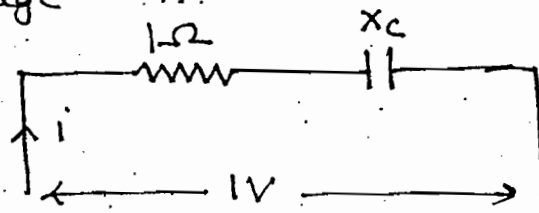Ques:- In the circuit shown power dissipation in the resistor is 500 mW. Find angle of current w.r.t source voltage



Soln:- $P = i^2 R \Rightarrow P = \left(\frac{V}{Z}\right)^2 R$

$$\Rightarrow P = \frac{V^2}{R^2 + X_c^2} R$$

$$\Rightarrow \frac{500}{1000} = \frac{1^2}{1^2 + X_c^2} \quad (1) \Rightarrow X_c = 1$$

$$Z = R - jX_c$$

$$Z = 1 - j1 \Rightarrow \theta = \tan^{-1}\left(\frac{-1}{1}\right) = -45^\circ$$

$$i = \frac{V \angle 0}{Z \angle -45} = \frac{V \angle +45}{Z} \Rightarrow \theta = 45^\circ \text{ Ans}$$



R-L-C Series Circuit:-

By KVL

$$V = V_R \angle 0 + V_L \angle 90 + V_C \angle -90$$


$$\Rightarrow IZ = IR + jIX_L - jX_C$$
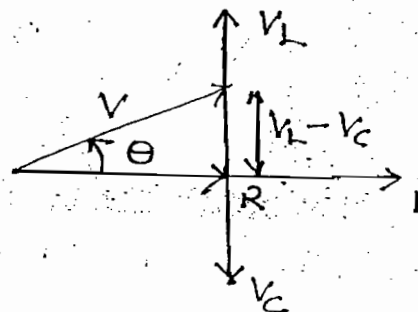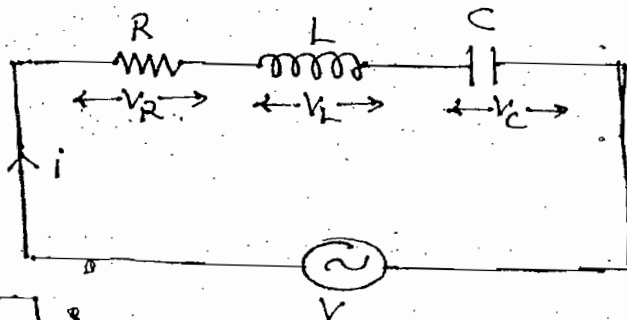
$$\Rightarrow \boxed{Z = R + j(X_L - X_C)}$$




$$\boxed{V = \sqrt{V_R^2 + (V_L - V_C)^2}}$$
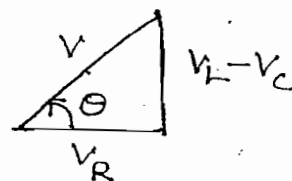
$$\boxed{\theta = \tan^{-1}\left(\frac{V_L - V_C}{V_R}\right)}$$




$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$
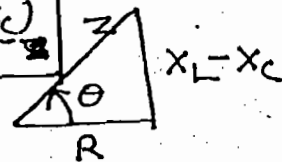
$$\theta = \tan^{-1} \left(\frac{X_L - X_C}{R} \right)$$



$$S = \sqrt{P^2 + (Q_L - Q_C)^2}$$
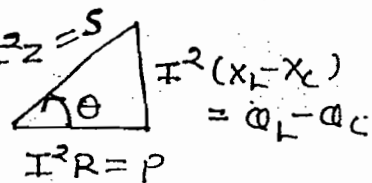
$$\theta = \tan^{-1} \left(\frac{Q_L - Q_C}{P} \right)$$



Power factor :-


$$\cos \theta = \frac{V_R}{V} = \frac{R}{Z} = \frac{P}{S}$$

(i) If $V_L > V_C \rightarrow$ lagging power factor

(ii) If $V_L < V_C \rightarrow$ leading power factor

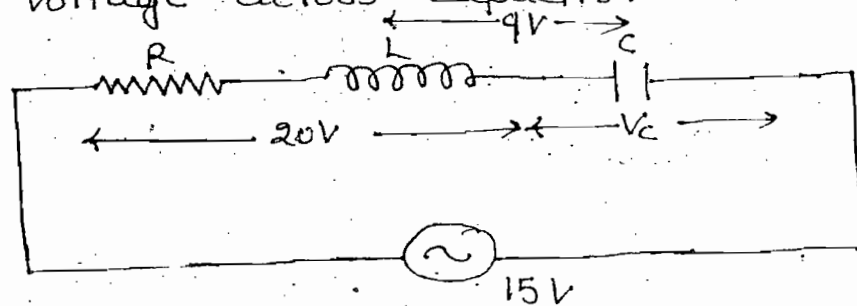(iii) If $V_L = V_C \rightarrow$ Unity power factor

Ques:- Find voltage across capacitor of circuit shown



(a) 7

(b) 25

(c) 7 or 25

(d) 20

Soln:-

$$V_L - V_C = 9V$$

$$V = 15V$$

$$V = \sqrt{V_R^2 + (V_L - V_C)^2}$$

$$\Rightarrow 15^2 = V_R^2 + 9^2$$

$$V_R = \sqrt{225 - 81} = 12V$$

$$20 = \sqrt{V_R^2 + V_L^2} = \sqrt{12^2 + V_L^2} \Rightarrow V_L = 16$$

$$V_L - V_C = 9 \Rightarrow V_C = 7V, \text{ Ans}$$

d/

