

## Thyristor Commutation Techniques

Commutation means bringing the thyristor from forward conduction state to forward blocking state i.e. it is a process of turning off a thyristor.

### Remember:

- Commutation technique use resonant LC or underdamped RLC circuits to force the current or voltage of SCR to zero to turn-off the device.

### Types of Commutation

1. **Natural Commutation (Line Commutation):** Here nature of supply take cares of commutation process.


**Example:** Phase controlled rectifier and AC voltage controller.

2. **Force Commutation:** Here external component bring anode current to zero forcefully.

**Example:** Chopper and inverter.

### Types of Force Commutation Circuit

#### (a) Class A (Load Commutation):

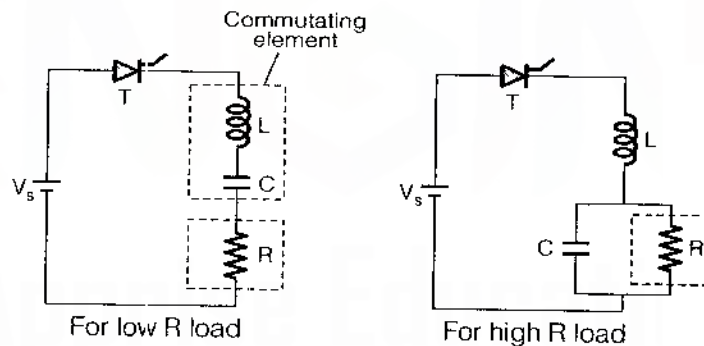

Over all circuit must be underdamped.

i.e.

$$R^2 < \frac{4L}{C}$$


- This type of commutation is possible in dc circuit not in ac circuit.
- Load commutation is also called resonant commutation or self commutation.

#### (b) Class B Commutation:

- It is also called as current commutation or resonant pulse commutation.

Assumption:

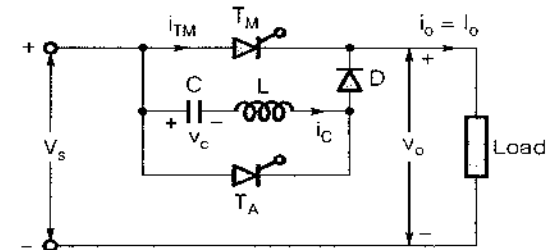- Load current is assumed constant.
- The capacitor is initially charged with  $V_s$  volt with left plate positive and right plate negative.




Here,

$T_A$  = Auxiliary thyristor and

$T_M$  = Main thyristor

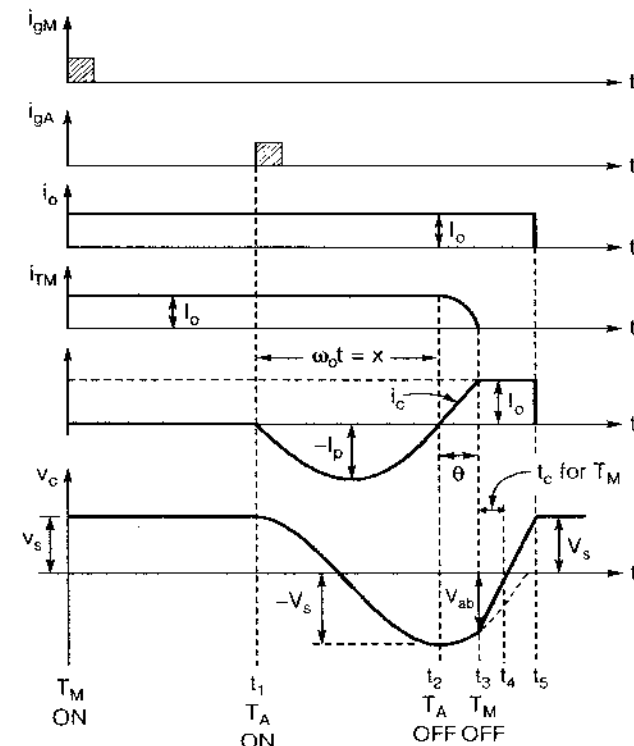- Commutation process is initiated by switching ON the auxiliary thyristor.



□ Resonant current

$$i_c = -V_s \sqrt{\frac{C}{L}} \sin \omega_o t = -I_p \sin \omega_o t$$

□ Peak resonant current

$$I_p = V_s \sqrt{\frac{C}{L}}$$

□ Circuit turn-off time for main thyristor ( $T_m$ )

$$t_c = C \frac{V_{ab}}{I_o}$$



□ Reverse voltage across main thyristor

$$V_{ab} = V_s \cos \left[ \sin^{-1} \left( \frac{I_o}{I_p} \right) \right]$$

Conduction time of auxiliary thyristor =  $\pi \sqrt{LC}$

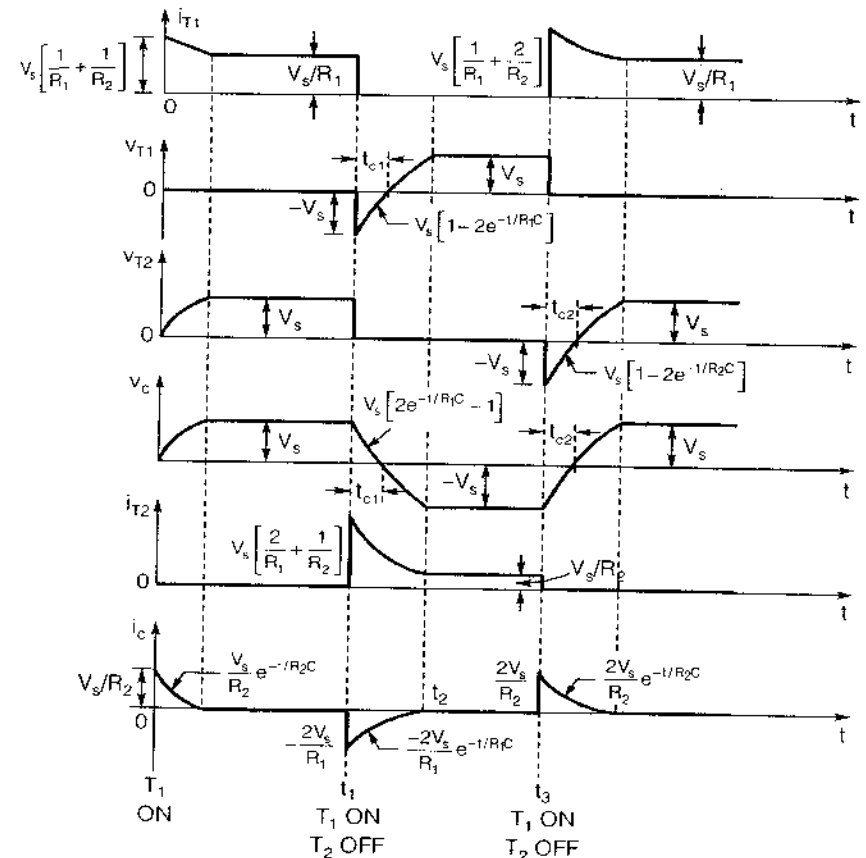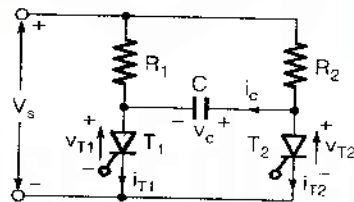(c) **Class C Commutation:**

It is also called, complementary impulse commutation.



Case-1: When  $T_1$  is turned ON at  $t = 0$ ,  $T_2$  is off

□ The charging current (when capacitor is initially uncharged)

$$i_c = \frac{V_s}{R_2} e^{-t/R_2 C}$$

□ Voltage across capacitor C

$$v_c(t) = V_s (1 - e^{-t/R_2 C})$$

Case-2: When  $T_1$  is to be turned OFF,  $T_2$  is turned ON at  $t_1$

❑ The charging current

$$i_c(t) = -\frac{2V_s}{R_1} e^{-t/R_1 C}$$

❑ Voltage across capacitor C

$$v_c(t) = V_s \cdot [2e^{-t/R_1 C} - 1]$$

Note: In last equation, time is measured from the instant  $t_1$ .

❑ Peak current through  $T_1$

$$I_{T1,P} = V_s \left[ \frac{1}{R_1} + \frac{2}{R_2} \right]$$

❑ Peak current through  $T_2$

$$I_{T2,P} = V_s \left[ \frac{2}{R_1} + \frac{1}{R_2} \right]$$

❑ Circuit turn-off time for  $T_1$

$$t_{c1} = R_1 C \ln(2)$$


❑ Circuit turn-off time for  $T_2$

$$t_{c2} = R_2 C \ln(2)$$

**(d) Class D Commutation:**

Also known as:

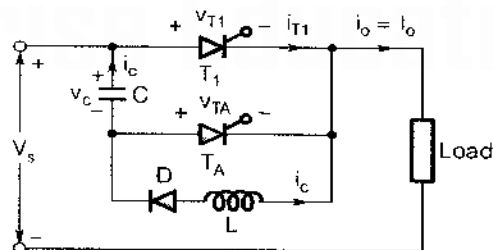
1. Impulse commutation
2. Voltage commutation
3. Auxiliary commutation
4. Parallel-capacitor commutation



where,

$T_1$  = Main thyristor

$T_A$  = Auxiliary thyristor

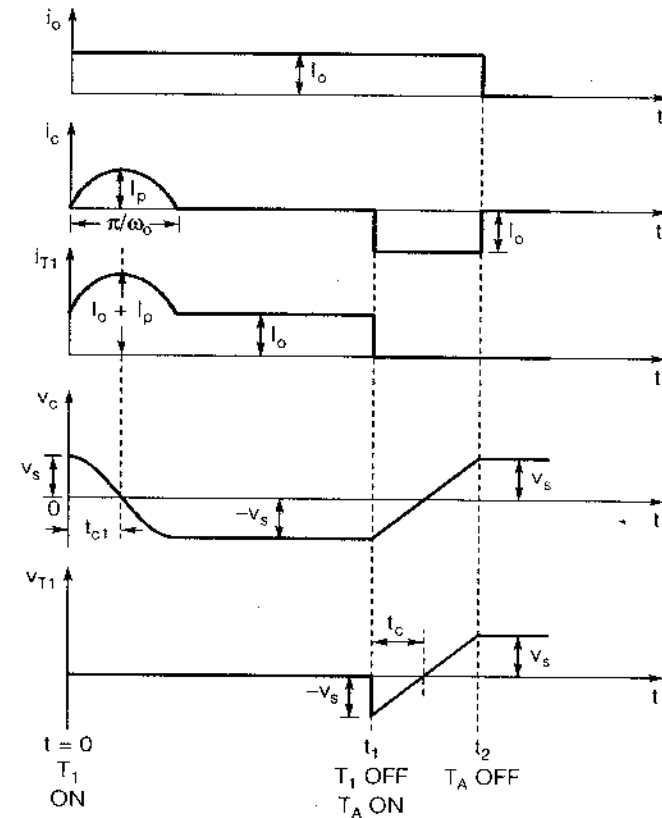

**Assumption:**

1. Load current is assumed constant.
2. The capacitor is initially charged to  $V_s$  as shown in figure.

❑ Capacitor current

$$i_c = I_p \sin \omega_0 t$$

$$I_p = V_s \sqrt{\frac{C}{L}} \sin \omega_0 t$$

❑ Peak value of current through capacitor

$$I_p = V_s \sqrt{\frac{C}{L}}$$

- Peak value of current through main thyristor ( $T_1$ )

$$(I_p)_{T_1} = I_p + I_o$$

- Peak value of current through auxiliary thyristor ( $T_A$ ) =  $I_o$
- Circuit turn-off time for main thyristor ( $T_1$ )

$$t_c = C \frac{V_s}{I_o}$$

- Circuit turn-off time for auxiliary thyristor ( $T_A$ )

$$t_{c1} = \frac{\pi}{2\omega_o} = \frac{\pi}{2} \sqrt{LC}$$

■ ■ ■ ■ ■