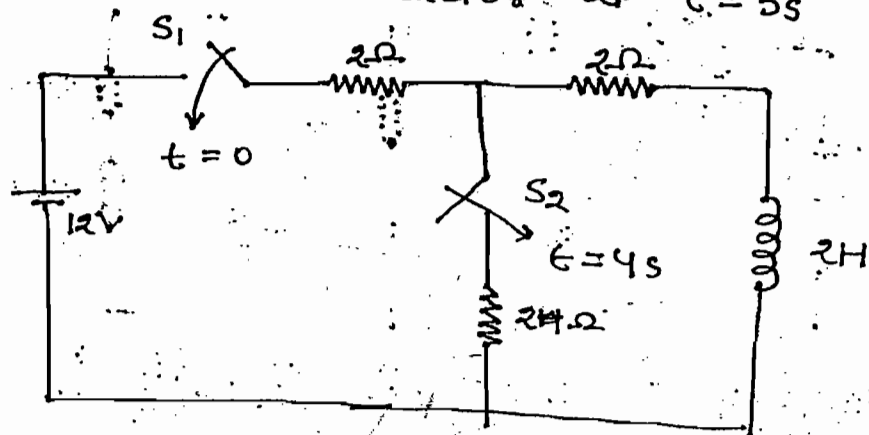


Lecture -10

Ques:- Find current in the inductor at $t = 5s$



Soln:-

S_1

$$i(t) = \frac{V}{R} (1 - e^{-Rt/L})$$

$$i(t) = \frac{12}{4} (1 - e^{-2t}) \Rightarrow i(t) = 3(1 - e^{-2t})$$

$t > 4s$, S_1 and $S_2 \rightarrow$ operated

$$i(t) = [i(0^+) - i(\infty)]e^{-Rt/L} + i(\infty)$$

$$\Rightarrow i(t) = [i(4) - i(\infty)]e^{-R'(t-4)} + i(\infty) \quad (1)$$

$t = 4$

$$i(4) = 3[1 - e^{-2(4)}] \approx 2.99A$$

$$t = \infty$$

$$i(\infty) = 2A$$



Time constant for $T > 4s$

$$R' = 3 \quad (11)$$


From - (1) & (11)

$$i(t) = [2.99 - 2]e^{-3/2(t-4)} + 2$$

$$t = 5 \text{ sec.}$$

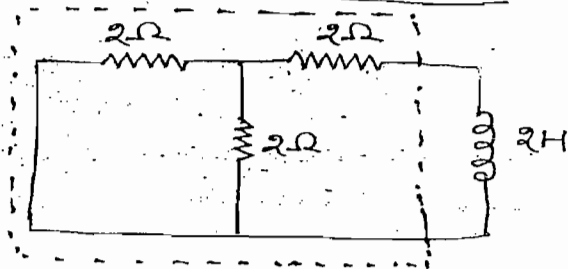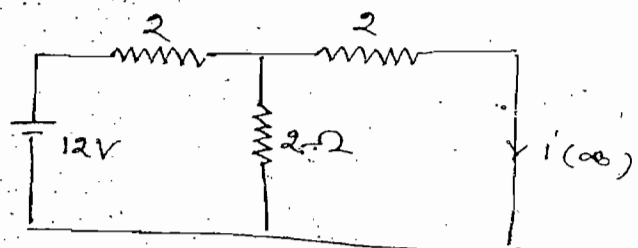

Prob:-

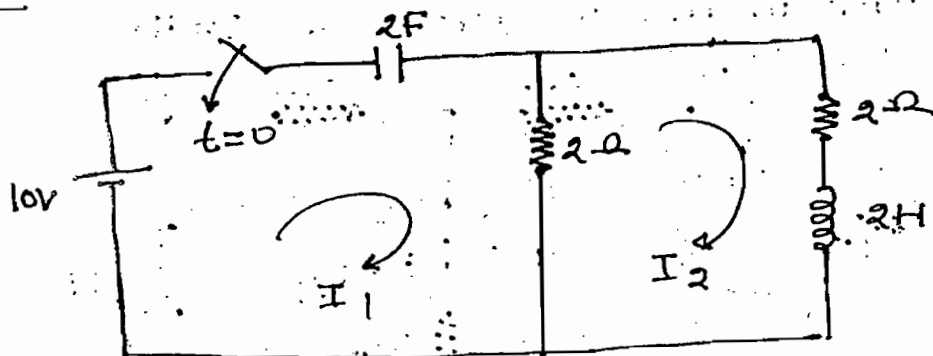

Find $i_1(0^+)$, $i_2(0^+)$, $V_C(0^+)$, $\frac{di_1(0^+)}{dt}$, $\frac{di_2(0^+)}{dt}$, $\frac{d^2 i_1(0^+)}{dt^2}$,

$$\frac{d^2 i_2(0^+)}{dt^2}$$

Soln:-

At $t=0^-$

$$i_1(0^-) = 0 \quad i_2(0^-) = 0 \quad V_C(0^-) = 0$$

At $t=0^+$

$$i_2(0^+) = 0 \quad V_C(0^+) = 0 \quad i_1(0^+) = \frac{10}{2} = 5A$$

$$(1) \quad 4I_2 + 2 \frac{di_2}{dt} - 2I_1 = 0 \quad \rightarrow t=0^+$$

$$4(0) + 2 \frac{di_2}{dt} - 2(5) = 0$$

$$\Rightarrow \frac{di_2}{dt} = 5 A/s$$

$$-10 + \frac{1}{2} \int i_1 dt + 2(I_1 - I_2) = 0$$

Diff. w.r.t. t

$$0 + \frac{i_1}{2} + 2 \left[\frac{di_1}{dt} - \frac{di_2}{dt} \right] = 0 \quad \text{--- (II)}$$

$$\Rightarrow \frac{5}{2} + 2 \left[\frac{di_1}{dt} - 5 \right] = 0$$

$$\Rightarrow \frac{5}{2} - 10 + 2 \frac{di_1}{dt} = 0$$

$$\Rightarrow \frac{di_1}{dt} = \frac{15}{4} = 3.75 A/s$$

Diff eq-(i) w.r.t t

$$4 \frac{di_2}{dt} + 2 \frac{d^2 i_2}{dt^2} - 2 \frac{di_1}{dt} = 0$$

$$\Rightarrow \frac{d^2 i_2}{dt^2} = -6.25 \text{ A/s}^2$$

Diff. eq-(ii), w.r.t t

$$\frac{1}{2} \frac{di_1}{dt} + 2 \left[\frac{d^2 i_1}{dt^2} - \frac{d^2 i_2}{dt^2} \right] = 0$$

$$\Rightarrow \frac{d^2 i_1}{dt^2} = -7.18 \text{ A/s}^2$$

RLC Series Circuit with AC Excitation :-

By KVL

$$V = IR + L \frac{di}{dt} + \frac{1}{C} \int i dt$$

Diff w.r.t t

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{i}{C}$$


Divide both sides by L we get

$$\boxed{\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0}$$

$$\left(s^2 + \frac{R}{L} s + \frac{1}{LC} \right) i = 0 \quad \left(\because \frac{d}{dt} = s \right)$$

$$s_1, s_2 = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - \frac{4}{LC}}}{2}$$
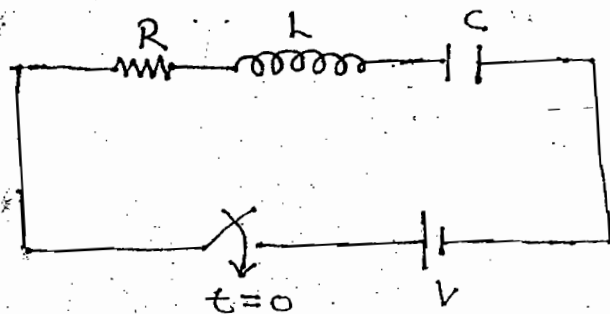
$$\boxed{s_1, s_2 = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$



Case - (I) :-

$$\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$$

overdamping

$$\alpha = -\frac{R}{2L} \quad \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \left(\frac{1}{LC}\right)}$$

$$i(t) = C_1 e^{(\alpha-\beta)t} + C_2 e^{(\alpha+\beta)t}$$

Case - (II) :-

$$\left(\frac{R}{2L}\right)^2 = \frac{1}{LC} \rightarrow \text{Critical damping}$$

$$i(t) = (C_1 + C_2 t) e^{\alpha t}$$

Case - (III) :-

$$\left(\frac{R}{2L}\right)^2 < \frac{1}{LC} \rightarrow \text{Under damping}$$

$$\alpha = -\frac{R}{2L}$$

$$\beta = \sqrt{\frac{1}{LC} - \left(\frac{R}{2L}\right)^2}$$

$$i(t) = (C_1 \cos \beta t + C_2 \sin \beta t) e^{\alpha t}$$

$$\text{Damping Coefficient} = \frac{R}{2L}$$

$$\text{Time Constant} = \frac{1}{\text{Damping Coefficient}} = \frac{2L}{R}$$

Case - (IV) :-

$$R = 0 \rightarrow \text{Underdamping}$$

$$\alpha = 0, \quad \beta = \frac{1}{\sqrt{LC}}$$


$$i(t) = C_1 \cos \beta t + C_2 \sin \beta t$$

RLC Parallel Circuit with AC Excitation:-

$$I = \frac{V}{R} + C \frac{dV}{dt} + \frac{1}{L} \int V dt$$

Diff. w.r.t. t
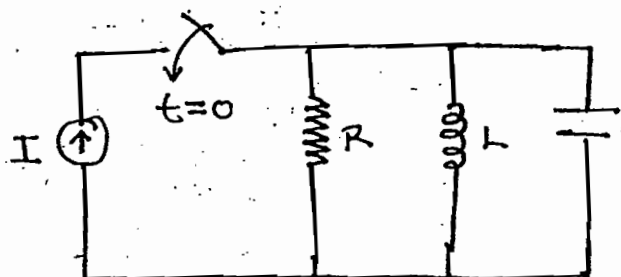
$$0 = \frac{1}{R} \frac{dV}{dt} + C \frac{d^2 V}{dt^2} + \frac{V}{L}$$



Divide the whole equation by C , we get

$$\frac{d^2 V}{dt^2} + \frac{1}{RC} \frac{dV}{dt} + \frac{V}{LC} = 0$$

$$\left(D^2 + \frac{1}{RC} D + \frac{1}{LC} \right) V = 0, \quad (\because D = \frac{d}{dt})$$

$$D_1, D_2 = \frac{-\frac{1}{RC} \pm \sqrt{\left(\frac{1}{RC}\right)^2 - \frac{4}{LC}}}{2}$$

$$D_1, D_2 = \frac{-1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

Case - (I) :-

$$\left(\frac{1}{2RC}\right)^2 > \frac{1}{LC} \rightarrow \text{over damping}$$

$$\alpha = -\frac{1}{2RC}$$

$$\beta = \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$V(t) = C_1 e^{(\alpha - \beta)t} + C_2 e^{(\alpha + \beta)t}$$

Case - (II) :-

$$\left(\frac{1}{2RC}\right)^2 = \frac{1}{LC} \rightarrow \text{Critical damping}$$

$$V(t) = (C_1 + C_2 t) e^{\alpha t}$$

Case-(III) :-

$$\left(\frac{1}{2RC}\right)^2 < \frac{1}{LC} \rightarrow \text{Under damping}$$

$$\alpha = -\frac{1}{2RC}$$

$$\beta = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

$$V(t) = (C_1 \cos \beta t + C_2 \sin \beta t) e^{\alpha t}$$

$$\text{Damping coefficient} = \frac{1}{2RC}$$

$$\text{Time constant} = \frac{1}{\text{Damping coefficient}} = 2RC$$

Case-(IV) :-

$$G = 0$$

$$\frac{1}{R} = 0 \Rightarrow R = \infty$$

$\rightarrow$ Underdamping

$$\alpha = 0, \beta = \frac{1}{\sqrt{LC}}$$

$$V(t) = C_1 \cos \beta t + C_2 \sin \beta t$$

Note:-

1. Steady state current response of RLC series circuit with AC excitation = 0

2. At $t = \infty$,

$L \rightarrow$ Uncharged ($I = 0$)

$C \rightarrow$ Charged ($V_C = V$)

3.

$$\xi = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$\rightarrow$ Series

$\xi > 1 \rightarrow$ overdamping

$\xi < 1 \rightarrow$ Underdamping

$\xi = 1 \rightarrow$ Critical damping

$\xi = 0 \rightarrow$ Undamping

$$\zeta = \frac{1}{2R} \sqrt{\frac{L}{C}}$$

→ Parallel

4. For over and critical damping system no oscillations are present




$$\frac{1}{2R} \sqrt{\frac{L}{C}} \geq 1 \rightarrow \text{Parallel}$$

$$\frac{R}{2} \sqrt{\frac{C}{L}} \geq 1 \rightarrow \text{Series}$$

$$\zeta \geq 1$$

→ In the underdamping system more than 1 oscillation are present


$$\zeta < 1$$

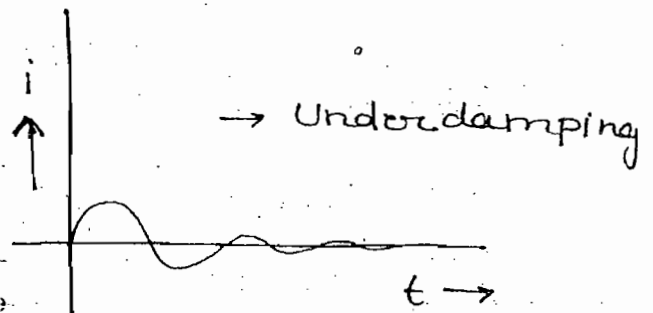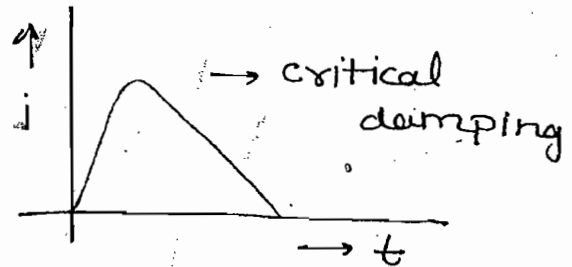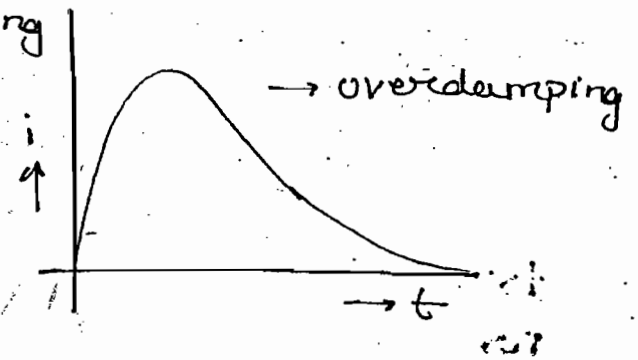

5. At $t = \infty$

L → Charged ($I_L = I$)

C → Uncharged ($V_C = 0$)

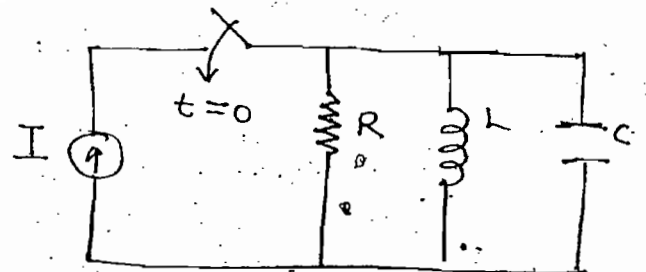


6. $t = \infty$

C_1 → Charged ($V_{C_1} = V$)

C_2 → Uncharged ($V_{C_2} = 0$)


L → Uncharged ($I_L = 0$)

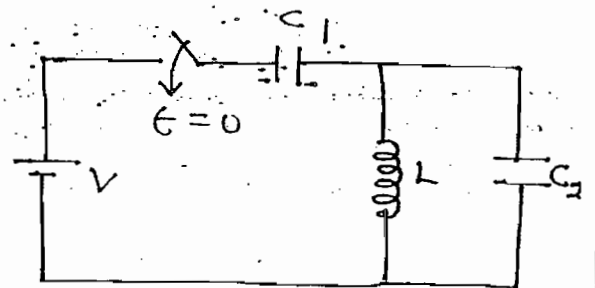



A.C Transients :-

→ DC transients intensity is more than intensity of AC transients

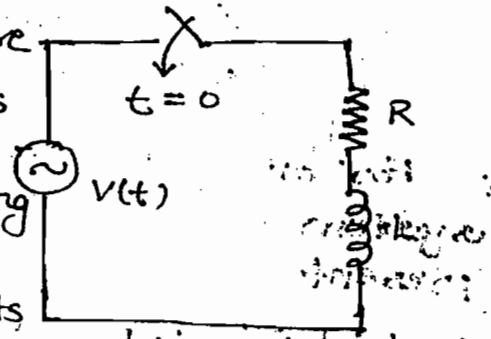→ Based on selection of operating frequency and switching operation and circuit elements it is possible to obtain transient free response. But in AC circuit it is not possible to obtain transient free response



$$V(t) = V_m \sin(\omega t + \theta)$$

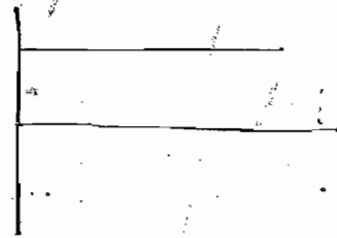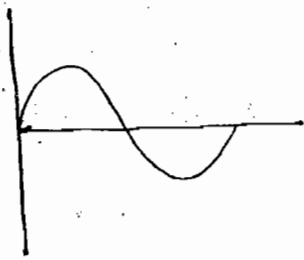

By KVL

$$V = iR + L \frac{di}{dt}$$

Divide both sides by L , we get

$$\frac{di}{dt} + \frac{R}{L} i = \frac{V}{L}$$

$$i(t) = C.F + P.I$$

↓
Transient Response

C.F :-

$$\frac{di}{dt} + \frac{R}{L} i = 0$$

$$\Rightarrow i(t) = A e^{-\frac{R}{L} t}$$

P.I → Steady state response

$$i = \frac{V}{Z \angle \alpha} = \frac{V L}{Z}$$

$$i(t) = \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$



$$X_L = \omega L$$

$$\alpha = \tan^{-1}\left(\frac{\omega L}{R}\right)$$

$$i(t) = C.F + P.I$$

$$i(t) = A e^{-\frac{R}{L}t} + \frac{V_m}{Z} \sin(\omega t + \theta - \alpha)$$

$$t = 0^- , \quad i = 0$$

$$t = 0^+ , \quad i = 0$$

$$0 = A + \frac{V_m}{Z} \sin(\theta - \alpha)$$

$$\Rightarrow \boxed{A = -\frac{V_m}{Z} \sin(\theta - \alpha)}$$

$$i(t) = \underbrace{-\frac{V_m}{Z} \sin(\theta - \alpha) e^{-\frac{R}{L}t}}_{T.R.} + \underbrace{\frac{V_m}{Z} \sin(\omega t + \theta - \alpha)}_{S.R.}$$

Case-(I) :-

$$V(t) = V_m \sin(\omega t + \theta) , \quad t = 0$$

$$\theta - \alpha = 0$$

$$\theta = \alpha \Rightarrow$$

$$\boxed{\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)}$$

→ Condition for transient free response

Case-(II) :-

$$V(t) = V_m \cos(\omega t + \theta) , \quad t = 0$$


$$\boxed{\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}}$$

→ condition for transient free response

Case-(III) :-

$$t = t_0^- \quad i = 0$$

$$t = t_0 \quad i = 0$$

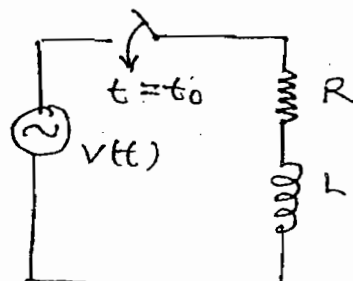

$$0 = A + \frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)$$

$$\Rightarrow A = -\frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha)$$

$$i(t) = \underbrace{-\frac{V_m}{Z} \sin(\omega t_0 + \theta - \alpha) e^{-R/L(t-t_0)}}_{\text{T.R}} + \underbrace{\frac{V_m}{Z} \sin(\omega t + \theta - \alpha)}_{\text{S.R}}$$

S.R

condition for transient free response for

Case-(III) is

$$V(t) = V_m \sin(\omega t + \theta), \quad t = t_0$$

$$\omega t_0 + \theta - \alpha = 0$$

$$\Rightarrow \omega t_0 = \alpha - \theta$$

$$\Rightarrow \omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$$

Case-(IV):-

$$V(t) = V_m \cos(\omega t + \theta), \quad t = t_0$$


$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta + \frac{\pi}{2}$$

	R_L	R_C
(i) $V(t) = V_m \sin(\omega t + \theta)$ $t = 0$	$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right)$	$\theta = \tan^{-1}(\omega C)$
(ii) $V(t) = V_m \cos(\omega t + \theta)$ $t = 0$	$\theta = \tan^{-1}\left(\frac{\omega L}{R}\right) + \frac{\pi}{2}$	$\theta = \tan^{-1}(\omega C) + \frac{\pi}{2}$
(iii) $V(t) = V_m \sin(\omega t + \theta)$ $t = t_0$	$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$	$\omega t_0 = \tan^{-1}(\omega C) - \theta$
(iv) $V(t) = V_m \cos(\omega t + \theta)$ $t = t_0$	$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$	$\omega t_0 = \tan^{-1}(\omega C) - \theta + \frac{\pi}{2}$

→ The above condition for series circuit for transient free response and also for parallel circuit.

→ In the RLC circuit it is not possible to obtain transient free response since circuit is having two energy storage element (simultaneously both charging and discharging action are present)

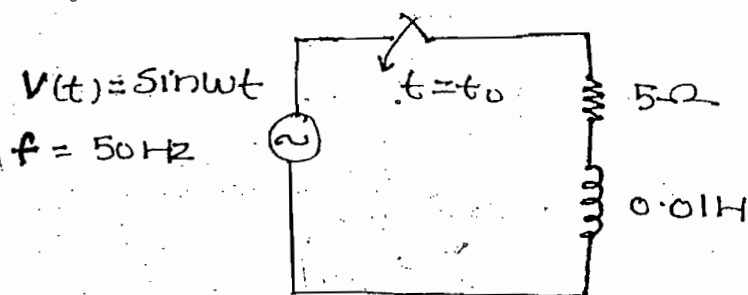ques:- Find t_0 to obtain transient free response



Soln:-

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta$$

$$t_0 = \frac{\tan^{-1}\left(\frac{\omega L}{R}\right)}{\omega} \rightarrow \text{rad} \rightarrow \text{rad/s}$$

$$t_0 = \frac{32.1 \times \pi / 180}{100\pi} = 1.78 \text{ ms, Ans}$$


Ques:- Find t_0 to obtain transient free response.

Soln:- $\omega t_0 = \tan^{-1}(\omega RC) - \theta + \frac{\pi}{2}$

$$\Rightarrow t_0 = \frac{\tan^{-1}(1) + \frac{\pi}{2}}{1}$$

$$\Rightarrow t_0 = \frac{\frac{\pi}{4} + \frac{\pi}{2}}{1} = \frac{3\pi}{4} \quad (\pi = \frac{22}{7})$$
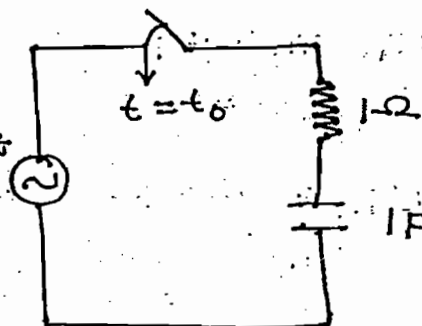
$$\Rightarrow t_0 = 7.35 \text{ s} \quad \text{Ans}$$



Laplace :-

$$1 \rightarrow \frac{1}{s}$$

$$e^{at} \rightarrow \frac{1}{s-a}$$

$$\sin \omega t \rightarrow \frac{\omega}{s^2 + \omega^2}$$

$$\cos \omega t \rightarrow \frac{s}{s^2 + \omega^2}$$

$$e^{at} \sin \omega t \rightarrow \frac{\omega}{(s-a)^2 + \omega^2}$$

$$e^{-at} \sin \omega t \rightarrow \frac{\omega}{(s+a)^2 + \omega^2}$$

$$e^{-at} \cos \omega t \rightarrow \frac{s+a}{(s+a)^2 + \omega^2}$$

$$\frac{df}{dt} \Rightarrow sF(s) - f(0)$$

$$u(t) \rightarrow \frac{1}{s}$$

$$\delta(t) \rightarrow 1$$

$$f(0^+) = \lim_{s \rightarrow \infty} sF(s) = \lim_{t \rightarrow 0} f(t)$$

→ Initial value theorem

Ques:- Find initial value of the following functions:-

$$F(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$$

Soln:- $f(0^+) = \lim_{s \rightarrow \infty} sF(s)$

$$= \lim_{s \rightarrow \infty} \frac{s \cdot s^2 \left(1 + \frac{1}{s}\right) \left(3 + \frac{3}{s}\right)}{s \cdot s^2 \left(2 + \frac{2}{s}\right) \left(4 + \frac{4}{s}\right)} = \frac{1}{2}$$

Ques:- Find initial value of the following function

$$f(t) = 3 + \delta(t)$$

Soln:- $F(s) = \frac{3}{s} + 1$

Note:-

For the above function initial value theorem can't be applied since to apply the initial value theorem denominator power should be greater than Numerator power

Final Value Theorem:-

$$f(\infty) = \lim_{s \rightarrow 0} sF(s) = \lim_{t \rightarrow \infty} f(t)$$

Ques:- Find final value of the following function

(i) $F(s) = \frac{(s+1)(s+3)}{s(s+2)(s+4)}$

(ii) $f(t) = 3 + e^{2t}$

Soln:- (i) $f(\infty) = \lim_{s \rightarrow 0} sF(s)$

$$= \lim_{s \rightarrow 0} \frac{s(s+1)(s+3)}{s(s+2)(s+4)} = \frac{3}{8}$$

(ii) $f(t) = 3 + e^{2t}$

$$F(s) = \frac{3}{s} + \frac{1}{s-2}$$

$$V_c(t) = \frac{1}{C} \int_{-\infty}^t i dt$$

$$\Rightarrow V_c(t) = \frac{1}{C} \int_{-\infty}^{0^-} i dt + \frac{1}{C} \int_{0^-}^t i dt$$

$$\Rightarrow V_c(t) = V_c(0^-) + \frac{1}{C} \int_{0^-}^t i dt$$

At $t=0^+$

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i dt$$

$\underbrace{\int_{0^-}^{0^+} i dt}_{=0}$

$$V_c(0^+) = V_c(0^-) \quad \text{--- (I)}$$

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} i dt$$

$$V_c(0^+) = V_c(0^-) + \frac{1}{C} \int_{0^-}^{0^+} \delta(t) dt$$

Area = 1

$$\boxed{V_c(0^+) = \frac{1}{C}} \quad \text{--- (II)}$$

$$W_c(0^+) = \frac{1}{2} C V_c^2(0^+) = \frac{1}{2} C \left(\frac{1}{C}\right)^2$$

$$\boxed{W_c(0^+) = \frac{1}{2C}} \quad \text{--- (III)}$$



Note:-

→ From eq-(I) it is concluded that capacitor does not allow instantaneous changes for given i/p.

→ From eq-(II) & (III) it is concluded that capacitor allows instantaneous changes for current impulse function.

$$V(t) = i(t) R$$

$$V(s) = I(s) R$$

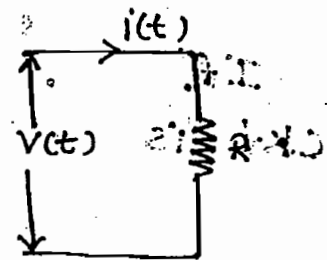
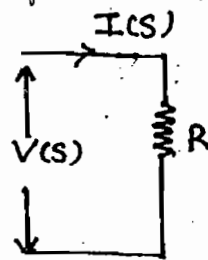


$$V = L \frac{di}{dt}$$

$$s = j\omega$$

$$V(s) = L [s I(s) - i(0^+)]$$
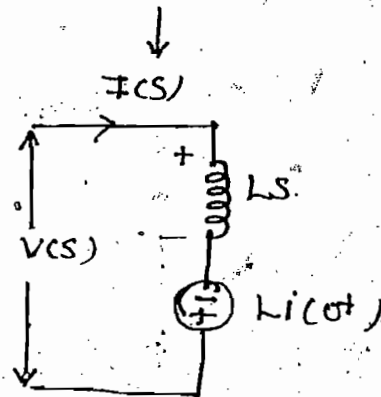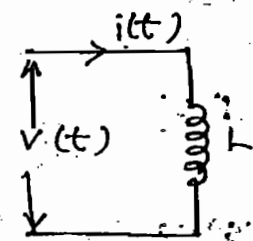
$$V(s) = L s I(s) - L i(0^+) \rightarrow \text{KVL}$$




$$Z(s) = \frac{V(s)}{I(s)}$$

$$\Rightarrow Z(s) = LS - \frac{L i(0^+)}{I(s)}$$

$$L s I(s) = V(s) + L i(0^+)$$

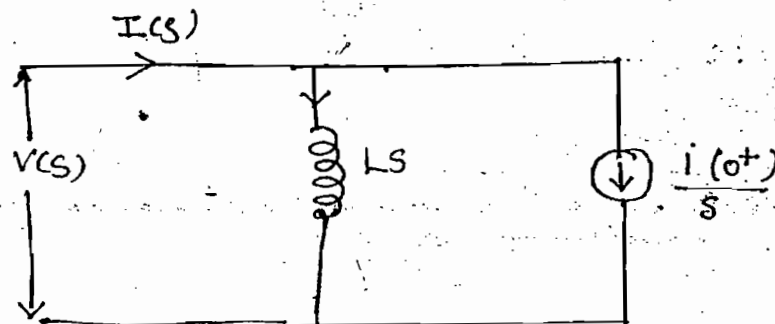
$$I(s) = \frac{V(s)}{L s} + \frac{L i(0^+)}{L s} \rightarrow \text{KCL}$$



$$Y(s) = \frac{I(s)}{V(s)}$$

$$Y(s) = \frac{1}{L s} + \frac{i(0^+)}{s V(s)}$$


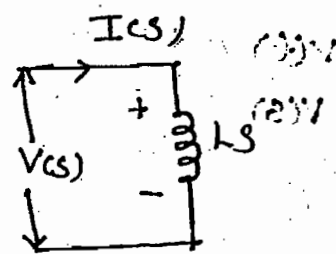
If $i(0^+) = 0$ then eq.
ckt is $\rightarrow$



$$i = C \frac{dV}{dt}$$

$$I(s) = C [sV(s) - V(0^+)]$$
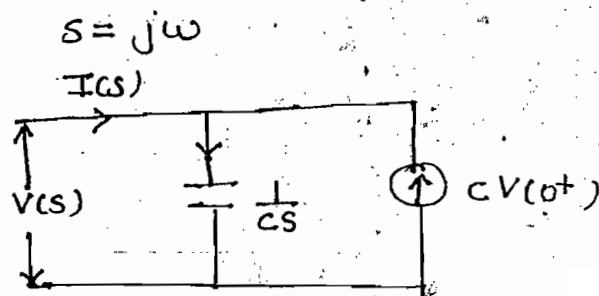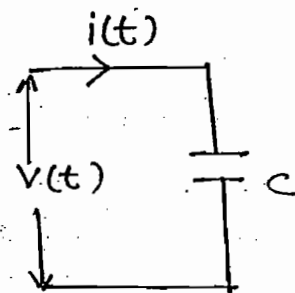
$$\Rightarrow I(s) = \frac{V(s)}{1/Cs} - C V(0^+) \rightarrow \text{KCL}$$




$$Y(s) = \frac{I(s)}{V(s)}$$

$$Y(s) = Cs - \frac{C V(0^+)}{V(s)}$$


$$\frac{V(s)}{1/Cs} = I(s) + C V(0^+)$$
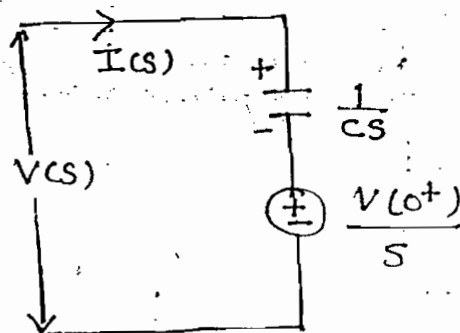
$$\Rightarrow V(s) = \frac{1}{Cs} I(s) + \frac{C V(0^+)}{Cs} \rightarrow \text{KVL}$$




$$Z(s) = \frac{V(s)}{I(s)} = \frac{1}{Cs} + \frac{V(0^+)}{sI(s)}$$


$$V(0^+) = 0 \rightarrow$$

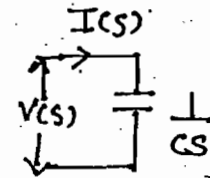

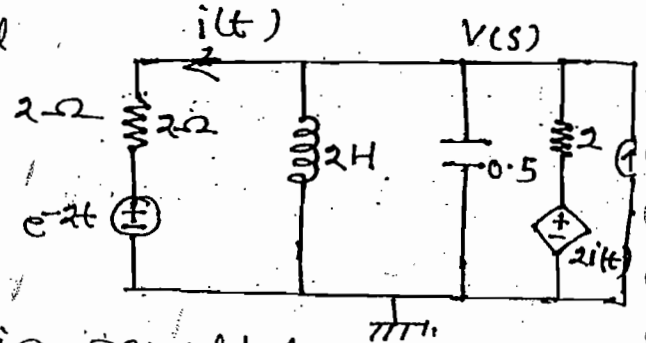Ques:- Find $V(s)$ when initial current of the inductor is $2A$ and initial voltage of the capacitor is $3V$



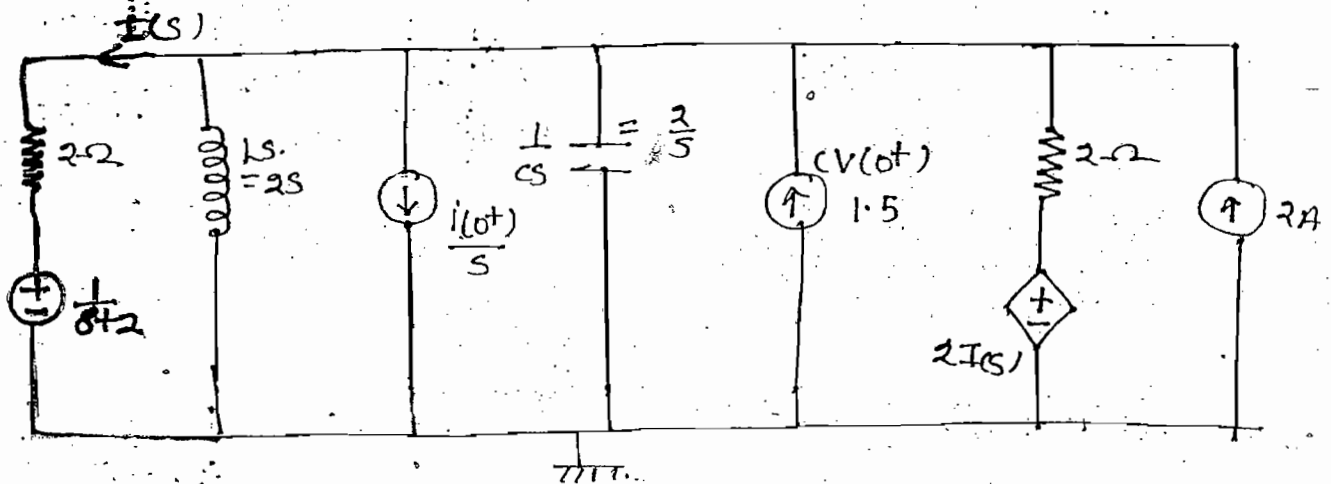
Soln:- When elements are in parallel then for simple calculation convert elements into current sources



$$\frac{V(s) - \frac{1}{s+2}}{2} + \frac{V(s)}{2s} + \frac{3}{s} + \frac{V(s)}{\frac{1}{Cs}} + \frac{V(s) - 2I(s)}{2} = 1.5 + 2 \quad \text{---(1)}$$

$$I(s) = \frac{V(s) - \frac{1}{s+2}}{2}$$

Ques:- Find $i(t)$ for $t > 0$

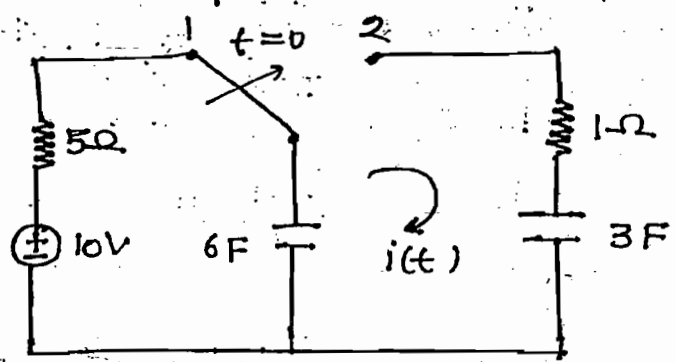

Soln:-

At $t = 0^-$

$$V_{C_6}(0^-) = 10V$$



$$V_{C_3}(0^-) = 0V$$

At $t > 0$

$$I(s) = \frac{10/s}{\frac{1}{6s} + \frac{1}{3s} + 1}$$

$$i(t) = \mathcal{L}^{-1} I(s)$$


$$\Rightarrow i(t) = 10 e^{-t/2}$$

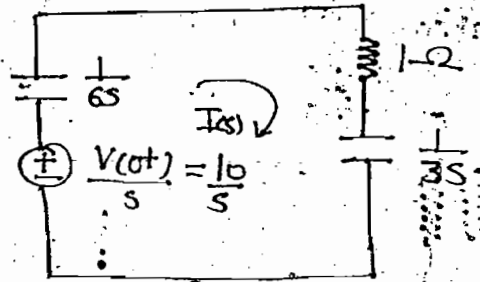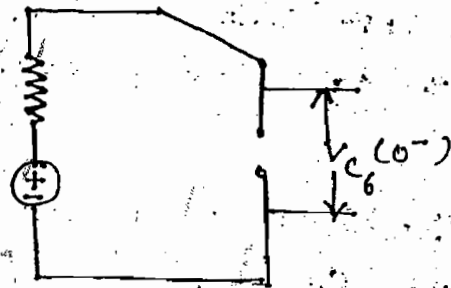


Verification:- $\rightarrow$ Method for MCA

$$i(t) = \frac{V_0}{R} e^{-t/RC}$$

$$i(t) = \frac{10}{1} e^{-t/2}$$

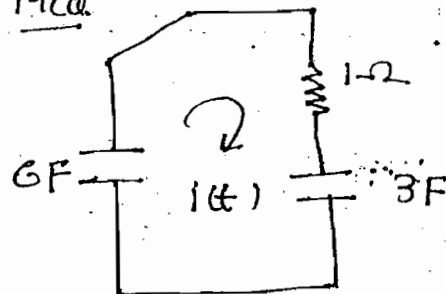


Ques:- Find $i(t)$ for $t > 0$

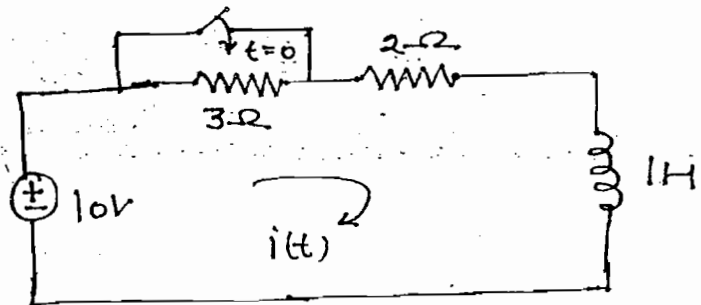

Soln:-

At $t = 0^-$

$$i(0^-) = \frac{10}{3+2} = 2A$$

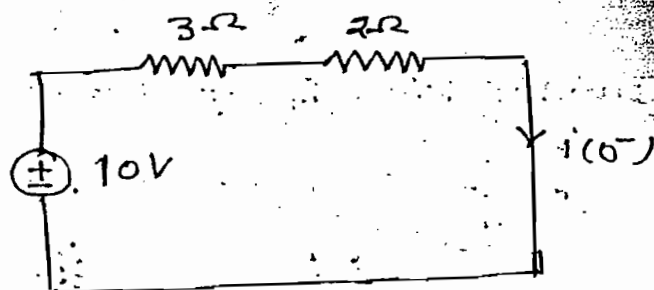


For $t > 0$

$$I(s) = \frac{\frac{10}{s} + 2}{2+s}$$

$$i(t) = \mathcal{L}^{-1} I(s)$$

$$i(t) = 5 - 3e^{-2t}$$

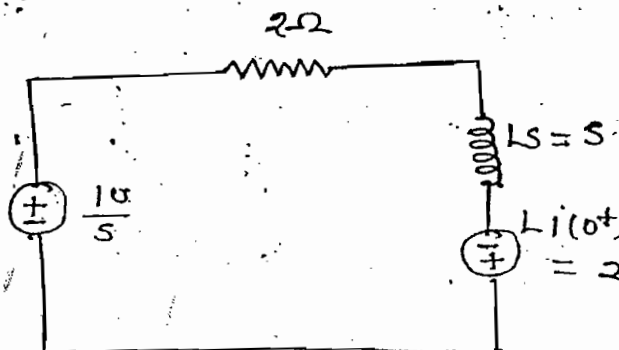

Alternate way:-

$$i(t) = [i(0^+) - i(\infty)]e^{-\frac{R}{L}t} + i(\infty)$$

$$i(0^+) = i(0^-) = 2$$

$$i(t) = [2 - 5]e^{-2t} + 5$$

