

ELECTRIC CIRCUITS AND FIELDS TEST 2

Number of Questions: 35


Section Marks: 90

Directions for questions 1 to 35: Select the correct alternative from the given choices.

1. Twelve 1H inductors are used as edges to form a cube. The inductance between two diagonally opposite corners of the cube is


(A) $\frac{5}{6}$ H (B) 1H
(C) $\frac{6}{5}$ H (D) $\frac{3}{2}$ H

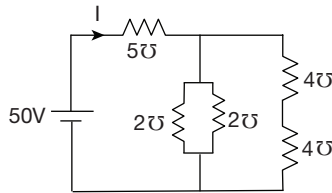2. Determine the current drawn from the battery of the given figure.




(A) 8.49 A (B) 49.8 A
(C) 36 A (D) 136.36 A

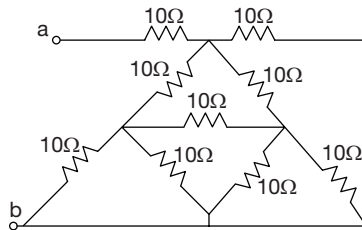3. Find equivalent resistance between 'a' and 'b' terminals.



(A) 6.3Ω (B) 4.3Ω
(C) 14.3Ω (D) 16.3Ω

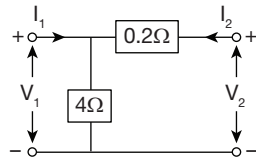4. Find Transition matrix of given 2 port network.




(A) $\begin{bmatrix} 1 & 5 \\ 4 & 21 \end{bmatrix}$

(B) $\begin{bmatrix} 1 & 4 \\ 5 & 21 \end{bmatrix}$

(C) $\begin{bmatrix} 1 & 0.2 \\ 0.25 & 1.05 \end{bmatrix}$

(D) transition matrix does not exist

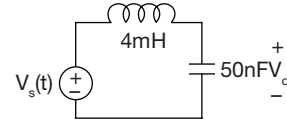5. If $V_c(t) = 5 \sin 10^5 t$ V in below circuit then $V_s(t)$ would be



(A) $5 \sin 10^5 t$ volts (B) $-5 \sin 10^5 t$ volts
(C) zero (D) $-10 \cos 10^5 t$ volts

6. How many Number of tie set matrixes are possible for a graph which has N nodes?

(A) $N^{\frac{N}{2}}$ (B) N^{2N}
(C) N^{N-2} (D) N^{N+2}


7. Two set of Networks are connected in series and each Network contains N number of Resistors each are having $R \Omega$ are connected in parallel then find R – equivalence of Total Network?

(A) $\frac{R}{2n}$ (B) $\frac{2R}{n}$
(C) $\left(\frac{R}{n}\right)^2$ (D) $\sqrt{\frac{R}{n}}$

8. A voltage of $V(t) = 8 \sin 314 t$ volts is applied to an inductance of 4mH. Determine the instantaneous power (p)


(A) zero (B) $-25.48 \sin 628 t$ W
(C) $-6.37 \cos 314 t$ W (D) $-50.96 \cos 314 t$ W

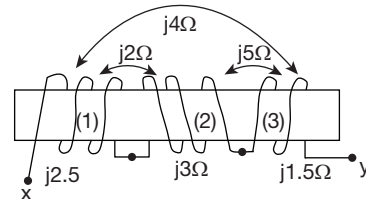9. Find the net inductance of the iron core coupled coils are in series connection.




(A) $j7$ H (B) $j1$ H
(C) $j4$ H (D) $j13$ H

10. Find time constant of below circuit

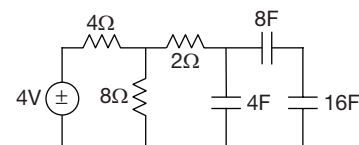


(A) 45.6sec (B) 43.56sec
(C) 53.4sec (D) 54.3sec

11. A series LCR circuit with $R = 20\Omega$, $|X_L| = |X_C| = 40\Omega$ is connected across an AC supply of 200 V rms. The rms voltage across the inductor is
 (A) $200\angle -90^\circ\text{V}$ (B) $200\angle 90^\circ\text{V}$
 (C) $400\angle -90^\circ\text{V}$ (D) $400\angle 90^\circ\text{V}$
12. If half power frequencies are given as 5 KHz, 8 KHz respectively. Then resonance frequency is
 (A) 13 KHz (B) 3 KHz
 (C) 7 KHz (D) 6.32 KHz
13. Consider the following circuit

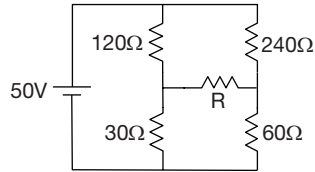


What is the power delivered to resistor R in the above circuit?

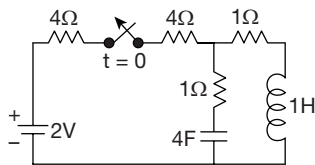- (A) 156 watts (B) -156 W
 (C) zero (D) 82.52 W
14. The conditions, under which a passive two – port network represented by h if parameters is reciprocal and symmetrical,
 (A) $h_{12} = h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
 (B) $h_{12} = -h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
 (C) $h_{12} = h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
 (D) $h_{12} = -h_{21}$, $h_{11}h_{22} - h_{12}h_{21} = 1$
15. In the circuit shown, the switch is opened at $t = 0$. Then the circuit is



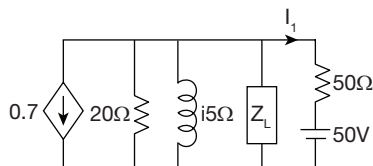- (A) critically damped (B) under damped
 (C) over damped (D) undamped
- 16.




In the given circuit, the maximum power delivered to Z_L if its value is

- (A) $(0.084 - j0.2)\Omega$ (B) $(0.084 + j0.2)\Omega$
 (C) $(1.785 - j4.25)\Omega$ (D) $(1.785 + j4.25)\Omega$
17. 2 – Two port Networks are connected in series with open circuit impedance parameter matrix is $\begin{bmatrix} 3 & 4 \\ 5 & 2 \end{bmatrix}$ and other two port Network has short circuit

admittance parameters matrix $\begin{bmatrix} 5 & 10 \\ 4 & 2 \end{bmatrix}$, then find overall twoport network impedance matrix


- (A) $\begin{bmatrix} 8 & 14 \\ 8 & 4 \end{bmatrix}$ (B) $\begin{bmatrix} 2 & 6 \\ -1 & 0 \end{bmatrix}$
 (C) $\begin{bmatrix} 37 & 38 \\ 33 & 54 \end{bmatrix}$ (D) $\begin{bmatrix} 2.933 & 4.333 \\ 5.133 & 1.833 \end{bmatrix}$

18. Find current flowing in 5Ω resistor

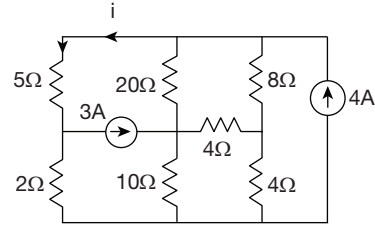


- (A) 3.2 A (B) 2.32 A
 (C) 1.25 A (D) 6.23 A

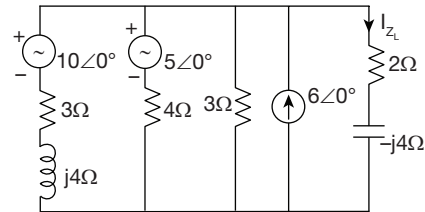19. Find the current in load Z_L in below Network.




- (A) $2.43\angle 60^\circ\text{A}$ (B) $24.3\angle 3^\circ\text{A}$
 (C) $34.2\angle -30^\circ\text{A}$ (D) $43.2\angle 60^\circ\text{A}$

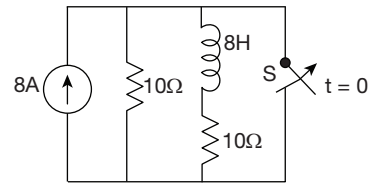20. Find the voltage across inductor ($t > 0$) where switch is opened at $t = 0$.



- (A) $80e^{-\frac{10t}{2}}\text{V}$ (B) $80e^{-\frac{4t}{5}}\text{V}$
 (C) $80e^{-\frac{5t}{2}}\text{V}$ (D) zero

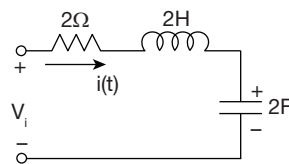
21. The circuit shown below has initial current $i(0^-) = -1\text{A}$ and initial voltage $V_c(0^-) = 1\text{V}$. For unit step response the voltage across the inductor is




- (A) $e^{-0.5t}\text{V}$ (B) $(2 - 0.5t)e^{-0.5t}\text{V}$
 (C) $(10 - t)e^{-0.5t}\text{V}$ (D) $10(2.4 - t)e^{-\frac{1}{2}t}\text{V}$

3.76 | Electric Circuits and Fields Test 2

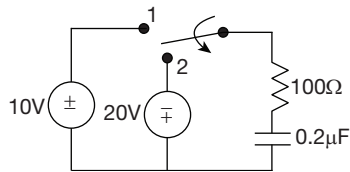
22. Given circuit is attains steady state when the switch at 1. At $t = 0$, the switch is moved to 2. Find energy stored across the capacitor at 0.1m sec



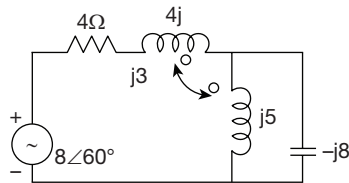- (A) 89.2 μ J (B) 392 μ J
(C) 19.79 μ J (D) 197 μ J
23. Two coupled coils have $K = 0.7$, $N_1 = 400$ turns, $N_2 = 800$ turns and mutual flux being 0.8 wb, if the primary current be 10A, then find the secondary coil inductance
(A) 45.7 H (B) 183 H
(C) 137 H (D) 173 H
24. Find the Voltage drop across the capacitor




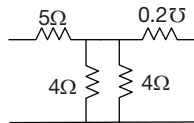- (A) $18\angle -90^\circ$ (B) $42.1\angle 15.95^\circ$
(C) $42.1\angle -20.5^\circ$ (D) $21.4\angle +90^\circ$
25. Find h parameters for below 2 port network.




- (A) $\begin{bmatrix} -6.428 & 35 \\ -35 & 0.142 \end{bmatrix}$ (B) $\begin{bmatrix} 4.8 & 0.285 \\ 1.4 & 0.142 \end{bmatrix}$
(C) $\begin{bmatrix} 4.8 & 1.4 \\ 0.285 & 0.2 \end{bmatrix}$ (D) $\begin{bmatrix} 6.428 & 0.285 \\ -0.285 & 0.142 \end{bmatrix}$
26. A three phase 440V, 50Hz supply is applied to a balanced delta connected three phase load. The phase currents being $I_{ab} = 20\angle -30$. The total power received by the load is
(A) 6.6 KW
(B) 22.86 KW
(C) 7.62 KW
(D) 13.19 KW
27. A 25HP induction motor is supplied from a 400V, 3- ϕ , 50Hz. System. The efficiency being 95% and the power factor of operation is 0.85. The total power is
(A) 23.09KVA
(B) 19.63KVA
(C) 19.63KW
(D) 23.09KW

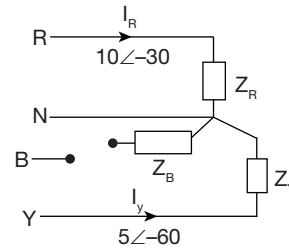
28. The neutral current for the following circuit is



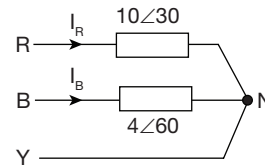- (A) $6.19\angle -6.20$ A (B) $14.54\angle -39.89$ A
(C) $6.19\angle 6.20$ A (D) $14.54\angle 39.89$ A
29. Three identical resistances are connected in a star fashion against a balanced three phase voltage supply. If one of the resistances be removed, the power can be.
(A) remains same (B) reduced by 50%
(C) Increases by 50% (D) None of the above
30. A 3 ϕ , 200V, 50Hz supply, a 3- ϕ load as shown in the figure. The expression for I_R is




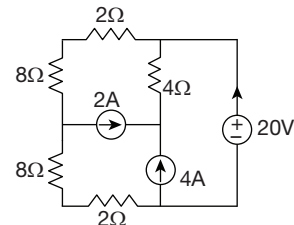- (A) $-20\sqrt{2} \sin(314t + 90^\circ)$ A
(B) $-20\sin(314t + 90^\circ)$ A
(C) $-20\sqrt{2} \sin(314t - 90^\circ)$ A
(D) $-20\sin(314t - 90^\circ)$ A
31. Find the power delivered by the voltage source is





- (A) 80 W (B) 20 W
(C) 40 W (D) -80 W

Common data for Questions 32 and 33:


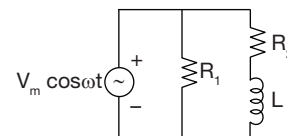


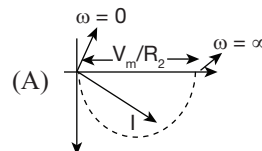32. In above network ω varies then locus of total current



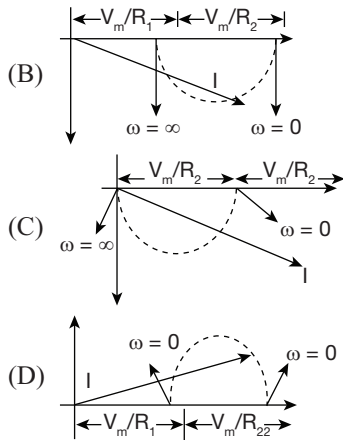


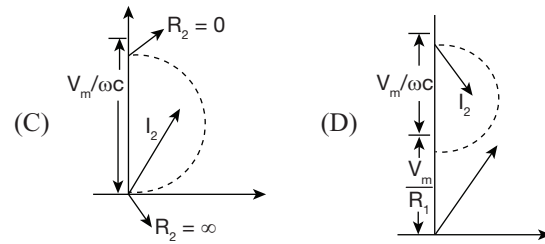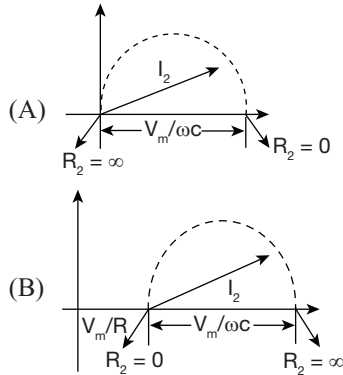33. In the above circuit inductor is replaced by a capacitor and instead of ω if R_2 is varied then locus of I_2 current.



Statement for Linked Answer Questions 34 and 35:

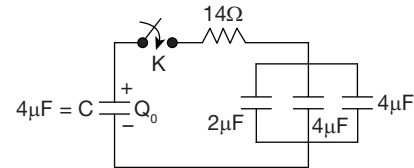A $4\mu\text{F}$ capacitor is initially charged with $600\mu\text{C}$. At $t = 0$, the switch is closed.



34. Determine the voltage drop across resistor at $t < T$ where T is time constant.

- (A) $600 e^{-25 \times 10^3 t} \text{ V}$
 (B) $600 e^{-14 \times 10^3 t} \text{ V}$
 (C) $150 e^{-25 \times 10^3 t} \text{ V}$
 (D) $150 e^{-14 \times 10^3 t} \text{ V}$

35. Find voltage drop across resistor at $40\mu\text{sec}$


- (A) 22 V (B) 339 V
 (C) 55.18 V (D) 85 V

ANSWER KEYS

- | | | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. A | 2. D | 3. C | 4. C | 5. B | 6. C | 7. B | 8. B | 9. B | 10. B |
| 11. D | 12. D | 13. C | 14. B | 15. C | 16. C | 17. D | 18. B | 19. A | 20. C |
| 21. B | 22. A | 23. B | 24. C | 25. D | 26. B | 27. A | 28. B | 29. B | 30. A |
| 31. D | 32. B | 33. C | 34. C | 35. C | | | | | |

HINTS AND EXPLANATIONS

1.

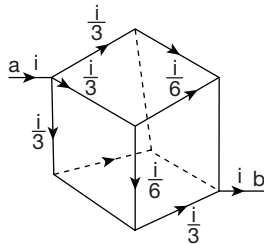



$$V_{ab} = \frac{1}{3} \frac{di}{dt} + \frac{1}{6} \frac{di}{dt} + \frac{1}{3} \frac{di}{dt}$$

$$= \frac{5}{6} \frac{di}{dt}$$

$$L_{eq} = \frac{5}{6} \text{ H}$$

Choice (A)

2.

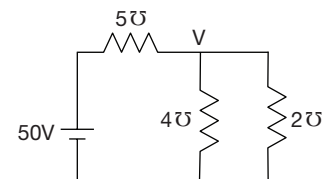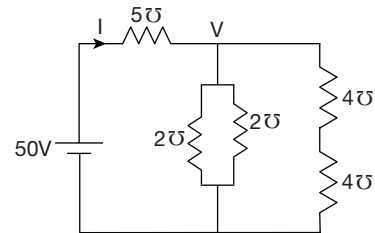

$$(V - 50) 5 + V 4 + 2 V = 0$$



$$11 V = 250$$

$$V = \frac{250}{11}$$


$$i = \left(50 - \frac{250}{11} \right) 5 = 136.36 \text{ A}$$

Choice (D)

3.

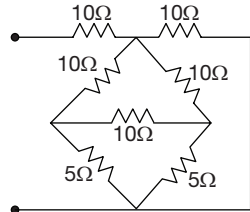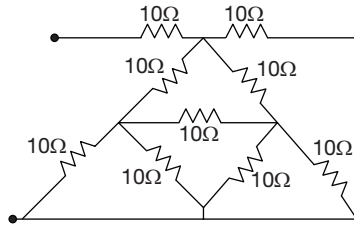


⇒ from bridge balance

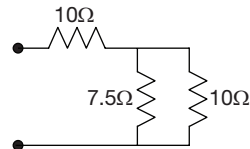

$$= R_{ab} = 14.28\Omega$$

Choice (C)

4.

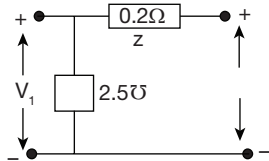


$$\Rightarrow \begin{bmatrix} 1 & z \\ y & zy+1 \end{bmatrix}$$

$$\Rightarrow \begin{bmatrix} 1 & 0.2 \\ 0.25 & 1.05 \end{bmatrix}$$

Choice (C)

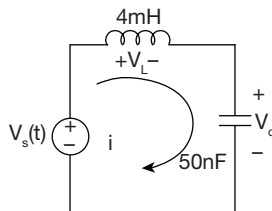5. If $V_c(t) = 5 \sin 10^5 t$ V in below circuit then $V_s(t)$



$$i_c = i = \frac{Cdv_c}{dt} \text{ where } (V_c) = 5 \sin 10^5 t$$

$$= 50 \times 10^{-9} \times 5 \times 10^5 \cos 10^5 t = 25 \cos 10^5 t \text{ mA}$$

$$V_s = V_L + V_C$$

$$V_L = L \frac{di}{dt} = 4 \times 10^{-3} 25 \times 10^5 \sin 10^5 t \times 10^{-3}$$



$$= -10 \sin 10^5 t$$

$$V_s = -5 \sin 10^5 t \text{ volts.}$$

Choice (B)

6. Choice (C)

7.

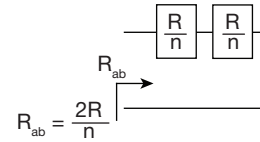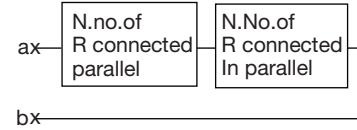

$$R_{ab} = \frac{2R}{n}$$

Choice (B)

8. Current through the inductance is

$$I = \frac{1}{L} \int V dt = \frac{10^3 \times 8}{4} \int \sin 314 t dt$$

$$= 2 \times 10^3 \left[\frac{-\cos 314 t}{314} \right]$$

$$= -6.37 \cos 314 t \text{ amps}$$

Instantaneous power

$$P = Vi = (8 \sin 314 t) (-6.37 \cos 314 t)$$

$$= -50.96 \sin 314 t \cos 314 t$$

$$= -25.48 \sin 628 t \text{ W}$$

Choice (B)

9. $L_1 = j2.5\Omega$; $M_{12} = j2\Omega$

$$L_2 = j3\Omega$$

$$L_3 = j1.5\Omega$$


$$\text{Net inductance is } L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} + 2M_{13}$$

$$= j(2.5 + 1.5 + 3) - 2 \times j2 - 2 \times j5 + 2 \times j4$$

$$= j7 - j4 - j10 + j8 = j1H$$

Choice (B)

10. Find time constant of below circuit

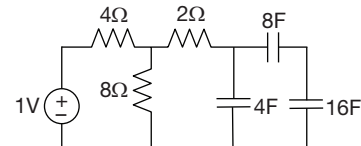

$$T = R_{eq} \cdot C_{eq}$$

$$= (4/8 + 2) (4 + 8/16) = \frac{28}{3} \times \frac{14}{3} = 43.56 \text{ sec}$$

Choice (B)

11. Quality factor

$$Q = \frac{|x_L|}{R} = \frac{|x_C|}{R} = 2$$

rms voltage across inductor


$$V_{Lrms} = QV \angle 90^\circ = 400 \angle 90^\circ$$

Choice (D)

$$12. f_r = \sqrt{f_1 f_2} = \sqrt{5 \times 8} = 6.32 \text{ KHz}$$

Choice (D)

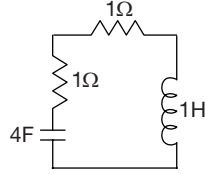13. It is balanced wheat stone bridge. The current through R is zero so power delivered to R is zero Choice (C)
14. Choice (B)
15. At $t = 0$ when the switch is opened then the circuit can be redrawn as



$$\times = \frac{R}{2} \sqrt{\frac{C}{L}}$$

$$R = 1 + 1 = 2\Omega$$


$$L = 1H$$

$$C = 4F$$

$$\xi = \frac{2}{2} \sqrt{\frac{4}{1}} = 2 > 1$$

Choice (C)

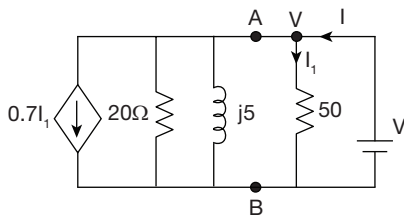16. maximum power delivered to open circuit Z



$$I_1 = \begin{bmatrix} 7 & 2 \\ 2 & 7 \end{bmatrix} \Rightarrow \text{KCL at node } V$$

$$\frac{V}{20} + \frac{V}{j5} + \frac{V}{50} + 0.7I_1 = I$$

$$V \left[\frac{1}{20} + \frac{1}{50} + \frac{0.7}{50} - \frac{j}{5} \right] = I$$

$$\frac{I}{V} = \left[\frac{1}{20} + \frac{1.7}{50} - \frac{j}{5} \right] = (0.084 - j0.2)$$


$$\frac{V}{I} = Z_{th} = \frac{1}{(0.084 - j0.2)} = (1.785 + j4.25)\Omega$$

$$\text{But } Z_L = Z_{th}^*$$

$$Z_L = (1.785 - j4.25)\Omega$$

Choice (C)

- 17.

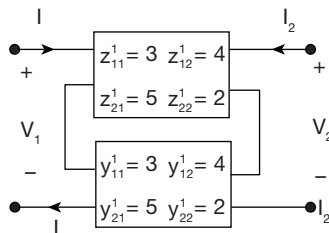

$$z_{eq} = [Z_1] + [Z_2]$$



→ Convert y matrix in to Z - matrix

$$[Z_2] = [y_2]^{-1} = \begin{bmatrix} 5 & 10 \\ 4 & 2 \end{bmatrix}^{-1} = \begin{bmatrix} 2 & -10 \\ -4 & 5 \end{bmatrix} \times \frac{1}{-30}$$

$$\Rightarrow Z_{eq} = \begin{bmatrix} 3 & 4 \\ 5 & 2 \end{bmatrix} + \begin{bmatrix} -1/15 & 1/3 \\ 2/15 & -1/6 \end{bmatrix} = \begin{bmatrix} 2.933 & 4.333 \\ 5.133 & 1.833 \end{bmatrix}$$

Choice (D)

- 18.

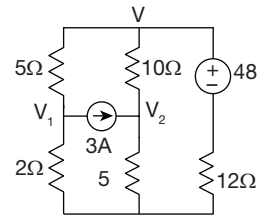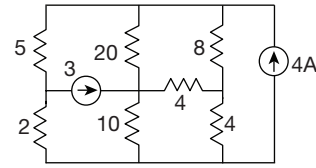

⇒ KCL at V

$$\frac{V - V_2}{10} + \frac{V - V_2}{10} + \frac{V - V_1}{5} = 0$$

$$23V = 6V_2 + 12V_1 + 240$$

$$\text{KCL at } V_1, \frac{V_1}{2} + \frac{V_1 - V}{5} = 3$$

$$7V_1 - 2V = 30 \quad (2) \Rightarrow V_1 = \frac{30 + 2V}{7}$$

$$\text{KCL at } V_2, 3 = \frac{V_2 - V}{10} + \frac{V_2}{5}$$

$$15V_2 - 5V = 150$$

$$3V_2 - V = 50$$

$$\frac{50 + V}{3} = V_2$$

→ (3)

$$\Rightarrow 23V = 6 \left(\frac{50 + V}{3} \right) + 12 \left(\frac{30 + 2V}{7} \right) + 240$$

$$V \left[23 - \frac{6}{3} - \frac{24}{7} \right] = 100 + \frac{360}{7} + 240$$

$$\frac{123V}{7} = \frac{2740}{7}$$

$$V = 22.3$$


$$V_1 = 10.65$$

$$5i = V - V_1$$

$$i = \frac{V - V_1}{5} = 2.32A$$

Choice (B)

19. redrawing given circuit

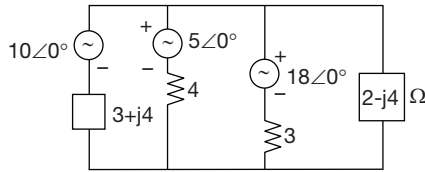

According to millman's theorem

$$V = \frac{V_1 Y_1 + V_2 Y_2 + V_3 Y_3}{Y_1 + Y_2 + Y_3}$$

$$E = \frac{\frac{10}{3+j4} + \frac{5}{4} + \frac{18}{3}}{\frac{1}{3+j4} + \frac{1}{4} + \frac{1}{3}}$$

$$= \frac{\frac{10(3-j4)}{5} + \frac{5}{4} + \frac{18}{3}}{\frac{3-j4}{5} + \frac{1}{4} + \frac{1}{3}} = \frac{6-j8+6+1.25}{\frac{71-j48}{60} - \frac{j48}{60}}$$


$$= \frac{(13.25-j8)60}{71-j48} = \frac{15.48\angle-31 \times 60}{85.7\angle-34}$$

$$E = 10.83\angle-3^\circ$$

$$i_{ZL} = \frac{E}{Z_L} = \frac{10.88\angle-3^\circ}{2-j4} = \frac{10.88\angle-3^\circ}{4.47\angle-63^\circ} = 2.43\angle60^\circ \text{ A}$$


Choice (A)

20.

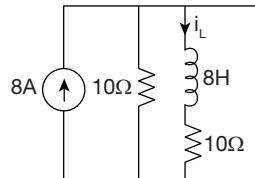

$$i_L = 0 \text{ at } t = 0^-$$

$$\text{at } t \Rightarrow \infty$$

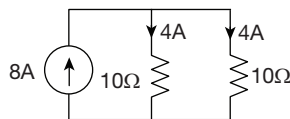

$$i_L = 4\text{A}$$

$$T = \frac{L}{R} = \frac{8}{20} = 0.4$$

$$i_L = 4 + (0-4)e^{-\frac{t}{0.4}} = 4\left(1 - e^{-\frac{5t}{2}}\right)$$

$$V_L = \frac{L di_L}{dt} \text{ volts.} = 8 \times 4 \times \frac{5}{2} e^{-\frac{5t}{2}}$$

$$V_L = 80 e^{-\frac{5t}{2}} \text{ V}$$


Choice (C)

21. From the given data

$$I(0^-) = -1\text{A and } V_c(0^-) = 1\text{V.}$$

$$V_i(t) = u(t) \text{ volts.}$$

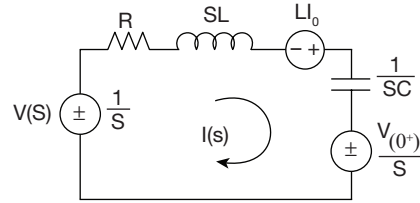Converting the given circuit into S-Domain. It becomes.



Applying KVL

$$\therefore \frac{1}{S} = \left(R + SL + \frac{1}{SC}\right) I(S) - L I_0 + \frac{V_0}{s}$$

$$\frac{1}{S} = \left(2 + 2s + \frac{1}{2s}\right) I(s) + 2 + \frac{1}{s}$$

$$I(s) = \frac{-2 \times 2s}{4s^2 + 4s + 1} = \frac{-s}{s^2 + s + \frac{1}{4}}$$

$$I(s) = \frac{-s}{\left(s + \frac{1}{2}\right)^2}$$

$$V_L = L \cdot \frac{di}{dt(t)}$$

$$I(s) = \frac{A}{s + \frac{1}{2}} + \frac{B}{\left(s + \frac{1}{2}\right)^2}$$

$$B \text{ at } s = -\frac{1}{2}$$

$$B = \frac{1}{2}.$$

$$-s = A \left(s + \left(s + \frac{1}{2}\right)\right) + B.$$

Compare both sides S^1 terms.

$$A = -1.$$

$$\therefore I(s) = \frac{-1}{(s+2)} + \frac{\left(\frac{1}{2}\right)}{\left(s + \frac{1}{2}\right)}$$

$$I(t) = \left\{-e^{-\frac{t}{2}} + \frac{1}{2}te^{-\frac{t}{2}}\right\} \text{ wts.}$$

$$V_{2(t)} = L \cdot \frac{di(t)}{dt} = 2 \left\{\frac{d}{dt} \left\{-e^{-\frac{t}{2}}\right\} + \frac{d}{dt} \left\{t \cdot e^{-\frac{t}{2}}\right\}\right\}$$


$$= e^{-\frac{t}{2}} + t \left\{-\frac{1}{2} \cdot e^{-\frac{t}{2}}\right\} + e^{-\frac{t}{2}} \cdot 1$$

$$V_L(t) = (2 \cdot e^{-0.5t} - 0.5t \cdot e^{-0.5t})$$

$$V_L(t) = \{2 - 0.5t\} \cdot e^{-0.5t} \cdot V(t).$$

Choice (B)

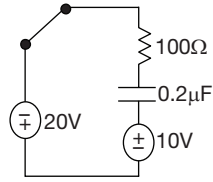22. From the given data $V_c(0^+) = 10V_c(0^-)$ for $t \geq 0$, the circuit becomes.



$$V_c(\infty) = 30V.$$

$$\tau = RC = 100 \times 0.2 \times 10^{-6} = 20 \mu \text{ sec}$$

$$V_c(t) = V_c(\infty) + \{V_c(0^+) - V_c(\infty)\} \cdot e^{-t/\tau} \text{ volts}$$

$$= 30 - 20 \cdot e^{-50 \times 10^3 t} \text{ volts}$$

$$\text{at } t = 0.1 \text{ in sec.}$$

$$V_c = 30 - 20 \cdot e^{-5}$$

$$= 29.86$$

$$E = \frac{1}{2} CV^2 = \frac{1}{2} \times 0.2 \times 10^{-6} \times 892$$

$$\approx 89.2 \mu \text{J}$$

Choice (A)

23. Let ϕ_1 = primary flux ; ϕ_{12} mutual flux, K co-efficient of coupling $I_1 = 10 \text{ A}$

$$\phi_{12} = K \phi \Rightarrow 0.8 = 0.7 \phi_1$$

$$\Rightarrow \phi_1 = 1.1428$$


$$L_1 = \frac{N_1 \phi_1}{I_1} = \frac{400 \times 1.1428}{10} = 45.7 \text{ H}$$

$$M = K \sqrt{L_1 L_2}$$

$$N_2 = \frac{\phi_{12}}{I_1} = M = 800 \times \frac{0.8}{10}$$

$$\Rightarrow 64 = 0.7 \sqrt{45.7 L_2} \Rightarrow L_2 = 183 \text{ H} \quad \text{Choice (B)}$$

24.

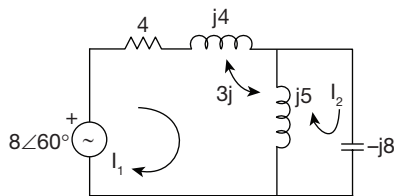

Applying KVL in loop 1

$$8 \angle 60^\circ = 4I_1 + j4I_1 + j5(I_1 - I_2) - j3(I_1 - I_2)$$

$$8 \angle 60^\circ = I_1(4 + j6) - j2I_2$$

Apply KVL in loop 2

$$j5(I_2 - I_1) - j8I_2 - j3I_1 = 0$$

$$\Rightarrow I_1 8j = 3j I_2$$

$$I_1 = \frac{3}{8} I_2 \Rightarrow 8 \angle 60^\circ = I_2 \left(\frac{3}{8}(4 + j6) - 2j \right)$$


$$8 \angle 60^\circ I_2 \left(\frac{3}{2} - \frac{j}{4} \right)$$

$$I_2 = \frac{8 \angle 60^\circ}{1.52 \angle -9.5^\circ} = 5.263 \angle 69.5^\circ$$

$$\text{Drop across capacitors is } (-j8) \times (5.263 \angle 69.5^\circ) = 8 \angle -90^\circ \times 5.263 \angle 69.5^\circ = 42.1 \angle -20.5^\circ$$

Choice (C)

25.

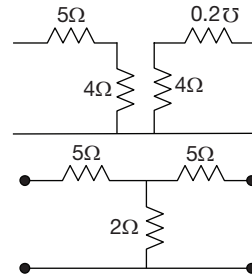

$$Z \text{ matrix is } \begin{bmatrix} 7 & 2 \\ 2 & 7 \end{bmatrix}$$

Converting zmatrix in h parameter

$$h_{11} = \frac{Z_{11}Z_{22} - Z_{12}Z_{21}}{Z_{22}} = 6.428 \Omega$$

$$h_{12} = \frac{Z_{12}}{Z_{22}} = \frac{2}{7} = 0.285$$

$$h_{21} = \frac{-Z_{12}}{Z_{22}} = \frac{-2}{7} = -0.285$$

$$h_{22} = \frac{1}{Z_{22}} = \frac{1}{7} = 0.142$$

$$\Rightarrow h \text{ matrix is } \begin{bmatrix} 6.428 & 0.285 \\ -0.285 & 0.142 \end{bmatrix}$$

Choice (D)

26. Total power received by the load = $3V_{\text{ph}} I_{\text{ph}} \cos \phi$
 $= 3 \times 440 \times 20 \times \cos 30 = 22.863 \text{ KW}$ Choice (B)

$$27. \text{ Power input} = \frac{25 \times 746}{0.95} = 19.63 \text{ KW}$$

$$\text{Total power (or) apparent power} = \frac{19630}{0.85}$$

$$= 23.09 \text{ KVA}$$

Choice (A)

$$28. I_N = I_R + I_Y \\ = 10 \angle -30 + 5 \angle -60 \\ = 14.54 \angle -39.89 \text{ A}$$

Choice (B)

$$29. P_1 = \frac{3V_{\text{pm}}^2}{R}$$

$$= \frac{V_L^2}{2R}$$

$$P_2 = \frac{V_L^2}{2R}$$

$$\text{Power} = \frac{\frac{V_L^2}{R} - \frac{V_L^2}{2R}}{\frac{V_L^2}{R}} \times 100 = 50\%$$

Choice (B)

3.82 | Electric Circuits and Fields Test 2


30. $V_{RB} = 200 \angle 0^\circ \text{ V}$
 $V_{BY} = 200 \angle -120^\circ \text{ V}$
 $V_{YR} = 200 \angle +120^\circ \text{ V}$

$$I_R = \frac{-V_{YR}}{Z_R} = \frac{-200 \angle 120^\circ}{10 \angle 30^\circ} = -20 \angle 90^\circ$$

$$I_R = -20 \sqrt{2} \sin(314t + 90^\circ) \text{ A.}$$

Choice (A)

31. Given Network is

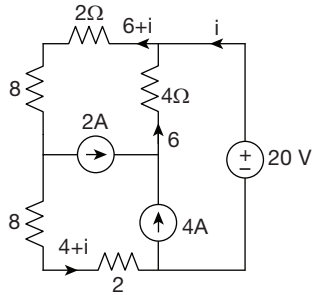

Apply KVL

$$20 = 10(6+i) + 10(4+i)$$

$$20 = 10[10 + 2i]$$

$$2 = 10 + 2i$$


$$\Rightarrow 2i = -8$$

$$i = -4$$

$$\text{Power} = 20 \times -4 = -80 \text{ W}$$

Choice (D)

32.

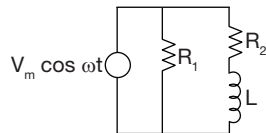


$$I = I_1 + I_2$$

$$= \frac{V_m \angle 0^\circ}{R_1} + \frac{V_m \angle 0^\circ}{R_2 + j\omega L}$$

$$\frac{V_m \angle 0^\circ}{R_1} + \frac{V_m}{\sqrt{R_2^2 + \omega^2 L^2}} - \tan^{-1}\left(\frac{\omega L}{R_2}\right)$$


Choice (B)

33.

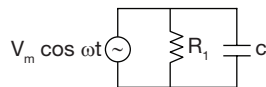

If $R_2 = 0$

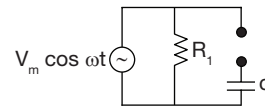
$$I_2 = \frac{E_m}{\frac{1}{\omega C}} \angle -90^\circ = E_m \omega C \angle -90^\circ$$



If $R_2 = \infty$ $I_2 = 0$

Choice (C)

34. Given circuit is

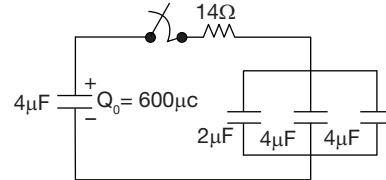

$$T = RC_{eq}$$

$$= 14 \left(\frac{10}{4}\right) \times 10^{-6}$$

$$= 14 \times \frac{20}{7} \times 10^{-6}$$

$$= 40 \mu \text{ sec}$$

The initial voltage V_0 across capacitor C_0 is given as

$$V_0 = \frac{Q_0}{C_0}$$

$$= \frac{600 \times 10^{-6}}{4 \times 10^{-6}}$$

$$= 150 \text{ V}$$

→ With closing of k_1 the capacitor C_0 will start discharging, & at $t = 0^+$ there will be no voltage across $2 \mu \text{ F}$, $4 \mu \text{ F}$, $4 \mu \text{ F}$, because at $t = 0^-$ switch is opened. So the entire voltage drop across R at $t = 0^+$ time

$$V_R = V_0 e^{-t/RC}$$

$$= 150 e^{\frac{-t}{40 \times 10^{-6}}}$$

$$= 150 e^{-25 \times 10^3 t} \text{ V}$$

Choice (C)

35. $V_R = 150 e^{-25 \times 10^3 \times 40 \times 10^{-6}}$
 $= 150 e^{-1}$
 $= 55.18 \text{ V}$

Choice (C)