




Multiple Choice Questions

- Q.1** A series resonant circuit has an inductive reactance of 1000Ω , a capacitive reactance of 1000Ω and a resistance of 0.1Ω . If the resonant frequency is 10 MHz , then the bandwidth of the circuit will be
- (a) 1 kHz (b) 10 kHz
(c) 1 MHz (d) 0.1 kHz

[ESE-1999]

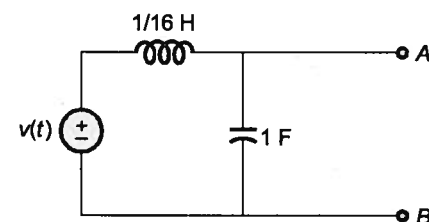
- Q.2** The circuit shown in the figure below, will act as an ideal current source with respect to terminals A and B, when frequency is



- (a) zero (b) 1 rad/s
(c) 4 rad/s (d) 16 rad/s


[ESE-2000]

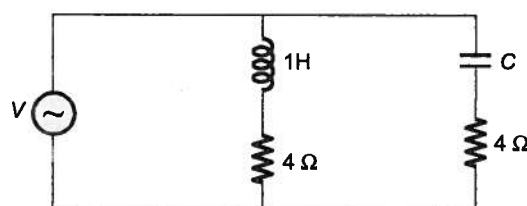- Q.3** The value of the capacitance 'C' in the given ac circuit to make it a constant resistance circuit OR for the supply current to be independent of its frequency is



- (a) $1/16 \text{ F}$ (b) $1/12 \text{ F}$
(c) $1/8 \text{ F}$ (d) $1/4 \text{ F}$ [ESE-2001]

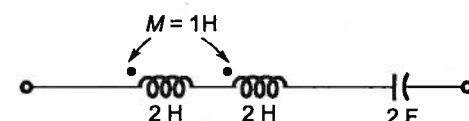- Q.4** The resonant frequency of the given series circuit is



- (a) $1/2\pi\sqrt{3} \text{ Hz}$ (b) $1/4\pi\sqrt{3} \text{ Hz}$
(c) $1/4\pi\sqrt{2} \text{ Hz}$ (d) $1/\pi\sqrt{2} \text{ Hz}$

[ESE-2001]

- Q.5 Assertion (A):** A series $R_1 - L$ and a series $R_2 - C$ are connected in parallel. Parallel resonance will occur at all frequencies when $R_1^2 = R_2^2 = L/C$.

Reason (R): An inductor must be operated below the self-resonant frequency.

- (a) Both A and R are true and R is the correct explanation of A
(b) Both A and R are true but R is NOT the correct explanation of A
(c) A is true but R is false
(d) A is false but R is true [ESE-2002]

- Q.6** The impedance of a parallel RLC network is $Z(s) = \frac{5s}{s^2 + 0.5s + 100}$. Then the value of R, L and C are, respectively


- (a) $10 \Omega, 1/20 \text{ H}, 1/5 \text{ F}$
(b) $1 \Omega, 1/2 \text{ H}, 1/5 \text{ F}$
(c) $10 \Omega, 1/20 \text{ H}, 1/2 \text{ F}$
(d) $2 \Omega, 1/20 \text{ H}, 1/5 \text{ F}$

[ESE-2003]

- Q.7** A series L-C-R circuit has a resonant frequency f_0 , with $R = 1 \Omega$, $L = 1 \text{ H}$ and $C = 1 \text{ F}$. If the components' values are tripled, the new resonant frequency will be

- (a) $3f_0$ (b) unaltered
(c) $\frac{f_0}{\sqrt{3}}$ (d) $\frac{f_0}{3}$ [ESE-2012]

- Q.8** Consider the following circuit:

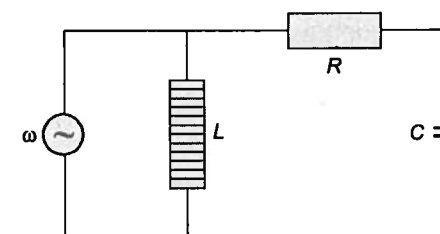

For what value of ω , the circuit shown above exhibits unity power factor?

- (a) $\frac{1}{\sqrt{LC}}$ (b) $\frac{1}{\sqrt{LC + R^2C^2}}$
(c) $\frac{1}{\sqrt{LC - R^2C^2}}$ (d) $\frac{1}{RC}$ [ESE-2004]


- Q.9** The transfer function $H(s) = \frac{V_0(s)}{V_1(s)}$ of an R-L-C circuit is given by $H(s) = \frac{10^6}{s^2 + 20s + 10^6}$. The

Quality factor (Q-factor) of this circuit is

- (a) 25 (b) 50
(c) 100 (d) 5000

[GATE-2004]

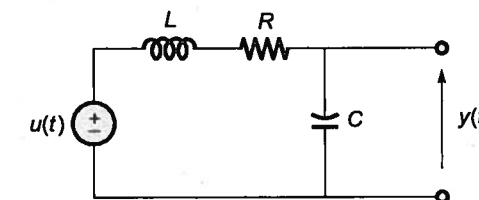- Q.10** The condition on R, L and C such that the step response $y(t)$ in the figure has no oscillations, is



- (a) $R \geq \frac{1}{2}\sqrt{\frac{L}{C}}$ (b) $R \geq \sqrt{\frac{L}{C}}$
(c) $R \geq 2\sqrt{\frac{L}{C}}$ (d) $R = \frac{1}{\sqrt{LC}}$

[GATE-2005]

- Q.11** In a series RLC circuit,


$$R = 2 \text{ k}\Omega, L = 1 \text{ H, and } C = \frac{1}{400} \mu\text{F}.$$

The resonant frequency is

- (a) $2 \times 10^4 \text{ Hz}$ (b) $\frac{1}{\pi} \times 10^4 \text{ Hz}$
(c) 10^4 Hz (d) $2\pi \times 10^4 \text{ Hz}$

[GATE-2005]

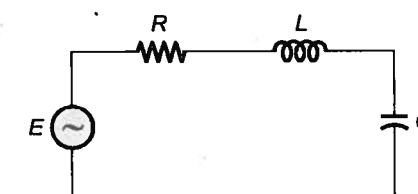- Q.12** Which one of the following statements is not correct for the circuit shown below at resonant frequency?



- (a) The current is maximum
(b) The equivalent impedance is real
(c) The inductive and capacitive reactances are equal in magnitude
(d) The quality factor equals $\frac{1}{R}\sqrt{\frac{C}{L}}$

[ESE-2005]

- Q.13** In a series R-L-C circuit, the maximum voltage across the capacitor occurs at a frequency

- (a) double the resonant frequency
(b) equal to resonant frequency
(c) $\sqrt{2}$ times the resonant frequency
(d) below the resonant frequency


[ESE-2006]

- Q.14** A series R-L-C circuit, excited by a 100 V , variable frequency source has a resistance of 10Ω and an inductive reactance of 50Ω at 100 Hz . If the resonance frequency is 500 Hz , what is the voltage across the capacitor at resonance?

- (a) 100 V (b) 500 V
(c) 2500 V (d) 5000 V

[ESE-2006]

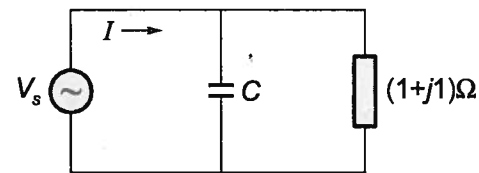Q.15 In the circuit shown in the figure below, for what value of C will the current I be in phase with the sinusoidal source voltage $V_s = \sin 2t$?



- (a) $\frac{1}{4}F$ (b) $\frac{1}{2}F$
(c) $\frac{1}{\sqrt{2}}F$ (d) $1F$ [ESE-2006]

Q.16 Width of resonance curve in an R - L - C network is determined by which one of the following?

- (a) R alone (b) L alone
(c) C alone (d) All R , L and C [ESE-2008]

Q.17 A series RLC circuit has a bandwidth of 300 rad/sec at a resonant frequency of 3000 rad/sec when excited by a voltage source of 100 V. The inductance of the coil is 0.1 H. The value of R and the voltage across C are, respectively


- (a) 10 Ω and 100 V
(b) 30 Ω and 100 V
(c) 30 Ω and 1000 V
(d) 300 Ω and 1000 V [ESE-2013]

Q.18 Two magnetically uncoupled inductive coils have Q factors q_1 and q_2 at the chosen operating frequency. Their respective resistance are R_1 and R_2 . When connected in series, their effective Q factor at the same operating frequency is

- (a) $q_1 + q_2$
(b) $(1/q_1) + (1/q_2)$
(c) $(q_1 R_1 + q_2 R_2)/(R_1 + R_2)$
(d) $(q_1 R_2 + q_2 R_1)/(R_1 + R_2)$

[ESE-2013]

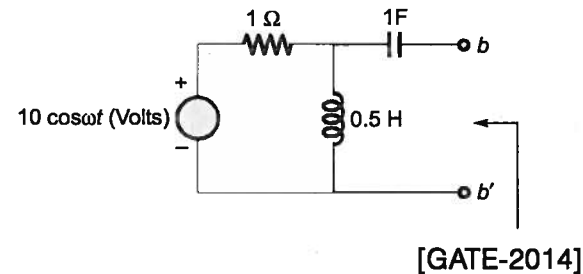Q.19 In the circuit shown in the figure, the angular frequency ω (in rad/s), at which the Norton equivalent impedance as seen from terminals b - b' is purely resistive, is _____.




Q.20 The low-frequency circuit impedance and the high-frequency circuit impedance for a series resonant circuit respectively are


- (a) capacitive and inductive
(b) inductive and capacitive
(c) resistive and inductive
(d) capacitive and resistive [ESE-2015]

Numerical Data Type Questions

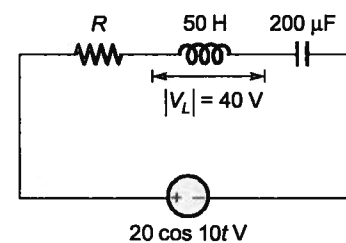
Q.21 The quality factor of the circuit shown in figure is



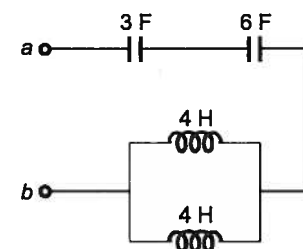Q.22 The resonant frequency of the circuit shown in figure is _____ rad/sec.




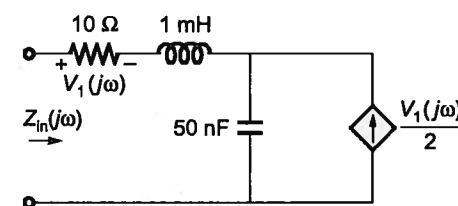Q.23 For the circuit shown below resonant frequency f_0 is _____ kHz.




Try Yourself

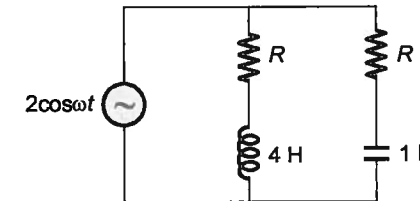T1. In the given network. Find the value of ' R ' such that the reactive power generated by the source is zero. Value of ' R ' in ohms _____



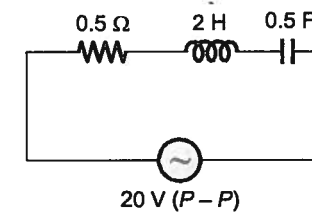T2. Find the voltage across capacitor when voltage across resistor is maximum




- (a) $\frac{40}{\sqrt{2}}$ V (b) 40 V
(c) 20 V (d) 10 V

T3. In a series RLC circuit with frequency of resonance as f_0 , voltage across resistor, capacitor and inductor are V_R , V_C and V_L respectively. Then at any frequency f , which of the following is true

- (i) $|V_C| > |V_L|$ if $f > f_0$
(ii) $|V_C| < |V_L|$ if $f < f_0$
(iii) V_R leads source voltage if $f < f_0$
(iv) $|V_L| = |V_C| = |V_R|$ if $f = f_0$
(a) (i) and (ii) (b) (iii) and (iv)
(c) (iii) only (d) (iv) only

T4. Find impedance (Z) at resonance.

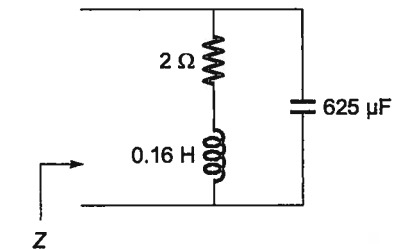

- (a) 1.28 Ω (b) 12.8 Ω
(c) 2 Ω (d) 128 Ω

T5. Find average power consumer by the circuits at resonance.

