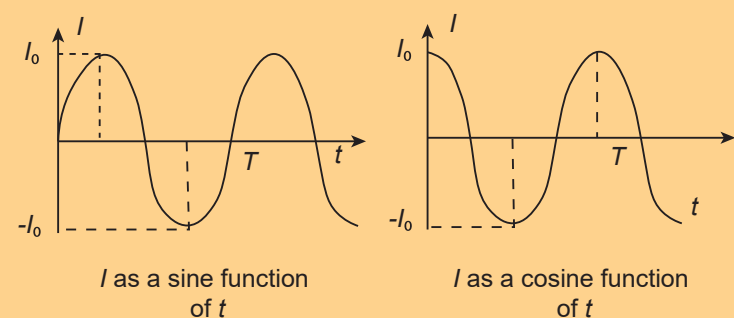


ALTERNATING CURRENT AND VOLTAGE


When the magnitude and direction of current and voltage change continuously with time, then current or voltage is said to be alternating.



$$I = I_0 \sin(\omega t + \phi) \text{ or } I = I_0 \cos(\omega t + \phi)$$

I = instantaneous values of current
 I = peak value or amplitude
 ω = angular frequency
 ϕ = initial phase.


Average or Mean Value

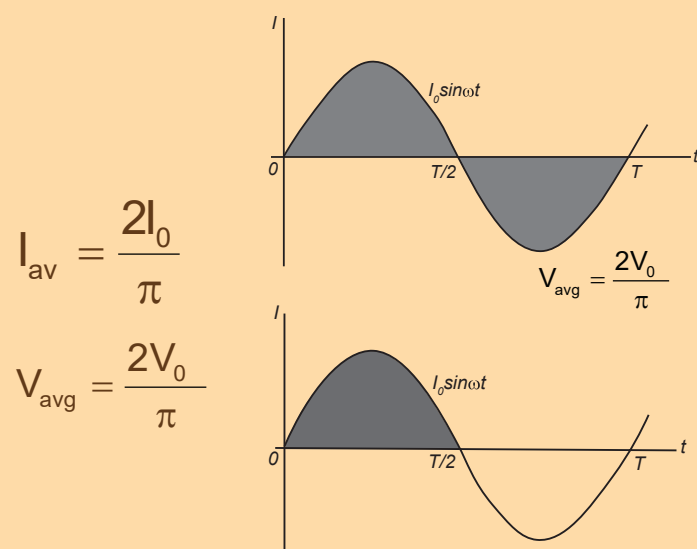

ROOT MEAN SQUARE VALUE

$$I_{av} = \frac{2I_0}{\pi}$$

$$V_{av} = \frac{2V_0}{\pi}$$

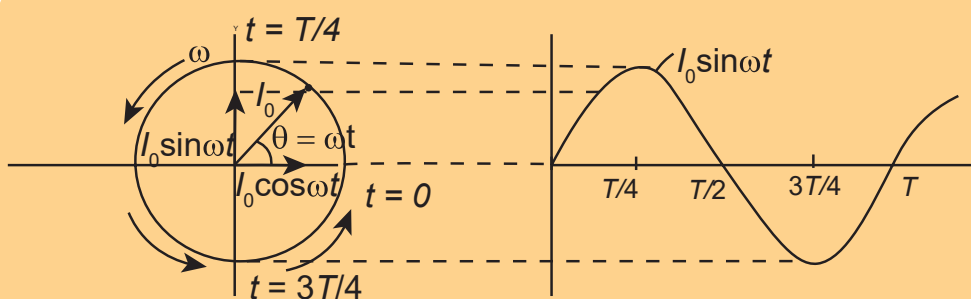


- The projection phasor on x - axis or y - axis gives the instantaneous value of Alternating current/voltage.
- A Phasor rotates with angular Speed ω about the origin.
- Arrow length of this vector is equal to the peak value of Alternating current/voltage.


ALTERNATING CURRENT

AC SERIES CIRCUIT ANALYSIS


RESISTIVE CIRCUIT

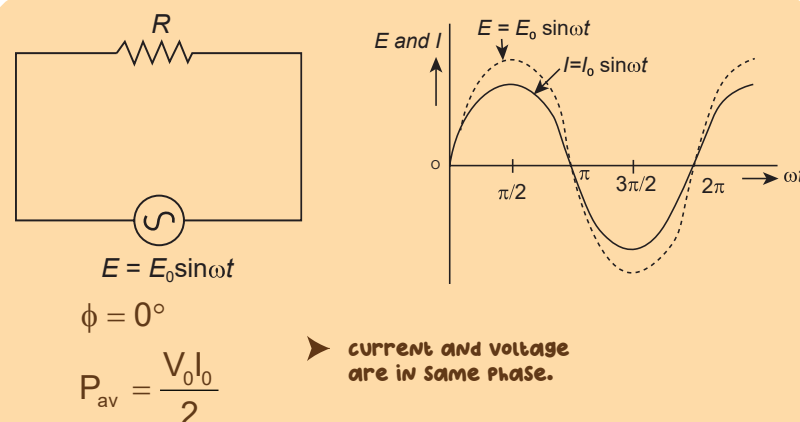


INDUCTIVE CIRCUIT

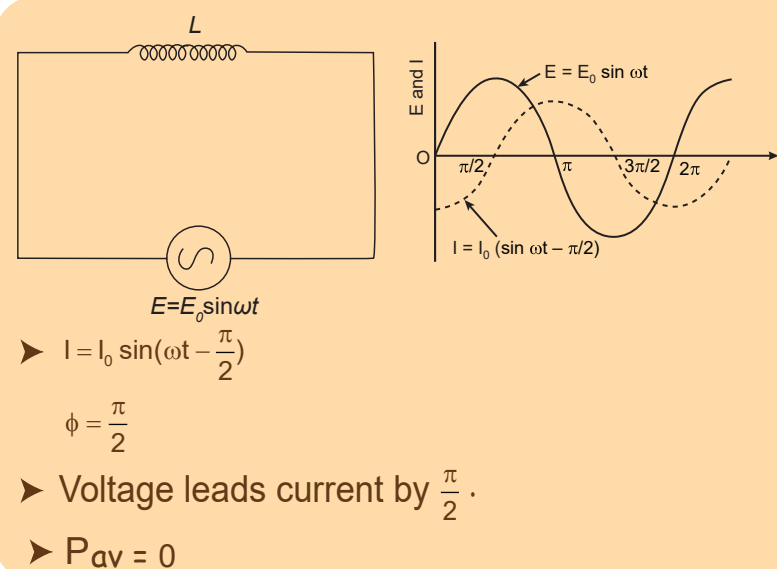

CAPACITIVE CIRCUIT

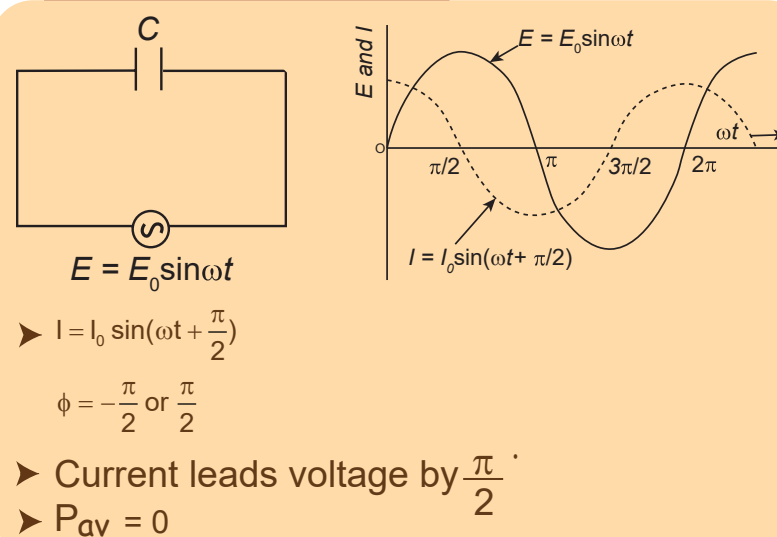


L - R CIRCUIT

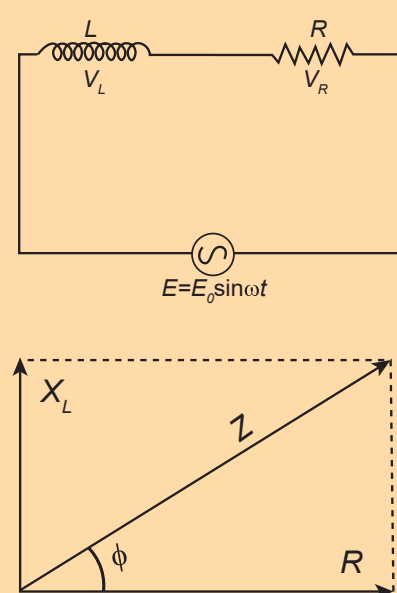


- $I = I_0 \sin(\omega t - \phi)$
- $Z = \sqrt{R^2 + X_L^2}$
- Inductive reactance, $X_L = \omega L$
- Phase angle $\phi = \tan^{-1}(\frac{X_L}{R})$

R - C CIRCUIT

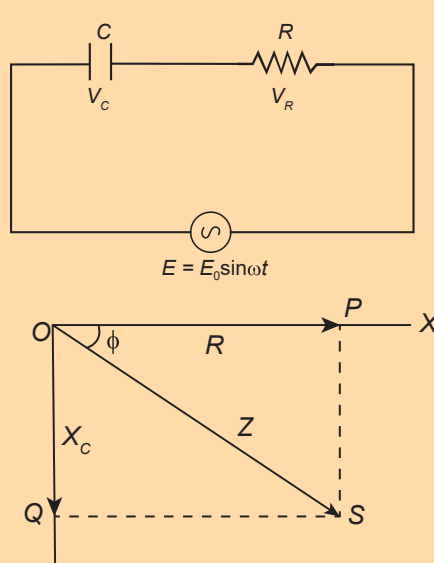


- $I = I_0 \sin(\omega t + \phi)$
- $Z = \sqrt{R^2 + X_C^2}$
- Capacitive reactance, $X_C = \frac{1}{\omega C}$
- $\phi = \tan^{-1}(\frac{X_C}{R})$

L C OSCILLATIONS

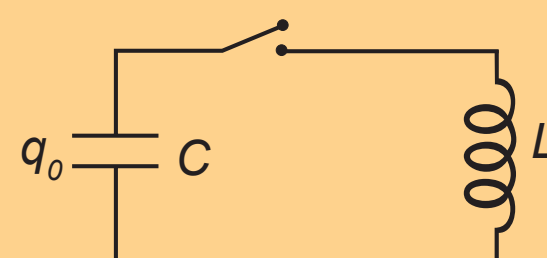


It is defined as the oscillation of energy between capacitor and inductor.

Frequency of Oscillation.

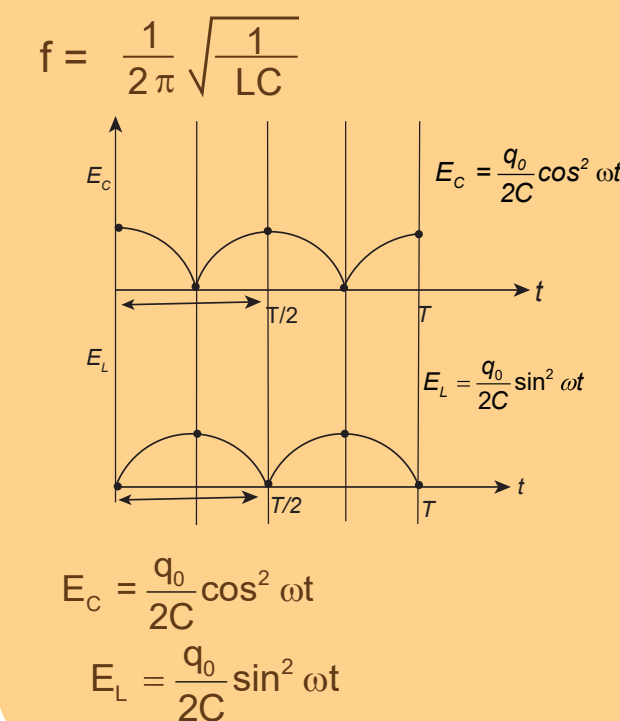


LCR CIRCUIT

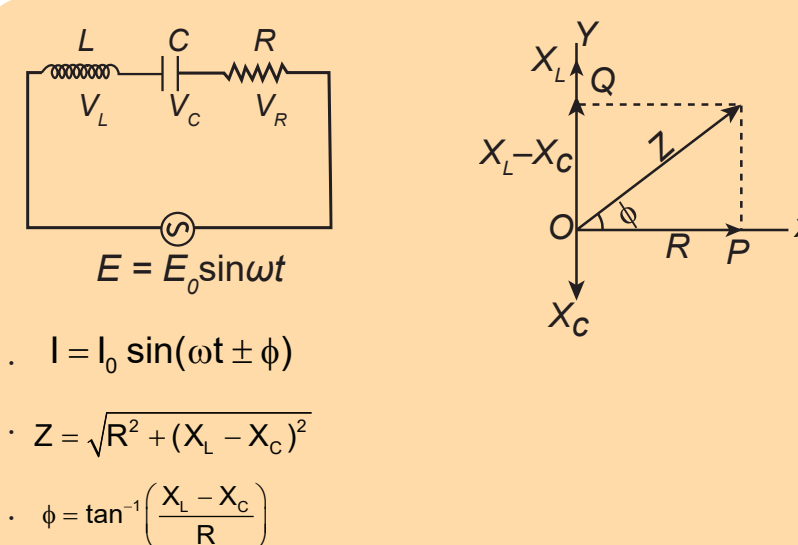


Variation of Z with F

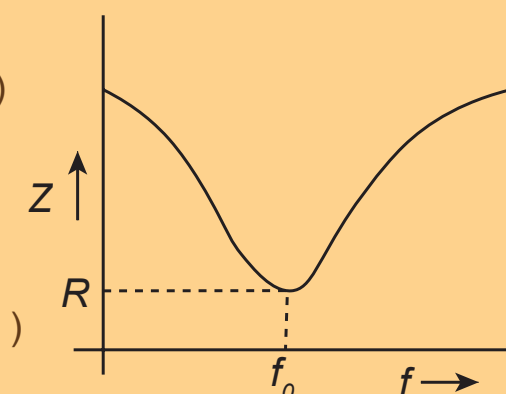- $f < f_0$, $X_L < X_C \Rightarrow \phi$ (negative)
 > Capacitive in nature.
- $f = f_0$, $X_L = X_C \Rightarrow \phi = 0$
 > Resistive in nature
- $f > f_0$, $X_L > X_C \Rightarrow \phi$ (Positive)
 > Inductive in nature.



TRANSFORMER

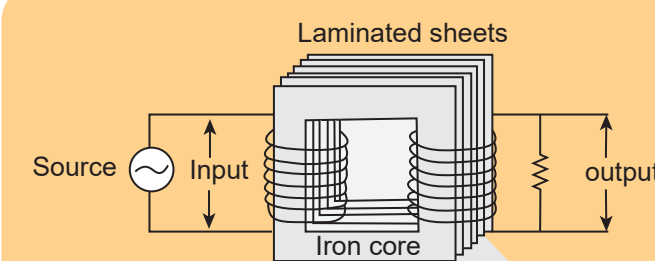

> Transformer ratio.

$$K = \frac{N_s}{N_p} = \frac{\text{No. of turns in Secondary}}{\text{No. of turns in Primary}}$$

ASSUMPTIONS

> No magnetic flux leakage.

$$\frac{E_s}{E_p} = \frac{N_s}{N_p}$$

> No power loss. efficiency (n) = 100%.


$$n = \frac{P_{out}}{P_{in}} \times 100\%, P_{in} = P_{out}$$

$$\frac{I_p}{I_s} = \frac{E_s}{E_p} = \frac{N_s}{N_p}$$

POWER CONSUMED IN AC CIRCUIT

- Average Power dissipation, $\langle P \rangle = E_{rms} I_{rms} \cos \phi$
- Power factor, $\cos \phi = \frac{\text{Average Power}}{\text{rms Power}} = \frac{R}{Z}$

wattless Current

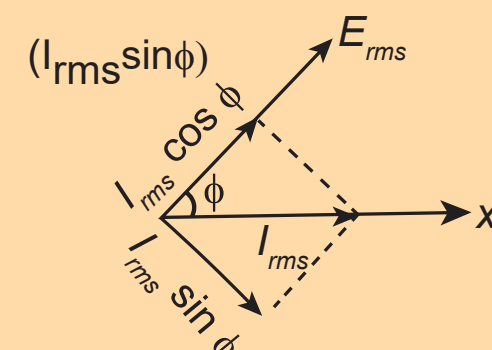


- When the power consumption in AC circuit is zero, then current is said to be wattless current.
- wattless current is a sine component of current

Half Power Frequency

- Frequency at which power becomes half of its maximum value.
- At half Power frequency, $\cos \phi = \frac{1}{2}$ or $\phi = 60^\circ$


Quality Factor

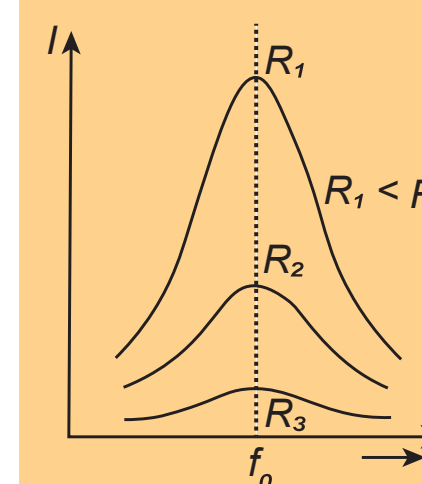

- It represents sharpness curve (I vs f).
- It is unitless and dimensionless.
- $Q = \frac{\omega_0 L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$
- $Q = \frac{f_0}{\text{band width } (\Delta f)}$
- Sharpness $\propto Q$

Variation of I with f

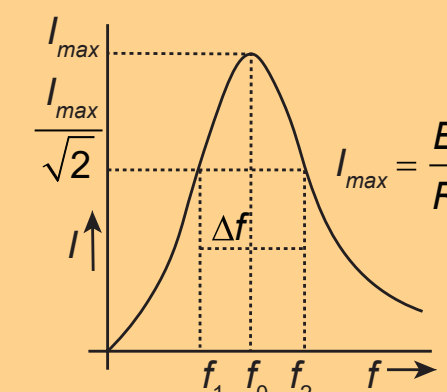- As frequency (f) increases current (I) decreases
- Band width, $\Delta f = f_2 - f_1$



RESONANCE IN SERIES LCR CIRCUIT

