
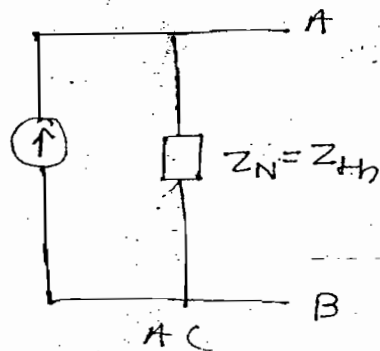
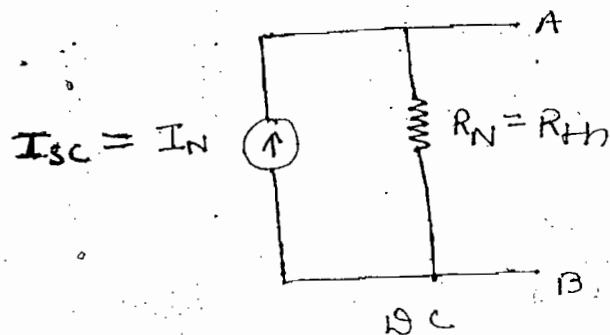



Lecture-7

Norton's theorem:-

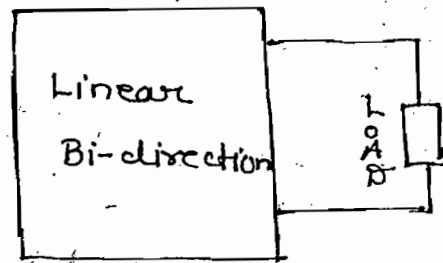In any linear bidirection circuit having more no. of active and passive element, it can be replaced by single equivalent ckt consisting of equivalent current source (I_N) in parallel with equivalent resistance (R_N)



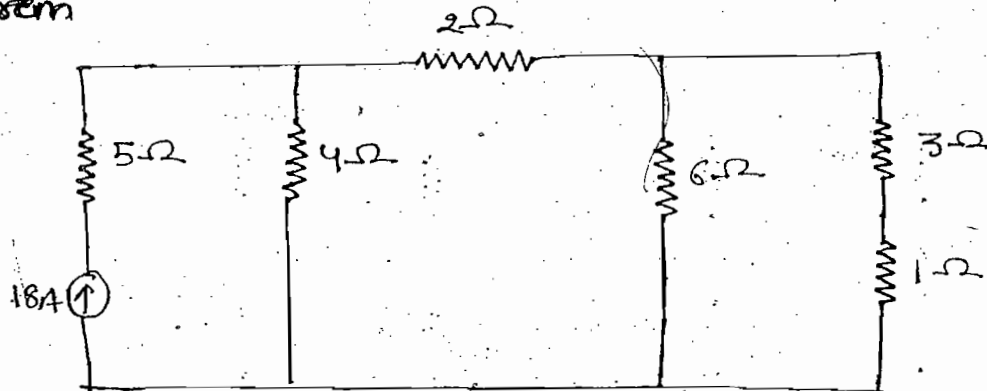ques:- Find current in 1Ω resistor using Norton's theorem




Soln:-


Case-(i):-

Replace the load resistor by S.C and find SC current

$$I_{sc} = 9 \times \frac{6}{6+3} = 6A$$

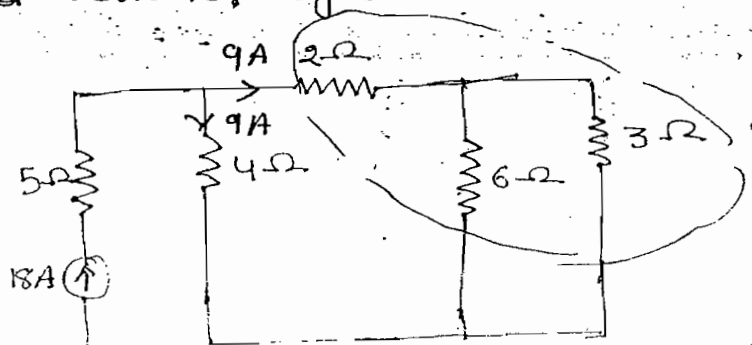


$$I_{sc} = 9A, \text{ Ans.}$$

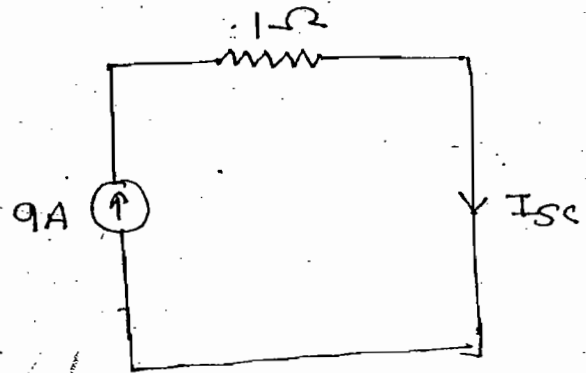

Ques:- Find o.c voltage and SC current w.r.t A & B


Soln:-

$$V_{oc} = 10V$$

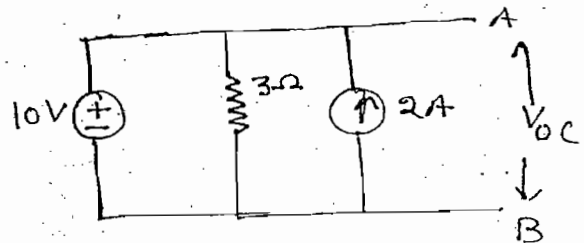

For I_{sc} :-


$$I_{sc} = \text{not possible}$$


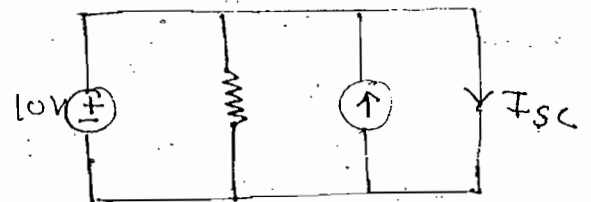


Note:-

In the above circuit it is not possible to find I_{sc} since it is not satisfying KVL

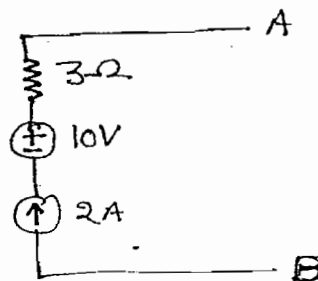Ques:- Find V_{oc} and I_{sc} w.r.t A and B



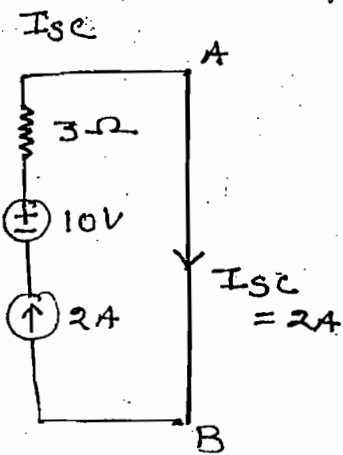
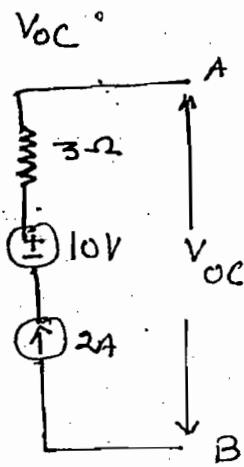


Note:-

In above circuit it is not possible to find O.C voltage since it is not satisfying KCL

ques:- Find I_{sc} w.r.t A and B

Soln:-

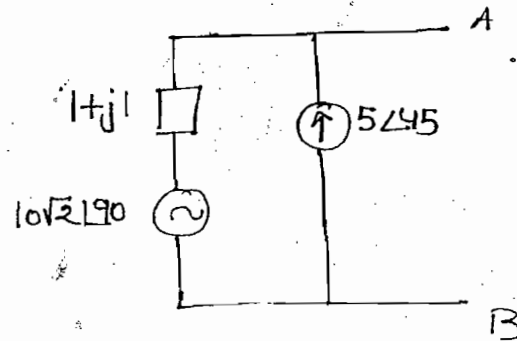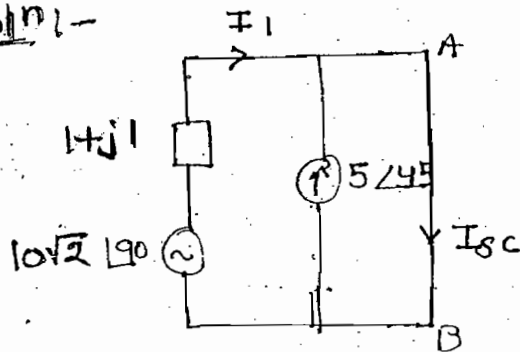

$$I_1 = \frac{10\sqrt{2} \angle 90^\circ}{\sqrt{2} \angle 45^\circ} = 10 \angle 45^\circ$$

$$I_1 + 5 \angle 45^\circ = I_{sc}$$

$$10 \angle 45^\circ + 5 \angle 45^\circ = I_{sc}$$

$$\Rightarrow I_{sc} = 15 \angle 45^\circ$$

ques:- Find current in 4Ω resistor using the following data:


soln:-

$$V_{oc} = 60$$

$$I_{sc} = 10A$$


$$R_{th} = \frac{V_{oc}}{I_{sc}} = \frac{60}{10} = 6\Omega$$

V	60	0
I	0	10A

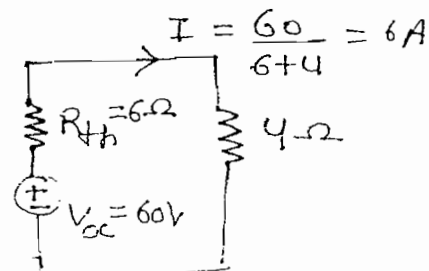

Reciprocity theorem:-

Case-(i):-

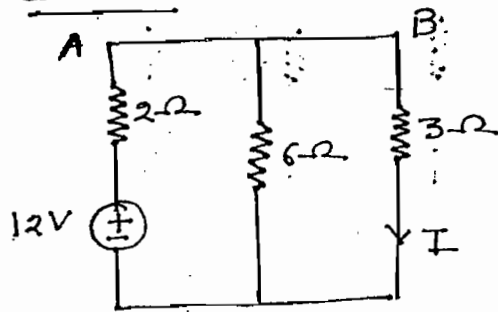


$$R_{eq} = 2 + \frac{6 \times 3}{6+3} = 4$$

$$I_T = \frac{12}{4} = 3A$$

$$I = 3 \times \frac{6}{6+3} = 2A$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{12} = \frac{1}{6}$$

Case-(ii):-

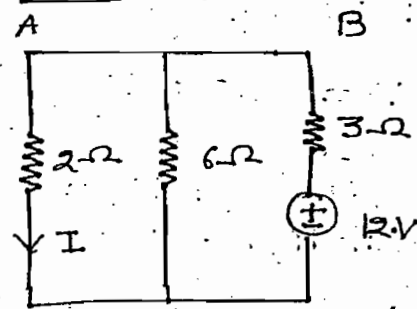

$$R_{eq} = 3 + \frac{6 \times 2}{6+2}$$


$$I_T = \frac{12}{R_{eq}}$$

$$I = I_T \times \frac{6}{6+2} = 2A$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{12} = \frac{1}{6}$$

In above N/w after interchanging position of response and excitation the ratio of response to excitation is constant. Hence given N/w satisfy the reciprocity (Linear bi-directional element)

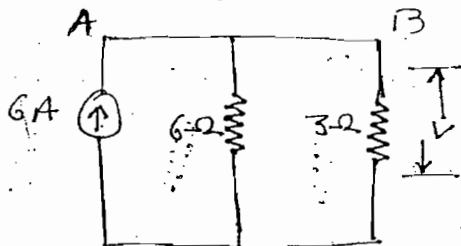ques:- Verify Reciprocity theorem of the circuit shown.




Soln:- Case-(i):-

$$I = 6 \times \frac{6}{6+3} = 4A$$

$$V = 3 \times 4 = 12$$
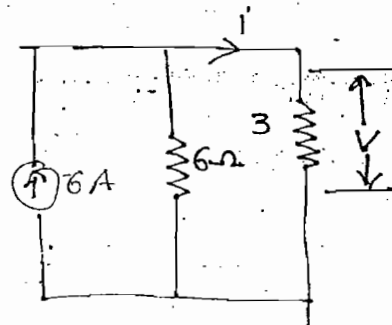
$$\frac{\text{Response}}{\text{Excitation}} = \frac{12}{6} = 2$$




Case-(11):-

$$i_1 = 6 \frac{3}{3+6} = 2A$$


$$V = 6 \times 2 = 12$$

$$\frac{\text{Response}}{\text{Excitation}} = \frac{12}{6} = 2$$

→ Satisfy Reciprocity

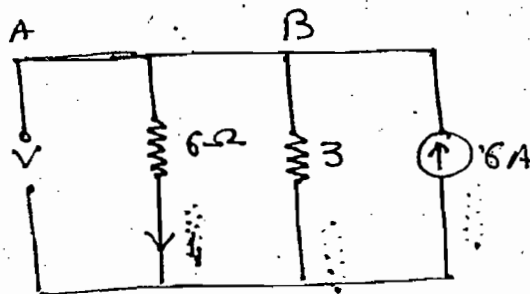

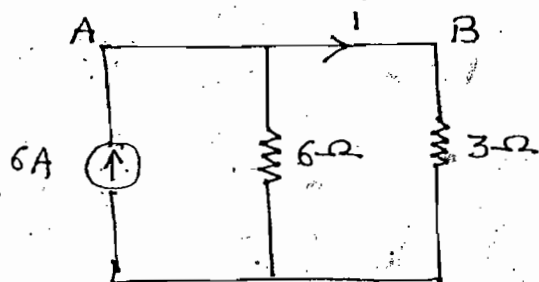
ques:- Verify Reciprocity theorem of the ckt shown:-



Soln:-


Case-(1)

$$i = 6 \frac{6}{6+3} = 4A$$

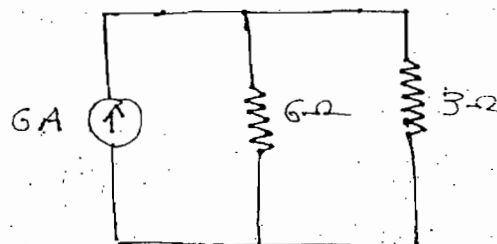

Case-(11)

$$i = 0$$

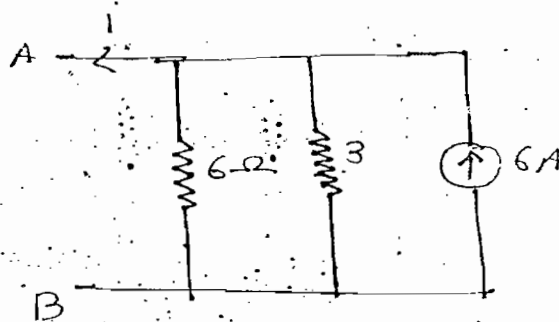

Note:- For above problem

$$(i) \frac{\text{Response}}{\text{Excitation}} = \frac{I}{V_s} = \text{mho}$$

$$(iii) \frac{\text{Response}}{\text{Excitation}} = \frac{i}{I_s}$$

$$(ii) \frac{\text{Response}}{\text{Excitation}} = \frac{V}{I_s} \rightarrow \Omega$$

$$(iv) \frac{\text{Response}}{\text{Excitation}} = \frac{V}{V_s}$$

No units


Note:-

For the above N/w Reciprocity theorem can't be applied since unit of response to excitation should be neither mho or Ω

Note:-

- 1- To apply Reciprocity theorem unit of Res/Exc. should be either mho or ohm
2. While applying reciprocity theorem N/w should consist of only one independent source
3. While applying reciprocity theorem N/w should not consist of any dependent sources

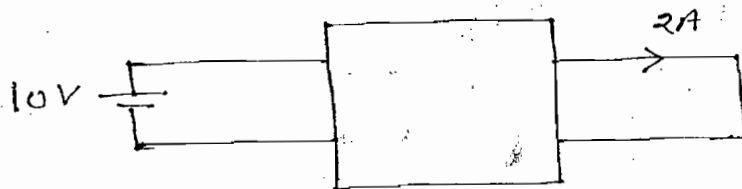
Ques:- When given N/w satisfy the Reciprocity then find the value of I



Soln:-

$$\frac{\text{Response}}{\text{Excitation}} = \frac{2}{10} = \frac{-I}{30} \Rightarrow I = -6A$$

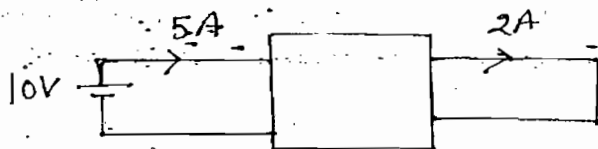Ques:- When given N/w satisfy the Reciprocity then find the value of I




Solⁿ:- Solⁿ by using Superposition & Reciprocity
 (∵ more than one independent sources are present)

Case-(I) (30V):-

$$\frac{\text{Response}}{\text{Excitation}} = \frac{I^I}{30} = \frac{2}{10}$$


$$\Rightarrow I^I = 6A$$

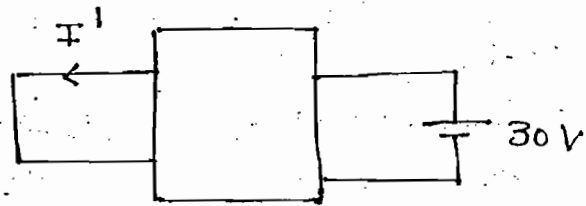

Case-(II) (30V):-


$$\frac{\text{Response}}{\text{Excitation}} = \frac{-I^{II}}{30} = \frac{5}{10}$$

$$\Rightarrow I^{II} = -15$$

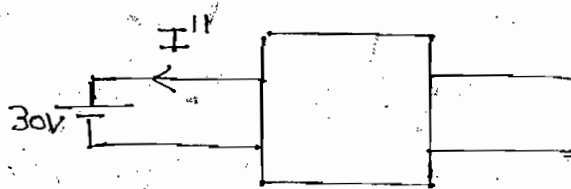

$$I = I^I + I^{II} = 6 - 15 = -9A$$

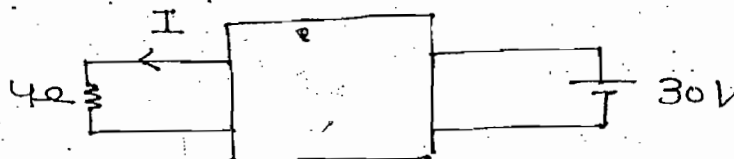Ques:- When given N/w satisfy the Reciprocity find the value of I



Solⁿ:- Case-(I) (I_{sc}):- (Norton's theorem)


$$\frac{\text{Response}}{\text{Excitation}} = \frac{I_{sc}}{30} = \frac{2}{10}$$

$$I_{sc} = 6A$$




Case 2 (R_{th}) :-


$$R_{th} = \frac{10}{5} = 2\Omega$$

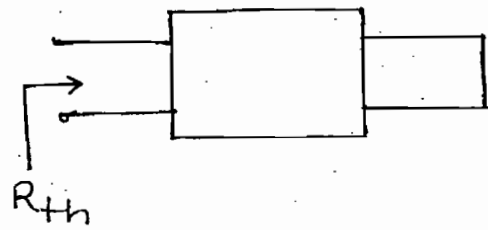

$$I = 6 \times \frac{2}{2+4} = 2A$$

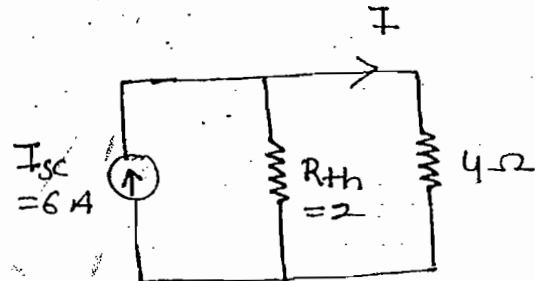

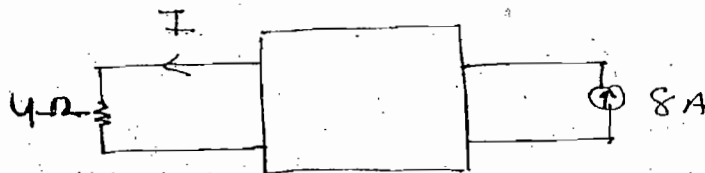ques:- When given N/w satisfy the Reciprocity Find the value of I



Soln:- Case (I) (V_{th}) :-


$$\frac{\text{Response}}{\text{Excitation}} = \frac{V_{th}}{8} = \frac{4}{5}$$

$$\Rightarrow V_{th} = \frac{32}{5}$$




Case (II) (R_{th}) :-

$$R_{th} = \frac{10}{5} = 2\Omega$$

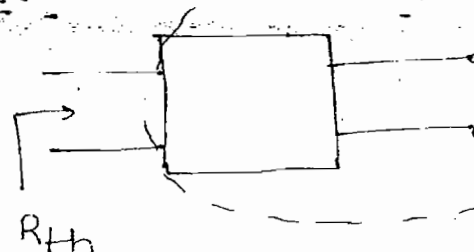
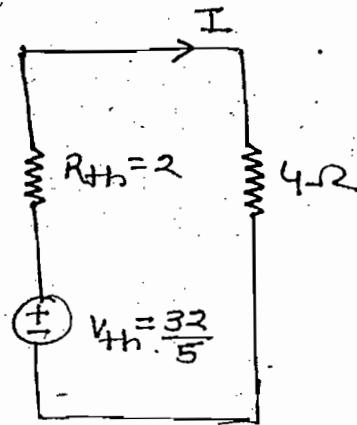
$$I = \frac{32/5}{2+4} = \frac{32}{5} \times \frac{1}{6} = \frac{16}{15} A$$



Maximum Power Transfer theorem: — (variable = constant)

$$I = \frac{V_s}{R_s + R_L}$$

$$P_L = I^2 R_L$$

$$\Rightarrow P_L = \left(\frac{V_s}{R_s + R_L} \right)^2 R_L \quad \text{--- (1)}$$

Diff. eq. (1) w.r.t. R_L and equated to zero, we get

$$R_L = R_s$$


$$P_{\max} = \frac{V_s^2}{(R_L + R_L)^2} R_L$$


$$\Rightarrow \boxed{P_{\max} = \frac{V_s^2}{4R_L}}$$

$$\eta = \frac{\text{o/p}}{\text{i/p}} \times 100$$

$$\eta = \frac{I^2 R_L}{I^2 (R_L + R_s)} \times 100 \Rightarrow \eta = \frac{R_L}{R_L + R_L} \times 100$$

$$\Rightarrow \boxed{\eta = 50\%}$$

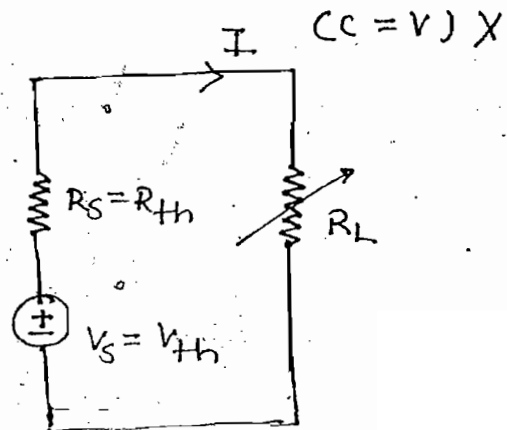

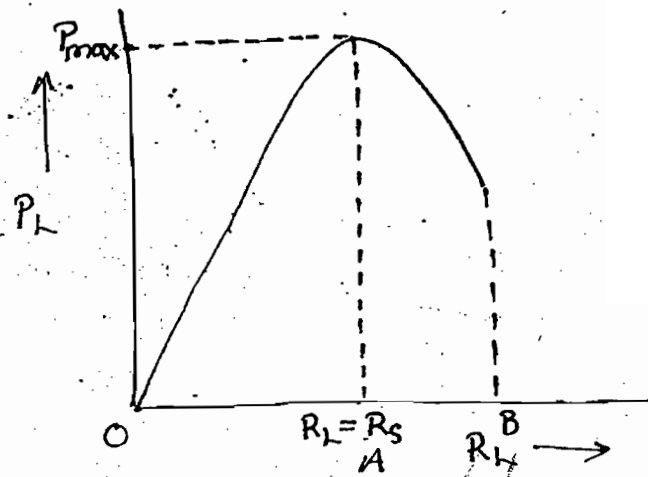

Case - (I) :-

$OA \Rightarrow R_S > R_L$

$\eta < 50\%$

Case - (II) :-

At point A $\Rightarrow R_S = R_L = R_S$


$\eta = 50\%$

Case - (III) :-


$AB \Rightarrow R_L > R_S$

$\eta > 50\%$


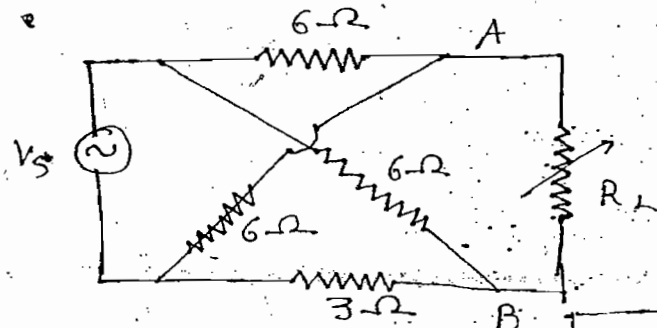
ques :- Find R_L to obtain max. power from source to load



Soln :-

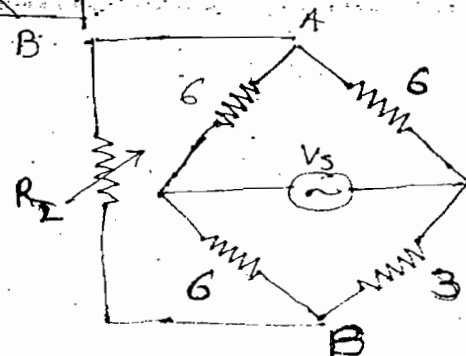


R_{th} :-

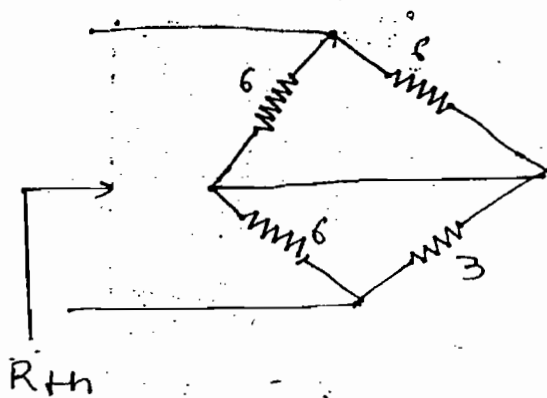
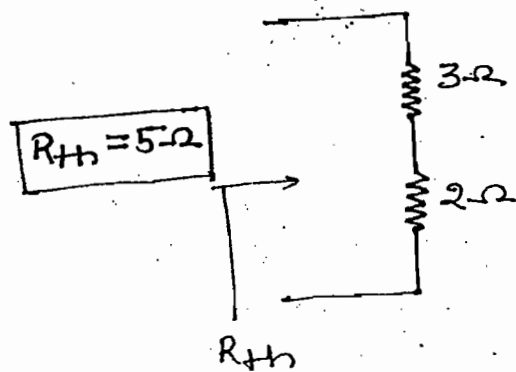


$$R_L = R_{th} = 5\Omega$$

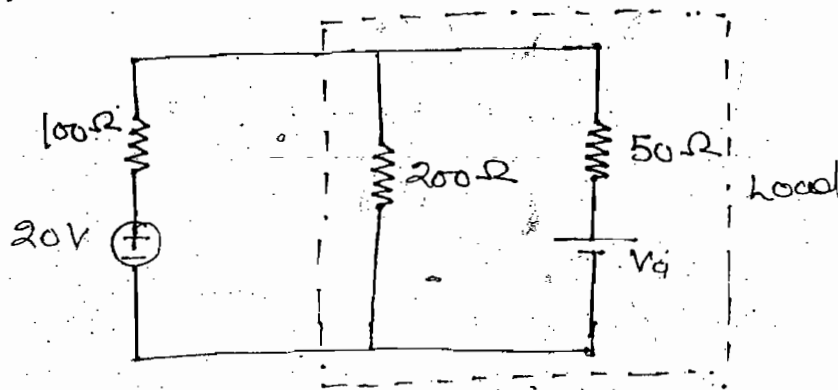ques:- Find V_a to obtain max. power from source to load.



Note:-

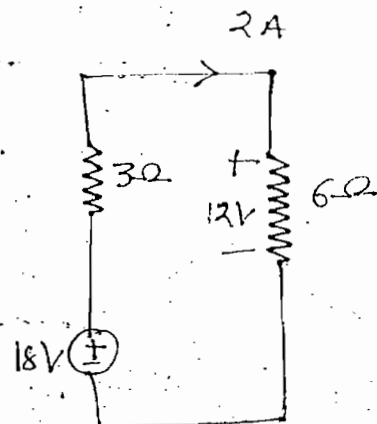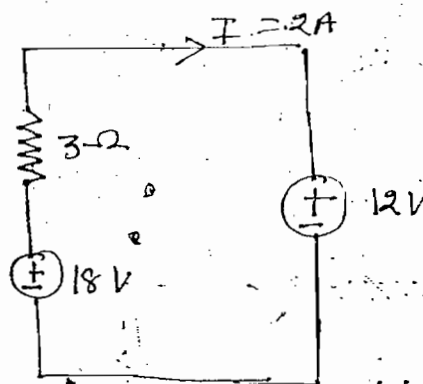


Soln:- $(R_{eq})_L = R_S = 100$

$$(R_{eq})_L = \frac{200(50+R)}{200+50+R}$$

$$\Rightarrow 100 = \frac{200(50+R)}{250+R}$$

$$\Rightarrow \boxed{R = 150\Omega}$$

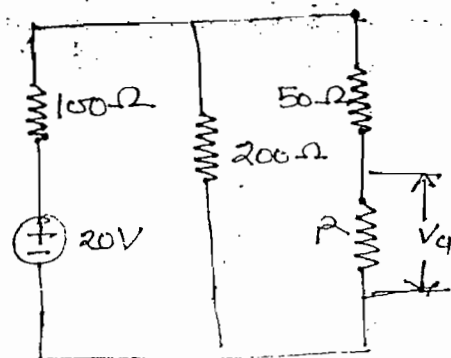


$$I_T = \frac{20}{R_S + (R_{eq})_L}$$

$$I_T = \frac{20}{100+100} = \frac{1}{10} \text{ A}$$

$$V_d = \frac{I_T}{2} R = 7.5 \text{ volts, Ans}$$

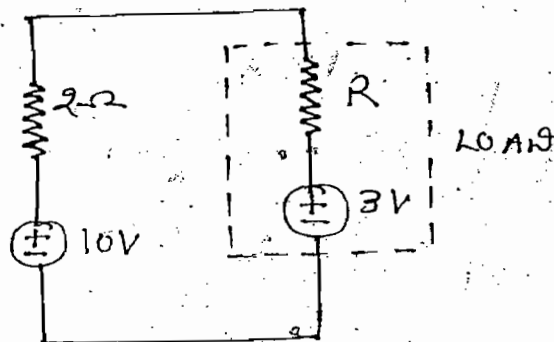ques:- Find resistance R to obtain maximum power from source to load




Soln:- $(R_{eq})_L = R_S = 2\Omega$

$$I_T = \frac{10}{R_S + (R_{eq})_L}$$


$$I_T = \frac{10}{2+2} = 2.5 \text{ A}$$

$$I_T = \frac{10-3}{2+R} = 2.5 \Rightarrow \boxed{R = 0.8\Omega} \text{ Ans}$$

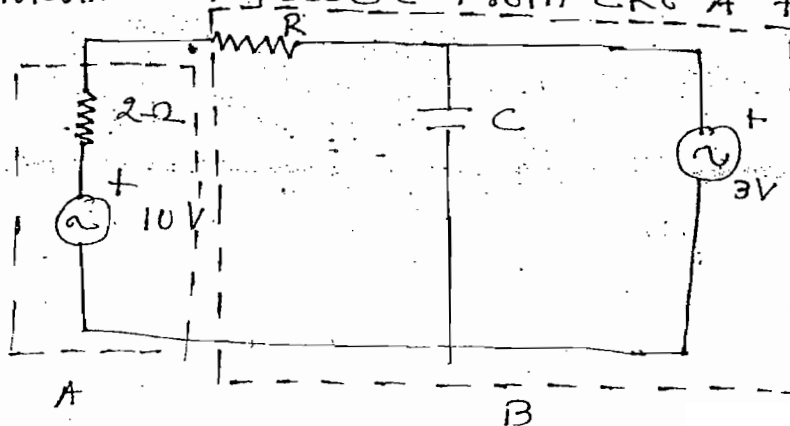ques:- In the figure shown find resistance R to obtain maximum power from ckt A to ckt B



Note:-

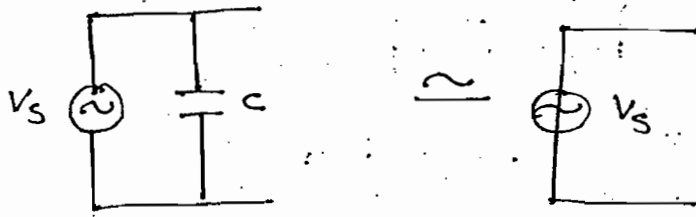


Solⁿ:-

$$R = 0.8 \Omega$$

Maximum Power Transfer theorem (For AC):-

$$i = \frac{V_{th}}{(R_L + R_{th}) + j(X_L + X_{th})}$$
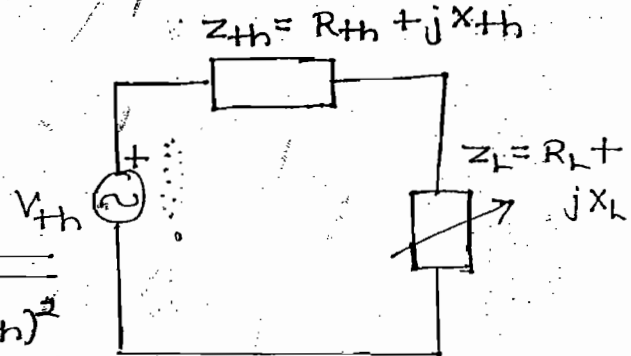
$$i = \frac{V_{th}}{\sqrt{(R_L + R_{th})^2 + (X_L + X_{th})^2}}$$



$$P_L = i^2 R_L$$

$$P_L = \frac{V_{th}^2 R_L}{(R_L + R_{th})^2 + (X_L + X_{th})^2} \quad \text{--- (1) ---}$$

→ Max Power transfer is applicable only for active power

Case (I):-

Both R_L & X_L are variable

(i) Diff. eq-(1) w.r.t R_L and equated to zero

(ii) Diff. eq-(1) w.r.t X_L and equated to zero

we get

$$\boxed{R_L + jX_L = R_{th} - jX_{th}}$$
$$\boxed{Z_L = Z_{th}^*}$$

Putting these values in eq-(1), we get

$$\boxed{P_{max} = \frac{V_{th}^2}{4R_L}}$$
$$\boxed{\eta = 50\%}$$

Case (II): —

Only R_L is variable. ($X_L = \text{constant}$)

→ Diff. eq-(I) w.r.t R_L and equated to zero

$$R_L = |Z_{th} + jX_L| = |R_{th} + j(X_{th} + X_L)|$$

$$R_L = \sqrt{R_{th}^2 + (X_L + X_{th})^2}$$

$$\eta = \frac{R_L}{R_L + R_{th}} \times 100$$

$$\boxed{\eta \geq 50\%}$$

Case (III): —

Load impedance is only resistive ($X_L = 0$)

$$P_L = \frac{V_{th}^2 R_L}{(R_L + R_{th})^2 + X_{th}^2} \quad \text{--- (II)}$$

Diff. eq-(II) w.r.t R_L and equated to zero, we get

$$R_L = \sqrt{R_{th}^2 + X_{th}^2}$$

$$R_L = |Z_{th}|$$

$$R_L > R_{th}$$

$$\boxed{\eta > 50}$$

Case-(IV): —

Both R_L & $X_L \rightarrow$ Variable But load


impedance $\rightarrow$ Cons
angle $\rightarrow$ const

$$Z_L = R_L + jX_L$$

$$\text{load impedance angle} = \theta_L = \tan^{-1}\left(\frac{X_L}{R_L}\right) = \text{constant}$$

$$R_L = Z_L \cos \theta_L$$

$$X_L = Z_L \sin \theta_L$$

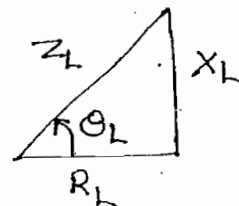


$$P_L = \frac{V_{th}^2 Z_L \cos \theta_L}{(Z_L \cos \theta_L + R_{th})^2 + (Z_L \sin \theta_L + X_{th})^2} \quad \text{--- (iii)}$$

Diff. eq-(iii) w.r.t Z_L and equated to zero, we get

$$Z_L = Z_{th}$$

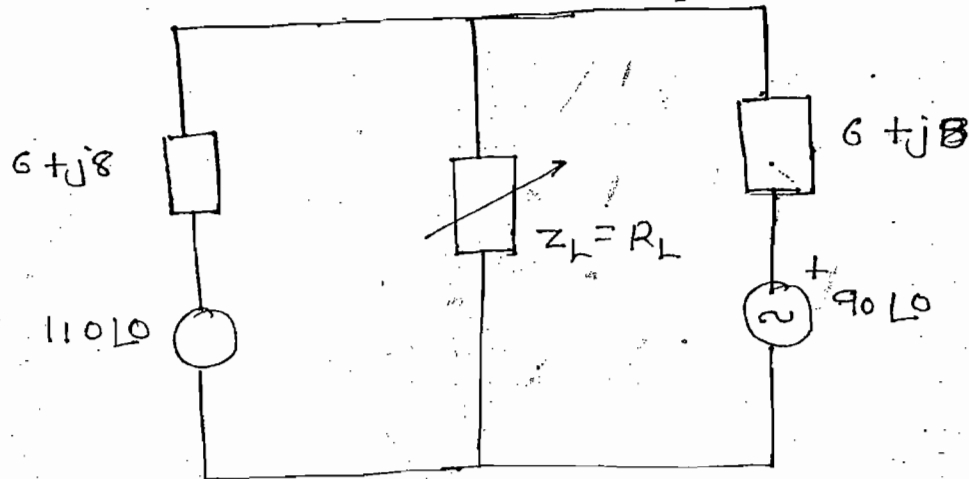
ques:- Find max. power dissipation in load impedance



Soln:- Case-(i) :- (V_{th})

$$\frac{V_{th} - 110\angle 0}{6 + j8} + \frac{V_{th} - 90\angle 0}{6 + j8} = 0$$


$$V_{th} = 100\angle 0$$

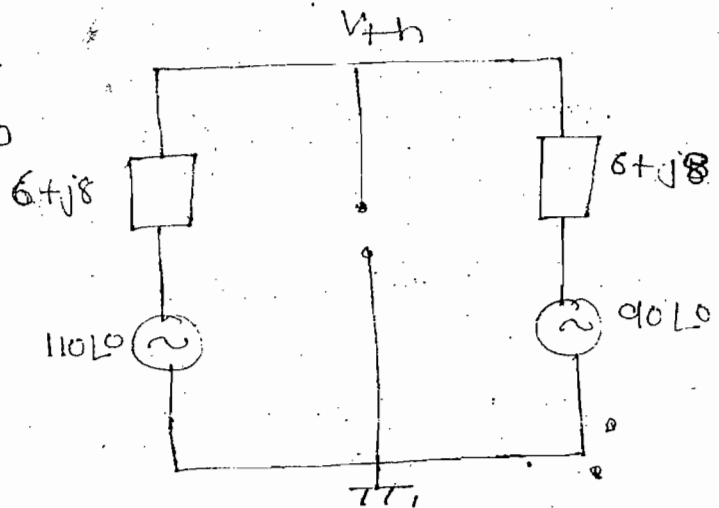

Case-(ii) (Z_{th}) :-

$$Z_{th} = \frac{6 + j8}{2}$$

$$Z_{th} = 3 + j4$$

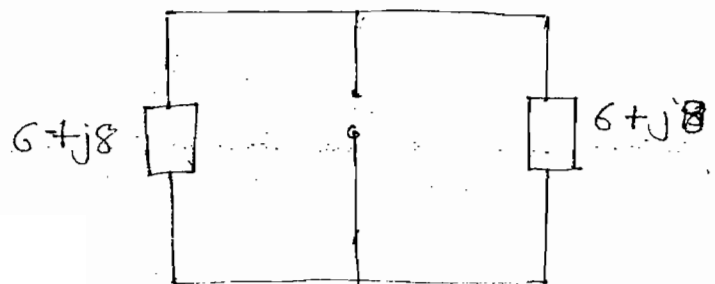

$$R_L = \sqrt{R_{Th}^2 + X_{Th}^2} = \sqrt{3^2 + 4^2} = 5$$


$$i = \frac{100 \angle 0}{3 + j4 + 5} = \frac{100}{8 + j4}$$

$$= \frac{100}{\sqrt{8^2 + 4^2}}$$


$$P_L = i^2 R_L$$

 $\Rightarrow$

$$P_L = 625 \text{ W}$$

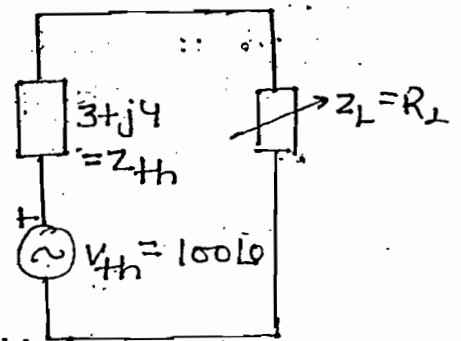

Millman's theorem:-

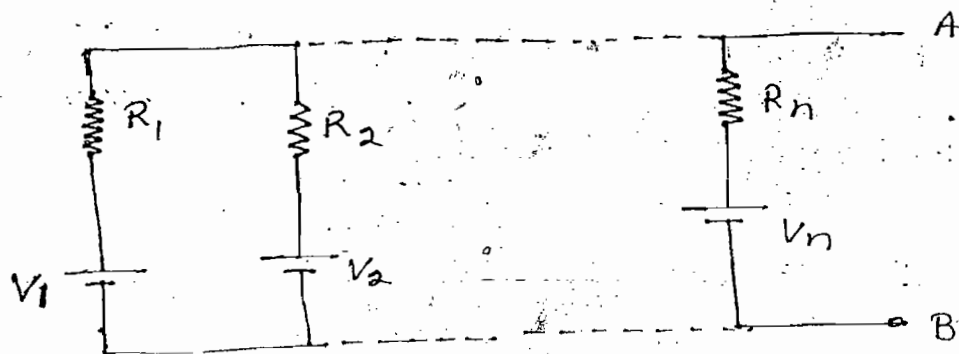


$$R' = R_{Th}$$

$$\frac{1}{R'} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}$$

$$R' = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_n}}$$
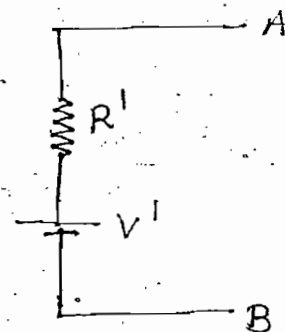
$$R' = \frac{1}{G_1 + G_2 + \dots + G_n}$$




$$V_{Th} = I_{Sc} R_{Th}$$

$$V' = I' R'$$

$$V' = \frac{V_1/R_1 + V_2/R_2 + \dots + V_n/R_n}{1/R_1 + 1/R_2 + \dots + 1/R_n}$$


49
4A 4A
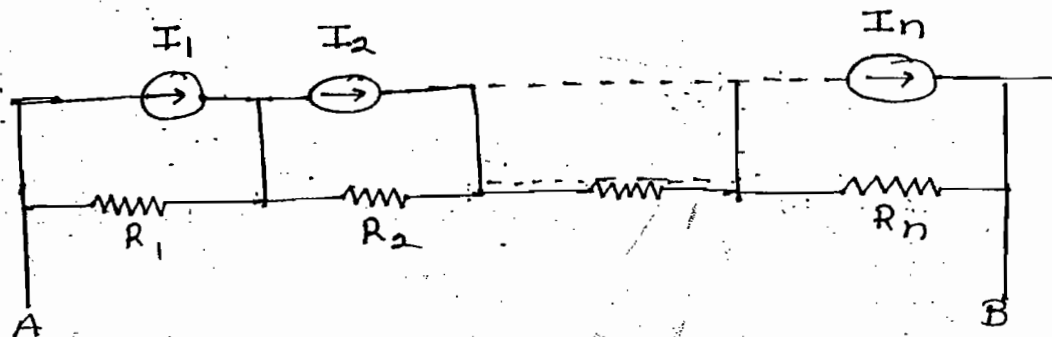
$$V' = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$



$$R' = R_{th}$$

$$R' = R_1 + R_2 + \dots + R_{th}$$


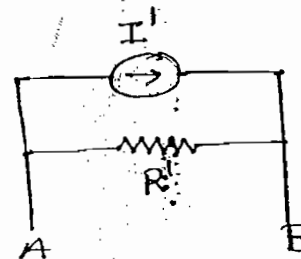


$$I_{sc} = \frac{V_{oc}}{R_{th}}$$

$$I' = \frac{V'}{R'}$$

$$I' = \frac{I_1 R_1 + I_2 R_2 + \dots + I_n R_n}{R_1 + R_2 + \dots + R_n}$$

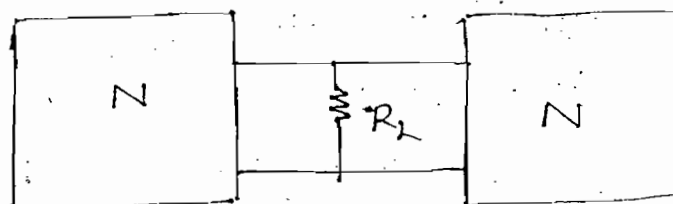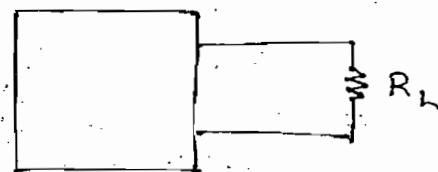Ques:- When complex N/w of N is connected to load resistor power dissipation in the load resistor is P Watts. When two identical complex N/w of N are connected to same load resistor. Find power dissipation in the load resistor



(a) P (b) 2P

(c) 4P (d) P to 4P

Soln]-





$$I = \frac{V_{th}}{R_L + R_{th}}$$

$$P = I^2 R_L$$

$$P = \left(\frac{V_{th}}{R_L + R_{th}} \right)^2 R_L \quad (i)$$

$$V' = \frac{\frac{V_{th}}{R_{th}} + \frac{V_{th}}{R_{th}}}{\frac{1}{R_{th}} + \frac{1}{R_{th}}} = V_{th}$$
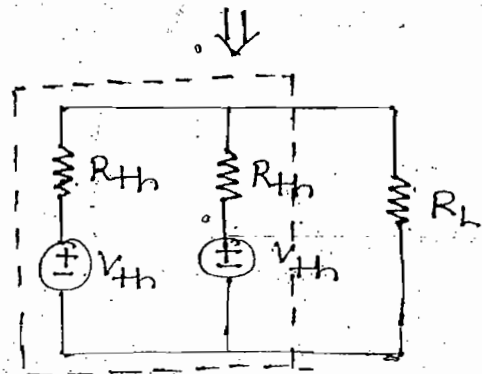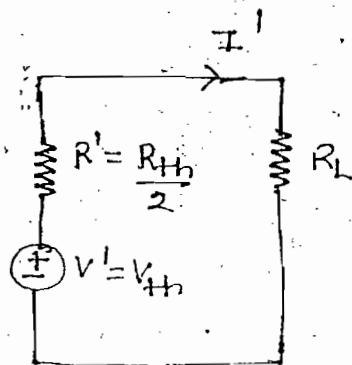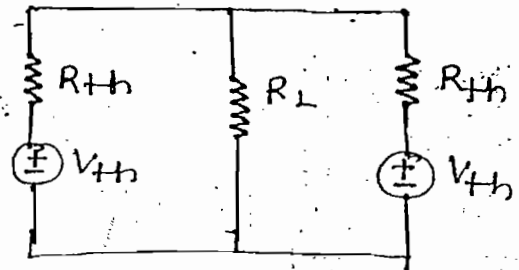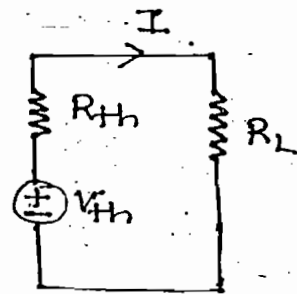
$$R' = \frac{1}{\frac{1}{R_{th}} + \frac{1}{R_{th}}} = \frac{R_{th}}{2}$$




$$I' = \frac{V_{th}}{R_L + \frac{R_{th}}{2}} = \frac{2V_{th}}{2R_L + R_{th}}$$

$$P' = I'^2 R_L = \left(\frac{2V_{th}}{2R_L + R_{th}} \right)^2 R_L \quad (ii)$$

Comparing eq-(i) & (ii) we get option-d

Ques]- Find I of the circuit shown

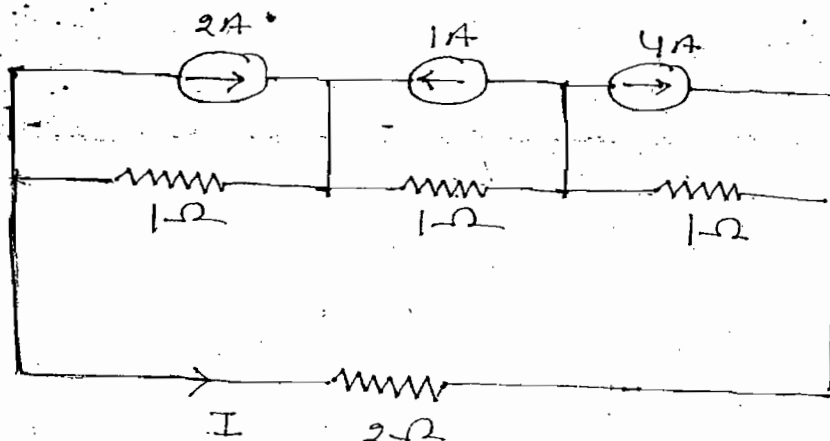


Soln)-

$$I' = \frac{(2 \times 1) - (1 \times 1) + (4 \times 1)}{1+1+1} = \frac{5}{3} \quad I' = \frac{5}{3} A$$


$$R' = 1+1+1 = 3 \Omega$$
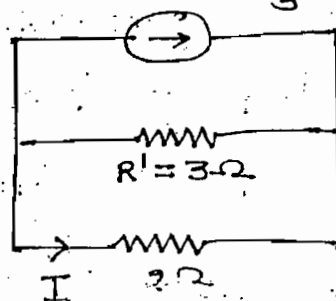
$$I = -\frac{5}{3} \frac{3}{3+2} = -1 A$$



Tellegen's theorem:-

$$\sum_{k=1}^n V_k I_k = 0$$

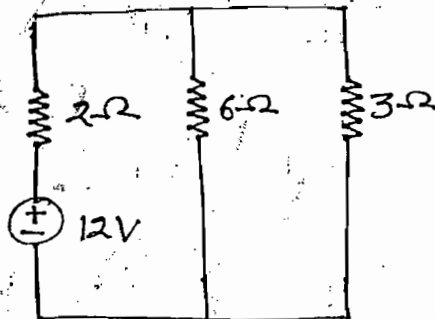

Tellegen's theorem states that algebraic sum of the powers in any circuit at any instant is equal to zero (linear, non-linear, unidirectional, bidirectional, time variant and time invariant elements)

$$R_{eq} = 2 + \frac{6 \times 3}{6+3} = 4$$

$$I_T = \frac{12}{4} = 3 A$$

$$I_6 = 3 \frac{3}{3+6} = 1 A \quad I_3 = 3 - 1 = 2 A$$

$$V_2 = I_T \times 2 = 6$$

$$V_6 = V_3 = 2 \times 3 = 6$$

$$V_2 I_T + V_6 I_6 + V_3 I_3 - V_S I_T$$


$$18 + 6 + 12 - 12 \times 3 = 0$$

Note:-

→ Tellegen's theorem is verified by using KCL and KVL equations

→ Tellegen's theorem works, based on the principle of law of conservation of energy.

Compensation theorem:-

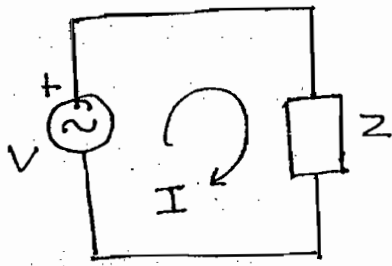


$$I = \frac{V}{Z}$$



$$\Delta I = |I - I'|$$


(Clockwise)
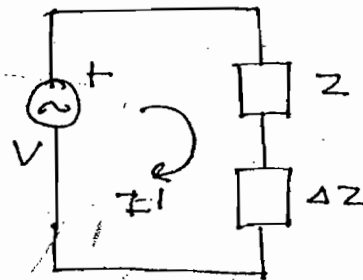
$$\Delta I = \frac{-I\Delta Z}{Z + \Delta Z}$$



$$I' = \frac{V}{Z + \Delta Z}$$

Modified circuit:-

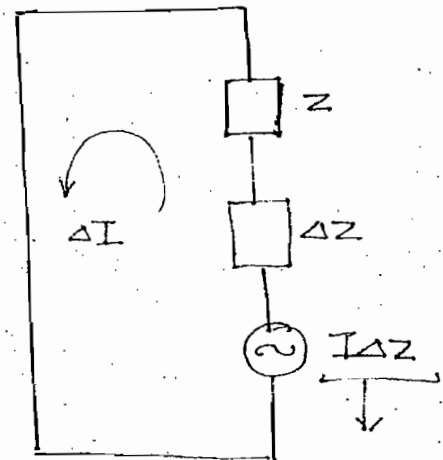

Compensation
emf
or
opposing emf