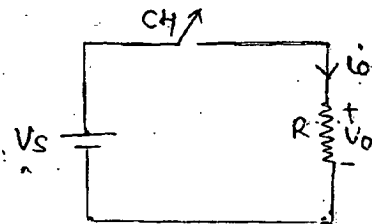


Choppers

Fixed dc $\longrightarrow$ Variable dc
 (V_s) (V_o)

(1) Step down chopper $\longrightarrow$ $(V_o < V_s)$ (Buck converter)

For R load $\rightarrow$




$$V_o = V_s \left(\frac{T_{on}}{T} \right)$$

$$V_o = \alpha V_s$$

$$V_{or} = \sqrt{\alpha} V_s$$

$$\alpha = \frac{T_{on}}{T}$$

(duty cycle)

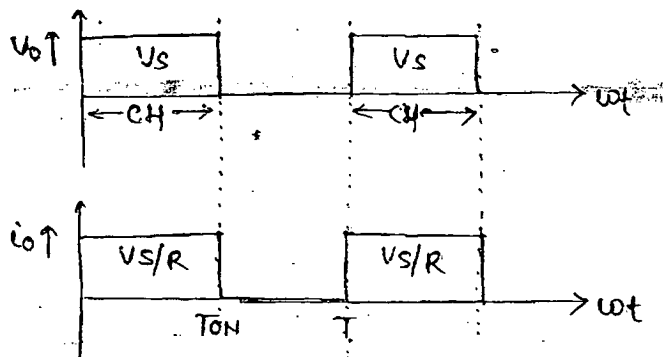

Fourier Series for o/p voltage

$$V_o = \alpha V_s + \sum_{n=1}^{\infty} \frac{2V_s}{n\pi} \sin n\pi\alpha \cdot \sin(n\omega t + \phi_n)$$

where $\phi_n = \tan^{-1} \left(\frac{\cos n\alpha}{\sin n\alpha} \right)$

$$V_{on} = \frac{2V_s}{n\pi} \sin n\pi\alpha \sin(n\omega t + \phi_n)$$

$V_{on} = 0$. then $n\alpha = 1$

$$\alpha = \frac{1}{n}$$

Condⁿ to eliminate n th harmonics

$$FF = \frac{V_{on}}{V_o} = \frac{\sqrt{\alpha} V_s}{\alpha V_s}$$

$$FF = \frac{1}{\sqrt{\alpha}}$$

$$V_{RF} = \sqrt{FF^2 - 1}$$


$$\downarrow V_{RF} = \sqrt{\frac{1}{\alpha} - 1}$$

$$\boxed{\alpha \uparrow, V_{RF} \downarrow \therefore \text{Harmonics} \downarrow}$$


* If it is continuous conduction there is ^{effect of} no back emf in the o/p voltage waveform.

Therefore the o/p Vol. waveform is remain same for RL & RLE load.

For RLE load $\rightarrow$

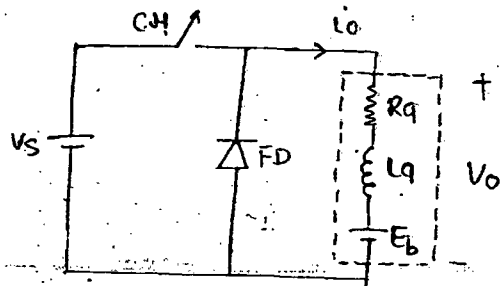

DC Motor

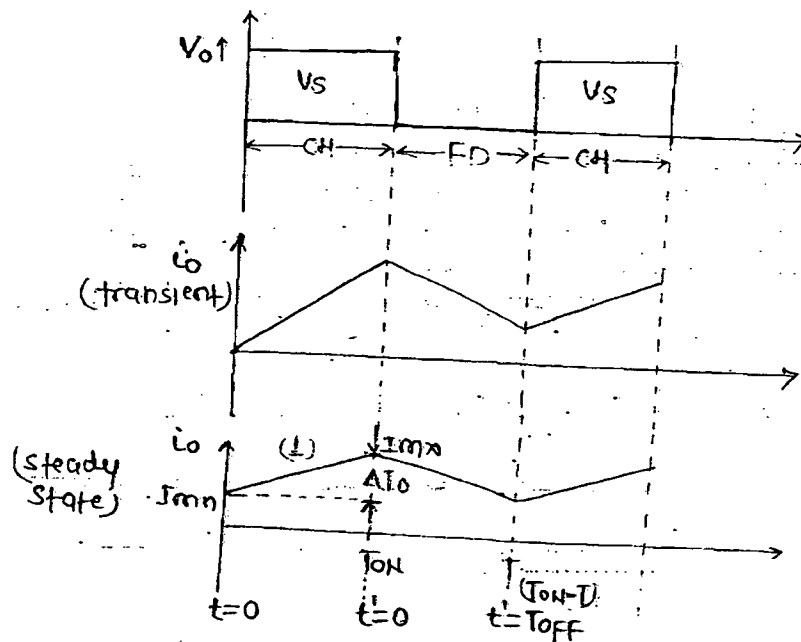

At transient the value of current will 1st starts from 0 value & then goes to steady state value

$$V_o = V_s \left(\frac{T_{ON}}{T} \right)$$

$$\boxed{V_o = \alpha V_s}$$

$$\boxed{V_{or} = \sqrt{\alpha} V_s}$$

RL & RLE

$$I_o = \frac{V_o - E_b}{R_q}$$

$$\boxed{I_o = \frac{\alpha V_s - E_b}{R_q}}$$

RLE

$$\boxed{I_o = \frac{\alpha V_s}{R_q}}$$

RL


 * Avg. current does not depend on load inductance but the ripple current depends on the load inductance.

* mod(I.) ($0 \leq t \leq T_{ON}$)

CH $\rightarrow$ ON (KVL)

$$V_s = R_a i_o + L_a \frac{di_o}{dt} + E_b$$

$$V_s - E_b = R_a i_o + L_a \frac{di_o}{dt}$$

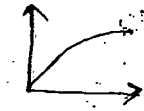($\tau_a = \frac{L_a}{R_a}$) $i_o = \frac{V_s - E_b}{R_a} (1 - e^{-t/\tau_a})$ [eqn from starting to 0] (transient) 

$i_o = \frac{V_s - E_b}{R_a} (1 - e^{-t/\tau_a}) + I_{mn} e^{-t/\tau_a}$ [From the I_{mn} value (steady state)] (i)

$I_{mx} = \frac{V_s - E_b}{R_a} (1 - e^{-T_{ON}/\tau_a}) + I_{mn} e^{-T_{ON}/\tau_a}$ (ii)

mode (II) $\rightarrow$ ($T_{ON} \leq t \leq T$) (or) ($0 \leq t' \leq T_{OFF}$)

FD $\rightarrow$ ON $\therefore$ (KVL)

$$R_a i_o + L_a \frac{di_o}{dt} + E_b = 0$$

$$-E_b = R_a i_o + L_a \frac{di_o}{dt}$$

$i_o = \frac{-E_b}{R_a} (1 - e^{-t'/\tau_a}) + I_{mx} e^{-t'/\tau_a}$ (iii)

$I_{mn} = \frac{-E_b}{R_a} (1 - e^{-T_{OFF}/\tau_a}) + I_{mx} e^{-T_{OFF}/\tau_a}$ (iv)

By solving the eqn (ii) & (iv) we can find the values of I_{mx} & I_{mn} .

$I_{mx} = \frac{V_s}{R_a} \left[\frac{1 - e^{-T_{ON}/\tau_a}}{1 - e^{-T/\tau_a}} \right] - \frac{E_b}{R_a}$ (v)

$I_{mn} = \frac{V_s}{R_a} \left[\frac{e^{T_{ON}/\tau_a} - 1}{e^{T/\tau_a} - 1} \right] - \frac{E_b}{R_a}$ (vi)

$$\text{Ripple Current} = I_{mx} - I_{mn}$$

$$\Delta I_o = \frac{V_s}{R_q} \left[\frac{(1 - e^{-T_{on}/\tau_q})}{(1 - e^{-T/\tau_q})} - \frac{(e^{-T_{on}/\tau_q} - 1)}{(e^{-T/\tau_q} - 1)} \right]$$

$$\Delta I_o = \frac{V_s}{R_q} \left[\frac{(1 - e^{-T_{on}/\tau_q})(1 - e^{-T_{off}/\tau_q})}{(1 - e^{-T/\tau_q})} \right] \quad [T = T_{off} + T_{on}]$$

$$\Delta I_o = \frac{V_s}{R_q} \left[\frac{(1 - e^{-\alpha T/\tau_q})(1 - e^{-(1-\alpha)T/\tau_q})}{1 - e^{-T/\tau_q}} \right] \quad \begin{matrix} T_{on} = \alpha T \\ T_{off} = (1-\alpha)T \end{matrix}$$

For max^m value of the max^m Ripple current

$$\frac{d(\Delta I_o)}{d\alpha} = \frac{d}{d\alpha} \left\{ \frac{V_s}{R_q} \left[\frac{(1 - e^{-\alpha T/\tau_q})(1 - e^{-(1-\alpha)T/\tau_q})}{(1 - e^{-T/\tau_q})} \right] \right\} = 0$$

$$\boxed{\alpha = 0.5}$$

$$(\Delta I_o)_{max} = \frac{V_s}{R_q} \left[\frac{(1 - e^{-0.5T/\tau_q})(1 - e^{-0.5T/\tau_q})}{(1 - e^{-T/\tau_q})} \right]$$

$$(\Delta I_o)_{max} = \frac{V_s}{R_q} \tanh \frac{T}{4\tau_q} \quad (\tanh x = x)$$

$$(\Delta I_o)_{max} = \frac{V_s}{R_q} \times \frac{T}{4\tau_q} = \frac{V_s}{R_q} \times \frac{T}{4 \times \frac{L_q}{R_q}} = \frac{V_s}{f} \times \frac{1}{4L_q}$$

$$\boxed{(\Delta I_o)_{max} = \frac{V_s}{4f \cdot L_q}}$$

(max^m value of Ripple current at $\alpha = 0.5$)

$$(1) \downarrow (\Delta I_o) \propto \frac{1}{f(L \uparrow)} \quad (\text{But equipment size will increase})$$

* By increasing the load inductance the ripple current reduce.


$$(2) \downarrow (\Delta I_o) \propto \frac{1}{(\uparrow f)L} \quad |$$

* At high chopping freq, we can eliminate the ripple current without increasing the size of inductor.

* Smc operates based on the above chopper principle.


* At low values of T_{ON} it gives discontinuous.

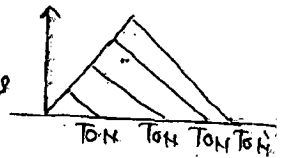$\alpha' =$ duty cycle limit for continuous



* Duty cycle limit for continuous conduction $\rightarrow$

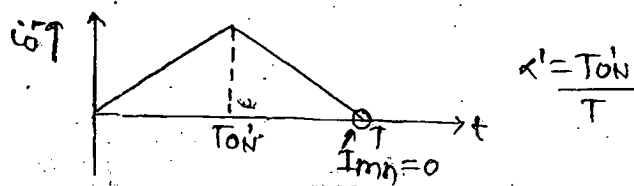* α' is the duty cycle at the boundary between continuous & discontinuous conduction.



at $t = T$, $I_m = 0$

$$\frac{V_s}{Rq} \left[\frac{e^{T_{ON}/\tau q} - 1}{e^{T/\tau q} - 1} \right] - \frac{E_b}{Rq} = 0$$

$$\frac{V_s}{Rq} \left[\frac{e^{T_{ON}/\tau q} - 1}{e^{T/\tau q} - 1} \right] = \frac{E_b}{Rq}$$

$$\frac{e^{T_{ON}/\tau q} - 1}{e^{T/\tau q} - 1} = \frac{E_b}{V_s}$$

$$(e^{T_{ON}/\tau q} - 1) = m(e^{T/\tau q} - 1) \quad \left(\frac{E_b}{V_s} = m \right)$$

$$e^{T_{ON}/\tau q} = m + 1 + m(e^{T/\tau q} - 1)$$

$$\frac{T_{ON}}{\tau q} = \ln [1 + m(e^{T/\tau q} - 1)]$$


$$\alpha' = \frac{T_{ON}}{T} = \frac{\tau q}{T} \ln [1 + m(e^{T/\tau q} - 1)]$$

$$\boxed{\alpha' = \frac{T_{ON}}{T} = \frac{\tau q}{T} \ln [1 + m(e^{T/\tau q} - 1)]}$$

$\alpha < \alpha' \rightarrow$ discontinuous

$\alpha > \alpha' \rightarrow$ Continuous

* Discontinuous Conduction $\rightarrow$

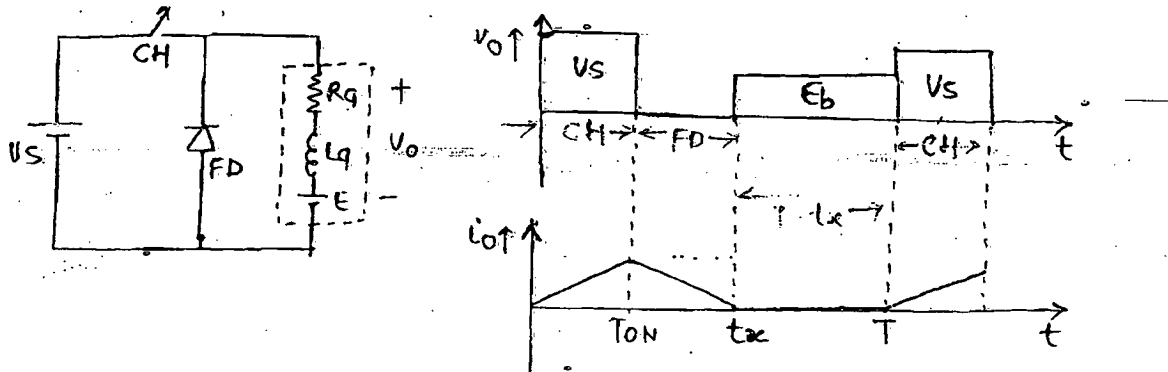

$$V_o = V_s \left(\frac{T_{ON}}{T} \right) + E_b \left(\frac{T - t_x}{T} \right)$$


($t_x \rightarrow$ Extinction time)

$$V_o = V_s \alpha + E_b \left(1 - \frac{t_x}{T} \right)$$

$$V_{or} = \left[V_s^2 \left(\frac{T_{ON}}{T} \right) + E_b^2 \left(\frac{T - t_x}{T} \right) \right]^{1/2}$$

$$V_{or} = \left[\alpha V_s^2 + E_b^2 \left(1 - \frac{t_x}{T} \right) \right]^{1/2}$$

Step up chopper $\rightarrow$

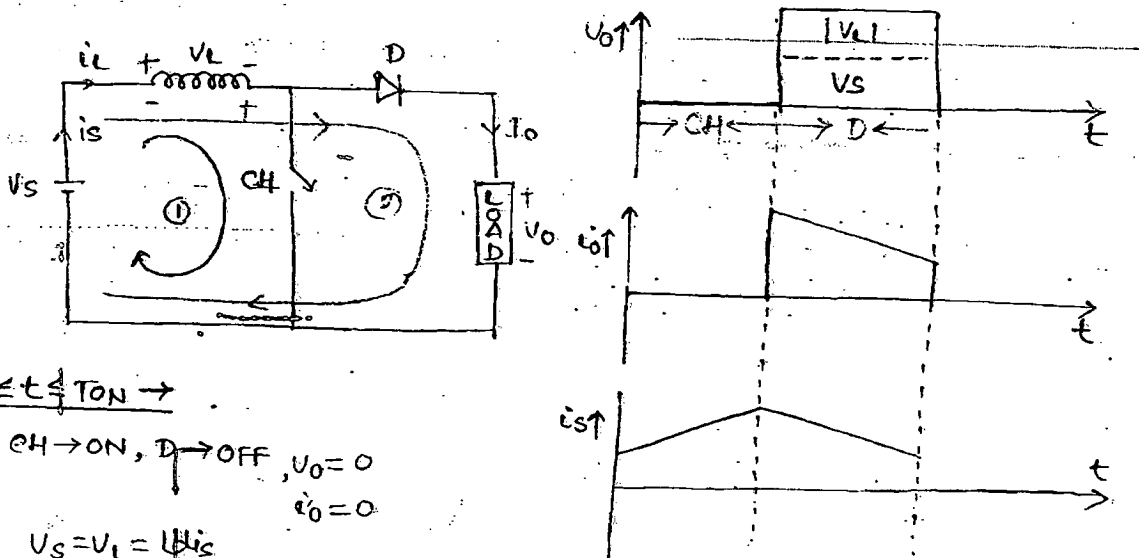

(I) $0 \leq t \leq T_{ON} \rightarrow$

CH $\rightarrow$ ON, D $\rightarrow$ OFF, $V_o = 0$
 $i_o = 0$


$$V_s = V_L = L \frac{di_o}{dt}$$

L $\rightarrow$ stores energy

(II) $T_{ON} \leq t \leq T \rightarrow$

CH $\rightarrow$ OFF, D $\rightarrow$ ON, $i_s = i_o$

Step up chopper
Boost converter

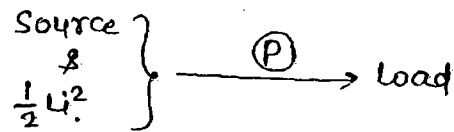

L $\rightarrow$ Releasing energy

$$V_o = V_s + |V_L|$$

$$V_o = \frac{V_s}{1-\alpha}$$


$$\alpha < 1, V_o > V_s$$

* In step up chopper power flows from low vol. side to high voltage side

* Step up chopper principle can be used for regenerative braking of dc m/c.

* Choppers with filters $\rightarrow$ * In order to reduce the harmonics & improve the quality of o/p waveform we have to use filters.

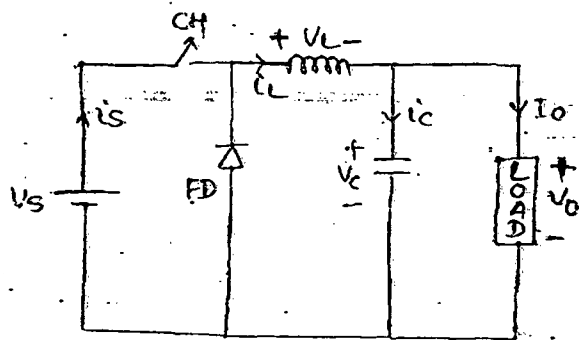* Step down chopper (Buck Converter) $\rightarrow$ For 1st order low pass filter we use resistance but in the resistance power loss occurs.



DC Component (I_L avg)
AC Component (At multiple Harmonic Freq.)



$$Area = \frac{\Delta I}{2} + I_{min}$$

* Let us assume very large value of filter capacitance. So that the o/p V_o remains almost constant.


$$X_c = \frac{1}{\omega C} \approx 0 \text{ (Ac comp) (Short circuited)}$$

$$X_c = \frac{1}{\omega C} \approx \infty \text{ (dc comp) (open circuited)}$$

* Capacitor will only allow only Ac comp. (Ripple)

* All the AC comp. will bypass through capacitor then,

$$\boxed{(\Delta I_L) = (\Delta I_C)}$$

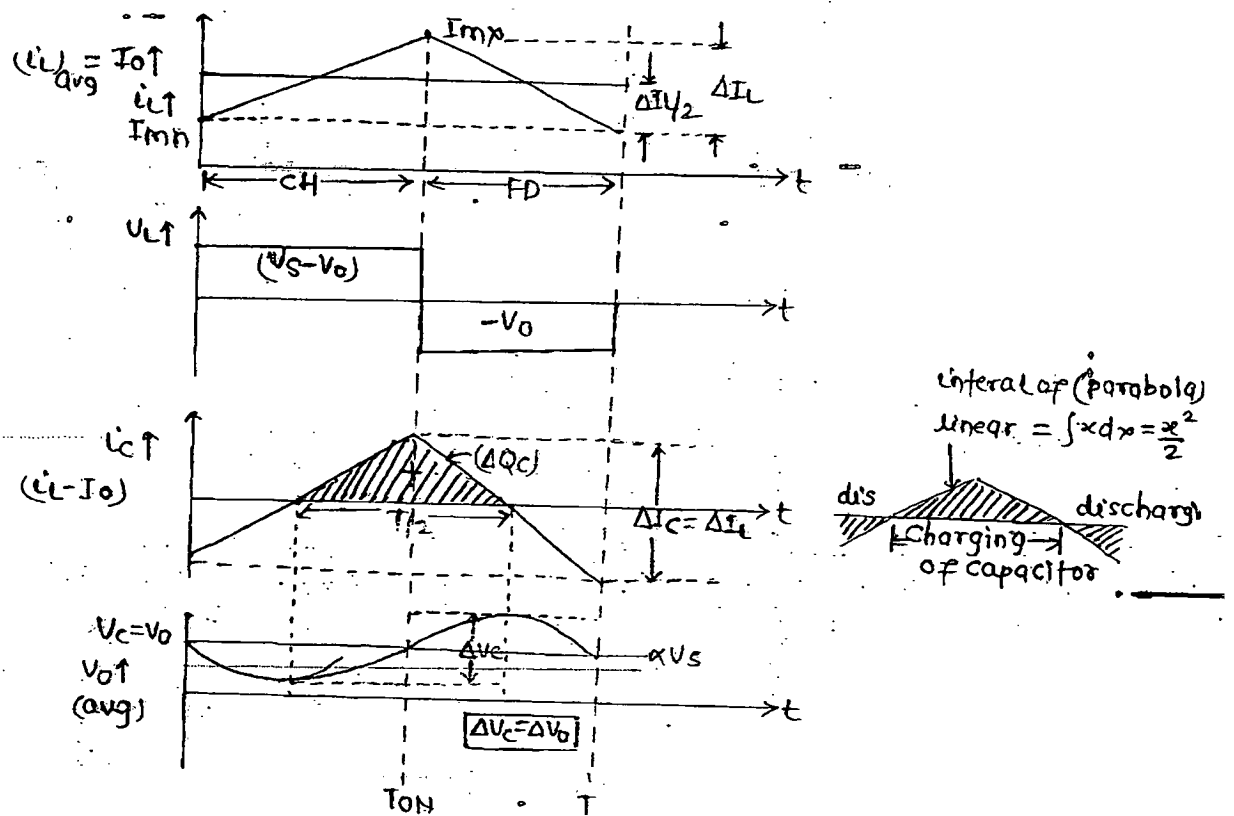

(1) $0 \leq t \leq T_{ON} \rightarrow CH \rightarrow ON$

$$-V_s + V_L + V_o = 0$$

$$V_L = V_s - V_o$$

$$L \frac{di_L}{dt} = V_s - V_o$$

$$\frac{di_L}{dt} = \frac{V_s - V_o}{L}$$

$$\int_{I_{min}}^{I_{max}} di_L = \frac{V_s - V_o}{L} \int_0^{T_{ON}} dt$$

$$\Delta I_L = \frac{V_s - V_o}{L} \cdot T_{ON}$$

$$= \frac{V_s - \alpha V_s}{L} \cdot \frac{\alpha}{f}$$

$$\left\{ \begin{array}{l} T_{ON} = \alpha T \\ = \frac{\alpha}{f} \end{array} \right.$$

$$\boxed{\Delta I_L = \frac{\alpha(1-\alpha)V_s}{fL}}$$

$$\boxed{(\Delta I_L)_{max} = \frac{V_s}{4fL} \rightarrow \text{at } \alpha = 0.5}$$

III) $T_{ON} \leq t \leq T \rightarrow CH \rightarrow OFF, FD \rightarrow ON$

$$+V_L + V_o = 0$$

$$V_L = -V_o$$

$$(V_L)_{avg} = 0$$


$$+ve \text{ area} + (-ve) \text{ area} = 0$$

$$(V_s - V_o) T_{ON} + V_o T_{OFF} = 0$$

$$V_s T_{ON} = V_o [T_{ON} + T_{OFF}]$$

$$V_o = V_s \kappa$$

$$\kappa = \frac{T_{ON}}{T}$$

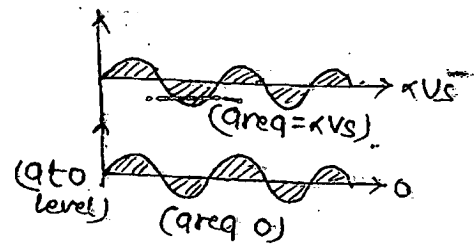

From the area of Δ in the waveform

$$\Delta Q = C \cdot \Delta V_c$$

$$\Delta V_c = \frac{\Delta Q}{C}$$

$$\Delta V_c = \frac{\Delta I_L}{8 f C}$$

$$\text{where } \Delta Q = \frac{1}{2} \cdot \frac{I}{2} \cdot \frac{\Delta I t}{2}$$


$$\Delta Q = \frac{\Delta I t}{8 f}$$

$$\Delta V_c = \frac{\kappa(1-\kappa)V_s}{8 f^2 L C} \quad \text{--- (2)}$$

* If we increase the value of $f \uparrow$ then ΔV_c will decrease. & we will get pure dc current ($\Delta V_c = 0$)

Critical inductance (L_c) It is the value of inductance at which I_L waveform is just discontinuous.

If L

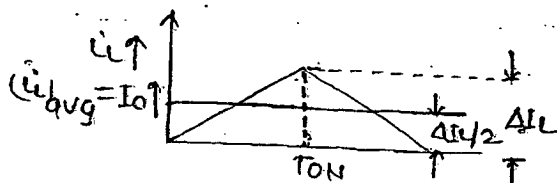

$$I_o = \frac{\Delta I_L}{2}$$

$$\frac{\kappa V_s}{R} = \frac{\kappa(1-\kappa)V_s}{2 f L C}$$

$$L_c = \frac{(1-\kappa) R}{2 f} \quad \text{--- (3)}$$

Critical capacitance $\rightarrow$ It is the value of capacitance at which the v_c - waveform is just discontinuous.

$$V_o = \frac{\Delta V_c}{2} \text{ (at } C_c)$$

$$V_o = \frac{\kappa(1-\kappa) V_s}{16 f^2 L C}$$

$$\kappa V_s = \frac{\kappa(1-\kappa) V_s}{16 f^2 L C_c}$$

$$C_c = \frac{(1-\kappa)}{16 f^2 L C} \text{ ----- (4.)}$$


$$P_o = P_{in}$$

$$V_o I_o = V_s I_s$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \kappa$$

$$I_s = \kappa I_o$$

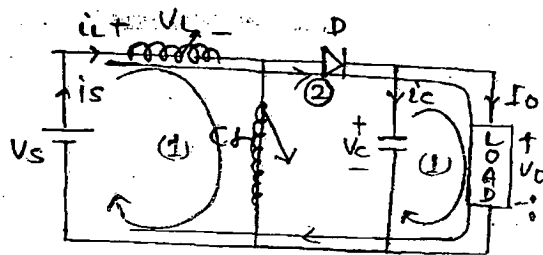* Step up chopper (Boost Converter) $\rightarrow$




$$i_L = i_c + i_o$$

$$(I_L)_{min} > (I_o)$$

139

* Let us assume large value of filter capacitance. So that the o/p vol. remains const

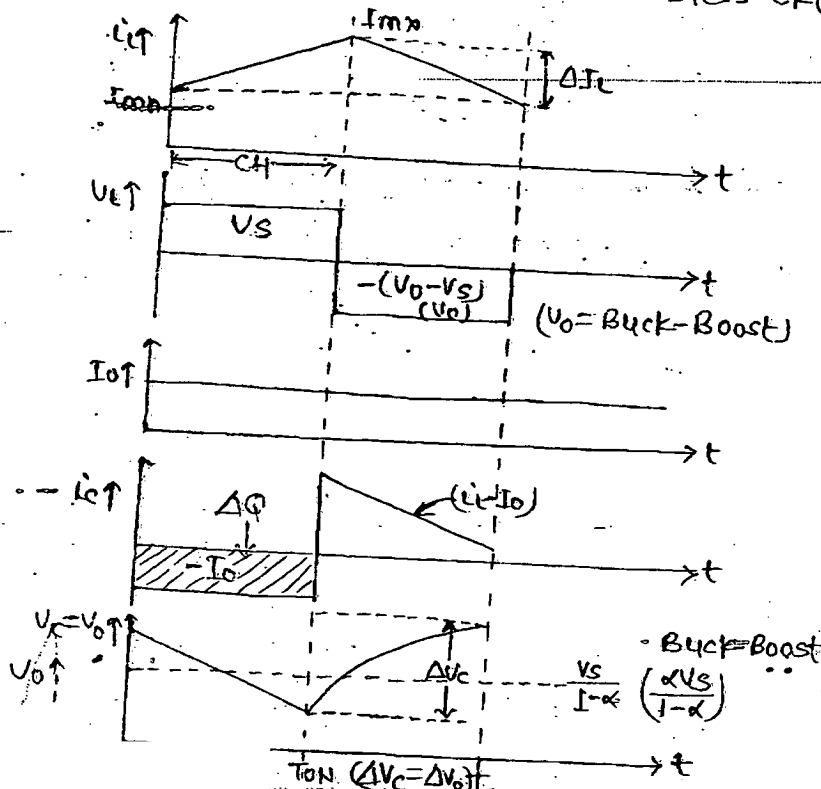* Let us assume const load current & it is a lossless ckt (ideal ckt)



(I) $0 \leq t \leq T_{ON}$

CH $\rightarrow$ ON, D $\rightarrow$ OFF

$$i_C = -I_O$$

$$V_L = V_S$$

$$L \frac{di_L}{dt} = V_S$$

$$\int_{I_{min}}^{I_{max}} di_L = \int_0^{T_{ON}} \frac{V_S}{L} dt$$

$$\Delta I_L = \frac{V_S}{L} T_{ON}$$

$$\Delta I_L = \frac{\alpha V_S}{fL} \quad (1)$$

(II) $T_{ON} \leq t \leq T$

CH $\rightarrow$ OFF, D $\rightarrow$ ON

$$i_C = i_C + I_O$$

$$-V_S + V_L + V_O = 0$$

$$V_L = V_S - V_O$$

$$* V_L = -(V_S - V_O)$$

* $(V_O > V_S)$
step up

$$V_{avg} = 0$$

$$V_S T_{ON} - (V_O - V_S) T_{OFF} = 0$$

$$V_S (T_{ON} + T_{OFF}) = V_O T_{OFF}$$

$$V_S \alpha = V_O (1 - \alpha)$$

$$V_O = \frac{V_S}{1 - \alpha}$$

$$P_O = P_{in}$$

$$V_O I_O = V_S I_S$$

$$\frac{V_O}{V_S} = \frac{I_S}{I_O} = \frac{1}{(1 - \alpha)}$$

$$I_S = \frac{I_O}{(1 - \alpha)}$$

$$\Delta Q = C \Delta V_C$$

$$\Delta V_C = \frac{\Delta Q}{C} = \frac{I_O T_{ON}}{C}$$

$$\Delta V_C = \frac{\alpha I_O}{fC} \quad (2)$$

$$T_{ON} = \alpha T = \frac{\alpha}{f}$$

Critical Inductance (L_c) →

$$I_o = \frac{\Delta I_L}{2} \quad (\text{at } L_c)$$

$$\frac{V_s}{(1-\alpha)R} = \frac{\alpha V_s}{2fL_c}$$

$$L_c = \frac{\alpha(1-\alpha)R}{2f} \quad \text{--- (3.)}$$

Critical capacitance (C_c) →

$$V_o = \frac{\Delta V_c}{2}$$

$$I_o R = \frac{\alpha I_o}{2fC_c}$$

$$C_c = \frac{\alpha}{2fR} \quad \text{--- (4.)}$$


Non-ideal case → (Practical)

r → internal resistance of inductance


R → Load resistance.

$$V_o = \frac{V_s(1-\alpha)}{\frac{r}{R} + (1-\alpha)^2} \quad \text{(Not in syllabus)}$$

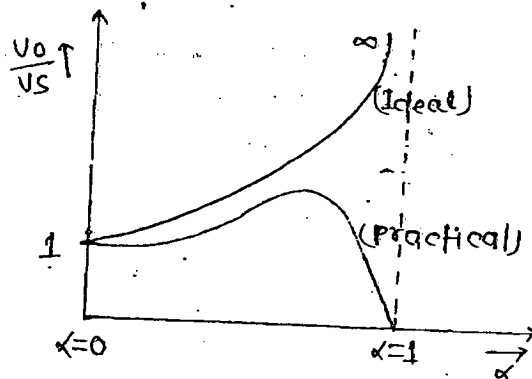If question is ask in the form of internal ^{resistor} inductance of inductance



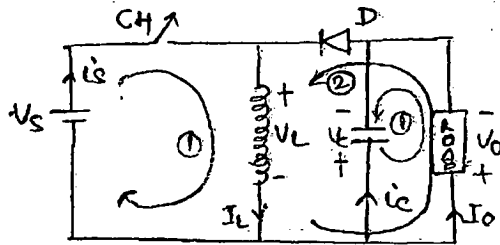Step down/up chopper (Buck-Boost Converter) →



* Let us assume constant o/p vol. & current & it is a lossless ckt.

(I) $0 \leq t \leq T_{ON} \rightarrow CH \rightarrow ON, D \rightarrow OFF$

$$i_c = -I_o$$

$$V_L = V_s$$

$$L \frac{di_L}{dt} = V_s$$

$$\int_{I_{mn}}^{I_{mp}} di_L = \frac{V_s}{L} \int_0^{T_{ON}} dt$$

$$\Delta I_L = \frac{\alpha V_s}{fL} \quad \text{--- (i)}$$

(II) $T_{ON} \leq t \leq T \rightarrow$

$CH \rightarrow OFF, D \rightarrow ON$

$$i_L = i_c + I_o$$

$$+V_L + V_o = 0$$

$$V_L = -V_o$$

$$(V_o)_{avg} = 0$$

$$V_s T_{ON} - V_o T_{OFF} = 0$$

$$V_s T_{ON} = V_o T_{OFF}$$

$$V_s (\alpha T) = V_o (1 - \alpha) T$$

$$V_o = \frac{\alpha V_s}{(1 - \alpha)}$$

$$V_o I_o = V_s I_s$$

$$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{\alpha}{(1 - \alpha)}$$

$$I_s = \frac{\alpha I_o}{(1 - \alpha)}$$

$$\Delta Q = C \cdot \Delta V_c$$

$$\Delta V_c = \frac{\Delta Q}{C} = \frac{I_o T_{ON}}{C}$$

$$\Delta V_c = \frac{\alpha I_o}{fC} \quad \text{--- (ii)}$$

Inductance (L_c) $\rightarrow$

$$I_0 = \frac{\Delta I_L}{2} \text{ (at } L_c)$$

$$\frac{\alpha V_S}{(1-\alpha)R} = \frac{\alpha V_S}{2fL_c}$$

$$L_c = \frac{(1-\alpha)R}{2f} \text{ ---- (3)}$$

Critical Capacitance (C_c) $\rightarrow$


$$V_0 = \frac{\Delta V_C}{2}$$

$$I_0 R = \frac{\alpha I_0}{2fC_c}$$

$$C_c = \frac{\alpha}{2fR} \text{ ---- (4)}$$

Non-ideal case $\rightarrow$
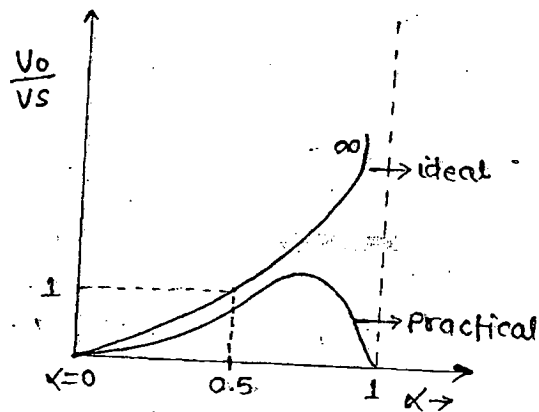
$$V_0 = \frac{V_S \alpha (1-\alpha)}{\frac{f}{R} + (1-\alpha)^2}$$





$$\begin{aligned} \alpha < 0.5, V_0 < V_S \\ \alpha > 0.5, V_0 > V_S \end{aligned}$$


Parameters	Step down (Buck Con ^r)	Step up chopper (Boost Con ^r)	Step up/down chopper (Buck-Boost con ^r)
* ΔI_L	$\frac{\alpha(1-\alpha)V_s}{fL}$	$\frac{\alpha V_s}{fL}$	$\frac{\alpha V_s}{fL}$
* $(\Delta I_L)_{\max}$ ($\alpha=0.5$)	$\frac{V_s}{4fL}$	$\frac{V_s}{2fL}$	$\frac{V_s}{2fL}$
* V_o	αV_s	$\frac{V_s}{(1-\alpha)}$	$\frac{\alpha V_s}{(1-\alpha)}$
* ΔQ_c	$\frac{\Delta I_L}{8f}$	—	—
* ΔV_c	$\frac{\alpha(1-\alpha)V_s}{8f^2LC}$	$\frac{\alpha I_o}{fC}$	$\frac{\alpha I_o}{fC}$
* L_c	$\frac{(1-\alpha)R}{2f}$	$\frac{\alpha(1-\alpha)R}{2f}$	$\frac{(1-\alpha)R}{2f}$
* C_c	$\frac{(1-\alpha)}{16f^2LC}$	$\frac{\alpha}{2fR}$	$\frac{\alpha}{2fR}$
* Ratio	$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \alpha$	$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{1}{(1-\alpha)}$	$\frac{V_o}{V_s} = \frac{I_s}{I_o} = \frac{\alpha}{1-\alpha}$
* I_s	αI_o	$I_o \left(\frac{1}{1-\alpha} \right)$	$\frac{\alpha I_o}{(1-\alpha)}$
* V_o (practical)	$V_{B/K} =$	$\frac{V_s(1-\alpha)}{\frac{r}{R} + (1-\alpha)^2}$	$\frac{V_s \alpha(1-\alpha)}{\frac{r}{R} + (1-\alpha)^2}$

Classification of chopper based on quadrant operation →

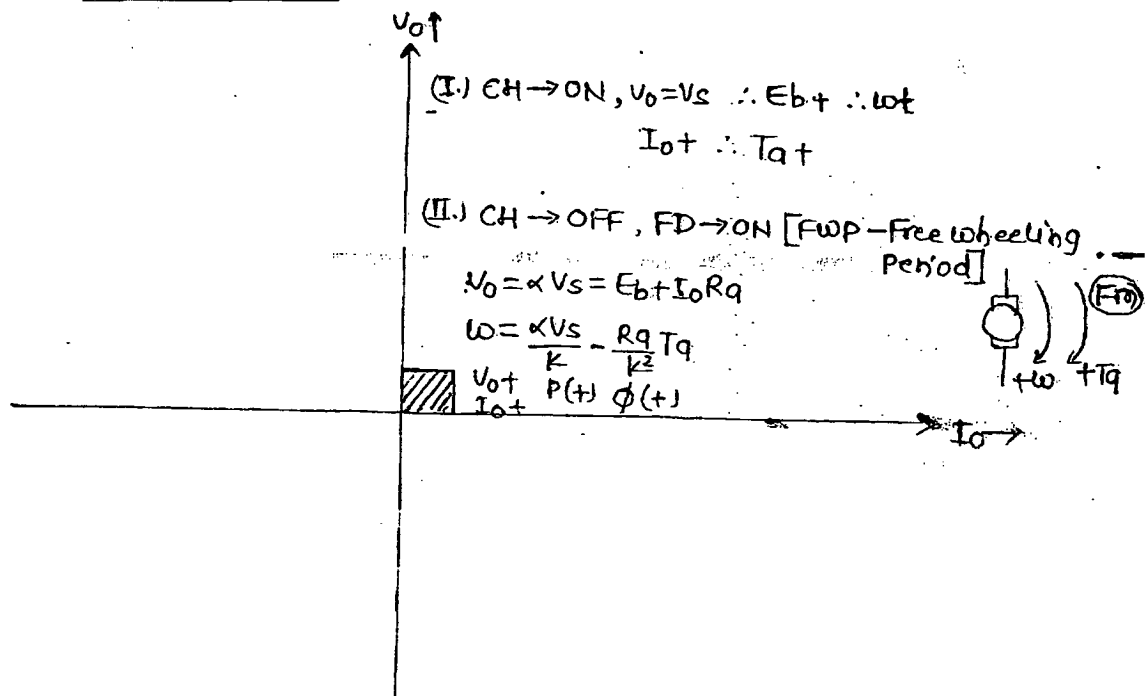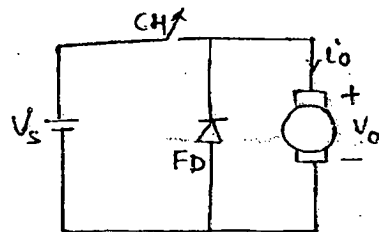1st quadrant chopper: (Type A) → (step down chopper)



(2) 2nd quadrant Chopper (Type B) →

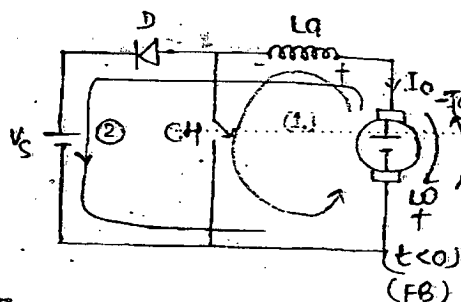

Let us assume that the m/c is running at rated speed in the forward direction before $t=0$.

Brake energy at $t=0 = \frac{1}{2} J \omega^2$

(I) $0 \leq t \leq T_{on} \rightarrow$

$CH \rightarrow ON, D \rightarrow OFF$

$(V_o = 0) \therefore (I_o^-), (T_a^-)$

$\frac{1}{2} J \omega^2 \rightarrow \frac{1}{2} L i^2$


(II) $T_{on} \leq t \leq T \rightarrow$

$CH \rightarrow OFF, D \rightarrow ON$

$\frac{1}{2} L i^2 \rightarrow$ source

$L \rightarrow$ releasing energy



$V_o = V_s$

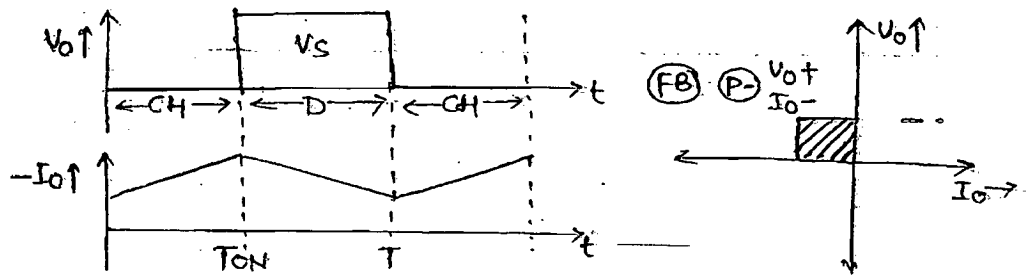




Source $\xleftarrow{(P)}$ Brake energy
 $\therefore$ Regenerative Braking
 $HV \xleftarrow{\quad} LV$

Regenerative Power = $V_o I_o$ ($V_o < V_s$)
 $= (1 - \alpha) V_s I_o$

3.) Two quadrant Chopper $\rightarrow$

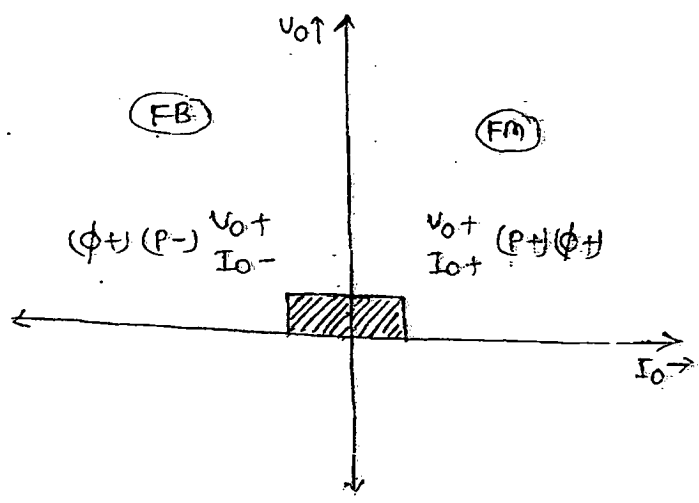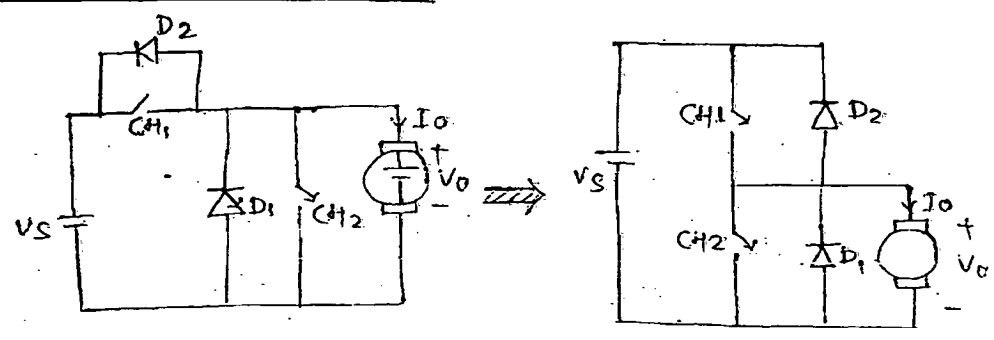

Four Quadrant Chopper →

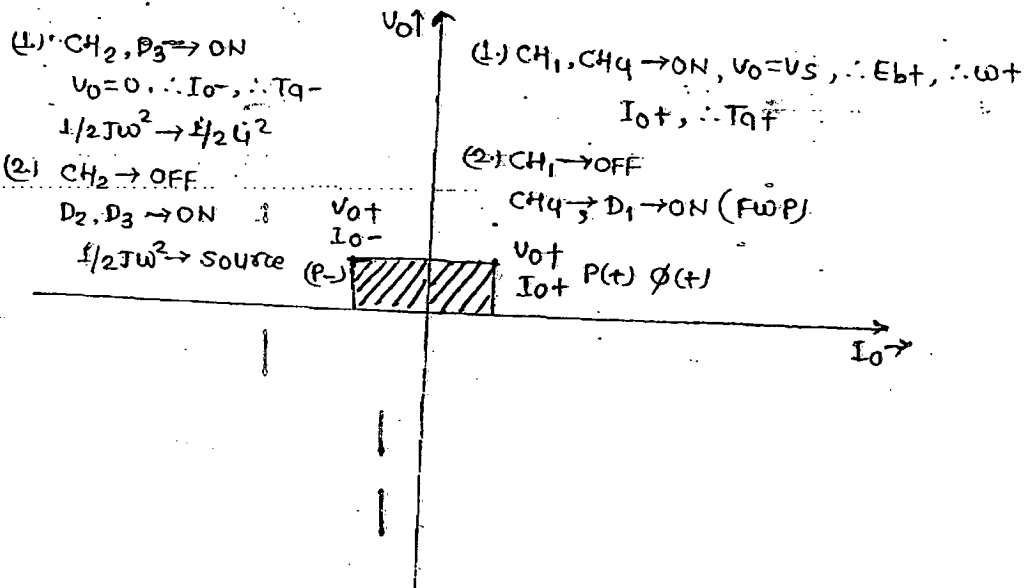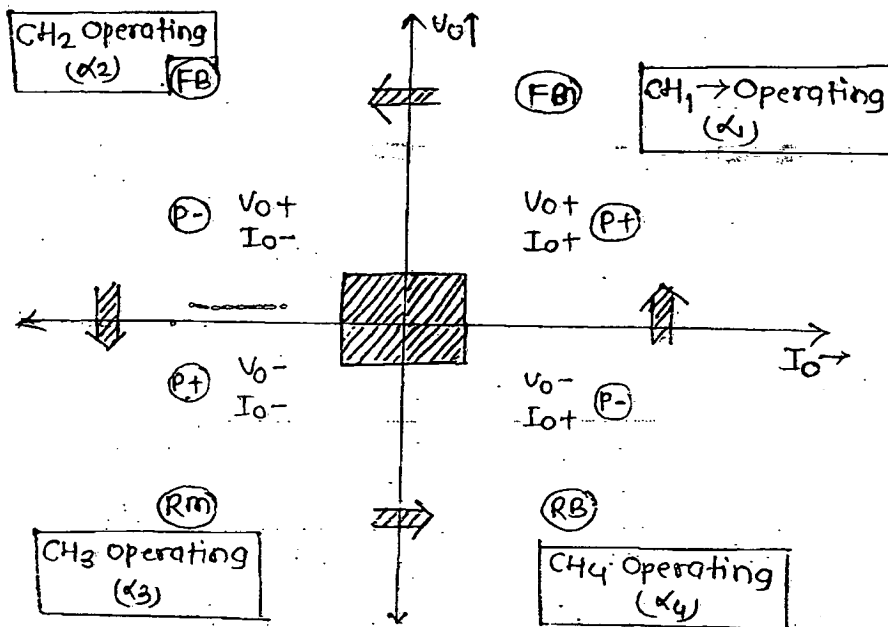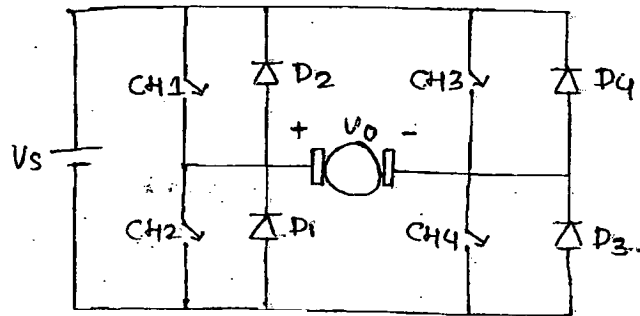

AC Voltage Controller

Fixed AC $\longrightarrow$ Variable AC


$f(\text{const})$

(1) Phase Control tech.

(2) Integral cycle control (ON/OFF)

(1) Phase Control tech $\rightarrow$

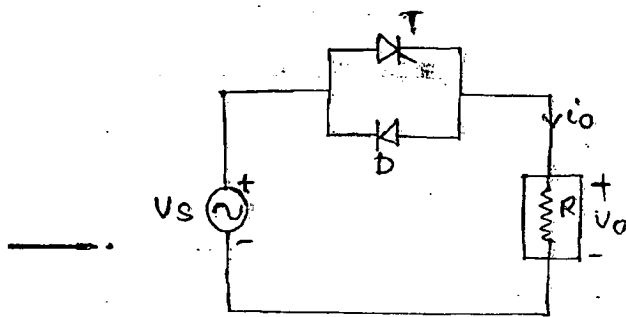(i) Single phase half controlled AC vol. Controller $\rightarrow$




$$V_o = \frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m \sin \omega t \cdot d(\omega t)$$

$$V_o = \frac{V_m}{2\pi} [\cos \alpha - 1]$$

$$(I_s)_{avg} = I_o = \frac{V_m}{2\pi R} [\cos \alpha - 1]$$

↓
DC comp.

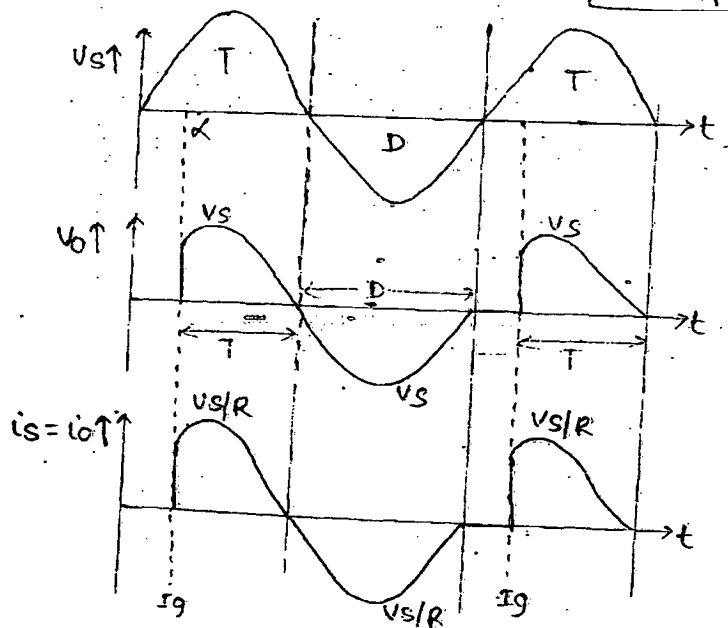

Drawback $\rightarrow$

* The source current contains dc comp. & saturates the supply Xmer core.
Therefore this type of AC vol. controllers are not preferred in applications.



$$V_{or} = \left\{ \frac{1}{2\pi} \int_{\alpha}^{2\pi} V_m^2 \sin^2 \omega t \cdot d(\omega t) \right\}^{1/2}$$


$$V_{or} = \frac{V_m}{2\sqrt{\pi}} \left\{ (2\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\}^{1/2}$$

For R Load $\rightarrow$

$$PF = \frac{V_{or}}{V_{sr}} = \frac{1}{\sqrt{2\pi}} \left\{ (2\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\}^{1/2}$$

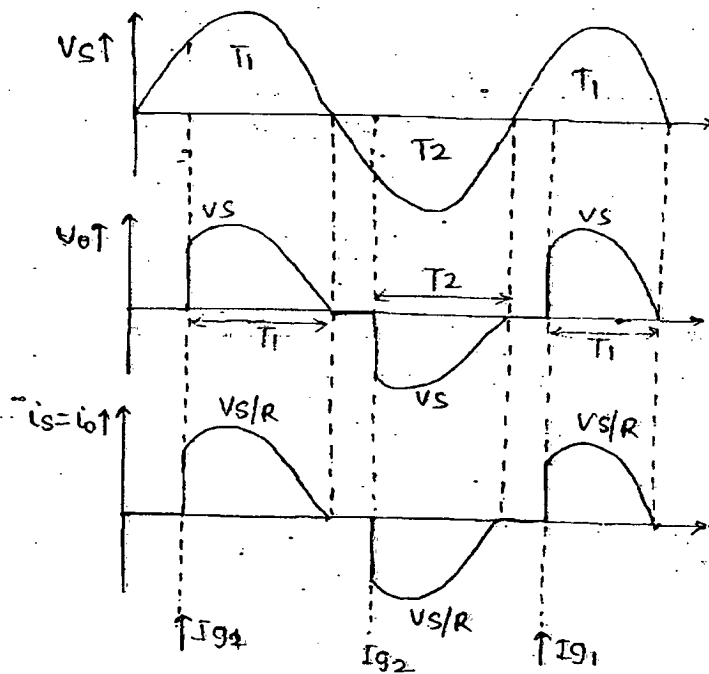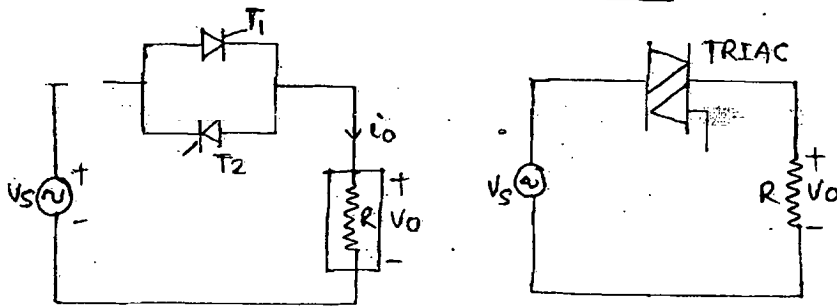(2) 1 ϕ Full Controlled AC voltage Controller $\rightarrow$



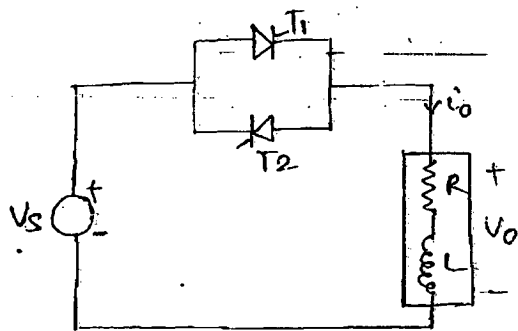


After reaching steady state,

i_o lags V_o by $\phi = \tan^{-1} \frac{\omega L}{R}$

(i) $\alpha > \phi$, V_o is controlled

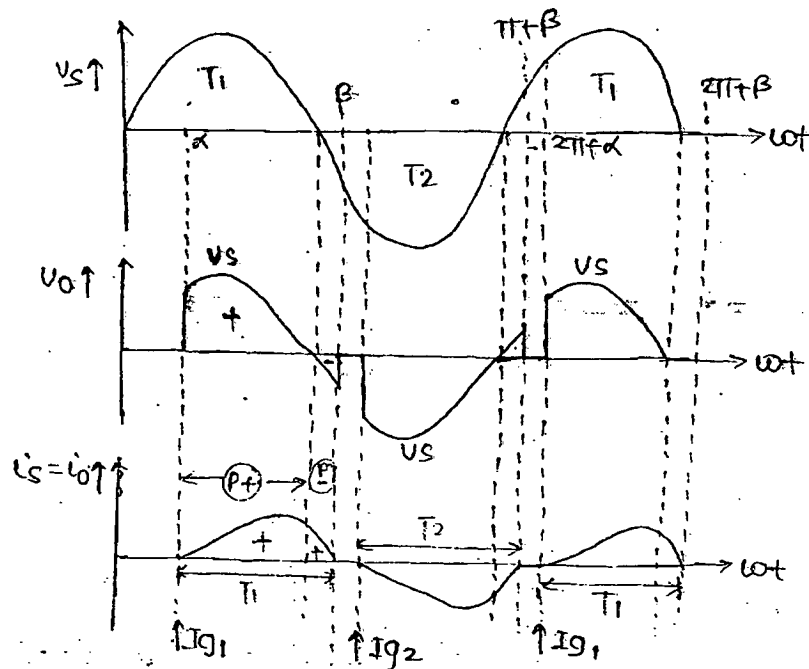(ii) $\alpha \leq \phi$, V_o is uncontrolled.



(i) $\alpha > \phi$, V_o is controlled $\rightarrow$

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left[(\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right]^{1/2}$$


$$I_{or} = \frac{V_{or}}{|Z|}$$

$$\text{where } |Z| = \sqrt{R^2 + (\omega L)^2}$$

(ii) $\alpha \leq \phi$, V_o is uncontrolled $\rightarrow$

$$(V_{or})_{max} = V_{sr} = \frac{V_m}{\sqrt{2}}$$

$$(I_{or})_{max} = \frac{(V_{or})_{max}}{|Z|}$$

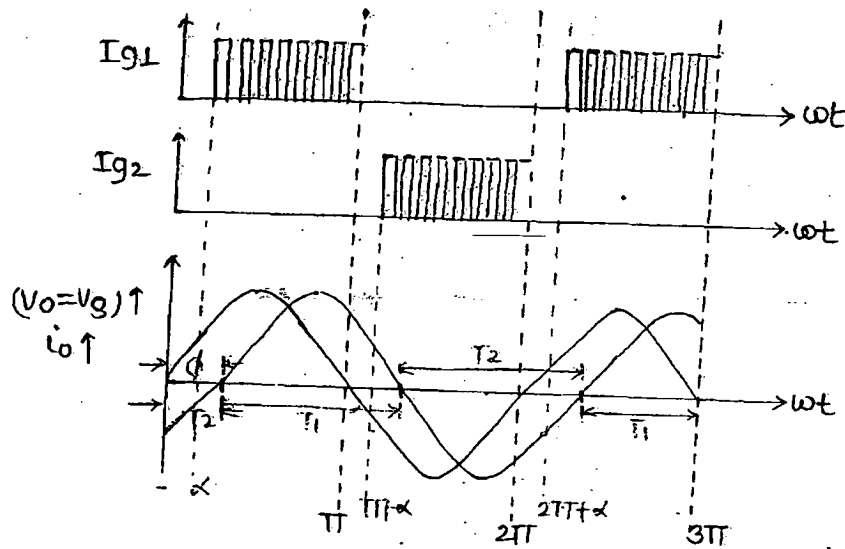


* If pulse gate signal is given tho thy. in AC vol. controller with inductive load then it may behave like half wave rectifier.

To rectify this prob. we must provide continuous gate pulse (or) high freq. gate pulse as shown in fig.


Drawback → In phase control tech. at high values of α harmonics distortion is higher & it operates at high low PF.

Two-stage AC Vol. Controller →

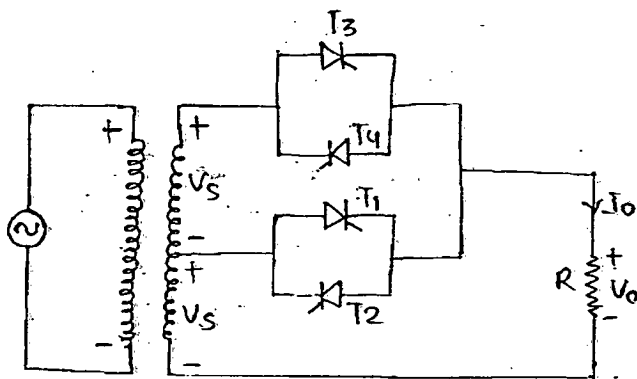

+ve $T_1 T_3 (F)$



-ve $T_2 T_4 (F)$

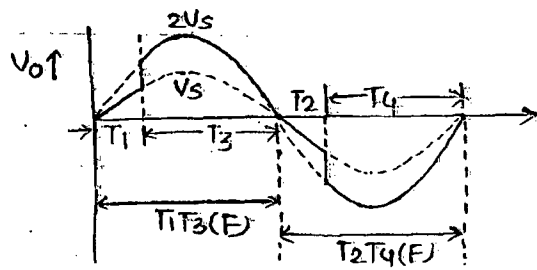


$$V_{or} = \left[\frac{1}{\pi} \left[\int_0^{\alpha} V_m^2 \sin^2 \omega t \cdot d(\omega t) + \int_{\alpha}^{\pi} 4V_m^2 \sin^2 \omega t \cdot d(\omega t) \right] \right]^{1/2}$$

$$V_{or} = \frac{V_m}{\sqrt{2\pi}} \left\{ \left[\alpha - \frac{1}{2} \sin 2\alpha \right] + 4 \left[(\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right] \right\}^{1/2}$$


Multi-stage AC Voltage Controller →

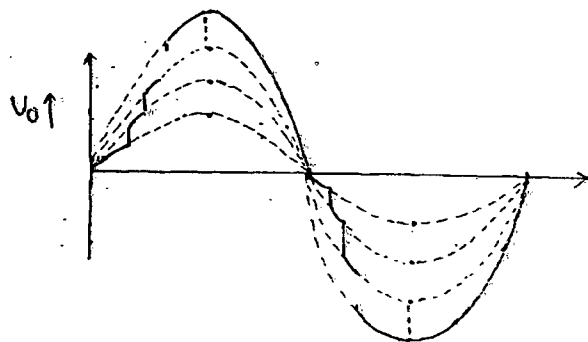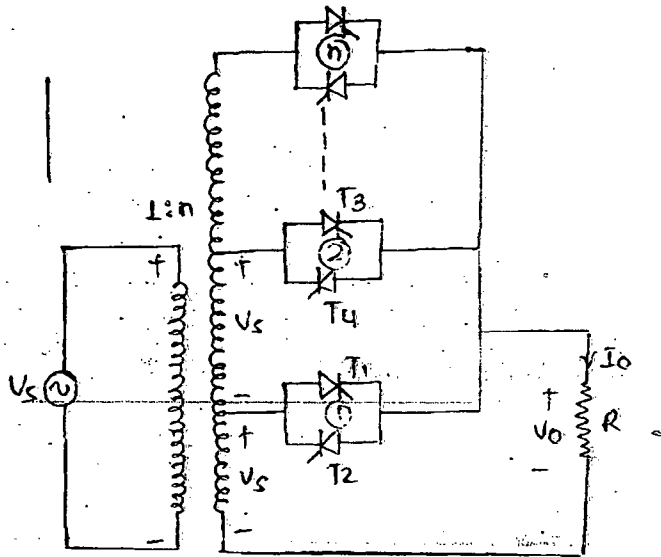

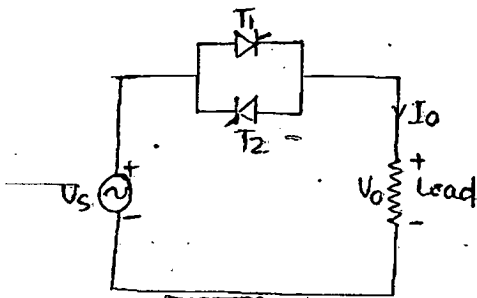2.1.1 Integral Cycle Control $\rightarrow$ (ON/OFF)



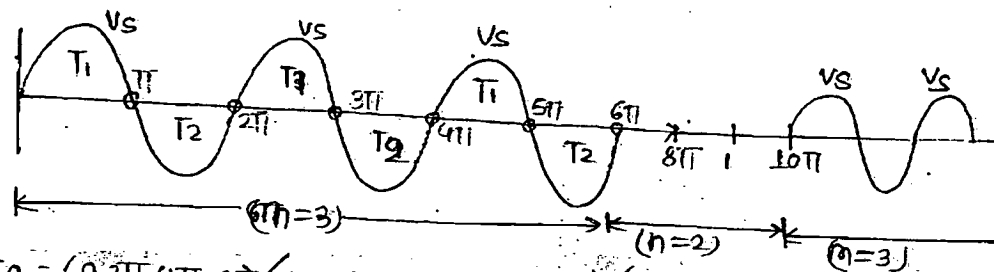m cycles $\rightarrow$ ON ($V_o = V_s$) let $m=3$
 n cycles $\rightarrow$ OFF ($V_o = 0$) $n=2$



$$I_{g1} = (0, 2\pi, 4\pi, 6\pi, 8\pi, 10\pi, 12\pi, 14\pi, 16\pi, 18\pi, \dots)$$

$$I_{g2} = (\pi, 3\pi, 5\pi, 7\pi, 9\pi, 11\pi, 13\pi, 15\pi, 17\pi, 19\pi, 21\pi, \dots)$$

$$V_{or} = V_{sr} \left(\frac{m}{m+n} \right)^{1/2}$$

$$V_{or} = \sqrt{k} \cdot V_{sr}$$

$$PF = \sqrt{k}$$

$$\left(k = \frac{m}{m+n} \right)$$

Application $\rightarrow$ It can be used for the AC loads with high time constant.

For eg:- It can be used for Indⁿ motor with high m & i mech. time constant.

Limitation $\rightarrow$ We can't get wide range of voltage control with this method.

* Cycloconverter $\rightarrow$