
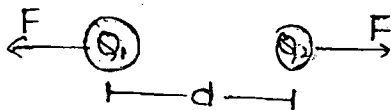


Capacitance of transmission line:

Coulombs law

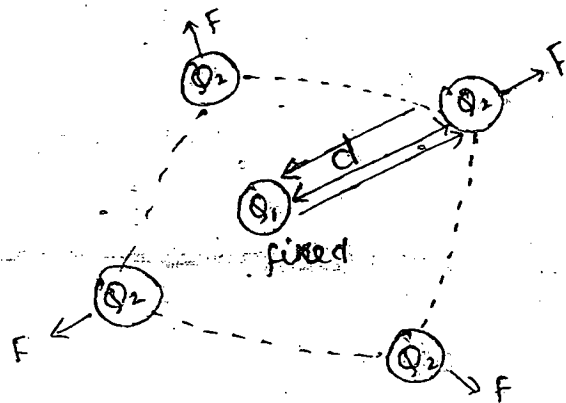

$$F = \frac{Q_1 Q_2}{4\pi\epsilon_0\epsilon_r d^2}$$




$$E = \frac{F}{Q_2} = \frac{Q_1}{4\pi\epsilon_0\epsilon_r d^2}$$

$$\text{Voltage } dv = \frac{\text{Work done}}{\text{charge}} = \frac{E dx}{Q_2} = \frac{F dx}{Q_2}$$

$$V = - \int_d^{\infty} E \cdot dx$$

$$C = Q/V$$

Single tr. lines

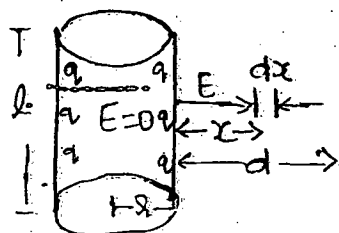

ASCR

$\sigma = \text{high}$

$$J = \sigma \cdot E$$

$$E \propto \frac{J}{\sigma}$$

$$E \propto 0$$

$Q =$ line charge C/m

$$E = \frac{Q}{2\pi\epsilon_0\epsilon_r x}$$


$$V = - \int_r^d E dx$$

$$V = - \int_r^d \frac{Q}{2\pi\epsilon_0\epsilon_r x} dx$$

$$V = \frac{Q}{2\pi\epsilon_0\epsilon_r} \ln \frac{d}{r}$$

$$C = \frac{Q}{V} = \frac{2\pi\epsilon_0\epsilon_r}{\ln(d/r)}$$

Capacitance of 1- Φ 2-wire line:

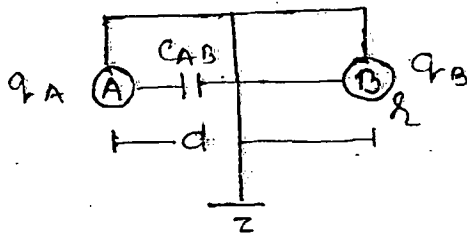

At balance $q_A + q_B = 0$

$$C_{AB} = \left| \frac{q_A}{V_{AB}} \right| = \left| \frac{q_B}{V_{AB}} \right|$$

$$V_{AB} = V_A - V_B$$

$$= \frac{q_A}{2\pi\epsilon_0\epsilon_r} \ln \frac{d}{r} - \frac{q_B}{2\pi\epsilon_0\epsilon_r} \ln \frac{d}{r}$$


$$q_B = -q_A$$

$$V_{AB} = \frac{q_A}{2\pi\epsilon_0\epsilon_r} \ln \left(\frac{d}{r} \right)^2$$

$$51. V_{AB} = \frac{q_A}{\pi \epsilon_0 \epsilon_r} \ln(d/r)$$

$$C_{AB} = \frac{q_A}{V_{AB}} = \frac{\pi \epsilon_0 \epsilon_r}{\ln(d/r)}$$

capacitance to neutral:

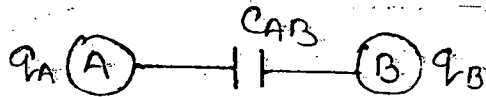

$$C_{AB} = \frac{C_n \cdot C_n}{C_n + C_n} = \frac{C_n}{2}$$

$$C_n = 2C_{AB}$$

$$C_n = \frac{2\pi \epsilon_0 \epsilon_r}{\ln(d/r)}$$


⊕ 3φ transposed line:

C_n = capacitance per phase $\Rightarrow$ F/m/ph

$$C_n = \frac{2\pi \epsilon_0 \epsilon_r}{\ln[(D_1 D_2 D_3)^{1/3} / r]}$$

if $D_1 = D_2 = D_3 = D$
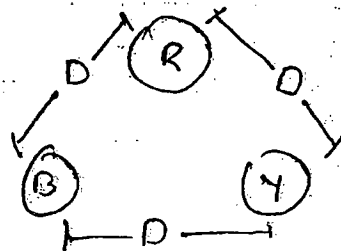
$$C_n = \frac{2\pi \epsilon_0 \epsilon_r}{\ln(D/r)}$$



② Bundle conductor

$$C_n = \frac{2\pi\epsilon_0\epsilon_r}{\ln\left(\frac{D_m}{D_s}\right)}$$

③ Double ckt line:

$$C_n = \frac{2\pi\epsilon_0\epsilon_r}{\ln\left(\frac{D_{m1} D_{m2} D_{m3}}{D_{s1} D_{s2} D_{s3}}\right)^{1/3}}$$


④ $X_c = \frac{1}{2\pi f C_n} \quad \Omega/\text{m/Ph}$

⑤ $B = \frac{1}{X_c} = 2\pi f C_n \quad \text{V/m/Ph}$


⑥ $I_c = \text{charging current}$
 $= 2\pi f C_n V_{ph} \quad \text{A/m/Ph};$

⑦ Reactive power Q_{ph}
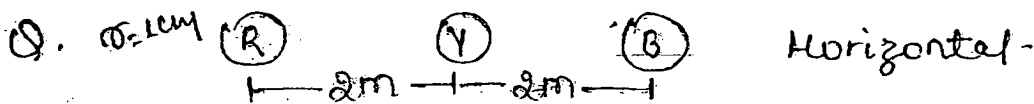
$$Q_{ph} = 2\pi f C_n V_{ph}^2 \quad \text{Vars/Am/Ph}$$


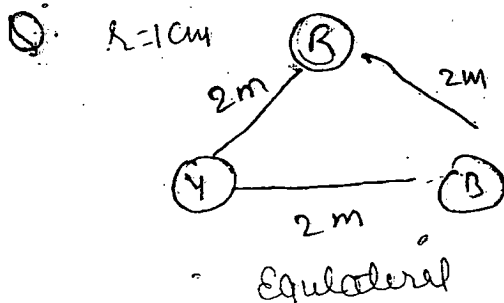
$$C_n = \frac{2\pi}{\ln\left(\frac{D_m}{D_s}\right)}$$



$$C_n = \frac{2\pi}{\ln\left(\frac{D_m}{D_s}\right)}$$

→ Effect of Earth on the capacitance b/w earth cond^r:


Earth consist of infinite no. of charge carriers both +ve & -ve. This charge carriers produces additional electrical field. So that 'C' b/w conductor & es. This increment causes increase in transmission line voltage which causes insulation failure.

If this increment in voltage more than critical disruptive voltage [a min^m voltage required to initiate 'corona'] so that corona occurs in the system for eliminating or reducing earth effect, The height of the tower is fixed as the operating voltage is rising.

Method of images:

It is the mathematical techniques adopted from electromagnetic fields used as calculation of effect of earth on the capacitance b/w cond^r. In this method image charges are assumed below their line which have the same mag. of charges but opp.

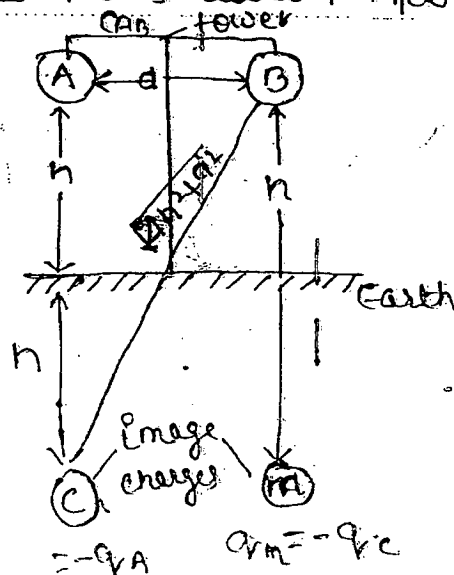Sign. the no. of image charges equal to no. of cond^r existing in the transmission N/w above ground.



Voltage⁵⁴ b/w A/B

$$V_{AB} = \frac{1}{2\pi\epsilon_0\epsilon_r} \left[q_A \ln \frac{D_{AB}}{r} + q_B \ln \frac{r}{D_{BA}} + q_C \ln \frac{D_{CB}}{D_{CA}} + q_m \ln \frac{D_{mA}}{D_{mB}} \right]$$

At balanced

$$q_A + q_B = 0$$

$$q_A = -q_B, \quad q_C = -q_A, \quad q_m = -q_B = q_A$$

$$D_{AB} = D_{BA} = d, \quad D_{CA} = D_{mB} = 2h, \quad D_{CB} = D_{mB} = \sqrt{4h^2 + d^2}$$

$$V_{AB} = \frac{q_A}{\pi\epsilon_0\epsilon_r} \ln \left(\frac{d}{r \sqrt{1 + \frac{r^2}{4h^2}}} \right)$$

$$C_{AB} = \frac{q_A}{V_{AB}} = \frac{\pi\epsilon_0\epsilon_r}{\ln \left(\frac{d}{r \sqrt{1 + \frac{d^2}{4h^2}}} \right)} \quad \text{With Earth effect}$$


Note: By increasing high of tower

$$\frac{d^2}{4h^2} \approx 0$$

$$C_{AB} = \frac{\pi\epsilon_0\epsilon_r}{\ln(d/r)} \quad \text{NO Earth effect}$$

V_L (KV)	11	33	132	220	440	765
h (m)	7	11	20	35	50	65

→ Voltage Regulation of Tr. line:

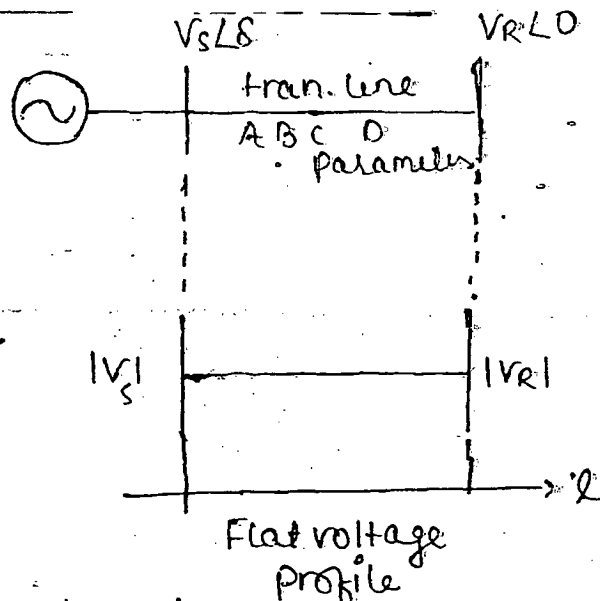

$$\% \text{Vreg} = \frac{|V_{RNL}| - |V_{RFL}|}{|V_{RFL}|} \times 100$$

V_{RNL} = NO load receiving end voltage

$$V_S = A V_R + B I_R$$

At no load $I_R = 0$

$$V_S = A V_R$$

$$\therefore A = \frac{V_S}{V_R} = \frac{V_S}{V_{RNL}}$$

$$\Rightarrow \boxed{V_{RNL} = \frac{V_S}{A}}$$

V_{RFL} = Full load receiving end voltage

$$= |V_R|$$

$$\boxed{\% \text{VREG} = \frac{\left| \frac{V_S}{A} \right| - |V_R|}{|V_R|} \times 100}$$

The above eqn applicable for All type of transmission line

Ex: Short transmission line $A=1$

$$\% V_{REG} = \frac{|V_S| - |V_R|}{|V_R|} \times 100$$


If $|V_S| = |V_R|$

$$\% V_{REG} = 0\%$$


$$\% V_{REG} = \pm 5\%$$

concept


HAVE

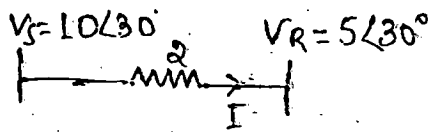

$$I \neq 0$$

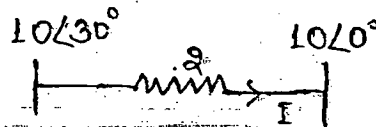


$$I \neq 0$$

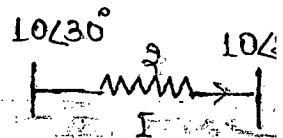


$$I = 0$$

* In case of HAVE, voltage b/w sending and receiving end must have different magnitude of voltage or phase difference. then power will flow.

HVDC

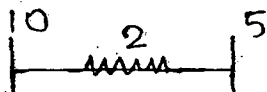

$$I \neq 0$$

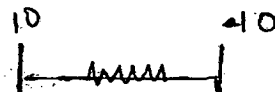


$$I = 0$$

* For max^m power transfer due to unequal magnitude of the voltage

57
 → Effects of load on the voltage Regulation of the tr. line:-

(A) Short trans. line:


(a) lag load.

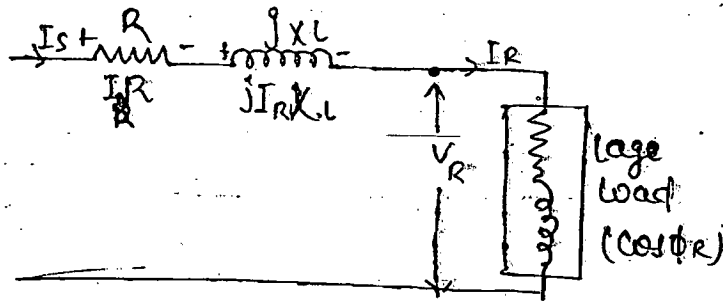

$$Z = R + jX_L$$

$$V_S = V_R + IRZ$$

$$V_S = V_R + IR R + jIX_L$$

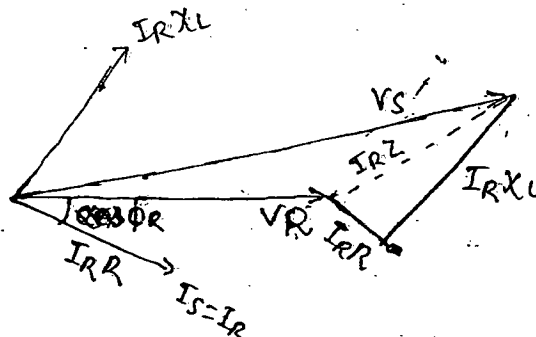

From phasor diagram


$$|V_S| > |V_R| \quad |V_S| = +V_e$$

$$\% V_{REG} = \frac{|V_S| - |V_R|}{|V_R|} \times 100$$

$$\% V_{REG} = +V_e$$

Peak load time




For unity power load

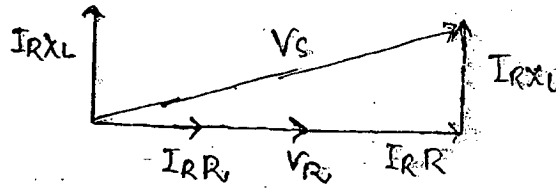


$$|V_s| > |V_R|$$

$$\%V_{REG} = +ve$$

For leading load:

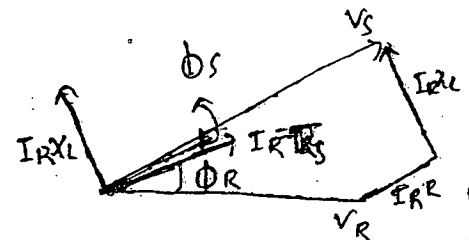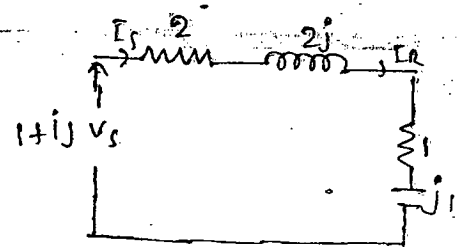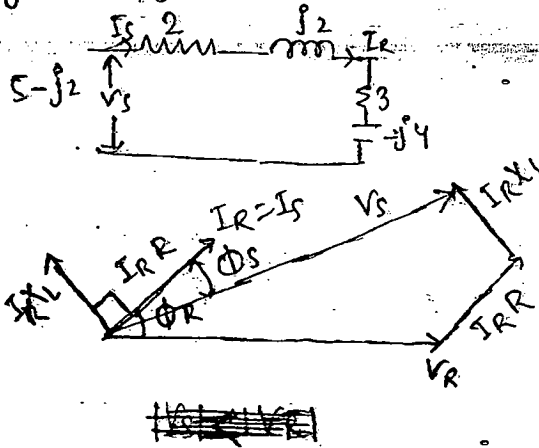


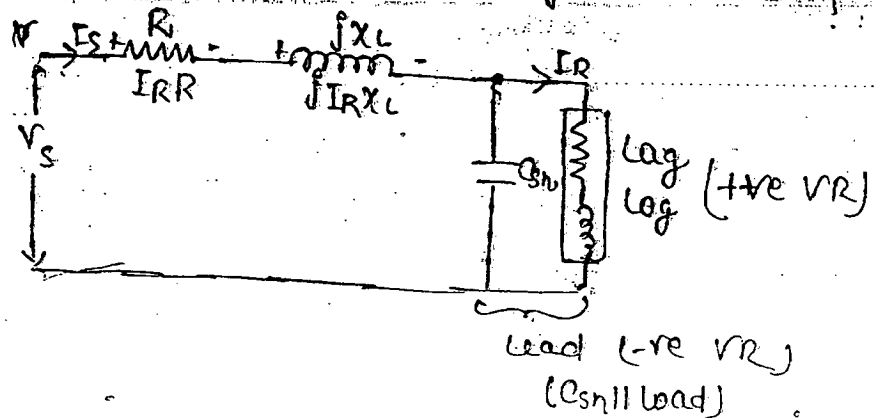Q. Why Designer using Shunt capacitor during load cond?



Conclusion about above CKT:-

1) Lag load

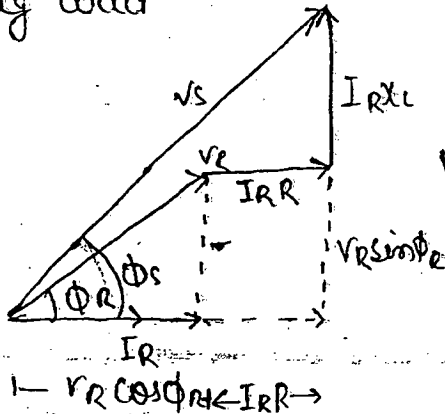

$$V_S^2 = (V_R \cos \phi_R + I_R R)^2 + (V_R \sin \phi_R + I_R X_L)^2$$

$$= \cancel{V_R^2 + I^2(R^2 + X_L^2) + 2I_R V_R (\cos \phi_R + X_L \sin \phi_R)}$$

$$V_S^2 = V_R^2 + I^2(R^2 + X_L^2) + 2I_R V_R (R \cos \phi_R + X_L \sin \phi_R)$$

$$I^2(R^2 + X_L^2) \ll V_R^2$$

$$V_S^2 = V_R^2 + 2I_R V_R (R \cos \phi_R + X_L \sin \phi_R)$$

$$V_S^2 = V_R^2 \left[1 + \frac{2I_R}{V_R} (R \cos \phi_R + X_L \sin \phi_R) \right]$$

$$\therefore V_S = \left[V_R^2 \left(1 + \frac{2I_R}{V_R} (R \cos \phi_R + X_L \sin \phi_R) \right) \right]^{1/2}$$

$$V_S = V_R \left[1 + \frac{2I_R}{V_R} (R \cos \phi_R + X_L \sin \phi_R) \right]^{1/2}$$

60 A/c

$$(1+x)^{1/2} = 1+x/2$$

$$V_S = V_R \left[1 + \frac{I_R}{V_R} (R \cos \phi_R + X_L \sin \phi_R) \right]$$

$$V_S - V_R = I_R (R \cos \phi_R + X_L \sin \phi_R)$$

$$\% V_{REG} = \frac{|V_S| - |V_R|}{|V_R|} \times 100$$

$$\% V_{REG} = \frac{I_R (R \cos \phi_R + X_L \sin \phi_R)}{|V_R|} \times 100$$

For max^m Regulation

$$\frac{d}{d\phi_R} [I_R (R \cos \phi_R + X_L \sin \phi_R)] = 0$$

$$-I_R [R \sin \phi_R - X_L \cos \phi_R] = 0$$

$$R \sin \phi_R = X_L \cos \phi_R$$

$$\tan \phi_R = \frac{X_L}{R}$$

$$\phi_R = \tan^{-1} \left(\frac{X_L}{R} \right)$$

↑
condn for max^m Regulation

If $Z = R + jX_L = |Z| \angle \theta$ = trans. line parameter

$$\theta = \tan^{-1} \left| \frac{X_L}{R} \right| = \phi_R$$

∴ P.F factor of lag^y load for max^m V_{REG}

$$\cos \phi_R = \cos \theta = R/Z$$

condition for $V_{REG} = 0$

$$\Phi_R = -ve$$

$$R \cos \Phi_R - X_L \sin \Phi_R = 0$$

$$\Phi_R = \tan^{-1} \left(\frac{R}{X_L} \right) = \left(\frac{\pi}{2} - \theta \right)$$

P.F of leading load for $V_{REG} = 0\%$

$$\cos \Phi_R = \cos \left(\frac{\pi}{2} - \theta \right) = \sin \theta = \frac{X_L}{Z}$$

↑ leading

$$\frac{V_{REG}(\text{lag})}{V_{REG}(\text{lead})} = \frac{R \cos \Phi_R + X_L \sin \Phi_R}{R \cos \Phi_R - X_L \sin \Phi_R}$$

lag angle lead angle

• calculation of P_R if $|V_S| = |V_R|$ (or) $V_{REG} = 0\%$

$$V_S^2 = V_R^2 + I_R^2 (R^2 + X_L^2) + 2 V_R I_R (R \cos \Phi_R + X_L \sin \Phi_R)$$

Substitute $V_S = V_R$ calculate I_R

$$|I_R| = \frac{2 V_R (R \cos \Phi_R + X_L \sin \Phi_R)}{(R^2 + X_L^2)}$$

where $V_R = V_{ph} = \frac{V_L}{\sqrt{3}}$

∴ X_L, R per phase value

$$P_R = \sqrt{3} V_R I_R \cos \Phi_R$$

5. Procedure for cal of C_{sh} required at desired V_{REG} (Improve voltage Regulation)

(i) Calculate $|V_S|$ corresponding to new V_{REG} using:

$$V_{REG} = \frac{|V_S| - |V_R|}{|V_R|} \times 100$$

(ii) calculate ϕ_2


$$V_S - V_R = I_S (R \cos \phi_2 + X_L \sin \phi_2)$$

$$= \frac{P_R}{V_R \cos \phi_2} (R \cos \phi_2 + X_L \sin \phi_2)$$

$$V_S V_R - V_R^2 = P_R R + P_R X_L \tan \phi_2$$

$$\phi_2 = \tan^{-1} \left[\frac{V_S V_R - P_R R - V_R^2}{P_R X_L} \right]$$


Concept:

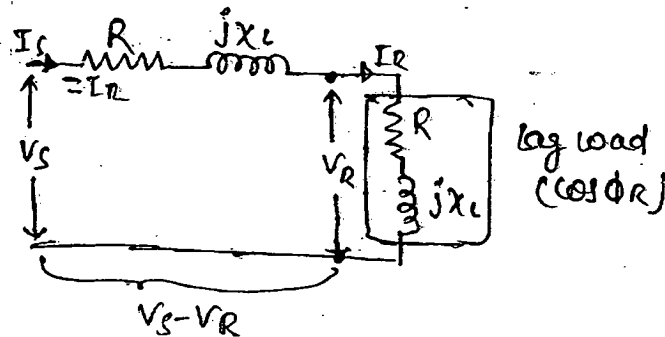

$$V_S - V_R = I_S (R \cos \phi_R + X_L \sin \phi_R)$$

$$|V_R| < |V_S| \quad V_{REG} \Rightarrow +ve \pm 10\%$$

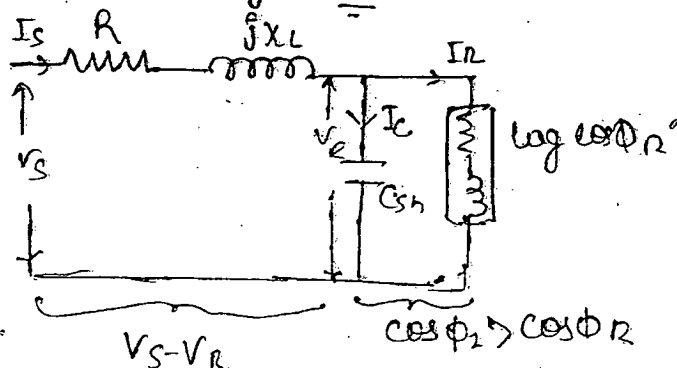to reduce the V_{REG} upto 3 to 5% C_{sh} is used parallel to lag load



$$V_S - V_R = \dot{I}_S [R \cos \phi_2 + jX_L \sin \phi_2]$$

$$P_R = V_R I_S \cos \phi_2$$

$$I_S = \frac{P_R}{V_R \cos \phi_2}$$

$$V_S - V_R = \frac{P_R}{V_R \cos \phi_2} [R \cos \phi_2 + jX_L \sin \phi_2]$$

$$V_R(V_S - V_R) = P_R R + P_R jX_L \tan \phi_2$$

$$\phi_2 = \tan^{-1} \left(\frac{V_S V_R - V_R^2 - P_R R}{P_R X_L} \right)$$

③ $|I_S| = \frac{P_R}{V_R \cos \phi_2}$
per phase value

④ $\vec{I}_S = \vec{I}_R + \vec{I}_C$

$$I_C = |I_S| \angle -\phi_2 - I_R \angle -\phi_R = |I_C| \angle 90^\circ$$

⑤ $I_C = 2\pi f C_{sh} \cdot V_R$

$$C_{sh} = \frac{I_C}{2\pi f V_R}$$

Workbook

Q.30 ~~soln~~ given data

$$V_R = 220 \text{ kV} \quad R = 0.15 \Omega / \text{km} / \text{ph} \quad L = 1.5923 \text{ mH} / \text{km} / \text{ph}$$

$$S_R = 381 \text{ mVA} \quad \cos \phi_R = 0.8 \text{ lag} \quad l = 40 \text{ km} \quad f = 50 \text{ Hz}$$

Find ① $V_S = ?$ $P_S = ?$

② $V_{REG} = ?$ $\eta\%$

Soln:

$$R = 0.15 \times 40 = 6 \Omega / \text{phase}$$

$$X_L = 2\pi f L \cdot l$$

$$= 2\pi \times 50 \times 1.592 \times 10^{-3} \times 40 = 20 \Omega$$

$$Z = R + jX_L = 6 + j20$$

$$= 20.8 \angle 73.3^\circ \Omega$$

For short tr. line

$$A = D = 1 \quad B = Z, \quad C = 0$$

$$I_R = \frac{P_R}{\sqrt{3} V_{RL} \cos \phi_R}$$

$$P_R = \sqrt{3} S_{ph} \cos \phi_R$$

$$\therefore I_R = \frac{S_{ph} \cdot \cos \phi_R}{\sqrt{3} V_{RL} \cdot \cos \phi_R}$$

$$= \frac{381 \times 10^3}{\sqrt{3} \times 220 \times 10^3}$$

$$I_R = 1000 \text{ A} = I_S$$

$$\cos \phi_R = 0.8 \text{ lag}$$

$$\therefore \phi_R = 36.86^\circ$$

$$I_R = I_S = 1000 \angle -36.86^\circ \text{ A lag}$$

$$\textcircled{1} \textcircled{2} V_S$$

$$V_S = A V_R + B I_R$$

$$V_{Sph} = A V_{Rph} + B I_R$$

$$= 1 \cdot \frac{220 \times 10^3}{\sqrt{3}} + 20.8 \angle 73.3^\circ \times 1000 \angle -36.86^\circ$$

$$= 145.3 \angle 4.8^\circ \text{ kV/ph}$$

$$V_{SL} = \sqrt{3} V_{Sph}$$

$$= \sqrt{3} \times 145.3 \angle 4.8^\circ = 250 \angle 4.8^\circ \text{ kV}$$

$$(b) P_s = \sqrt{3} V_{SL} I_L \cos \phi_s$$

$$= \sqrt{3} \times 250 \times 10^3 \times 1000 \cos(48+36.86^\circ)$$

$$P_s = 323 \text{ MW}$$

Alternatives:

For $\Delta\phi$ short T.L

$$P_L = 3 I_R^2 R$$

$$= 3 \times 6 \times 1000^2 = 18 \text{ MW}$$

$$P_s = P_R + P_L$$

$$= 381 \times 0.8 + 18 = 323 \text{ MW}$$

$$(2) (a) V_{Reg}$$

$$= \frac{|V_s| - |V_R|}{|V_R|} \times 100$$

$$= \frac{250 - 220}{220} \times 100 = 13.674\%$$

(b) Efficiency

$$\eta\% = \frac{P_R}{P_s} \times 100$$

$$= \frac{381 \times 0.8}{323} \times 100$$

$$\eta\% = 94.45\%$$

$$\text{Or } \eta\% = \frac{P_R}{P_R + P_L} \times 100 = 94.45\%$$

66
 In the previous problem calculate the capacitance required /phase for reducing V_R .

(1) -- 50% 2) 25% $V_R = 220 \text{ kV}$

(i) $V_{REG} = 50\%$

$$V_{REG} = 13.67 \times 50/100 = 6.835$$

$$\frac{V_S - V_R}{V_R} \times 100 = 6.835\%$$

$$\frac{V_S - 220}{200} \times 100 = 6.835$$

$$V_S = 235 \text{ kV} = V_L$$

$$V_{Sph} = \frac{235}{\sqrt{3}} = 135.69 \text{ kV}$$

$$(2) \quad \phi_2 = \tan^{-1} \left(\frac{V_S V_R - V_R^2 - P_R R}{X_L P_R} \right)$$

$$P_{R3\phi} = 3 \times P_{Rph}$$

$$P_{Rph} = \frac{P_{R3\phi}}{3} = \frac{381 \times 10^3}{3} = 101.6 \text{ mW}$$

$$V_{Sph} = 135.69 \text{ kV/ph}$$

$$V_{Rph} = \frac{220}{\sqrt{3}} = 127 \text{ kV/ph}$$

$$R = 6 \Omega / \text{ph} \quad \phi_2 = 13.61^\circ$$

$$X_L = 20 \Omega / \text{ph}$$

$$(3) \quad I_S = \frac{P_{Sph}}{V_{Rph} \cos \phi_2} = \frac{101.6 \times 10^3}{127 \times 10^3 \times \cos 13.61^\circ}$$

$$|I_S| = 823.11 \angle -13.61^\circ$$


$$\begin{aligned}
 (4) \quad I_C &= I_S - I_R \\
 &= 823.11 \angle -13.61^\circ - 1000 \angle -36.86^\circ \\
 &= 405.9 \angle 90^\circ
 \end{aligned}$$

$$(5) \quad C_{sh} = \frac{I_C}{2\pi f V_{Rph}} = \frac{405.9}{2\pi \times 50 \times 127 \times 10^3}$$

$$C_{sh} = 10.1 \mu F$$


MEDIUM TRANSMISSION-LINE:

NOMINAL π -N/W:

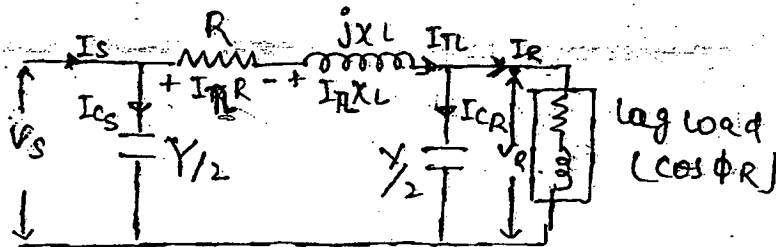


Steps:

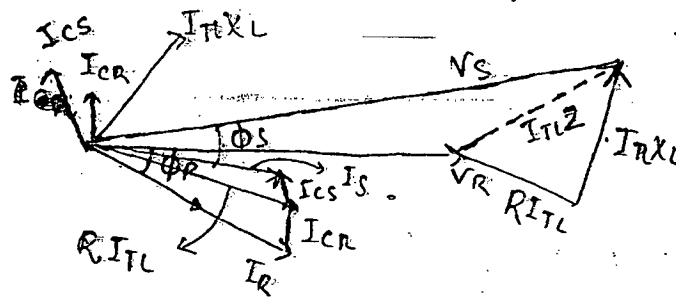- (1) V_R as Ref
- (2) I_R lags V_R by ϕ_R
- (3) $I_{CR} = V_R \cdot Y/2$
 I_{CR} leads V_R by 90°
- (4) $I_{TL} = I_R + I_{CR}$
- (5) $I_{TL}Z = I_{TL}R + j I_{TL}X_L$
- (6) $I_{CS} = V_S \cdot Y/2$ (I_{CS} leads by 90°)
- (7) $V_S = V_R + I_{TL}Z$
- (8) $I_S = I_{CS} + I_{TL}$
- (9)





Nominal T-11/0

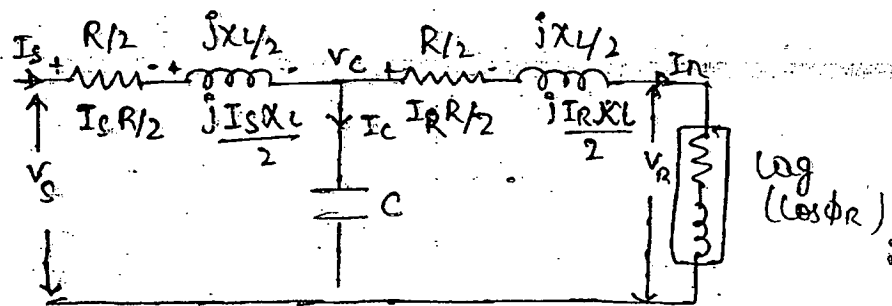

Steps

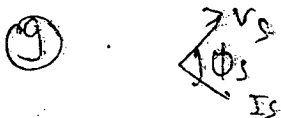- (1) V_R as Ref
- (2) I_R lags V_R by ϕ_R
- (3) $I_R Z_{/2} = I_R R_{/2} + j I_R X_{/2}$
- (4) $V_c = V_R + I_R Z_{/2}$
- (5) $I_c = V_c Y_c$ (I_c lead V_c 90°)
- (6) $I_s = I_c + I_R$
- (7) $I_s Z_{/2} = I_s R_{/2} + j I_s X_{/2}$
- (8) $V_s = V_c + I_s Z_{/2}$





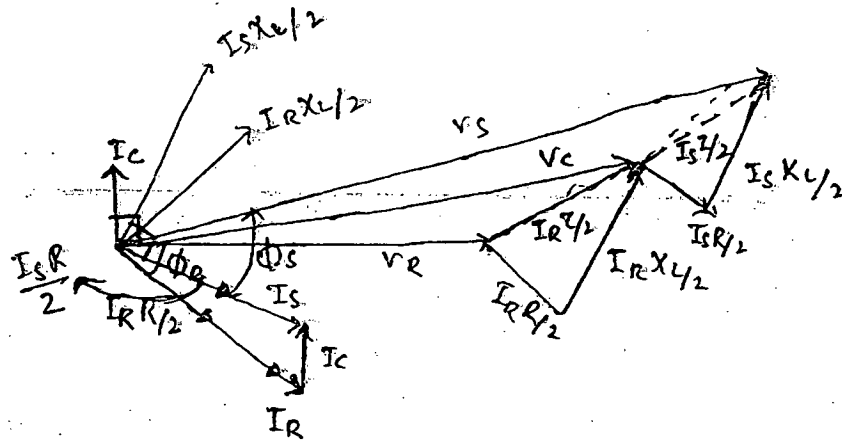

Comparison b/w Short medium line/Medium



Parameter	Short	Medium
I_s	$ I_s > I_r $	$ I_s < I_r $ due to I_c
V_{REG}	$\uparrow$	$\downarrow$
P_L	$\uparrow$	$\downarrow$
α	$\downarrow$	$\uparrow$
P_s	$\uparrow$	$\downarrow$
$\cos \phi_s$	$\downarrow$	$\uparrow$

Comparison b/w π and T-N/w

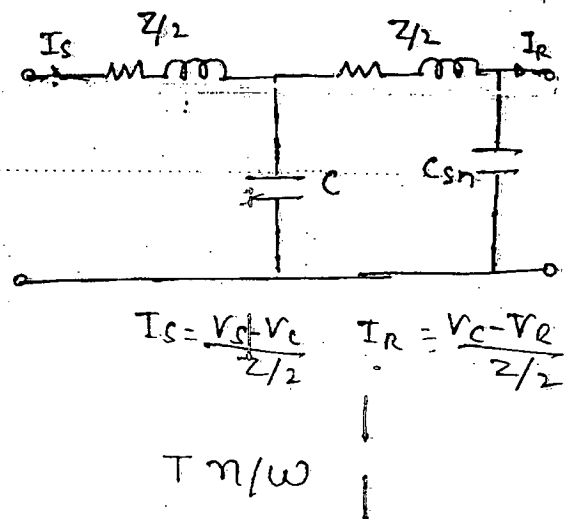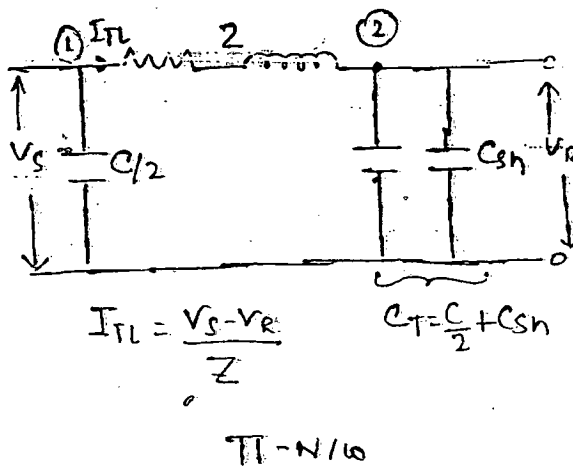

- 1) No of Nodes are two.
Sb, no of Eqⁿ less
- 2) External compensator connected can easily combine and match with line capacitance
- 3) Capacitance of line is Equally distributed both Sending & Receiving End.
- 4) Because of the advantages π η/w is practically used as one Eqⁿ ckt of the Trans line in the load flow analysis
- (i) No of Nodes = 3
No of Eqⁿ = more
- (ii) Capacitance of line is Equally distributed: it is Defult to combine and matching
- (iii) It is concentrated in the centre.
- (iv) For analysis the Effect of the line capacitance at the middle of the line it is used.

3) End Condenser η/w

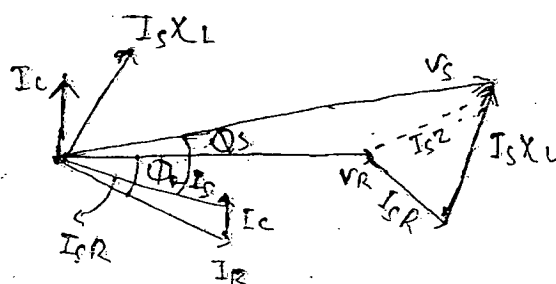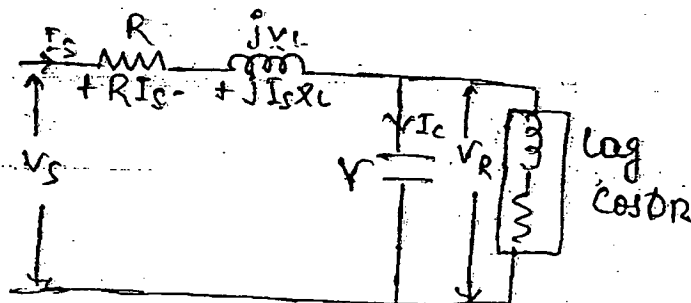

(1) Take reference


(2) IR lags V_R by ϕ_R

(3) $V_C = I_C \cdot jX_C$ (I_C leads V_C by 90°)

(4) $I_S = I_C + I_R$

(5) $I_S Z = I_S R + j I_S X_L$

(6) $V_S = V_R + I_S Z$

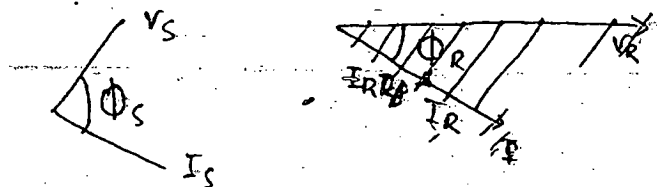


→ Power Factor:

It is degree to which a given load (R & X_L)

matches with pure resistive load

(1) R-load

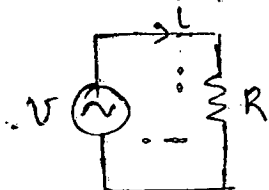

$$V = V_m \sin \omega t$$

$$i = I_m \sin \omega t$$

$$I_m = V_m / R$$

Instantaneous power


$$P = V \cdot i$$

$$= V_m \sin \omega t \cdot I_m \sin \omega t = V_m I_m \sin^2 \omega t$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} V_m I_m \sin^2 \omega t d\omega = \frac{V_m I_m}{2} = \frac{V_m}{\sqrt{2}} \cdot \frac{I_m}{\sqrt{2}}$$

$$P_{avg} = V_{RMS} \cdot I_{RMS}$$

(2) RL-load:

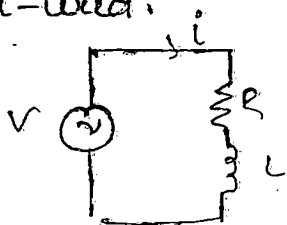

$$V = V_m \sin \omega t$$

$$i = I_m (\sin(\omega t - \phi))$$

$$I_m = \frac{V_m}{Z}$$

$$Z = R + j\omega L$$

$$\phi = \tan^{-1} \left(\frac{\omega L}{R} \right)$$

$$P = V \cdot I$$

$$= V_m I_m \sin \omega t \cdot \sin(\omega t - \phi)$$

$$p = P [1 - \cos 2\omega t] - Q \sin 2\omega t$$


$$\text{Where } P = VI \cos \phi$$

$$Q = VI \sin \phi$$

$$P_{avg} = \frac{1}{2\pi} \int_0^{2\pi} p \cdot d(\omega t)$$


$$P_{avg} = P = VI \cos \phi$$
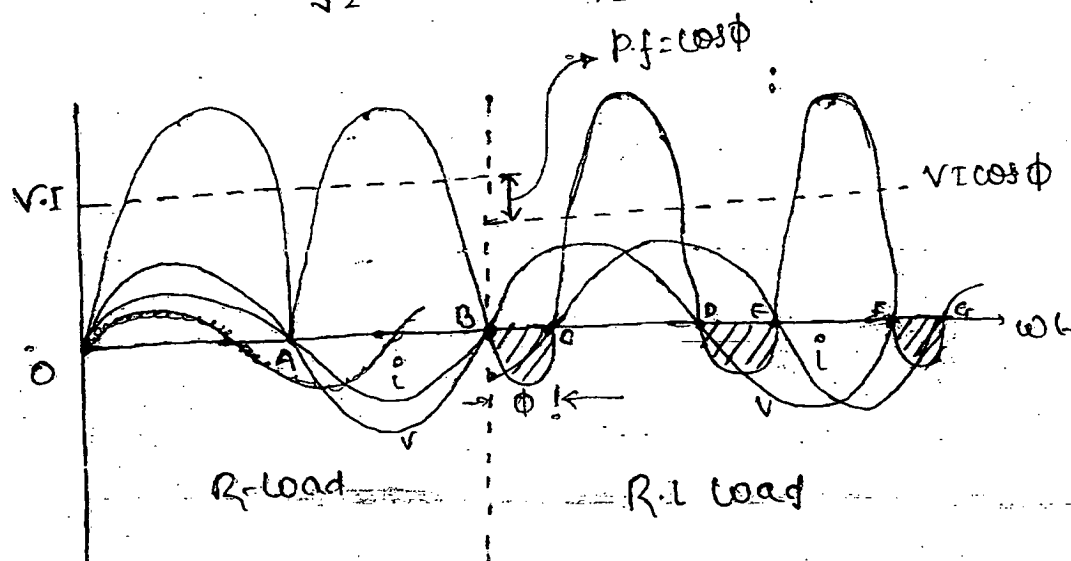
$$\text{Where } \frac{V_m}{\sqrt{2}} = V \quad I = \frac{I_m}{\sqrt{2}}$$




$$\frac{P_{avg RL}}{P_{avg R}} = \frac{VI \cos \phi}{VI} = \cos \phi$$

Concepts:

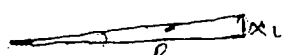

$$\cos \phi \downarrow, \cos \phi \uparrow$$
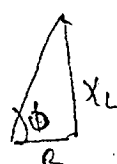
$$P_{avg} \text{ is max } - X_L \downarrow$$




$$\phi \uparrow, \cos \phi \downarrow$$

$$X_L \uparrow, P_{avg} \text{ is min}$$

* Up - Resistance dominates


* down - inductor domin.

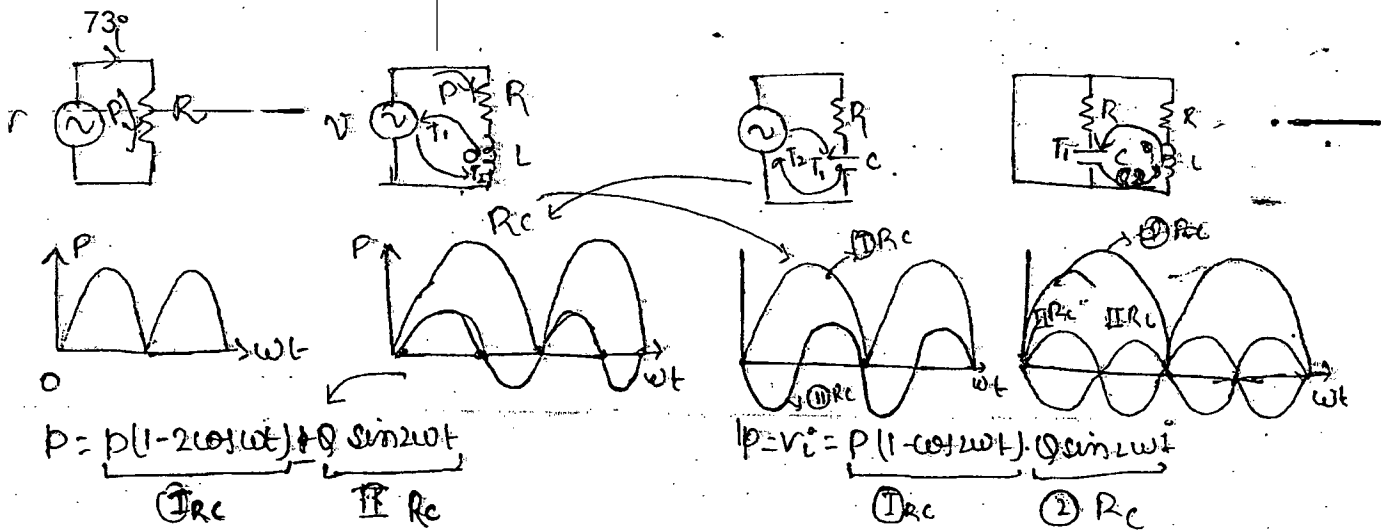

	Source	Sink
L	lead vars	lag vars
C	lag vars	lead vars

Chapter 1

Q 6.

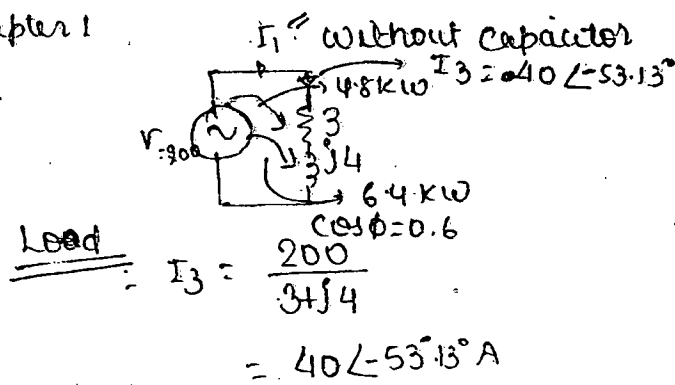

$$\underline{\text{Load}}: I_3 = \frac{200}{3 + j4} = 40 \angle -53.13^\circ \text{ A}$$

$$\cos \phi_3 = \cos 53.13^\circ = 0.6 \text{ lag}$$

$$\begin{aligned}
 S_3 &= I_3^* V^* \\
 &= 200 \times 40 \angle 53.13^\circ \\
 &= 200 (40 \cos 53.13^\circ + j 40 \sin 53.13^\circ) \\
 &= 200 (40 \times 0.6 + j 40 \times 0.8) \\
 &= 4800 + j 6400
 \end{aligned}$$

$$\begin{aligned}
 P_3 &= 4800 & Q_3 &= 6400 \\
 &= 4.8 \text{ kW} & &= 6.4 \text{ kVAR}
 \end{aligned}$$

Source (-ve for delivering)

$$I_3 = -40 \angle -53.13^\circ$$

$$\begin{aligned}
 S &= V (-I_3^*)^* \\
 &= -200 \times 40 \angle 53.13^\circ \\
 &= -200 (40 \cos 53.13^\circ + j 40 \sin 53.13^\circ) \\
 &= -4800 - j 6400
 \end{aligned}$$

$$P_1 = -4.8 \text{ kW}$$


$$Q_1 = -6.4 \text{ kVAR}$$

$$|S_1| = \sqrt{6.4^2 + 4.8^2}$$

$$\cos \phi = 0.6$$

Q with capacitor

(i) $X_c = -j6.25 \Omega$

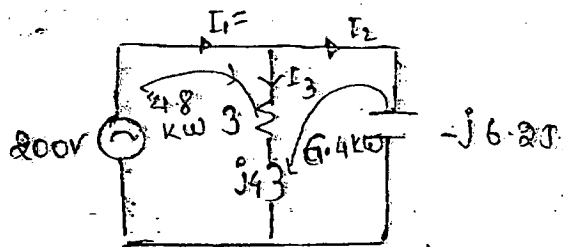

Soln: $\cos \phi = 1$ $\cos \phi = 0.6$ $\cos \phi = 0$
Load

$$I_3 = 40 \angle -53.13^\circ$$

$$P_3 = 4.8 \text{ kW}$$

$$Q_3 = 6.4 \text{ KVAR}$$

$$\cos \phi = 0.6 \text{ lag}$$

Capacitor

$$I_2 = \frac{200}{j6.25} = 32 \angle 90^\circ$$

$$S_2 = V \cdot I_2^*$$

$$= -j6.4 \times 10^3$$

$$P_2 = 0$$

$$Q_2 = -6.4 \text{ KVAR}$$

$$\cos \phi_2 = 0$$

Source:

$$I_1 = I_2 + I_3$$

$$= 40 \angle -53.13^\circ + 32 \angle 90^\circ$$

$$= 24 \angle 0^\circ$$

$$S_1 = V_1 (-I_1^*)$$

$$= 200 (-24 \angle 0^\circ)$$

$$= -4.8 + j0$$

$$P_1 = -4.8 \text{ kW}$$



$$\phi_1 = 0$$

$$\cos \phi = 1$$

$$S_1 = \sqrt{P_1^2 + Q_1^2}$$
$$= 4.8 \text{ KW}$$

- (1) Capacity of the generator reduced so the cost of the electrical energy is min
- (2) Tr. line current reduces
- (3) line losses reduce
- (4) efficiency improve
- (5) voltage regulation improve
- (6)

Importance of Reactive power:

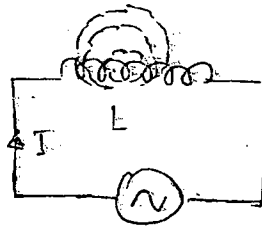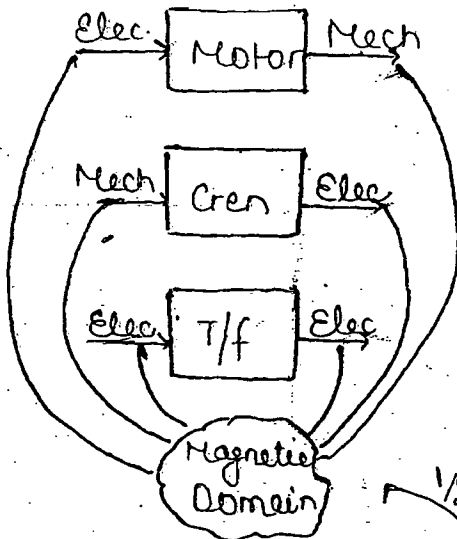

$$\text{Energy} = \frac{1}{2} L \cdot I^2$$

$$= \text{Power} \times T$$

$$P = VI \cos \phi$$



$$Q = VI \sin \phi$$

$$P = VI \cos 90^\circ$$

$$Q = VI \sin 90^\circ$$

$$P = 0$$

$$Q = VI$$

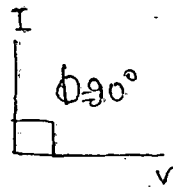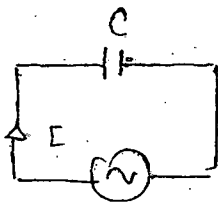

$$\text{Energy} = \frac{1}{2} C V^2$$



$$= \text{Power} \times \text{time}$$

$$P = VI \cos 90^\circ$$

$$Q = VI \sin 90^\circ$$

$$P = 0$$

$$Q = VI$$

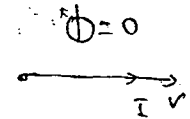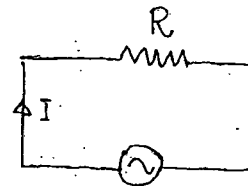

$$\text{Energy} = I^2 R t$$

$$= \text{power} \times \text{time}$$

$$P = VI \cos 0$$

$$Q = VI \sin 0$$


$$P = VI$$

$$Q = 0$$

$$P = \frac{2\pi n T}{60}$$

$$P \propto T$$

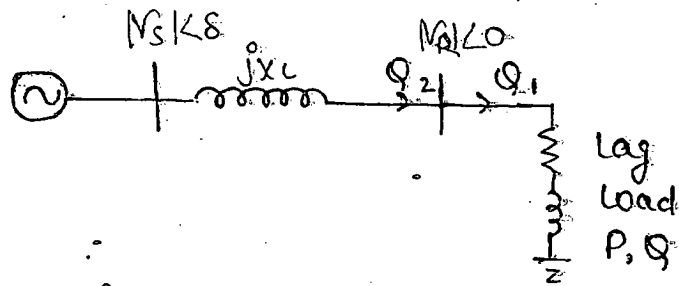N.B. to produce torque active power is used.



Q_1 = Reactive power demand by load

Q_2 = Reactive power supply

$$Q_R = Q_1 - Q_2$$

$$Q_R = \left| \frac{V_S V_R}{X_L} \right| \cos \delta - \left| \frac{V_R^2}{X_L} \right|$$

Assume δ is small $\cos \delta = 1$

$$\Phi_R = \left| \frac{V_S V_R}{X_L} \right| - \frac{V_R^2}{X_L}$$

$$V_R^2 - V_S V_R + X_L \Phi_R = 0$$

$$V_R = \frac{V_S}{2} \pm \sqrt{\frac{V_S^2 - 4X_L \Phi_R}{2}}$$

if $V_R = \frac{V_S}{2} + \sqrt{\frac{V_S^2 - 4X_L \Phi_R}{2}}$

After constructed the trans. line

V_S and X_L constant

$\therefore$ only $\Phi_R \propto V_R$

(a) if $\Phi_R = 0 \Rightarrow Q_1 = Q_2$

$$V_R = V_S$$

$$V_R = 0\%$$

(b) if $\Phi_R > 0 \Rightarrow Q_1 > Q_2$

$$|V_R| < |V_S| \Rightarrow V_{Reg} = +ve$$

Peak load time

(c) if $\Phi_R < 0 \Rightarrow Q_1 < Q_2$


$$|V_R| > |V_S| \Rightarrow V_{Reg} = -ve$$

$\Rightarrow$ ferranti effect

$\Rightarrow$ off peak load time

Q5.

78

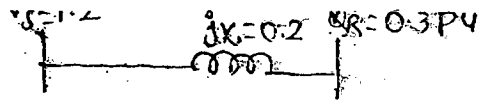

$$\Delta V = (V_S - V_R)$$

$$1.2 - 0.3$$

$$V_R = \frac{V_S}{2} + \sqrt{\frac{V_S^2 - 4X_L Q_R}{2}}$$

$$= \frac{1.2}{2} + \sqrt{\frac{(1.2)^2 - 4 \times 0.2 \times 0.3}{2}}$$

$$= 0.6 + \sqrt{\frac{(1.2)^2 - 0.24}{2}}$$

$$= 0.6 + \sqrt{\frac{1.44 - 0.24}{2}}$$

$$= 1.147 \text{ A.u.}$$

$$0.86 + 0.8j$$

$$-1$$


$$-0.14 + 0.5j$$

$$-0.51 \angle 105^\circ$$

$$0.5 \angle 90^\circ$$

$$0.5 \angle 15^\circ$$

Concept 1

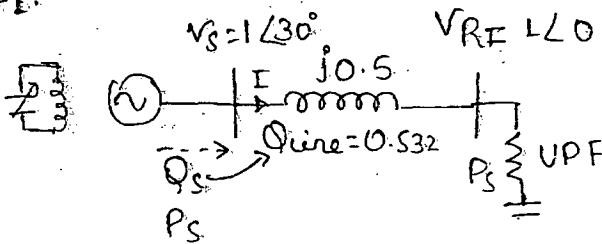

$$I = \frac{V_S - V_R}{jX} = \frac{1 \angle 30^\circ - 1 \angle 0^\circ}{j0.5} = \frac{0.5 \angle 105^\circ}{0.5 \angle 90^\circ} = 1.03 \angle 15^\circ$$

$$Q_{line} = |I|^2 X_L = 1.03^2 \times 0.5 = 0.532$$

Concept 2:

$$Q_S = \frac{V_S^2}{X_L} - \frac{V_S V_R \cos \delta}{X_L} = \frac{V_S}{X_L} (V_S - V_R) \cos \delta = 1$$

$$Q_R = \frac{V_R}{X_L} (V_S - V_R)$$






$$Q_S \propto (V_S - V_R)$$

$$Q_R \propto (V_S - V_R)$$

$$P_R = \left| \frac{V_R V_S}{X_L} \right| \sin \delta$$

$$P_R \propto \sin \delta$$

79.
Q3 use of compensator:

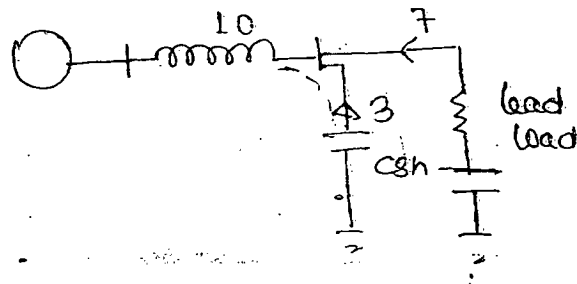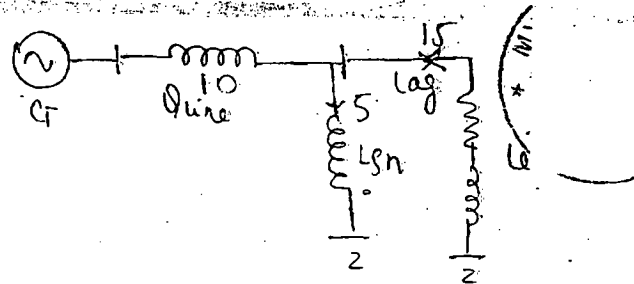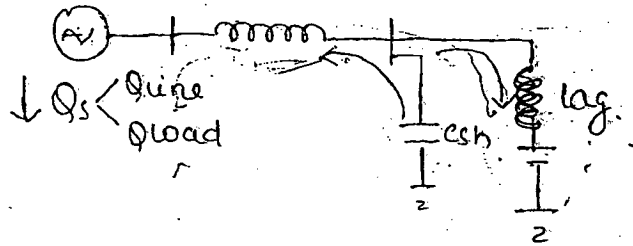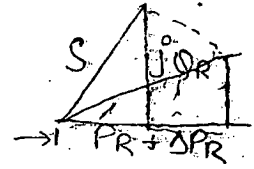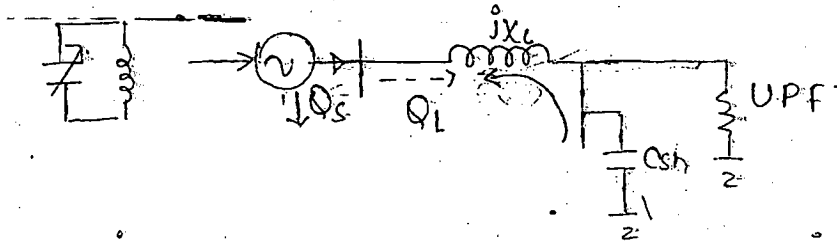

Compensator is used to reduce Reactive power to the delivered max^m active power at load

Q. A Tr. Line has reactance 0.5 pu operates at $V_R = 1 \angle 0^\circ$. calculate V_S and δ for supplying loads.

Soln. (a) UPF ahpv (b) 1 P.u active power at 0.8

Soln (a) $P_R = \frac{V_R |V_S|}{X_L} \sin \delta$
 $1 = \frac{V_S \cdot 1}{0.5} \sin \delta$

$$V_S \sin \delta = 0.5 \quad \text{--- (i)}$$

$$Q_R = \frac{V_S V_R}{X_L} \cos \delta - \frac{V_R^2}{X_L}$$

For UPF $Q_R = 0$

$$0 = \frac{0.5 \times V_S}{0.5} \cos \delta - \frac{1}{0.5}$$

$$V_S \cos \delta = 1 \quad \text{--- (ii)}$$

from eqn (i) $\cos \delta = \frac{1}{0.5}$

$$\tan \delta = \frac{0.5}{1}$$

$$\begin{cases} \delta = 26.56^\circ \text{ Ans} \\ V_S = 1.11 \text{ P.u} \end{cases}$$

(b) $P_R = \frac{V_R |V_S|}{X_L} \sin \delta$

$$1 = \frac{V_S \cdot 1}{0.5} \sin \delta$$

$$V_S \sin \delta = 0.5 \quad \text{--- (i)}$$

$$Q_R = \left| \frac{V_S V_R}{X_L} \right| \cos \delta - \left| \frac{V_R^2}{X_L} \right|$$


$$\Phi_R = P_R \tan \phi = 0.75$$

$$0.75 = \left| \frac{V_S \times 1}{0.5} \right| \cos \delta - \frac{1^2}{0.5}$$

$$V_S \cos \delta = 1.75 \quad \text{--- (ii)}$$

$$V_S = 1.42$$

$$\delta = 20^\circ$$

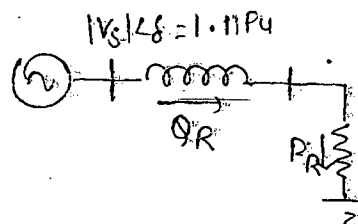

concept

$$* P_R \sin \delta$$

$$* Q_R \sin \delta - V_R$$

$$P_R = \frac{V_S |V_S|}{X_L}$$


Note: ⁸¹ With uncompensated Tr. line For supplying active & reactive power, δ and $(V_S - V_R)$ has to be maintain this is not practically valid for continuously variable load. To compensate this effect, all power factor correction device like shunt capacitor and reactor to be installed at the load end so $|V_S|$ and $|V_R|$ can be maintained.

The reactive power Burden at the Gen end is reduces so that max^m active power is delivered by generator.

Q. In the previous problem calculate the rating and type of the compensator required for maintaining $|V_S| = |V_R| = 1 \text{ p.u.}$ for the following load.

- (a) 1 P.U UPF (b) 1 P.U 0.8 lag (c) 1 P.U 0.8 lead
(C) 1 P.U 0.995 lead.

Soln:-

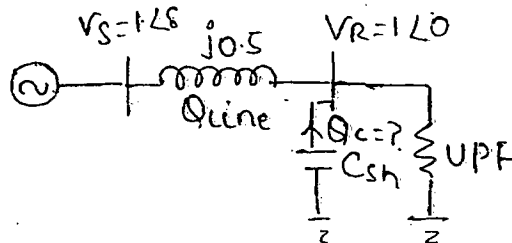


for V_S = reduce 1.11 to 1

$$P_R = \frac{V_S V_R \sin \delta}{X_L}$$

$$I = \frac{P_R}{V_R \cos \delta}$$

$$\delta = 30^\circ$$

$$Q_{\text{line}} = I^2 X_L = 0.536$$

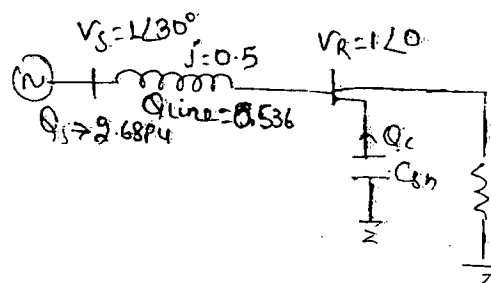

$$Q_s = \frac{V_s^2}{X_L} - \frac{V_s V_R}{X_L} \cos \delta$$

$$= \frac{1^2}{0.5} - \frac{1 \times 1}{0.5} \cos 30^\circ = 0.268 \text{ pu}$$


$$Q_c = 0.536 - 0.268 = 0.268 \text{ pu supplied by } C_{sh}$$

Method II


$$Q_R = \left| \frac{V_s V_R}{X_L} \right| \cos \delta - \frac{V_R^2}{X_L}$$

$$= \frac{1 \times 1}{0.5} \cos 30^\circ - \frac{1}{0.5}$$

$$Q_R = -0.268 \text{ pu} = +0.268$$

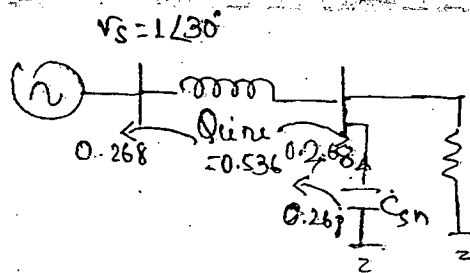

② 1 pu 0.8 lag

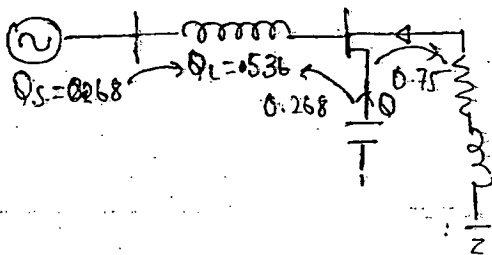

$$Q_{load} = 1 \times \tan^{-1}(\cos^{-1} 0.8) = 0.75$$


$$Q_s = 0.268$$

$$Q_L = 0.536$$

$$Q_c = (Q_{load} + Q_{line}) - Q_s$$

$$= 1.018 \text{ pu}$$

(3)

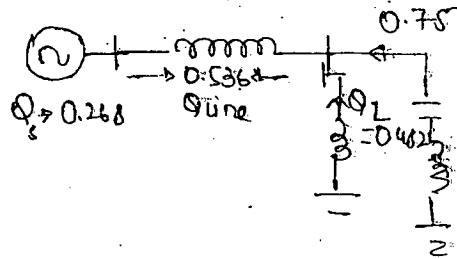

$$\underline{Z} = \frac{P + jQ}{P - jQ}$$

$$\underline{Z} = R + jX = X_d$$

$$X_d > X_c$$


$$\underline{Z} = R +$$

$$Q_{load} = 1 \times \tan^{-1}(-\cos^{-1} 0.8) = -0.75$$

load deliver 0.75 lag vars

$$Q_L = 0.75 - 0.268 = 0.482 \text{ pu of lag vars absorbed by } L_{sh}$$

(4)

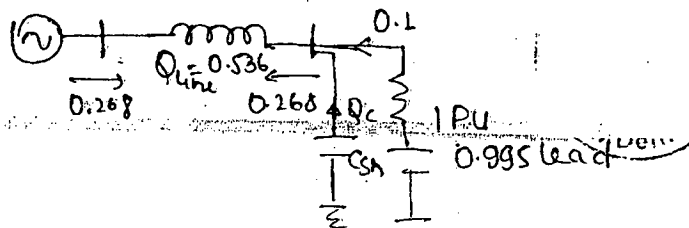

$$Q_{load} = 1 \times \tan^{-1}(-\cos^{-1} 0.995) = -0.1 \text{ pu}$$

load deliver 0.1 pu of lag vars

$$Q_c = 0.268 - 0.1 = 0.168 \text{ lags vars supplied by } C_{sh}$$