

An inverter is a circuit which converts a dc power into an ac power at desired output voltage and frequency.

Note:

For low and medium power output, we use BJTs, MOSFET, IGBT, GTO. But for high power output, thyristor should be used.

Types of Inverter

1. Voltage Source Inverter (VSI)

VSI is one in which dc source has small impedance. Because of a low internal impedance, the terminal voltage of a voltage source inverter remains substantially constant with variation in load.

2. Current Source Inverter (CSI)


Current source inverter is supplied with a controlled current from a dc source of high impedance. Typically, a phase controlled thyristor rectifier feeds the inverter with a regulated current through a large series inductor. Thus, load current is controlled.

Remember:

- CSI does not required any feedback diodes whereas, these are required in a VSI.
- To make input current almost ripple free ,L-filter is used before CSI.
- CSI may be load or force commutated. Load commutation is possible when load p.f. is leading. For lagging p.f. loads, force commutation is essential.

Single Phase Bridge Inverter

1. Single-Phase Half Bridge Inverter

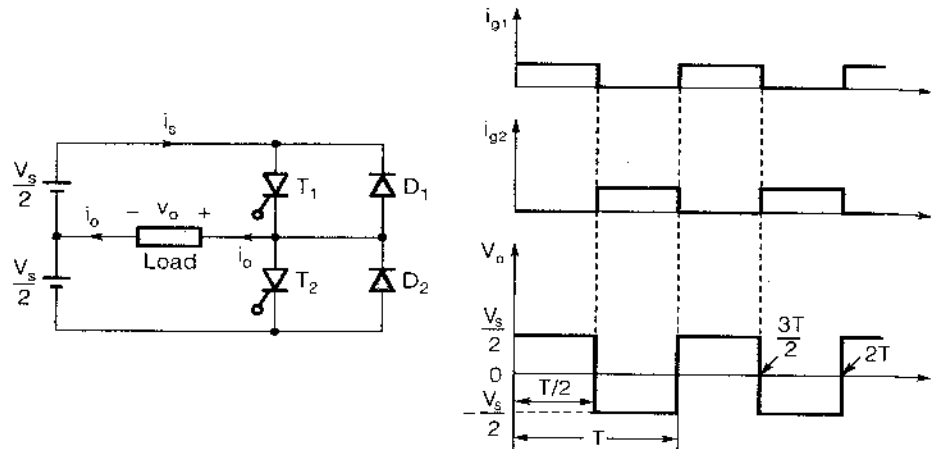

For R load

- RMS output voltage

$$V_{or} = \frac{V_s}{2}$$

- n^{th} harmonic output voltage

$$V_{on} = \frac{2V_s}{n\pi} \sin n\omega t$$

- n^{th} harmonic current

$$I_{on} = \frac{2V_s}{n\pi R} \sin n\omega t$$

- Fundamental output voltage

$$V_{o1} = \frac{2V_s}{\pi} \sin \omega t$$

- RMS fundamental output voltage

$$(V_{o1})_{RMS} = \frac{\sqrt{2} V_s}{\pi}$$

- Fundamental distortion factor (FDF)



$$g = \frac{(V_{o1})_{RMS}}{V_{or}} = \frac{2\sqrt{2}}{\pi}$$

- Total harmonic distortion (THD)

$$THD = \left(\frac{1}{g^2} - 1 \right)^{1/2}$$

$$THD = 48.34\%$$

2. Single Phase-Full Bridge Inverter

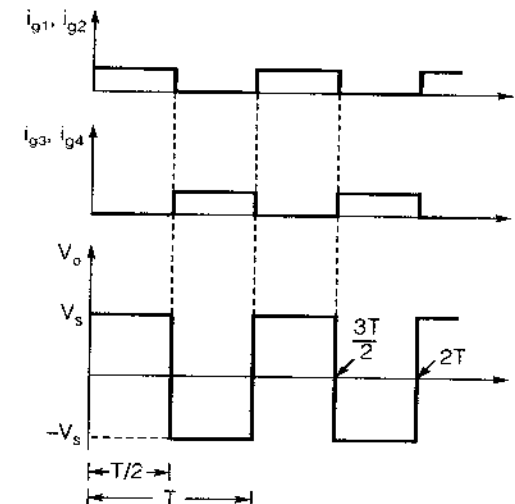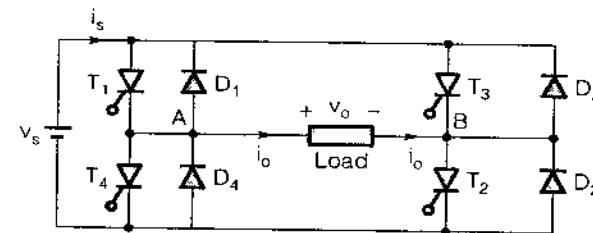

For R load

- RMS output voltage

$$V_{or} = V_s$$

- n^{th} harmonic output voltage

$$V_{on} = \frac{4V_s}{n\pi} \sin n\omega t$$

- Fundamental output voltage

$$V_{o1} = \frac{4V_s}{\pi} \sin \omega t$$

- RMS fundamental output voltage

$$(V_{o1})_{RMS} = \frac{2\sqrt{2}}{\pi} V_s$$



- Fundamental distortion factor (FDF)

$$g = \frac{2\sqrt{2}}{\pi}$$

- Total harmonic distortion (THD)

$$THD = 48.34\%$$

Single Phase VSI for Different Loads

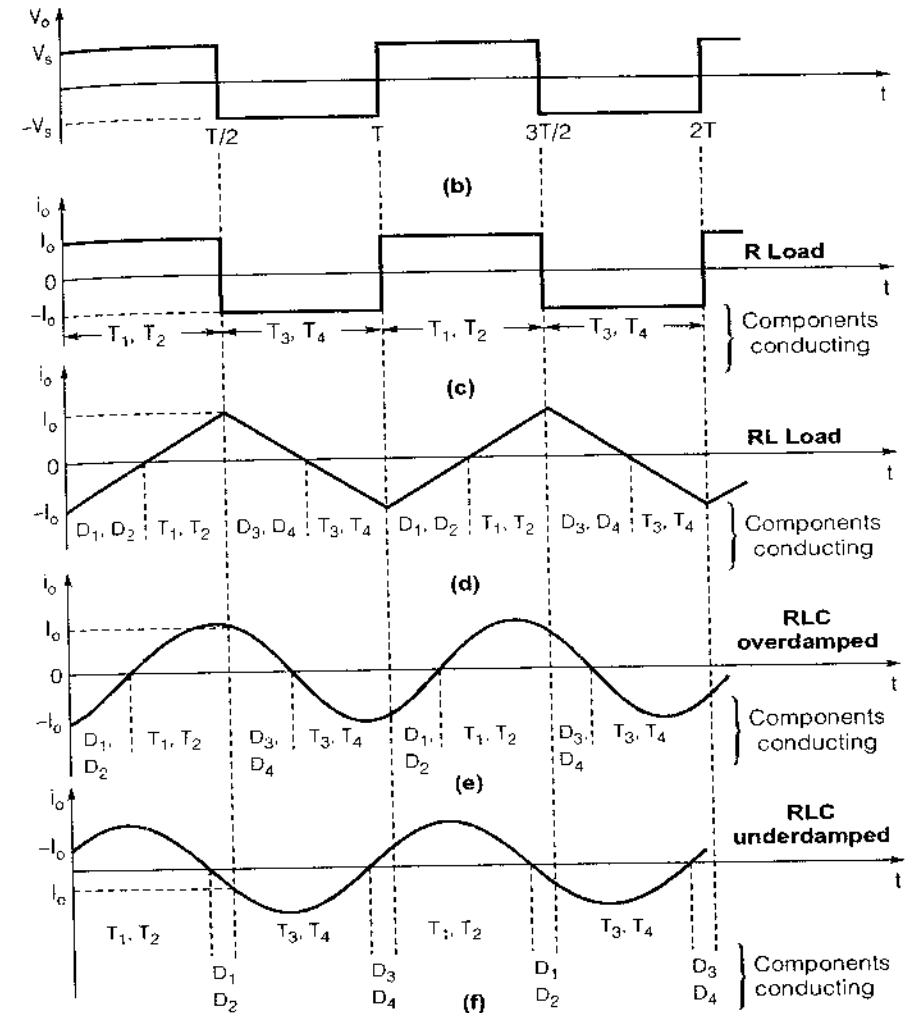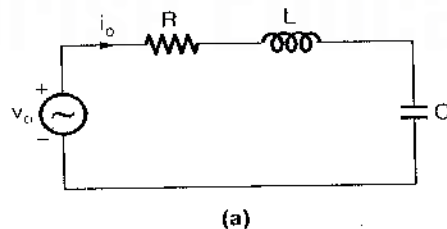

- Load impedance at frequency ($n\omega$)

$$Z_n = \left[R^2 + \left(n\omega L - \frac{1}{n\omega C} \right)^2 \right]^{1/2}$$

- Phase angle

$$\phi_n = \tan^{-1} \left[\frac{n\omega L - \frac{1}{n\omega C}}{R} \right] \text{ rad}$$

□ Output current at the instant of commutation

$$I_o = \frac{V_o}{Z_n} \quad \omega t = \pi$$

□ Fundamental load power

$$P_{o1} = I_{o1}^2 R = V_{o1} I_{o1} \cos \theta_1$$


where, I_{o1} = RMS value of fundamental output current
 V_{o1} = RMS value of fundamental output voltage

Note:


- If circuit turn-off time (t_c) is more than device turn-off time (t_q) then it does not require force commutation.
- If $t_q > t_c$ then force commutation required.
- The fundamental output power P_{o1} does the useful work and the output power associated with harmonic current is dissipated as heat, leading to rise in load temperature.
- Feedback diode (D) conducts only when there is presence of energy storing element L and C in load.

Three Phase Bridge Inverter

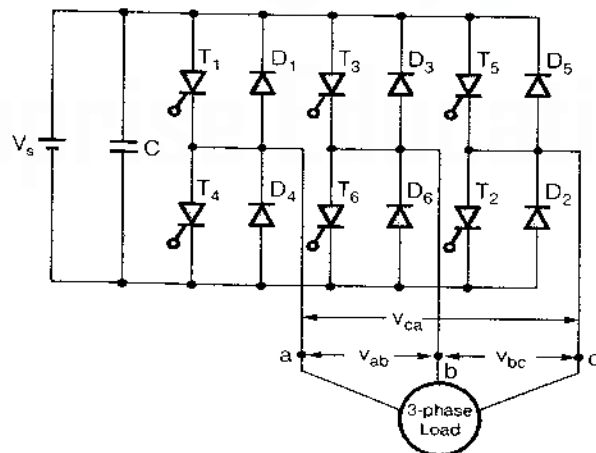For providing adjustable frequency power to industrial application, 3 ϕ bridge inverter are used. A large capacitor is connected at the input terminals tend to make the input DC voltage constant.



1. 3 ϕ 180° Mode VSI

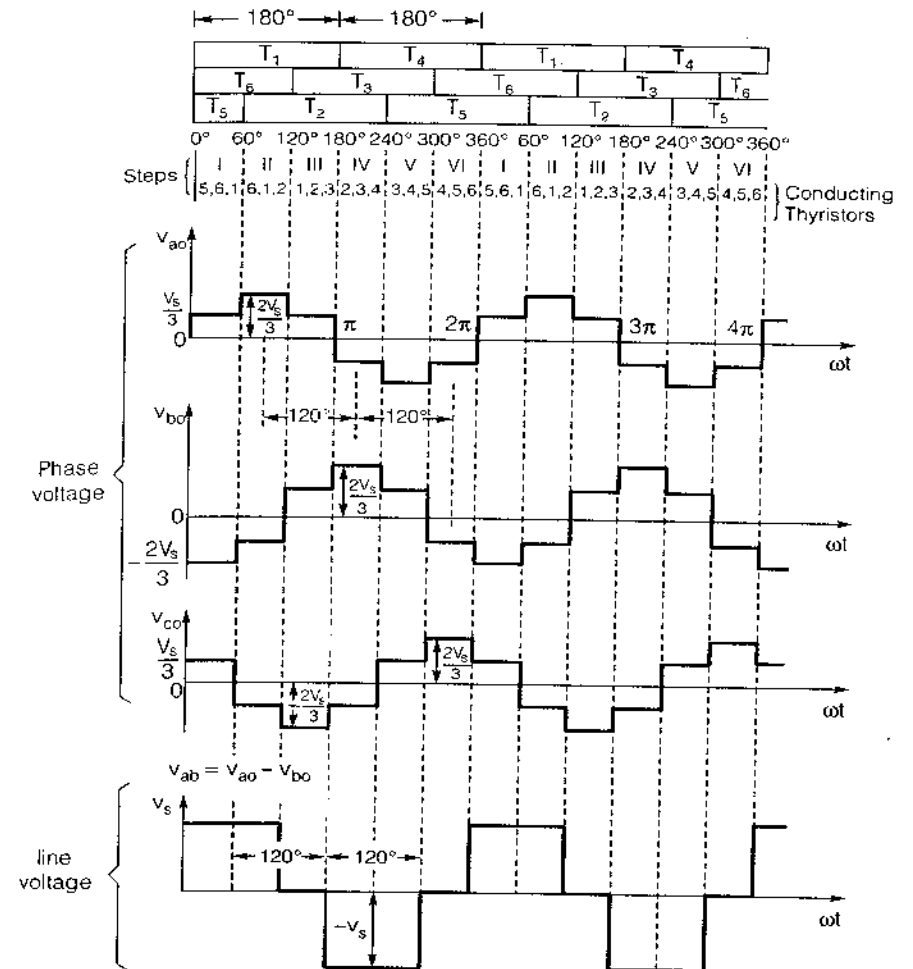

□ Phase RMS voltage

$$(V_{ph})_{RMS} = \frac{\sqrt{2}}{3} V_s$$

□ Line RMS voltage

$$(V_L)_{RMS} = \sqrt{\frac{2}{3}} V_s$$

- n^{th} harmonic output voltage for phase "a"

$$V_{an} = \frac{2V_s}{n\pi} \sin n\omega t$$

- Fundamental phase RMS voltage

$$(V_{a1}) = \frac{\sqrt{2} V_s}{\pi}$$

□

$$\text{FDF (g)} = \frac{3}{\pi}$$

□

$$\text{THD} = 31\%$$

- n^{th} harmonic line output voltage

$$(V_{ab})_n = \frac{4V_s}{n\pi} \cos \frac{n\pi}{6} \sin n\left(\omega t + \frac{\pi}{6}\right)$$

- Fundamental RMS line value

$$(V_{ab})_{\text{RMS}} = \frac{2\sqrt{2}}{\pi} \cos \frac{\pi}{6} = \frac{\sqrt{6}}{\pi} V_s$$

□

$$\text{FDF (g)} = \frac{3}{\pi}$$


□

$$\text{THD} = 31\%$$

Remember:

- The phase as well as line voltage are out of phase by 120° .
- For $n = 3$, all triplen harmonics are absent from the line voltage.

2. 3ϕ 120° Mode VSI

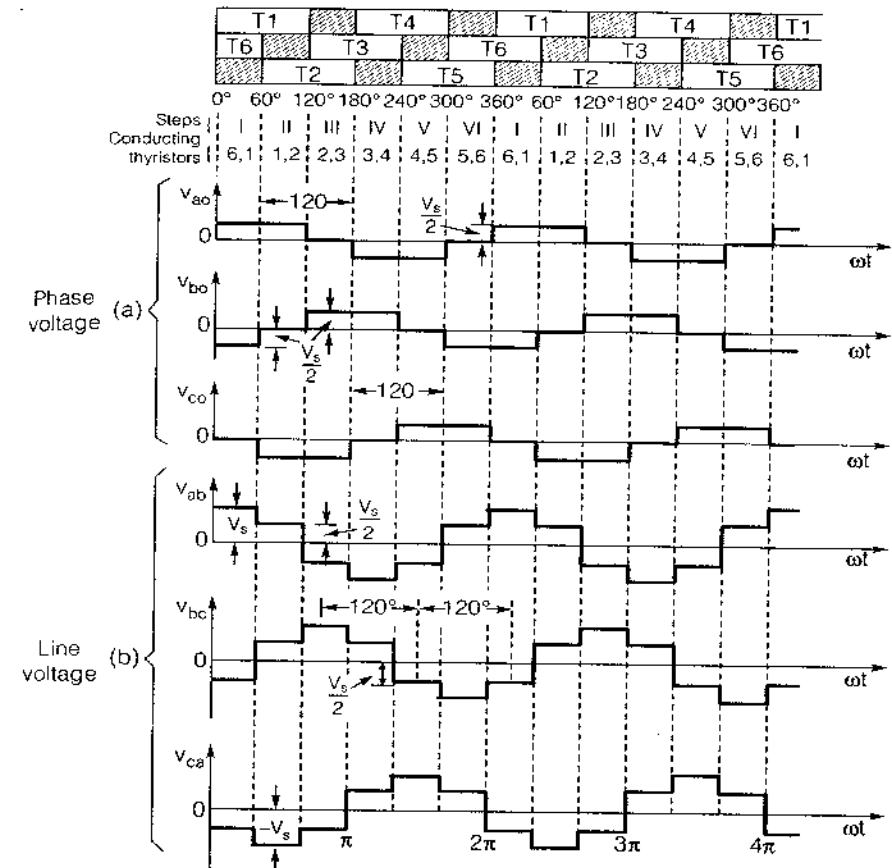

- Line voltage

$$V_{ab} = \sum_{n=6k \pm 1} \frac{3V_s}{n\pi} \sin n\left(\omega t + \frac{\pi}{3}\right)$$

where, $k = 0, 1, 2 \dots$

- Phase voltage

$$V_{a0} = \sum_{n=1,3,5,\dots} \frac{2V_s}{n\pi} \cos \frac{n\pi}{6} \sin n\left(\omega t + \frac{\pi}{6}\right)$$

- RMS value of phase voltage

$$V_p = \frac{V_s}{\sqrt{6}} = 0.4082 V_s$$

- RMS value of line voltage

$$V_L = \frac{V_s}{\sqrt{2}} = 0.7071 V_s$$

For both line and phase voltage:


- $FDF = \frac{3}{\pi}$ and THD = 31%

Remember:

- Generally we used IGBT in 1 ϕ and 3 ϕ inverter.

Pulse Width Modulated Inverters

1. Single-pulse Modulation

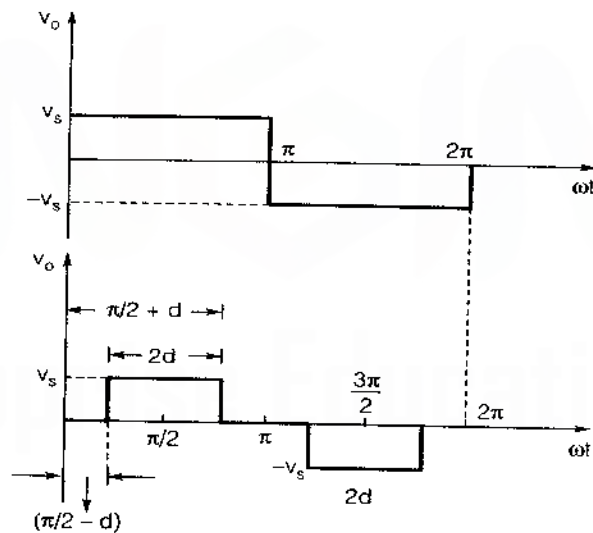

- Output voltage

$$V_0 = \sum_{n=1,3,5,\dots} \frac{4V_s}{n\pi} \sin \frac{n\pi}{2} \sin nd \cdot \sin n\omega t$$

- Pulse width

$$\text{Pulse width} = 2d$$

- Peak value of n^{th} harmonic

$$V_{onm} = \frac{4V_s}{n\pi} \sin nd$$

- RMS value of output voltage

$$V_{or} = V_s \left[\frac{2d}{\pi} \right]^{1/2}$$


$$FDF(g) = \frac{2\sqrt{2} \sin d}{\sqrt{\pi} \cdot 2d}$$

$$THD = \sqrt{\frac{1}{g^2} - 1}$$

Remember:

When pulse width $2d = \frac{2\pi}{n}$, then n^{th} harmonic eliminated.

2. Multiple Pulse Width Modulation

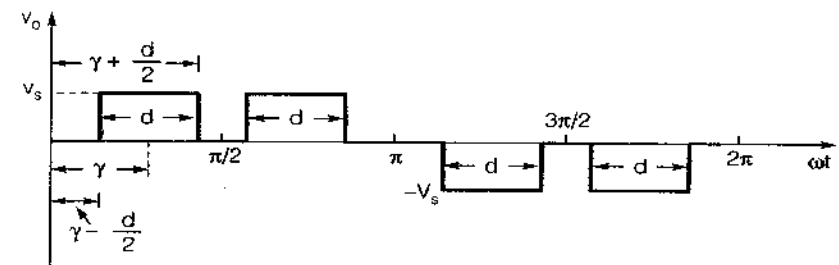

- Output voltage

$$V_0 = \sum_{n=1,3,5,\dots} \frac{8V_s}{n\pi} \sin n\gamma \sin \frac{nd}{2} \sin n\omega t$$

$$\gamma = \frac{\pi - 2d}{N+1} + \frac{d}{N}$$

where, N = Number of pulses per half cycle.

- Amplitude of the n^{th} harmonic of the two pulse wave form

$$V_n = \frac{8V_s}{n\pi} \sin n\gamma \cdot \sin \frac{nd}{2}$$

- Condition to eliminate n^{th} harmonic

$$(i) \gamma = \frac{\pi}{n} \quad (ii) 2d = \frac{4\pi}{n}$$

Remember:

- By using PWM technique, we can get variable voltage and frequency within inverter itself by eliminating some of the lower order harmonics.
 - In PWM inverter, force commutation is essential.
-

