

RC Circuit with Source

By KVL

$$V = iR + \frac{1}{C} \int i dt$$

Diff. w.r.t t

$$0 = R \frac{di}{dt} + \frac{i}{C}$$

Divide both sides by R we get

$$\frac{di}{dt} + \frac{i}{RC} = 0$$

$$i(t) = CF + PI$$

CF $\rightarrow$ Transient Response

$$\frac{di}{dt} + \frac{i}{RC} = 0$$

$$i(t) = A e^{-t/RC}$$

PI $\rightarrow$ steady state response

$$C \rightarrow \infty$$

$$i = 0$$

$$i(t) = CF + PI$$

$$i(t) = A e^{-t/RC} + 0$$

$$A = i(0^+) - i(\infty)$$

$$t = 0^-, V_C = 0$$


$$t = 0^+, V_C = 0$$

By KVL

$$t = 0^+ \quad V = V_R + V_C \\ = iR + 0$$

$$\text{at } t \rightarrow \infty \quad i = \frac{V}{R}$$


$$i(t) = CF + PI$$

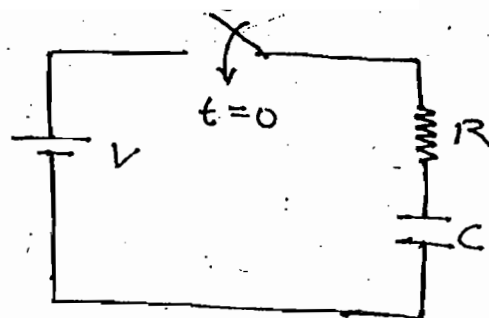

$$A = i(0^+) - i(\infty)$$


$$A = \frac{V}{R} - 0$$

$$i(t) = \frac{V}{R} e^{-t/RC}$$

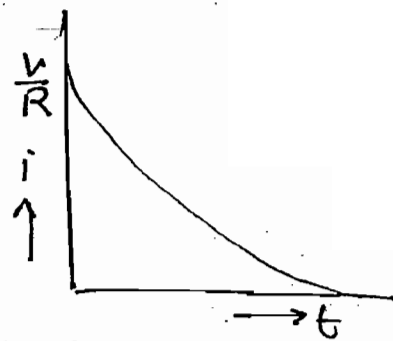

$$V_R = iR$$

$$V_R = V e^{-t/RC}$$

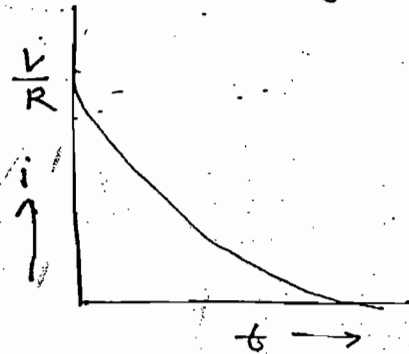


$$V_C = \frac{1}{C} \int_0^t i dt$$

$$V_C = \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$

$$V_C = -V e^{-t/RC} + V$$


$$V_C(t) = [V_C(0^+) - V_C(\infty)] e^{-t/RC} + V_C(\infty)$$

$$V_C(t) = V(1 - e^{-t/RC})$$

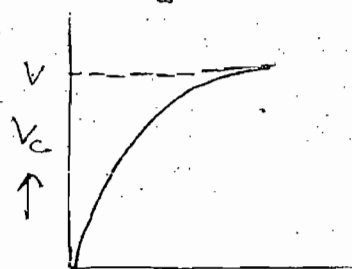


Ques:- Find response of V_C , I_C and V_x when initial voltage of the capacitor is 3V

Soln:-

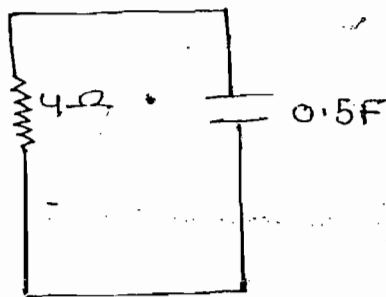

$$V_C = V_0 e^{-t/RC}$$

$$V_C = 3 e^{-t/2}$$

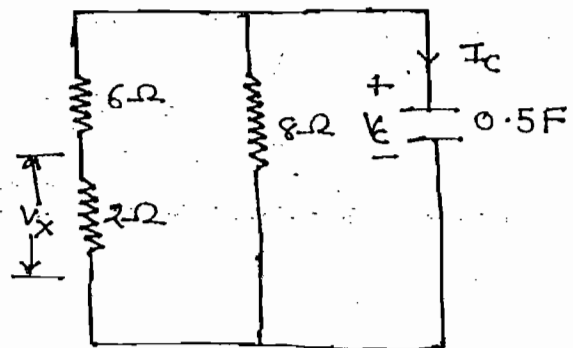

$$V_x = V_c \frac{2}{2+t} \Rightarrow V_x = 3e^{-t/2} \cdot \frac{1}{4}$$

$$\Rightarrow V_x = \frac{3}{4} e^{-t/2}$$


$$I_c = C \frac{dV_c}{dt}$$

$$I_c = \frac{1}{2} \frac{d(3e^{-t/2})}{dt} = 3 \left(\frac{1}{2}\right) \left(-\frac{1}{2}\right) e^{-t/2}$$

$$\Rightarrow \boxed{I_c = -\frac{3}{4} e^{-t/2}} \quad \text{Ans}$$

Ques:- Find rate of rise of voltage across the capacitor at $t = 0^+$

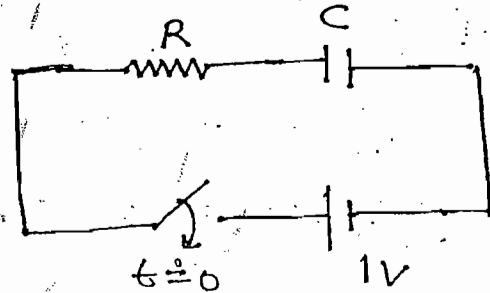(a) RC (b) $\frac{1}{RC}$ (c) 0 (d) $2RC$



Soln:-

$$V_c = -V e^{-t/RC} + V$$

$$\frac{dV_c}{dt} = (-V) \left(-\frac{1}{RC}\right) e^{-t/RC} + 0$$

$$\frac{dV_c}{dt} = \frac{V}{RC} e^{-t/RC}$$


$$t = 0^+$$

$$\frac{dV_c}{dt} (0^+) = \frac{V}{RC} = \frac{1}{RC}$$

Ques:- Find $\frac{dI_1}{dt}$ at $t = 0^+$

Soln:- Step-(1): -

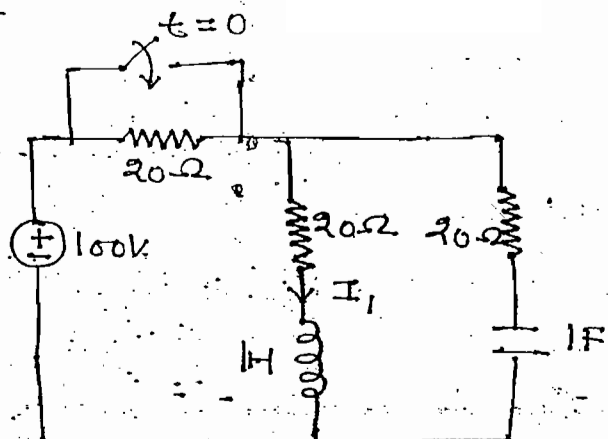Develop eq. circuit at $t = 0^-$ and find initial current of conductor and initial voltage of capacitor



→ In the above ckt at $t = 0^-$ for DC source inductor behaves as S.C. and C behaves as O.C

$$i_L(0^-) = \frac{100}{20+20} = 2.5A$$

$$V_C(0^-) = 2.5 \times 20 = 50$$

Step-2:-

Develop eq. ckt at $t=0^+$ and indicate initial current of the inductor and initial voltage of the capacitor.



$t=0^+$

$$i_L(0^+) = i_L(0^-) = 2.5A$$


$$V_C(0^+) = V_C(0^-) = 50V$$

$$V_L = L \frac{di}{dt}$$
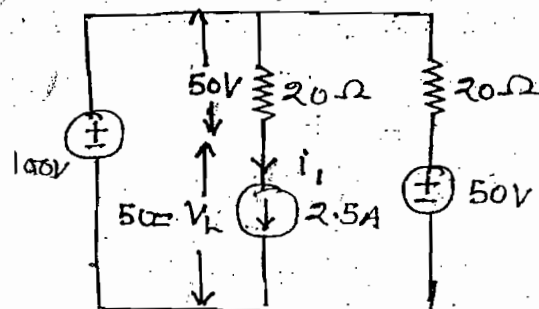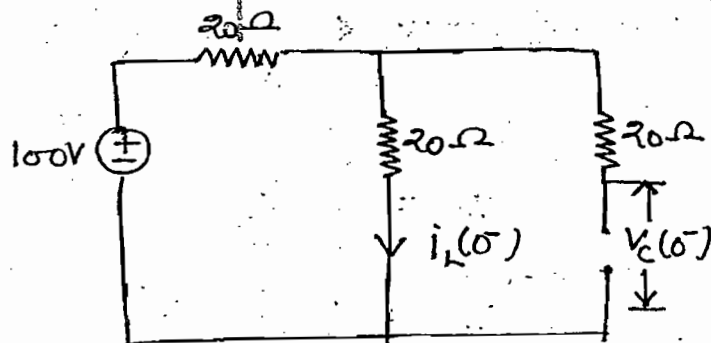
$$\Rightarrow 50 = 1 \frac{di}{dt} \Rightarrow \frac{di}{dt} = 50 A/s \quad Ans$$



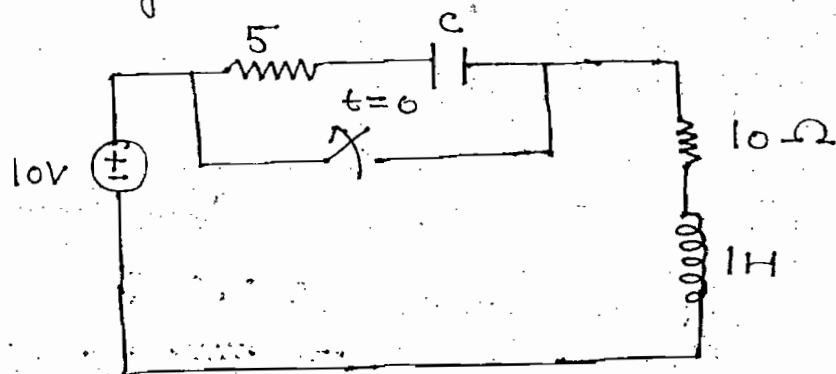
ques:- Find voltage across the switch at $t=0^+$



Soln:- At $t=0^-$

→ Develop equivalent circuit at $t=0^-$

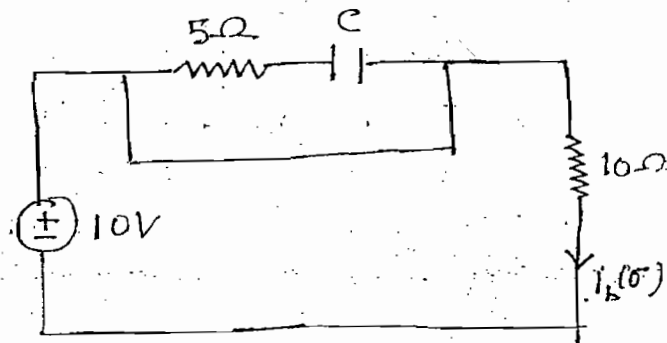→ In the above ckt. at $t=0^-$ capacitor is uncharged & for DC source inductor behaves as a S.C



$$i_L(0^-) = \frac{10}{10} = 1A, \quad V_C(0^-) = 0$$


Step-2:-

At $t = 0^+$

$$i_L(0^+) = i_L(0^-) = 1A$$

$$V_C(0^+) = V_C(0^-) = 0$$


$$V(0^+) = 5 \times 1 = 5V$$

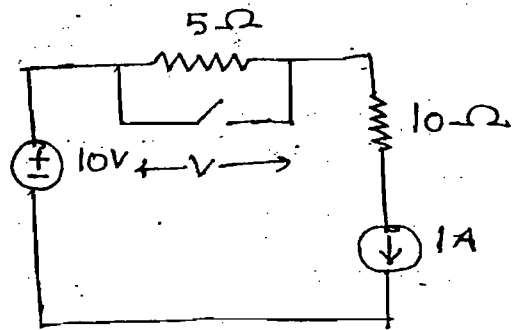

ques:- Find I in capacitor and voltage across inductor at $t = 0^+$

Soln:- Step (I):-

Develop eq. ckt. at $t = 0^-$

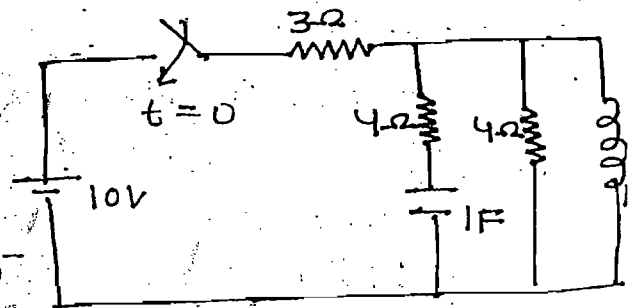

→ In the above ckt at $t = 0^-$ capacitor and inductor are uncharged elements.

$$t = 0^-, V_C(0^-) = 0$$

$$i_L(0^-) = 0$$

Step-(II):-


At $t = 0^+$

$$i_L(0^+) = i_L(0^-) = 0$$

$$V_C(0^+) = V_C(0^-) = 0$$

$$I_C(0^+) = 1A$$



$$V_L(0^+) = 4 \times 1 = 4V$$

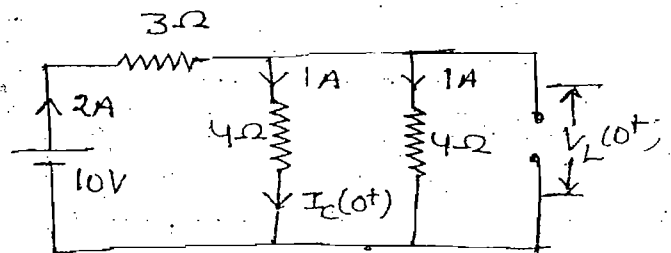

ques:- Find initial voltage and final voltage of the capacitor

Soln:- Step (I):-

$t = 0^-$

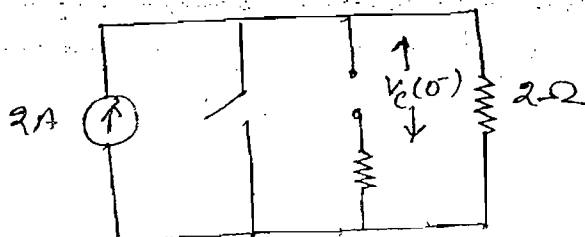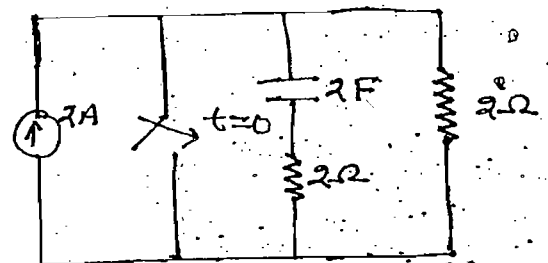


$$V_C(0^-) = 2 \times 2 = 4V$$

Step-(ii):-

$$\text{At } t = 0^+$$

$$V_C(0^+) = V_C(0^-) = 4V$$

$$V_C(\infty) = 0$$

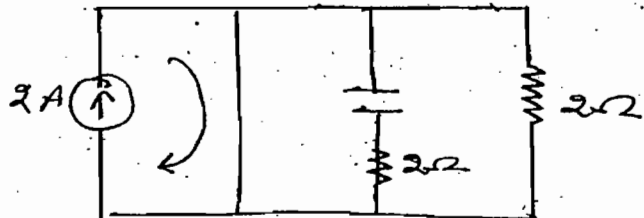


Ques:- Find

(i) Energy of Capacitor at $t = \infty$

(ii) Current in the capacitor at $t = 1\text{sec}$

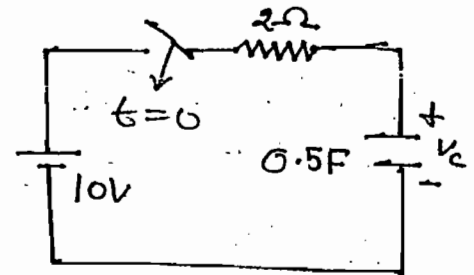(iii) Energy of the resistor from 0 to ∞ interval




When initial charge of the capacitor is $10C$


Soln:- At $t = 0^+$ ($\because Q_{in} = 10C$)

$$V_0 = \frac{Q_0}{C} = \frac{10}{0.5} \Rightarrow V_0 = 20$$

At $t = \infty$

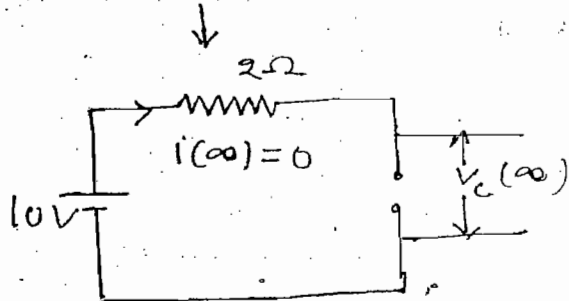

$$V_C(\infty) = 10V$$

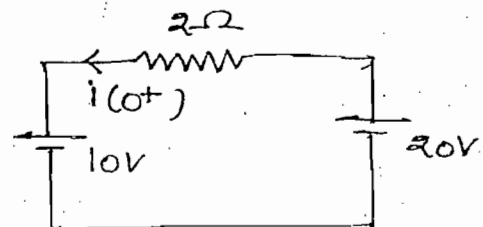

$$W_C(\infty) = \frac{1}{2} C V_C^2(\infty) = \frac{1}{2} \cdot \frac{1}{2} \cdot (10)^2 = 25J$$

$$(ii) i(t) = [i(0^+) - i(\infty)] e^{-t/RC} + i(\infty)$$

$$\Rightarrow i(t) = [-5 - 0] e^{-t/1} + 0$$

$$i(t) = -5 e^{-t}$$

At $t = 1\text{sec}$

$$i(1s) = -5 e^{-1} = -\frac{5}{e}$$

$$= -1.84$$

(iii)

$$W_R = \int_0^{\infty} P dt = \int_0^{\infty} i^2 R dt = \int_0^{\infty} (-5e^{-t})^2 2 dt$$

$$\Rightarrow W_R = 25J \quad , \text{Ans.}$$


Time Constant :-

→ Time constant can be define either w.r.t charging or discharging action of energy storage element


→ Time constant is the time taken for response to rise 63.2% of max. value and it is given by

$$\boxed{\begin{array}{l} T = \frac{L}{R} \text{ sec.} \\ T = RC \end{array}}$$

RC ckt with source

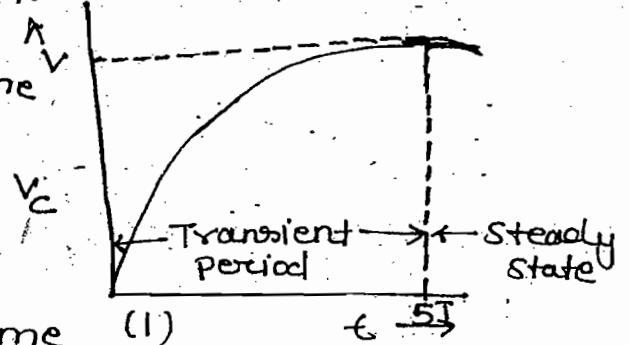

RL ckt with source

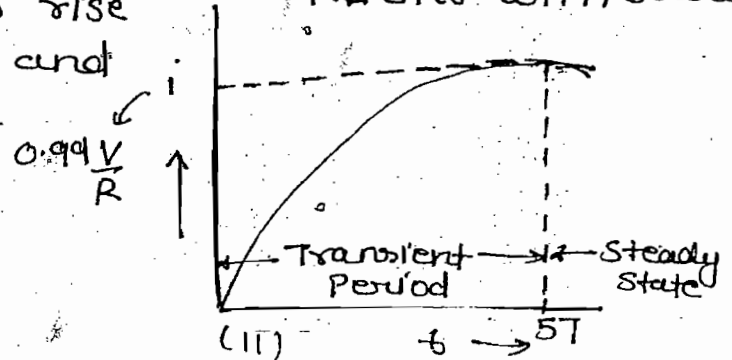

$$V_C(t) = V(1 - e^{-t/T})$$

$$(i) \quad t = T \quad V_C = V(1 - e^{-1}) = 0.632V$$

$$(i) \quad V_C(t) = V(1 - e^{-t/RC})$$


$$(ii) \quad i(t) = \frac{V}{R}(1 - e^{-Rt/L})$$

$$t = 5T \quad V_C = V(1 - e^{-5}) = 0.99V$$

$$R_1 = 10\Omega \quad P_1 = I^2 R_1 \quad t = 10\text{sec}$$

$$R_2 = 20\Omega \quad P_2 = i^2 R_2 \quad t = 7\text{sec}$$
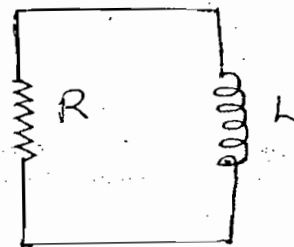
$$R_3 = 100\Omega \quad P_3 = i^2 R_3 \quad t = 2\text{sec}$$



$$\text{Hence } T = \frac{L}{R}$$

$$R_1 = 10\Omega$$

$$P_1 = \frac{V^2}{R_1}$$

$$t = 10\text{sec}$$

$$R_2 = 20\Omega$$


$$P_2 = \frac{V^2}{R_2}$$

$$t = 15\text{sec}$$

$$R_3 = 100\Omega$$

$$P_3 = \frac{V^2}{R_3}$$

$$t = 50\text{sec}$$

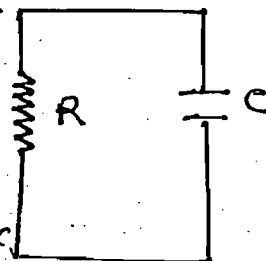


$$\text{Hence } T = RC$$

Ques:- Find V_o response for $t > 0$

$$V_{C_1}(0) = 24\text{V}$$

$$V_{C_2}(0) = 6\text{V}$$

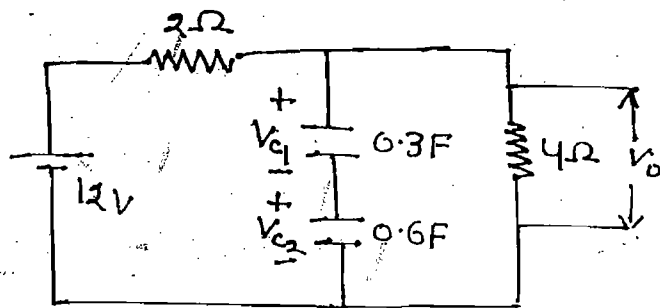

$$(a) 8 + 22e^{-3.75t}$$

$$(b) 8 + 22e^{-t/3.75}$$


$$(c) 8 + 22e^{-t/1.2}$$

$$(d) 8 + 22e^{-1.2t}$$

Soln:- For time constant, deactivate all the independent sources

$$R_{eq} = \frac{2 \times 4}{2 + 4}$$
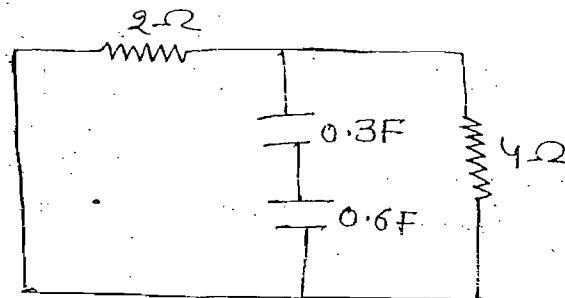
$$C_{eq} = \frac{0.3 \times 0.6}{0.3 + 0.6}$$



$$T = R_{eq} C_{eq} = RC$$

$$V(t) = [V(0^+) - V(\infty)]e^{-t/RC} + V(\infty)$$

$$V_o(t) = [V_o(0^+) - V_o(\infty)]e^{-t/RC} + V_o(\infty)$$

$$V_o = V_{C_1} + V_{C_2}$$

$$t = 0^+$$

$$V_o(0^+) = V_{C_1}(0^+) + V_{C_2}(0^+) = 24 + 6 = 30$$


$$\text{At } t = \infty$$

$$\text{At } t = \infty$$


$$V_0(\infty) = 2 \times 4 = 8$$

$$V_0(t) = [30 - 8] e^{-3.75t} + 8$$

$$= 8 + 22 e^{-3.75t}$$

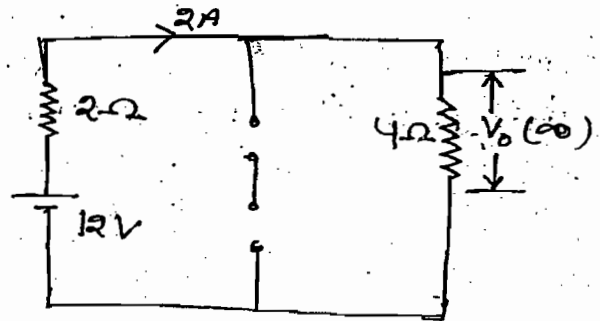


(I)

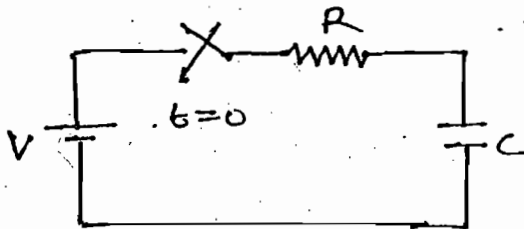


$$\text{At } t = 0^-, V_C = 0$$

$$t = 0^+, V_C = 0$$

$$T = RC$$

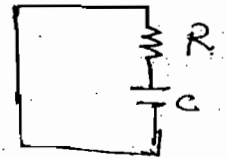


(II)

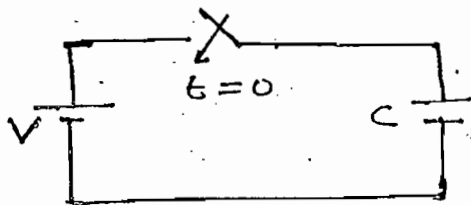


$$t = 0^-, V_C = 0$$

$$t = 0^+, V_C = V$$

$$T = RC = 0$$

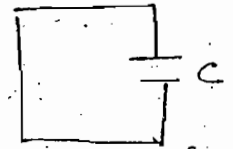


(III)

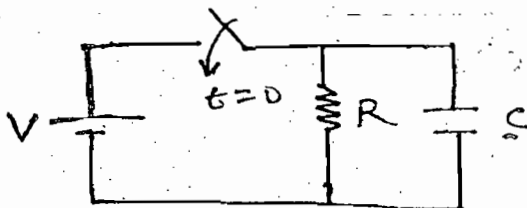

$$t = 0^-, V_C = 0$$


$$t = 0^+, V_C = V$$

$$T = RC = 0$$

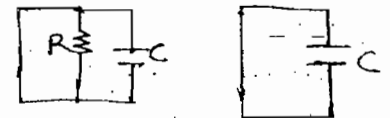

$$T = RC = 0$$


(IV)

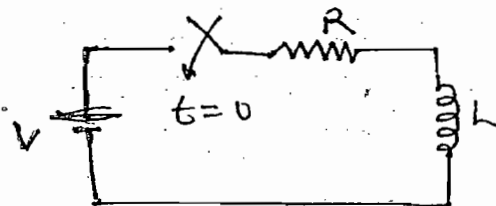


$$t = 0^-, i = 0$$

$$t = 0^+, i = 0$$

$$T = L/R$$

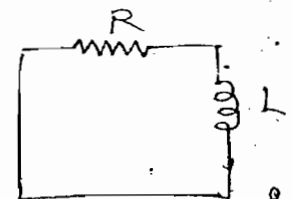

(V)

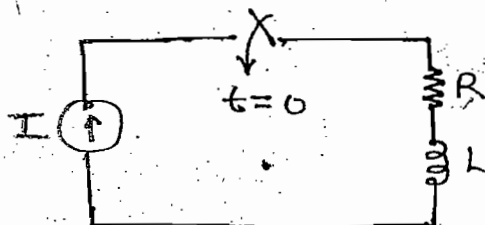


$$t = 0^-, i = 0$$

$$t = 0^+, i = I$$


$$R_{eq} = R_{oc} + R = \infty$$

$$T = \frac{L}{R_{eq}} = 0$$

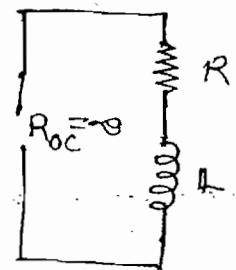

Ques:- Find time constant of the circuit shown

Soln:-


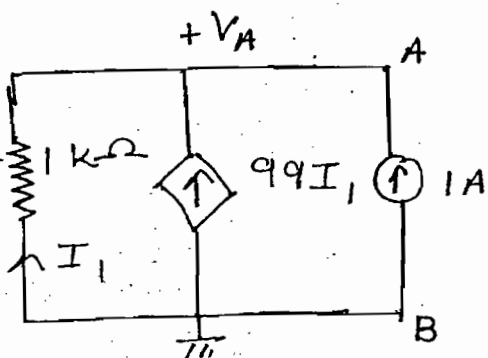


$$\frac{V_A}{1 \times 10^3} = 99I_1 + 1 \quad \text{--- (i)}$$

$$I_1 = -\frac{V_A}{1 \times 10^3} \quad \text{--- (ii)}$$

$$R_{th} = \frac{V_A}{I_S} = \frac{10}{1} = 10 \Omega$$

$$T = \frac{L}{R_{th}} = \frac{4}{10}$$

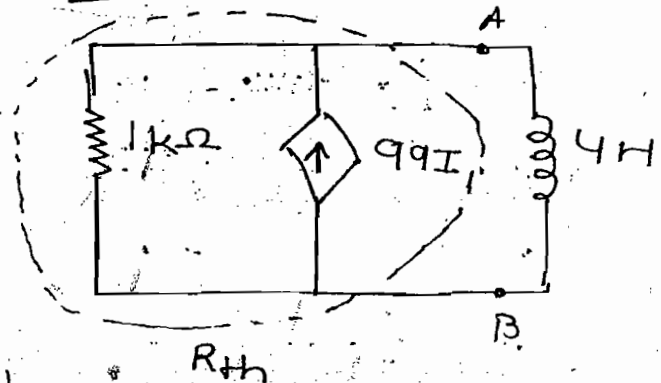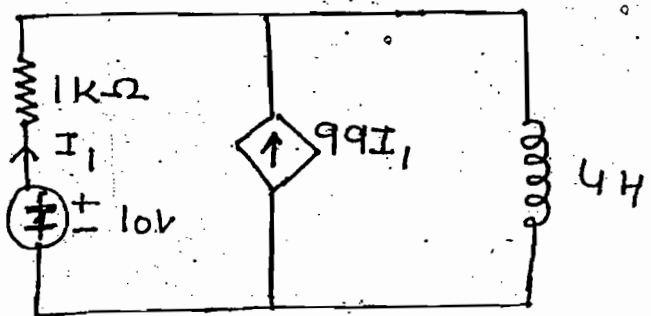

From (i) & (ii)

$$V_A = 10V$$

