

Lecture-13

LC N/w Foster - II form:- (Parallel)

$$Y(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + Hs$$

$\downarrow$
 $B_L = \frac{1}{LS}$

$B_C = SC$



Ques:- obtain foster - I & II from $Z(s)$

$$Z(s) = \frac{(s^2+2)(s^2+4)}{s(s^2+3)}$$

Soln:- Foster - I :-

Pole $\rightarrow \infty \rightarrow HS$
 Pole $\rightarrow \text{origin} \rightarrow k_0/s$
 Pole $\rightarrow \text{conjugate pair} \rightarrow \frac{2ks}{s^2 + \omega^2}$

$$Z(s) = \frac{k_0}{s} + \frac{2ks}{s^2 + \omega^2} + HS$$

$$\frac{(s^2+2)(s^2+4)}{s(s^2+3)} = \frac{k_0}{s} + \frac{2ks}{s^2+3} + HS \quad (\text{Partial Fraction})$$


$$k_0 = \frac{8}{3} \quad 2k \rightarrow \frac{1}{3} \quad H \rightarrow 1$$

$$Z(s) = \frac{8/3}{s} + \frac{s/3}{s^2+3} + s$$

$$\Rightarrow Z(s) = \frac{1}{\frac{3}{8}s} + \frac{1}{\frac{s^2}{\frac{3}{8}} + \frac{3}{\frac{3}{8}}} + s$$

$$\Rightarrow Z(s) = \frac{1}{\frac{3}{8}s} + \frac{1}{\frac{3s+9}{s}} + s$$

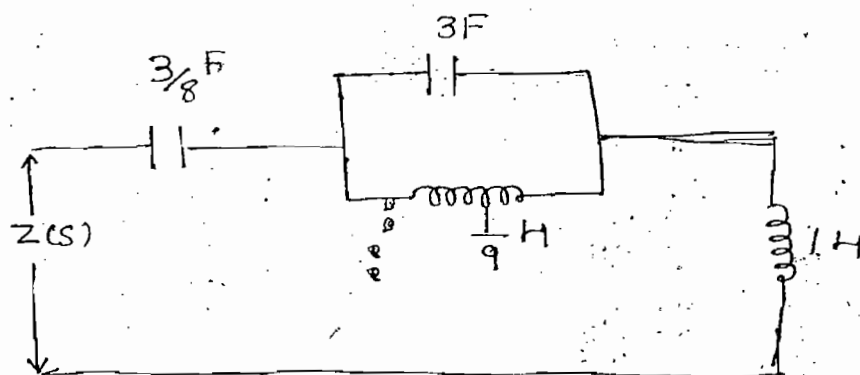$\downarrow \quad \downarrow \quad \downarrow$
 $X_C = \frac{1}{Cs} \quad R_C = s \quad B_L = \frac{1}{sL}$
 $\frac{1}{X_A + Y_B}$



Foster - II :-

Note :- If $F(s)$ is given by using same function - Foster - I and II form are obtained.

$\rightarrow$ If $Z(s)$ is given by using $\frac{1}{Z(s)}$ function Foster-II form is obtained.

$\rightarrow$ If $Y(s)$ is given by using $\frac{1}{Y(s)}$ function Foster-I form is obtained.

$$Y(s) = \frac{s(s^2+3)}{(s^2+2)(s^2+4)}$$

$P \rightarrow \infty$ X

$P \rightarrow \text{origin}$ X

$P \rightarrow \text{conjugate pair}$ ✓

$$Y(s) = \frac{2k_1 s}{s^2 + \omega_1^2} + \frac{2k_2 s}{s^2 + \omega_2^2}$$


$$\frac{s(s^2+3)}{(s^2+2)(s^2+4)} = \frac{2k_1 s}{s^2+2} + \frac{2k_2 s}{s^2+4}$$

$$2k_1 \rightarrow \frac{1}{2} \quad \& \quad 2k_2 \rightarrow \frac{1}{2}$$

$$Y(s) = \frac{s/2}{s^2+2} + \frac{s/2}{s^2+4}$$

$$\Rightarrow Y(s) = \frac{1}{\frac{s^2}{s/2} + \frac{2}{s/2}} + \frac{1}{\frac{s^2}{s/2} + \frac{4}{s/2}}$$
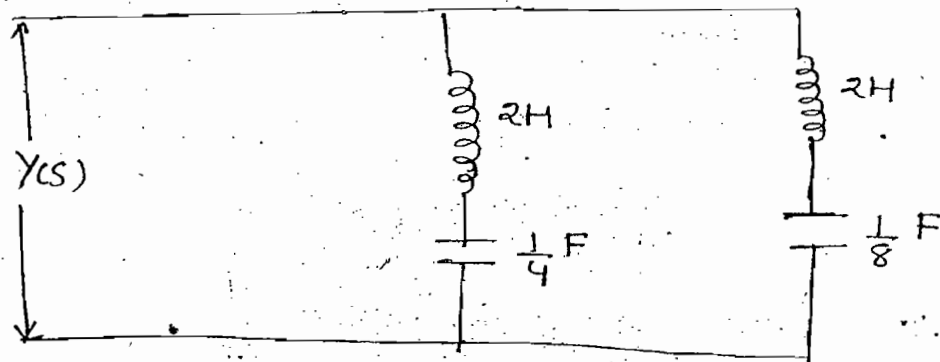
$$\Rightarrow Y(s) = \frac{1}{\left(\begin{array}{c} 2s + \frac{4}{s} \\ x_L = Ls \quad x_C = \frac{1}{Cs} \end{array} \right) \frac{1}{Z_a + Z_b}} + \frac{1}{\left(\begin{array}{c} 2s + \frac{8}{s} \\ x_L \quad x_C \end{array} \right) \frac{1}{Z_c + Z_d}}$$



LC N/w Cauer-I form:-

→ Ladder

(1) Removal of Pole at ∞ :-

$$Z_2(s) = Z(s) - H_1 s \quad (X_L = Ls)$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - H_2 s \quad (B_C = Sc)$$



$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - H_3 s$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - H_4 s$$

$$Y_4(s) = Y_5(s) + H_4 s$$

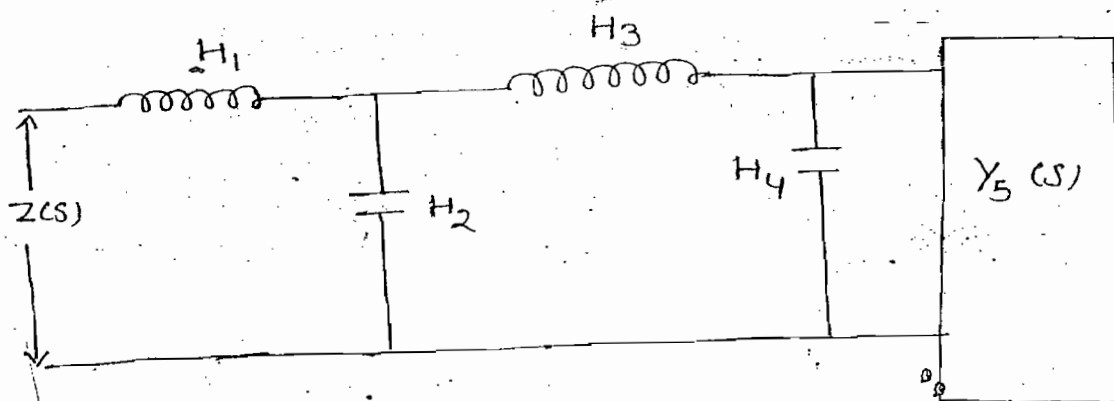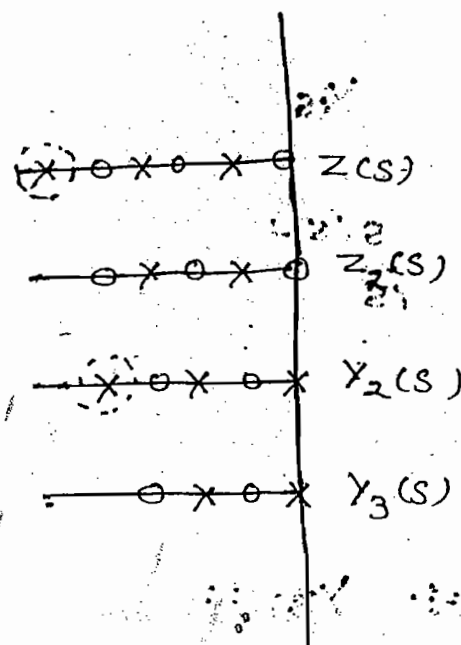

LC N/w Cauer-II form:-

Removal of Pole at origin:-

$$Z_2(s) = Z(s) - \frac{k_{01}}{s}$$


$$Y_2(s) = \frac{1}{Z_2(s)}$$

$$Y_3(s) = Y_2(s) - \frac{k_{02}}{s}$$

$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$(X_C = \frac{1}{Cs})$$

$$(B_L = \frac{1}{Ls})$$

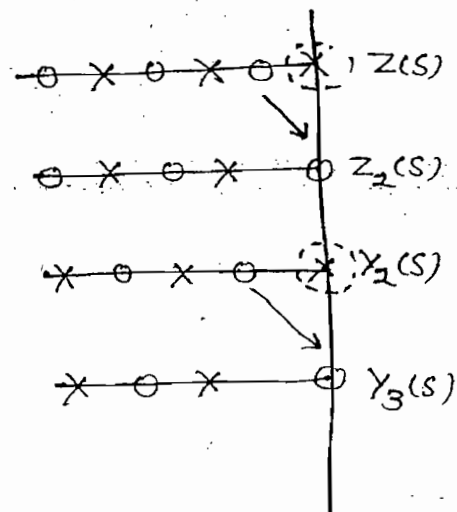


$$Z_4(s) = Z_3(s) - \frac{k_{03}}{s}$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - \frac{k_{04}}{s}$$

$$Y_4(s) = Y_5(s) + \frac{k_{04}}{s}$$

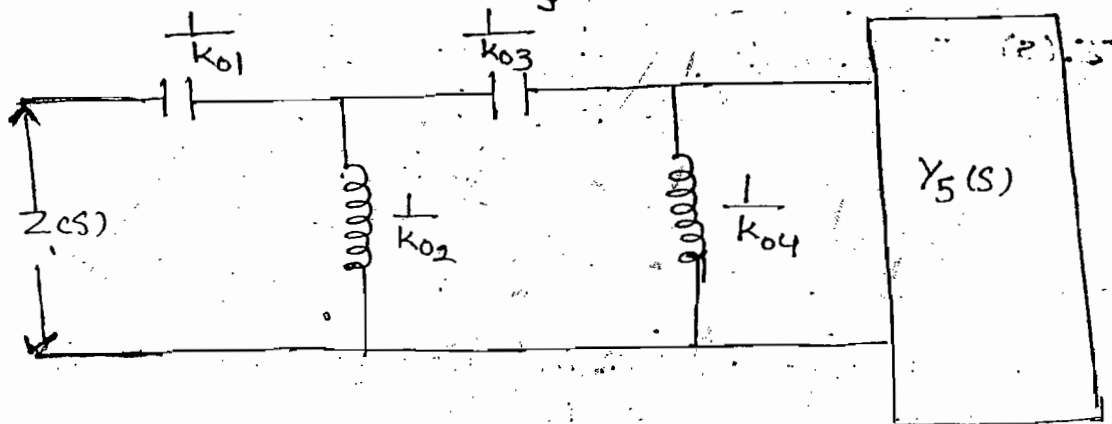

ques:- Obtain Cauer - I and II form

$$Z(s) = \frac{s^3 + 2s}{s^4 + 5s^2 + 4}$$

Soln:-


Cauer - I

Pole at $\infty \rightarrow$ not present

then reciprocal

$$Y(s) = \frac{s^4 + 5s^2 + 4}{s^3 + 2s}$$

$$\begin{aligned} & \frac{s^3 + 2s}{s^4 + 5s^2 + 4} \xrightarrow{\text{Long Division}} \frac{s^3}{s^4 + 5s^2 + 4} \rightarrow B_C = sC \rightarrow Y \\ & \frac{s^3}{s^4 + 5s^2 + 4} \xrightarrow{\text{Long Division}} \frac{s^3}{4s^2 + 4} \rightarrow X_L = \frac{1}{4}s \rightarrow Z \\ & \frac{s^3}{4s^2 + 4} \xrightarrow{\text{Long Division}} \frac{s^3}{4s^2} \rightarrow B_C = \frac{1}{4}sC \rightarrow Y \\ & \frac{s^3}{4s^2} \xrightarrow{\text{Long Division}} \frac{s^3}{4s^2} \rightarrow X_L = \frac{1}{4}s \rightarrow Z \end{aligned}$$

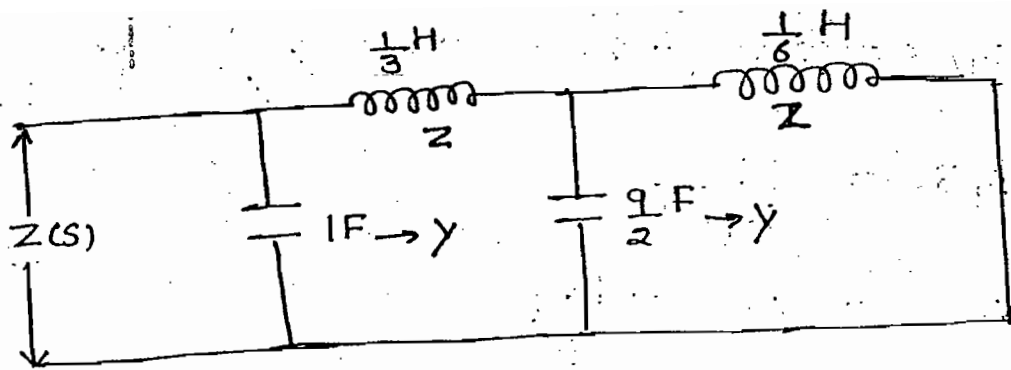

$$Z(s) = s + \frac{1}{\frac{s}{3} + \frac{1}{\frac{9s}{2} + \frac{1}{\frac{s}{6}}}}$$

Cauer - II Form:-

Pole $\rightarrow$ origin not present then take reciprocal

$$Z(s) = \frac{s(s^2+2)}{s^4+5s^2+4}$$

$$Y(s) = \frac{s^4+5s^2+4}{s^3+2s}$$


$$2s+s^3 \overline{) s^4+5s^2+4} \left(\frac{2}{s} \rightarrow B_L = \frac{1}{1s} \right. \\ \left. \frac{2}{s} \rightarrow y \right)$$

$$\frac{2s^2+4}{3s^2+s^4} \overline{) 2s+s^3} \left(\frac{2}{3s} \rightarrow X_C = \frac{1}{3s} \right. \\ \left. \frac{2}{3s} \rightarrow Z \right)$$

$$\frac{s^3}{3} \overline{) 3s^2+s^4} \left(\frac{9}{s} \rightarrow B_L \right. \\ \left. \frac{9}{s} \rightarrow y \right)$$

$$\frac{s^3}{3} \overline{) \frac{s^3}{3}} \left(\frac{1}{3s} \rightarrow X_C \right. \\ \left. \frac{1}{3s} \rightarrow Z \right)$$

X

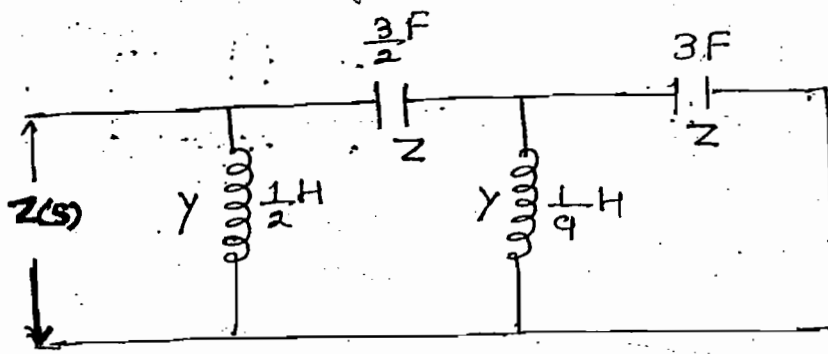

$$Z(s) = \frac{3}{2s} + \frac{1}{\frac{2}{3s} + \frac{1}{\frac{9}{s} + \frac{1}{3s}}}$$

RC N/w Foster-I form:-


$$Z_{RC}(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{2k_i s}{s^2 + \omega_i^2} + Hs$$

$$Z_{RC}(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \sigma_i} + K_\infty$$

$$X_C = \frac{1}{Cs}$$

$$\frac{k}{s + \sigma} = \frac{1}{\frac{s}{k} + \frac{\sigma}{k}} = \frac{1}{X_a + Y_b}$$

$B_C = SC \quad G_1$

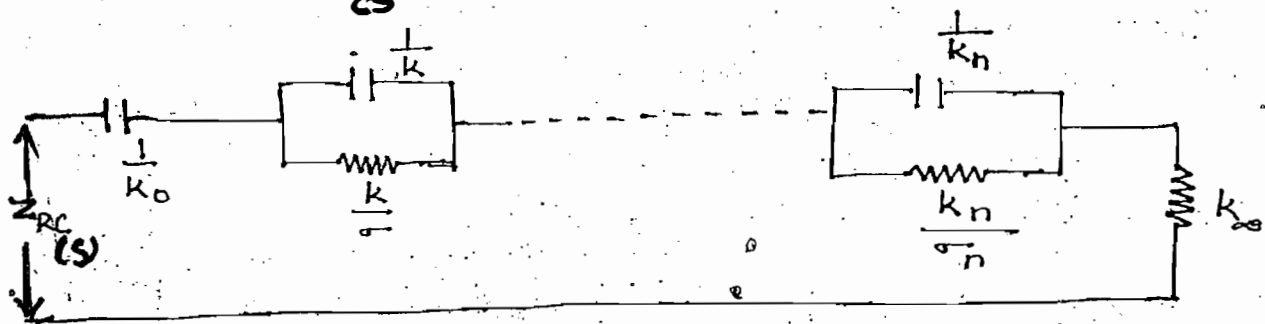


→ Series N/w is obtained

RC N/w Foster-II form:-

$$Z_{RC}(s) = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \sigma_i}$$

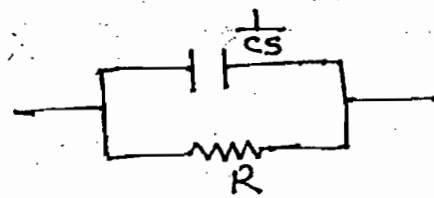
$$\rightarrow Z_{RC}(s) = \frac{R \frac{1}{Cs}}{R + \frac{1}{Cs}}$$



$$Z_{RC}(s) = \frac{R}{Rcs + 1}$$

$$Z_{RC}(s) = \frac{R}{RC(s + \frac{1}{RC})}$$
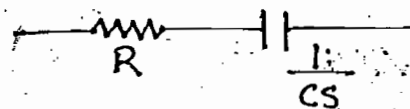
$$\rightarrow Y_{RC}(s) = \frac{1}{R + \frac{1}{Cs}}$$



$$Y_{RC}(s) = \frac{Cs}{Rcs + 1}$$

$$Y_{RC}(s) = \frac{Cs}{RC(s + \frac{1}{RC})}$$



$$\frac{Y_{RC}(s)}{s} = \frac{1}{R(s + \frac{1}{RC})}$$

Note:-

→ Pole-zero pattern of Z_{RC} and $Y_{RC}(s)$ are identical
Thereby both functions can be represented by same mathematical equation.

$$\frac{Y_{RC}(s)}{s} = \frac{k_0}{s} + \sum_{i=1}^n \frac{k_i}{s + \sigma_i} + k_\infty$$
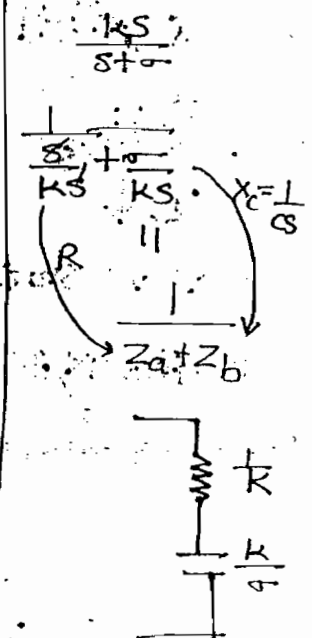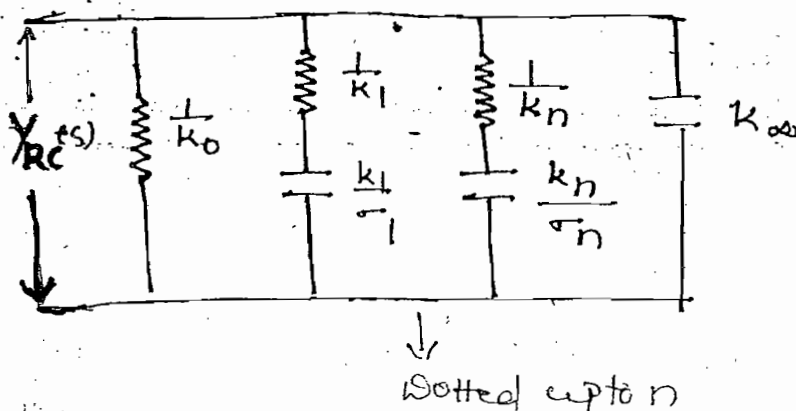
$$Y_{RC}(s) = k_0 + \sum_{i=1}^n \frac{k_i s}{s + \sigma_i} + k_\infty s$$



RC N/w Cauer - I form:-

$$LC \rightarrow Z_2(s) = Z(s) - H_1 s \quad Y_2(s) = \frac{1}{Z_2(s)}$$

($X_L = s$)

$$Y_3(s) = H_2 s$$

RC $\rightarrow$ Step-I:-

Removal of constant from $Z(s)$

$$Z_2(s) = Z(s) - K_1$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

Step-II:-

Removal of Pole at ∞ from $Y(s)$

$$Y_3(s) = Y_2(s) - H_1 s$$


$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - K_2$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - H_2 s$$

$$Y_4(s) = Y_5(s) + H_2 s$$

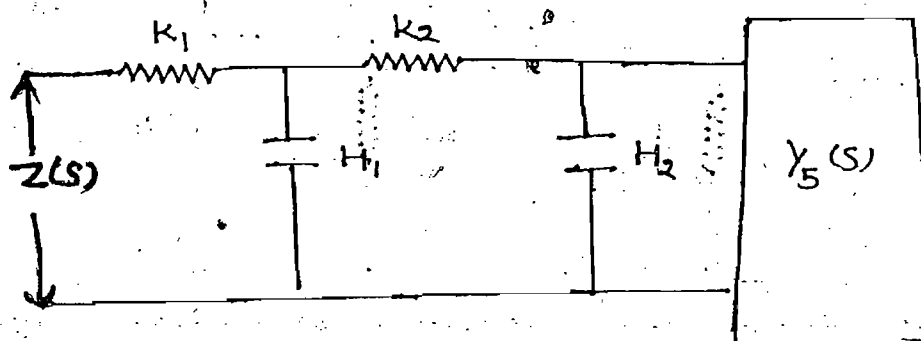

$\rightarrow$ ladder N/w is obtained

Note:-

Step-I and Step-II are alternatively repeated until the total function is realised

RC N/w Cauer-II form:-

$$LC \rightarrow Z_2(s) = Z(s) - \frac{k_{01}}{s} \quad Y_2(s) = \frac{1}{Z_2(s)} \quad Y_3(s) = \frac{k_{02}}{s}$$

$$\left(X_c = \frac{1}{Cs} \right) \quad \left(B_L = \frac{1}{Ls} \right)$$

RC $\rightarrow$ Step-I:-

Removal of pole at origin from $Z(s)$

$$Z_2(s) = Z(s) - \frac{k_{01}}{s}$$

$$Y_2(s) = \frac{1}{Z_2(s)}$$

Step-II:-

Removal of constant from $Y(s)$

$$Y_3(s) = Y_2(s) - k_1$$


$$Z_3(s) = \frac{1}{Y_3(s)}$$

$$Z_4(s) = Z_3(s) - \frac{k_{02}}{s}$$

$$Y_4(s) = \frac{1}{Z_4(s)}$$

$$Y_5(s) = Y_4(s) - k_2$$

$$Y_4(s)' = Y_5(s) + k_2$$

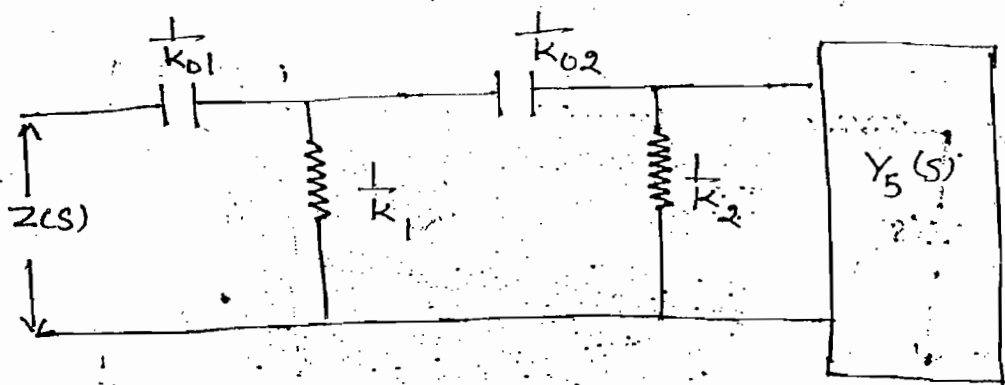

$\rightarrow$ Ladder N/w is obtained.

Note:-

Step-I and II are alternatively repeated until the total function is realised.