

Network Laws and Theorems

2

Ohm's Law

The ratio of potential difference (V) between any two points on a conductor to the current (I) flowing through it is constant, provided the temperature of the conductor does not change.


$$\frac{V}{I} = \text{constant} \quad \text{or} \quad \frac{V}{I} = R$$

Where, R is the resistance of the conductor between the two points considered.

Kirchoff's Laws

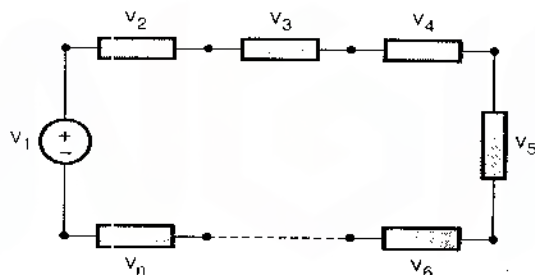1. Kirchoff's Voltage Law (KVL)

For any closed path in a network, the algebraic sum of the voltages is zero.




$$\sum_{k=1}^n v_k(t) = 0 \quad \dots \text{in a closed loop}$$

where, \$v_k\$ is the voltage drop or voltage gain across \$k^{th}\$ element

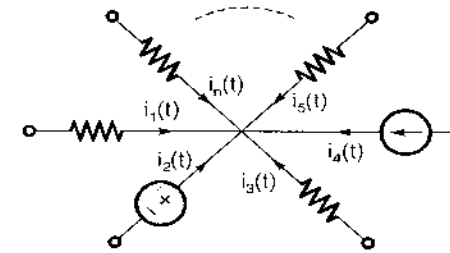2. Kirchoff's Current Law (KCL)

The algebraic sum of the currents at a node is zero. Alternatively the sum of the currents entering a node is equal to the sum of the currents leaving that node.




$$\sum_{k=1}^n i_k(t) = 0 \quad \dots \text{at any node}$$

where \$i_k(t)\$ is the current through \$k^{th}\$ branch


Note:

- A network is an interconnection of elements or devices, whereas a circuit is a network providing one or more closed paths.
 - Number of KVL equations = \$b - (n - 1)\$
 - Number of KCL equations = \$(n - 1)\$
- where, \$b\$ is number of branches and \$n\$ is number of nodes.
- At node, current changes and in branch, current remains same.

Voltage Division Equations

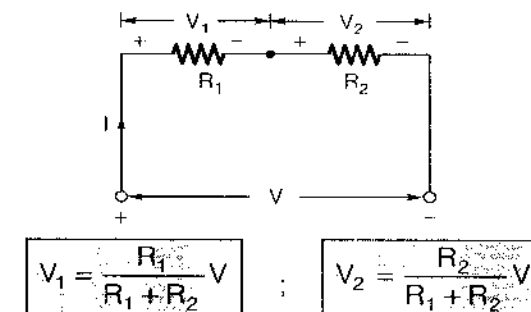


Current Division Equations

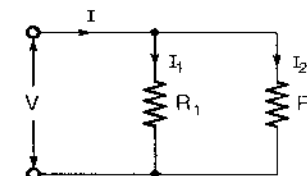

$$I_1 = \frac{R_2 I}{R_1 + R_2} \quad ; \quad I_2 = \frac{R_1 I}{R_1 + R_2}$$

Star to Delta Transformation

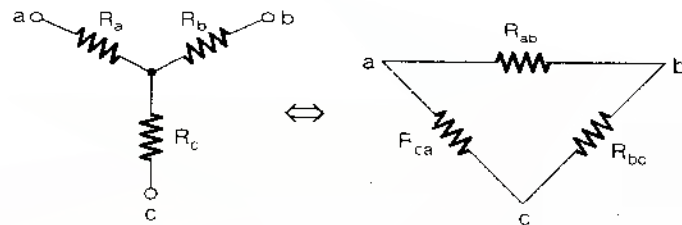

$$R_{ab} = \frac{\Delta}{R_c}, R_{bc} = \frac{\Delta}{R_a}, R_{ca} = \frac{\Delta}{R_b}$$

where, $\Delta = (R_a R_b + R_b R_c + R_c R_a)$

Delta to Star Transformation


$$R_a = \frac{R_{ca} R_{ab}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_b = \frac{R_{ab} R_{bc}}{R_{ab} + R_{bc} + R_{ca}}$$

$$R_c = \frac{R_{bc} R_{ca}}{R_{ab} + R_{bc} + R_{ca}}$$

Source Transformation

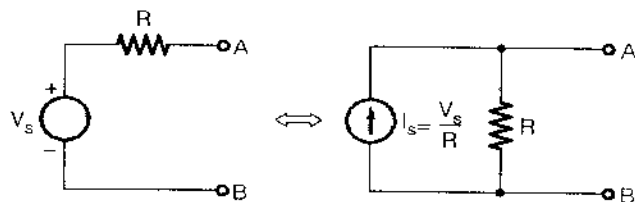Transformation of a resistive voltage source to a resistive current source or vice-versa.



Network Theorems

1. Super Position Theorem

The response in any element of a linear, bilateral RLC network containing more than one independent voltage or current source is the algebraic sum of responses produce by the independent source when each of them acting alone with


- All other independent voltage sources are short circuited (S.C.).
- All other independent current sources are open circuited (O.C.).
- All dependent voltage and current sources remain as they are and therefore, they are neither S.C. nor O.C.

Note:

- The theorem is not applicable to the network containing
 - Non linear elements.
 - Unilateral elements such as diode or BJT.
- The theorem is not applicable to power since it is a non linear parameter.
- The theorem is also applicable for circuit having initial condition.

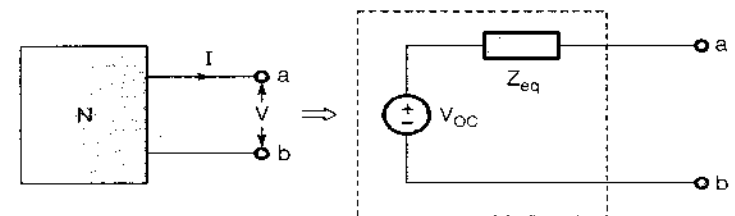2. Thevenin's Theorem

A linear active RLC network which contains one or more independent or dependent voltage or current sources can be replaced by a single voltage source V_{OC} in series with equivalent impedance Z_{eq} .



where, V_{OC} = Open circuit voltage between a and b (when $I = 0$).

Z_{eq} = Equivalent impedance between a and b, when

- All independent sources are replaced by their internal impedances.
- All dependent voltage and current sources are remain as they are.


Note:

Theorem is not applicable to the network containing:


- Non linear element.
- Unilateral element.

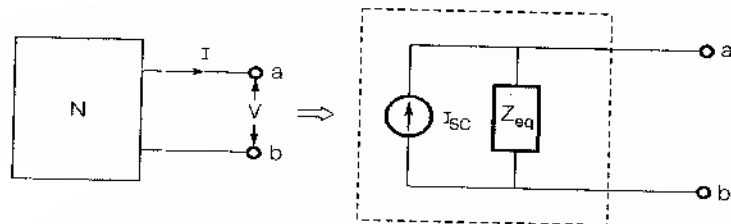3. Norton's Theorem

A linear, active RLC network which contains one or more independent or dependent voltage or current sources can be replaced by a single current source I_{SC} in shunt with equivalent impedance Z_{eq} .



where, I_{SC} = Short circuit current between a and b (when $V = 0$)
 Z_{eq} = Same as that of Thevenin's theorem

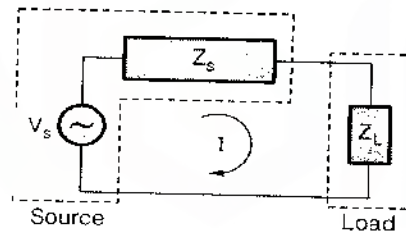4. Maximum Power Transfer Theorem

$Z_L = Z_s^*$ for maximum power transfer

Case 1: If

$$Z_s = R_s + jX_s \text{ and } Z_L = R_L + jX_L$$

then

$$R_L = R_s \text{ and } X_L = -X_s$$

Case 2: If

$$Z_s = R_s + jX_s \text{ and } Z_L = R_L$$

then

$$R_L = \sqrt{R_s^2 + X_s^2}$$

Case 3: If

$$Z_L = R_L \text{ and } Z_s = R_s$$

then

$$R_L = R_s$$

5. Tellegen's Theorem

- In any network, the sum of instantaneous power consumed by various elements of the branches is always equal to zero.
- Total power given out by different voltage sources is equal to total power consumed by various passive elements in various branches of the network.


$$\sum_{k=1}^b v_k \cdot i_k = 0$$

where,

b = Number of branches

Note:

The theorem is valid for any type of network so long as KVL and KCL equations are valid.

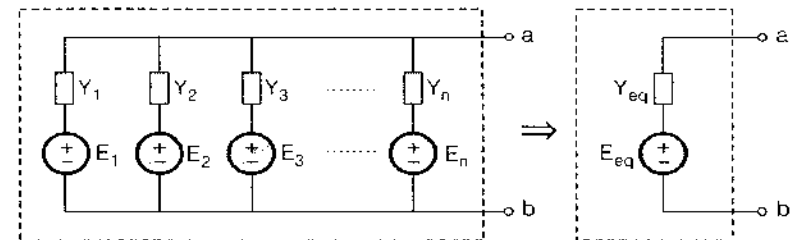
6. Millman's Theorem

$$E_{eq} = \frac{\sum_{i=1}^n E_i Y_i}{\sum_{i=1}^n Y_i}$$

$$Y_{eq} = \sum_{i=1}^n Y_i$$

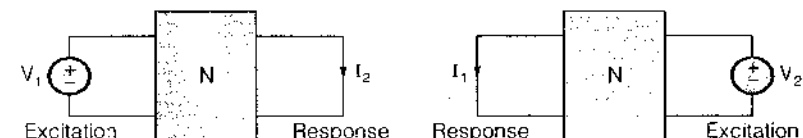7. Reciprocity Theorem

In a linear bilateral single source network, the ratio of excitation to the response is constant when the position of excitation and response are interchange.



$$\frac{V_1}{I_2} = \frac{V_2}{I_1} ; Z_{12} = Z_{21}$$


Note:

- $$\begin{matrix} Z_{12} = Z_{21} \\ Z_{13} = Z_{31} \\ Z_{23} = Z_{32} \end{matrix}$$



 ... for reciprocal network.
- The basis of the theorem is the symmetry of impedance or admittance of matrix.
- The theorem is valid for network in which linear and bilateral elements are present.
- The theorem is valid only when single independent voltage or current source is present.
- The initial conditions are assumed to be zero in reciprocity theorem.

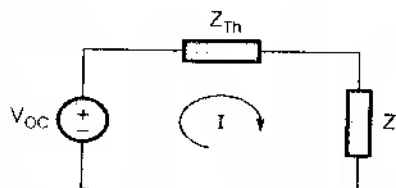8. Compensation Theorem

If impedance ' z ' of any branch of a network is changed by ' δz ', then the incremental current ' δI ' in such branch is that which will be produced by a compensating voltage source $V_c = I \delta z$ introduced in the same branch with polarity opposing the original direction of current I .



(a) Compensation network

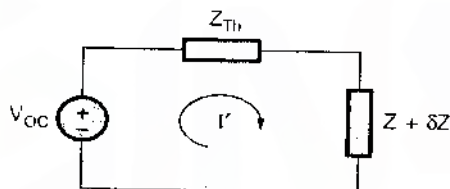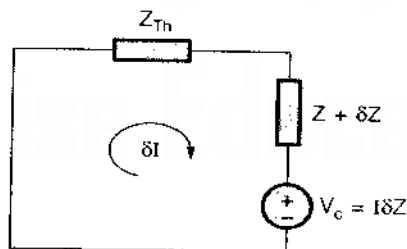(b) Z changes to $Z + \delta Z$ Ideal voltage source V_c connected in series