# 5

### **Semiconductor Memories**



#### Multiple Choice Questions

- Q.1 Which one of the following statements is correct?
  - (a) PROM contains a programmable 'AND' array and a fixed 'OR' array
  - (b) PLA contains a fixed 'AND' array and a programmable 'OR' array
  - (c) PROM contains a fixed 'AND' array and a programmable 'OR' array
  - (d) PLA contains a programmable 'AND' array and a programmable 'NOR' array

[ESE-2004]

- Q.2 A ROM is to be used to implement a "squarer", which outputs the square of a 4-bit number. What must be the size of the ROM?
  - (a) 16 address lines and 16 data lines
  - (b) 4 address lines and 8 data lines
  - (c) 8 address lines and 8 data lines
  - (d) 4 address lines and 16 data lines

[ESE-2004]

- Q.3 A single ROM is used to design a combinational circuit described by a truth table. What is the number of address lines in the ROM?
  - (a) Number of input variables in the truth table
  - (b) Number of output variables in the truth table
  - (c) Number of input plus output variables in the truth table
  - (d) Number of lines in the truth table

[ESE-2006]

- Q.4 How may address inputs, data outputs are required for a 16k × 12 memory
  - (a) 12,12
- (b) 16,12
- (c) 14,12
- (d) 16,16
- Q.5 Consider the following statements for a DRAM:
  - 1. Bit is stored as a charge.
  - 2. It is made of MOS transistors.
  - 3. Speed of DRAM is faster than processors.
  - 4. Each memory cell requires six transistors. Which of these statements are correct?
  - (a) 1 and 2 only
- (b) 2 and 3 only
- (c) 3 and 4 only
- (d) 1, 2, 3 and 4




## Numerical Data Type Questions

- Q.6 A semiconductor RAM has a 12 bit address register and an 8 bit data register. The total number of bits in the memory is \_\_\_\_\_.
- Q.7 It is desired to have  $64 \times 8$  memory and if only  $16 \times 4$  size chips are available then number of chips required are \_\_\_\_\_.
- Q.8 The minimum number of MOS transistors required to make a dynamic RAM cell are \_\_\_\_\_.
- Q.9 The minimum number of MOS transistors required to make a static RAM cell are \_\_\_\_\_.



#### Try Yourself

T1. Consider the ROM shown below.

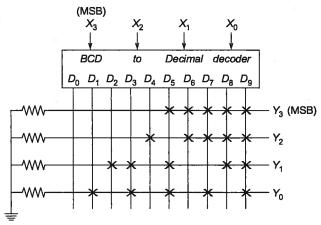

If the coding scheme for  $X_3\,X_2\,X_1\,X_0$  is BCD then find coding scheme for  $Y_3\,Y_2\,Y_1\,Y_0$  .

意 泰 尊 着

**T2.** Impliment the following logical expression using ROM circuit.

$$Y_3(A, B, C) = \Sigma m(1, 2, 4, 7)$$

$$Y_2(A, B, C) = \Sigma m(1, 3, 5, 6)$$

$$Y_1(A, B, C) = \Sigma m(0, 2, 3, 4, 7)$$

$$Y_0(A, B, C) = \Sigma m(3, 5, 6, 7)$$

T3. Implement BCD to excess - 3 convertor.