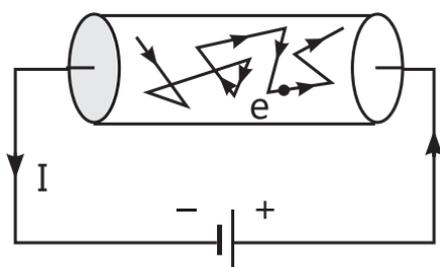


Current Electricity

Case Study Based Questions

Case Study 1

Metals have a large number of free electrons nearly 10^{28} per cubic metre. In the absence of electric field, average terminal speed of the electrons in random motion at room temperature is of the order of 10^5 m s^{-1} . When a potential difference V is applied across the two ends of a given conductor, the free electrons in the conductor experience a force and are accelerated towards the positive end of the conductor. On their way, they suffer frequent collisions with the ions/atoms of the conductor and lose their gained kinetic energy. After each collision, the free electrons are again accelerated due to electric field, towards the positive end of the conductor and lose their gained kinetic energy in the next collision with the ions/atoms of the conductor. The average speed of the free electrons with which they drift towards the positive end of the conductor under the effect of applied electric field is called drift speed of the electrons.



Read the given passage carefully and give the answer of the following questions:

Q1. Magnitude of drift velocity per unit electric field is:

- a. current density
- b. current
- c. resistivity
- d. mobility

Q2. The drift velocity of the electrons depends on:

- a. dimensions of the conductor
- b. number density of free electrons in the conductor
- c. Both a. and b.
- d. Neither a. nor b.

Q3. We are able to obtain fairly large currents in a conductor because:

- a. the electron drift speed is usually very large
- b. the number density of free electrons is very high and this can compensate for the low values of the electron drift speed and the very small magnitude of the electron charge
- c. the number density of free electrons as well as the electron drift speeds are very large and these compensate for the very small magnitude of the electron charge
- d. the very small magnitude of the electron charge has to be divided by the still smaller product of the number density and drift speed to get the electric current

Q4. Drift speed of electrons in a conductor is very small i.e., $v_d = 10^{-4} \text{ m s}^{-1}$. The electric bulb glows immediately when the switch is closed because:

- a. drift velocity of electron increases when switch is closed
- b. electrons are accelerated towards the negative end of the conductor
- c. the drifting of electrons takes place at the entire length of the conductor
- d. the electrons of conductor move towards the positive end and protons of conductor move towards negative end of the conductor

Q5. The number density of free electrons in a copper conductor is $8.5 \times 10^{28} \text{ m}^{-3}$. How long does an electron take to drift from one end of a wire 3.0 m long to its other end? The area of cross-section of the wire is $2.0 \times 10^{-6} \text{ m}^2$ and it is carrying a current of 3.0 A.

- a. $8.1 \times 10^4 \text{ s}$
- b. $2.7 \times 10^4 \text{ s}$
- c. $9 \times 10^3 \text{ s}$
- d. $3 \times 10^3 \text{ s}$

Solutions

1. (d) mobility

Mobility is defined as the magnitude of drift velocity per unit electric field.

$$\text{Mobility, } \mu = \frac{|v_d|}{E}$$

2. (c) Both a. and b.

Drift velocity, $v_d = \frac{I}{neA}$

Here, the symbols have their usual meanings.

3. (b) the number density of free electrons is very high and this can compensate for the low values of the electron drift speed and the very small magnitude of the electron charge

$$I = neAv_d$$

v_d is of order of few m s^{-1} , $e = 1.6 \times 10^{-19} \text{C}$

A is of the order of mm^2 , so a large I is due to a large value of n in conductors.

4. (c) the drifting of electrons takes place at the entire length of the conductor.

When we close the circuit, an electric field is established instantly with the speed of electromagnetic wave which causes electrons to drift at every portion of the circuit due to which the current is set up in the entire circuit instantly. The current which is set up does not wait for electrons to flow from one end of the conductor to another.

Thus, the electric bulb glows immediately when switch is closed.

5. (b) $2.7 \times 10^4 \text{ s}$

Here, number density of free electrons,

$$n = 8.5 \times 10^{28} \text{ m}^{-3}$$

Area of cross-section of a wire, $A = 2.0 \times 10^{-6} \text{ m}^2$

Length of wire, $l = 3.0$, Current, $I = 3.0 \text{ A}$

Then drift velocity of an electron is

$$v_d = \frac{I}{neA} \quad \dots(1)$$

Then time taken by the electron to drift from one end to other end of the wire is

$$t = \frac{l}{v_d} = \frac{lneA}{I} \quad \text{[Using eq. (1)]}$$

$$= \frac{(3.0 \text{ m})(8.5 \times 10^{28} \text{ m}^{-3})(1.6 \times 10^{-19} \text{ C})(2.0 \times 10^{-6} \text{ m}^2)}{(3.0 \text{ A})}$$

$$= 2.7 \times 10^4 \text{ s}$$

Case Study 2

According to Ohm's law, the current flowing through a conductor is directly proportional to the potential difference across the ends of the conductor *i.e.*, $I \propto V \Rightarrow \frac{V}{I} = R$, where R is

resistance of the conductor.

Electrical resistance of a conductor is the obstruction possessed by the conductor to the flow of electric current through it. It depends upon length, area of cross-section, nature of material and temperature of the conductor. We can write,

$R \propto \frac{l}{A}$ or $R = \rho \frac{l}{A}$, where ρ is electrical resistivity

of the material of the conductor.

Read the given passage carefully and give the answer of the following questions:

Q 1. Dimensions of electric resistance is:

- a. $[ML^2T^{-2}A^{-2}]$
- b. $[ML^2T^{-3}A^{-2}]$
- c. $[M^{-1}L^{-2}T^{-1}A]$
- d. $[M^{-1}L^2T^2A^{-2}]$

Q 2. If $1\mu A$ current flows through a conductor when potential difference of 2V is applied across its ends, then the resistance of the conductor is:

- a. $2 \times 10^6 \Omega$
- b. $3 \times 10^6 \Omega$
- c. $1.5 \times 10^5 \Omega$
- d. $5 \times 10^7 \Omega$

Q 3. Specific resistance of a wire depends upon:

- a. length
- b. cross-sectional area
- c. mass
- d. None of these

Q 4. The slope of the graph between potential difference and current through a conductor is:

- a. a straight line
- b. curve
- c. first curve then straight line
- d. first straight line then curve

Q 5. The resistivity of the material of a wire 1.0 m long, 0.4 mm in diameter and having a resistance of 2.0Ω is:

- a. $1.57 \times 10^{-6} \Omega m$
- b. $5.25 \times 10^{-7} \Omega m$
- c. $7.12 \times 10^{-5} \Omega m$
- d. $2.55 \times 10^{-7} \Omega m$

Solutions

1. (b) $[ML^2T^{-3}A^{-2}]$

2. (a) $2 \times 10^6 \Omega$

$$R = \frac{V}{I} = \frac{2}{10^{-6}} = 2 \times 10^6 \Omega$$

3. (d) None of these

Specific resistance depends upon the nature of material and does not depend on mass and length and cross-sectional area of conductor.

4. (a) a straight line

5. (d) $2.55 \times 10^{-7} \Omega m$

$$l = 1.0 \text{ m}; D = 0.4 \text{ mm} = 4 \times 10^{-4} \text{ m}$$

$$R = 2\Omega$$

$$A = \frac{\pi D^2}{4} = \frac{\pi(4 \times 10^{-4})^2}{4}$$

$$= 4\pi \times 10^{-8} \text{ m}^2$$

$$\text{Now, } \rho = \frac{RA}{l} = \frac{2 \times 4\pi \times 10^{-8}}{1}$$

$$= 2.55 \times 10^{-7} \Omega m$$

Case Study 3

Kirchhoff's circuit laws are two equalities that deal with the current and potential difference in the lumped element model of electrical circuits. They were first described in 1845 by German physicist Gustav Kirchhoff.

Kirchhoff's Current Law

This law states that, for any node in an electrical circuit, the sum of currents flowing into that node is equal to the sum of currents flowing out of that node.

Kirchhoff's Voltage Law

The directed sum of the potential differences (voltages) around any closed loop is zero.

Read the given passage carefully and give the answer of the following questions:

Q 1. Kirchhoff's current law is conservation of:

- a. charge
- b. energy
- c. potential
- d. momentum

Q 2. Kirchhoff's current law can be written as:

- a. $\Sigma V = 0$
- b. $\Sigma I = 0$
- c. $\Sigma R = 0$
- d. $\Sigma q = 0$


Q 3. Kirchhoff's voltage law is the conservation of:

- a. energy
- b. charge
- c. current
- d. momentum

Q 4. Kirchhoff's voltage law is applied over:

- a. closed circuit loop
- b. at a circuit node
- c. across battery
- d. None of these

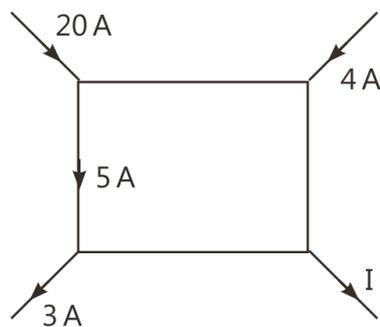Q 5. The value of I in the figure shown is:



- a. 19 A
- b. 21 A
- c. 4 A
- d. 8 A

Solutions

1. (a) charge
2. (b) $\Sigma I = 0$
3. (a) energy
4. (a) closed circuit loop
5. (b) 21 A

Using Kirchhoff's first law,

At junction A :

$$I_1 = 20 - 5 = 15 \text{ A}$$


At junction B:

$$I_3 = I_1 + 4$$

$$\therefore I_3 = 15 + 4 = 19 \text{ A}$$

At junction C :

$$I_2 = 5 - 3 = 2 \text{ A}$$

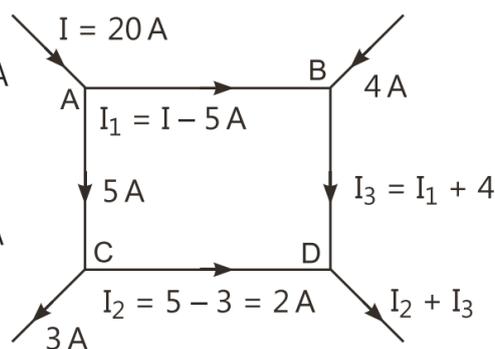


At junction D :

$$\begin{aligned} I &= I_2 + I_3 \\ &= 2\text{A} + 19\text{A} = 21\text{A} \end{aligned}$$

Case Study 4

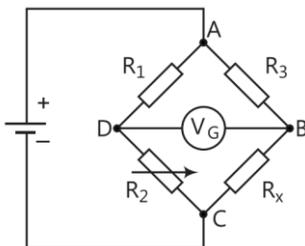A Wheatstone bridge is an electrical circuit used to measure an unknown electrical resistance by balancing two legs of a bridge circuit, one leg of which includes the unknown component. The primary benefit of the circuit is its ability to provide extremely accurate measurements.



The resistance is adjusted until the bridge is 'balanced' and no current flows through the galvanometer. At this point, the voltage between the two mid-points (B and D) will be zero.

Therefore, the ratio of the two resistances in the known leg is equal to the ratio of the two resistances in the unknown leg.

Read the given passage carefully and give the answer of the following questions:

Q1. In balanced Wheatstone bridge:

- a. potential at points B and D remain same
- b. large current flows through the circuit
- c. battery becomes over heated
- d. resistances become small

Q2. Wheatstone bridge is used to measure:

- a. unknown current
- b. unknown voltage
- c. unknown charge
- d. unknown resistance

Q3. Wheatstone bridge is implemented in lab using:

- a. ammeter
- b. voltmeter
- c. meter bridge
- d. potentiometer

Q4. Condition for balanced Wheatstone bridge:

- a. $R_1/R_2 = R_3/R_x$
- b. $R_3 = R_1 \times R_x$
- c. $R_1 = R_3 \times R_x$
- d. None of these

Q5. Wheatstone bridge is analogous to:

- a. cantilever
- b. simple level system
- c. gear train
- d. mechanical clutch

Solutions

1. (a) potential at points B and D remain same

A Wheatstone bridge is said to be balanced if no current flows through V_G .

2. (d) unknown resistance

In a Wheatstone bridge, if the battery and galvanometer are interchanged, then the deflection in galvanometer will not change.

3. (c) meter bridge

Wheatstone bridge is based on the principle of meter bridge.

4. (a) $R_1/R_2 = R_3/R_x$

The ratio of the two resistances in the known leg is equal to the ratio of the two resistances in the unknown leg.


5. (b) simple level system

The best suited option is simple level system.

Case Study 5

Emf of a cell is the maximum potential difference between two electrodes of the cell when no current is drawn from the cell.

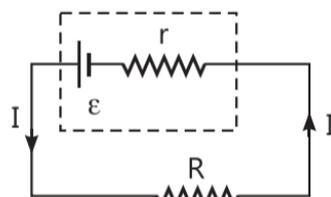Internal resistance is the resistance offered by the electrolyte of a cell when the



electric current flows through it. The internal resistance of a cell depends upon the following factors: (i) distance between the electrodes, (ii) nature and temperature of the electrolyte, (iii) nature of electrodes and (iv) area of electrodes.

For a freshly prepared cell, the value of internal resistance is generally low and goes on increasing as the cell is put to more and more use. The potential difference between the two electrodes of a cell in a closed circuit is called terminal potential difference and its value is always less than the emf of the cell in a closed circuit. It can be written as $V = \varepsilon - Ir$.

Read the given passage carefully and give the answer of the following questions:

- Q 1. A cell of emf E and internal resistance r is connected across a resistance R . If internal resistance is equal to R , what will be the potential difference between the terminals of the cell?**
- Q 2. A cell of emf ε and internal resistance r give a current of 0.5 A with an external resistance of 12Ω and a current of 0.25 A with an external resistance of 25Ω . What is the value of internal resistance of the cell?**
- Q 3. Two batteries of emfs 2 V and 1 V of internal resistances 1Ω and 2Ω respectively are connected in parallel. What is the effective emf of the combination?**

Q 4. An external resistance R is connected to a cell of internal resistance r . At which condition, the maximum current flows in the external resistance?

Q 5. If external resistance connected to a cell has been increased to 5 times, the potential difference across the terminals of the cell increases from 10 V to 30 V. Then what will be the value of the emf of the cell?

Solutions

1. We know that,
$$V = \frac{ER}{R+r}$$

$$= \frac{ER}{R+R} \quad [\because R=r]$$

$$= \frac{ER}{2R} = \frac{E}{2}$$

2. As,
$$I = \frac{\varepsilon}{R+r}$$

In first case, $I = 0.5 \text{ A}$; $R = 12 \Omega$

$$0.5 = \frac{\varepsilon}{12+r} \Rightarrow \varepsilon = 6.0 + 0.5r \quad \dots(1)$$

In second case, $I = 0.25 \text{ A}$; $R = 25 \Omega$

$$\varepsilon = 6.25 + 0.25r \quad \dots(2)$$

From eqs. (1) and (2), $r = 1 \Omega$

3. As, in parallel combination of cells,

$$E_{\text{eff}} = E_{\text{max}} = 2 \text{ V}$$

4. Current in the circuit,
$$I = \frac{\varepsilon}{R+r}$$

Power delivered to the resistance R is

$$P = I^2 R = \frac{\varepsilon^2 R}{(R+r)^2}$$

It is maximum when $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = \varepsilon^2 \left[\frac{(r+R)^2 - 2R(r+R)}{(r+R)^4} \right] = 0$$

or $(r+R)^2 = 2R(r+R)$
or $R = r$

When $R = r$, then maximum current will flow in the external resistance.

5. For first case, $\frac{\varepsilon}{R+r} = \frac{10}{R}$... (1)

For second case, $\frac{\varepsilon}{5R+r} = \frac{30}{5R}$... (2)

Dividing eq. (1) by eq. (2), we get, $r = 5R$

From eq. (1), $\frac{\varepsilon}{R+5R} = \frac{10}{R}$

$$\varepsilon = 60V$$

Solutions for Questions 6 to 15 are Given Below


Case Study 6

Electric Current and Current Density

The flow of charge in a particular direction constitutes the electric current. Current is measured in Ampere. Quantitatively, electric current in a conductor across an area held perpendicular to the direction of flow of charge is defined as the amount of charge is flowing across that area per unit time.

Current density at a point in a conductor is the ratio of the current at that point in the conductor to the area of cross section of the conductor of that point.

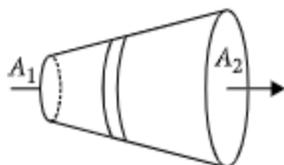The given figure shows a steady current flows in a metallic conductor of non uniform cross section. Current density depends inversely on area, so, here $J_1 > J_2$, as $A_1 < A_2$.



(i) What is the current flowing through a conductor, if one million electrons are crossing in one millisecond through a cross-section of it ?

- (a) 2.5×10^{-10} A (b) 1.6×10^{-10} A
(c) 7.5×10^{-9} A (d) 8.2×10^{-11} A

(ii) SI unit of electric current is


- (a) C s (b) N s^{-2} (c) C s^{-1} (d) $\text{C}^{-1} \text{s}^{-1}$

(iii) A steady current flows in a metallic conductor of non-uniform cross-section. Which of these quantities is constant along the conductor?

- (a) Electric field (b) Drift velocity (c) Current (d) Current density

(iv) A constant current I is flowing along the length of a conductor of variable cross-section as shown in the figure. The quantity which does not depend upon the area of cross-section is

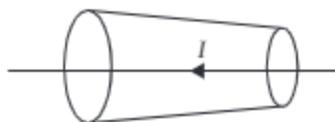- (a) electron density (b) current density
(c) drift velocity (d) electric field



- (v) When a current of 40 A flows through a conductor of area 10 m^2 , then the current density is
 (a) 4 A/m^2 (b) 1 A/m^2 (c) 2 A/m^2 (d) 8 A/m^2

Case Study 7

Factors Affecting Resistance

According to Ohm's law, the current flowing through a conductor is directly proportional to the potential difference across the ends of the conductor *i.e.*, $I \propto V \Rightarrow \frac{V}{I} = R$, where R is resistance of the conductor.

Electrical resistance of a conductor is the obstruction posed by the conductor to the flow of electric current through it. It depends upon length, area of cross-section, nature of material and temperature of the conductor.

We can write, $R \propto \frac{l}{A}$ or $R = \rho \frac{l}{A}$, where ρ is electrical resistivity of the material of the conductor.

- (i) Dimensions of electric resistance is
 (a) $[\text{ML}^2\text{T}^{-2}\text{A}^{-2}]$ (b) $[\text{ML}^2\text{T}^{-3}\text{A}^{-2}]$ (c) $[\text{M}^{-1}\text{L}^{-2}\text{T}^{-1}\text{A}]$ (d) $[\text{M}^{-1}\text{L}^2\text{T}^2\text{A}^{-1}]$
- (ii) If $1 \mu\text{A}$ current flows through a conductor when potential difference of 2 volt is applied across its ends, then the resistance of the conductor is
 (a) $2 \times 10^6 \Omega$ (b) $3 \times 10^5 \Omega$ (c) $1.5 \times 10^5 \Omega$ (d) $5 \times 10^7 \Omega$
- (iii) Specific resistance of a wire depends upon
 (a) length (b) cross-sectional area (c) mass (d) none of these
- (iv) The slope of the graph between potential difference and current through a conductor is
 (a) a straight line (b) curve
 (c) first curve then straight line (d) first straight line then curve
- (v) The resistivity of the material of a wire 1.0 m long, 0.4 mm in diameter and having a resistance of 2.0 ohm is
 (a) $1.57 \times 10^{-6} \Omega \text{ m}$ (b) $5.25 \times 10^{-7} \Omega \text{ m}$ (c) $7.12 \times 10^{-5} \Omega \text{ m}$ (d) $2.55 \times 10^{-7} \Omega \text{ m}$

Case Study 8

Temperature Dependence of Resistivity

The resistance of a conductor at temperature $t^\circ\text{C}$ is given by $R_t = R_0 (1 + \alpha t)$




where R_t is the resistance at $t^\circ\text{C}$, R_0 is the resistance at 0°C and α is the characteristics constants of the material of the conductor.

Over a limited range of temperatures, that is not too large. The resistivity of a metallic conductor is approximately given by $\rho_t = \rho_0(1 + \alpha t)$.

where α is the temperature coefficient of resistivity. Its unit is K^{-1} or $^\circ\text{C}^{-1}$.

For metals, α is positive *i.e.*, resistance increases with rise in temperature.

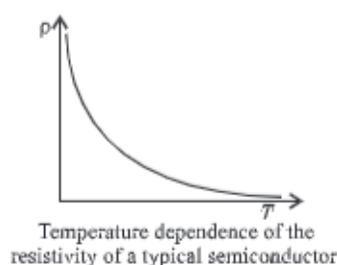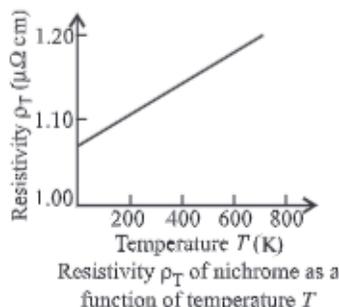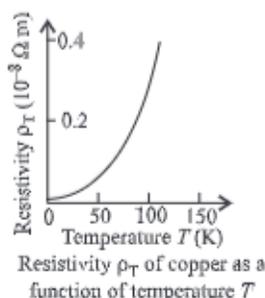For insulators and semiconductors, α is negative *i.e.*, resistance decreases with rise in temperature.




- (i) Fractional increase in resistivity per unit increase in temperature is defined as
 (a) resistivity (b) temperature coefficient of resistivity
 (c) conductivity (d) drift velocity
- (ii) The material whose resistivity is insensitive to temperature is
 (a) silicon (b) copper (c) silver (d) nichrome
- (iii) The temperature coefficient of the resistance of a wire is 0.00125 per °C. At 300 K its resistance is 1 ohm. The resistance of wire will be 2 ohms at
 (a) 1154 K (b) 1100 K (c) 1400 K (d) 1127 K
- (iv) The temperature coefficient of resistance of an alloy used for making resistors is
 (a) small and positive (b) small and negative (c) large and positive (d) large and negative
- (v) For a metallic wire, the ratio V/I (V = applied potential difference and I = current flowing) is
 (a) independent of temperature
 (b) increases as the temperature rises
 (c) decreases as the temperature rises
 (d) increases or decreases as temperature rises depending upon the metal

Case Study 9

Relation between V , ϵ and r of a Cell

Emf of a cell is the maximum potential difference between two electrodes of the cell when no current is drawn from the cell. Internal resistance is the resistance offered by the electrolyte of a cell when the electric current flows through it. The internal resistance of a cell depends upon the following factors; (i) distance between the electrodes (ii) nature and temperature of the electrolyte (iii) nature of electrodes (iv) area of electrodes.

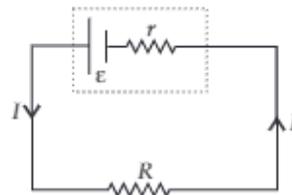For a freshly prepared cell, the value of internal resistance is generally low and goes on increasing as the cell is put to more and more use. The potential difference between the two electrodes of a cell in a closed circuit is called terminal potential difference and its value is always less than the emf of the cell in a closed circuit. It can be written as $V = \epsilon - Ir$.



- (i) The terminal potential difference of two electrodes of a cell is equal to emf of the cell when
 (a) $I \neq 0$ (b) $I = 0$ (c) both (a) and (b) (d) neither (a) nor (b)
- (ii) A cell of emf ϵ and internal resistance r gives a current of 0.5 A with an external resistance of 12Ω and a current of 0.25 A with an external resistance of 25Ω . What is the value of internal resistance of the cell?
 (a) 5Ω (b) 1Ω (c) 7Ω (d) 3Ω
- (iii) Choose the wrong statement.
 (a) Potential difference across the terminals of a cell in a closed circuit is always less than its emf.
 (b) Internal resistance of a cell decrease with the decrease in temperature of the electrolyte.
 (c) Potential difference versus current graph for a cell is a straight line with a -ve slope.
 (d) Terminal potential difference of the cell when it is being charged is given as $V = \epsilon + Ir$.
- (iv) An external resistance R is connected to a cell of internal resistance r , the maximum current flows in the external resistance, when
 (a) $R = r$ (b) $R < r$ (c) $R > r$ (d) $R = 1/r$


(v) If external resistance connected to a cell has been increased to 5 times, the potential difference across the terminals of the cell increases from 10 V to 30 V. Then, the emf of the cell is

- (a) 30 V (b) 60 V (c) 50 V (d) 40 V

Case Study 10

Mechanism of Current Flow in a Conductor

Metals have a large number of free electrons nearly 10^{28} per cubic metre. In the absence of electric field, average terminal speed of the electrons in random motion at room temperature is of the order of 10^5 m s^{-1} . When a potential difference V is applied across the two ends of a given conductor, the free electrons in the conductor experiences a force and are accelerated towards the positive end of the conductor. On their way, they suffer frequent collisions with the ions/atoms of the conductor and lose their gained kinetic energy. After each collision, the free electrons are again accelerated due to electric field, towards the positive end of the conductor and lose their gained kinetic energy in the next collision with the ions/atoms of the conductor. The average speed of the free electrons with which they drift towards the positive end of the conductor under the effect of applied electric field is called drift speed of the electrons.

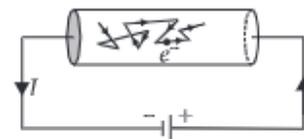

- (i) Magnitude of drift velocity per unit electric field is
- (a) current density (b) current (c) resistivity (d) mobility
- (ii) The drift speed of the electrons depends on
- (a) dimensions of the conductor
(b) number density of free electrons in the conductor
(c) both (a) and (b)
(d) neither (a) nor (b)
- (iii) We are able to obtain fairly large currents in a conductor because
- (a) the electron drift speed is usually very large
(b) the number density of free electrons is very high and this can compensate for the low values of the electron drift speed and the very small magnitude of the electron charge
(c) the number density of free electrons as well as the electron drift speeds are very large and these compensate for the very small magnitude of the electron charge
(d) the very small magnitude of the electron charge has to be divided by the still smaller product of the number density and drift speed to get the electric current.
- (iv) Drift speed of electrons in a conductor is very small *i.e.*, $v = 10^{-4} \text{ m s}^{-1}$. The Electric bulb glows immediately. When the switch is closed because
- (a) drift velocity of electron increases when switch is closed
(b) electrons are accelerated towards the negative end of the conductor
(c) the drifting of electrons takes place at the entire length of the conductor
(d) the electrons of conductor move towards the positive end and protons of conductor move towards negative end of the conductor.
- (v) The number density of free electrons in a copper conductor is $8.5 \times 10^{28} \text{ m}^{-3}$. How long does an electron take to drift from one end of a wire 3.0 m long to its other end? The area of cross-section of the wire is $2.0 \times 10^{-6} \text{ m}^2$ and it is carrying a current of 3.0 A.
- (a) $8.1 \times 10^4 \text{ s}$ (b) $2.7 \times 10^4 \text{ s}$ (c) $9 \times 10^3 \text{ s}$ (d) $3 \times 10^3 \text{ s}$


Case Study 11

Grouping of Cells

A single cell provides a feeble current. In order to get a higher current in a circuit, we often use a combination of cells. A combination of cells is called a battery. Cells can be joined in series, parallel or in a mixed way.

Two cells are said to be connected in series when negative terminal of one cell is connected to positive terminal of the other cell and so on. Two cells are said to be connected in parallel if positive terminal of each cell is connected to one point and negative terminal of each cell connected to the other point. In mixed

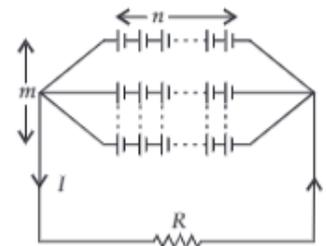grouping of cells, a certain number of identical cells are joined in series, and all such rows are then connected in parallel with each other.



- (i) To draw the maximum current from a combination of cells, how should the cells be grouped?
- Parallel
 - Series
 - Mixed grouping
 - Depends upon the relative values of internal and external resistances
- (ii) The total emf of the cells when n identical cells each of emf ϵ are connected in parallel is
- $n\epsilon$
 - $n^2\epsilon$
 - ϵ
 - $\frac{\epsilon}{n}$
- (iii) 4 cells each of emf 2 V and internal resistance of 1Ω are connected in parallel to a load resistor of 2Ω . Then the current through the load resistor is
- 2 A
 - 1.5 A
 - 1 A
 - 0.888 A
- (iv) If two cells out of n number of cells each of internal resistance ' r ' are wrongly connected in series, then total resistance of the cell is
- $2nr$
 - $nr - 4r$
 - nr
 - r
- (v) Two identical non-ideal batteries are connected in parallel. Consider the following statements.
- The equivalent emf is smaller than either of the two emfs.
 - The equivalent internal resistance is smaller than either of the two internal resistances.
- Both (i) and (ii) are correct.
 - (i) is correct but (ii) is wrong.
 - (ii) is correct but (i) is wrong.
 - Both (i) and (ii) are wrong.


Case Study 12

Kirchhoff's Rules

In 1942, a German physicist Kirchhoff extended Ohm's law to complicated circuits and gave two laws, which enable us to determine current in any part of such a circuit.

According to Kirchhoff's first rule, the algebraic sum of the currents meeting at a junction in a closed electric circuit is zero. The current flowing in a conductor towards the junction is taken as positive and the current flowing away from the junction is taken as negative.

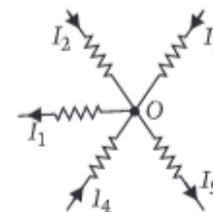According to Kirchhoff's second rule, in a closed loop, the algebraic sum of the emf's and algebraic sum of the products of current and resistance in the various arms of the loop is zero. While traversing a loop, if negative pole of the cell is encountered first, then its emf is negative, otherwise positive.




- (iii) When a metal conductor connected to left gap of a meter bridge is heated, the balancing point
 (a) shifts towards right (b) shifts towards left (c) remains unchanged (d) remains at zero.
- (iv) The percentage error in measuring resistance with a meter bridge can be minimized by adjusting the balancing point close to
 (a) 0 (b) 20 cm (c) 50 cm (d) 80 cm
- (v) In a meter bridge experiment, the ratio of left gap resistance to right gap resistance is 2 : 3. The balance point from left is
 (a) 20 cm (b) 50 cm (c) 40 cm (d) 60 cm

Case Study 14

Potentiometer : An Ideal Voltmeter

Potentiometer is an apparatus used for measuring the emf of a cell or potential difference between two points in an electrical circuit accurately. It is also used to determine the internal resistance of a primary cell. The potentiometer is based on the principle that, if V is the potential difference across any portion of the wire of length l and resistance R , then $V \propto l$ or $V = kl$ where k is the potential gradient. Thus, potential difference across any portion of potentiometer wire is directly proportional to length of the wire of that portion. The potentiometer wire must be uniform. The resistance of potentiometer wire should be high.

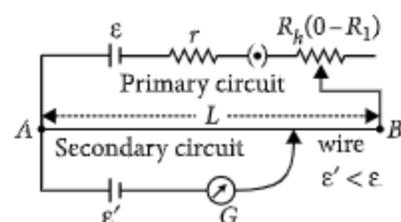


- (i) Which one of the following is true about potentiometer?
 (a) Its sensitivity is low.
 (b) It measures the emf of a cell very accurately.
 (c) It is based on deflection method.
- (ii) A current of 1.0 mA is flowing through a potentiometer wire of length 4 cm and of resistance 4 Ω. The potential gradient of the potentiometer wire is
 (a) 10^{-3} V m^{-1} (b) 10^{-5} V m^{-2} (c) $2 \times 10^{-3} \text{ V m}^{-1}$ (d) $4 \times 10^{-3} \text{ V m}^{-1}$
- (iii) Sensitivity of a potentiometer can be increased by
 (a) decreasing potential gradient along the wire (b) increasing potential gradient along the wire
 (c) decreasing current through the wire (d) increasing current through the wire
- (iv) A potentiometer is an accurate and versatile device to make electrical measurements of EMF because the method involves
 (a) potential gradients
 (b) a condition of no current flow through the galvanometer
 (c) a combination of cells, galvanometer and resistances
 (d) cells
- (v) In a potentiometer experiment, the balancing length is 8 m, when the two cells E_1 and E_2 are joined in series. When the two cells are connected in opposition the balancing length is 4 m. The ratio of the e. m. f. of two cells (E_1/E_2) is
 (a) 1 : 2 (b) 2 : 1 (c) 1 : 3 (d) 3 : 1

Case Study 15

Heat produced by Electric Current

Whenever an electric current is passed through a conductor, it becomes hot after some time. The phenomenon of the production of heat in a resistor by the flow of an electric current through it is called heating effect of current or Joule heating. Thus, the electrical energy supplied by the source of emf is converted into heat. In purely resistive circuit, the energy expended by the source entirely appears as heat. But if the circuit has an active element like a motor, then a part of the energy supplied by the source goes to do useful work and the rest appears as heat. Joule's law of heating form the basis of various electrical appliances such as electric bulb, electric furnace, electric press etc.

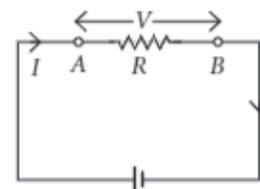

- (i) Which of the following is a correct statement?
- (a) Heat produced in a conductor is independent of the current flowing.
 - (b) Heat produced in a conductor varies inversely as the current flowing.
 - (c) Heat produced in a conductor varies directly as the square of the current flowing.
 - (d) Heat produced in a conductor varies inversely as the square of the current flowing.
- (ii) If the coil of a heater is cut to half, what would happen to heat produced ?
- (a) Doubled
 - (b) Halved
 - (c) Remains same
 - (d) Becomes four times
- (iii) A 25 W and 100 W are joined in series and connected to the mains. Which bulbs will glow brighter ?
- (a) 100 W
 - (b) 25 W
 - (c) both bulbs will glow brighter
 - (d) none will glow brighter
- (iv) A rigid container with thermally insulated wall contains a coil of resistance 100Ω , carrying current 1 A. Change in its internal energy after 5 min will be
- (a) 0 kJ
 - (b) 10 kJ
 - (c) 20 kJ
 - (d) 30 kJ
- (v) The heat emitted by a bulb of 100 W in 1 min is
- (a) 100 J
 - (b) 1000 J
 - (c) 600 J
 - (d) 6000 J

HINTS & EXPLANATIONS

6. (i) (b): $q = 10^6 \times 1.6 \times 10^{-19} \text{ C} = 1.6 \times 10^{-13} \text{ C}$
 $t = 10^{-3} \text{ s}$

$$I = \frac{q}{t} = \frac{1.6 \times 10^{-13}}{10^{-3}} = 1.6 \times 10^{-10} \text{ A}$$

(ii) (c): C s^{-1}

(iii) (c): The current flowing through a conductor of non-uniform cross-section remain same in the whole of the conductor.

(iv) (a): When a constant current is flowing through a conductor of non-uniform cross-section, electron density does not depend upon the area of cross section, while current density, drift velocity and electric field all vary inversely with area of cross-section.

(v) (a): Given, $I = 40 \text{ A}$; $A = 10 \text{ m}^2$

\therefore Current density, $J = \frac{I}{A}$ or $J = \frac{40}{10} = 4 \text{ A/m}^2$

7. (i) (b)

(ii) (a): $R = \frac{V}{I} = \frac{2}{10^{-6}} = 2 \times 10^6 \Omega$

(iii) (d): Specific resistance depends upon the nature of material and is independent of mass and dimensions of the material.

(iv) (a)

(v) (d): $l = 1.0 \text{ m}$; $D = 0.4 \text{ mm} = 4 \times 10^{-4} \text{ m}$
 $R = 2 \Omega$

$$A = \frac{\pi D^2}{4} = \frac{\pi \times (4 \times 10^{-4})^2}{4} = 4\pi \times 10^{-8} \text{ m}^2$$

Now, $\rho = \frac{RA}{l} = \frac{2 \times 4\pi \times 10^{-8}}{1} = 2.55 \times 10^{-7} \Omega \text{ m}$

8. (i) (b): Temperature coefficient of resistivity is defined as the fractional increase in resistivity per unit increase in temperature.

(ii) (d): Nichrome (which is an alloy of nickel, iron and chromium) exhibits a very weak dependence of resistivity with temperature.

(iii) (d): Using, $R_T = R_0(1 + \alpha T)$

$$\therefore \frac{R_{T_2}}{R_{T_1}} = \frac{R_0(1 + \alpha T_2)}{R_0(1 + \alpha T_1)} = \frac{2}{1} = \frac{(1 + \alpha T_2)}{(1 + \alpha \times 300)}$$

$$\Rightarrow 2 + \alpha \times 600 = 1 + \alpha T_2$$

$$\Rightarrow 1 = \alpha (T_2 - 600) \Rightarrow \frac{1}{0.00125} = (T_2 - 600)$$

$$\Rightarrow 800^\circ\text{C} = T_2 - 600$$

$$T_2 = 800 + 273 + 600$$

$$T_2 = 1127 \text{ K}$$

(iv) (a): The temperature coefficient of resistance of an alloy used for making resistors is small and positive.

(v) (b): The resistance of a metallic wire at temperature $t^\circ\text{C}$ is given by

$$R_t = R_0(1 + \alpha t), \text{ where } \alpha \text{ is the temperature coefficient of resistance and } R_0 \text{ is the resistance of a wire at } 0^\circ\text{C}.$$

For metals, α is positive. Hence, resistance of a wire increases with increase in temperature.

Also, from Ohm's law

$$\frac{V}{I} = R$$

Hence on increasing the temperature, the ratio $\frac{V}{I}$ increases.

9. (i) (b)

(ii) (b): As $I = \frac{\epsilon}{R + r}$

In first case, $I = 0.5 \text{ A}$; $R = 12 \Omega$

$$0.5 = \frac{\epsilon}{12 + r} \Rightarrow \epsilon = 6.0 + 0.5r \quad \dots(i)$$

In second case, $I = 0.25 \text{ A}$; $R = 25 \Omega$

$$\epsilon = 6.25 + 0.25r \quad \dots(ii)$$

From equation (i) and (ii), $r = 1 \Omega$

(iii) (b)

(iv) (a): Current in the circuit $I = \frac{E}{R + r}$

Power delivered to the resistance R is

$$P = I^2 R = \frac{E^2 R}{(R + r)^2}$$

It is maximum when $\frac{dP}{dR} = 0$

$$\frac{dP}{dR} = E^2 \left[\frac{(r + R)^2 - 2R(r + R)}{(r + R)^4} \right] = 0$$

or $(r + R)^2 = 2R(r + R)$ or $R = r$

(v) (b): For first case, $\frac{\epsilon}{R + r} = \frac{10}{R} \quad \dots(i)$

For second case, $\frac{\epsilon}{5R+r} = \frac{30}{5R}$... (ii)

Dividing (i) by (ii), we get $r = 5R$

From (i), $\frac{E}{R+5R} = \frac{10}{R}$

$E = 60 \text{ V}$

10. (i) (d): Mobility is defined as the magnitude of drift velocity per unit electric field.

Mobility, $\mu = \frac{|v_d|}{E}$

(ii) (c): Drift velocity, $v_d = \frac{I}{neA}$

where the symbols have their usual meanings.

(iii) (b): $I = neAv_d$

v_d is of order of few m s^{-1} , $e = 1.6 \times 10^{-19} \text{ C}$,

A is of the order of mm^2 , so a large I is due to a large value of n in conductors.

(iv) (c): When we close the circuit, an electric field is established instantly with the speed of electromagnetic wave which causes electrons to drift at every portion of the circuit, due to which the current is set up in the entire circuit instantly. The current which is set up does not wait for electrons to flow from one end of the conductor to another. Thus, the electric bulb glows immediately when switch is closed.

(v) (b): Here,

Number density of free electrons, $n = 8.5 \times 10^{28} \text{ m}^{-3}$

Area of cross-section of a wire, $A = 2.0 \times 10^{-6} \text{ m}^2$

Length of the wire, $l = 3.0 \text{ m}$

Current, $I = 3.0 \text{ A}$

The drift velocity of an electron is

$v_d = \frac{I}{neA}$... (i)

The time taken by the electron to drift from one end to other end of the wire is

$t = \frac{l}{v_d} = \frac{lneA}{I}$ (Using (i))

$= \frac{(3.0 \text{ m})(8.5 \times 10^{28} \text{ m}^{-3})(1.6 \times 10^{-19} \text{ C})(2.0 \times 10^{-6} \text{ m}^2)}{(3.0 \text{ A})}$

$= 2.7 \times 10^4 \text{ s}$

11. (i) (d)

(ii) (c): For parallel combination of n cells, $\epsilon_{eq} = \epsilon$.


(iii) (d): $I = \frac{mE}{mR+r}$, $m = \text{number of cells} = 4$

$E = 2 \text{ V}$, $R = 2 \Omega$, $r = 1 \Omega$

$I = \frac{8}{8+1} = \frac{8}{9} = 0.888 \text{ A}$

(iv) (b)

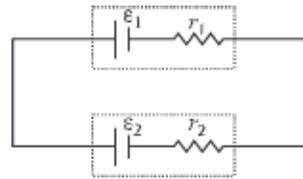(v) (c): Let two cells of emf's ϵ_1 and ϵ_2 and of internal resistance r_1 and r_2 respectively are connected in parallel.



The equivalent emf is given by

$\epsilon_{eq} = \frac{\epsilon_1 r_2 + \epsilon_2 r_1}{r_1 + r_2}$... (i)

The equivalent internal resistance is given by

$\frac{1}{r_{eq}} = \frac{1}{r_1} + \frac{1}{r_2}$ or $r_{eq} = \frac{r_1 r_2}{r_1 + r_2}$... (ii)

Let us consider, two cells connected in parallel of same emf ϵ and same internal resistance r .


From equation (i), we get $\epsilon_{eq} = \frac{\epsilon r + \epsilon r}{r + r} = \epsilon$

From equation (ii), we get

$r_{eq} = \frac{r^2}{r + r} = \frac{r}{2}$

12. (i) (a): Kirchhoff's Ist law is based on law of conservation of charge whereas Kirchhoff's IInd law is based on law of conservation of energy.

(ii) (c):

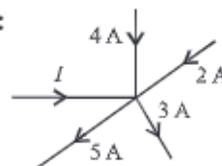


According to Kirchhoff's junction law

$(+I) + (+4 \text{ A}) + (+2 \text{ A}) + (-5 \text{ A}) + (-3 \text{ A}) = 0$
 $I + 6 \text{ A} - 8 \text{ A} = 0$ or $I = 2 \text{ A}$

(iii) (c)

(iv) (d)

(v) (b):

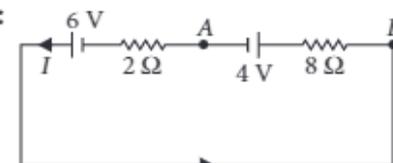

Apply KVL in the given circuit,

$6 - 8I - 4 - 2I = 0$

or, $2 - 10I = 0$, or, $I = 2/10 = 0.2 \text{ A}$

$V_{AB} = 4 + I \times 8 = 4 + 0.2 \times 8 = 5.6 \text{ V}$


13. (i) (b): $(S + x) = \frac{Q}{P} R$

$$x = \frac{Q}{P} R - S = \frac{6}{5} \times 10 - 5 = 7 \Omega$$

(ii) (a): A Wheatstone bridge consisting of four arms of resistance P, Q, R, S is most sensitive when all the resistances are equal.

(iii) (a): When metal wire is heated, its resistance increases. R_1 increases, l_1 increases.

The null point shift to the right.

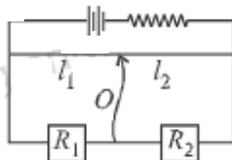

(iv) (c): The percentage error in measuring resistance with a metre bridge can be minimized by adjusting the balancing point near the middle of the bridge *i.e.* close to 50 cm.

$$(v) (c): \frac{P}{Q} = \frac{l_1}{100 - l_1} \text{ or } \frac{2}{3} = \frac{l_1}{100 - l_1}$$

$$\text{or } 5l_1 = 200 \text{ or } l_1 = 40 \text{ cm}$$

14. (i) (b)

(ii) (a): Given, $I = 1.0 \text{ mA} = 10^{-3} \text{ A}$; $R = 4 \Omega$; $L = 4 \text{ m}$
Potential drop across potentiometer wire,

$$V = IR = 10^{-3} \times 4 \text{ V}$$

$$\text{Potential gradient, } k = \frac{V}{L} = \frac{4 \times 10^{-3}}{4} \\ = 10^{-3} \text{ V m}^{-1}$$

(iii) (a)

(iv) (b): A potentiometer is an accurate and versatile device to make electrical measurements of EMF because the method involves a condition of no current flow through the galvanometer. It can be used to measure potential difference, internal resistance of a cell and compare EMF's of two sources.

$$(v) (d): \frac{E_1}{E_2} = \frac{l_1 + l_2}{l_1 - l_2} = \frac{8 + 4}{8 - 4} = \frac{12}{4} = \frac{3}{1}$$

15. (i) (c): According to Joule's law of heating,

Heat produced in a conductor, $H = I^2 R t$

where, I = Current flowing through the conductor

R = Resistance of the conductor

t = Time for which current flows through the conductor.

$$\therefore H \propto I^2$$

(ii) (a): If the coil is cut into half, its resistance is also halved.

$$\text{As } H = \frac{V^2}{R} t \quad \therefore H' = 2$$

$$(iii) (b): P = \frac{V^2}{R} \text{ or } R = \frac{V^2}{P}$$

The bulbs are joined in series. Current in both the bulbs will same.

\therefore The heat produced in them is given by $H = I^2 R t$

$$\text{or } H \propto R \Rightarrow H \propto \frac{1}{P}$$

Therefore the bulb with low wattage or high resistance will glow brighter or we can say the 25 W bulb will glow brighter than the 100 W bulb.

(iv) (d): $R = 100 \Omega$; $I = 1 \text{ A}$; $t = 5 \text{ min.} = 5 \times 60 = 300 \text{ s}$
change in internal energy = heat generated in coil
 $= I^2 R t = ((1)^2 \times 100 \times 300) \text{ J}$
 $= 30000 \text{ J} = 30 \text{ kJ}$

(v) (d): Here, $P = 100 \text{ W}$, $t = 1 \text{ min} = 60 \text{ s}$

Heat developed in time t

$$H = P \times t = (100 \text{ W})(60 \text{ s}) = 6000 \text{ J}$$