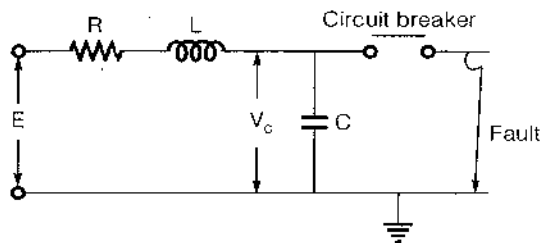


circuit Breakers

12

□ Restriking voltage



$$V = E \left(1 - \cos \frac{1}{\sqrt{LC}} t \right)$$

where, L, C = Inductance and capacitance per phase of the system upto the point of circuit breaker location.

E = System voltage at the instant of arc interruption

V = Restriking voltage

□ The maximum value of restriking voltage = $2 \times E_{\text{peak}}$

where, E_{peak} = Peak value of the system voltage

□ Natural frequency of oscillation

$$f_n = \frac{1}{2\pi} \frac{1}{\sqrt{LC}}$$


□ Rate of rise of restriking voltage (RRRV)

$$\text{RRRV} = \omega_n E \sin \omega_n t$$

□ The maximum value of RRRV = $\omega_n E_{\text{peak}}$

Resistance Switching

□ Frequency of damped oscillation

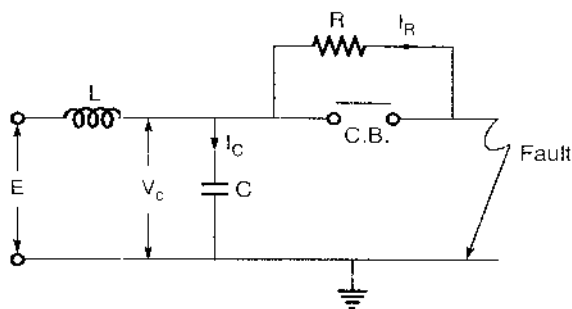


$$f = \frac{1}{2\pi} \sqrt{\frac{1}{LC} - \frac{1}{4R^2C^2}}$$

Note:

If value of the resistance connected across the contacts of circuit breaker, is equal to or less than $\frac{1}{2}\sqrt{\frac{L}{C}}$, then there will be no transient oscillation.

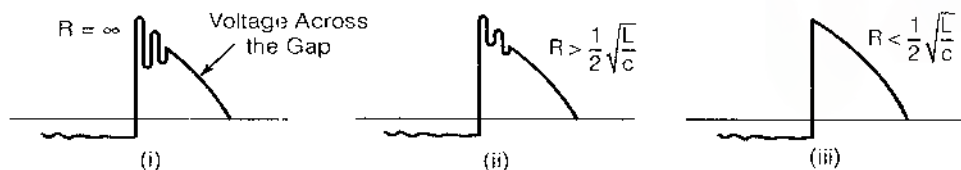Transient Oscillation for Different Values of R



Transient oscillations for different values of R

- If $R > \frac{1}{2}\sqrt{\frac{L}{C}}$. There will be oscillation.
- $R = \frac{1}{2}\sqrt{\frac{L}{C}}$ is known as critical resistance. There will be no oscillation.