

# Chapter 6

## Differential and Feedback Amplifiers


### LEARNING OBJECTIVES

After reading this chapter, you will be able to understand:

- The differential amplifier
- FET differential amplifiers
- Feed back amplifiers
- Power amplifiers
- Amplifier efficiency
- Maximum theoretical efficiency
- Dissipation
- Class 'AB' amplifier
- Class 'C' amplifier
- Resonant frequency
- 555 timer
- Schmitt trigger
- Voltage controlled oscillator
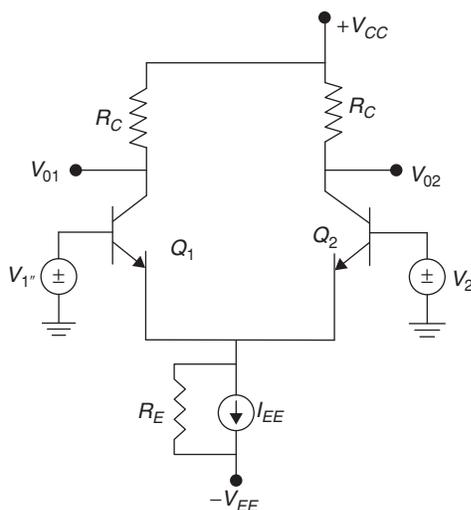
### THE DIFFERENTIAL AMPLIFIER

The emitter coupled differential amplifier is an essential building block in modern IC amplifiers.



Differential mode voltage gain  $A_{DM} = -g_m R_C$

Common mode voltage gain  $A_{CM} = \frac{-R_C}{2R_E}$

Common mode rejection ratio

$$\text{CMRR} = \frac{A_{DM}}{A_{CM}} = 1 + 2g_m R_E$$

**Output for arbitrary input signals:** If  $V_1$  and  $V_2$  are inputs applied to transistors  $Q_1$  and  $Q_2$

$$V_{DM} = \frac{V_1 - V_2}{2}, V_{CM} = \frac{V_1 + V_2}{2}$$

$$\begin{aligned} V_{01} &= A_{DM} V_{DM} + A_{CM} V_{CM} \\ &= A_{DM} \left( V_{DM} + \frac{V_{CM}}{\text{CMRR}} \right) \end{aligned}$$


$$\begin{aligned} V_{02} &= -A_{DM} V_{DM} + A_{CM} V_{CM} \\ &= -A_{DM} \left( V_{DM} - \frac{V_{CM}}{\text{CMRR}} \right) \end{aligned}$$

**Input and output resistances:** Differential mode output resistance

$$R'_{O(DM)} = R_C \parallel r_o \cong R_C$$

Differential mode input resistance  $R_{i(DM)} = 2r_e$

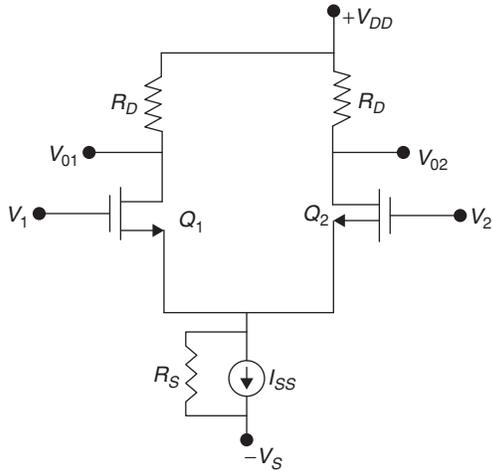**FET differential Amplifiers:** The source-coupled pair differential amplifier with MOSFETs is shown in the figure







$$CMRR = 1 + \frac{2R_S (1 + \mu)}{r_d + R_D}$$

For  $r_d \gg R_D$  and  $\mu \gg 1$

$$CMRR = 1 + 2g_m R_S \cong 2g_m R_S$$

## FEEDBACK AMPLIFIERS

### Feedback Amplifier Topologies

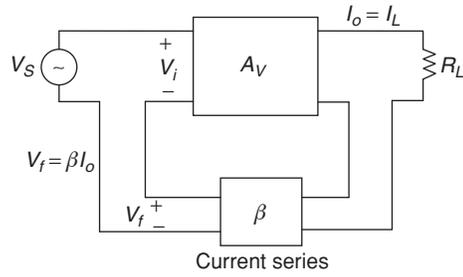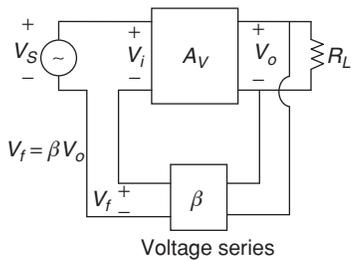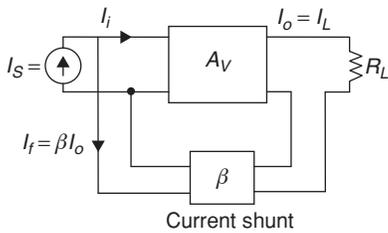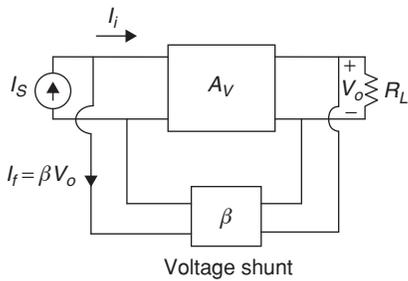

## Classification of Amplifiers

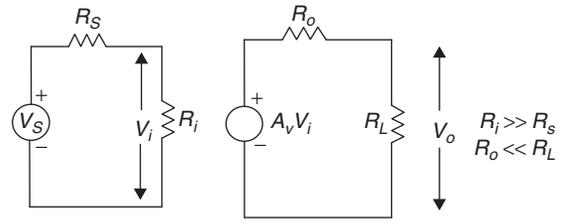


Figure 1 Voltage amplifier

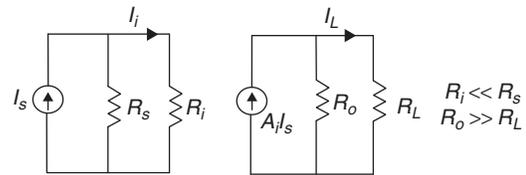


Figure 2 Current amplifier

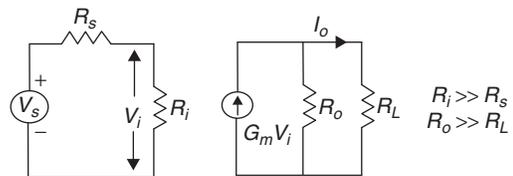


Figure 3 Transconductance amplifier

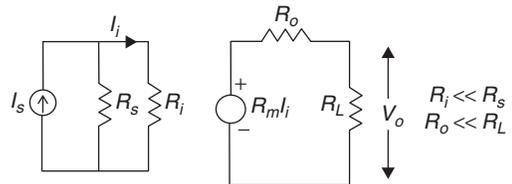


Figure 4 Transresistance amplifier

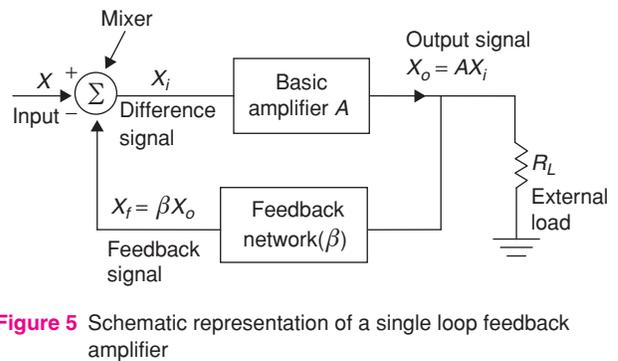


Figure 5 Schematic representation of a single loop feedback amplifier

**Advantages of negative feedback**

High input resistance of a voltage amplifier can be made higher, and its lower output resistance can be lowered. The transfer gain  $A_f$  of the amplifier with feedback can be stabilized against variations of h-parameters of transistor. It improves frequency response.

**Stability of gain**

$$A_f = \frac{A}{1 + A\beta}$$

if  $A\beta \gg 1$ ,  $A_f = \frac{A}{A\beta} = \frac{1}{\beta}$

$$\frac{\partial A_f}{A_f} = \frac{1}{(1 + A\beta)} \frac{\partial A}{A}$$

$\frac{\partial A_f}{A_f}$  = fractional change in amplifier voltage gain with feedback

$\frac{\partial A}{A}$  = fractional change in amplifier voltage gain without feedback

$$\text{Sensitivity} = \frac{1}{1 + A\beta}$$

$$\text{Desensitivity} = 1 + A\beta$$

Increase in input impedance,  $Z_{if} = Z_i (1 + A\beta)$

Decrease in output impedance,  $Z_{of} = \frac{Z_o}{1 + A\beta}$

Reduction in distortion and noise

$$D_f = \frac{D}{1 + A\beta}, N_f = \frac{N}{1 + \beta}$$

Increase in bandwidth with negative feedback lower cut-off frequency

$$f'_L = \frac{f_L}{1 + A_v\beta}$$

Upper cut-off frequency  $f'_H = f_H (1 + A_v\beta)$

$\therefore$  Overall B.  $W_f = BW (1 + A\beta)$ .

**Table 1** Effect of negative feedback on amplifier

	Voltage series	Current series	Current shunt	Voltage shunt
$R_{\text{output}}$	Decreases	Increases	Increases	Decreases
$R_{\text{input}}$	Increases	Increases	Decreases	Decreases
Improves characteristics of	Voltage amplifier	Trans conductance amplifier	Current amplifier	Transresistance amplifier
Desensitizes	$A_v$	$G_m$	$A_{if}$	$R_{mf}$
Bandwidth	Increases	Increases	Increases	Increases
Non linear distortion	Decreases	Decreases	Decreases	Decreases

**Example 1:** The gain of an amplifier with feedback is to be nominally 20, and a variation of 5% is permissible. If the magnitude of loop gain must be at least 1000 (so that  $A\beta \gg 1$ ), then maximum permissible variation in open loop gain is \_\_\_\_\_

- (A) 20
- (B) 50
- (C) 40
- (D) 30

**Solution:** (B)

Given  $A_f = 20$

If  $A\beta \gg 1 \Rightarrow A_f = \frac{1}{\beta} \therefore \beta = \frac{1}{20} = 0.05$

$$\left| \frac{dA_f}{A_f} \right| = \frac{1}{|1 + A\beta|} \left| \frac{dA}{A} \right|$$

$$\Rightarrow \left| \frac{dA}{A} \right| = 50$$

**Example 2:** If the input impedance and voltage gain of a open loop voltage series feedback amplifier are 3 kΩ and 100, and the feedback factor is  $\frac{1}{50}$ , then the input impedance of closed loop configuration is \_\_\_\_\_

- (A) 9 kΩ
- (B) 6 kΩ
- (C) 3 kΩ
- (D) 12 kΩ

**Solution:** (A)

$$A = 100, R_{in} = 3 \text{ k}\Omega$$

$$R_{inf} = R_{in} (1 + A\beta)$$

$$= 3 \text{ k}\Omega \left( 1 + 100 \frac{1}{50} \right)$$


$$R_{inf} = 9 \text{ k}\Omega$$

**Note:** Voltage-series feedback

(i)  $R_{inf} = R_{in} (1 + A\beta)$

(ii)  $R_{of} = \frac{R_o}{(1 + A\beta)}$

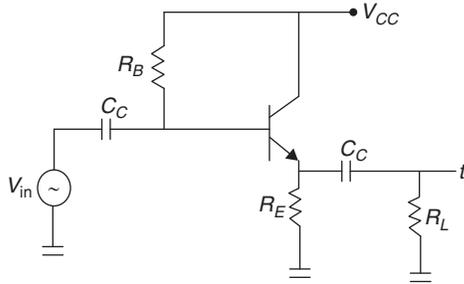
**Example 3:** Find the type of the feedback in the given circuit



- (A) Current series
- (B) Voltage shunt
- (C) Voltage series
- (D) Current shunt


**Solution:** (C)

AC equivalent circuit:

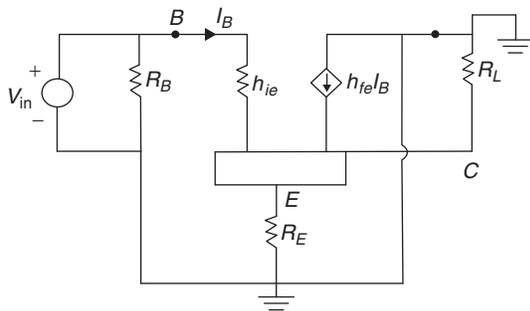

Input-series connection  
Output-shunt connection  
∴ Voltage series feedback.

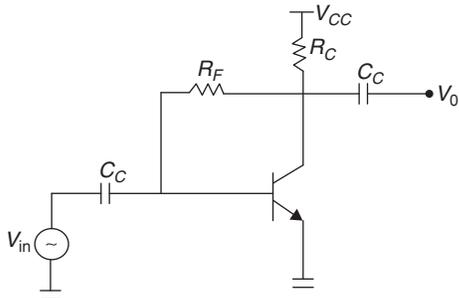
**Example 4:** Find the type of the feedback in the given circuit.



- (A) Voltage-series
- (B) Current-series
- (C) Current-shunt
- (D) Voltage-shunt

**Solution:** (D)

AC equivalent model:

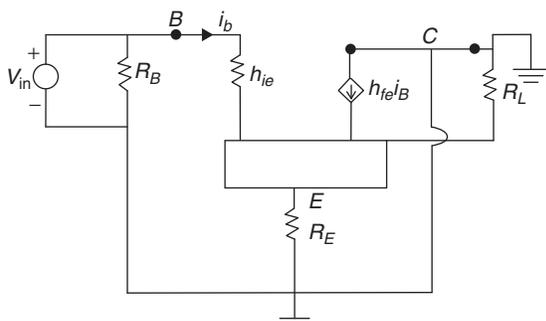

Input-shunt connection  
Output-shunt connection  
∴ Voltage-shunt feedback

## POWER AMPLIFIERS

### Classification

#### Class A

Class A amplifier is one in which the operating point and the input signal are such that the current in the output circuit flows all the times. Normally class A amplifier operates essentially over a linear portion of its characteristic.

#### Class B

A class B amplifier is one in which the operating point is at an extreme end of its characteristic, so that the quiescent power is very small, hence either the quiescent current or voltage is approximately zero. If the input signal is sinusoidal, amplification takes place for only one half of the cycle.

#### Class AB

A class AB, amplifier is one operating between the two extremes defined for class A and class B, hence the output signal is zero, for part but less than one half of an input sinusoidal signal cycle.

#### Class C

A class C amplifier is one in which the operating point is chosen so that the output current (voltage) is zero, for more than one half of an input sinusoidal signal cycle.

### Efficiency of Class A Amplifier

$$\eta = \frac{\text{signal power delivered to load}}{\text{DC power supplied to output circuit}} \times 100$$

$$\eta = \frac{\frac{1}{2} \cdot V_m \cdot I_m}{V_{cc} \cdot I_{CQ}} \times 100$$

Where  $V_m$  ( $I_m$ ) represents the peak sinusoidal voltage (current) swing.

Class of Operation	Conduction Angle	Efficiency
Class 'A'	360°	25–50%
Class 'AB'	108° to 360°	50–75%
Class 'B'	180°	78.5%
Class 'C'	Less than 180°	80–90%
Class 'D'	Pulse operation	>90%

- (i) Class A
  - Series-fed
  - Transformer Coupled
- (ii) Class B
  - Push-Pull
  - Complementary symmetry

(iii) Class C circuits are used in tuned circuits, such as radio communications.

3.202 | Analog and Digital Electronics

Amplifier efficiency ( $\eta$ ):


$$\eta = \frac{\text{AC power delivered to the load}}{\text{DC input power}}$$

$$P_i(\text{DC}) = \frac{V_{CC}^2}{2R_C}$$


$$\therefore \eta = 25\%$$

$\therefore$  Maximum efficiency of class A amplifier is 25%.

Series Fed Class A Amplifier

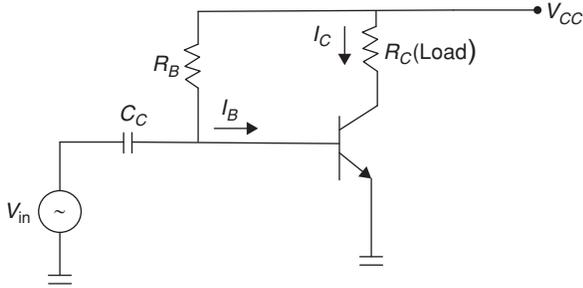

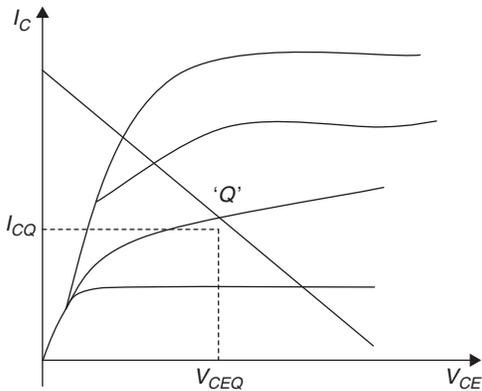To have maximum output swing, 'Q' point should be located at the middle of the DC load line



Efficiency calculations

$$\eta = \frac{P_o(\text{AC})}{P_i(\text{DC})}$$

$$P_i(\text{DC}) = V_{cc} \cdot I_{CQ}$$

$$P_o(\text{AC}) = \frac{V_{CE}(P-P)I_C(P-P)}{8}$$



To have maximum output swing,

$$V_{CE}(P-P) = V_{cc}$$

$$I_C(P-P) = \frac{V_{CC}}{R_C}, P_o(\text{AC}) = \frac{V_{CC}^2}{8R_C}$$

$$I_{CQ} = \frac{V_{cc}}{2R_C}$$

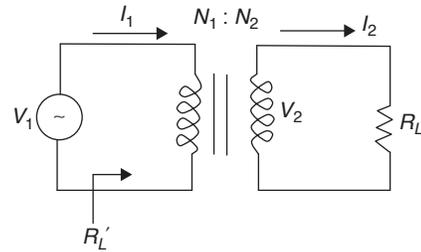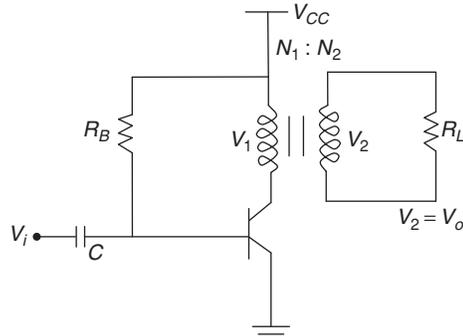Transformer coupled class A power amplifies



$$\frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$\frac{I_1}{I_2} = \frac{N_2}{N_1}$$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 R_L$$

**Example 5:** Calculate the effective resistance seen looking into the primary of a 15 : 1 transformer connected to an 8  $\Omega$  load

- (A) 2 k $\Omega$
- (B) 1.8 k $\Omega$
- (C) 3 k $\Omega$
- (D) 4 k $\Omega$

**Solution:** (B)

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 R_L = (15)^2 8$$

$$R_L' = 1.8 \text{ k}\Omega$$

**Maximum theoretical efficiency:**

$$\eta = 50 \left( \frac{V_{CE_{\max}} - V_{CE_{\min}}}{V_{CE_{\max}} + V_{CE_{\min}}} \right)^2 \%$$

### Class B Push-Pull Amplifier

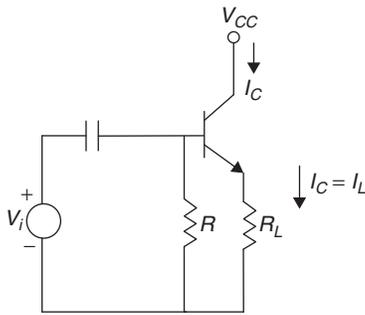


Figure 6 Emitter follower with zero bias operating as class B amplifier


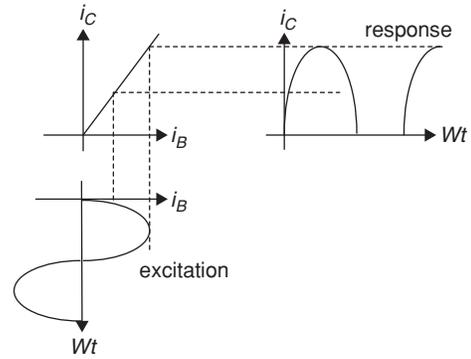


Figure 7 Dynamic transfer characteristic

The emitter follower operates in class B. Let us assume that the transistor output characteristics are equally spaced for equal intervals of excitation for such an idealized transistor the dynamic transfer curve ( $i_c$  vs  $i_B$ ) is a straight line, passing through the origin. The graphical construction from which to determine the collector current wave shape is indicated.
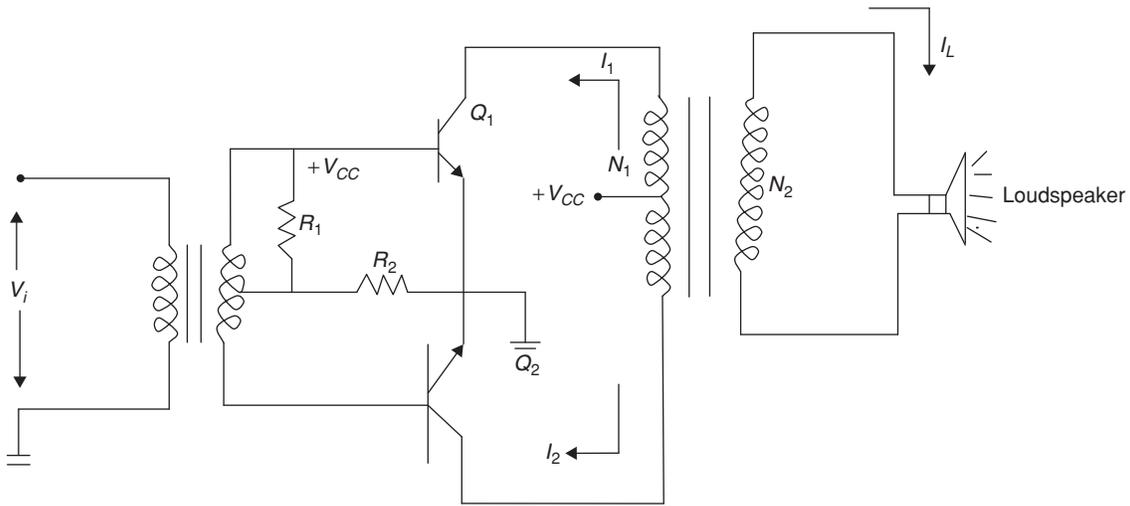
### Transformer coupled push-pull amplifier



During positive half cycle:  $Q_1$  ON and  $Q_2$  OFF  
 Negative half cycle:  $Q_1$  OFF and  $Q_2$  ON


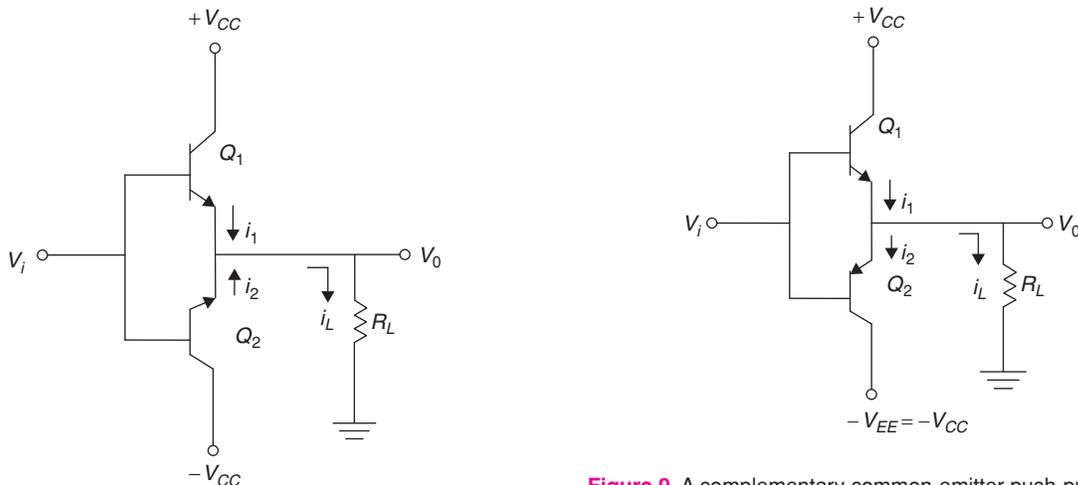


Figure 9 A complementary common-emitter push-pull amplifier

Figure 8 A complementary emitter follower
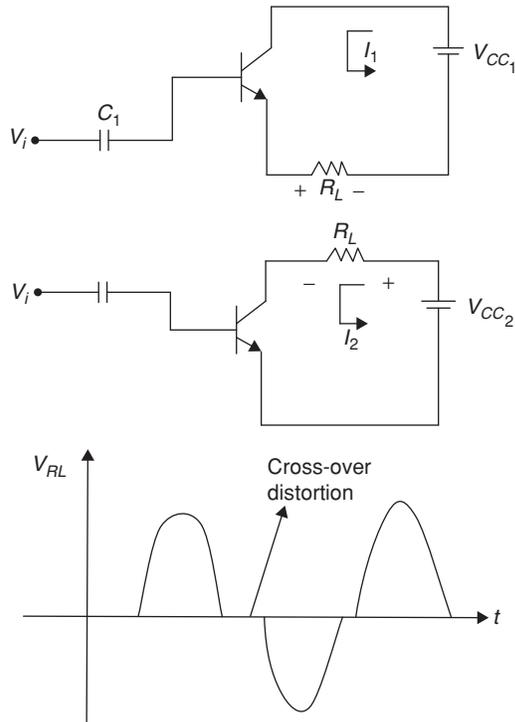
### Transformer coupled push-pull amplifier



For positive values of sinusoidal input ( $V_i$ )  $Q_1$  conducts and  $Q_2$  is OFF ( $i_2 = 0$ ) so that  $i_1$  is the positive half sine wave.

For negative values of  $V_i$ ,  $Q_1$  is non conducting ( $i_1 = 0$ ) and  $Q_2$  conducts, resulting in a positive half sinusoid for  $i_2$  which is  $180^\circ$  out of phase with that  $i_1$ .

Since load current is difference between the two transistor emitter currents  $i_L = i_1 - i_2$

Consequently for idealized transfer characteristics the load current is a perfect sinusoid.

The advantage of class B as compared with class A operating are:

It is possible to obtain greater power output, and efficiency is higher, and there is negligible power loss at no signal.

The disadvantages are higher harmonic distortion and power supply voltages must have good regulation.

**Efficiency:** If peak load voltage  $V_m = I_m R_L$

$$\eta = \frac{P}{P_i} \times 100 = \frac{\pi}{4} \left[ 1 - \frac{V_{\min}}{V_{cc}} \right] \times 100\%$$

### Dissipation

$$P_c = P_i - P = \frac{2}{\pi} \cdot \frac{V_{cc} \cdot V_m}{R_L} - \frac{V_m^2}{2R_L}$$

$$P_c(\max) = \frac{2V_{cc}^2}{\pi^2 R_L} = \frac{4}{\pi^2} \cdot P_{\max}$$

$P_c(\max)$  = maximum power dissipation

$P_{\max}$  = maximum power which can be delivered


**Example 6:** Calculate the efficiency of a class B amplifier for a supply voltage of 24 V with peak voltage of 8 V.

- (A) 26.18%                      (B) 35.62%  
(C) 40.25%                      (D) 52.36%

**Solution:** (A)


$$\eta = 78.54 \frac{V_L(p)}{V_{cc}} \% = 78.54 \times \frac{8}{24} = 26.18 \%$$

### Class AB Amplifier

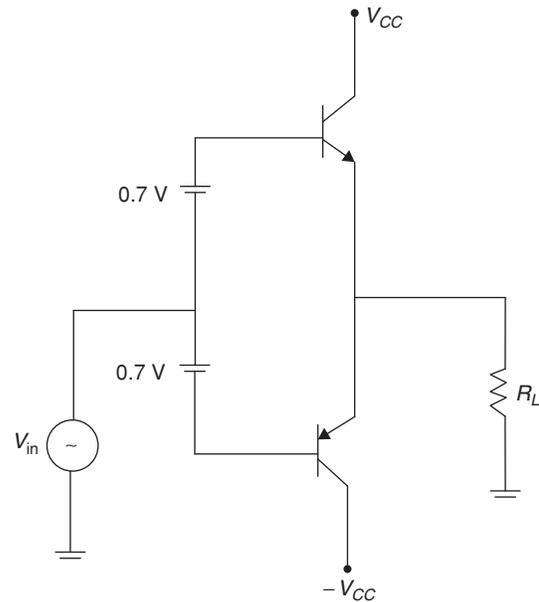

Cross over distortion is eliminated by adding two diodes whose cut in voltages were  $+0.7 \text{ V}$  and  $-0.7 \text{ V}$ .

### Class C Amplifier

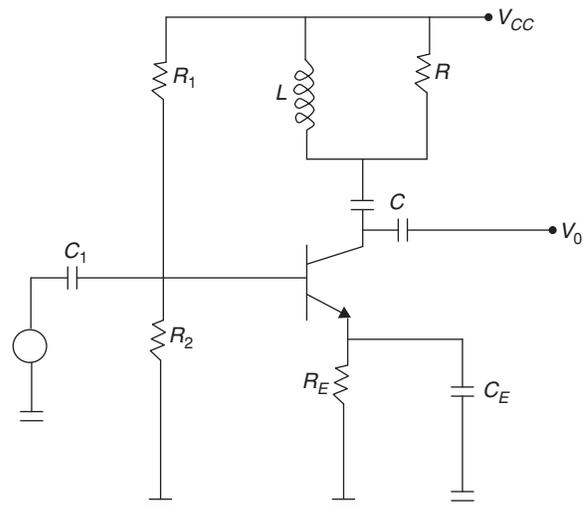

Class C amplifier is used to generate a pulse wave form whose conduction angle is less than  $180^\circ$ . Efficiency of class C amplifier is 90%.

### Resonant frequency

$$Z_L = (R \parallel SL) + \frac{1}{sC}$$

$$R \parallel SL = \frac{(R)(sL)}{(R) + (sL)}$$

$$Z_L = \frac{(R)(sL)}{(R) + (sL)} + \frac{1}{sC}$$

$$Z_L = \frac{s^2 LCR + R + sL}{sC(R + sL)}$$

$$Y_L = \frac{sC(R + sL)}{s^2 LCR + R + sL}$$

Put  $S = j\omega$

$$Y_L = \frac{j\omega RC - \omega^2 LC}{-\omega^2 LCR + R + j\omega L}$$

$$Y_L = \frac{j\omega RC - \omega^2 LC}{[R - \omega^2 LCR] + (j\omega L)} \frac{[R - \omega^2 LCR] - j\omega L}{[R - \omega^2 LCR] + (j\omega L) [R - \omega^2 LCR] - (j\omega L)}$$

To find resonant frequency, make imaginary part = 0  
 i.e.,  $j\omega RC [R - \omega^2 LC] + j\omega^3 L^2 C = 0$

$$\omega^2 R^2 C - \omega^2 RLC^2 + \omega^3 L^2 C = 0$$

$$R^2 C = \omega^2 [RLC^2 - L^2 C]$$

$$\omega^2 = \frac{R^2 C}{RLC^2 - L^2 C}$$

$$\omega = \sqrt{\frac{R^2 C}{RLC^2 - L^2 C}}$$

### 555 TIMER

The 555 timer is a highly stable device for generating accurate time delay or oscillation.

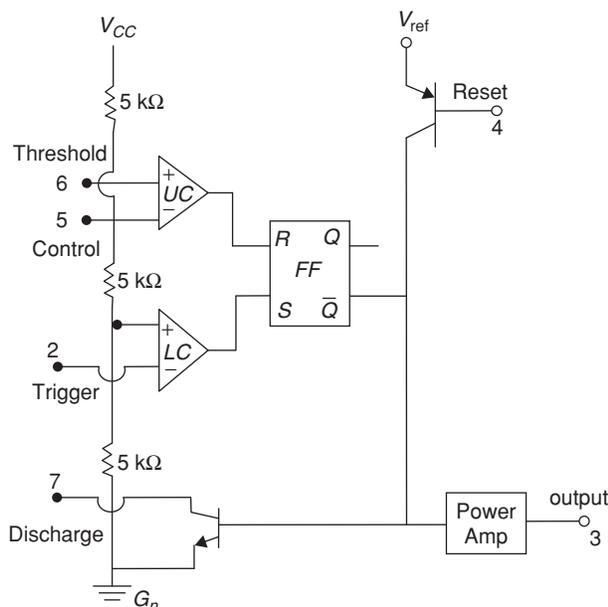


Figure 10 Functional diagram of 555 timer

Three 5 kΩ internal resistors act as voltage divider, providing bias voltage of  $\frac{2}{3}V_{CC}$  to upper comparator (UC) and  $\frac{1}{3}V_{CC}$  to lower comparator (LC). Since these two voltages fix the necessary comparator threshold voltage, they also aid in determining the timing interval. It is possible to vary time by applying a modulating voltage to control input terminal.


In applications where no such modulation is intended, it is recommended to connect a capacitor between control and ground.

The reset pin provides a mechanism to reset FF, when reset is not used, it is returned to  $V_{cc}$ .


#### Operation:

- $V_{cc}$  is typically 5 V, The R's are 5 kΩ each, and act as a voltage divider, to create voltages of value  $\frac{V_{CC}}{3}$ ,  $\frac{2V_{CC}}{3}$
- Comparator 1 compares the voltage applied at the 'threshold' terminal with  $\frac{2V_{CC}}{3}$ , and comparator 2 compares the voltage at the 'trigger' terminal with  $\frac{V_{CC}}{3}$ .
- External connection to the 'control' terminal will override the  $\frac{2V_{CC}}{3}$  existing at that node, and allows the user added flexibility.
- When the comparator 2 output is high, it 'sets' the RS flip-flop whose output (Q) goes high. This turns on the discharge transistor  $Q_1$ , and causes the 'discharge' terminal to be discharged to the ground.
- When the comparator 1 output is high, it resets the RS-flipflop, whose output goes low, which turns  $Q_1$  OFF.

#### Monostable Operation

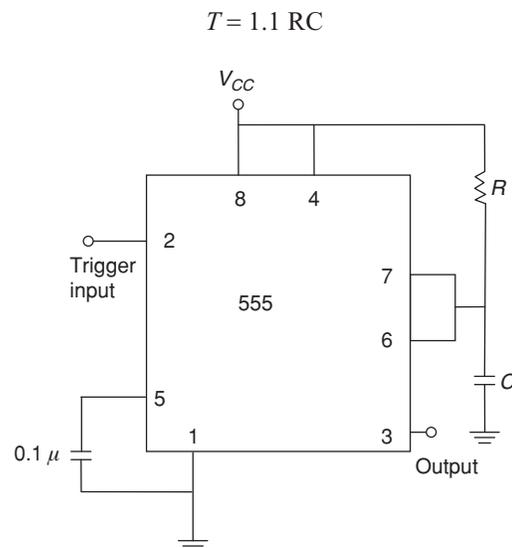

### 3.206 | Analog and Digital Electronics

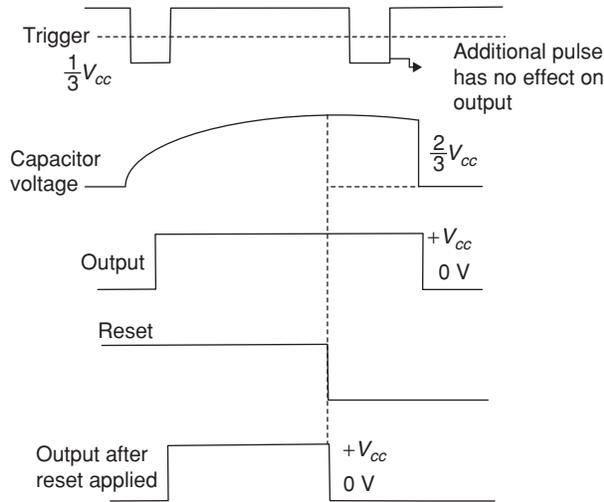

#### Operation

Condition	R	S	Q	Output = Q	Transistor status
$V_{cc} > \frac{2}{3}V_{cc}$	1	0	1	0	ON, capacitor starts discharging
$V_{cc} = 0V$	0	0	1	0	No change in state
Apply Trigger	0	1	0	1	OFF, capacitor starts charging
$V_{cc} > \frac{1}{3}V_{cc}$	0	0	0	1	No change in state
$V_{cc} > \frac{2}{3}V_{cc}$	1	0	1	0	ON, capacitor starts discharging
$V_{cc} = 0V$	0	0	1	0	no change in state



$$V_C(t) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}})e^{-\frac{t}{RC}}$$

$$V_C(t) = V_{CC} + (0 - V_{CC})e^{-\frac{t}{RC}}$$

At  $t = T$ ,  $V_C(t) = \frac{2}{3}V_{CC}$ , where 'T' represents duration which 'Q' output goes high

$$\therefore \frac{2}{3}V_{CC} = V_{CC} \left[ 1 - e^{-\frac{T}{RC}} \right] \Rightarrow T = 1.1 RC$$

#### Astable Operation

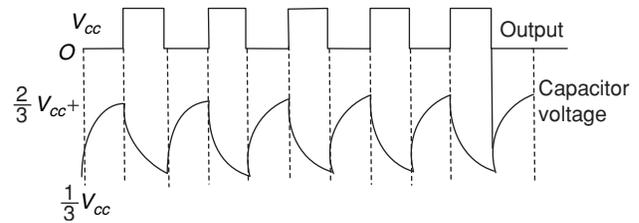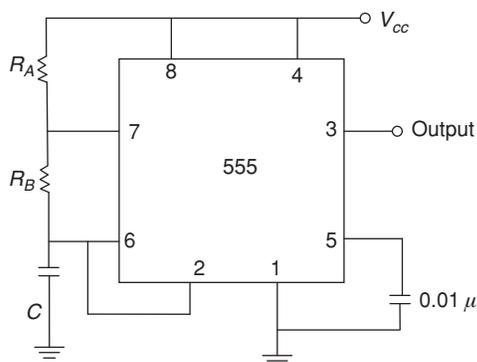

Assume capacitor discharges, when power is switch ON,  $V_{\text{trigger}} = V_{\text{threshold}} = 0$

$\Rightarrow$  comparator 2 will have a high output

Comparator 1 will have a low output.

$\Rightarrow R = 0, S = 1$  and  $Q = 1$

So capacitor will charge through  $(R_A + R_B)$

$V_C(t) > \frac{V_{CC}}{3}$ , comparator 2 output will go low  $\Rightarrow S = 0$

$V_C(t) > \frac{2V_{CC}}{3}$ , comparator 2 output will go high  $\Rightarrow Q = 0$

$$V_C(t) = \frac{2V_{CC}}{3} \exp\left(\frac{-t}{R_B \cdot C}\right)$$

$$V_C(T_1) = \frac{V_{CC}}{3} = \frac{2V_{CC}}{3} \exp\left(\frac{-T_1}{R_B C}\right)$$

$$T_1 = R_B C \ln(2) = 0.69 R_B C$$

Similarly, during the time period  $T_2$

$$V_C(t) = V_{CC} - \left( V_{CC} - \frac{V_{CC}}{3} \right) \exp\left[\frac{-t}{(R_A + R_B)C}\right]$$

$$T_2 = (R_A + R_B) \ln(2) = 0.69 (R_A + R_B) C$$

$$T = T_1 + T_2 = 0.69 (R_A + 2R_B)C$$

$$\text{Duty cycle} = \frac{T_1}{T_1 + T_2} = \frac{R_A + R_B}{R_A + 2R_B}$$

$$t_{\text{high}} = 0.69(R_A + R_B)C$$

$$t_{\text{low}} = 0.69R_B C$$

$$T = t_{\text{high}} + t_{\text{low}}$$

$$= 0.69(R_A + 2R_B)C$$

$$f = \frac{1}{T} = \frac{1.45}{(R_A + 2R_B)C}$$

$$\text{Duty Cycle} = \frac{t_{\text{high}}}{T} \times 100 = \frac{R_A + R_B}{R_A + 2R_B} \times 100$$

When  $R_A$  is much smaller than  $R_B$  duty cycle approaches to 50%. If  $R_A$  is much greater than  $R_B$  duty cycle approaches to 100%. The circuit can be modified to enabled the duty cycle less than 50%. By placing a diode across  $R_B$  (anode at pin 7).

The capacitor will effectively charge through  $R_A$  and diode. The capacitor will discharge through  $R_B$ ,  $D = \frac{R_A}{R_A + R_B}$


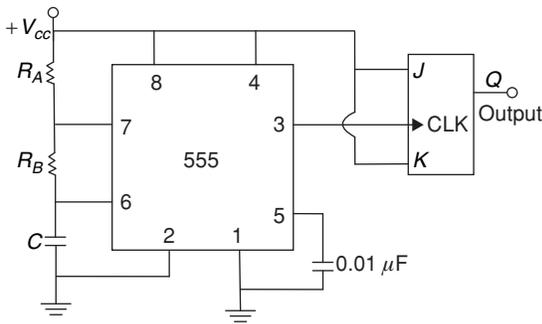



Figure 11 Symmetrical wave form generator.

The clocked flip-flop acts as binary divider to the timer output. The output frequency in this case will be one half that of the timer, the advantage of this circuit is of having output of 50% duty cycle, without any restriction on the choice of  $R_A$  and  $R_B$ .

### Schmitt Trigger

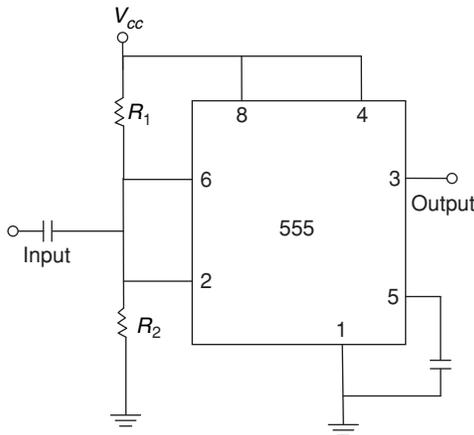

The use of 555 timer as a Schmitt trigger input is shown in figure. Here the two internal comparators are tied together and externally biased at  $\frac{V_{cc}}{2}$  by  $R_1$  and  $R_2$  resistors. The threshold levels of (UC) =  $\frac{2}{3}V_{cc}$  and LC =  $\frac{1}{3}V_{cc}$  and the bias provided by  $R_1$  and  $R_2$  determine the output wave form. Thus sine wave of sufficient amplitude,  $\left( > \frac{V_{cc}}{6}, \text{ i.e., } \frac{2}{3}V_{cc} - \frac{V_{cc}}{2} \right)$  to exceed the reference levels causes the internal flip-flop to alternately set and reset, providing a square wave output

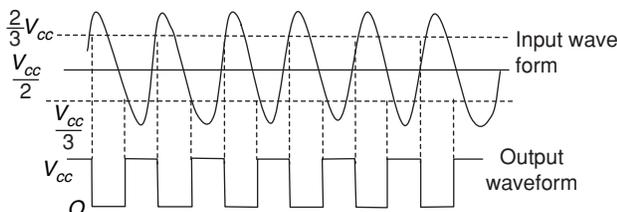

Unlike multivibrators, no frequency division is taking place and frequency of square wave remains same as that of input signal.

### VOLTAGE CONTROLLED OSCILLATOR

Voltage controlled oscillator (VCO) or voltage to frequency converter can be found in Applications like frequency modulation, tone generators, and frequency shift keying (FSK) etc, where frequency needs to be controlled by input voltage.

A typical example for VCO is IC 566, which provides simultaneous square wave and triangular wave outputs as a function of input voltage.

The frequency of osculation is determined by an external resistor  $R_1$ , capacitor  $C_1$ , and the voltage  $V_c$  applied.

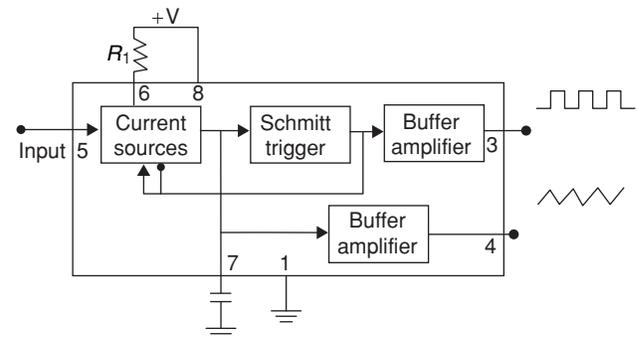


Figure 12 Block diagram. of 566

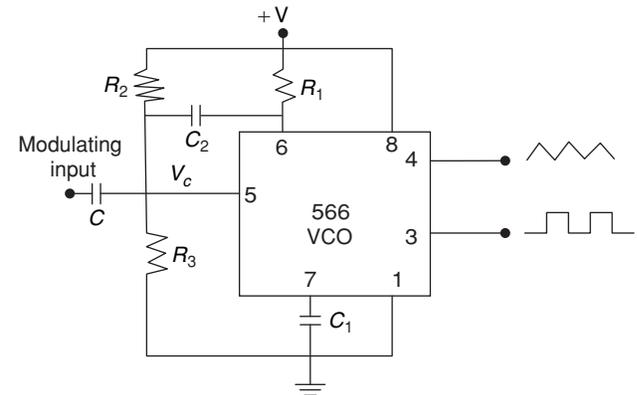


Figure 13 Typical connection diagram

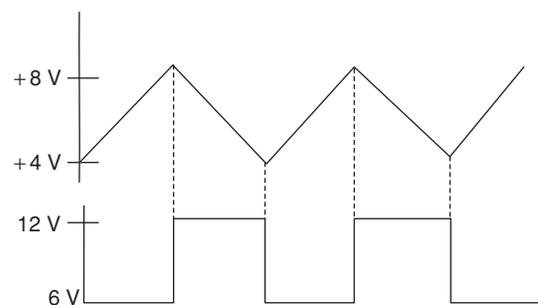


Figure 14 Output waveforms

3.208 | Analog and Digital Electronics

$$f_o = \frac{2(V - V_c)}{R_1 C_1 (+V)}$$


Where  $\frac{3}{4}(+V) \leq V_c \leq (+V)$  and  $2 \text{ k}\Omega < R, < 20 \text{ k}\Omega$

VCO is commonly used in converting low frequency signal such as electroencephalograms (EEG) or electrocardiograms (ECG) into an audio frequency range.

**Solved Examples**

**Directions for questions 7 to 11:** Select the correct alternative from the given choices.

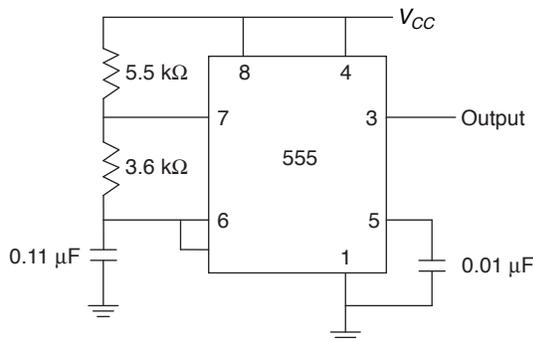**Example 7:** The 555 timer circuit to generate a rectangular waveform is shown in figure. The frequency and duty cycle of the waveform are



- (A) 1 kHz, 0.43
- (B) 2 kHz, 0.43
- (C) 2 kHz, 0.28
- (D) 1 kHz, 0.28

**Solution:** (D)



$$f = \frac{1.45}{(R_A + 2R_B)C} = \frac{1.45}{(5.5 + 2 \times 3.6) \times 0.11 \times 10^{-3}}$$

$$= 1.04 \text{ kHz} \approx 1 \text{ kHz}$$

$$\text{Duty cycle} = \frac{R_B}{R_A + 2R_B} = \frac{3.6}{5.5 + 2 \times 3.6}$$

$$= 0.28$$

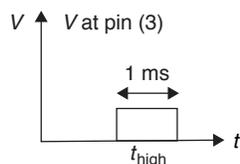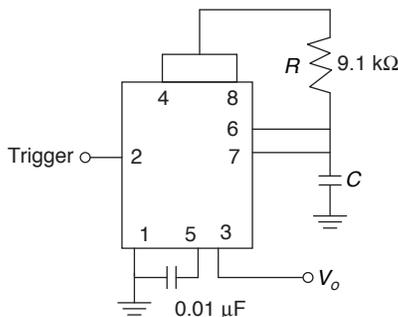**Example 8:** A monostable multivibrator circuit is shown in the figure. The value of  $C$  would be nearly




- (A) 0.01 μF
- (B) 0.001 μF
- (C) 0.1 μF
- (D) 1 μF

**Solution:** (C)

$$T_{\text{high}} = 1.1 R.C$$

$$\Rightarrow C = \frac{1.0 \times 10^{-3}}{1.1 \times 9.1 \times 10^3} = 0.1 \mu\text{F}$$

**Common Data for Questions 9 to 10:** For the circuit shown in the figure, the transistor parameters are  $h_{fe} = 100$ ,  $h_{ie} = 1 \text{ k}\Omega$ ,  $R_s = 2 \text{ k}\Omega$ ,  $R_L = 20 \text{ k}\Omega$ ,  $R_f = 200 \text{ k}\Omega$ .

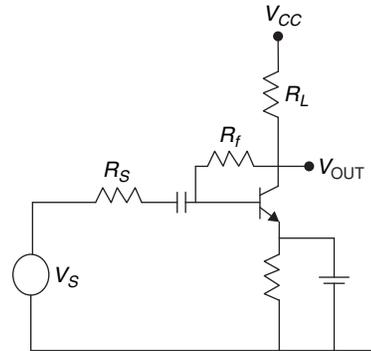

**Example 9:** The type of feedback used in this circuit is

- (A) Voltage shunt.
- (B) Current shunt.
- (C) Voltage series.
- (D) Current series.

**Solution:** (A)

$R_f$  is across the output and samples the output voltage  $V_o$ . At the input it is in shunt, resulting current feedback, the feedback in voltage shunt is

$$\beta = \frac{I_f}{V_o} = -\frac{1}{R_f} = \frac{1}{200 \times 10^3} \text{ mho}$$


This feedback amplifier is a current controlled voltage source, hence both input and output impedances are reduced by feedback.

**Example 10:** The feedback factor is

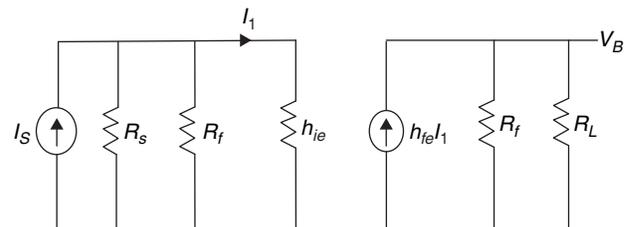- (A) 5.543
- (B) 4.636
- (C) 3.423
- (D) 2.942

**Solution:** (B)

The equivalent current of the amplifier without feedback will have  $R_f$  across input, and  $R_f$  across load resistance  $R_L$



$$A_z = \frac{V_o}{I_s} = \frac{V_o}{I_i} \times \frac{I_i}{I_s} \text{ (Total gain without feedback)}$$

Here  $R_s = 2\text{ K}$ ,  $h_{ie} = 1\text{ K}$ ,  $R_f = 200\text{ K} \gg h_{ie}$   
 Input resistance  $R_i = 0.66\text{ k}\Omega$

$$\frac{I_i}{I_s} = \frac{0.66}{1 + 0.66} = 0.397$$

$$R_f \parallel R_L = 200\text{ K} \parallel 20\text{ K} = 18.18\text{ k}\Omega$$

$$\frac{V_o}{I_i} = -h_{ie} \times R_f \parallel R_L = -100 \times 18.18\text{ k}\Omega$$

$$A_z = \frac{V_o}{I_i} \times \frac{I_i}{I_s} = 72.72 \times 10^4$$

$$D = 1 + A_z \beta = 1 + 72.72 \times 10^4 \times \frac{1}{200 \times 10^3} = 4.636$$

**Example 11:** The input and output impedance values in mid-band are

- (A) 142  $\Omega$ , 3.92 k $\Omega$
- (B) 3.92 k $\Omega$ , 142  $\Omega$
- (C) 0.66 k $\Omega$
- (D) 18.18 k $\Omega$ , 0.66 k $\Omega$

**Solution:** (A)

$$R_{in} = \text{Input resistance} = \frac{0.66\text{ k}\Omega}{4.636} = 0.142\text{ k}\Omega$$

$$R_{out} = \text{Output resistance} = \frac{18.182}{4.636} = 3.92\text{ k}\Omega$$

### EXERCISES

#### Practice Problems 1


**Directions for questions 1 to 43:** Select the correct alternative from the given choices.

- An amplifier has an open loop gain of 100 with 10% harmonic distortion at output. If 40 dB of negative feedback is applied, the distortion with feedback is \_\_\_\_\_.  
 (A) 0.1% (B) 10%  
 (C) 100% (D) None
- The gain of amplifier is 1000 and  $\beta = 0.1$ . Due to temperature variations, gain is changed by 15%, the change in gain with -ve feedback is \_\_\_\_\_.  
 (A) 0% (B) 1.5%  
 (C) 0.15% (D) 1%
- An amplifier has an open loop gain of 200, an input impedance of 5 k $\Omega$  and output impedance of 600  $\Omega$ . A feedback factor of  $\beta = 20\%$  is connected to the amplifier in a voltage shunt feedback mode, the new input and output impedances are \_\_\_\_\_.  
 (A)  $Z_{if} = 205\text{ k}\Omega$   $Z_{of} = 14.63\text{ }\Omega$   
 (B)  $Z_{if} = 122\text{ }\Omega$   $Z_{of} = 24.6\text{ k}\Omega$   
 (C)  $Z_{if} = 205\text{ k}\Omega$   $Z_{of} = 24.6\text{ k}\Omega$   
 (D)  $Z_{if} = 122\text{ }\Omega$   $Z_{of} = 14.63\text{ }\Omega$
- The mid-band gain of an amplifier is 1000. Its lower and upper cut-off frequencies are 60 Hz and 80 kHz respectively. A feedback Network with  $\beta = 0.05$  is taken, the new lower and upper cut-off frequencies are \_\_\_\_\_.  
 (A)  $f'_L = 3.1\text{ kHz}$   $f'_H = 1.568\text{ kHz}$   
 (B)  $f'_L = 3.1\text{ kHz}$   $f'_H = 4.08\text{ MHz}$   
 (C)  $f'_L = 1.176\text{ Hz}$   $f'_H = 4.08\text{ MHz}$   
 (D)  $f'_L = 1.176\text{ Hz}$   $f'_H = 1.568\text{ kHz}$
- The gain-band width product of amplifier without feedback is 6 MHz. with negative feedback, the bandwidth is 1 MHz, the closed loop gain is \_\_\_\_\_.

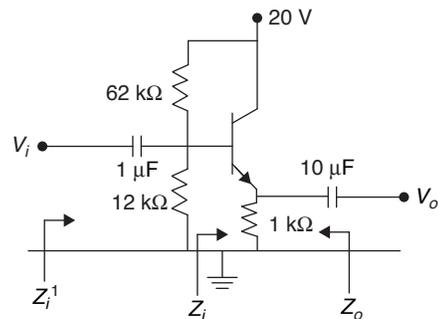- (A) 6 (B) 60
- (C) 100 (D) 10

- An amplifier has a voltage gain 200 with  $Z_i = 10\text{ k}\Omega$  and  $Z_o = 1\text{ k}\Omega$ . A negative feedback with  $\beta = 0.04$  in current shunt feedback is applied, the result input and output impedance are \_\_\_\_\_.  
 (A)  $Z_{if} = 1.11\text{ k}\Omega$   $Z_{of} = 0.11\text{ k}\Omega$   
 (B)  $Z_{if} = 1.11\text{ k}\Omega$   $Z_{of} = 9\text{ k}\Omega$   
 (C)  $Z_{if} = 90\text{ k}\Omega$   $Z_{of} = 0.11\text{ k}\Omega$   
 (D)  $Z_{if} = 90\text{ k}\Omega$   $Z_{of} = 9\text{ k}\Omega$


**Common Data for Questions 7 to 9:** For the given emitter follower, the specifications are  $\beta = 100$ ,  $h_{ie} = 2\text{ k}\Omega$




- The input impedance  $Z_i$  is \_\_\_\_\_.  
 (A) 1 k $\Omega$  (B) 101 k $\Omega$   
 (C) 103 k $\Omega$  (D) 10.05 k $\Omega$
- The input impedance  $Z'_i$  as seen from source is \_\_\_\_\_.  
 (A) 9.156 k $\Omega$  (B) 10.05 k $\Omega$   
 (C) 12 k $\Omega$  (D) 62 k $\Omega$
- The output impedance  $Z_o$  is \_\_\_\_\_.  
 (A) 1 k $\Omega$  (B) 20  $\Omega$   
 (C) 1.02 k $\Omega$  (D)  $\infty$

3.210 | Analog and Digital Electronics

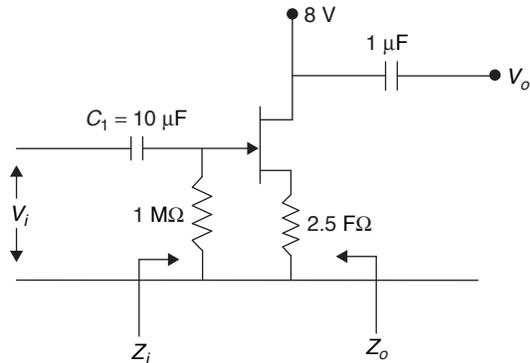**Common Data for Questions 10 to 12:** A source follower is shown below with following specifications  $I_{DSS} = 12 \text{ mA}$ ,  $V_p = 4 \text{ V}$ ,  $g_m = 2.28 \text{ ms}$  and  $r_d = \infty$



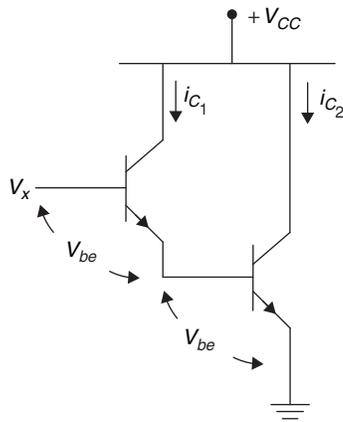10. The input impedance  $Z_i$  is  
 (A)  $\infty$  (B) 0  
 (C)  $1 \text{ M}\Omega$  (D) None
11. The output impedance  $Z_o$  is  
 (A)  $2.5 \text{ k}\Omega$  (B)  $37 \Omega$   
 (C)  $3.7 \text{ k}\Omega$  (D)  $372 \Omega$
12. Voltage gain  $A_v$  is  
 (A) 0.85 (B) 1  
 (C) 99 (D) None
13. The Darlington pair stage is shown in the following figure. If the transconductance of  $Q_1$  is  $8 \times 10^{-3} \text{ S}$  and  $Q_2$  is  $6 \times 10^{-3} \text{ S}$ , the overall transconductance  $g_m$  is \_\_\_\_\_.



- (A)  $14 \times 10^{-3} \text{ S}$   
 (B)  $2 \times 10^{-3} \text{ S}$   
 (C)  $3 \times 10^{-3} \text{ S}$   
 (D)  $6 \times 10^{-3} \text{ S}$
14. The feedback N/w of Hartley oscillator have  $L_1 = 10 \text{ mH}$ ,  $L_2 = 5 \text{ mH}$  and  $C = 100 \text{ PF}$ . The mutual inductance b/w  $L_1$  and  $L_2$  is  $2.5 \text{ mH}$ . The frequency of oscillation is \_\_\_\_\_.  
 (A) 0.13 MHz (B) 11.3 kHz  
 (C) 0.113 MHz (D) None


15. The expression for output collector current in a power amplifier is given by  
 $I_C = 4 \sin \omega t + 1.5 \sin 2 \omega t + 0.6 \sin 3 \omega t$  amp  
 The % increase in power due to harmonic distortion is \_\_\_\_\_.  
 (A) 16.2% (B) 30.5%  
 (C) 12% (D) 1.6%

**Common Data for Questions 16 to 18:** A power amplifier working in class A operation has a zero signal collector current of  $120 \text{ mA}$  at  $V_{CC} = 10 \text{ volt}$

16. The maximum ac Output power is \_\_\_\_\_.  
 (A) 0.3 W (B) 0.15 W  
 (C) 0.6 W (D) 1.2 W
17. The power rating of transistor is \_\_\_\_\_.  
 (A)  $\geq 1.2 \text{ W}$  (B)  $\geq 0.6 \text{ W}$   
 (C)  $\leq 1.2 \text{ W}$  (D)  $\geq 0.3 \text{ W}$
18. The power amplifier maximum collector efficiency is \_\_\_\_\_.  
 (A) 50% (B) 25%  
 (C) 78.5% (D) 18%


**Common Data for Questions 19 and 20:** A class B amplifier works on  $20 \text{ V}$  DC supply. The output impedance is  $10 \Omega$  and turn ratio is 5. The peak voltage across the load is  $15 \text{ V}$ .

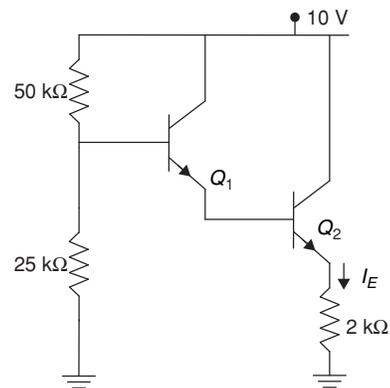19. The collector efficiency is \_\_\_\_\_.  
 (A) 28% (B) 50%  
 (C) 78.5% (D) 58.8%
20. The power rating of transistor is \_\_\_\_\_.  
 (A) 0.45 W (B) 0.225 W  
 (C) 4.5 W (D) 2.25 W
21. What is the emitter current  $I_E$  if  $\beta = 100$  and  $V_{BE} = 0.7 \text{ V}$  for each transistor of the Darlington pair given below



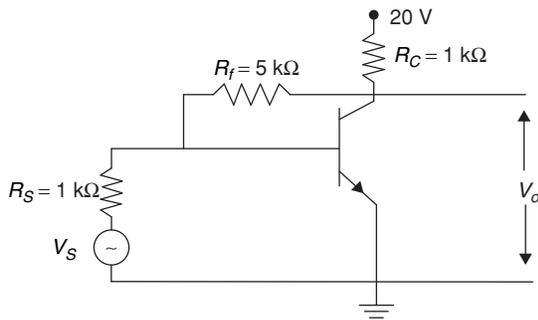
- (A) 1.5 mA (B) 0.964 mA  
 (C) 0.48 mA (D) None

**Common Data for Questions 22 to 24:** The feedback amplifier shown below has an open loop gain 1000.



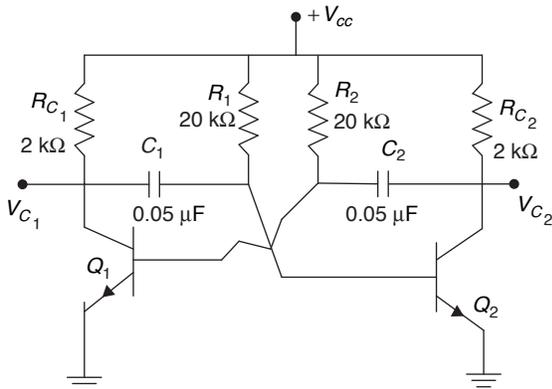22. What is the type of feedback employed?  
 (A) series-series feedback  
 (B) series-shunt feedback  
 (C) shunt-series feedback  
 (D) shunt-shunt feedback
23. The feedback ratio  $\beta$  is \_\_\_\_\_.  
 (A)  $1.6 \times 10^{-4}$  (B)  $1 \times 10^{-3}$   
 (C)  $2 \times 10^{-4}$  (D)  $0.2 \times 10^{-4}$
24. The closed loop gain  $A_f$  is \_\_\_\_\_.  
 (A) 833.3 (B) 100  
 (C) 1000 (D) None

**Common Data for Questions 25 and 26:** An astable multi vibrator is shown below



25. The frequency of square wave Output is \_\_\_\_\_.  
 (A) 7.24 kHz (B) 5 kHz  
 (C) 0.5 kHz (D) 0.724 kHz
26. The minimum value of  $h_{fe}$  of transistor to ensure oscillations is \_\_\_\_\_.  
 (A) 1 (B) 0.2  
 (C) 10 (D) 8
27. An astable multi vibrator using Si transistor is designed to generate a square wave of amplitude 12 V and frequency 1 kHz.

The transistor has


$h_{fe_{min}} = 40$ ,  $I_{C_{sat}} = 6$  mA and  $V_{CE_{sat}} = 0.2$  V. Assume  $R_1 = R_2 = R$ ,  $C_1 = C_2 = C$ , calculate the value of  $R$  and  $C$ .

- (A)  $R = 1.96$  kΩ  $C = 9$  nF  
 (B)  $R = 1.96$  kΩ  $C = 0.9$  μF  
 (C)  $R = 196$  Ω  $C = 9$  nF  
 (D)  $R = 196$  Ω  $C = 9$  μF
28. The AC power output of a class A amplifier is 4 W. If the collector efficiency is 45%, what is the power rating of transistor?  
 (A)  $\geq 8.9$  W  
 (B)  $< 8.9$  W  
 (C)  $\geq 4$  W  
 (D)  $< 4$  W
29. A class B push-pull amplifier uses 15 V DC supply, with sinusoidal input; a max peak to peak of 24 V is desired across a load of 100 Ω. What is the power dissipated by each transistor?  
 (A) 426 mW (B) 213 mW  
 (C) 1.146 W (D) 0.72 W
30. Match List I and List II:

List I	List II
P Class A amplifier	1 Hifidelity
Q Class B amplifier	2 Tuned amplifier
R Class C amplifier	3 Power amplifier
S Class AB amplifier	4 Low distortion power amplifier

	P	Q	R	S
(A)	4	3	2	1
(B)	1	2	3	4
(C)	4	2	3	1
(D)	1	3	2	4

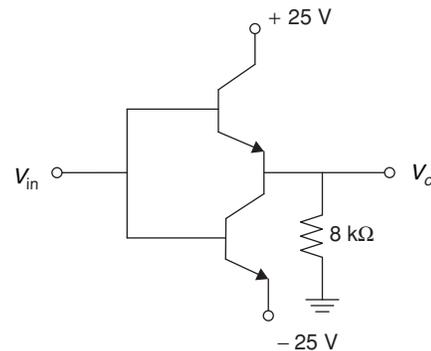
31. The circuit of a class B push pull amplifier is shown in the figure. If the peak output voltage  $V_o$  is 16 V. The power drawn from the DC source would be



- (A) 10 W (B) 15 W  
 (C) 27 W (D) 32 W

3.212 | Analog and Digital Electronics

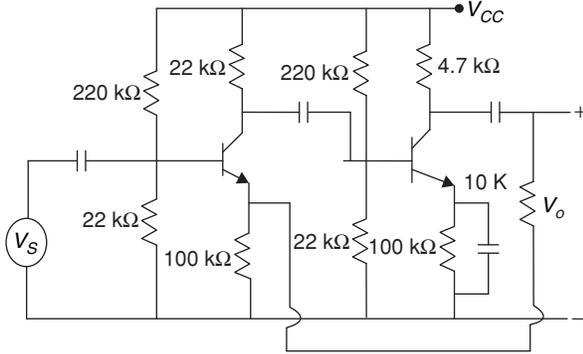**Common Data for Questions 32 to 34:** For the two stage feed back amplifier shown in figure  $h_{ie} = 1.1 \text{ k}\Omega$ ,  $h_{fe} = 50$




32. The nature of over-all feedback is?  
 (A) Voltage shunt  
 (B) Voltage series  
 (C) Current series  
 (D) Current shunt
33. The values of over-all gain without feedback, and feedback factor are  
 (A) 600 and 10  
 (B) 1163 and 10  
 (C) 600 and 12.5  
 (D) 1163 and 12.5
34. The values of overall input and output resistance with feedback are  
 (A) 6.2 kΩ and 3.3 kΩ  
 (B) 77.63 kΩ and 3.3 kΩ  
 (C) 77.63 kΩ and 0.25 kΩ  
 (D) 6.2 kΩ and 0.25 kΩ

**Common Data for Questions 35 to 39:** A differential amplifier is shown below with following specifications.

$$R_{C_1} = R_{C_2} = 2.2 \text{ k}\Omega, R_E = 4.5 \text{ k}\Omega, \beta = 100, V_{BE} = 0.7 \text{ V}$$

And  $r_e = 28 \Omega$

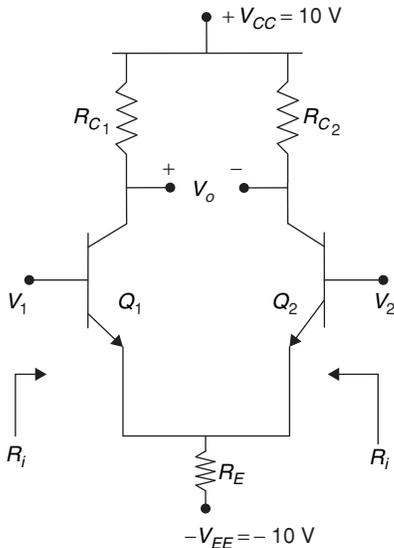

35. The input resistance  $R_i$  seen from each source is  
 (A) 5.6 kΩ  
 (B) 28 Ω  
 (C) 1.4 kΩ  
 (D) 2.8 kΩ


36. The output resistance  $R_o$  is  
 (A) 6.9 kΩ  
 (B) 4.7 kΩ  
 (C) 2.2 kΩ  
 (D) None

37. The differential mode gain is  
 (A) 39.3  
 (B) 78.5  
 (C) 0.48  
 (D) ∞

38. The common mode gain  $A_c$  is  
 (A) 0.48  
 (B) 0.24  
 (C) 0.97  
 (D) 0


39. CMRR in dB is  
 (A) 50.29 dB  
 (B) 25.14 dB  
 (C) 2.51 dB  
 (D) 44.27 dB

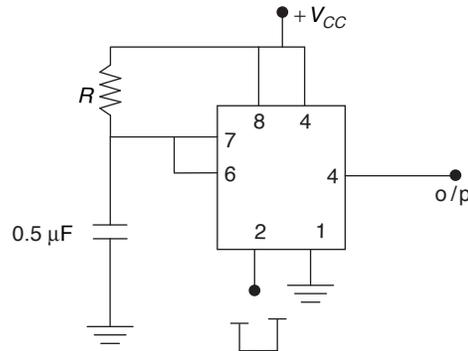40. A monostable multi vibrator is shown below. What is the value of  $R$  required for output rectangular frequency of 500 Hz.




- (A) 5.8 kΩ  
 (B) 3.63 kΩ  
 (C) 6.2 kΩ  
 (D) 9.1 kΩ

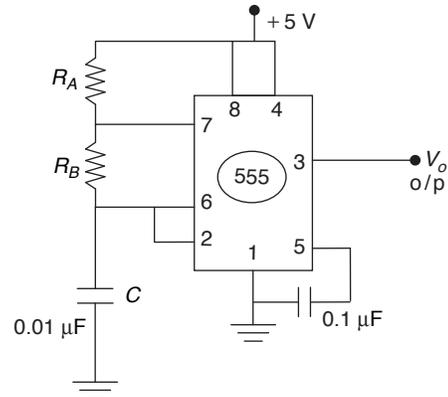41. An astable multivibrator using IC 555 timer is given below; generate a square pulse of frequency 1 kHz with duty cycle 60%, what is the Relation between  $R_A$  and  $R_B$ ?



- (A)  $R_B = R_A$   
 (B)  $R_B = \frac{R_A}{2}$   
 (C)  $R_B = 2R_A$   
 (D)  $R_B = \frac{R_A}{3}$

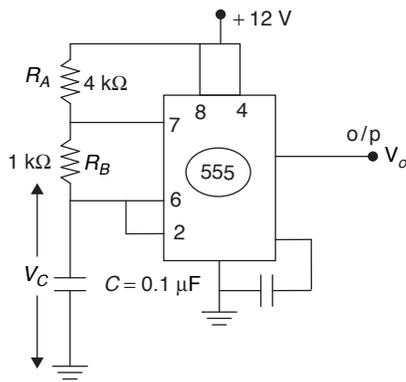42. An astable multivibrator using IC 555 is given below



The capacitor voltage  $V_c$  limits are

- (A) 12 V and -12 V
- (B) 4 V and -4 V
- (C) 4 V and 8 V
- (D) 8 V and -8 V

43. The frequency of output is

- (A) 2.4 kHz
- (B) 1 kHz
- (C) 1.2 kHz
- (D) None of these

### Practice Problems 2

**Directions for questions 1 to 27:** Select the correct alternative from the given choices.


1. An amplifier with -ve feedback has a voltage gain of 80, without feedback, an input signal of 40 mV is required to produce a given output where as with feedback; the input signal must be 0.5 V for the same output. The feedback ratio  $\beta$  is \_\_\_\_\_.
  - (A) 1.5%
  - (B) 1.15%
  - (C) 10%
  - (D) 6.25%
2. An amplifier gives 1000 mV output with input of 1 mV without feedback. The desensitivity factor with negative feedback is 10. The feedback ratio  $\beta$  is \_\_\_\_\_.
  - (A)  $2 \times 10^{-3}$
  - (B)  $9.9 \times 10^{-2}$
  - (C)  $1 \times 10^{-2}$
  - (D)  $9 \times 10^{-3}$
3. The open loop gain of amplifier is  $1000 \pm 200$  and feedback ratio is 4.2%, the % change in negative feedback gain is \_\_\_\_\_.
  - (A) 2.1%
  - (B) 4.2%
  - (C) 0.46%
  - (D) None
4. An amplifier has  $A = 48000$  and  $A_f = 6000$ . The amounts of feedback in dB and feedback factor  $\beta$  are \_\_\_\_\_ respectively.
  - (A) 18.06 dB, 1.45%
  - (B) 18.06 dB,  $0.145 \times 10^{-3}$
  - (C) 8 dB,  $0.145 \times 10^{-3}$
  - (D) 8 dB, 1.45%

**Common Data for Questions 5 and 6:** The total harmonic distortion of an amplifier is reduced from 20% to 8% when 5% negative feedback is used.

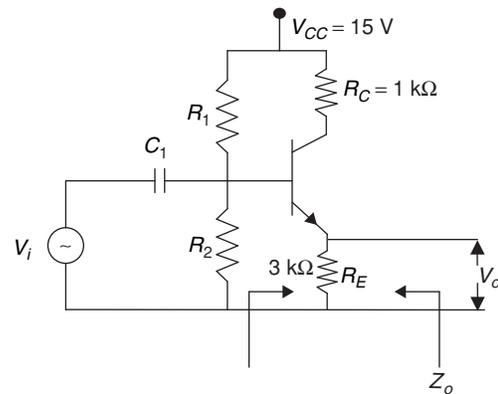5. The voltage gain without feedback is \_\_\_\_\_.
  - (A) 12
  - (B) 3
  - (C) 18
  - (D) 30
6. The voltage gain with negative feedback is \_\_\_\_\_.
  - (A) 1.2
  - (B) 30
  - (C) 8
  - (D) 12

**Common Data for Questions 7 to 10:** An emitter follower has following specifications.

$$h_{ie} = 1000 \Omega, h_{fe} = 100 \text{ and } R_1 \parallel R_2 = 10 \text{ k}\Omega$$




7. The voltage gain without feedback is \_\_\_\_\_.
  - (A) 1
  - (B) 300
  - (C) 101
  - (D)  $\infty$
8. The voltage gain with feedback is \_\_\_\_\_.
  - (A) 0.99
  - (B) 0.85
  - (C) 30
  - (D) None
9. The input and output impedance are \_\_\_\_\_.
  - (A)  $Z_i = 304 \text{ k}\Omega$  and  $Z_o = 10 \Omega$
  - (B)  $Z_i = 10 \Omega$  and  $Z_o = 304 \text{ k}\Omega$
  - (C)  $Z_i = 1.3 \text{ k}\Omega$  and  $Z_o = 3 \text{ k}\Omega$
  - (D)  $Z_i = 1 \text{ k}\Omega$  and  $Z_o = 3 \text{ k}\Omega$
10. Current gain  $A_i$  is \_\_\_\_\_.
  - (A) 25
  - (B) 101
  - (C) 0.98
  - (D) 3

**Common Data for Questions 11 to 14:** Each transistor in the Darlington pair has following specifications

$$h_{fe} = 99, h_{ie} = 1 \text{ k}\Omega$$

3.214 | Analog and Digital Electronics

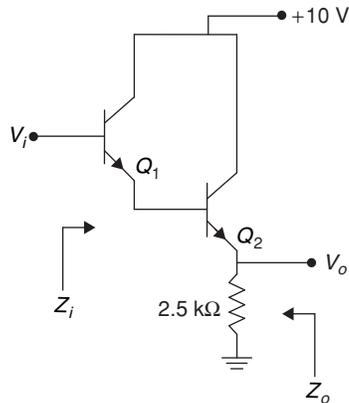

11. The input impedance  $Z_i$  is \_\_\_\_\_.  
 (A)  $2.5\text{ k}\Omega$  (B)  $25\text{ M}\Omega$   
 (C)  $2.5\text{ M}\Omega$  (D)  $25\text{ }\Omega$
12. The output impedance  $Z_o$  is \_\_\_\_\_.  
 (A)  $2.5\text{ k}\Omega$  (B)  $1\text{ k}\Omega$   
 (C)  $100\text{ }\Omega$  (D)  $10.1\text{ }\Omega$
13. Current gain  $A_i$  is \_\_\_\_\_.  
 (A)  $10^2$  (B)  $10^4$   
 (C) 1 (D) 10
14. Voltage gain  $A_v$  is \_\_\_\_\_.  
 (A) 0.8 (B) 10  
 (C) 1 (D) 12
15. An amplifier has a gain of 60 dB without feedback. What is the % loss in gain if  $\frac{1}{50}$  of Output is feedback to input in out of phase?  
 (A) 4.76% (B) 8.3%  
 (C) 1% (D) 15%
16. In a certain amplifier, an output of 40 V is obtained when the input signal is 0.4 V. If 20% of the output is feedback to input in out of phase, by what value is the input signal to be changed so that the Output voltage remains constant?  
 (A) 10 V (B) 0.4 V  
 (C) 6 V (D) 8.4 V
17. In an astable multi vibrator each transistor is cutoff for 1m sec. The frequency of square wave output is \_\_\_\_\_.  
 (A) 500 Hz (B) 1 kHz  
 (C) 2 kHz (D) None
18. A transformer coupled class A amplifier has a turn ratio of 6:1 and the load is  $25\text{ }\Omega$ . If the zero signal collectors current is 80 mA, the maximum AC Output power is \_\_\_\_\_.  
 (A) 1.4 W (B) 2.88 W  
 (C) 5 W (D) 0.8 W

**Common Data for Questions 19 and 20:** An amplifier has voltage gain with feedback 50. If the gain without feedback change by 10% and the gain with feedback should not vary more than 1%.


19. The value of open loop gain  $A$  is \_\_\_\_\_.  
 (A) 500 (B) 250  
 (C) 1000 (D) 125
20. The feedback ratio  $\beta$  is \_\_\_\_\_.

- (A) 0.9% (B) 0.45%
- (C) 2.2% (D) 1.8%

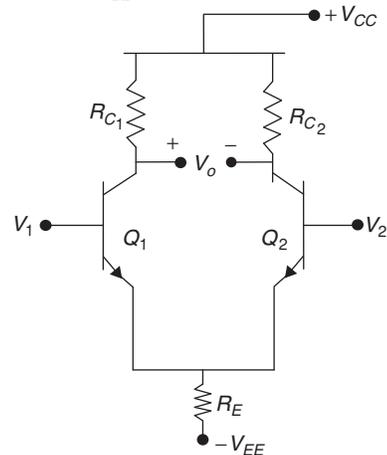21. An amplifier has 10% non linear distortion generated in its output stage. The amplifier gain without feedback is 200. If the distortions are reduced to 2% with negative feedback, the feedback ratio is \_\_\_\_\_.  
 (A) 0.5 (B) 0.2  
 (C) 0.02 (D) 1
22. Calculate the value of the capacitors to be used in astable multi vibrator to provide a train of pulse  $4\text{ }\mu\text{s}$  wide at a repetition rate of 80 kHz if  $R_1 = R_2 = 10\text{ k}\Omega$ .  
 (A)  $C_1 = 0.58\text{ nF}$  and  $C_2 = 0.58\text{ nF}$   
 (B)  $C_1 = 1.23\text{ nF}$  and  $C_2 = 1.23\text{ nF}$   
 (C)  $C_1 = 0.58\text{ nF}$  and  $C_2 = 1.23\text{ nF}$   
 (D)  $C_1 = 1.23\text{ nF}$  and  $C_2 = 0.58\text{ nF}$
23. A power transistor used in class A amplifier is transformer coupled to a load of  $10\text{ }\Omega$ . If the signal has peak to peak swing of 200 mA and transformer turn ratio of 10, the AC Output power is \_\_\_\_\_.  
 (A) 5 W (B) 50 mW  
 (C) 10 W (D) 2.5 W

**Common Data for Questions 24 to 26:** A differential amplifier is shown below, has following specifications.


$R_{C1} = R_{C2} = 1.8\text{ k}\Omega$ ,  $R_E = 4\text{ k}\Omega$ ,  $V_{CC} = 10\text{ V}$ ,  $-V_{EE} = -10\text{ V}$ ,  $\beta = 100$  and  $V_{BE} = 0.7\text{ V}$



24. The emitter current  $I_E$  is  
 (A) 2.3 mA (B) 1.16 mA  
 (C) 1.7 mA (D) 0.98 mA
25. The differential mode voltage gain  $A_d$  is  
 (A) 10 (B) 8  
 (C) 80 (D) 40
26. What is the output  $V_o$  if  $V_1 = 30\text{ mV}$  and  $V_2 = 40\text{ mV}$   
 (A) 0.8 V (B) 5.6 V  
 (C) 2.8 V (D) 0 V
27. In the mono stable multivibrator using IC555 timer, the external circuit elements connected is  $C = 0.01\text{ }\mu\text{F}$  and  $R = 2.7\text{ k}\Omega$ . Calculate the duration of output pulse width.  
 (A) 18.6  $\mu\text{s}$  (B) 29.7  $\mu\text{s}$   
 (C) 37.2  $\mu\text{s}$  (D) None






PREVIOUS YEARS' QUESTIONS

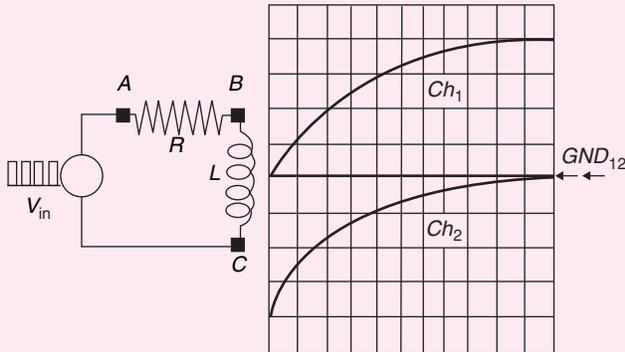1. The probes of a non-isolated, two-channel oscilloscope are clipped to points  $A$ ,  $B$  and  $C$  in the circuit of the adjacent figure.  $V_{in}$  is a square wave of a suitable low frequency. The display on  $Ch_1$  and  $Ch_2$  are as shown on the right. Then the 'Signal' and 'Ground' probes  $S_1, G_1$  and  $S_2, G_2$  of  $Ch_1$  and  $Ch_2$  respectively are connected to points. [2007]




- (A)  $A, B, C$  and  $A$                       (B)  $A, B, C$  and  $B$   
 (C)  $C, B, A$  and  $B$                       (D)  $B, A, B$  and  $C$

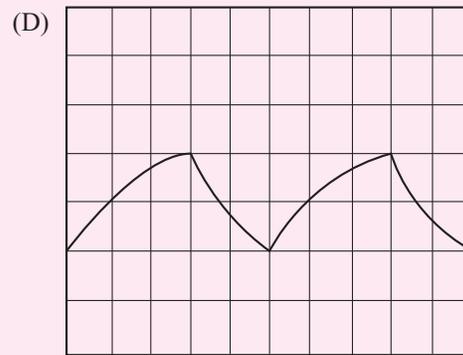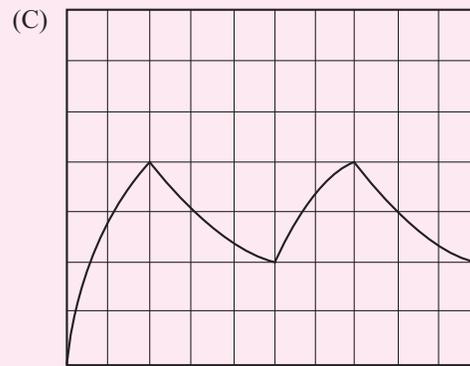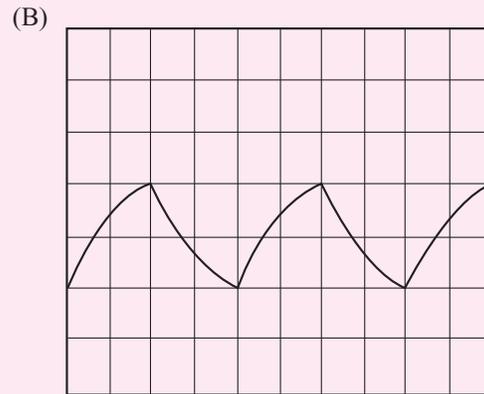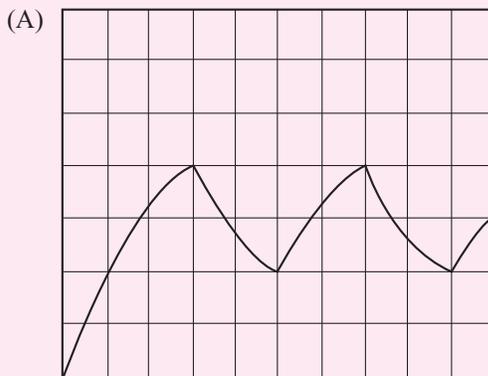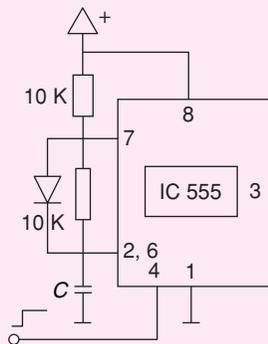2. IC 555 in the adjacent figure is configured as an astable multi-vibrator. It is enabled to oscillate at  $t = 0$  by applying a high input to pin 4. The pin description is: 1 and 8—supply; 2—trigger; 4—reset; 6—threshold; 7—discharge. The waveform appearing across the capacitor starting from  $t = 0$ , as observed on a storage CRO is [2007]



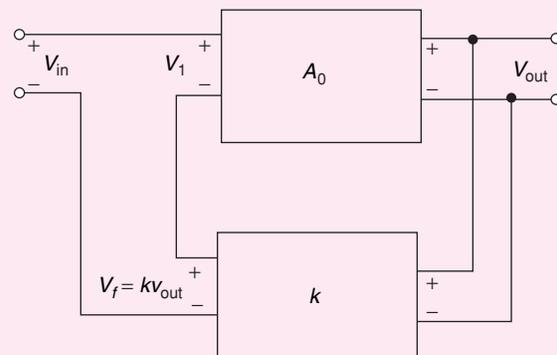3. In the feedback network shown below, if the feedback factor  $k$  is increased, then the [2013]



### 3.216 | Analog and Digital Electronics

- |   |  |
|---|--|
| (A) Input impedance increases and output impedance decreases.     | (C) Input impedance decreases and output impedance also decreases. |
| (B) Input impedance increases and output impedance also increases | (D) Input impedance decreases and output impedance increases.      |

## ANSWER KEYS

### EXERCISES

#### Practice Problems 1

- |       |       |       |       |       |       |       |       |       |       |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. A  | 2. C  | 3. D  | 4. C  | 5. A  | 6. B  | 7. C  | 8. A  | 9. B  | 10. C |
| 11. D | 12. A | 13. C | 14. C | 15. A | 16. C | 17. A | 18. A | 19. D | 20. B |
| 21. B | 22. D | 23. C | 24. A | 25. D | 26. C | 27. A | 28. A | 29. B | 30. D |
| 31. D | 32. B | 33. D | 34. C | 35. C | 36. C | 37. B | 38. B | 39. A | 40. B |
| 41. C | 42. C | 43. A |       |       |       |       |       |       |       |

#### Practice Problems 2

- |       |       |       |       |       |       |       |       |       |       |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 1. B  | 2. D  | 3. C  | 4. B  | 5. D  | 6. D  | 7. B  | 8. A  | 9. A  | 10. B |
| 11. B | 12. D | 13. B | 14. C | 15. A | 16. D | 17. A | 18. B | 19. A | 20. D |
| 21. C | 22. C | 23. A | 24. B | 25. C | 26. A | 27. B |       |       |       |

#### Previous Years' Questions

- |      |      |      |
|------|------|------|
| 1. B | 2. A | 3. A |
|------|------|------|