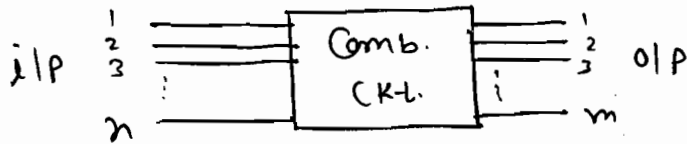


★

Digital Circuits

Combinational Ckt

Sequential Ckt.



→ Outputs = $F(\text{Present I/P})$


E.g. = Code Converter,

Adder & Subtractor,

Decoder, Mux,

Mag. Comparators, PLA,

✓ Rom

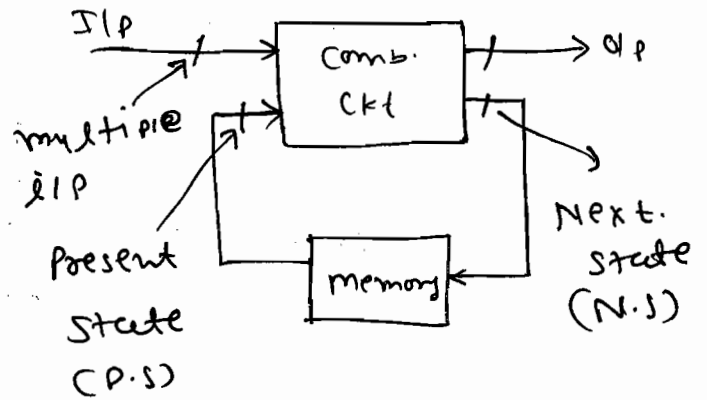

$O/P = F(\text{present state, present inputs})$

$\text{Next state} = F(\text{present state, present I/P.})$

→ Mooore Seq Ckt.

$O/P = F(\text{present state only})$


$N.S. = F(\text{present Inputs, present state}).$

E.g. Shift register,
Counters, calculators,
MP, PC.

* Arithmetic Combinational Ckt.

53

(1) Half Adder:

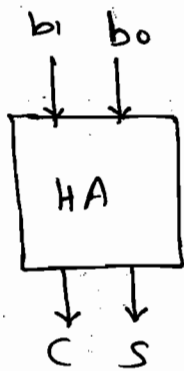


A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

$$S = \bar{A}B + A\bar{B}$$

$$S = A \oplus B$$


$$C = A \cdot B$$

⇒ Half Adder using NAND Gates.

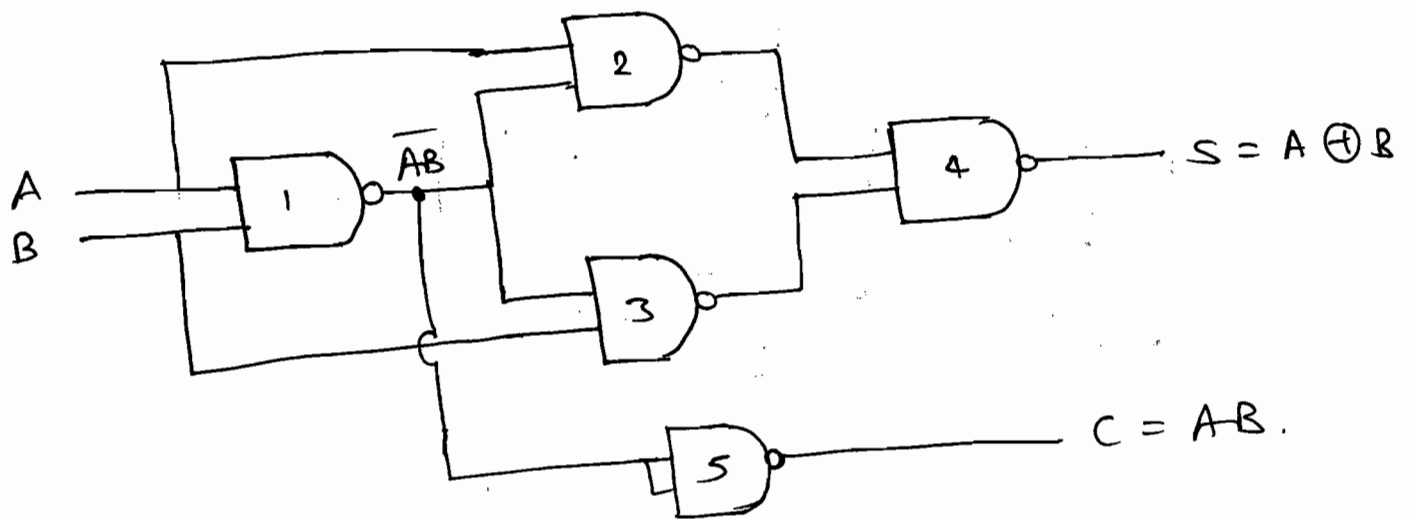


So, ⑤ NAND gate required.

⇒ Half Adder using NOR gate

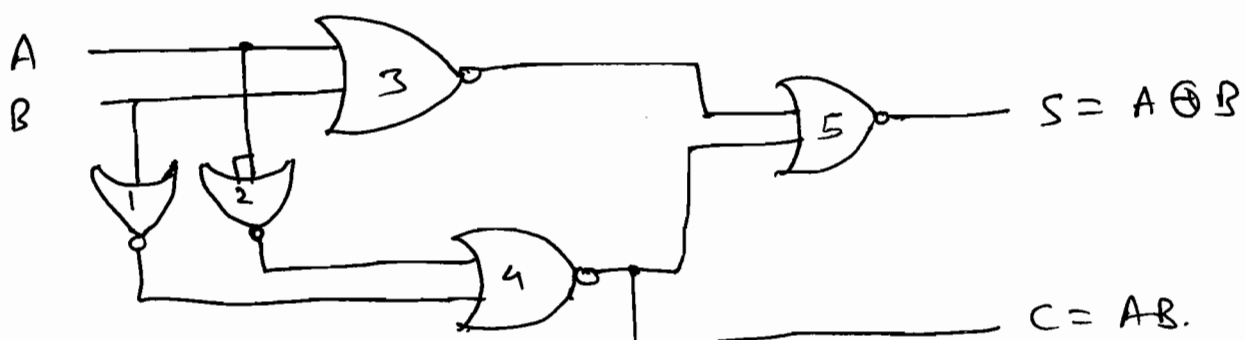

So, ⑤ NOR gate required

(2) Half Subtractor:

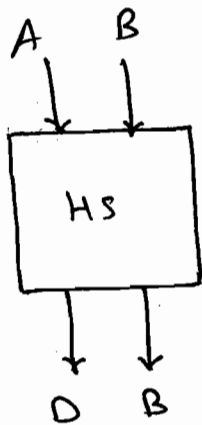


A	B	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

$$D = A \oplus B$$

$$B = \bar{A} \cdot B$$


$$\begin{array}{r} 10 \\ B - 1 \\ \hline 1 \rightarrow D \end{array}$$

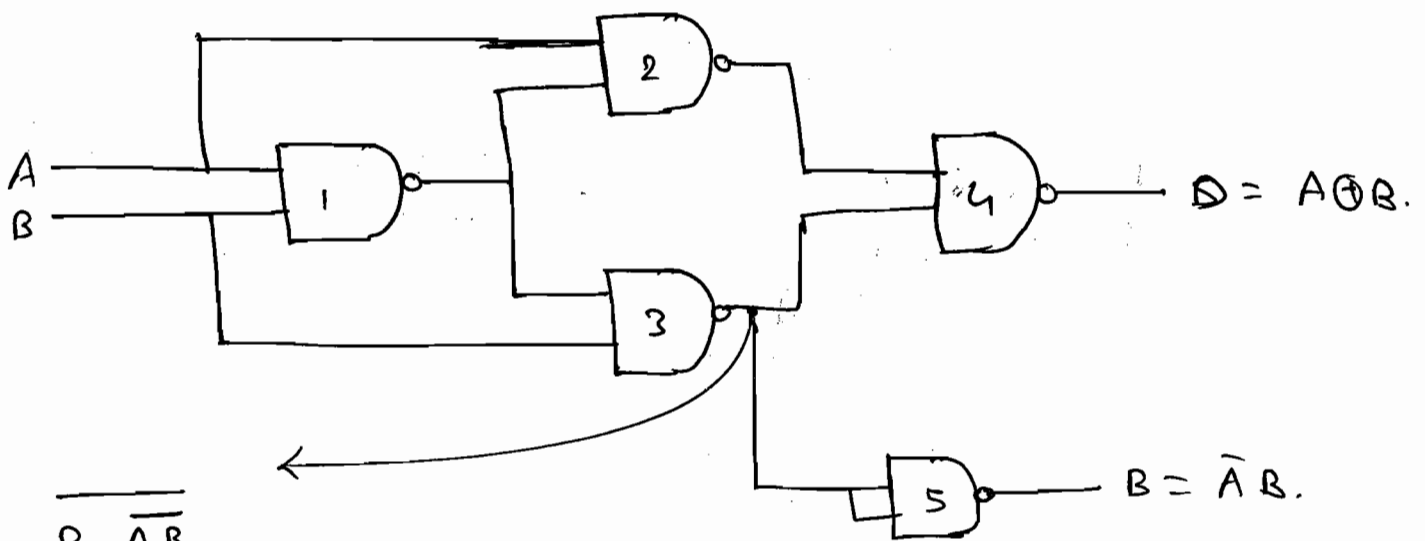⇒ Half Subtractor ~~using~~ using NAND gate only:




$$\begin{aligned} & \overline{B \cdot \bar{A} B} \\ &= \bar{B} + AB \\ &= A + \bar{B} = \overline{\bar{A} \cdot B} \end{aligned}$$

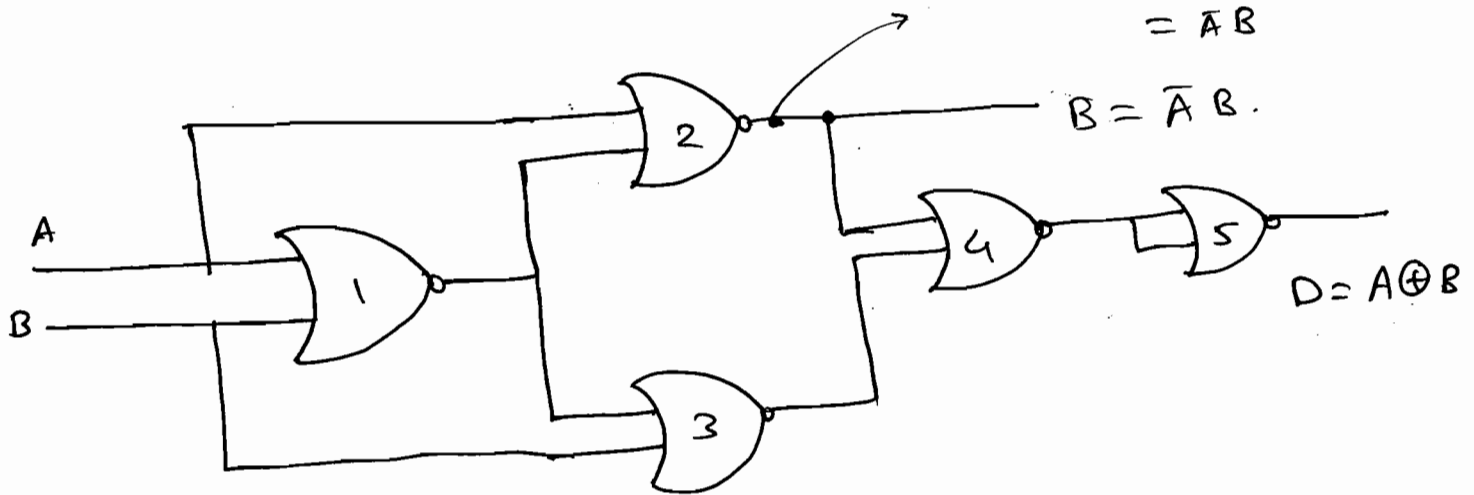
⇒ Half Subtractor using NOR gate only. 65



(3) Full Adder: (1 bit adder).

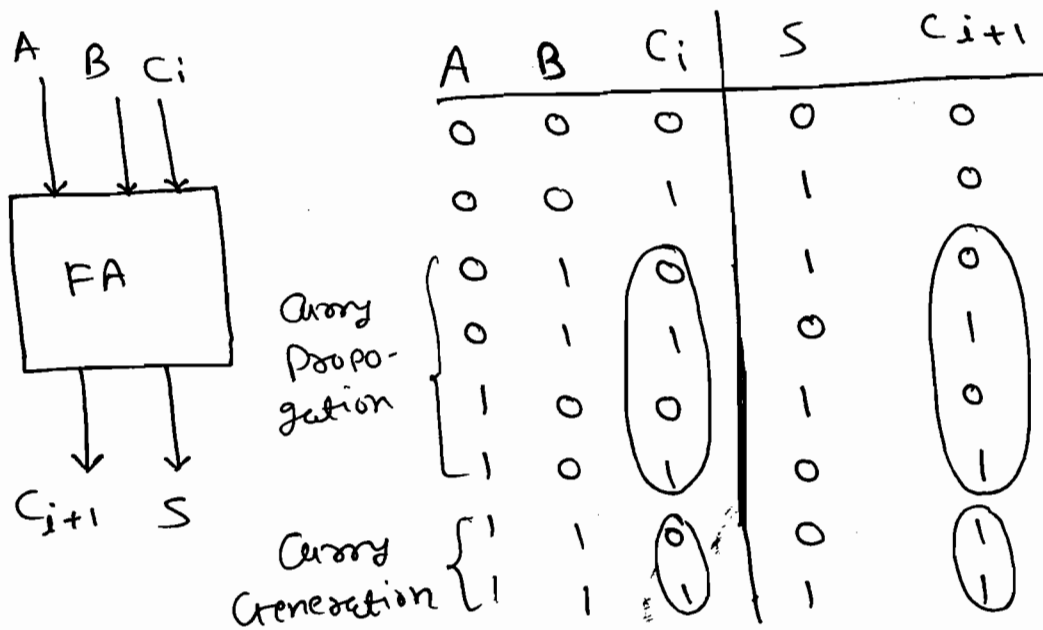

$$S(A, B, C_i) = \sum m(1, 2, 4, 7)$$

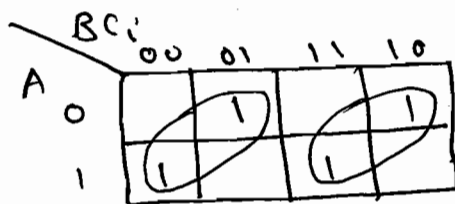

$$S = A \oplus B \oplus C_i \quad (\text{or}) \quad A \odot B \odot C_i$$

$$C_{i+1} = \sum m(3, 5, 6, 7)$$

$$= \bar{A}BC_i + A\bar{B}C_i + AB\bar{C}_i + ABC_i$$

$$= C_i (\bar{A}B + A\bar{B}) + AB$$

$$\therefore C_{i+1} = C_i (A \oplus B) + AB$$

	BC_i			
	00	01	11	10
A				
0			1	
1		1	1	1


$$C_{i+1} = AB + BC_i + AC_i$$

NOTE: Full adder

- (i) Require 9 NAND gate
- (ii) Require 12 NOR gate.

(4) Full Subtractor:

→

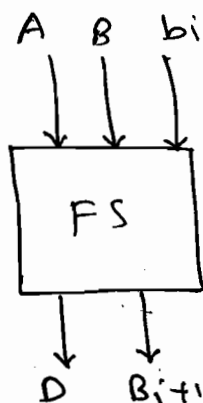

A	B	bi	D	bi+1
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

$$\rightarrow D(A, B, b_i) = \sum m(1, 2, 4, 7).$$

	Bb_i			
	00	01	11	10
A				
0	0	1	1	1
1	1	1	1	1

$$D = A \oplus B \oplus b_i \text{ (or) } A \odot B \odot b_i.$$

$$\rightarrow b_{i+1}(A, B, b_i) = \sum m(1, 2, 3, 7).$$

$$b_{i+1} = m_1 + m_2 + m_3 + m_7$$

$$= \bar{A}\bar{B}b_i + \bar{A}B\bar{b}_i + \bar{A}Bb_i + ABb_i$$

$$= b_i(\bar{A}\bar{B} + AB) + \bar{A}B.$$

$$b_{i+1} = b_i(A \odot B) + \bar{A}B.$$

	Bb_i			
	00	01	11	10
A				
0	0	1	1	1
1	0	1	1	0

$$\therefore b_{i+1} = \bar{A}B + Bb_i + \bar{A}b_i$$


NOTE: Full subtractor

(i) Required 9 NAND gate


(ii) Required 12 NOR gate.

Ex-1 Implement Full Adder using HAs and Logic gate:

Ans:

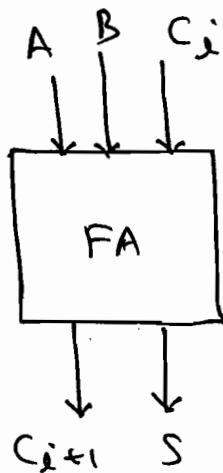

$\equiv$

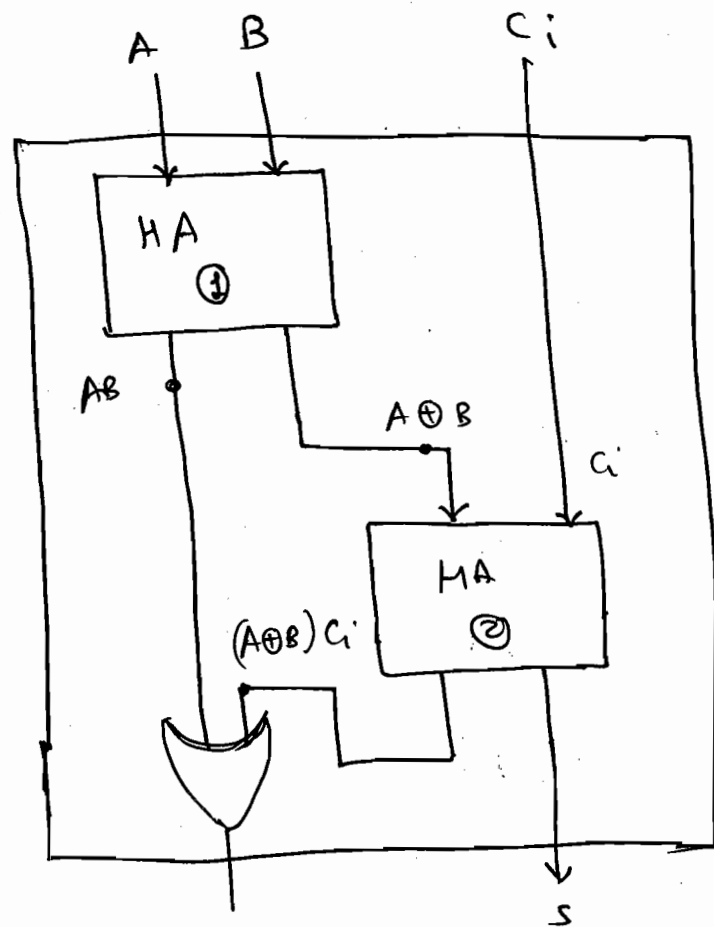

$$C_{i+1} = AB + C_i(A \oplus B)$$

1 Full adder = 2 Half adder + 1 OR gate

Ex-2 How many HA required to implement the following bⁿ.s.

$$F_1 = \bar{A}C + AB\bar{C} + \bar{B}C.$$

$$F_2 = A \oplus B \oplus C.$$

$$F_3 = \bar{A}BC + A\bar{B}C.$$

Ans: (i) $F_1 = \bar{A}C + AB\bar{C} + \bar{B}C.$

$$= \overline{AB} \cdot C + AB\bar{C}$$

$$= (\overline{A \cdot B}) \cdot C$$


$$X = \overline{AB}$$

$$= \bar{X} \cdot C + X\bar{C}$$

$$F_1 = A \cdot B \oplus C \rightarrow$$

For (ii) $F_2 = A \oplus B \oplus C.$

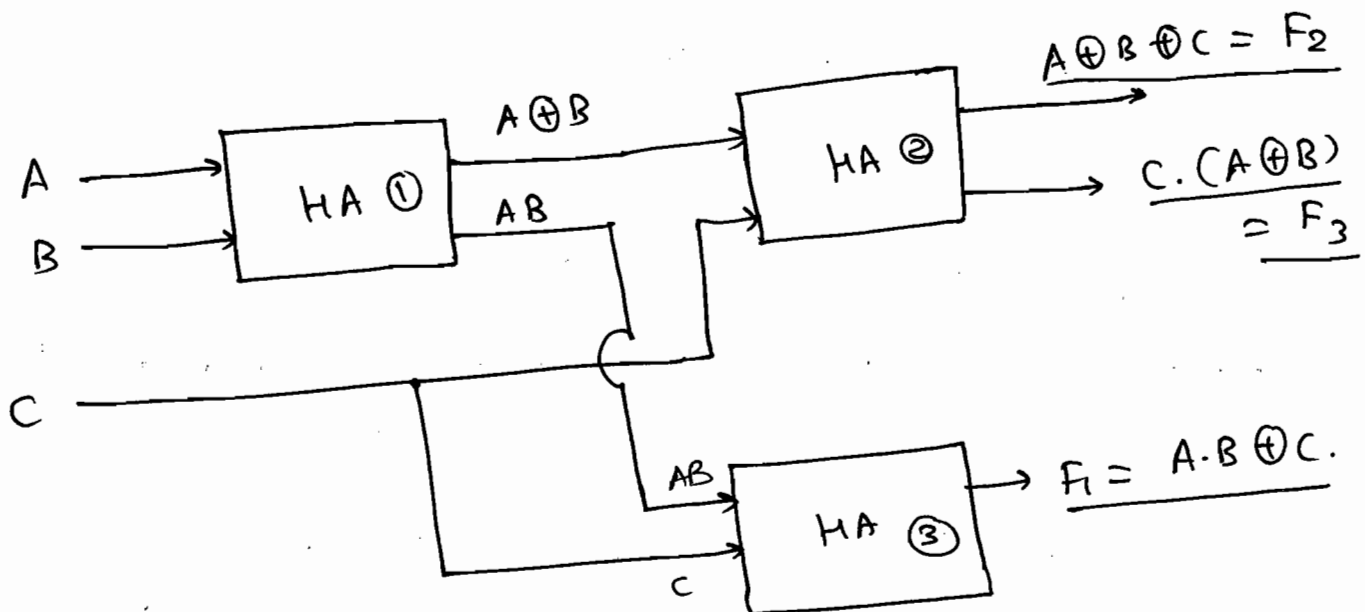(iii) $F_3 = (\bar{A}B + A\bar{B})C = C \cdot (A \oplus B)$



* Binary Adder:

- (1) Parallel binary Adder:
- (2) Carry Look Ahead Adder:
- (3) Serial Adder.

(1) Parallel binary Adder: (4 bit):


→ ~~IC = 74LS83~~

[IC = 74LS83]

$$\begin{array}{r}
 A = A_4 \ A_3 \ A_2 \ A_1 \\
 + B_4 \ B_3 \ B_2 \ B_1 \\
 \hline
 C_5 \ S_4 \ S_3 \ S_2 \ S_1
 \end{array}$$

$\xrightarrow{\text{FA}}$
 $\xrightarrow{\text{HA (OR) FA}}$

~~IC = 74LS83~~ + 3 FA + 1 HA (OR)
4 FA

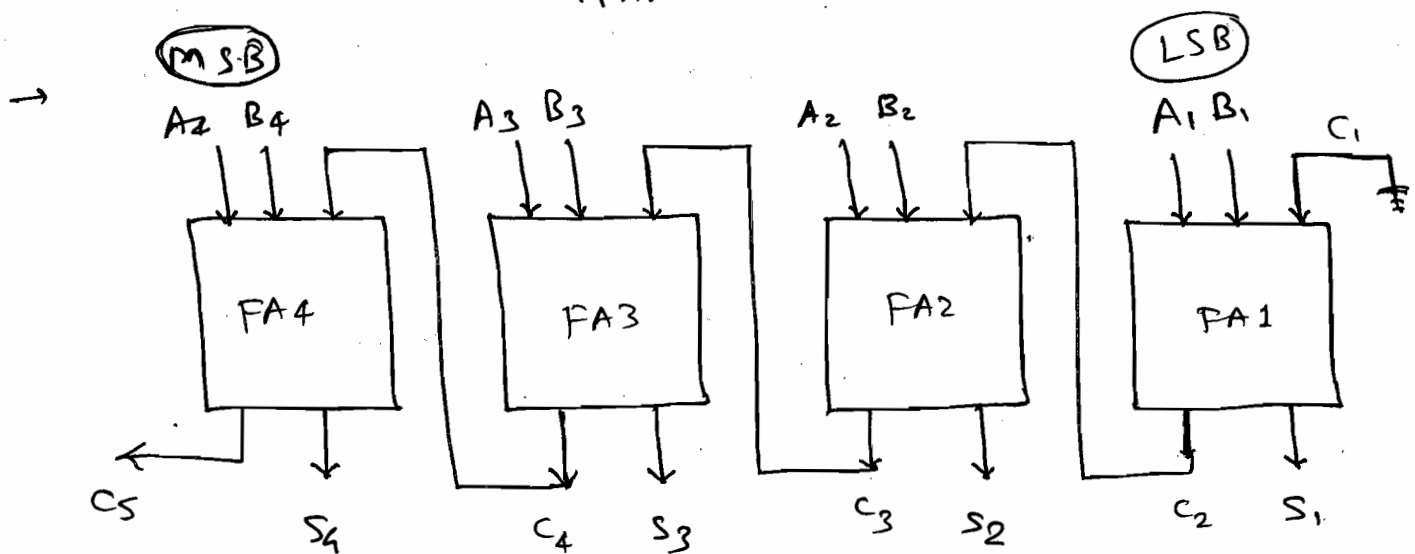

Q: how many HA. required to implement 4-bit parallel adder

Ans: 7 HA &
3 OR gate

Q.

→ In a 4 bit parallel binary adder a FA takes 32 ns to produce the sum and 14 ns to produce the carry. Determine

- Time required for addition.
- the addition rate of the adder.

Ans:

a)

Time required for Addition in N-bit parallel adder = $T = (N-1)t_c + \max(t_s, t_c)$.

$$\Rightarrow T = (4-1)14 + \max(32, 14)$$

$$= 42 + 32$$

$$T = 74 \text{ ns}$$

b)

$$\text{Addition Rate} = \frac{1}{T} = \frac{1}{74 \times 10^{-9}} \text{ Hz}$$

→ This can be used upto 4 bit.



→ Disadvantages:

→ as the size of the Adder increases the Speed operation decreases as the carry

✓ has to propagate through all the FAs to overcome this we use Carry Look ahead Adder.

(2) Carry Look Ahead Address:

→ Principle:

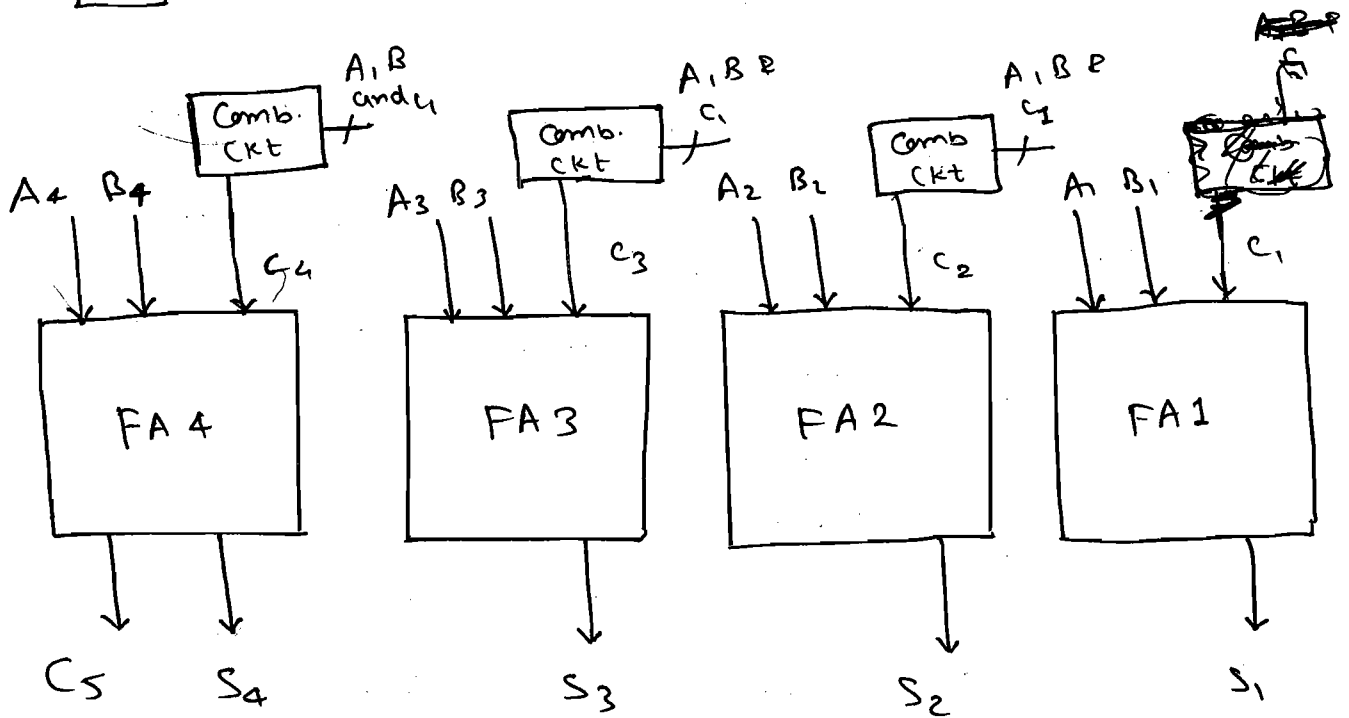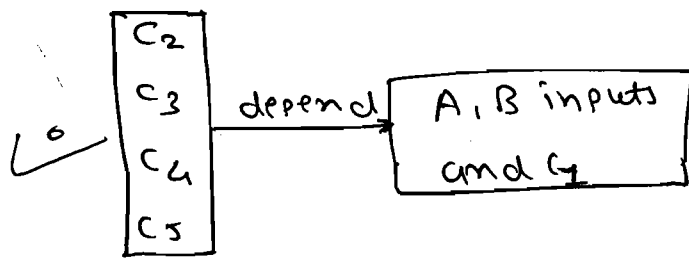

$$\rightarrow C_{i+1} = C_i (A \oplus B) + AB$$

$$P_i = A \oplus B = \text{Propagation of carry}$$

$$C_i = AB = \text{Carry generation}$$

$$\therefore C_{i+1} = C_i P_i + C_i$$

$$\rightarrow \boxed{C_2 = C_1 P_1 + C_1} \quad - \textcircled{1}$$



$$\rightarrow C_3 = C_2 P_2 + C_2$$

$$\boxed{C_3 = C_1 P_1 P_2 + C_1 P_2 + C_1} \quad - \textcircled{2}$$

$$\rightarrow C_4 = C_3 P_3 + C_3$$

→ $C_4 = C_1 P_1 P_2 P_3 + C_1 P_2 P_3 + C_2 P_3 + C_3$ — ③ 73

*

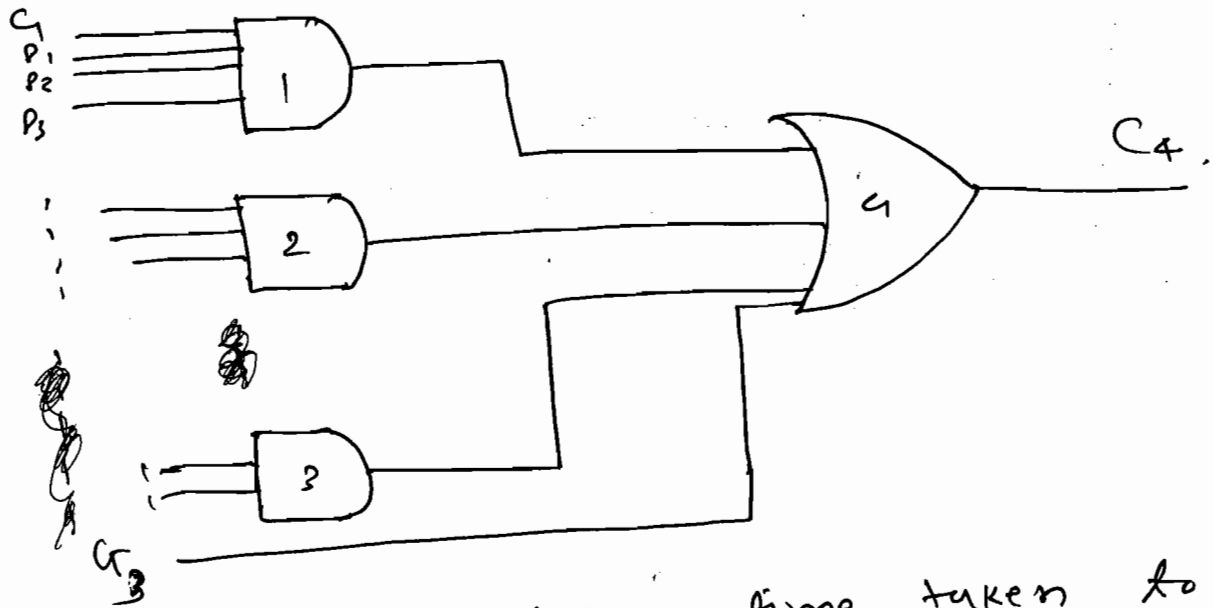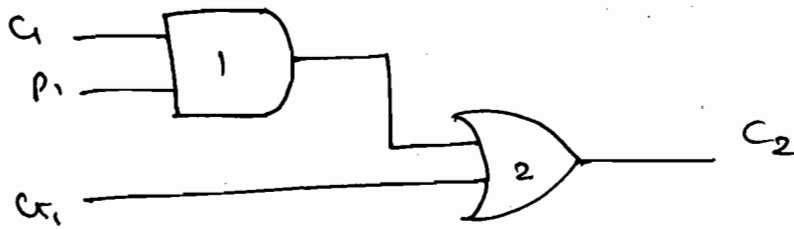

→ In Carry Look-Ahead time taken to generate the carries C_2, C_3, C_4 is same as they are implemented by 2 level Logic.


* Advantage:

→ Its Speed of operation is very high and doesn't depend on the size of the adder.

* Disadvantage:

→ It has more hardware complexity. To overcome this we use carry look ahead generator IC.

⇒ Carry Look Ahead generator IC

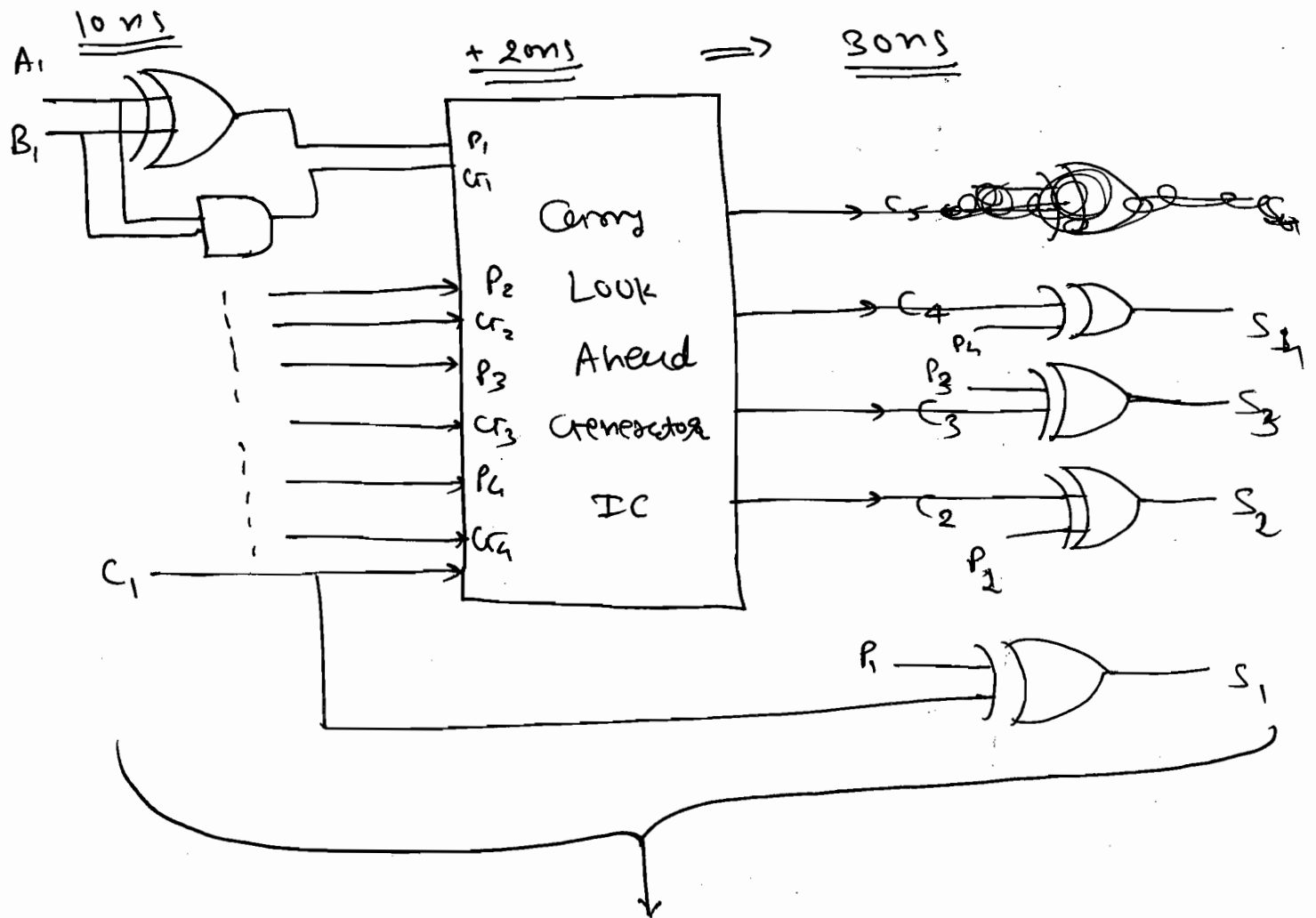

Carry Look Ahead Adder

$$S_i = A_i \oplus B_i \oplus C_i$$

$$S_i = P_i \oplus C_i$$

$$S_1 = P_1 \oplus C_1$$



$$S_2 = P_2 \oplus C_2$$

$$S_3 = P_3 \oplus C_3$$

$$S_4 = P_4 \oplus C_4$$

(3) Serial Adder: (sequential CKT)


75

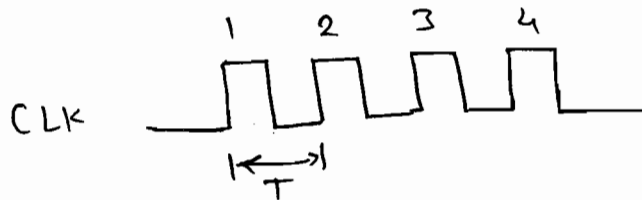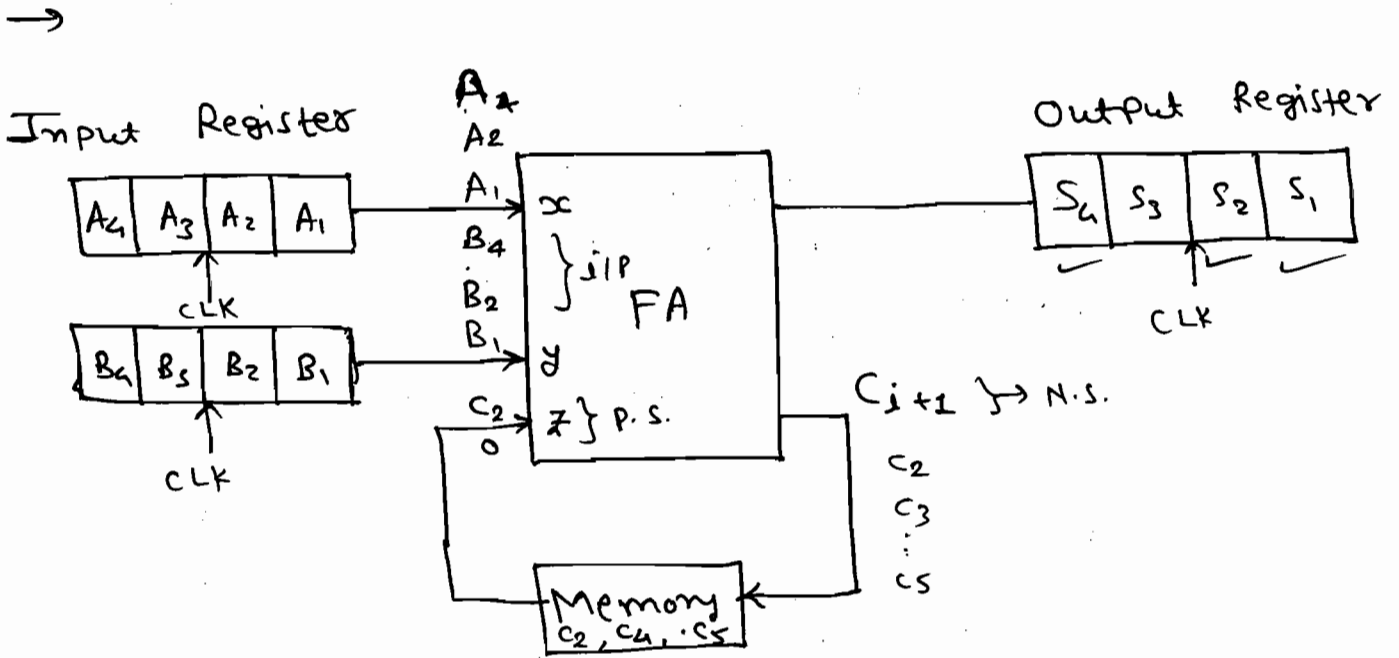

$T = \text{CLK period}$

Time for 4-bit serial addition = $4T$

* 4-bit Parallel Adder/Subtractor

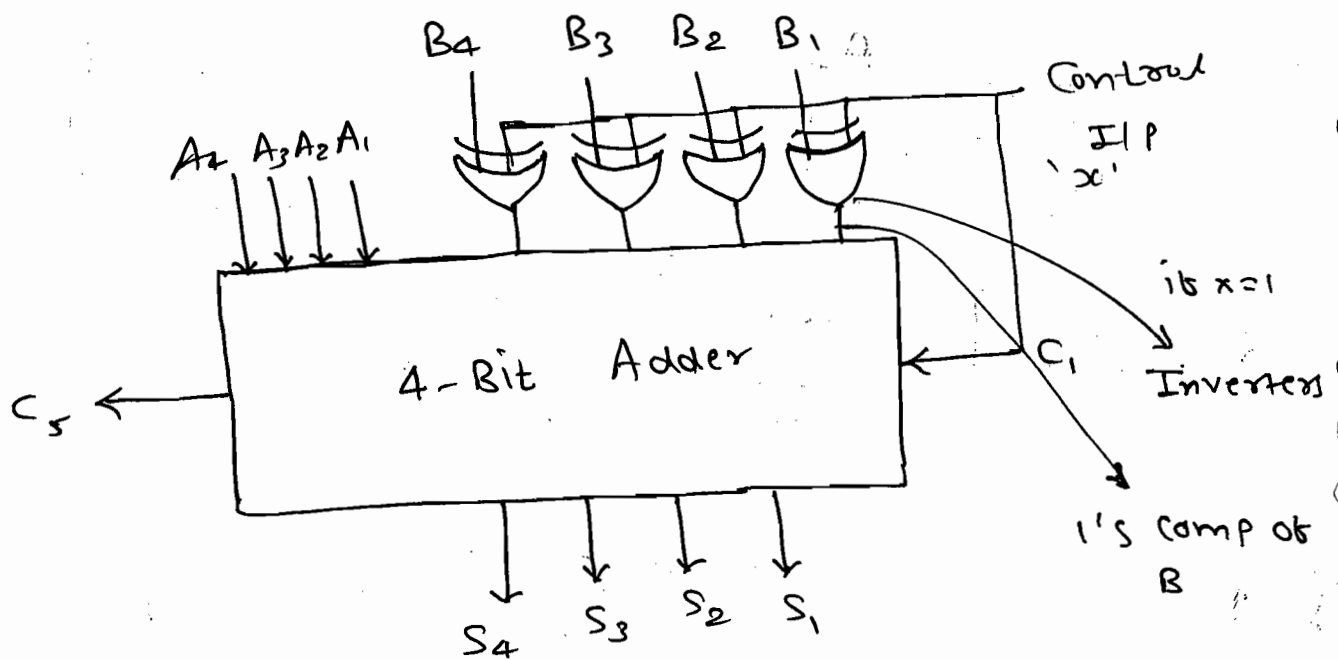

(1) If $x=1 \Rightarrow$ Ex-OR gate $\rightarrow$ Inverters

$\rightarrow A + 1's \text{ Comp of } B + (C_1=1)$

$\rightarrow A + (2's \text{ Comp of } B)$

$\Rightarrow \boxed{A - B} \rightarrow \boxed{\text{Binary Subtraction}}$

(2) If $x=0 \Rightarrow$ Ex-OR gate $\Rightarrow$ Buffer

$\rightarrow A + B + (C_1=0)$

$= \boxed{A + B} \rightarrow \boxed{\text{Binary Adding}}$

Ex-1 Determine the f^n of the above 77 circuit if the inputs are as given below:

① $x=1$; $A = \text{Ex-3 code}$; $B = 0011 \Rightarrow \text{Function}=?$

$$\begin{aligned}\Rightarrow A - B &= \text{Ex-3} - 0011 \\ &= \text{Ex-3} + (1100) + 1 \\ &= \text{BCD code.}\end{aligned}$$

Ex-3 to BCD code converter.

$\therefore$ let, $\text{Ex-3} \xrightarrow{\text{or } 4} 0111 \Rightarrow 0100 \rightarrow \text{BCD}$

$\uparrow$
Ex-3

$$\begin{array}{r} 111 \\ 0111 \\ + 1100 \\ + 1 \quad (\because C=1) \\ \hline 0100 \end{array} \Rightarrow 4_{10} = (0100)_{\text{BCD}}$$

② $x=1$, $A = 1001$; $B = \text{BCD} \Rightarrow \text{Function}=?$

Ans: $A = 1001$, let, $B = \text{BCD of } 3$
 $B = 0011$.

$$\begin{array}{r} A \\ + 1 \\ \hline A - B = \begin{array}{r} 1001 \\ + 1100 \\ + 1 \\ \hline 10110 \end{array} \end{array}$$

$= 6_{10}$ which is 9's comp. of 3_{10}

$\therefore$ So, BCD to 9's Comp. of BCD.

$$A + 1's \text{ comp of } B + C_1 = 1.$$


$$= A + (2's \text{ comp of } B).$$

$$= A - \text{BCD.}$$

$$= 9_{10} - \text{BCD}$$

$$= 9's \text{ complement of BCD.}$$

(c)

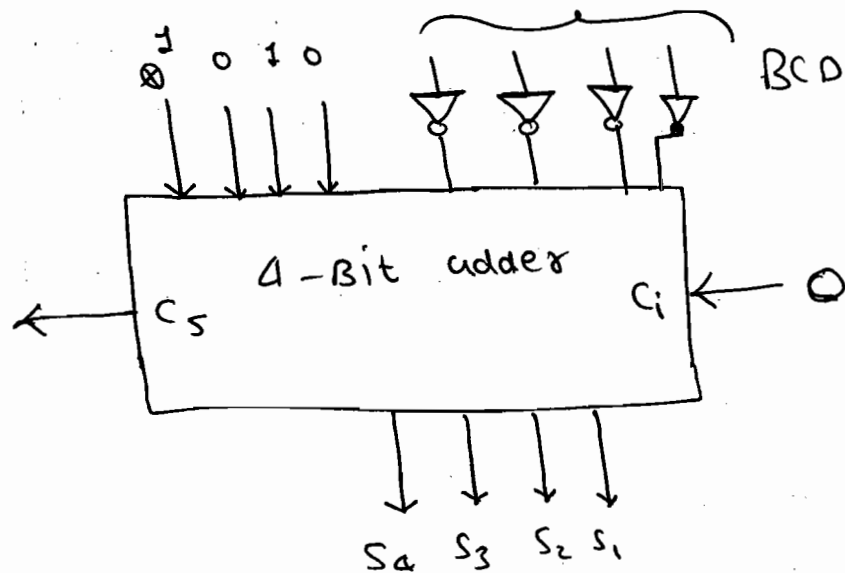

$$\Rightarrow 1010 + 1's \text{ Comp. of } BCD \quad \boxed{C_i = 0}$$

$$= \cancel{1001} + 1 + 1's \text{ Comp. of } BCD$$

$$\Rightarrow 1001 + 2's \text{ Comp. of } BCD.$$

$$= 9_{10} - BCD.$$


→ 9's Complement of CKt .

NOTE: The above, 9's Complement CKt can be

Converted to a 10's Complement either
by choosing $C_i = 1$ (or) by choosing

A value as $A = 1011$

* BCD Adder

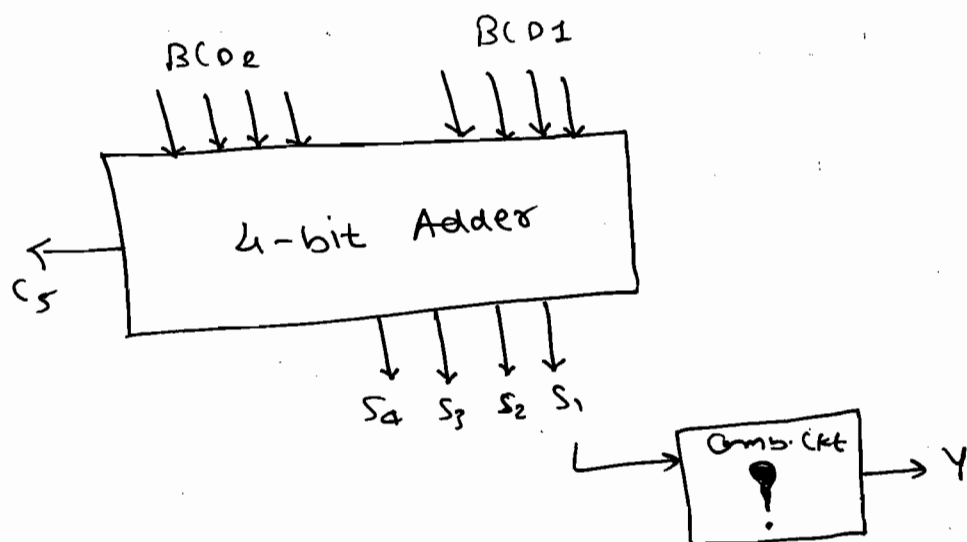


* Output is invalid BCD if


$$S_4S_3S_2S_1 > 9 \text{ (or) } C_5 = 1.$$

S_2S_1	00	01	11	10
S_4S_3				
00				
01				
11	1	1	1	1
10			1	1

→ i.e. output is invalid if

$$Y = S_4S_3 + S_4S_2 + C_5$$

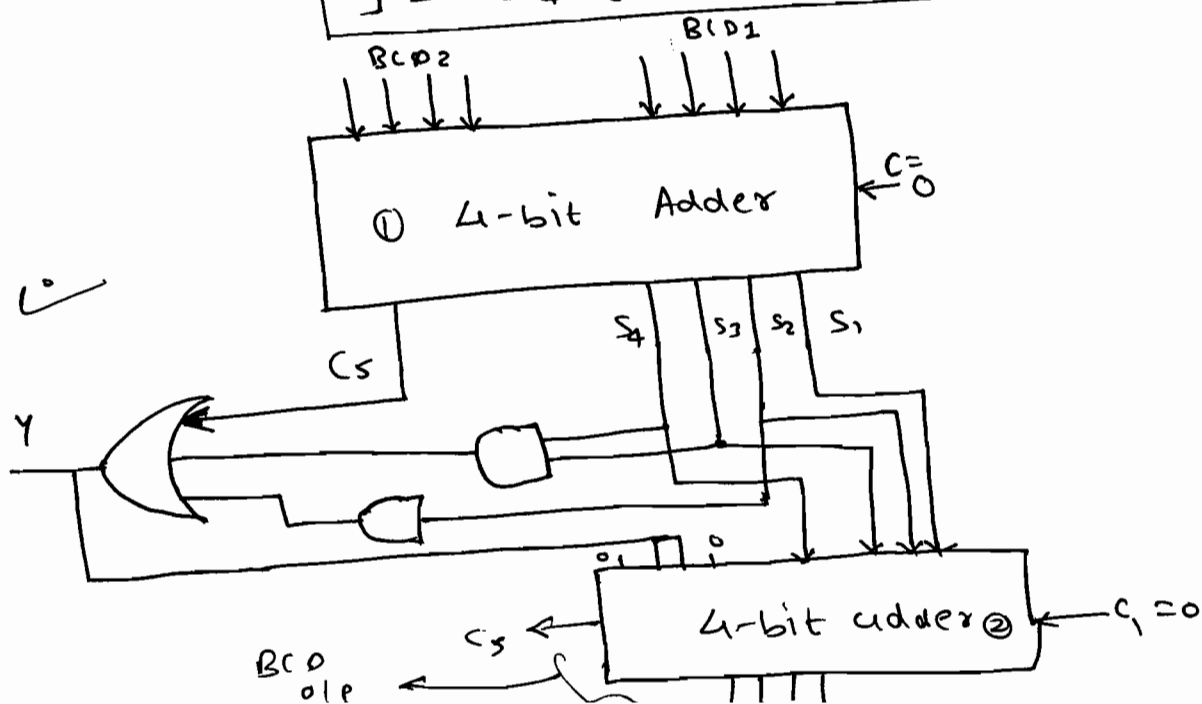

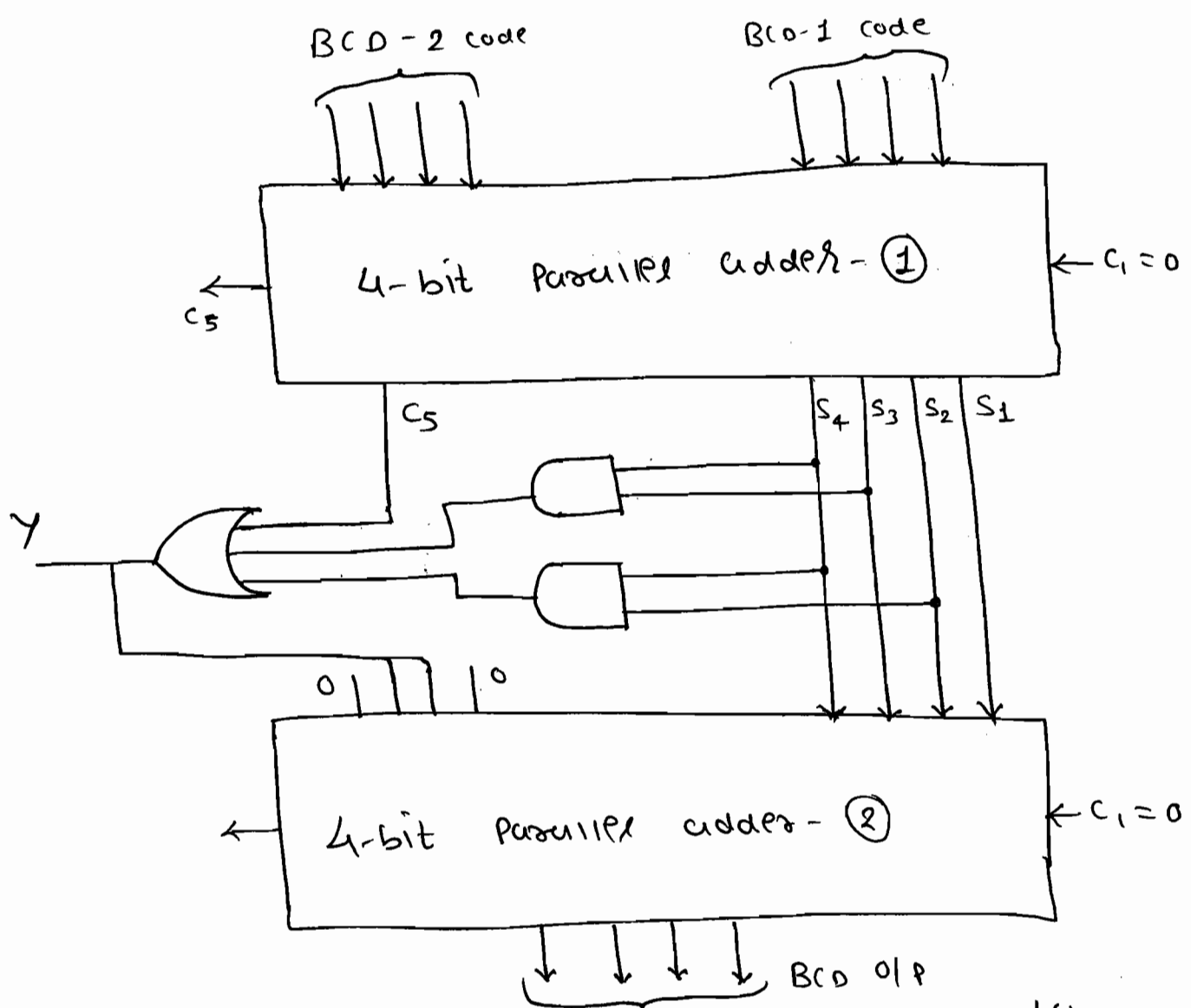


→ Hence, one BCD adder requires ^{two} 4-bit parallel adders

* Ex-3 Adder

(1) If $C_5 = 1 \Rightarrow$ Add $\begin{array}{ccc} \bar{C}_5 & \bar{C}_5 & C_5 \\ 0 & 0 & 11 \\ \hline \end{array}$

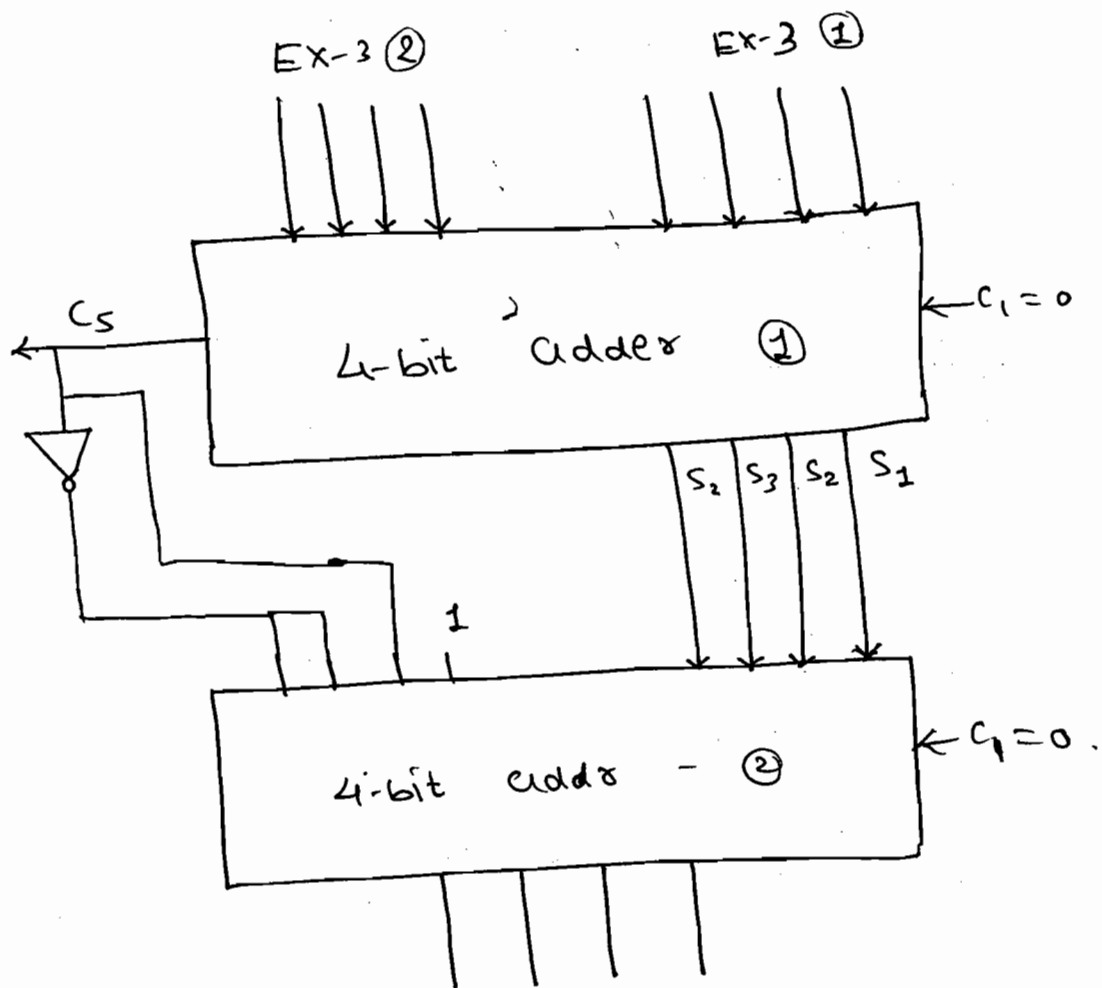(2) If $C_5 = 0 \Rightarrow$ Subtract 0011
 $=$ Add 2's Comp of 0011
 $=$ Add $\begin{array}{ccc} \bar{C}_5 & \bar{C}_5 & C_5 \\ 1 & 1 & 01 \\ \hline \end{array}$



* 2-Bit Magnitude Comparator:

→ The truth table of n bit magnitude Comparator is not preferred for the design as the no. of rows in the table is 2^{2n} .

n -bit Mag Comparator $\rightarrow$ No. of rows = 2^{2n}
 $= 2^{2n}$



*Q → How many possible way in 2 bit mag. Comparator that $A > B$?

Ans:


$A_2 A_1$	$B_2 B_1$	
0 0	—	
0 1	0 0	$\rightarrow$ ①
1 0	0 0 0 1	$\rightarrow$ ②
1 1	0 0 0 1 1 0	$\rightarrow$ ③

So, 6 possibility that $A > B$.

*

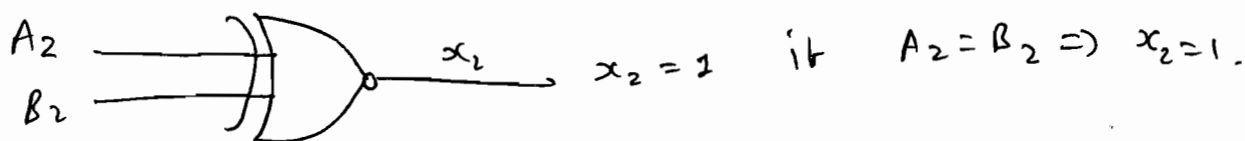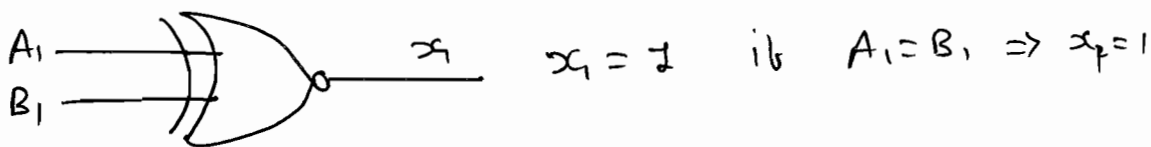

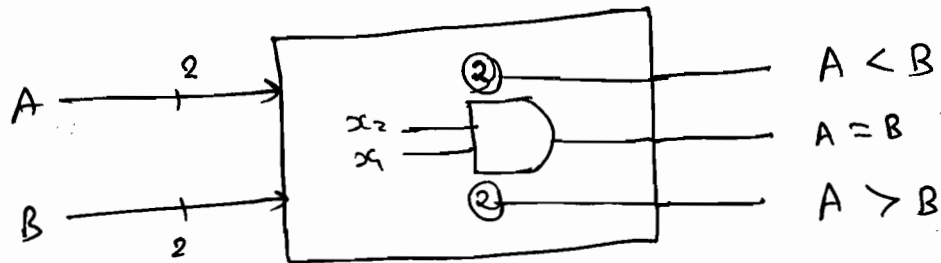- ① $A=B$ if $A_2=B_2$ and ~~$x_2=1$~~ $A_1=B_1$ 83
i.e. $A=B$ if $x_2=1$ and $x_1=1$.
i.e. $A=B$ if $x_1 \cdot x_2 = 1$.




$$A = A_2 B_1$$

$$B = B_2 B_1$$

- ② $A > B$ if $A_2 > B_2$ (or) $A_2 = B_2$ and $A_1 > B_1$.
i.e. $A > B$ if $A_2 \bar{B}_2 + x_2 \cdot A_1 \bar{B}_1 = 1$ — ②
- ③ $A < B$ if $A_2 < B_2$ (or) $A_2 = B_2$ and $A_1 < B_1$.
i.e. $A < B$ if $\bar{A}_2 B_2 + x_2 \cdot \bar{A}_1 B_1 = 1$ — ③

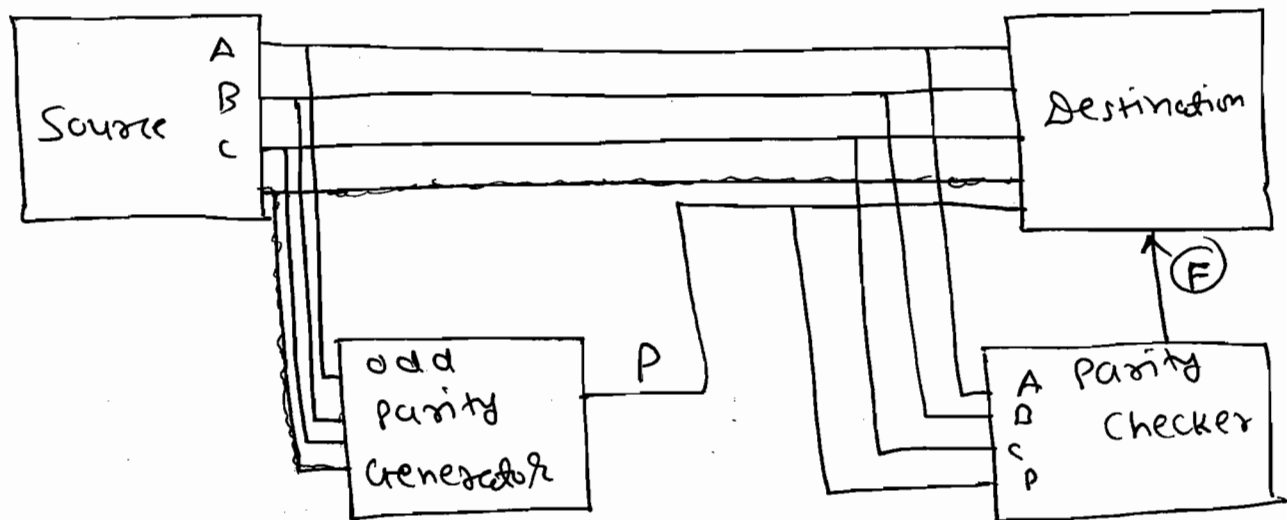* Odd parity generator and parity checker.



P is chosen so that
 $A, B, C, P \rightarrow \text{odd parity.}$

$F = 1$ if even parity
 $F = 0$ if odd parity
 occurs for $A, B, C, P.$

$\rightarrow$ odd parity generator:

A	B	C	P
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$P(A, B, C) = \sum m(0, 3, 5, 6)$$

	BC			
	00	01	11	10
A	0	1	0	1
		0	1	0
	1	0	1	0
		1	0	1

$$P = A \oplus B \oplus C$$

(or)

$$P = A \odot B \oplus C$$

A	B	C	P	F
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$F = \sum m(A, B, C, P)$$

$$= \sum m(0, 3, 5, 6, 9, 10, 12, 15).$$

		C D			
		00	01	11	10
A B	00	1		1	
	01		1		1
	11	1		1	
	10		1		1


* All minterms have
Even no of 0's.

$$\Rightarrow F = A \oplus B \oplus C \oplus P.$$

* Decoder:

→ It converts the binary information on i/p lines to one of many o/p lines.

→ n to m decoder = (1 out of m decoder).

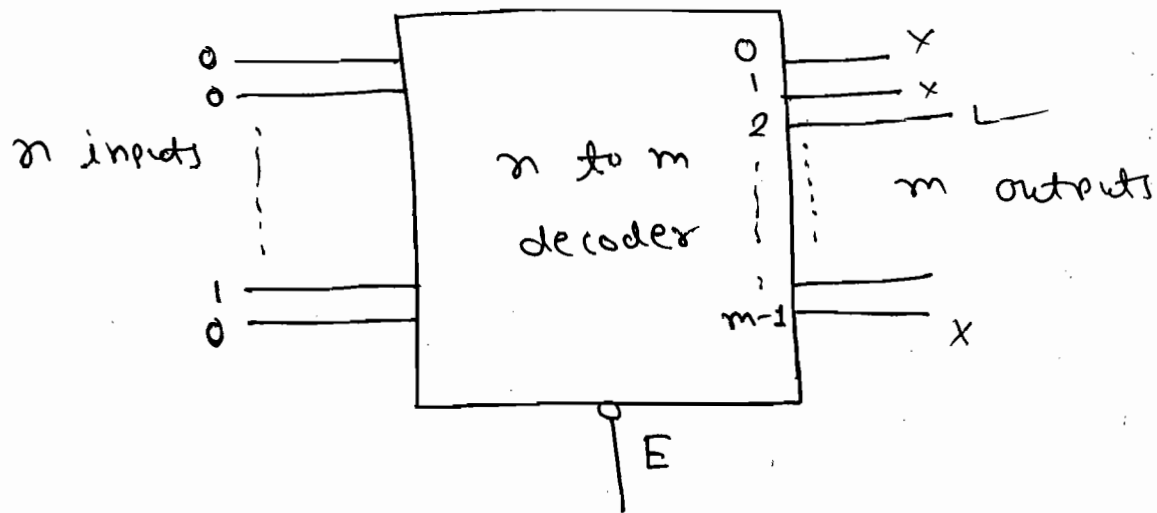


$E=0 \Rightarrow$ Decoder is enabled


$E=1 \Rightarrow$ Decoder is disabled

$$m \leq 2^n$$

* 2 to 4 decoder (Active High O/p).

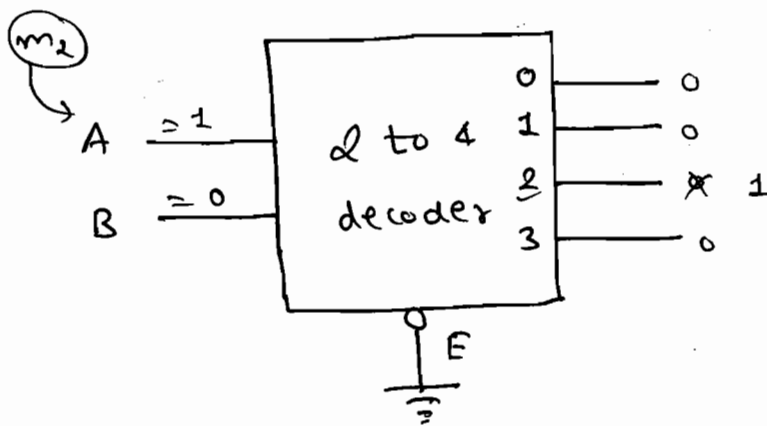


* 2 to 4 decoder (Active Low O/p).

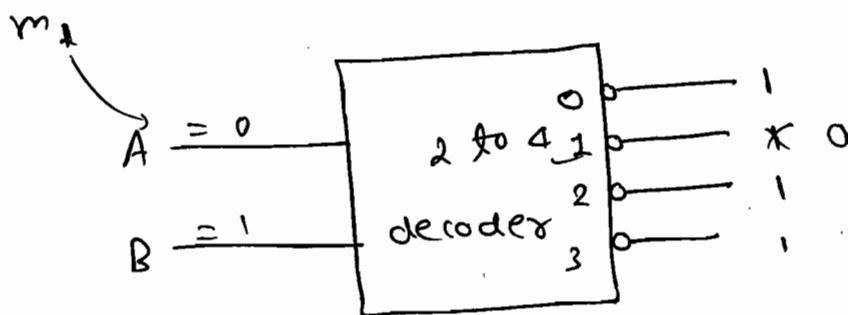

Most widely used in practice. because it generate less noise compare to Active High Decoder.

⇒ Internal circuits:

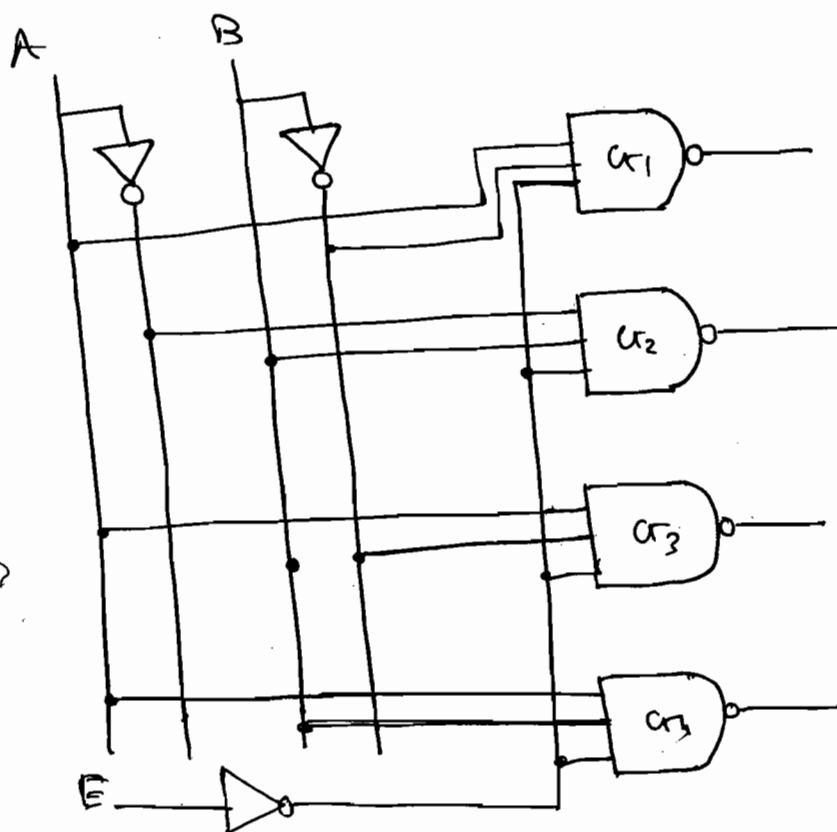


* Decoders
⇒ AND, NAND gates.

Ex-1 Implement $F(A,B) = \sum m(0,2,3)$ using
a decoder (a) with active high o/p.s
(b) with active Low o/p.s.


Ans: (a) With active high o/p.

A	B	F
0	0	1
0	1	0
1	0	1
1	1	1

m_0
 m_2
 m_3

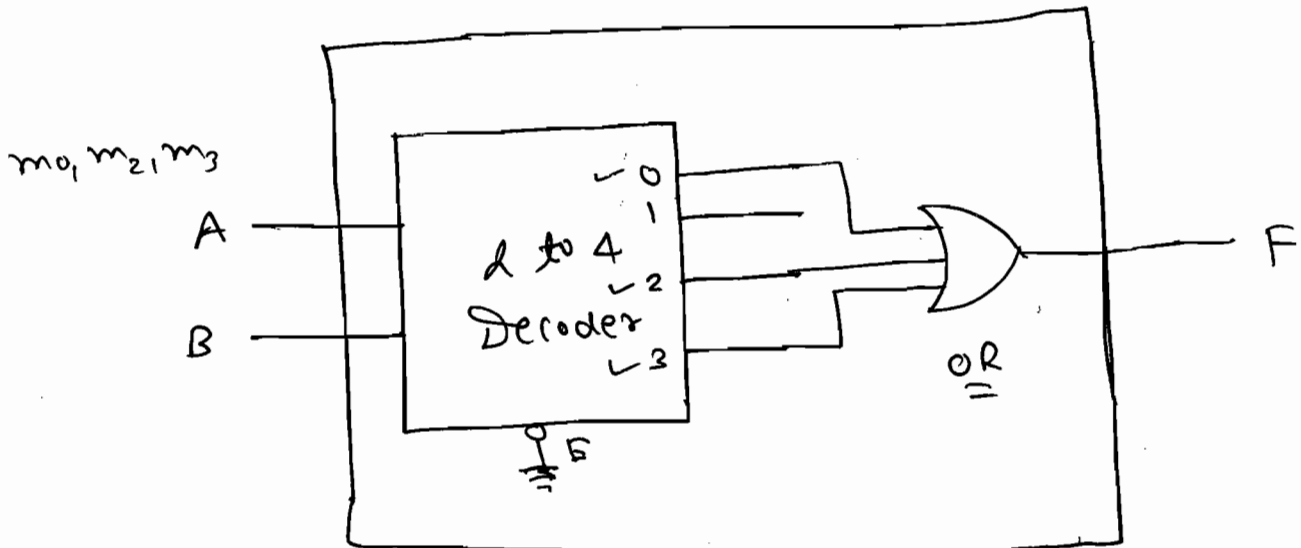

(b) With active Low o/p.

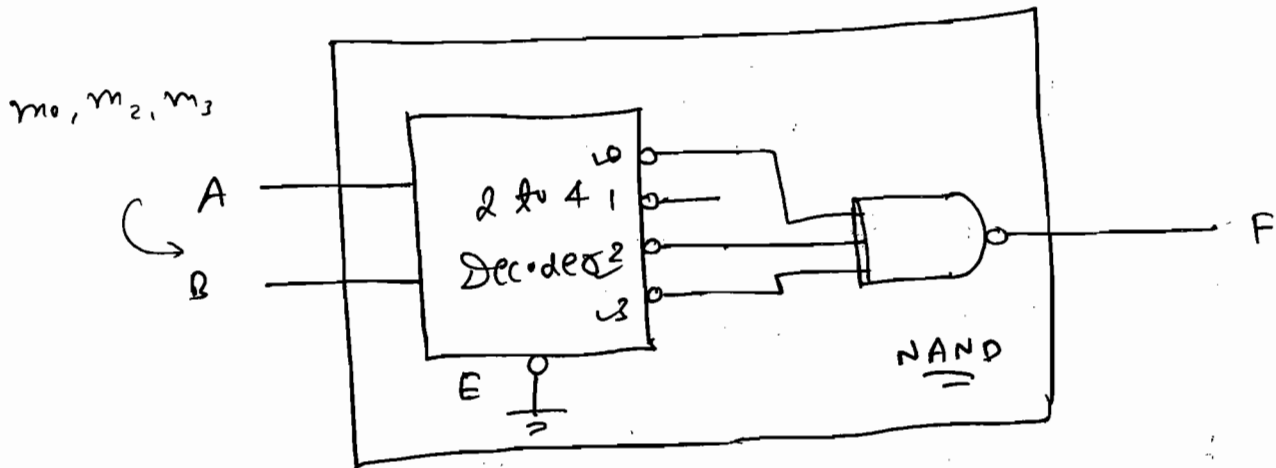


Ex-2 Implement a full Subtractor using a decoder with active Low outputs.

Ans:

$$D(A, B, b_i) = \sum m(1, 2, 4, 7).$$

$$B(A, B, b_i) = \sum m(1, 2, 3, 7).$$

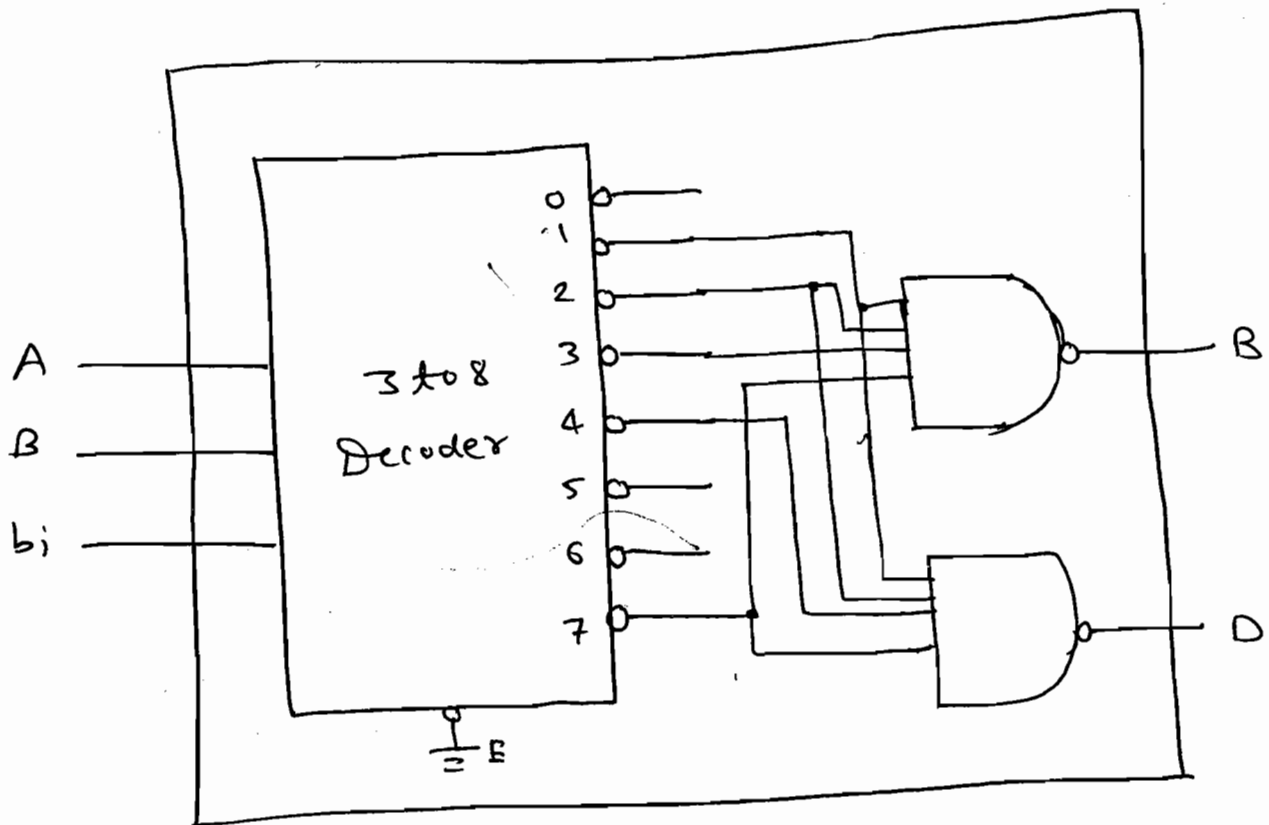


Ex-3 How many 2 to 4 decoder required to construct 1 out of 32 decoder.

Ans: Short cut:



Required No. of O/P	Given no. of o/p	No. of Decoders
$\frac{32}{4} = 8$		8
$\frac{8}{4} = 2$		+ 2
$\frac{2}{4} = 0.5 \approx 1$		+ 1
		<u>11</u>

3 levels.

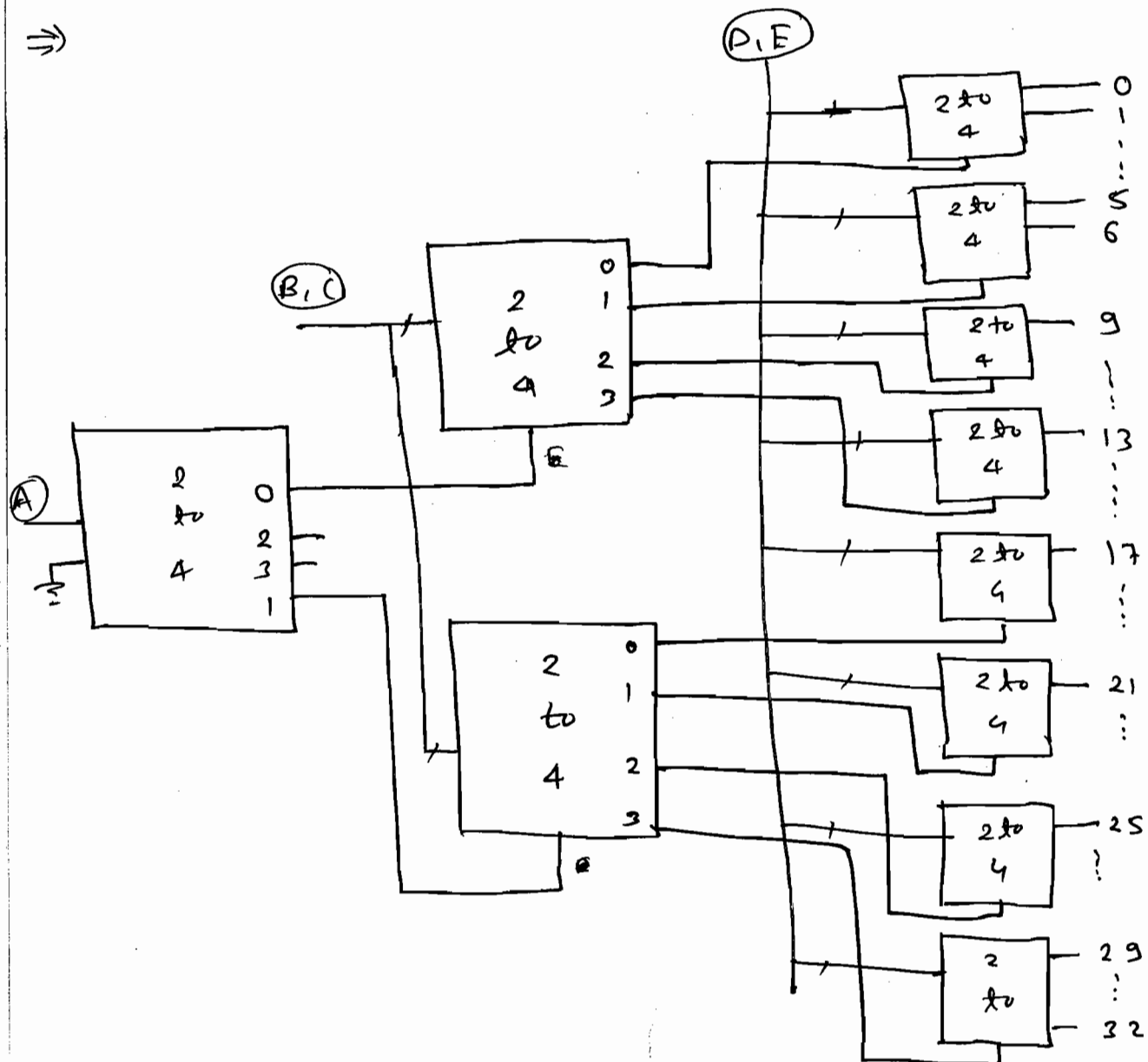

* Demultiplexer (one to many ckt, Serial to parallel converter). 91

1:4 Demux

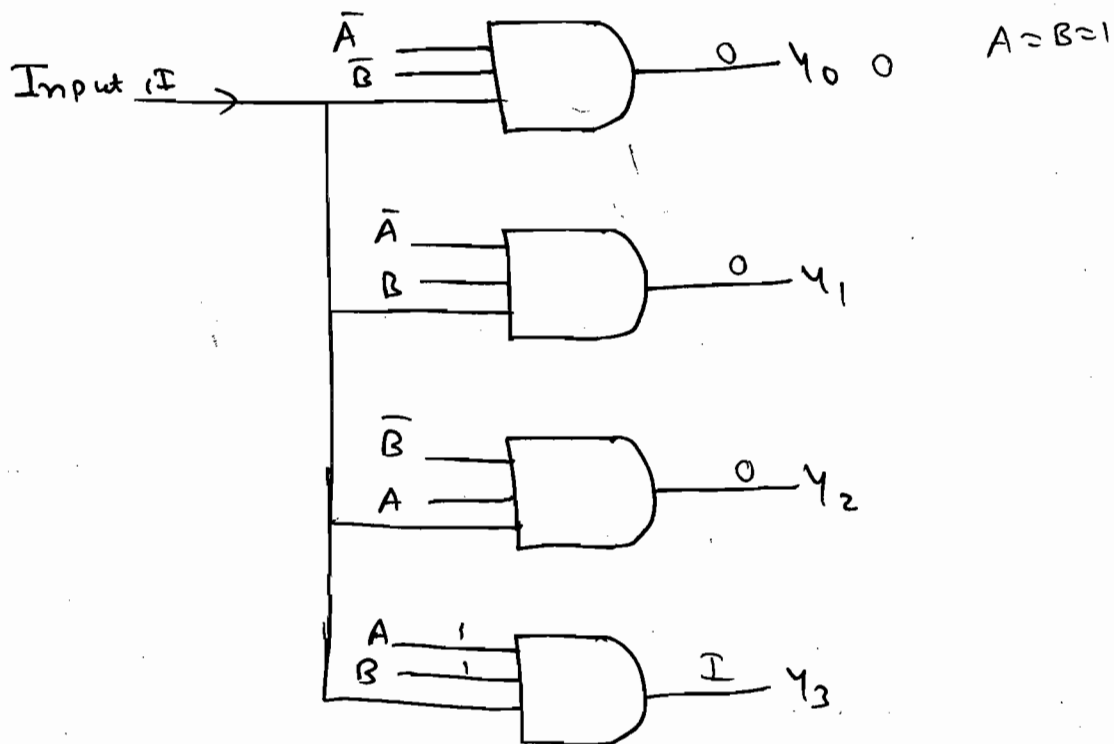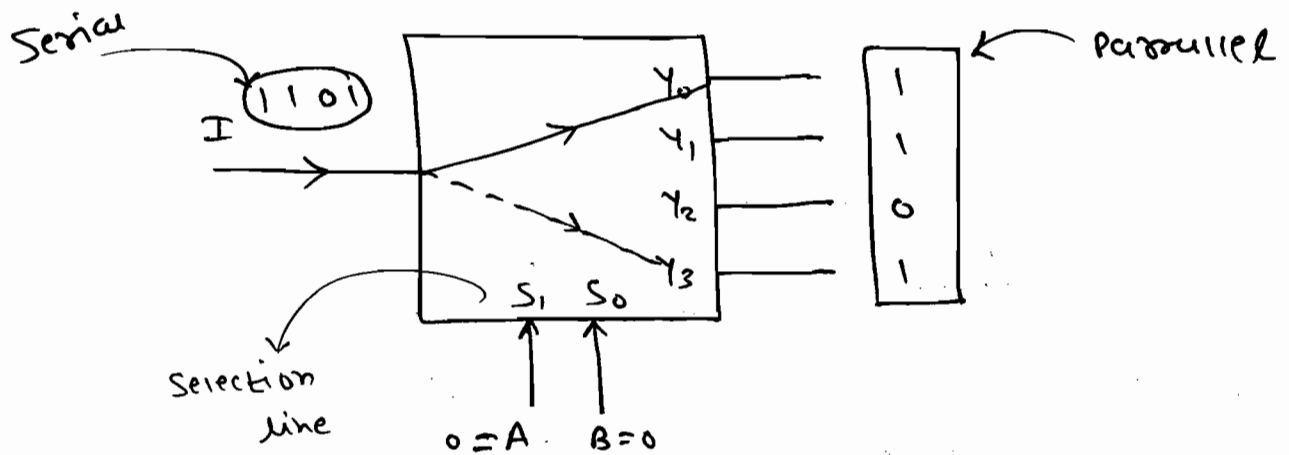

→ A Demux is similar to a decoder.

→ A 1:4 Demux is converted to a 2 to 4

Decoder by making two changes.

(1) Selection of Demux are converted to the inputs of 2 to 4 decoder.

1
2
3
840

3



1



1

C.

11)

$$A = 0_4 + 0_5 + 0_6 + 0_7.$$

$$B = 0_2 + 0_3 + 0_6 + 0_7.$$


$$C = 0_1 + 0_3 + 0_5 + 0_7.$$

NOTE:

→ The encoder follows the OR Logic.

→ The limitation of encoder is it can't performed the coding if more than 1 input is active simultaneously. To overcome this, we use priority encoder.

* Priority Encoder:

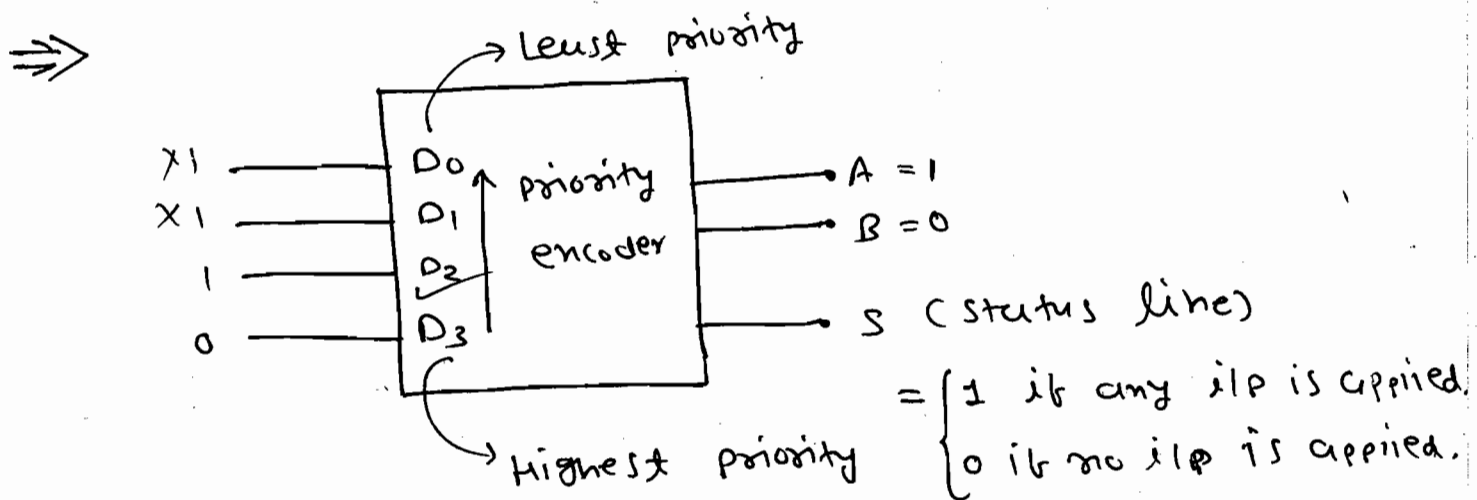

⇒

	D_3	D_2	D_1	D_0	A	B	S
$m_0 \leftarrow$	0	0	0	0	0	0	0
$m_1 \leftarrow$	0	0	0	1	0	0	1
$m_2, m_3 \leftarrow$	0	0	1	X	0	1	1
$m_4 \text{ to } m_7 \leftarrow$	0	1	X	X	1	0	1
$m_8 \text{ to } m_{15} \leftarrow$	1	X	X	X	1	1	1

(b) Priority Encoder table.

$$\rightarrow B(D_3, D_2, D_1, D_0) = \sum m(2, 3, \cancel{4}, \cancel{5}, \cancel{6}, \cancel{7}, 8, 9, 10, \dots, 15).$$

		$D_1 D_0$			
		00	01	11	10
$D_3 D_2$	00			1	1
	01				
	11	1	1	1	1
	10	1	1	1	1

$$B = D_3 + \overline{D_2} D_1$$

$$\rightarrow A(D_3, D_2, D_1, D_0) = \sum m(4, 5, 6, 7, \dots, 15).$$

		$D_1 D_0$			
		00	01	11	10
$D_3 D_2$	00				
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$A = D_2 + D_3$$

$$\rightarrow S = \sum m(1, 2, 3, \dots, 15).$$

		$D_1 D_0$			
		00	01	11	10
$D_3 D_2$	00	1	1	1	1
	01	1	1	1	1
	11	1	1	1	1
	10	1	1	1	1

$$\therefore S = \overline{D_3} + \overline{D_2} + \overline{D_1} + \overline{D_0}$$

$$S = D_3 + D_2 + D_1 + D_0$$

NOTE:

74LS138 $\Rightarrow$ $\begin{cases} 3 \text{ to } 8 \text{ decoder} \\ (\text{Active low outputs}). \end{cases}$


74LS148 $\Rightarrow$ $\begin{cases} 8\text{-input, 3-output} \\ \text{priority encoder.} \end{cases}$

* Multiplexer:

(Many to one circuit,
parallel to serial converter).

*

4:1 MUX.

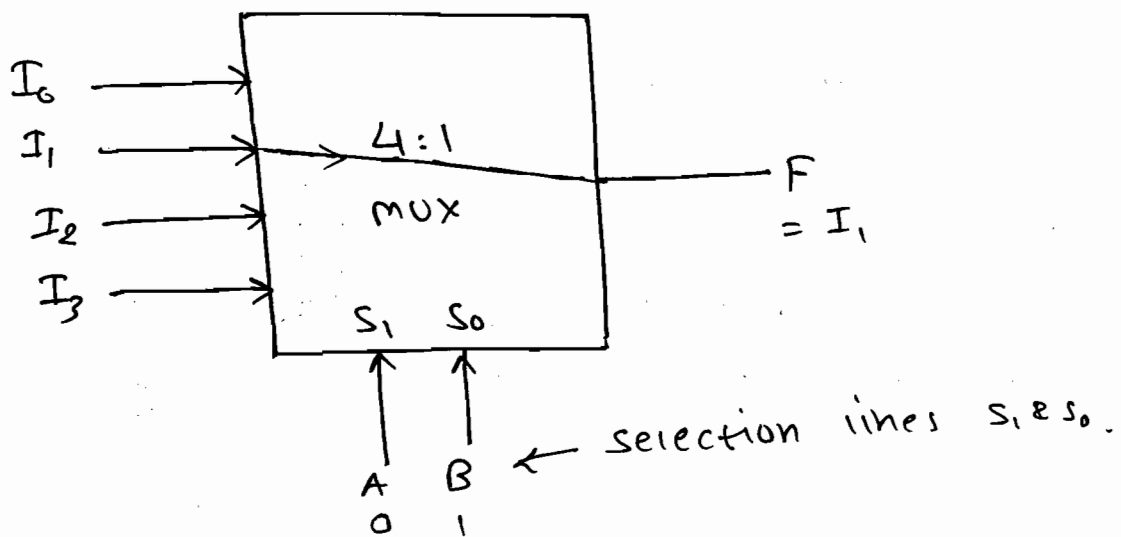

$\therefore$

A	B	F
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

$\Rightarrow$ 4:1 MUX $\Rightarrow F = \bar{A}\bar{B}I_0 + \bar{A}BI_1 + A\bar{B}I_2 + ABI_3$

$$\therefore F = m_0 I_0 + m_1 I_1 + m_2 I_2 + m_3 I_3.$$

* E.g.: Given $I_0 = I_1 = 1$; $I_2 = I_3 = 0$.

$$\therefore F = m_0 \cdot 1 + m_1 \cdot 1 + 0 + 0.$$

$$\therefore F = m_0 + m_1$$

$$\therefore F = \sum m(0, 1).$$


Ex-1 Implement the Sum of half Adder using 4:1 MUX.

Ans:

$$S(A, B) = \sum m(1, 2).$$

$$S(A, B) = m_1 + m_2$$

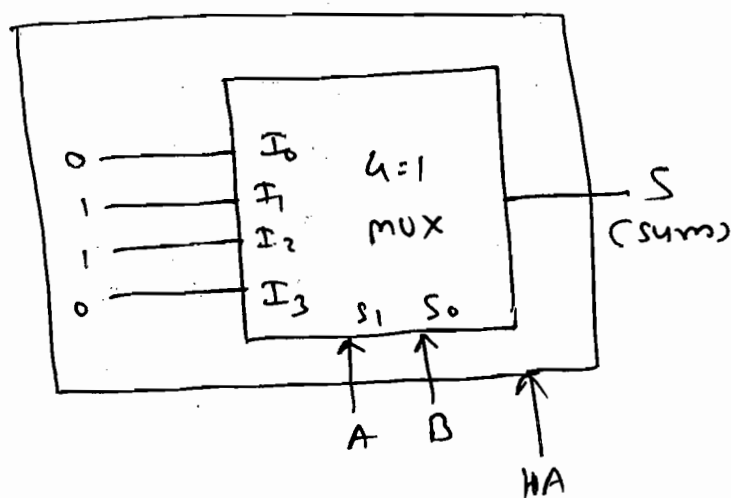Choose $I_1 = I_2 = 1$ &
 $I_0 = I_3 = 0$




Ex-2 Which of the following is implemented by the following mux.

- (a) Sum output of Full adder.
- (b) Carry output of Full adder.
- (c) Difference output of Full Subtractor.
- ✓ (d) Borrow output of Full Subtractor.

Q Sum up the given circuit.


97

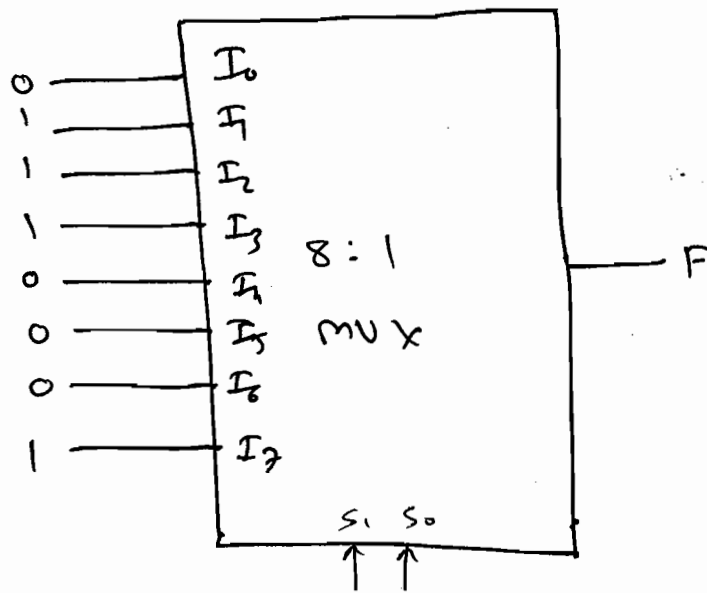

$$F = \sum m(1, 2, 3, 7)$$

Ex-2 What are the Logic gates represented by the following mux circuits.

Q

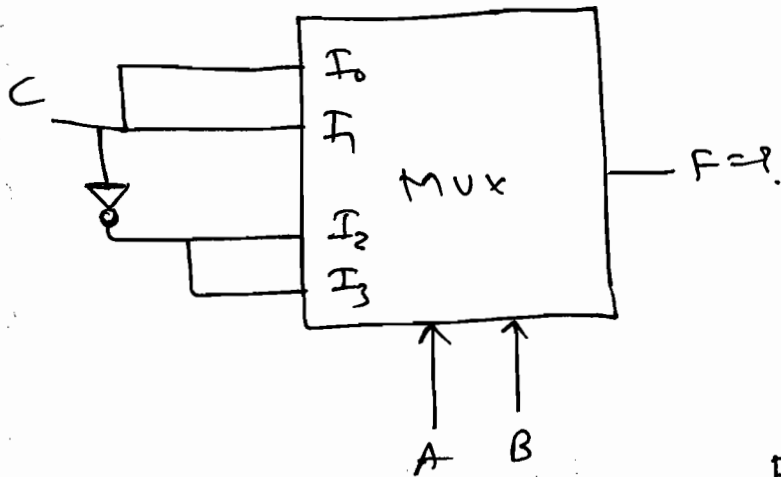

$$F = m_0 C + m_1 C + m_2 \bar{C} + m_3 \bar{C}$$

$$F = (\bar{A}\bar{B} + \bar{A}B)C + (A\bar{B} + AB)\bar{C}$$

$$F = \bar{A}C + A\bar{C}$$

$$F = (A \oplus B)C$$

$$F = \bar{A}B + A\bar{B}$$


$$F = (\bar{A}\bar{B} + \bar{A}B)C + (A\bar{B} + AB)\bar{C}$$

$$= \bar{A}C + A\bar{C}$$

$$F = A \oplus C$$

∴ XOR gate

(b)

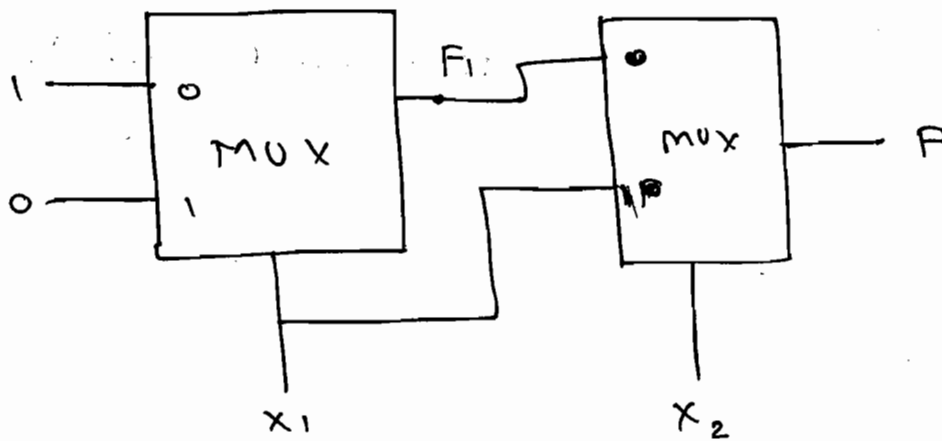

$$\therefore F_1 = m_0 = \bar{x}_1$$

$$\therefore F_1 = \bar{x}_1$$


$$\therefore F = F_1 \bar{x}_2 + x_2 x_1$$

$$= \bar{x}_1 \bar{x}_2 + x_2 x_1$$

$$\therefore \boxed{F = x_1 \oplus x_2}$$

Ex-4 Determine the output of the following MUX.

Ans.

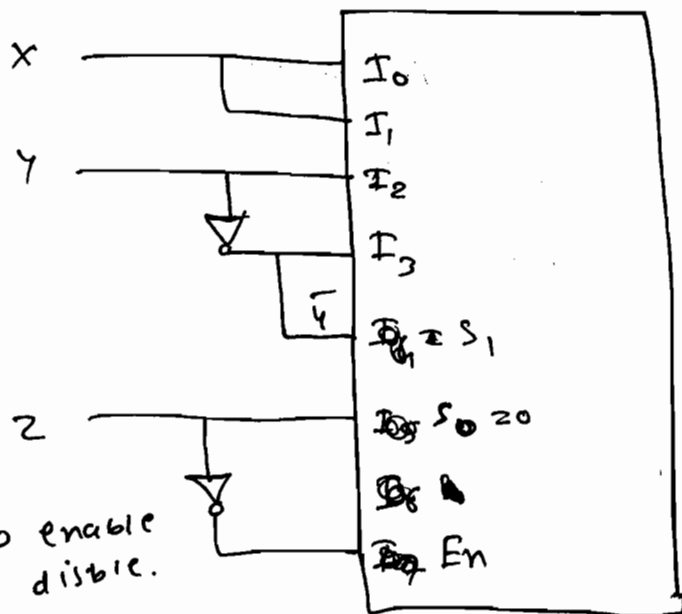

$Z=0$ enable
 $Z=1$ disable.

$$F = (m_0 + m_1) X$$

$$+ m_2 Y + m_3 \bar{Y}$$

$$= (\bar{S}_1 \bar{S}_0 + \bar{S}_1 S_0) X$$

$$+ S_1 \bar{S}_0 Y + S_1 S_0 \bar{Y}$$

$$= \bar{S}_1 X + S_1 \bar{S}_0 Y + S_1 S_0 \bar{Y}$$

$$= \bar{S}_1 X + S_1 Y + 0$$

$$= XY + 0$$

$$= XY$$

$\Rightarrow$

$$F = x \cdot y \cdot \bar{z}$$

 $\Rightarrow z=0 \rightarrow \text{enable.}$
 $z=1 \rightarrow \text{disable.}$

Ex-5 How many 4:1 mux required to construct 128:1 MUX.

Ans: $\frac{\text{Required No. of Inputs}}{\text{Given No. of I/P}}$

$$= \frac{128}{4} = 32 \xrightarrow{\text{No. of MUX}} 32$$

$$\downarrow +$$

$$\therefore \frac{32}{4} = 8 \xrightarrow{\text{No. of MUX}} 8$$


$$\downarrow +$$

$$\frac{8}{4} = 2 \xrightarrow{\text{No. of MUX}} 2$$


$$\downarrow +$$

$$\frac{2}{4} = 0.5 \xrightarrow{\text{No. of MUX}} 1$$

$$\underline{43}$$

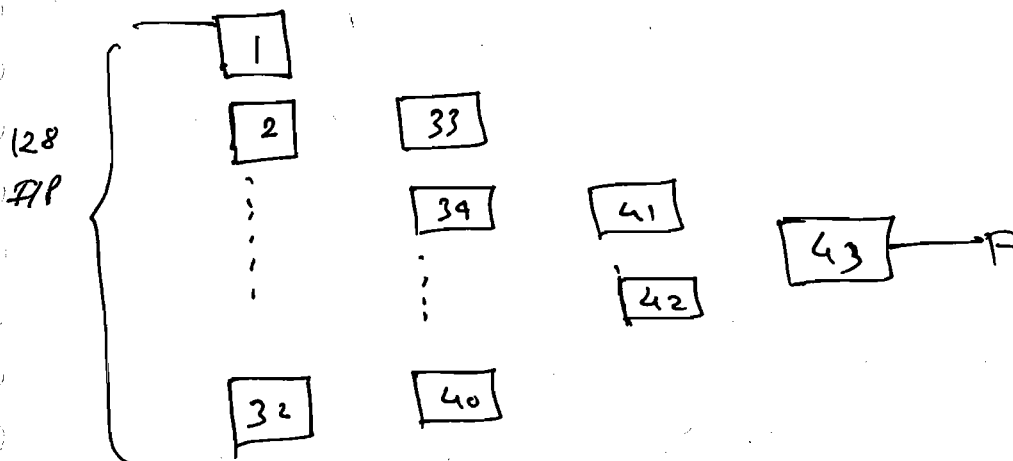

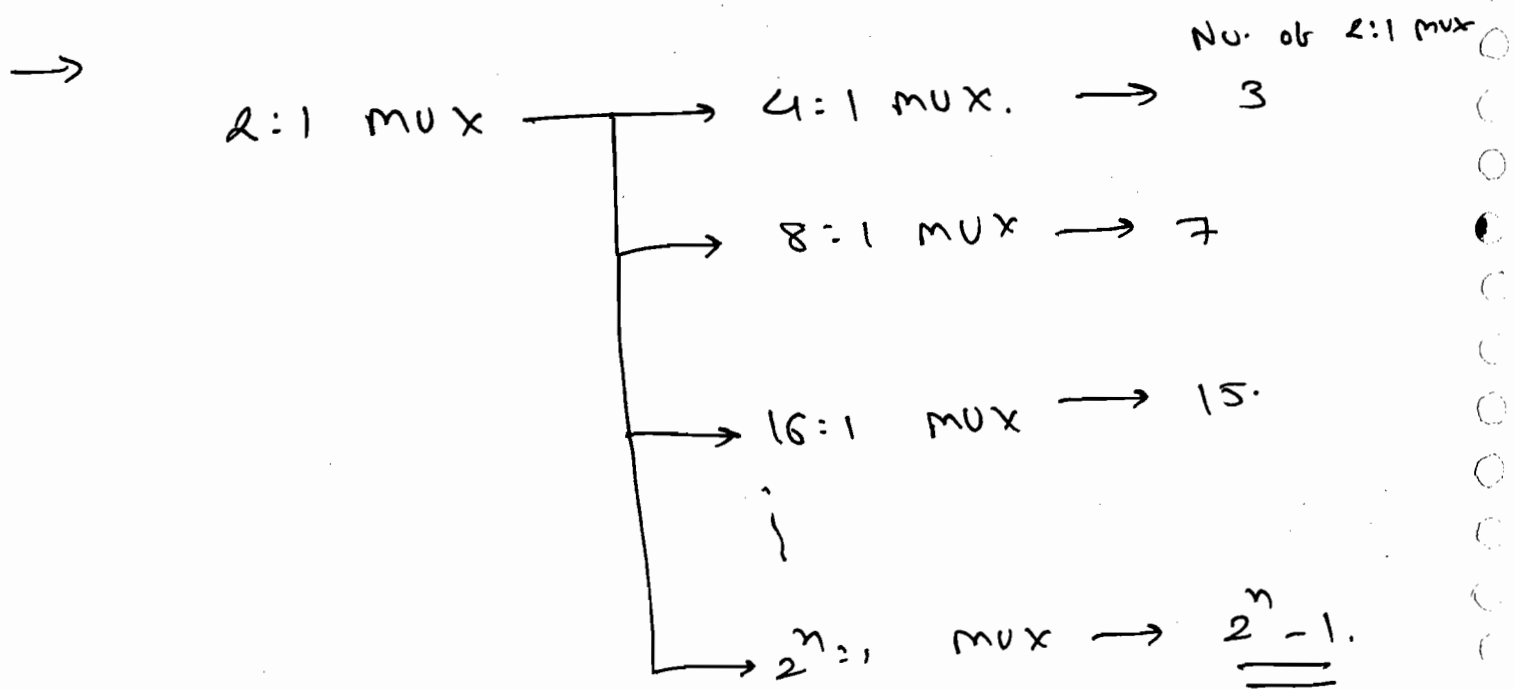(b) $2:1 \text{ MUX} \longrightarrow 2^n:1 \text{ MUX.}$



So, $\boxed{2^n - 1}$ $2:1$ MUX required for $2^n:1$ MUX.

Ex-5 How many $2:1$ MUX are req. to realize

- (a) AND gate
- (b) OR gate
- (c) EX-OR gate.

Ans:

$$F = \bar{A}I_0 + AI_1$$


$$F = AB$$

$$F = AB + 0 \cdot \bar{A}$$

$$F = 0 \cdot \bar{A} + B \cdot A$$

$$F = \bar{A}I_0 + AI_1$$

So, $I_0 = 0, I_1 = B.$

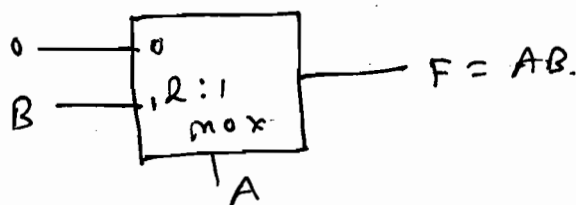

(b) OR gate:

$$\therefore F = \bar{A}I_0 + AI_1$$


$$F = A + B.$$

$$= A + \bar{A}B$$

$$F = \bar{A}B + A \cdot 1.$$

$$\therefore F = \bar{A}I_0 + A \cdot I_1$$

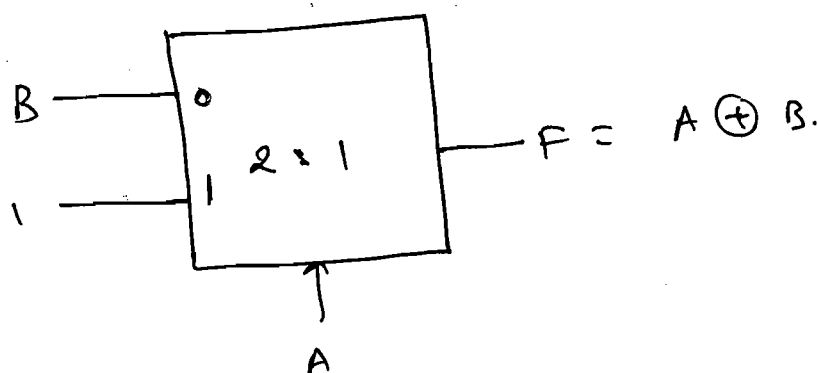
$\therefore$ So, Choose $I_0 = B, I_1 = 1.$



(c) Ex-or gate:


$$\rightarrow F = \bar{A}B + A\bar{B} = A \oplus B.$$

$\uparrow$ $\uparrow$
 I_0 I_1

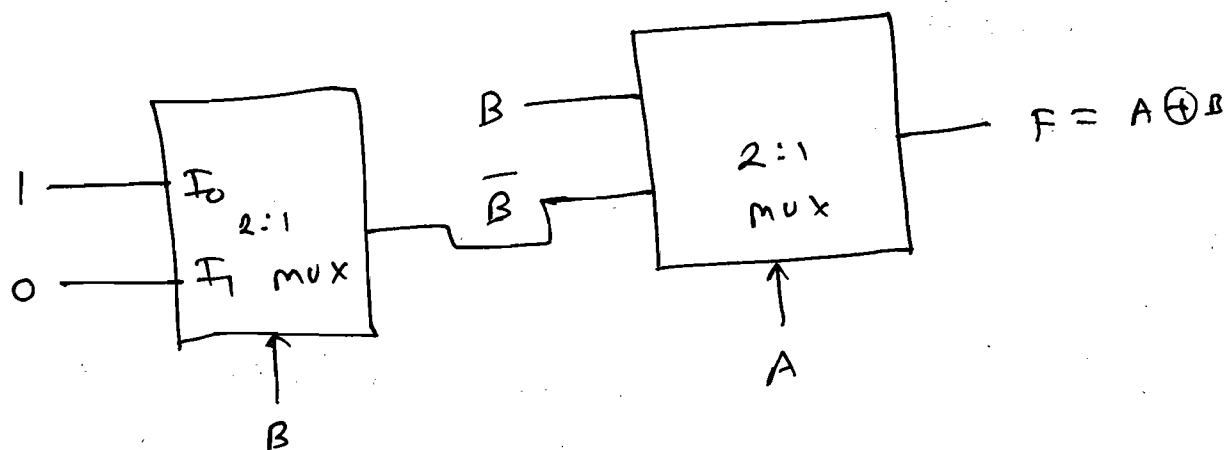

Ex-6 Implement $F(A, B, C, D) = \sum m(0, 1, 3, 5, 6, 10, 11, 13, 14)$ using 4:1 MUX.

Ans:

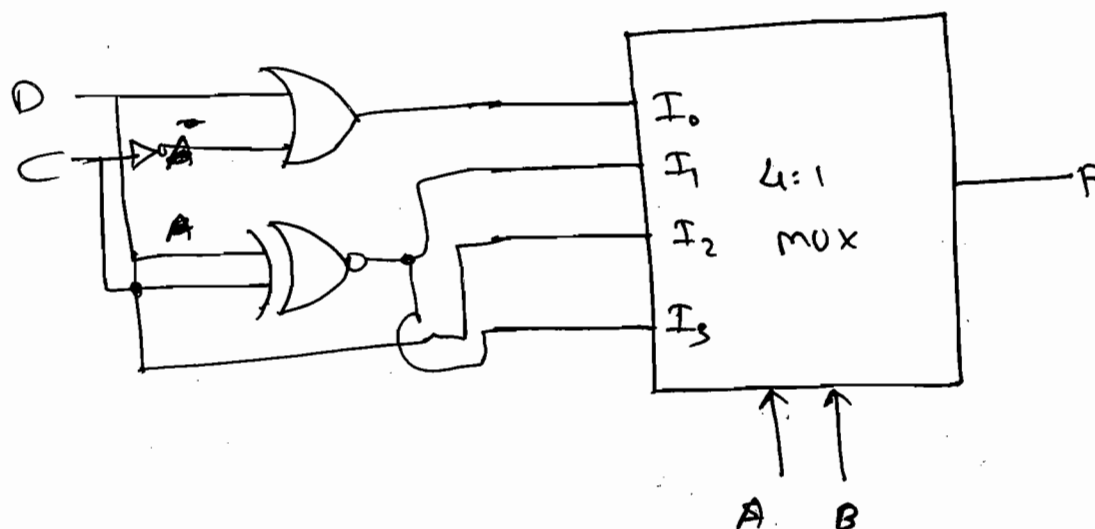

Method - 1

AB =		00	01	10	11
		I_0	I_1	I_2	I_3
00	$\bar{C}\bar{D}$	(0)	4	8	12
01	$\bar{C}D$	(1)	(5)	9	(13)
10	$C\bar{D}$	2	(6)	(10)	(14)
11	CD	(3)	7	(11)	15
		$\bar{C}\bar{D} + \bar{C}D + CD = \bar{C} + D$	$C\bar{D}$	C	$C \oplus D$

Method :- 2

If A, B are selection line

AB	CD				
	00	01	11	10	
00	1	1	1		$\rightarrow I_0 = \bar{C}\bar{D} + \bar{C}D + CD = \bar{C} + D$
01		1		1	$\rightarrow I_1 = \bar{C}D + C\bar{D} = C \oplus D$
10		1	1	1	$\rightarrow I_2 = \bar{C}D + C\bar{D} = C \oplus D$
11			1	1	$\rightarrow I_3 = CD + C\bar{D} = C$

→ NOTE: If C & D are selection lines

103


CD \ AB	00	01	11	10
00	1	1	1	
01		1		1
11		1		1
10			1	1

$I_0 = \bar{A}\bar{B}$ $I_1 = \bar{A}B$ $I_2 = A\bar{B}$ $I_3 = AB$
 $I_0 + I_1 = \bar{A}$ $I_2 + I_3 = B$

Ex-1 $F(A, B, C) = \sum m(0, 3, 5, 6)$ using 4:1 mux.

Ans:

Method-I:

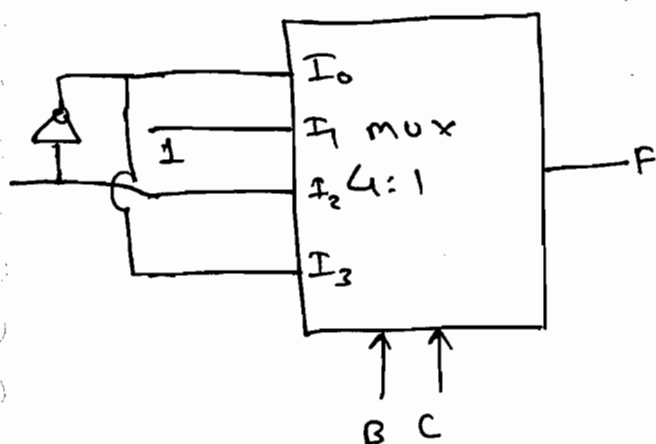


	I_0	I_1	I_2	I_3
$\bar{A}$	0	1	2	3
A	4	5	6	7
	$\bar{A}$	1	A	$\bar{A}$

Method-II (K-Map)

BC \ A	00	01	11	10
0	1	1	1	
1		1		1

$I_0 = \bar{A}$ $I_1 = 1$ $I_2 = \bar{A}$ $I_3 = A$

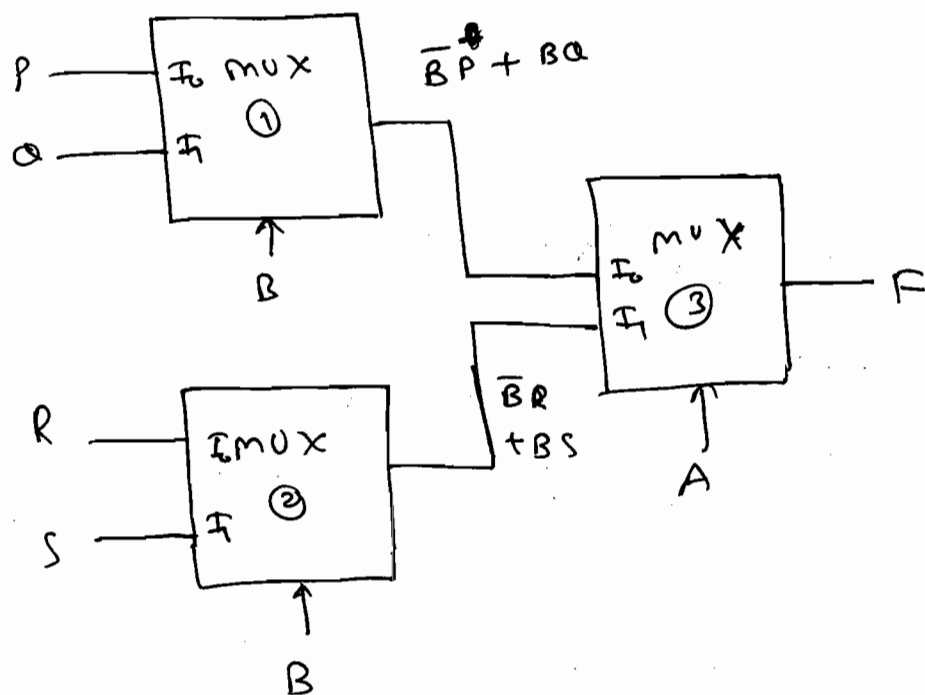Ex-2 In the following Mux tree, determine the values of $P, Q, R, S = ?$
 Where, $F(A, B, C) = \sum m(1, 2, 4, 5, 6)$.



$$\therefore F = \bar{A}(\bar{B}P + BQ) + A(\bar{B}R + BS)$$

$$\therefore F = \bar{A}\bar{B}P + \bar{A}BQ + A\bar{B}R + ABS$$

AB		00	01	11	10
AC	0	0	1	1	1
	1	1	3	7	1

$$I_0 = C \quad I_1 = \bar{C} \quad I_2 = \bar{C} \quad I_3 = 1$$

$\uparrow \quad \quad \uparrow \quad \quad \uparrow \quad \quad \uparrow$
 $P \quad \quad Q \quad \quad R \quad \quad S$

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C + ABC$$

$$\therefore F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A$$

Ex-2 Using $n=1$ MUX we can implement 105
all ' $\log_2 N$ ' variable function and
Some of " $\log_2 N + 1$ " variable functions
[T/F].

Ans: let, $n=1$ MUX


$$\text{So, } \log_2 4 = 2$$

→ True : because the other functions required
external logic gates along with MUX.

* Rom (Read only Memory).

$\Rightarrow$ Decoder + Prog. OR gates } = Rom.
(Fixed AND gates) (encoder)

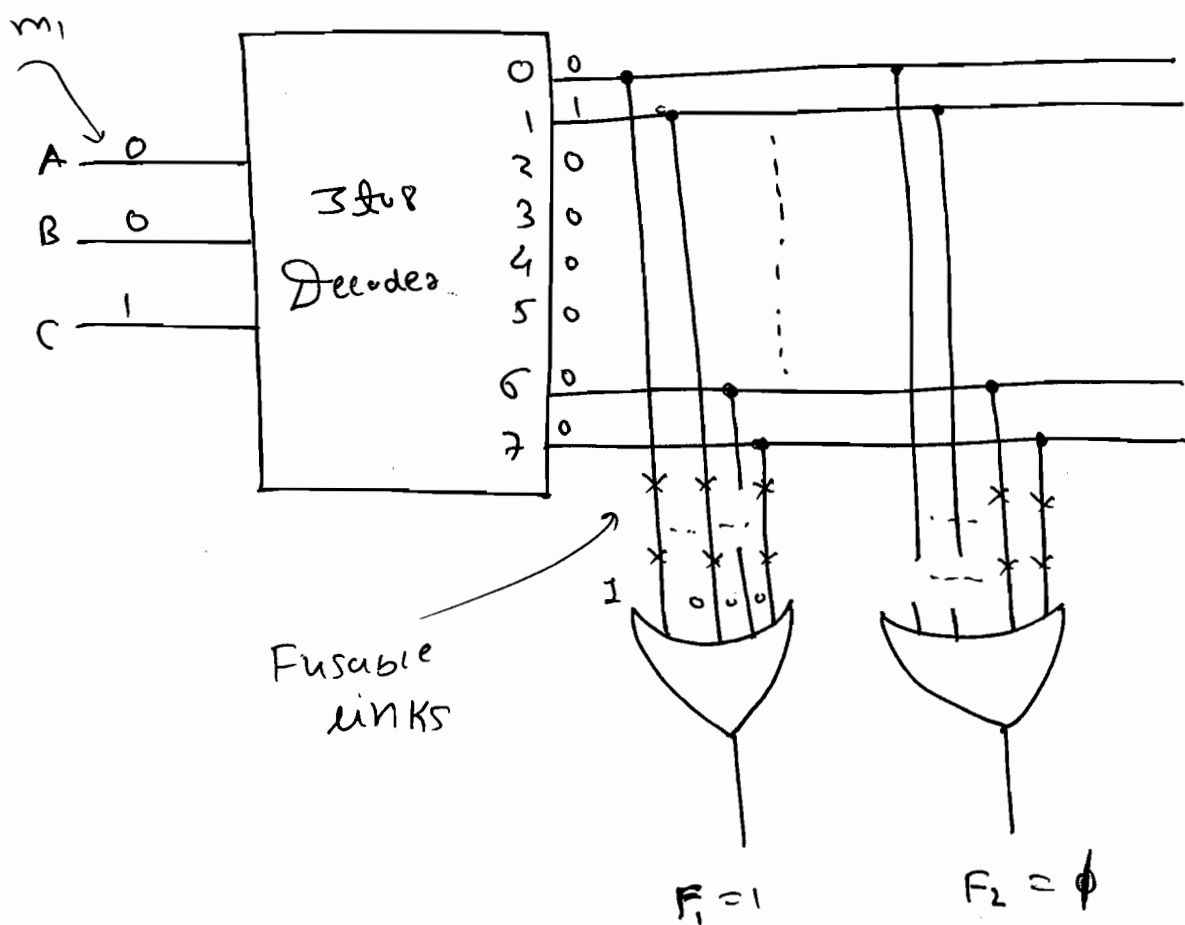$\rightarrow$ Rom is a Combinational circuits and we can use it to implement sum of minterms expression as shown in the following example:




$$F_1(A, B, C) = \sum m(0, 1, 6, 7).$$

$$F_2(A, B, C) = \sum m(2, 3, 4, 5).$$


$$\text{size} = 2^3 \times 2 = 16.$$

⇒

Read only memory

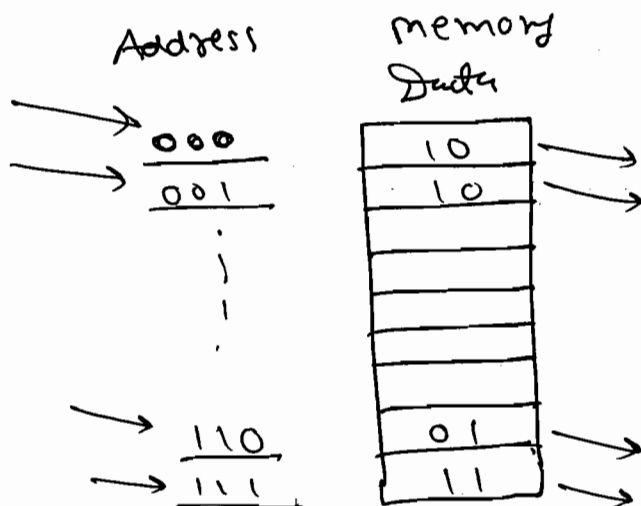

⇒

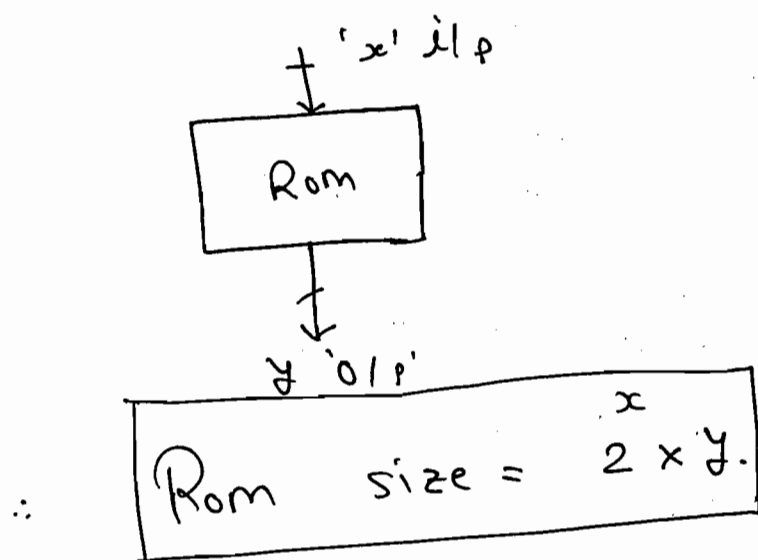


→ Rom size indicates that how many bits can be stored.

Ex-1 Determine the size of the Rom for the following functions.

① Rom as 3 bit binary multiplier.

②

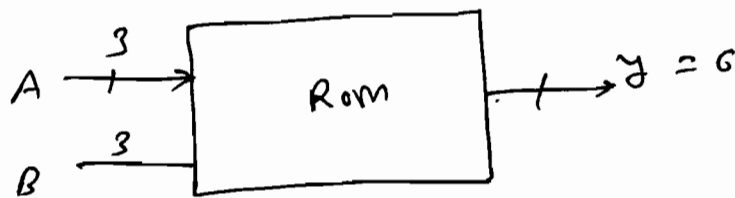

$$x = 3 + 3 = 6$$

$$y = 6$$

$$7_{10} * 7_{10} = 49_{10}$$

$$2^y > 49$$

$$y = 6$$

$$\therefore \text{Rom size} = 2^x \times y = 2^6 \times 6 = 384.$$

② Rom as 4-bit squarer.

Ans:

$$x = 8$$



~~64~~

1111

1111

~~64~~

~~64 x 64~~

~~4 x 4~~

~~2 x 2~~

~~y = 8~~

$$x = 4$$

$$2^4 \times 8 = 16 \times 8 = 128$$

$$15 \times 15 = 225_{10}$$

$\therefore$

$$2^y > 225$$


$$y = 8, x = 4$$

$$\therefore \text{size} = 2^4 \times 8 = 128.$$

* PLA (Prog. Logic Array):

109

⇒ Prog. AND gates + Prog. OR gates.

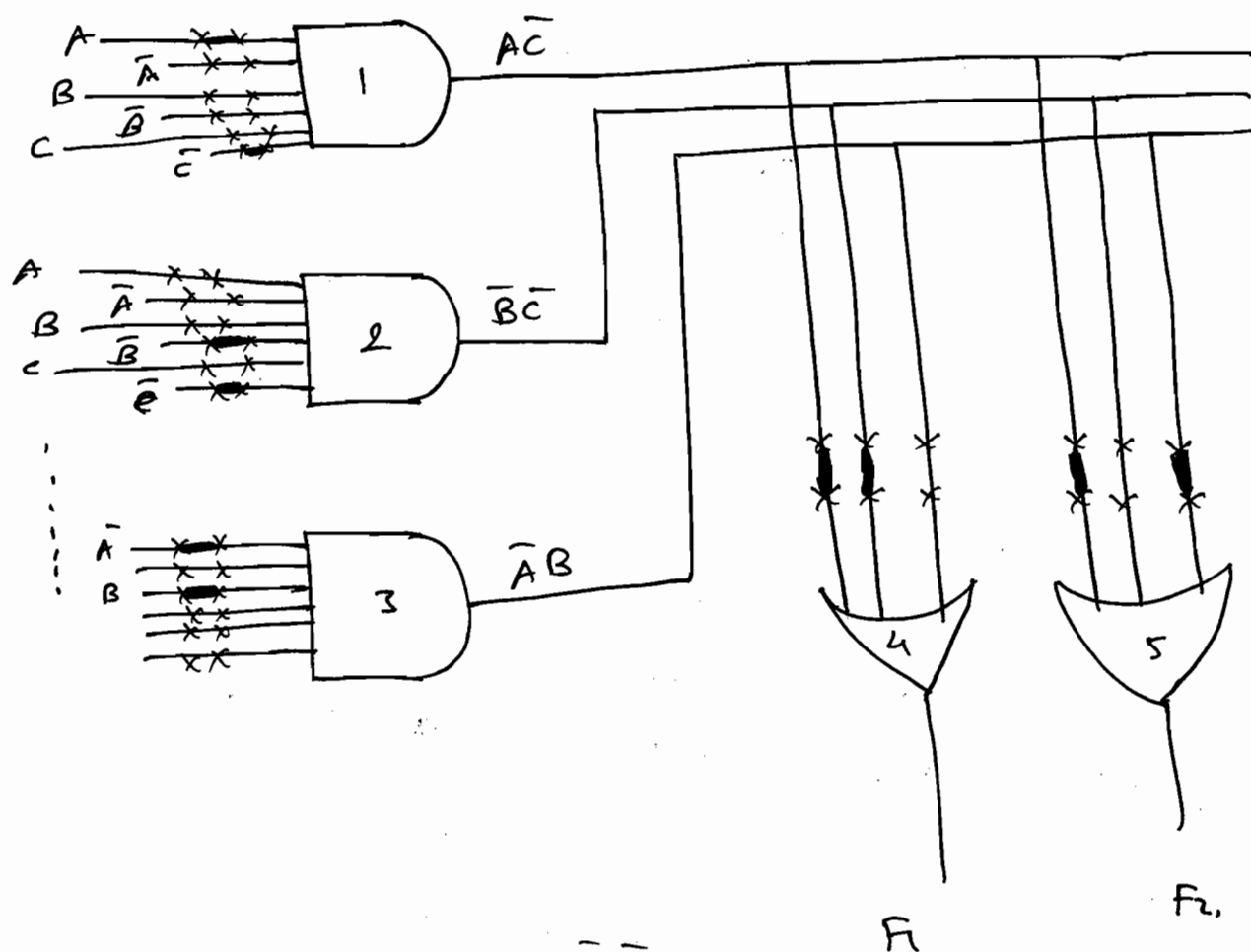

$$F_1(A, B, C) = A\bar{B}\bar{C} + \bar{A}B\bar{C}$$

$$F_2(A, B, C) = \bar{A}B + A\bar{C}$$

Product terms $\rightarrow$


$$P_1 = A\bar{B}\bar{C}$$

$$P_2 = \bar{A}B\bar{C}$$

$$P_3 = \bar{A}B$$

PLA size $\Rightarrow$ (3 inputs, 3 product terms, 2 outputs).

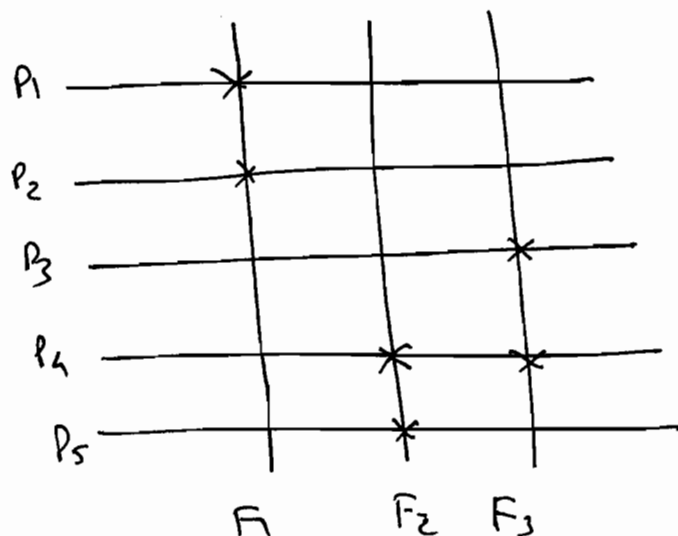Ex-1 In the following PLA Determine the product terms P_1, P_2, P_3, P_4, P_5



$$F_1(A, B, C) = \bar{A}B\bar{C} + A\bar{B}C + AB$$

$$= \bar{A}B\bar{C} + (\bar{B}C + B)A$$

$$= \bar{A}B\bar{C} + AC + AB$$

$$= B(\bar{A}\bar{C} + A) + AC$$

$$F_1(A, B, C) = \bar{A}B\bar{C} + AB + AC = \bar{A}B\bar{C} + AC$$

$$F_2(A, B, C) = \bar{A}\bar{B}\bar{C} + ABC + \bar{A}C$$

$$= \bar{A}\bar{B}\bar{C} + C(AB + \bar{A})$$

$$= \bar{A}\bar{B}\bar{C} + BC + \bar{A}B$$

$$= \bar{A}(\bar{B}\bar{C} + B) + BC$$

$$= \bar{A}(\bar{C} + B) + BC$$

$$F_2 = \bar{A}\bar{C} + \bar{A}B + BC = \bar{A}\bar{C} + BC$$

$$F_3 = \bar{A}B\bar{C} + BC + A\bar{B}C$$

$$= \bar{A}B\bar{C} + C(A + B)$$

$$= AC + BC + \bar{A}B\bar{C}$$

$$= AC + B(C + \bar{A})$$

$$= AC + BC + \bar{A}B$$

$$= AC + \bar{A}B$$

$F_1 =$

	BC			
	00	01	11	10
A	0			1
1		1		1

$$F_1 = \underline{AC} + BC$$

$F_2 =$

	BC			
	00	01	11	10
A	0	1		
1			1	

$$F_2 = \bar{A}\bar{B} + BC$$

$F_3 =$

	BC			
	00	01	11	10
A	0		1	1
1		1	1	

$$F_3 = \underline{AC} + \bar{A}B$$

$$\therefore P_2 = AC, P_1 = BC, P_3 = \bar{A}B$$

$$P_4 = \bar{A}B, P_5 = BC \text{ or}$$

$$P_5 = \bar{A}B, P_4 = BC$$

size = (3, 5, 3)
 (input product output term)

* PAL : Prog. AND gate + fixed OR gate.

GRAL : Generic Array logic

= Prog. AND gates + fixed OR gate

+ Prog. Output Logic

(E.g. Tri-state O/P, Normal d.p etc).

Ex-1 How many invalid 10 combinations occur at input of BCD adder?

Ans: No. of Invalid BCD combinations at Input.


= Total Input combinations
- No. of Valid combinations.

$$= (16 \times 16) - (10 \times 10) \\ = 156.$$

* Overflow:

- overflow is used in signed arithmetic.
- overflow occurs whenever the result exceeds the range of signed no.s.
- The overflow condition can be verified by the following methods:

①

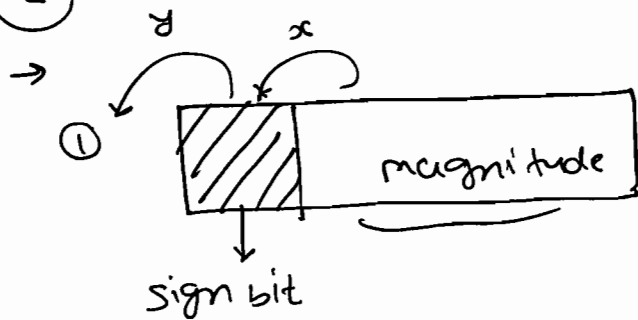

If $x=1$ and $y=0$ (or) $x=0$ and $y=1$ } overflow occurred.



② Overflow occurs if 2 +ve no.s are added the result is -ve or 2 -ve no.s are added the result is +ve.

E.g. Consider 2's comp. nos.

⑥ $\begin{array}{r} x=0 \\ y=1 \end{array}$

$$\begin{array}{r} 1 \ 0 \ 1 \ (-3) \\ + \ 1 \ 1 \ 0 \ (-2) \\ \hline 0 \ 0 \ 1 \end{array}$$

Overflow occurred
(or)

Two -ve nos are added result is +ve

⑦ $\begin{array}{r} y=0 \rightarrow x=1 \\ 0 \ 1 \ 0 \ (2) \\ + \ 0 \ 1 \ 1 \ (3) \\ \hline 1 \ 0 \ 1 \ (-3) \end{array}$

Overflow occurred
(or)

Two +ve nos are added result is -ve

⑧ $\begin{array}{r} y=1 \rightarrow x=1 \\ 1 \ 1 \ 0 \ (-2) \\ + \ 1 \ 1 \ 0 \ (-2) \\ \hline 1 \ 0 \ 0 \ (-4) \end{array}$

No overflow

Ex-1

$$\begin{array}{r} x \\ + y \\ \hline z \end{array}$$

overflow

If $x=1, y=1$ but $z=0$
(or)

$x=0, y=0$ but $z=1$

Expression for overflow i.e. $\bar{x} \cdot \bar{y} \cdot z + x \cdot y \cdot \bar{z}$