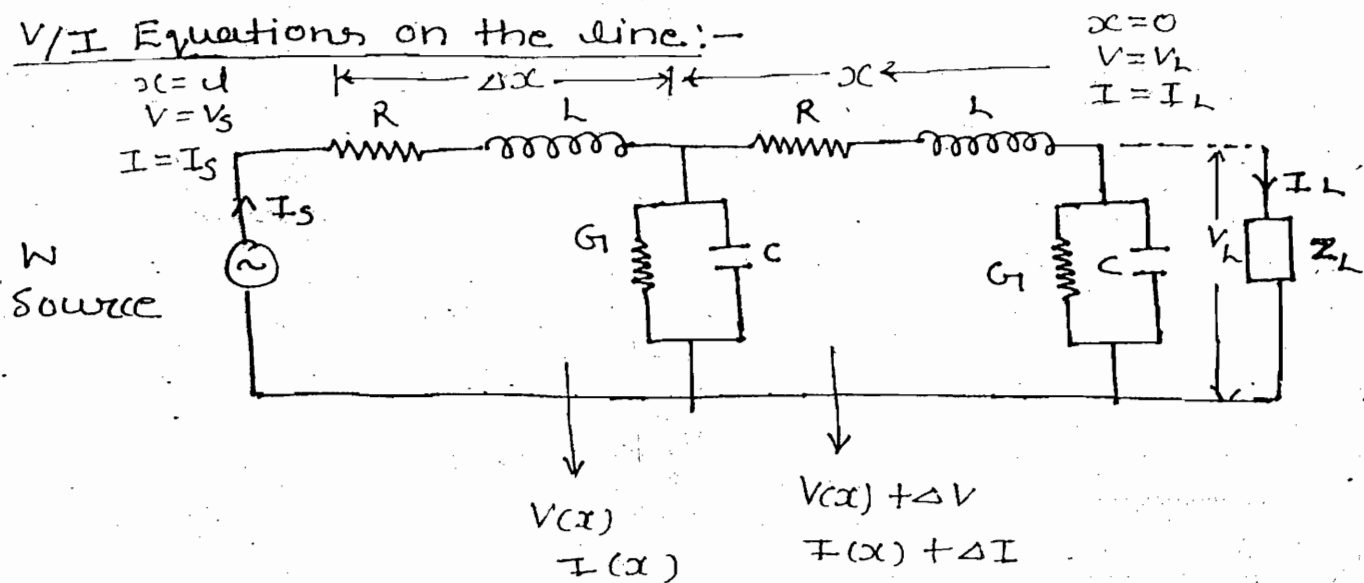


Lecture - 12

V/I Equations on the line:-



$$Z_{\text{series of } \Delta x \text{ length}} = (R + j\omega L) \cdot \Delta x$$

$$Y_{\text{shunt of } \Delta x \text{ length}} = (G + j\omega C) \cdot \Delta x$$

$$\Delta V = I (R + j\omega L) \cdot \Delta x$$

$$\frac{\Delta V}{\Delta x} = \frac{dV}{dx} = (R + j\omega L) I \quad \text{--- (I)}$$


$$\frac{\Delta I}{\Delta x} = \frac{dI}{dx} = (G + j\omega C) V \quad \text{--- (II)}$$

Take I from (I) & put in (II)

$$\frac{d}{dx} \left[\left(\frac{1}{R + j\omega L} \right) \frac{dV}{dx} \right] = (G + j\omega C) V$$

$$\frac{d^2 V}{dx^2} = (R + j\omega L) (G + j\omega C) \quad \text{--- (III)}$$
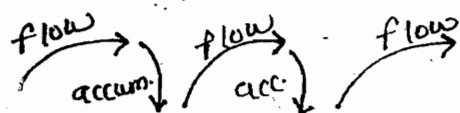
$$\frac{d^2 I}{dx^2} = (R + j\omega L) (G + j\omega C) \quad \text{--- (IV)}$$



→ meaning of Harmonic

Note:-

If the source is time harmonic at one end the effect is space harmonic all along the length of the line.

Let $\sqrt{(R+j\omega L)(G+j\omega C)} = Y$ (per cm)
 Eq-(III) & (IV) can be written as Unit

$$\frac{d^2 V}{dx^2} - Y^2 V = 0$$

$$\frac{d^2 I}{dx^2} - Y^2 I = 0$$

The V/I solution on the line is

$$V(x) = c_1 e^{-Yx} + c_2 e^{Yx} \quad \text{--- (V)}$$

$$I(x) = c_3 e^{-Yx} + c_4 e^{Yx} \quad \text{--- (VI)}$$

Applying initial conditions, $(x=0, V=V_L, I=I_L)$

$$V_L = c_1 + c_2 \quad \text{--- (VII)}$$

$$I_L = c_3 + c_4 \quad \text{--- (VIII)}$$

Using eq-(I) in eq-(V)

$$\frac{dV}{dx} = -Y c_1 e^{-Yx} + Y c_2 e^{Yx} = (R+j\omega L) I$$

Put $x=0$

$$\begin{aligned} \frac{c_2 - c_1}{\sqrt{(R+j\omega L)(G+j\omega C)}} &= \frac{(R+j\omega L) I_L}{\sqrt{(R+j\omega L)(G+j\omega C)}} \\ &= \sqrt{\frac{R+j\omega L}{G+j\omega C}} I_L = I_L Z_0 \end{aligned}$$

$$\text{where } Z_0 = \sqrt{\frac{R+j\omega L}{G+j\omega C}}$$

$$I_L Z_0 = c_2 - c_1 \quad \text{--- (IX)}$$

$$\text{Similarly } \frac{V_L}{Z_0} = c_4 - c_3 \quad \text{--- (X)}$$

$$\boxed{c_1 = \frac{V_L - I_L Z_0}{2} \quad c_2 = \frac{V_L + I_L Z_0}{2}}$$

$$\zeta_3 = \frac{I_L - V_L/Z_0}{2}, \quad \zeta_4 = \frac{I_L + V_L/Z_0}{2}$$

$$V(x) = \frac{V_L}{2} \left[\left(1 - \frac{Z_0}{Z_L}\right) e^{-\gamma x} + \left(1 + \frac{Z_0}{Z_L}\right) e^{\gamma x} \right]$$

$$V(x) = \frac{V_L (Z_L + Z_0)}{2Z_L} \left[e^{\gamma x} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-\gamma x} \right]$$

$$V(x) = V_0 \left(e^{\gamma x} + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-\gamma x} \right)$$



$$I(x) = \frac{I_L (Z_L + Z_0)}{2Z_0} \left[e^{\gamma x} + \left(\frac{Z_0 - Z_L}{Z_0 + Z_L} \right) e^{-\gamma x} \right]$$

$e^{\gamma x} \rightarrow -x$, Source-load forward wave

$e^{-\gamma x} \rightarrow +x$, load-source, reflected wave

→ Every transmission line has two waveforms i.e. the forward and reflected and the reflected wave does not exist in one single condition i.e. $Z_L = Z_0$. This is called as matched condition and this is a condition where complete source power is absorbed by the load.

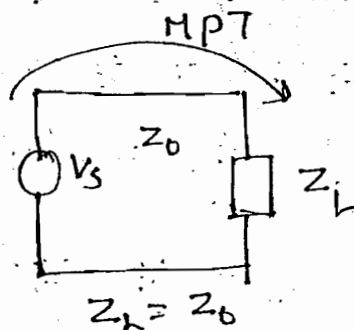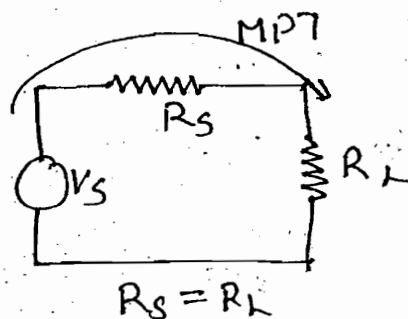
→ This is similar to max. power transfer in N/w or EM wave reflections b/w materials



Note:-

Z_0 is a unique impedance of the line with which if the line is terminated the reflections on the line and hence called as characteristic impedance

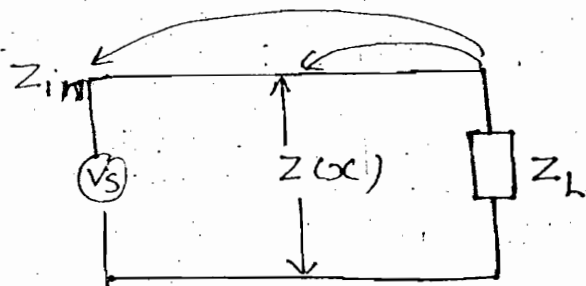Impedance on line (Z) and i/p impedance (Z_{in}):-



Note:-

Due to the loaded one end and primary constant in the line, impedance is different on different point of line such that

$$Z(x) = \frac{V(x)}{I(x)} \quad Z_{in} = Z(l)$$

$$V(x) = \frac{V_L}{Z_L} \left(\frac{(Z_L + Z_0)}{2} e^{\gamma x} + \frac{(Z_L - Z_0)}{2} e^{-\gamma x} \right)$$


$$V(x) = V_L \cosh(\gamma x) + I_L Z_0 \sinh(\gamma x)$$

Similarly

$$I(x) = I_L \cosh(\gamma x) + \frac{V_L}{Z_0} \sinh(\gamma x)$$

$$Z(x) = Z_0 \left[\frac{Z_L \cosh(\gamma x) + Z_0 \sinh(\gamma x)}{Z_0 \cosh(\gamma x) + Z_L \sinh(\gamma x)} \right]$$

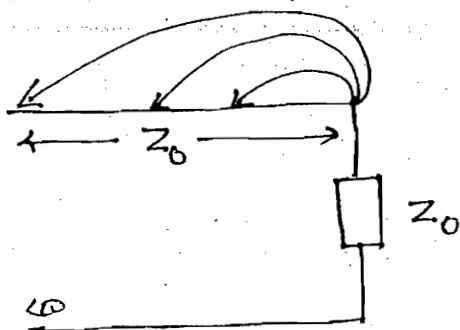If $Z_L = Z_0$ then $Z(x) = Z_0 = Z_L = Z_{in}$



Matched line

→ For a matched line the impedance anywhere on the line is also same Z_0

Note:-

Z_0 is that unique impedance with which if the line is terminated impedance on the line is also the same

Short circuit and open circuit lines:-

→ If $Z_L = 0 \Rightarrow$ SC line

$$Z_{in} = Z_{sc} = Z_0 \tanh(\gamma x)$$

→ If $Z_L = \infty \Rightarrow$ O.C line

$$Z_{in} = Z_{oc} = Z_0 \coth(\gamma x)$$

$$\Rightarrow \boxed{Z_0 = \sqrt{Z_{sc} \cdot Z_{oc}}}$$

It is geometric mean of S.C and O.C i/p impedances.



eg:-

$$Z_{oc} = 115 \Omega$$


$$Z_{sc} = 15 + \frac{100 \cdot 200}{100 + 200}$$

$$= 81.67 \Omega$$

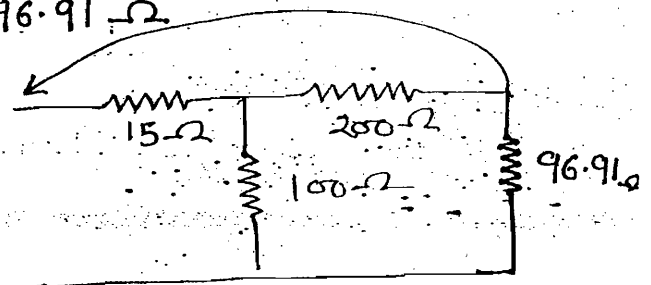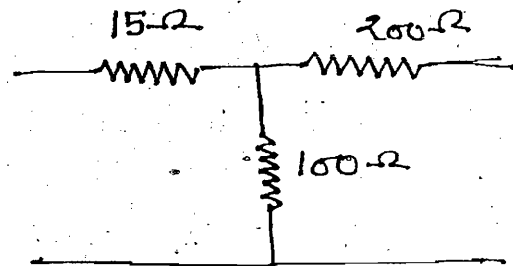
$$Z_0 = \sqrt{81.67 \times 115} = 96.91 \Omega$$



$$Z_{sc} = R + j\omega L$$

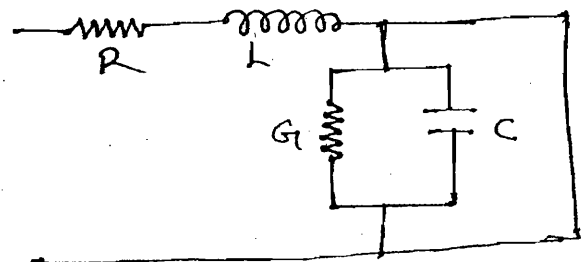

$$Z_{oc} = \frac{1}{G + j\omega C}$$

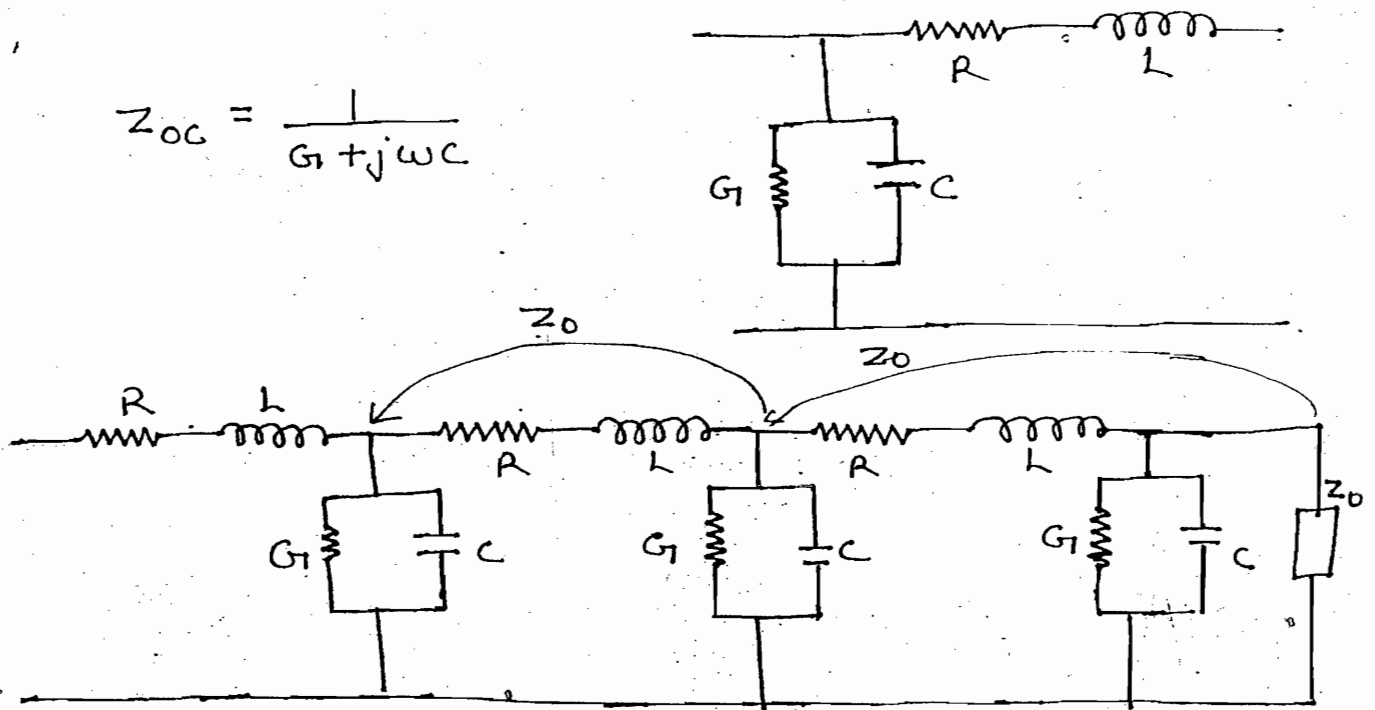

Note:-

- Any N/w either discrete or continuous when terminated with its characteristic impedance the same impedance appears on other end
- For a transmission line whose every RLC branch having Z_0 characteristic impedance when terminated with Z_0 at one end the loading effect appears to be the same anywhere on the line.
- Lossless line and distortionless line,

$$Y = \sqrt{R}$$

Lossless line and distortionless line:-

$$Y = \sqrt{(R + j\omega L)(G + j\omega C)} = \text{propagation constant} \\ = \alpha + j\beta$$

If $\alpha = 0$ everywhere on the line, the line is said to be lossless

$$(I) R = G = 0$$

$$(II) \left. \begin{array}{l} \omega L \gg R \\ \omega C \gg G \end{array} \right\} \text{High frequency lines}$$

$$Y = j\omega \sqrt{LC} \quad (\text{purely imaginary})$$

$$= j\beta$$

$$\beta = \omega \sqrt{LC}$$

$$v_p = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{\mu_0 \epsilon_0 \epsilon_r}} = \frac{3 \times 10^8}{\sqrt{\epsilon_r}}$$

$$Z_0 = \sqrt{\frac{R + j\omega L}{G + j\omega C}} = \sqrt{\frac{L}{C}} = \text{real}$$

$$= \sqrt{\frac{\mu_0 \ln(b/a) \ln(b/a)}{2\pi \cdot 2\pi \epsilon}}$$

$$= \sqrt{\frac{\mu_0}{\epsilon_0 \epsilon_r}} \cdot \frac{\ln(b/a)}{2\pi}$$

$$\boxed{Z_0 = \frac{60 \ln(b/a)}{\sqrt{\epsilon_r}}} \rightarrow \text{Co-Axial cable}$$

→ Z_0 is a design aspect of the line and depends on the cable dimensions but not on R, L, G, C or operational frequency of the line.

$$\boxed{Z_0 = \frac{120 \ln(b/a)}{\sqrt{\epsilon_r}}} \rightarrow \text{Parallel wire}$$

Distortionless line:-

If the phase is linear the wave is said to be distortionless i.e. $\beta \propto \omega$ → For distortionless line

→ Equal Rise time = Full time is characteristic of distortionless line.

Series arm time constant = Shunt arm time constant

$$\frac{L}{R} = \frac{C}{G} \Rightarrow \boxed{LG = RC}$$

$$Y = \sqrt{R \left(1 + j\omega L/R\right) G \left(1 + j\omega C/G\right)}$$

$$= \sqrt{RG} \left(1 + \frac{j\omega L}{R}\right) = \text{Complex}$$

$$Z_0 = \sqrt{\frac{R \left(1 + j\omega L/R\right)}{G \left(1 + j\omega C/G\right)}} = \sqrt{\frac{R}{G}} = \text{Real}$$

Note:-

Every lossless line $\Rightarrow$ Distortionless $\nRightarrow$ lossless


$$R = G = 0 \longrightarrow LG = RC$$

$$\beta = \omega \sqrt{LC} \longrightarrow \beta \propto \omega$$

Workbook:-

$$1) \quad Z_{in} = Z_0 \left[\frac{Z_L \cosh(j\beta l) + Z_0 \sinh(j\beta l)}{Z_0 \cosh(j\beta l) + Z_L \sinh(j\beta l)} \right]$$

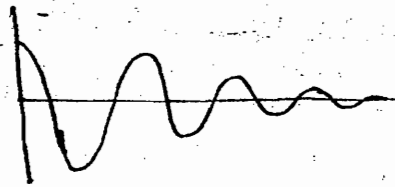
$$\cosh \theta = \frac{e^{\theta} + e^{-\theta}}{2}$$



$$\sinh(j\theta) = j \sin \theta$$

$$\cosh(j\theta) = \frac{e^{j\theta} + e^{-j\theta}}{2}$$

↓ = $\cos \theta$

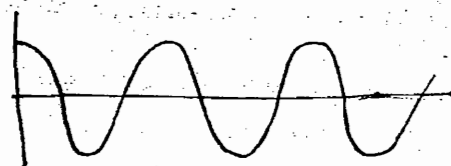

$$Z_{in} = Z_0 \left[\frac{Z_L \cos \beta l + j Z_0 \sin \beta l}{Z_0 \cos \beta l + j Z_L \sin \beta l} \right]$$

$$(i) \quad l = \frac{\lambda}{8} \quad \beta l = \frac{2\pi}{\lambda} \cdot \frac{\lambda}{8} = \frac{\pi}{4}$$

$$Z_{in} = Z_0 \left[\frac{Z_L + j Z_0}{Z_0 + j Z_L} \right]$$

$$(ii) \quad l = \lambda/4 \quad \beta l = \frac{\pi}{2} \quad Z_{in} = \frac{Z_0^2}{Z_L}$$

$$(iii) \quad l = \frac{\lambda}{2} \quad \beta l = \pi \quad Z_{in} = Z_L$$

$$Z_L = j50 \quad Z_0 = 50 \Omega$$

$$Z_{in} = 50 \left[\frac{j50 + j50}{50 + j50} \right] = \infty \rightarrow o/c$$

$$Z_{in} \quad (l/4) = \frac{50 \times 50}{j50} = -j50 \Omega$$

$$Z_{in} \quad (l/2) = Z_L = j50 \Omega$$


Note 1:-

→ βl is a critical aspect of the line that decides the nature and performance of the line and it is called an electrical path length.

→ length/ λ relationship is a critical aspect.

Note 2:-
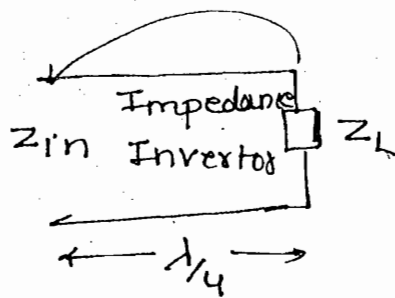
$$l = \lambda/4 \quad Z_{in} = \frac{Z_0^2}{Z_L}$$



It's one end impedance has opposite nature to other end impedance hence called as impedance inverter

Note 3:-

$$l = \lambda/2 \quad Z_{in} = Z_L$$



It is called as impedance reflector

Note 4:-

If $l \rightarrow 0$ or $l \rightarrow \infty$ where $\beta l \rightarrow 0$

$$Z(x) = Z_L$$

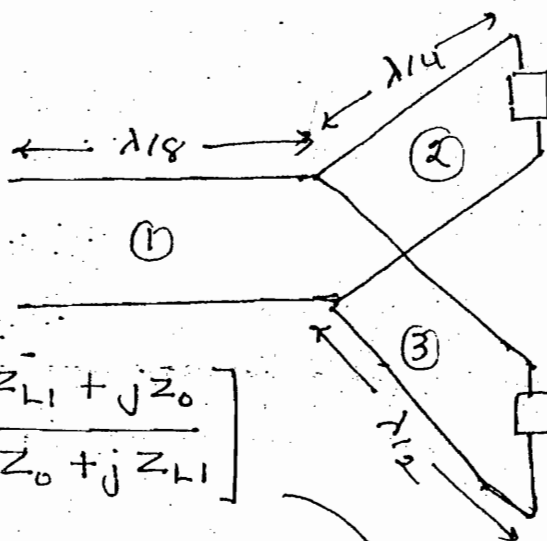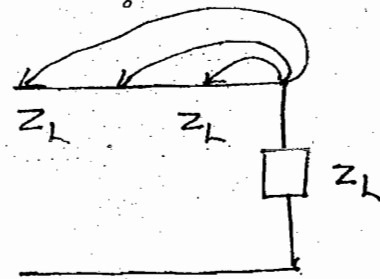For electrically short line the wire is a simple connecting wire or a short ckt



$$Z_{in2} = \frac{R_0^2}{R_0/2} = 2R_0$$

$$Z_{in1} = Z_0 \left[\frac{Z_L + jZ_0}{Z_0 + jZ_L} \right]$$

$$Z_{in3} = 2R_0$$

$$Z_L = Z_{in2} \parallel Z_{in3} = R_0 \left[\frac{R_0 + jR_0}{R_0 + jR_0} \right]$$

$$= R_0$$

When $z_{in2} = \frac{R_0^2}{2R_0} = \frac{R_0}{2}$ Interchanged

$$z_{in3} = \frac{R_0}{2} \quad (\lambda/2)$$

$$z_{in1} = z_0 \left[\frac{z_{L1} + jz_0}{z_0 + jz_{L1}} \right] = R_0 \left[\frac{R_0/4 + jR_0}{R_0 + j\frac{R_0}{4}} \right]$$

$$= R_0 \left[\frac{1 + j4}{4 + j} \right]$$

$$Y_{in} = Y_{in1} + Y_{in2}$$

$$Y_{in1} = \frac{z_L}{z_0^2} = 0 \quad (\lambda/4)$$


$$Y_{in2} = \frac{1}{z_L} = \frac{1}{-j50} \quad (\lambda/2)$$

$$= j0.02$$

$$Z_{in} = (Z_{in1} \parallel Z_{in2})$$

$$= (\infty \parallel -j50) = -j50$$

$$Y_{in} = j0.02 \Omega$$

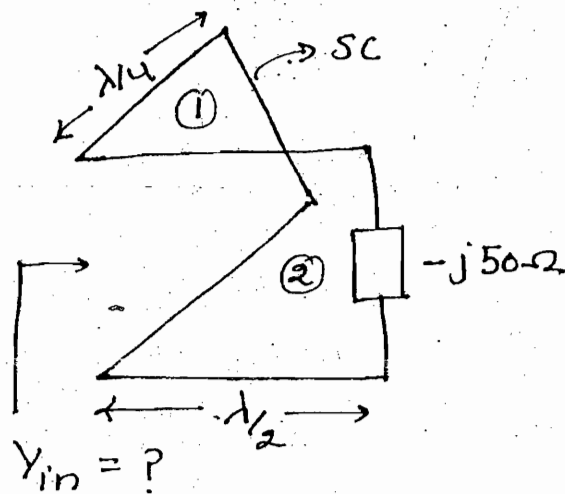


Stub $\Rightarrow$ SC line of finite length

$$Y_{in} = Y_{in1} + Y_{in2}$$

$$z_{in1} = z_0 \left[\frac{0 + jz_0}{z_0 + j0} \right] \quad (\lambda/8)$$

$$= jz_0 = j50 \Omega$$

$$Y_{in1} = \frac{1}{j50} = -j0.02$$

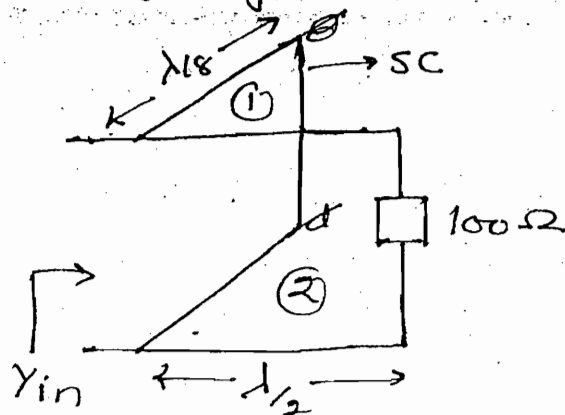

$$Y_{in2} = \frac{1}{Z_L} = \frac{1}{100} = 0.01$$

$$Y_{in} = Y_{in1} + Y_{in2} = 0.01 - j0.02 \text{ S}$$

8.

$$l = \lambda/4$$

$$Z_{in1} = R_0 \left[\frac{0 + jR_0}{R_0 + j0} \right]_{SC}$$

$$= jR_0$$



$$Z_{in2} = R_0$$

$$Z = \frac{jR_0 \cdot R_0}{jR_0 + R_0}$$

$$= \frac{jR_0}{j+1}$$

$$l = \lambda \quad Z = R_0$$

$$l = \lambda/8 \quad Z = SC$$

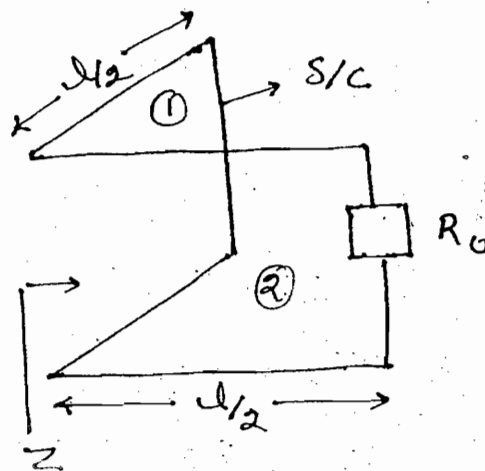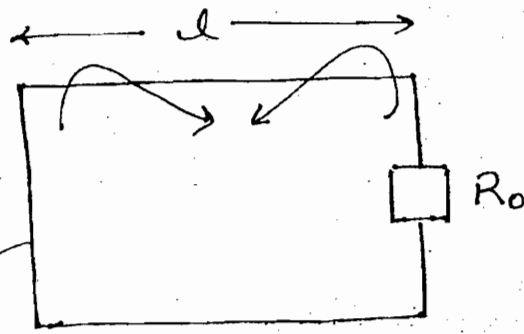

9.

$$V_p = 2 \times 10^8 \quad f = 10 \text{ MHz}$$

$$\lambda = 20 \text{ m}$$

$$l = 10 \text{ m} \quad \leftarrow l = \lambda/2$$

$$Z_{in} = Z_L = 30 - j40 \Omega$$

10.

$$f' = 5 \text{ MHz}$$

$$\lambda' = 40 \text{ m}$$

$$l = \frac{\lambda'}{4}$$

$$Z_{in} = \frac{Z_0^2}{Z_L} = \frac{50 \times 50}{30 - j40} = 30 + j40$$

11.

$$Z_{in} = j60 = Z_{sc} = Z_0 \tanh(j\beta l)$$

$$= jZ_0 \tanh \beta l$$

$$\beta l = \frac{\pi}{4}$$

$$= jZ_0$$

$$Z_0 = 60 \Omega$$

$$f' = 2f$$

$$12 \text{ MHz} \rightarrow 24 \text{ MHz}$$

$$\lambda' = \lambda/2$$

$$\beta l = 2\beta l = \pi/2$$

$$Z_{in} = Z_{sc} = jZ_0 \tan \pi/2 = \infty$$

$$f = 12 \text{ MHz}$$

$$Z_{in} = j60 = j\omega L \Rightarrow L = \frac{60}{2\pi \times 12 \times 10^6} = \frac{2.5}{\pi} \mu\text{H}$$

Summary:-

$$Z_{sc} = jZ_0 \tan \beta l$$

$$\left. \begin{array}{l} 0 < \beta l < \frac{\pi}{2} \\ 0 < l < \lambda/4 \end{array} \right\} Z_{in} \text{ is inductive}$$

$$\left. \begin{array}{l} \frac{\pi}{2} < \beta l < \pi \\ \lambda/4 < l < \lambda/2 \end{array} \right\} Z_{in} \text{ is capacitive}$$

$$Z_{oc} = -jZ_0 / \tan \beta l$$

$$Z_{in} \text{ inductive} \rightarrow Z_{in} \text{ is capacitive}$$

$$Z_{in} \text{ is capacitive} \rightarrow Z_{in} \text{ is inductive}$$

→ One end of a line is S.C or O.C then the other end is purely reactive

14. (a) $Z_{in} = -jZ_0$ For s/c line $\lambda/8$ length X
 $\downarrow$
 jZ_0

✓ (b) $Z_{in} = \pm j\infty$ for SC line $\lambda/4$ length

$$Z_{sc} = jZ_0 \tan \beta l$$

$$Z_{in} = \frac{Z_0^2}{Z_L}$$

✓ (c) $Z_{in} = -jZ_0 \rightarrow$ o/c line $\rightarrow \lambda/2$ length



$$Z_{in} = Z_L$$

✓ (d) $Z_{in} = Z_0$

15. $Z_0 = \sqrt{\frac{L}{C}} = \sqrt{\frac{LC}{C^2}} = \frac{\sqrt{\mu_0 \epsilon_0 \epsilon_R}}{C} = \frac{\sqrt{\epsilon_R}}{v_p \cdot C}$

16. (a) $\alpha = \text{even}$, $\beta = \text{odd}$ X

(b) $\alpha = \text{constant}$, $\beta = k\omega$ ✓

(c) X $\left(\frac{L}{C} = \text{constant} = \frac{R}{G} \right)$

(d) Matched line ($Z_L = Z_0$) X

17. $\beta l = \omega \sqrt{LC} l = 108^\circ$

Reflection Coefficient:-

$$V(x) = \underbrace{V_0 e^{j\beta x}}_{V_f} + \underbrace{V_0 \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta x}}_{V_r}$$

$$\frac{V_r}{V_f} = \text{Reflection coefficient for the voltages anywhere on the line} = \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j2\beta x}$$
$$= \Gamma(x)$$

$$\boxed{\Gamma(x) = \frac{Z(x) - Z_0}{Z(x) + Z_0}}$$

$$\text{At } x=0 \quad \Gamma_{\text{at load}} = \frac{Z_L - Z_0}{Z_L + Z_0} = \text{complex}$$

$$= |\Gamma| \angle \theta = \left| \frac{V_r}{V_f} \right| \angle \theta$$

$|\Gamma|$ $\rightarrow$ It is the ratio of reflected voltage to the forward voltage amplitude

$\angle \theta$ $\rightarrow$ It is the time delay or phase difference b/w the reflected and forward voltage.

Γ is the measure of mismatch b/w the expected impedance and the actual impedance Z_L at the load.

$\Gamma(x)$ is the measure of mismatch b/w the expected impedance Z_0 and the actual impedance $Z(x)$ anywhere on the line.

Note. -

$$(i) \quad \Gamma_I = \frac{Z_0 - Z_L}{Z_0 + Z_L} = -\Gamma_V$$

If V_f and I_f they are in phase

$$V_0 e^{j\beta x} + V_0 \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta x}$$

$$I_0 e^{j\beta x} - I_0 \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-j\beta x}$$

then V_r and I_r are out of phase by 180°

(ii)

$$0 \leq |\Gamma| \leq 1$$

Matched
line

Complete Reflection
(Mismatch)