

Thu – Science

1. Draw the diagram of an electric circuit using an electric cell, a bulb, wire and a switch.
2. Raj was studying on the desk with the table lamp on. Suddenly, the bulb of the table lamp got fuse. What could be the reason for the bulb to get fuse?
3. Rewrite the following incorrect sentences:-
 - a. The direction of electric current is from negative to positive terminal of the electric cell.
 - b. Electric cell has a metal disc which is its positive terminal.