# **Electronic Devices**

# **Question1**

# Which of the following circuits is reverse - biased ? [27-Jan-2024 Shift 1]

**Options:** 

A.

+2 V

B.



C.



D.

+ 2 V + 4 V

## Answer: D

## Solution:

**Solution:** P end should be at higher potential for forward biasing.

\_\_\_\_\_

# **Question2**

The truth table of the given circuit diagram is:



[27-Jan-2024 Shift 2]

### **Options:**

A. A B Y 001 010 100 111 B. A B Y 000 011 101 110 C. A B Y 000 010 100 111 D. A B Y 001 011

- 101
- 110

## Answer: B

## Solution:



 $Y = A \cdot B + A \cdot B$ This is XOR GATE



# **Question3**

In the given circuit, the breakdown voltage of the Zener diode is 3.0V. What is the value of  $\rm I_z$  ?



# [29-Jan-2024 Shift 1]

### **Options:**

A. 3.3 mA

B. 5.5 mA

C. 10 mA

D. 7 mA

Answer: B

## Solution:



 $V_z = 3V$ 

Let potential at B = 0VPotential at  $E(V_E) = 10V$ 

 $V_C = V_A = 3V$   $I_z + I_1 = I$   $I = \frac{10 - 3}{1000} = \frac{7}{1000}A$   $I_1 = \frac{3}{2000}A$ Therefore  $I_z = \frac{7 - 1.5}{1000} = 5.5 \text{ mA}$ 

# **Question4**

The truth table for this given circuit is :



# [29-Jan-2024 Shift 2]

**Options**:

A.

Α	в	Y
0	0	1
0	1	1
1	0	1
1	1	0

B.

А	В	Y
0	0	0
0	1	1
1	0	0
1	1	1

C.

Α	В	Y
0	0	0
0	1	0
1	0	0
1	1	1

D.

Α	в	Y
0	0	1
0	1	0
1	0	1
1	1	0

### Answer: B

Solution:



# **Question5**

A Zener diode of breakdown voltage 10V is used as a voltage regulator as shown in the figure. The current through the Zener diode is



[30-Jan-2024 Shift 1]

### **Options:**

A. 50 mA

B. 0

C. 30 mA

D. 20 mA

Answer: C



Zener is in breakdown region.

Zener is in breakdown region.

$$I_{3} = \frac{10}{500} = \frac{1}{50}$$

$$I_{1} = \frac{10}{200} = \frac{1}{20}$$

$$I_{2} = I_{1} - I_{3}$$

$$I_{2} = \left(\frac{1}{20} - \frac{1}{50}\right) = \left(\frac{3}{100}\right) = 30 \text{ mA}$$

\_\_\_\_\_

# **Question6**

In the given circuit, the voltage across load resistance ( $R_L$ ) is:



## [30-Jan-2024 Shift 2]

### **Options:**

A. 8.75V

B. 9.00V

C. 8.50V

D. 14.00V

### **Answer:** A

## **Solution:**



Identify the logic operation performed by the given circuit.





### **Options:**

A. NAND

B. NOR

C. OR

D. AND

Answer: C

# Solution:

 $Y = \overline{A \cdot B} = \overline{A} + \overline{B} = A + B$ 

(De-Morgan's law)

-----

# **Question8**

The output of the given circuit diagram is



# **Options**:

A.

	18 I I I I I I I I I I I I I I I I I I I	• • •
Α	в	Υ
0	0	0
1	0	0
0	1	0
1	1	1

В.

Α	В	Υ
0	0	0
1	0	1
0	1	1
1	1	0

C.

Α	в	Y
0	0	0
1	0	0
0	1	0
1	1	0

D.

Α	В	Y
0	0	0
1	0	0
0	1	1
1	1	0

## Answer: C



In the given circuit if the power rating of Zener diode is 10 mW, the value of series resistance  $\rm R_s$  to regulate the input unregulated supply is



## [1-Feb-2024 Shift 1]

## **Options:**

A. 5kΩ

Β. 10Ω

C.  $1k\Omega$ 

D.  $10k\Omega$ 

E. None of above

Answer: E

## Solution:



Pd across R

 $V_1 = 8 - 5 = 3V$ 

Current through the load resistor

$$I = \frac{5}{1 \times 10^3} = 5 \text{ mA}$$

Maximum current through Zener diode

$$I_{z \max} = \frac{10}{5} = 2 \text{ mA}$$

And minimum current through Zener diode

$$I_{z \text{ min.}} = 0$$
  

$$\therefore I_{s \text{ max.}} = 5 + 2 = 7 \text{ mA}$$
  
And  $R_{s \text{ min}} = \frac{V_1}{I_{s \text{ max}}} = \frac{3}{7} k\Omega$ 

Similarly

$$I_{s \min} = 5 \text{ mA}$$
  
And  $R_{s \max} = \frac{V_1}{I_{s \min}} = \frac{3}{5} \text{k}\Omega$   
$$\therefore \frac{3}{7} \text{k}\Omega < \text{R}_s < \frac{3}{5} \text{k}\Omega$$

\_\_\_\_\_

# **Question10**

Conductivity of a photodiode starts changing only if the wavelength of incident light is less than 660 nm. The band gap of photodiode is found

to be  $\left(\frac{X}{8}\right)$  eV. The value of X is : (Given, h = 6.6 × 10<sup>-34</sup> Js, e = 1.6 × 10<sup>-19</sup>C) [1-Feb-2024 Shift 2]

**Options:** 

A. 15

B. 11

C. 13

D. 21

Answer: A

```
E_{g} = \frac{hc}{\lambda} = \frac{6.6 \times 10^{-34} \times 3 \times 10^{8}}{660 \times 10^{-9}} J= \frac{6.6 \times 10^{-34} \times 3 \times 10^{8}}{660 \times 10^{-9} \times 1.6 \times 10^{-19}} eV= \frac{15}{8} eVSo x = 15
```

Given below are two statements : one is labelled as Assertion A and the other is labelled as Reason R

Assertion A : Photodiodes are preferably operated in reverse bias condition for light intensity measurement.

Reason R : The current in the forward bias is more than the current in the reverse bias for a p - n junction diode.

In the light of the above statement, choose the correct answer from the options given below :

[24-Jan-2023 Shift 1]

## **Options:**

A. A is false but R is true

- B. Both A and R are true but R is NOT the correct explanation of A  $% \mathcal{A}$
- C. A is true but R is false
- D. Both A and R are true and R is the correct explanation of A

## Answer: B

# Solution:

### Solution:

Photodiodes are operated in reverse bias as fractional change in current due to light is more easy to detect in reverse bias.

\_\_\_\_\_

# **Question12**

# The logic gate equivalent to the given circuit diagram is :



# [24-Jan-2023 Shift 2]

## **Options:**

A. OR

B. NAND

C. NOR

D. AND

Answer: B

# Solution:

 $Y = \overline{A_1 \odot B_1} NAND$ 

\_\_\_\_\_

# **Question13**

Given below are two statements : one is labeled as Assertion A and the other is labeled as Reason R

Assertion A: Photodiodes are used in forward bias usually for measuring the light intensity.

Reason R: For a p-n junction diode, at applied voltage V the current in the forward bias is more than the current in the reverse bias for

 $|V_z| > \pm V \ge |V_0|$  where  $V_o$  is the threshold voltage and  $V_z$  is the breakdown voltage.

In the light of the above statements, choose the correct answer from the options given below [25-Jan-2023 Shift 1]

## **Options:**

A. Both A and R are true and R is correct explanation A

B. Both A and R are true but R is NOT the correct explanation A

C. A is false but R is true

D. A is true but R is false

## Answer: C

# Solution:

### Solution:

Theory based Photodiodes are operated in reverse bias condition. For P-N junction current in forward bias (for  $V \ge V_0$ ) is always greater than current in reverse bias (. for  $V \le V_Z$ ). Hence Assertion if false but Reason is true

Statement I : When a Si sample is doped with Boron, it becomes P type and when doped by Arsenic it becomes N-type semi conductor such that P-type has excess holes and N-type has excess electrons.

Statement II : When such P-type and N-type semi-conductors, are fused to make a junction, a current will automatically flow which can be detected with an externally connected ammeter.

In the light of above statements, choose the most appropriate answer from the options given below. Options: [25-Jan-2023 Shift 2]

### **Options:**

A. Both Statement I and statement II are incorrect

B. Statement I is incorrect but statement II is correct

C. Both Statement I and statement II are correct

D. Statement I is correct but statement II is incorrect

### Answer: D

## Solution:

### Solution:

Statement - I is correct When P-N junction is formed an electric field is generated form N-side to P-side due to which barrier potential arises & majority charge carrier can not flow through the junction due to barrier potential so current is zero unless we apply forward bias voltage.

\_\_\_\_\_

# **Question15**

Which of the following statement is not correct in the case of light emitting diodes?

A. It is a heavily doped **p** – **n** junction.

B. It emits light only when it is forward biased.

C. It emits light only when it is reverse biased.

D. The energy of the light emitted is equal to or slightly less than the energy gap of the semiconductor used.

Choose the correct answer from the options given below : [29-Jan-2023 Shift 1]

## **Options:**

A. C and D

B. A

C. C

### D. B

### Answer: C

## Solution:

LED works in forward biasing and light energy maybe slightly less or equal to band gap.

-----

# **Question16**

## For the given logic gates combination, the correct truth table will be



[29-Jan-2023 Shift 2]

## **Options:**

A.

A	В	х
0	0	1
0	1	0
1	0	0
1	1	0

### B.

Α	в	х
0	0	0
0	1	1
1	0	1
1	1	0

## C.

A	В	X
0	0	1
0	1	0
1	0	1
1	1	0

D.



### Answer: B

## Solution:



# **Question17**

The output waveform of the given logical circuit for the following inputs A and B as shown below, is:



[30-Jan-2023 Shift 1]

**Options:** 

A.



Β.



## Solution:

 $\frac{(\overline{A \cdot A}) = \overline{A}}{\overline{B \cdot B} = \overline{B}}$  $(\overline{A \cdot B}) = A + B$ OR Gate

-----

# **Question18**

The output Y for the inputs A and B of circuit is given by



Truth table of the shown circuit is : [30-Jan-2023 Shift 2]

**Options:** 

A.

Β.

 $\begin{array}{c|ccccc} A & B & Y \\ \hline 0 & 0 & 1 \\ 0 & 1 & 0 \\ 1 & 0 & 0 \\ 1 & 1 & 1 \\ \end{array}$ C.  $\begin{array}{c|cccccc} A & B & Y \\ \hline 0 & 0 & 0 \\ 0 & 1 & 1 \\ 1 & 0 & 1 \\ 1 & 1 & 1 \\ \end{array}$ 

D.

### Answer: D

Solution:

**Solution:** Given circuit represent XOR.

-----

# **Question19**

The effect of increase in temperature on the number of electrons in conduction band (n<sub>e</sub>) and resistance of a semiconductor will be as: [31-Jan-2023 Shift 1]

### **Options:**

A. Both  $n_{\rho}$  and resistance decrease

B. Both  $n_{e}$  and resistance increase

C.  ${\rm n}_{\rm e}$  increases, resistance decreases

D.  $n_{_{\rm P}}$  decreases, resistance increases

Answer: C

## Solution:

### Solution:

As temperature increases, more electron excite to conduction band and hence conductivity increases, therefore resistance decreases.

-----

Given below are two statements: Statement I: In a typical transistor, all three regions emitter, base and collector have same doping level. Statement II: In a transistor, collector is the thickest and base is the thinnest segment. In the light of the above statements, choose the most appropriate answer from the options given below. [31-Jan-2023 Shift 2]

### **Options:**

- A. Both Statement I and Statement II are correct
- B. Both Statement I and Statement II are incorrect
- C. Statement I is incorrect but Statement II is correct
- D. Statement I is correct but Statement II is incorrect

### Answer: C

## Solution:

### Solution:

Emitter	Base	Collector
Moderate size	Thin	Thick
Maximum Doping	Minimum Doping	Moderate Doping

# **Question21**

# Match the List I with List II

List I	List II
A. IntrinsicSemiconductor	I. Fermi-level near conduction band
B. n-typesemiconductor	II. Fermi-level at middle
C. p-typesemiconductor	III. Fermi-level near valence band
D. Metals	IV. Fermi-level inside conduction band

## Choose the correct answer from the options given below: [1-Feb-2023 Shift 1]

### **Options:**

- A. (A)  $\rightarrow$  I, (B)  $\rightarrow$  II, (C)  $\rightarrow$  III, (D)  $\rightarrow$  IV
- B. (A)  $\rightarrow$  II, (B)  $\rightarrow$  I, (C)  $\rightarrow$  III, (D)  $\rightarrow$  IV

C. (A)  $\rightarrow$  II, (B)  $\rightarrow$  III, (C)  $\rightarrow$  I, (D)  $\rightarrow$  IV

D. (A)  $\rightarrow$  III, (B)  $\rightarrow$  I, (C)  $\rightarrow$  II, (D)  $\rightarrow$  IV

### Answer: C

### Solution:

Solution: Based on theory.

\_\_\_\_\_

# **Question22**

## Choose the correct statement about Zener diode: [1-Feb-2023 Shift 2]

### **Options:**

A. It works as a voltage regulator in reverse bias and behaves like simple pn junction diode in forward bias.

B. It works as a voltage regulator in both forward and reverse bias.

C. It works a voltage regulator only in forward bias.

D. It works as a voltage regulator in forward bias and behaves like simple pn junction diode in reverse bias.

**Answer:** A

## Solution:

**Solution:** Woks as voltage regulator in reverse bias and as simple P-n junction in forward bias.

\_\_\_\_\_

# **Question23**

## Name the logic gate equivalent to the diagram attached



[6-Apr-2023 shift 1]

### **Options:**

A. NOR

B. OR

C. NAND

D. AND

Answer: A

Solution:

Solution: NOR gate

\_\_\_\_\_

# **Question24**

# The resistivity ( $\rho$ ) of semiconductor varies with temperature. Which of the following curve represents the correct behavior [6-Apr-2023 shift 1]

**Options:** 

A.







C.



D.



Answer: C

## Solution:

#### Solution:

A semiconductor starts conduction more as the temperature increases. It means resistance decreases with increase in temperature. So, if temperature increases, its resistivity decreases.

```
Also, \rho = \frac{m}{ne^2\tau}
```

As Temperature increase,  $\tau$  decreases but n increases and n is dominant over  $\tau.$ 

\_\_\_\_\_

# **Question25**

Given below are two statements : one is labelled as Assertion A and the other is labelled as Reason R

Assertion A : Diffusion current in a p-n junction is greater than the drift current in magnitude if the junction is forward biased.

Reason R: Diffusion current in a p-n junction is from the n-side to the pside if the junction is forward biased. In the light of the above

statements, choose the most appropriate answer from the options given below

[6-Apr-2023 shift 2]

### **Options:**

A. A is not correct but R is correct

B. Both A and R are correct and R is the correct explanation of A

C. Both A and R are correct but R is NOT the correct explanation of A

D. A is correct but R is not correct

### Answer: D

## Solution:

Solution: Statement R is wrong as per the theory of p-n junction.

\_\_\_\_\_

# **Question26**

For the logic circuit shown, the output waveform at Y is:





# [8-Apr-2023 shift 1]

## **Options:**

A.



В.











### Answer: B





For a given transistor amplifier circuit in CE configuration  $V_{CC} = 1V$ ,  $R_C = 1k\Omega$ ,  $R_b = 100k\Omega$  and  $\beta = 100$ . Value of base current I<sub>b</sub> is



# [8-Apr-2023 shift 2]

## **Options:**

A.  $I_{b} = 100 \mu A$ 

B.  $I_{b} = 10 \mu A$ 

C.  $I_{b} = 0.1 \mu A$ 

D.  $I_{b} = 1.0 \mu A$ 

### Answer: B

## Solution:

Solution:  $V_{cc} = 1V$ 



A zener diode of power rating 1.6W is be used as voltage regulator. If the zener diode has a breakdown of 8V and it has to regulate voltage fluctuating between 3V and 10V. The value of resistance  $R_8$  for safe operation of diode will be



# [10-Apr-2023 shift 1]

## **Options:**

- Α. 13.3Ω
- Β. 13Ω
- C. 10Ω
- D. 12Ω

## Answer: C

# Solution:



# Question29

If each diode has a forward bias resistance of  $25\Omega$  in the below circuit,



## Which of the following options is correct: [10-Apr-2023 shift 2]

### **Options:**

A.  $\frac{I_1}{I_2} = 2$ B.  $\frac{I_2}{I_3} = 1$ C.  $\frac{I_3}{I_4} = 1$ 

D. 
$$\frac{I_1}{I_2} = 1$$

### Answer: A

## Solution:



Here we can see that  $D_1$  and  $D_3$  conducts but  $D_2$  is reversed biased. Current I  $_1$  will be equally distributed among I  $_3$  and I $_4$  and I $_3$  = 0

 $I_{1} = I_{2} + I_{4} + I_{3}$  $I_{1} = 2I_{2}$  $\frac{I_{1}}{I_{2}} = 2$ 



# Question30

The logic performed by the circuit shown in figure is equivalent to :



[11-Apr-2023 shift 1]

## **Options:**

A. NAND

- B. NOR
- C. AND
- D. OR
- Answer: C

## Solution:

\_\_\_\_\_

# Question31

The logic operations performed by the given digital circuit is equivalent to:



## [11-Apr-2023 shift 2]

**Options:** 

- A. OR
- B. NAND
- C. NOR
- D. AND
- **Answer: D**

- Solu<u>tion:</u>
- $Y = \overline{(A + B) \cdot (AB)}$
- $Y = (A + B) \cdot (AB)$ Y = AB + AB
- $Y = (A \cdot B)$
- Y = AND Gate



-----

# Question32

In an n-p-n common emitter (CE) transistor the collector current changes from 5 mA to 16 mA for the change in base current from 100µA and 200µA, respectively. The current gain of transistor is \_\_\_\_\_. [12-Apr-2023 shift 1]

**Options:** 

A. 110

B. 9

C. 0.9

D. 210

Answer: A

## Solution:

Solution: (1)  $\beta = \frac{\Delta I_C}{\Delta I_B}$   $\Delta I_C = 16 - 5 = 11 \text{ mA}, \Delta I_B = 200 - 100 = 100 \mu \text{A}$   $\beta = \frac{11 \times 10^{-3}}{100 \times 10^{-6}}$   $\beta = \frac{11000}{100}$  $\beta = 110$ 

# **Question33**

From the given transfer characteristic of a transistor in CE configuration, the value of power gain of this configuration is  $10^x$ , for  $R_B = 10k\Omega$ ,  $R_C = 1k\Omega$ . The value of x is \_\_\_\_\_



### Answer: 3

## Solution:

Current gain,  $\beta = \frac{\Delta I_C}{\Delta I_B}$   $\beta = \frac{10 \text{ mA}}{100 \mu \text{A}}$   $\beta = 100$ Power gain  $\beta^2 \frac{R_C}{R_B}$   $= 10^4 \times \frac{1}{10}$   $= 10^3$ So, x = 3

\_\_\_\_\_

# **Question34**

The output from a NAND gate having inputs A and B given below will be,



# [13-Apr-2023 shift 2]

### **Options:**

A.





### **Answer:** A

### Solution:

Truth table for NAND gate is

A	В	$Y = \overline{A.B}$
0	0	1
0	1	1
1	0	1
1	1	0

A	В	Y
1	1	0
0	0	1
0	1	1
1	0	1
1	1	0
0	0	1
0	1	1

On the basis of given input A and B the truth table is

\_\_\_\_\_

# **Question35**

A transistor is used in common-emitter mode in an amplifier circuit. When a signal of 10 mV is added to the base-emitter voltage, the base current changes by 10 $\mu$ A and the collector current changes by 1.5 mA. The load resistance is 5k $\Omega$ . The voltage gain of the transistor will be\_\_\_\_ [24-Jun-2022-Shift-1]

Answer: 750

**Solution:** 

 $R_{\rm B} = \frac{10 \times 10^{-3}}{10 \times 10^{-6}}$  $= 10^{3} \Omega$ 

$$\therefore A_{v} = \left(\frac{\Delta I_{C}}{\Delta I_{B}}\right) \times \left(\frac{R_{C}}{R_{B}}\right)$$

$$= \frac{1.5 \times 10^{-3}}{10 \times 10^{-6}} \times \frac{5 \times 10^{3}}{1 \times 10^{3}}$$

$$= \frac{1.5 \times 5}{10} \times (1000)$$

$$= 750$$

In the given circuit, the value of current  $I_L$  will be \_\_\_\_\_mA. (When  $R_L = 1k\Omega$ )  $\stackrel{800\Omega}{\longrightarrow}$   $\downarrow I_L$   $\downarrow I_V$   $\downarrow I_L$  $\downarrow R_L = 1k\Omega$ 



### Answer: 5

Solution:

V<sub>L</sub> = 5V as V<sub>Z</sub> = 5V  
∴I<sub>L</sub> = 
$$\frac{V_L}{R_L} = \frac{5}{10^3} = 5 \text{ mA}$$

------

# Question37

The photodiode is used to detect the optical signals. These diodes are preferably operated in reverse biased mode because : [25-Jun-2022-Shift-1]

### **Options:**

A. fractional change in majority carriers produce higher forward bias current

B. fractional change in majority carriers produce higher reverse bias current

C. fractional change in minority carriers produce higher forward bias current

D. fractional change in minority carriers produce higher reverse bias current

Answer: D

A photodiode is reverse biased. When light falling on it produces charge carriers, the fractional change, in minority carriers is high since the original current is very small.

\_\_\_\_\_

# Question38

# Identify the logic operation performed by the given circuit:



[25-Jun-2022-Shift-2]

### **Options:**

A. AND gate

B. OR gate

C. NOR gate

D. NAND gate

### **Answer:** A

## Solution:

```
Solution:
According to the circuit,
Y = (A + B)
\Rightarrow Y = AB
\Rightarrow AND gate
```

\_\_\_\_\_

# **Question39**

In an experiment of CE configuration of n - p - n transistor, the transfer characteristics are observed as given in figure.



If the input resistance is  $200\Omega$  and output resistance is  $60\Omega$ , the voltage gain in this experiment will be\_\_\_\_\_ [25-Jun-2022-Shift-2]

## Solution:

Voltage gain = 
$$\frac{I_C R_0}{I_B R_i}$$
  
=  $\frac{(10 \text{mA})(60 \Omega)}{(200 \mu \text{A})(200 \Omega)}$   
 $\Rightarrow$  Voltage gain = 15

# **Question40**

The I-V characteristics of a p-n junction diode in forward bias is shown in the figure. The ratio of dynamic resistance, corresponding to forward bias voltage of 2V and 4V respectively, is :



### **Options:**

A. 1 : 2

B. 5 : 1

C. 1:40

D. 20 : 1

Answer: B

## Solution:

 $\therefore R = \frac{\Delta v}{\Delta i}$ Now, dynamic resistance at V = 2V is  $R_2 = \frac{0.1}{5 \times 10^{-3}} \Omega$   $= 20\Omega$ Similarly,  $R_4 = \frac{0.2}{50 \times 10^{-3}} = 4\Omega$   $\frac{R_2}{R_4} = \frac{5}{1}$ 

### \_\_\_\_\_

# **Question41**

As per the given circuit, the value of current through the battery will be\_\_\_\_\_A.





Answer: 1

## Solution:



\_\_\_\_\_

# **Question42**

The positive feedback is required by an amplifier to act an oscillator. The feedback here means : [26-Jun-2022-Shift-2]

### **Options:**

- A. External input is necessary to sustain ac signal in output.
- B. A portion of the output power is returned back to the input.
- C. Feedback can be achieved by LR network.
- D. The base-collector junction must be forward biased.

### Answer: B

## Solution:

When the amplifier connects with positive feedback, it acts as the oscillator the feedback here is positive feedback which

means some amount of voltage is given to the input.

\_\_\_\_\_

# **Question43**

Identify the correct Logic Gate for the following output (Y) of two inputs A and B.



[27-Jun-2022-Shift-1]

**Options:** 

A.



В.



C.



D.



Answer: B

Solution:



------

# **Question44**

# For a transistor to act as a switch, it must be operated in [27-Jun-2022-Shift-2]

### **Options:**

A. Active region.

B. Saturation state only.

C. Cut-off state only.

D. Saturation and cut-off state.

Answer: D

## Solution:

### Solution:

Transistor act as a switch in saturation and cut ofregion.

\_\_\_\_\_

# **Question45**

The cut-off voltage of the diodes (shown in figure) in forward bias is 0.6V. The current through the resister of  $40\Omega$  is \_\_\_\_\_ mA.



[27-Jun-2022-Shift-2]

### Answer: 4

D <sub>1</sub> : conducting
D <sub>2</sub> : open circuit
$i = \frac{1 - 0.6}{60 + 40} A$
$= \frac{0.4}{100} A$
$\Rightarrow$ i = 4 mA

In the following circuit, the correct relation between output (Y) and inputs A and B will be :



[28-Jun-2022-Shift-1]

### **Options:**

A. Y = AB

B. Y = A + B

C. Y =  $\overline{AB}$ 

D. Y =  $\overline{A + B}$ 

### Answer: C

## Solution:

This is NAND gate

А	В	Y
0	0	1
1	0	1
0	1	1
1	1	0


## **Question47**

# For using a multimeter to identify diode from electrical components, choose the correct statement out of the following about the diode : [28-Jun-2022-Shift-1]

#### **Options:**

A. It is two terminal device which conducts current in both directions.

B. It is two terminal device which conducts current in one direction only.

C. It does not conduct current gives an initial deflection which decays to zero. It is three terminal device which conducts current in one direction only between central terminal and either of the remaining

D. two terminals

Answer: B

#### Solution:

**Solution:** In forward bias diode conducts In revers bias it does not conducts

\_\_\_\_\_

## **Question48**

Given below are two statements : One is labelled as Assertion A and the other is labelled as Reason R.

Assertion A : n-p-n transistor permits more current than a p-n-p transistor.

**Reason R : Electrons have greater mobility as a charge carrier.** 

## Choose the correct answer from the options given below : [28-Jun-2022-Shift-1]

#### **Options:**

A. Both A and R are true, and R is correct explanation of A.

B. Both A and R are true but R is NOT the correct explanation of A.

C. A is true but R is false.

D. A is false but R is true.

Answer: A

#### Solution:

(A) is true as n - p - n transistor permits more current than p - n - p transistor as electrons which are majority charge carriers in n-p-n have higher mobility than holes which are majority carriers in p-n-p transistor.  $\Rightarrow$  Statement R is correct explanation of statement A.

## **Question49**

In the given circuit the input voltage V<sub>in</sub> is shown in figure. The cut-in voltage of p-n junction diode ( $D_{1.}$  or  $.D_2$ ) is 0.6V. Which of the following output voltage (V<sub>0</sub>) waveform across the diode is correct?



#### [28-Jun-2022-Shift-2]

**Options:** 

A.



Β.







C.



#### Answer: D

#### Solution:

Till  $|V| \le 0.6V$  $|V_0| = |V|$ So correct graph will be D.

## **Question50**

A zener of breakdown voltage  $V_z = 8V$  and maximum zener current,  $I_{ZM} = 10 \text{ mA}$  is subject to an input voltage  $V_i = 10V$  with series resistance  $R = 100\Omega$ . In the given circuit  $R_L$  represents the variable load resistance. The ratio of maximum and minimum value of  $R_L$  is\_\_\_\_\_

![](_page_38_Figure_8.jpeg)

[28-Jun-2022-Shift-2]

#### Answer: 2

#### Solution:

Minimum value of  $\rm R_L$  for which the diode is shorted is  $\frac{\rm R_L}{\rm R_L+100}\times 10=8 \Rightarrow \rm R_L=400\Omega$  For maximum value of  $\rm R_L$ , current through diode is  $10\,\rm mA$  So  $\rm i_R=\rm i_{R_L}+I_{Z\,M}$ 

$$\frac{2}{100} = \frac{8}{R_{L}} + 10 \times 10^{-3}$$
$$10 \times 10^{-3} = \frac{8}{R_{L}}$$
$$R_{L} = 800\Omega$$
So  $\frac{R_{Lmax}}{R_{Lmin}} = 2$ 

\_\_\_\_\_

## Question51

A transistor is used in an amplifier circuit in common emitter mode. If the base current changes by 100µA, it brings a change of 10 mA in collector current. If the load resistance is  $2k\Omega$  and input resistance is  $1k\Omega$ , the value of power gain is  $x \times 10^4$ . The value of x is\_\_\_\_\_ [29-Jun-2022-Shift-1]

#### Answer: 2

#### Solution:

Power gain =  $\left[\frac{\Delta i_{C}}{\Delta i_{B}}\right]^{2} \times \frac{R_{o}}{R_{i}}$ =  $\left[\frac{10^{-2}}{10^{-4}}\right]^{2} \times \frac{2}{1}$ =  $2 \times 10^{4}$  $\Rightarrow x = 2$ 

## **Question52**

A potential barrier of 0.4V exists across a p-n junction. An electron enters the junction from the n-side with a speed of  $6.0 \times 10^5 \text{ms}^{-1}$ . The speed with which electron enters the p side will be  $\frac{x}{3} \times 10^5 \text{ms}^{-1}$  the value of x is\_\_\_\_\_ (Given mass of electron =  $9 \times 10^{-31}$  kg, charge on electron

 $= 1.6 \times 10^{-19}$ C.) [29-Jun-2022-Shift-2]

Answer: 14

Conserving energy,  

$$\frac{1}{2}mv^{2} = \frac{1}{2}m(6 \times 10^{5})^{2} - 0.4 \text{ eV}$$

$$\Rightarrow v = \sqrt{(6 \times 10^{5})^{2} - \frac{2 \times 1.6 \times 10^{-19} \times 0.4}{9 \times 10^{-31}}}$$

$$= \sqrt{36 \times 10^{10} - \frac{1.28}{9} \times 10^{12}}$$

$$\Rightarrow v = \frac{14}{3} \times 10^{5} \text{m/s}$$

$$\Rightarrow x = 14$$

## **Question53**

In the circuit, the logical value of A = 1 or B = 1 when potential at A or B is 5V and the logical value of A = 0 or B = 0 when potential at A or B is 0V.

![](_page_40_Figure_3.jpeg)

The truth table of the given circuit will be : [25-Jul-2022-Shift-1]

**Options:** 

Given circuit is equivalent to an AND gate.
ABY
000
010
100
111

\_\_\_\_\_

## **Question54**

Two ideal diodes are connected in the network as shown in figure. The equivalent resistance between A and B is  $\__\Omega$ .

![](_page_41_Figure_4.jpeg)

[25-Jul-2022-Shift-2]

Answer: 25

**Solution:** 

![](_page_41_Figure_8.jpeg)

\_\_\_\_\_

## Question55

In the circuit shown below, maximum zener diode current will be\_\_\_ mA.

![](_page_41_Figure_12.jpeg)

#### Solution:

![](_page_42_Figure_2.jpeg)

## **Question56**

The typical transfer characteristics of a transistor in CE configuration is shown in figure. A load resistor of  $2k\Omega$  is connected in the collector branch of the circuit used. The input resistance of the transistor is 0.50k $\Omega$ . The voltage gain of the transistor is \_\_\_\_\_.

![](_page_42_Figure_5.jpeg)

#### Answer: 200

#### Solution:

#### Solution:

Current gain in C – E configuration  $\Rightarrow \beta = \frac{\Delta I_C}{\Delta I_B}$   $R_C = 2k\Omega, R_B = 0.50k\Omega$ Voltage gain =  $\frac{\Delta I_C R_C}{\Delta I_B R_B} = \frac{5 \times 10^{-3}}{100 \times 10^{-6}} \times \frac{2}{0.5}$   $= \frac{10^{-2}}{5 \times 10^{-5}} = \frac{1000}{5} = 200$ 

## **Question57**

A logic gate circuit has two inputs A and B and output Y. The voltage waveforms of A, B and Y are shown below.

![](_page_43_Figure_2.jpeg)

The logic gate circuit is : [27-Jul-2022-Shift-1]

#### **Options:**

A. AND gate

B. OR gate

C. NOR gate

D. NAND gate

#### **Answer:** A

#### Solution:

#### Solution:

By making Truth table

A	В	Output
0	0	0
1	1	1
0	1	0
1	0	0

Comparing with output of AND gate

A	В	AND
0	0	0
0	1	0
1	0	0
1	1	1

⇒ logic gate present is AND gate

\_\_\_\_\_

## **Question58**

For a constant collector-emitter voltage of 8V, the collector current of a

#### transistor reached to the value of 6 mA from 4 mA, whereas base current changed from 20µA to 25µA value. If transistor is in active state, small signal current gain (current amplification factor) will be : [27-Jul-2022-Shift-2]

#### **Options:**

A. 240

B. 400

C. 0.0025

D. 200

Answer: B

#### Solution:

#### Solution:

 $\beta = \frac{\Delta I_{C}}{\Delta I_{B}}$   $= \frac{(6-4) \times 10^{-3}}{(25-20) \times 10^{-6}}$   $= \frac{2}{5} \times 10^{3}$  = 400

\_\_\_\_\_

## **Question59**

Identify the solar cell characteristics from the following options : [28-Jul-2022-Shift-1]

**Options:** 

A.

![](_page_44_Figure_15.jpeg)

B.

![](_page_44_Figure_17.jpeg)

![](_page_45_Figure_0.jpeg)

![](_page_45_Figure_1.jpeg)

D.

![](_page_45_Figure_3.jpeg)

![](_page_45_Figure_4.jpeg)

Solution:

![](_page_45_Figure_6.jpeg)

-----

## **Question60**

An n.p.n transistor with current gain  $\beta = 100$  in common emitter configuration is shown in figure. The output voltage of the amplifier will be

![](_page_45_Figure_10.jpeg)

[28-Jul-2022-Shift-2]

**Options:** 

A. 0.1V

B. 1.0V

C. 10V

D. 100V

Answer: B

#### Solution:

Solution:  $\frac{V_{out}}{V_{in}} = \beta \frac{R_{out}}{R_{in}}$   $v_{out} = \frac{100 \times 10 \times 10^{3}}{10^{3}} \times 10^{-3}$  = 1V

-----

## **Question61**

If the potential barrier across a p-n junction is 0.6V. Then the electric field intensity, in the depletion region having the width of  $6 \times 10^{-6}$ m, will be \_\_\_\_\_ × 10<sup>5</sup>N / C. [29-Jul-2022-Shift-1]

#### Answer: 1

Solution:

![](_page_46_Figure_10.jpeg)

\_\_\_\_\_

## **Question62**

A 8V Zener diode along with a series resistance R is connected across a 20V supply (as shown in the figure). If the maximum Zener current is 25 mA, then the minimum value of R will be \_\_\_\_\_  $\Omega$ 

![](_page_47_Figure_0.jpeg)

Answer: 480

#### Solution:

Solution:

R will be minimum when  $R_{L}^{}$  is infinitely large, so

 $R_{\text{Zener}} = \frac{8}{25 \times 10^{-3}} = 320\Omega$ So  $\frac{R}{R_{\text{Zener}}} = \frac{12}{8}$  $R = \frac{12}{8} \times 320 = 480\Omega$ 

\_\_\_\_\_

## **Question63**

If an emitter current is changed by 4mA, the collector current changes by 3.5mA. The value of  $\beta$  will be : [24feb2021shift1]

#### **Options**:

A. 7

B. 0.5

C. 0.875

D. 3.5

**Answer:** A

#### Solution:

**Solution:** Given,  $\Delta I_e = 4mA$   $\Delta I_c = 3.5mA$ For transistors,  $I_e = I_C + I_B$   $\therefore \Delta I_e = \Delta I_C + \Delta I_B$   $\Rightarrow 4mA = 3.5mA + \Delta I_B \Rightarrow \Delta I_B = 0.5mA$ Current gain for common emitter transistor,  $\beta = \frac{\Delta I_C}{\Delta I_B} \Rightarrow \beta = \frac{3.5}{0.5}$ 

 $\Rightarrow \beta = 7$ 

## **Question64**

In connection with the circuit drawn below, the value of current flowing through  $2k\Omega$  resistor is\_\_\_\_\_  $\times 10^{-4}$ A.

![](_page_48_Figure_2.jpeg)

![](_page_48_Figure_3.jpeg)

#### Answer: 25

#### Solution:

Solution: Current through  $2k\Omega$  resistance is I =  $\frac{5}{2 \times 10^3} = 2.5 \times 10^{-3}$ A I =  $25 \times 10^{-4}$ A

\_\_\_\_\_

## **Question65**

The Zener diode has a V  $_2$  = 30V. The current passing through the diode for the following circuit is ...... mA.

![](_page_48_Figure_10.jpeg)

[26 Feb 2021 Shift 2]

#### Answer: 9

#### Solution:

Given, Zener diode voltage,  $V_z = 30V$ Supply voltage, V = 90VAccording to figure,

![](_page_49_Figure_0.jpeg)

\_\_\_\_\_

## **Question66**

LED is constructed from GaAsP semiconducting material. The energy gap of this LED is 1.9eV. Calculate the wavelength of light emitted and its colour.

[h =  $6.63 \times 10^{-34}$ J s and c =  $3 \times 10^{8}$ ms<sup>-1</sup>] [26 Feb 2021 Shift 1]

#### **Options:**

A. 1046nm and red colour

B. 654nm and orange colour

C. 1046nm and blue colour

D. 654nm and red colour

Answer: D

#### Solution:

#### Solution:

Given, energy gap of LED, E = 1.9eVSpeed of light in free space,  $C = 3 \times 10^8 \text{ms}^{-1}$ Planck's constant,  $h = 6.63 \times 10^{-34} \text{J} - \text{s}$ As we know that,  $E = \frac{hc}{\lambda}$   $\Rightarrow \lambda = \frac{hc}{E}$   $\Rightarrow \lambda = \frac{6.63 \times 10^{-34} \times 3 \times 10^8}{19 \times 1.6 \times 10^{-19}}$   $= 654 \times 10^{-9} \text{m}$  = 654 nmAs, wavelength of red light is 600nm.  $\therefore$  Required wavelength will be of red colour.

## **Question67**

The circuit contains two diodes each with a forward resistance of  $50\Omega$  and with infinite reverse resistance. If the battery voltage is 6V, the current through the  $120\Omega$  resistance is ...... mA.

![](_page_50_Figure_2.jpeg)

[26 Feb 2021 Shift 1]

#### Answer: 20

#### Solution:

\_\_\_\_\_

## **Question68**

#### For extrinsic semiconductors when doping level is increased, [25 Feb 2021 Shift 2]

#### **Options:**

A. Fermi level of p-type semiconductor will go upward and Fermi level of n-type semiconductors will go downward

B. Fermi level of p-type semiconductors will go downward and Fermi level of n-type

semiconductor will go upward

C. Fermi level of p and n-type semiconductors will not be affected

D. Fermi level of both p-type and n-type semiconductors will go upward for T > T  $_FK$  and downward for T < T  $_FK$ , where T  $_F$  is Fermi temperature

#### Answer: B

#### Solution:

In case of  $\operatorname{n-type}$  semiconductor, the energy level diagram will be

![](_page_51_Figure_6.jpeg)

In case of n-type semiconductor n > p, so the fermi level will go upward. Similarly, in case of p-type semiconductor p > n, so the fermi level will go downward.

## **Question69**

A 5V battery is connected across the points X and Y. Assume  $D_1$  and  $D_2$  to be normal silicon diodes. Find the current supplied by the battery, if the positive terminal of the battery is connected to point X.

![](_page_51_Figure_10.jpeg)

#### [25 Feb 2021 Shift 1]

#### **Options:**

A. ∼0.5A

B. ∼1.5A

C. ~0.86A

D.  $\sim 0.43A$ 

#### Answer: B

![](_page_52_Figure_0.jpeg)

Let I current is coming from battery.  $\therefore D_1$  will act as closed circuit as forward biased and  $D_2$  will act as open circuit as reverse biased. Now, by using Kirchhoff's voltage law,  $5 - V_{D_1} - 10I = 0$   $\Rightarrow 5 - 0.7 - 10I = 0$  ( $\because V_{D_1} = 0.7V$ )  $\Rightarrow 4.3 = 101$  $\Rightarrow I = 0.43A$ 

\_\_\_\_\_

## **Question70**

#### Zener breakdown occurs in a p – n junction having p and n both [24 Feb 2021 Shift 2]

#### **Options:**

A. lightly doped and have wide depletion layer

B. heavily doped and have narrow depletion layer

C. lightly doped and have narrow depletion layer

D. heavily doped and have wide depletion layer

Answer: D

#### Solution:

#### Solution:

As we know that, Zener breakdown takes place, when we supply reverse bias voltage to Zener diode. Due to heavily dopping, the electrons in the valence band of p-type region can jump easily to the conduction band of n-type region, hence due to high electric field, zener breakdown occur. Thus, there is very high sudden increase in Zener current (I<sub>Z</sub>) that is caused by reverse breakdown voltage (V<sub>Z</sub>).

![](_page_52_Figure_13.jpeg)

Hence, Zener breakdown is easily observed in Zener diode which is heavily doped and having narrow depletion region.

\_\_\_\_\_

## **Question71**

Draw the output signal Y in the given combination of gates

![](_page_53_Figure_0.jpeg)

[26 Feb 2021 Shift 2]

#### **Options:**

A.

![](_page_53_Figure_4.jpeg)

B.

![](_page_53_Figure_6.jpeg)

![](_page_53_Figure_7.jpeg)

![](_page_53_Figure_8.jpeg)

D.

![](_page_53_Figure_10.jpeg)

#### Answer: D

#### Solution:

According to the given figure signals are

![](_page_53_Figure_14.jpeg)

The output of given circuit diagram is

![](_page_53_Figure_16.jpeg)

By using concept of de-Morgan's law,  $Y = \overline{A + B} = A \cdot \overline{B}$ 

Truth table of given signals is

Time interval	A	B	B	AB
(0 – 1)s	1	0	1	1
(1 – 2)s	1	1	0	0
(2 – 3)s	0	0	1	0
(3 – 4)s	1	1	0	0
(4 - 5)s	1	0	1	1

Hence, output signal is,

![](_page_54_Figure_3.jpeg)

\_\_\_\_\_

## **Question72**

#### The truth table for the following logic circuit is

![](_page_54_Figure_7.jpeg)

[25 Feb 2021 Shift 2]

#### **Options:**

A.

А	В	γ
0	0	0
0	1	1
1	0	1
1	1	0

#### В.

A	В	γ
0	0	1
0	1	0
1	0	0
1	1	1

1		
C	,	•

А	В	γ
0	0	1
0	1	0
1	0	1
1	1	0

#### D.

А	В	γ
0	0	0
0	1	1
1	0	0
1	1	1

#### Answer: B

#### Solution:

#### Solution:

Here A and B be the input and Y be the output.

![](_page_55_Figure_8.jpeg)

According to the truth table

A	B	Ā	B	AB	AB	$Y = AB + \overline{AB}$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

## **Question73**

![](_page_55_Figure_12.jpeg)

## The logic circuit shown above is equivalent to [24 Feb 2021 Shift 2]

#### **Options:**

![](_page_56_Figure_2.jpeg)

![](_page_56_Figure_3.jpeg)

Bo

#### Solution:

#### Solution:

The logic circuit is given as

![](_page_56_Figure_7.jpeg)

By using De-morgan's theorem,

 $C = \overline{A + B} = \overline{A} \cdot \overline{B} = \overline{A} \cdot B$ 

This relation can be shown by the circuit drawn below

![](_page_56_Figure_11.jpeg)

-----

## **Question74**

The correct relation between  $\alpha$  (ratio of collector current to emitter current) and  $\beta$  (ratio of collector current to base current) of a transistor is

[18 Mar 2021 Shift 2]

**Options:** 

A.  $\beta = \frac{\alpha}{1+\alpha}$ 

B. 
$$\alpha = \frac{\beta}{1-\alpha}$$
  
C.  $\beta = \frac{1}{1-\alpha}$   
D.  $\alpha = \frac{\beta}{1+\beta}$ 

Answer: D

#### Solution:

#### Solution:

Current gain in common base,  $\alpha = \frac{\Delta I_{C}}{\Delta I_{E}}$ Current gain in common emitter,  $\beta = \frac{\Delta I_{C}}{\Delta I_{B}}$ Here,  $\Delta I_{C}$  = change in collector current,  $\Delta I_{E}$  = change in emitter current and  $\Delta I_{B}$  = change in base current. We know that,  $\Delta I_{E} = \Delta I_{B} + \Delta I_{C}$ Divide by the  $\Delta I_{c}$  on both sides, we get  $\frac{\Delta I_{E}}{\Delta I_{C}} = \frac{\Delta I_{B}}{\Delta I_{C}} + \frac{\Delta I_{C}}{\Delta I_{C}}$   $\Rightarrow \frac{1}{\alpha} = \frac{1}{\beta} + 1 \Rightarrow \frac{1}{\alpha} = \frac{\beta + 1}{\beta}$   $\Rightarrow \alpha = \frac{\beta}{\beta + 1}$ 

\_\_\_\_\_

## **Question75**

Which one of the following will be the output of the given circuit?

![](_page_57_Figure_8.jpeg)

#### [17 Mar 2021 Shift 2]

#### **Options:**

A. NOR Gate

B. NAND Gate

C. AND Gate

D. XOR Gate

Answer: D

The given circuit, with the output of the respective gates is as given below.

$$A = \begin{pmatrix} (A \cdot B) \\ (A + B) \end{pmatrix} = \begin{pmatrix} \overline{A} \cdot \overline{B} \\ Y = (\overline{A} \cdot \overline{B}) \cdot (A + B) \end{pmatrix}$$

The Boolean expression of the output is

 $Y = (\overline{A \cdot B}) \cdot (A + B)$  $\Rightarrow Y = (\overline{A} + \overline{B}) \cdot (A + B)$ 

(using de-Morgan's theorem,  $\overline{x \cdot y} = \overline{x} + \overline{y}$ )

$$\Rightarrow Y = \overline{A} \cdot B + \overline{B} \cdot A$$

This represents the Boolean expression for XOR gate.

Alternate solution

This question can also be verified from the following truth table.

A	В	$P = \overline{A \cdot B}$	Q = A + B	$Y = P \cdot Q$
0	0	1	0	0
0	1	1	1	1
1	0	1	1	1
1	1	0	1	0

Hence, the output of this circuit represents the output of a XOR gate.

\_\_\_\_\_

## **Question76**

#### Answer: 100

#### Solution:

**Solution:** Given, The power gain of an n - p - n transistor,  $P = 10^6$ The input circuit of the resistance,  $r = 100\Omega$ The output load resistance of the circuit,  $R = 10k\Omega = 10000\Omega$ We know that, Power gain of common emitter amplifier,  $P = \frac{\beta^2 R}{r}$  Here,  $10^6 = \frac{\beta^2 \times 10000}{100}$  $\Rightarrow \beta = 100$ 

-----

## **Question77**

The value of power dissipated across the Zener diode (V  $_z = 15V$ ) connected in the circuit as shown in the figure is  $x \times 10^{-1}W$ .

![](_page_59_Figure_4.jpeg)

The value of x, to the nearest integer, is ...... [16 Mar 2021 Shift 1]

#### Answer: 5

#### **Solution:**

**Solution:** Consider the figure with current in the directions shown below.

$$R_{s}=35 \Omega$$

$$V_{z}=15 V$$

$$V_{z}=15 V$$

$$V_{z}=15 V$$

$$R_{L}=90 \Omega$$
Voltage across R<sub>s</sub>, V<sub>s</sub> = 22 - 15 = 7V  
Current through R<sub>s</sub>, I =  $\frac{V_{s}}{R_{s}}$ 

$$\Rightarrow I = \frac{7}{35} = \frac{1}{5}A$$
Current through 90 $\Omega$  resistance,  
I<sub>1</sub> =  $\frac{V_{z}}{R_{L}} = \frac{15}{90} = \frac{1}{6}A$ 

$$\therefore$$
 Current through Zener diode, I<sub>2</sub> =  $\frac{1}{5} - \frac{1}{6} = \frac{1}{30}A$ 

$$\therefore$$
 Power through Zener diode,  
P = V<sub>2</sub>I<sub>2</sub>

$$= 15 \times \frac{1}{30} = \frac{1}{2} = 0.5W = 5 \times 10^{-1}W$$
Comparing with the given value in question i.e., x × 10<sup>-1</sup>, the value of x

## **Question78**

In the logic circuit shown in the figure, if input A and B are 0 to 1 respectively, the output at Y would be x. The value of x is ........

= 5.

![](_page_60_Figure_0.jpeg)

#### [16 Mar 2021 Shift 1]

Answer: 0

#### Solution:

#### Solution:

Consider the figure given in the question and solve it using Boolean identities.

$$A \bullet A \bullet \overline{A + B} \bullet Y = (\overline{A + B}) (A + B)$$
  
$$B \bullet \overline{B} \bullet \overline{\overline{A + B}} \bullet \overline{\overline{A + B}} \bullet Y = (\overline{A + B}) (A + B)$$

Now, put the value of A and B in the output, we get

#### $Y = (\overline{0+1})(0+1) Y = \overline{1} \cdot 1 = 0$ Alternate method

We can directly put the given values in the logic circuit given in the question and can find its output. Let us consider the given logic circuit,

![](_page_60_Figure_10.jpeg)

The output is Y = 0.1 =... The value of x is 0.

\_\_\_\_\_

## **Question79**

#### The following logic gate is equivalent to

![](_page_60_Figure_15.jpeg)

#### [16 Mar 2021 Shift 2]

#### **Options:**

A. NOR Gate

B. OR Gate

C. AND Gate

D. NAND Gate

#### Answer: A

Let us consider the given logic circuit and solve it using Boolean algebra.

![](_page_61_Figure_1.jpeg)

## **Question80**

In a semiconductor, the number density of intrinsic charge carriers at  $27^{\circ}$ C is  $1.5 \times 10^{16}$  / m<sup>3</sup>. If the semiconductor is doped with impurity atom, the hole density increases to  $4.5 \times 10^{22}$  / m<sup>3</sup>. The electron density in the doped semiconductor is \_\_\_\_\_ × 10<sup>9</sup> / m<sup>3</sup> [25 Jul 2021 Shift 2]

Answer: 5

#### Solution:

$$n_{e}n_{h} = n_{i}^{2}$$

$$n_{e} = \frac{n_{i}^{2}}{n_{h}} = \frac{(1.5 \times 10^{16})^{2}}{4.5 \times 10^{22}}$$

$$= \frac{1.5 \times 1.5 \times 10^{32}}{4.5 \times 10^{22}}$$

$$5 \times 10^{9} / m^{3}$$

\_\_\_\_\_

## **Question81**

In a given circuit diagram, a 5V zener diode along with a series resistance is connected across a 50V power supply. The minimum value of the resistance required, if the maximum zener current is 90mA will be \_\_\_\_  $\Omega$ .

![](_page_61_Figure_10.jpeg)

[22 Jul 2021 Shift 2]

#### Answer: 500

#### Solution:

![](_page_62_Figure_2.jpeg)

## **Question82**

Consider a situation in which reverse biased current of a particular P-N junction increases when it is exposed to a light of wavelength  $\leq 621$  nm. During this process, enhancement in carrier concentration takes place due to generation of hole-electron pairs. The value of band gap is nearly.

[22 Jul 2021 Shift 2]

**Options:** 

A. 2 eV

- B. 4 eV
- C. 1 eV

D. 0.5 eV

Answer: A

#### Solution:

Solution: Band gap  $= \frac{hc}{\lambda_0}$  $\lambda_0$ ; threshold wavelength Band gap =  $\frac{1242ev - nm}{621nm} = 2eV$ 

## **Question83**

A zener diode having zener voltage 8V and power dissipation rating of 0.5W is connected across a potential divider arranged with maximum potential drop across zener diode is as shown in the diagram. The value of protective resistance  $R_n$  is ......  $\Omega$ .

![](_page_63_Figure_3.jpeg)

[20 Jul 2021 Shift 2]

#### Answer: 192

#### Solution:

**Solution:**  P = Vi 0.5 = 8i  $i = \frac{1}{16}A$   $E = 20 = 8 + iR_p$  $R_p = 12 \times 16 = 192\Omega$ 

\_\_\_\_\_

## **Question84**

For the forward biased diode characteristics shown in the figure, the dynamic resistance at I  $_{\rm D}$  = 3mAwill be \_\_\_\_\_Ω.

![](_page_63_Figure_11.jpeg)

#### Answer: 25

#### Solution:

![](_page_64_Figure_2.jpeg)

------

## **Question85**

## For the circuit shown below, calculate the value of I $_z$ :

![](_page_64_Figure_6.jpeg)

### [20 Jul 2021 Shift 1]

**Options:** 

A. 25 mA

B. 0.15 A

C. 0.1 A

D. 0.05 A

**Answer:** A

![](_page_64_Figure_15.jpeg)

## **Question86**

Find the truth table for the function Y of A and B represented in the following figure.

![](_page_65_Picture_2.jpeg)

**Options:** 

A.

А	в	Y
0	0	0
0	1	1
1	0	0
1	1	0

В.

Α	в	Y
0	0	1
0	1	0
1	0	1
1	1	1

C.

![](_page_65_Picture_9.jpeg)

D.

![](_page_65_Picture_11.jpeg)

Answer: B

![](_page_66_Figure_0.jpeg)

 $Y=A \, . \, B+\overline{B}$ 

A	в	Y
0	0	1
0	1	0
1	0	1
1	1	1

-----

## **Question87**

Choose the correct wave form that can represent the voltage across R of the following circuit, assuming the diode is ideal one.

![](_page_66_Figure_6.jpeg)

![](_page_66_Figure_7.jpeg)

#### **Options:**

A.

![](_page_66_Figure_10.jpeg)

B.

![](_page_66_Figure_12.jpeg)

C.

![](_page_67_Figure_0.jpeg)

D. None of the above

Answer: E

#### Solution:

#### Solution:

According to given circuit diagram,

![](_page_67_Figure_6.jpeg)

Let I current is flowing through the circuit.  $\therefore$  Kirchhoff's voltage loop equation will be  $10 \sin \omega t - IR - 3 = 0$   $IR = V = 10 \sin \omega t - 3$   $\therefore$  At time, t = 0, V = 0 - 3 = -3V...(i)  $t = \frac{T}{4}$ ,  $V = 10 \sin \left(\frac{2\pi}{T}\right) \cdot \frac{T}{4} - 3$  = 10 - 3 = 7V...(ii)  $t = \frac{T}{2}$  to T, diode is in reverse bias.  $\therefore V = 0$ ...(iii) We see that at t = 0, V = -3 and  $\frac{T}{2} \le t \le T$ , V = 0Therefore, no waveforms exist in option (a), (b) (c) and (d), which satisfies above condition. Hence, no option is correct.

## **Question88**

Statement I To get a steady DC output from the pulsating voltage received from a full wave rectifier we can connect a capacitor across the output parallel to the load  $R_L$ .

Statement II To get a steady DC output from the pulsating voltage received from a full wave rectifier we can connect an inductor in series with  $R_{L}$ .

In the light of the above statements, choose the most appropriate answer from the options given below. [31 Aug 2021 Shift 2]

#### **Options:**

A. Statement I is true but statement II is false.

- B. Statement I is false but statement II is true.
- C. Both statement I and statement II are false.

D. Both statement I and statement II are true.

#### Answer: D

#### Solution:

According to statement I and II, full wave rectifier with capacitor and inductor are as shown in figure.

![](_page_68_Figure_4.jpeg)

In figure (A), the capacitor is connected in parallel to load resistance ( $R_L$ ), as it can block DC current.

 $\div$  DC current can pass only through  $R_{_{\!\!\!\!L}}$  which gives DC output.

In figure (B), as the AC current is time varying current which can produce an opposition in current due to inductor that cancel the effect of AC in the load resistance ( $R_L$ ).

Hence, pure DC output is obtained across  $\boldsymbol{R}_{\!\!\!\!L}$ 

Hence, statement I and statement II are true.

## **Question89**

# A Zener diode of power rating 2W is to be used as a voltage regulator. If the Zener diode has a breakdown of 10V and it has to regulate voltage fluctuated between 6V and 14V, the value of $R_S$ for safe operation

![](_page_68_Figure_12.jpeg)

### [27 Aug 2021 Shift 2]

Answer: 20

#### Solution:

Given, power, P = 2W Zener breakdown voltage, V<sub>z</sub> = 10V Voltage range, (V<sub>1</sub> to V<sub>2</sub>) = 6V and 14V Let resistance be R. Since, P = VI<sub>z</sub> Zener current, I<sub>z</sub> =  $\frac{P}{V_z} = \frac{2}{10} = 0.2A$ For safe operation of Zener diode, I<sub>z</sub> = I<sub>s</sub> = 0.2A  $\therefore$  V<sub>2</sub> - V<sub>z</sub> = I<sub>s</sub>R<sub>s</sub>  $\Rightarrow 14 - 10 = I_s R_s$  $\Rightarrow R_s = \frac{4}{0.2}$  $= \frac{40}{2} = 20\Omega$ 

## **Question90**

For the given circuit, the power across Zener diode is ...... mW.  $_{1\,k\Omega}$ 

![](_page_69_Figure_3.jpeg)

[26 Aug 2021 Shift 2]

#### Answer: 120

#### Solution:

#### Solution:

The circuit diagram is shown below

$$\begin{array}{c}
 1 \\
 1 \\
 1 \\
 24 \\
 1 \\
 24 \\
 24 \\
 1 \\
 24 \\
 24 \\
 1 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24 \\
 24$$

The supply voltage,  $V_s = 24V$ 

Zener voltage,  $\rm V_z$  =  $10\rm V$ 

The value of supply voltage is greater than the Zener voltage.

Hence, the voltage across the load resistance of 5 k $\Omega$  will be equal to Zener voltage as they are connected in parallel combination.

Current  ${\rm I}_{\rm L}$  flowing through the load resistance can be calculated as

$$I_L = \frac{10}{5 \times 10^3} = 2 \times 10^{-3} A = 2 \text{ mA}$$

Since, the voltage drop across 5 k $\Omega$  is 10 V, then the voltage dropacross 1 k $\Omega$  resistance, V' = 24 - 10 = 14 V Current flowing through 1 k $\Omega$  resistance can be calculated as

 $I = \frac{V}{1 \times 10^3} = \frac{14}{1 \times 10^3} = 14 \times 10^{-3} \text{A} = 14 \text{ mA}$ From circuit diagram, I = I<sub>z</sub> + I<sub>L</sub> I<sub>z</sub> = I - I<sub>L</sub> = 14 - 2 = 12 mA Power across Zener diode is P = V<sub>z</sub> × I<sub>z</sub> = 10 × 12 = 120 mW Thus, the power across the Zener diode is 120 mW.

#### -----

## Question91

Statement I By doping silicon semiconductor with pentavalent material, the electrons density increases.

Statement II The n -type semiconductor has net negative charge.

#### In the light of the above statements, choose the most appropriate answer from the options given below. [26 Aug 2021 Shift 1]

#### **Options:**

- A. Statement I is true but statement II is false.
- B. Statement I is false but statement II is true.
- C. Both statement I and statement II are true.
- D. Both statement I and statement II are false.

#### Answer: A

#### Solution:

#### Solution:

We know that, the pentavalent impurities have excess free electrons. So, when a silicon semiconductor is doped with pentavalent impurities, the electron density increases. But on the other hand, the whole semiconductor is electrically neutral, therefore net charge on n-type semiconductor is zero. Hence, statement I true but statement II is false.

\_\_\_\_\_

## Question92

If  $V_A$  and  $V_B$  are the input voltages (either 5V or OV) and  $V_0$  is the output voltage then the two gates represented in the following circuit (A) and (B) are

![](_page_70_Figure_13.jpeg)

## [31 Aug 2021 Shift 2]

#### **Options:**

- A. AND and OR gate
- B. OR and NOT gate
- C. NAND and NOR gate
- D. AND and NOT gate

#### Answer: B

When  $V_A = 0$ ,  $V_B = 0$ Both  $D_1$  and  $D_2$  are OFF, so  $V_0 = 0$ , When  $V_A = 1$  i.e. 5V,  $V_B = 0$  i.e. 0V  $D_1$  is ON but  $D_2$  is OFF So,  $V_0 = 1$  i.e. 5V When  $V_A = 0$  i.e. 0V,  $V_B = 1$  i.e. 5V  $D_1$  is OFF and  $D_2$  is ON So,  $V_0 = 1$  i.e. 5V. Similarly, when  $V_A = V_B = 1$ Both  $D_1$  and  $D_2$  are ON So,  $V_0 = 1$  i.e. 5V.

We get the final truth table on the basis of inputs and their corresponding output.

А	В	Υ
0	0	0
0	1	1
1	0	1
1	1	1

 $\therefore$  The given circuit (A) is an OR gate.

In figure B, it is a transistor in common emitter configuration which gives high output at low input and low output at high input.

Hence, this circuit behaves as NOT Gate.

\_\_\_\_\_

## **Question93**

#### Four NOR gates are connected as shown in figure. The truth table for the given figure is

![](_page_71_Figure_9.jpeg)

#### [26 Aug 2021 Shift 2]

#### **Options:**

A.

А	в	Y
0	0	1
0	1	0
1	0	1
1	1	0

Β.
Α	в	Y
0	0	0
0	1	1
1	0	1
1	1	0

C.

Α	в	Y
0	0	0
0	1	1
1	0	0
1	1	1

D.

Α	в	Y
0	0	1
0	1	0
1	0	0
1	1	1

Answer: D

## Solution:

Given, logic circuit can be drawn as shown below.



А	В	A + B	$\overline{A+B}$	$A + \overline{A + B}$	$B + \overline{A + B}$	Y
0	0	0	1	1	1	1
0	1	1	0	0	1	0
1	0	1	0	1	0	0
1	1	1	0	1	1	1

\_\_\_\_\_

# **Question94**

A circuit is arranged as shown in figure. The output voltage  $V_0$  is equal to  $\ldots \ldots V.$ 



#### Answer: 5

### Solution:

#### Solution:

In the given circuit diagram shown in question, we can observe that diode  $D_1$  and diode  $D_2$  are in forward biasing. So, in forward biasing the diodes will offer zero resistance. Hence, given circuit diagram is redrawn as



The input voltage will become 0V and thus, the input current will be 0A. The output current will also be zero. Thus, the output voltage should be equal to 5 V.

\_\_\_\_\_

# **Question95**

Identify the logic operation carried out by the given circuit.



# [26 Aug 2021 Shift 1]

### **Options:**

A. OR

B. AND

C. NOR

D. NAND

Answer: C

# Solution:

### Solution:

The given circuit can be drawn as



The output,  $Z = \overline{A} \cdot \overline{B}$ 

 $=\overline{A+B}$ 

(Using de-Morgan theorem)

This is the expression of a NOR gate. So, the logic operation carried out by the given circuit is NOR.

**Alternate Method** The given question can be solved using truth table, which is as given below

Α	В	X	Y	Z
0	0	1	1	1
1	1	0	0	0
1	0	0	1	0
0	1	1	0	0

This truth table is similar to that of a NOR gate.

## \_\_\_\_\_

# **Question96**

For a transistor  $\alpha$  and  $\beta$  are given as  $\alpha = \frac{I_C}{I_E}$  and  $\beta = \frac{I_C}{I_B}$ . Then, the correct relation between  $\alpha$  and  $\beta$  will be [27 Aug 2021 Shift 2]

**Options:** 

A. 
$$\alpha = \frac{1-\beta}{\beta}$$
  
B.  $\beta = \frac{\alpha}{1-\alpha}$ 

C.  $\alpha\beta = 1$ D.  $\alpha = \frac{\beta}{1-\beta}$ 

#### Answer: B

### Solution:

Given,  $\alpha = \frac{I_C}{I_E}$  and  $\beta = \frac{I_C}{I_B}$ where,  $\alpha = \text{ current gain in common-base amplifier and } \beta = \text{ current gain in common-base amplifier.}$ Since,  $I_E = I_C + I_B$ where,  $I_E = \text{ emitter current,}$   $I_C = \text{ collector current.}$ and  $I_B = \text{ base current.}$   $\therefore \alpha = \frac{I_C}{I_E} = \frac{I_C}{I_C + I_B} = \frac{1}{1 + \frac{I_B}{I_C}} = \frac{1}{1 + \frac{1}{\beta}}$   $\Rightarrow 1 + \frac{1}{\beta} = \frac{1}{\alpha}$   $\Rightarrow \frac{1}{\beta} = \frac{1}{\alpha} - 1$   $\Rightarrow \frac{1}{\beta} = \frac{1 - \alpha}{\alpha}$  $\therefore \beta = \frac{\alpha}{1 - \alpha}$ 

# **Question97**

Both the diodes used in the circuit shown are assumed to be ideal and have negligible resistance when these are forward biased. Built in potential in each diode is 0.7 V. For the input voltages shown in the figure, the voltage (in Volts) at point A is \_\_\_\_\_.



[NA 9 Jan. 2020 I]

#### **Options:**

- A. 12
- B. 10
- C. 9

D. 11

#### Answer: A

Right hand diode is reversed biased and left hand diode is forward biased. Hence Voltage at 'A'  $V_{\rm A}$  = 12.7 – 0.7 = 12 volt

\_\_\_\_\_

# **Question98**

## The current i in the network is:



#### **Options:**

A. 0.2 A

B. 0.6 A

C. 0.3 A

D. 0 A

#### Answer: C

## Solution:

#### Solution:

Both the diodes are reverse biased, so, there is no flow of current through  $5\Omega$  and  $20\Omega$  resistances. Now, two resistors of  $10\Omega$  and two resistors of  $5\Omega$  are in series. Hence current I through the network = 0.3 A

# **Question99**

Two identical capacitors A and B, charged to the same potential 5V are connected in two different circuits as shown below at time t = 0. If the charge on capacitors A and B at time t = CR is  $Q_A$  and  $Q_B$  respectively, then (Here e is the base of natural logarithm)



[9 Jan. 2020 II]

#### **Options:**

A. 
$$Q_A = \frac{VC}{e}$$
,  $Q_B = \frac{CV}{2}$   
B.  $Q_A = VC$ ,  $Q_B = CV$   
C.  $Q_A = VC$ ,  $Q_B = \frac{VC}{e}$ 

D.  $Q_A = \frac{CV}{2}$ ,  $Q_B = \frac{VC}{e}$ 

#### Answer: C

#### Solution:

#### Solution:

In case I diode is reverse biased, so no current flows  ${\rm \dot{\cdot\cdot}Q}_{\rm A}={\rm CV}$ 

In case II, current will flow as diode is forward biased. So, it offers negligible resistance to the flow of current and thus be replaced by short circuit. Now, the charge of capacitor will leak through the resistance and decay exponentially with time. During discharging of capacitor

Potential difference across the capacitor at any instant

$$V' = V e^{-\frac{t}{CR}}$$
  
But t = CR  
V' = V e^{-1} =  $\frac{V}{e}$   
∴ Charge Q<sub>B</sub> = CV' =  $\frac{CV}{e}$ 

\_\_\_\_\_

# **Question100**

The circuit shown below is working as a 8 V dc regulated voltage source. When 12 V is used as input, the power dissipated (in mW) in each diode is; (considering both zener diodes are identical) \_\_\_\_.



## [NA 9 Jan. 2020 II]

#### **Options:**

A. 40 mW

B. 20 mW

C. 15 mW

 $D.\ 25\ mW$ 

#### Answer: A

## Solution:

Solution:

Current in the circuit, I =  $\frac{12 - 8}{400} = 10^{-2}$ A Power dissipited in each diode, P = V I  $\Rightarrow$ P = 4 × 10<sup>-2</sup> = 40mW

\_\_\_\_\_

# **Question101**

## In the figure, potential difference between A and B is:



## [7 Jan. 2020 II]

#### **Options:**

- A. 10 V
- B. 5 V
- C. 15 V
- D. zero

### Answer: A

## Solution:

#### Solution:

The given circuit has two  $10k\Omega$  resistances in parallel, so we can reduce this parallel combination to a single equivalent resistance of  $5k\Omega$ .



Diode is in forward bias. So it will behave like a conducting wire.  $V_A - V_B = \frac{30}{5+10} \times 5 = 10V$ 

#### ------

# **Question102**

Boolean relation at the output stage-Y for the following circuit is:



## [8 Jan. 2020 I]

### **Options:**

- A.  $\overline{A} + \overline{B}$
- B. A + B
- C. A . B
- D.  $\overline{A}$  .  $\overline{B}$
- Answer: D

## Solution:

Solution:



OR + NOT  $\rightarrow$  NOR Gate Hence Boolean relation at the output stage – Y for the circuit, Y =  $\overline{A + B} = \overline{A} \cdot \overline{B}$ 

-----

# **Question103**

## In the given circuit, value of Y is:



## [8 Jan. 2020 II]

**Options:** 

A. 0

- B. toggles between 0 and 1  $\,$
- C. will not execute
- D. 1

Answer: A

## Solution:

Solution:



-----

# **Question104**

## Which of the following gives a reversible operation? [7 Jan. 2020 I]

**Options:** 

A.



В.



C.



D.



#### Answer: D

## Solution:

**Solution:** A logic gate is reversible if we can recover input data from the output. Hence NOT gate.

\_\_\_\_\_

# **Question105**

# With increasing biasing voltage of a photodiode, the photocurrent magnitude : [Sep. 05, 2020 (I)]

#### **Options:**

A. remains constant

- B. increases initially and after attaining certain value, it decreases
- C. Increases linearly
- D. increases initially and saturates finally

#### Answer: D

### Solution:

#### Solution:

I-V characteristic of a photodiode is as follows :



On increasing the biasing voltage of a photodiode, the magnitude of photocurrent first increases and then attains a saturation.

\_\_\_\_\_

# **Question106**

Two Zener diodes (A and B) having breakdown voltages of 6V and 4V respectively, are connected as shown in the circuit below. The output voltage V $_0$  variation with input voltage linearly increasing with time, is given by:

 $(V_{input} = 0V \text{ at } t = 0)$ 



**Options:** 

A.



В.



C.







#### Answer: C

## Solution:

#### Solution:

Till input voltage reaches 4 V. No zener is in breakdown region so V<sub>0</sub> = V<sub>i</sub>. Then now when V<sub>i</sub> changes between 4V to 6V one zener with 4V will breakdown and P.D. across this zener will become constant and remaining potential will dorp across resistance in series with 4 V zener.

Now current in circuit increases abruptly and source must have an internal resistance due to which some potential will get drop across the source also so correct graph between V $_0$  and t will be



# **Question107**

Take the breakdown voltage of the zener diode used in the given circuit as 6V. For the input voltage shown in figure below, the time variation of the output voltage is :

(Graphs drawn are schematic and not to scale)





**Options:** 

A.



Β.



C.



D.



**Answer: C** 

## Solution:

Here two zener diodes are in reverse polarity so if one is in forward bias the other will be in reverse bias and above 6V the reverse bias will too be in conduction mode. Hence when V > 6V the output will be constant. And when V < 6V it will follow the inut voltage.

\_\_\_\_\_

# **Question108**

When a diode is forward biased, it has a voltage drop of 0.5V. The safe limit of current through the diode is 10mA If a battery of emf 1.5V is used in the circuit, the value of minimum resistance to be connected in series with the diode so that the current does not exceed the safe limit is :

[Sep. 03,2020 (I)]

**Options:** 

Α. 300Ω

Β. 50Ω

 $C.\ 100\Omega$ 

D. 200Ω

Answer: C

## Solution:



# **Question109**

If a semiconductor photodiode can detect a photon with a maximum wavelength of 400 nm, then its band gap energy is: Planck's constant,

## h = $6.63 \times 10^{-34}$ J . s Speed of light, c = $3 \times 10^8$ m / s [Sep. 03,2020 (II)]

#### **Options:**

- A. 1.1 eV
- B. 2.0 eV
- C. 1.5 eV
- D. 3.1 eV

#### Answer: D

### Solution:

#### Solution:

Given, Wavelength of photon,  $\lambda = 400$  nm A photodiode can detect a wavelength corresponding to the energy of band gap. If the signal is having wavelength greater than this value, photodiode cannot detect it.

: Band gap E  $_{g} = \frac{hc}{\lambda} = \frac{1237.5}{400} = 3.09 eV$ 

# **Question110**

The output characteristics of a transistor is shown in the figure. When V<sub>CE</sub> is 10V and I<sub>C</sub> = 4.0mA, then value of  $\beta_{ac}$  is \_\_\_\_\_.



[NA Sep. 06,2020 (II)]

#### Answer: 150

### **Solution**:

At V  $_{CE}$  = 10V and I  $_{C}$  = 4mA Change in base current,  $\Delta I_{B}$  = (30 - 20) = 10µA Change in collector current,  $\Delta I_{C}$  = (4.5 - 3) = 1.5mA

$$\beta = \left(\frac{\Delta I_{C}}{\Delta I_{B}}\right) = \frac{1.5mA}{10\mu A} = 150$$

# **Question111**

Identify the correct output signal Y in the given combination of gates (as shown) for the given inputs A and B.





**Options:** 

A.



Β.







D.



Answer: A

## Solution:

#### Solution:



# Question112

Identify the operation performed by the circuit given below:

------



[Sep. 04, 2020 (II)]

### **Options:**

A. NAND

B. OR

C. AND

D. NOT

### Answer: C

## Solution:

#### Solution:

When two inputs of NAND gate is shorted, it behaves like a NOT gate so boolen equation will be y = A + B + Cy = A - B - C

, II:D:0				
А	в	С		
0	0	0	0	
1	0	0	0	
0	1	0	0	
0	0	1	0	
1	1	0	0	
1	0	1	0	
0	1	1	0	
1	1	1	1	

Thus, whole arrangement behaves like a AND gate.

.....

# **Question113**

In the following digital circuit, what will be the output at 'Z', when the input (A, B) are (1, 0), (0, 0), (1, 1), (0, 1):



[Sep. 02, 2020 (II)]

#### **Options:**

A. 0, 0, 1, 0

B. 1, 0, 1, 1

C. 1, 1, 0, 1

D. 0, 1, 0, 0

#### Answer: A

### Solution:



A	B	$\overline{A \cdot B}$	$\overline{A+B}$	$W = \overline{A \cdot B} \cdot \overline{A + B}$	$Q = W + \overline{A \cdot B}$	$\overline{Q} = x$
1	0	1	0	0	1	0
0	1	1	0	0	1	0
1	1	0	0	0	0	1
0	0	1	1	1	0	0

# **Question114**



In the figure, given that V<sub>BB</sub> supply can vary from 0 to 5.0 V, V<sub>CC</sub> = 5V,  $\beta_{dc}$  = 200,  $R_B$  = 100k $\Omega$ ,  $R_C$  = 1K $\Omega$  and V<sub>BE</sub> = 1.0V. The minimum base current and the input voltage at which the transistor will go to saturation, will be, respectively: [12 Jan. 2019 II]

**Options:** 

A. 25  $\mu A$  and 3.5 V

B. 20  $\mu A$  and 3.5 V

C. 25  $\mu A$  and 2.8 V

D. 20  $\mu A$  and 2.8 V

### Answer: A

```
\begin{split} & \text{At saturation, V}_{CE} = 0 \\ & \text{V}_{CE} = \text{V}_{CC} - I_{C}R_{C} \\ & \Rightarrow I_{C} = \frac{\text{V}_{CC}}{R_{c}} = 5 \times 10^{-3}\text{A} \\ & \text{Current gain,} \\ & \beta_{d\,c} = \frac{I_{C}}{I_{B}} \end{split}
```

```
I_{B} = \frac{5 \times 10^{-3}}{200} = 25 \mu A
At input side
V_{BB} = I_{B}R_{B} + V_{BE}
= (25mA)(100k\Omega) + 1V
V_{BB} = 3.5V
```

# **Question115**

In the given circuit the current through Zener Diode is close to :



# [11 Jan. 2019 I]

### **Options:**

A. 0.0 mA

B. 6.7 mA

C. 4.0 mA

D. 6.0 mA

Answer: A

## Solution:

### Solution:

Since voltage across zener diode does not reach to breakdown voltage therefore its resistance will be infinite & current through it is 0.

\_\_\_\_\_

# **Question116**

The circuit shown below contains two ideal diodes, each with a forward resistance of 50  $\Omega$ . If the battery voltage is 6V, the current through the 100  $\Omega$  resistance (in Amperes) is :



# [11 Jan. 2019 II]

## **Options:**

A. 0.036

B. 0.020

C. 0.027

D. 0.030

Answer: B

### Solution:

#### Solution:

 $As\,D_2$  is reversed biased, so no current through  $75\Omega$  resistor.

now R<sub>eq</sub> = 150 + 50 + 100 = 300Ω So, required current I =  $\frac{BatteryVoltage}{300}$ I =  $\frac{6}{300}$  = 0.02

-----

# **Question117**

For the circuit shown below, the current through the Zener diode is:  ${}_{5\,k\Omega}$ 



## [10 Jan. 2019 II]

#### **Options:**

A. 9 mA

B. 5 mA

C. Zero

D. 14 mA

**Answer:** A

## Solution:

#### Solution:

The voltage across zener diode is constant



# **Question118**

Mobility of electrons in a semiconductor is defined as the ratio of their drift velocity to the applied electric field. If, for an n-type semiconductor, the density of electrons is  $10^{19}$ m<sup>-3</sup> and their mobility is  $1.6m^2/(V.s)$  then the resistivity of the semiconductor (since it is an n-type semiconductor contribution of holes is ignored) is close to: [9 Jan. 2019 I]

### **Options:**

A. 2 Ωm

 $B. \ 4 \ \Omega m$ 

 $C. \ 0.4 \ \Omega m$ 

 $D. \ 0.2 \ \Omega m$ 

Answer: C

## Solution:

Solution: As we know, current density,  $j = \sigma E = nev_d$   $\sigma = ne\frac{v_d}{E} = ne\mu$   $\frac{1}{\sigma} = \rho = \frac{1}{n_e e \mu_e} = \text{Resistivity}$   $= \frac{1}{10^{19} \times 1.6 \times 10^{19} - 19 \times 1.6}$ or P = 0.4 $\Omega$ m

------

# **Question119**

Ge and Si diodes start conducting at 0.3V and 0.7V respectively. In the following figure if Ge diode connection are reversed, the value of V  $_0$ 

changes by : (assume that the Ge diode has large breakdown voltage)



[9 Jan. 2019 II]

### **Options:**

A. 0.8 V

B. 0.6 V

C. 0.2 V

D. 0.4 V

Answer: D

## Solution:

#### Solution:

Initially Ge and Si are both forward biased so current will effectivily pass through Ge diode therefore V<sub>0</sub> = 12 - 0.3 = 11.7V And if "Ge" is revesed then current will flow through "Si" diode  $\therefore$ V<sub>0</sub> = 12 - 0.7 = 11.3V Clearly, V<sub>0</sub> changes by 11.7 - 11.3 = 0.4V

\_\_\_\_\_

# **Question120**

## The output of the given logic circuit is:



## [12 Jan. 2019 I]

### **Options:**

A.  $A\overline{B} + \overline{A}B$ 

B. AB +  $\overline{AB}$ 

C.  $A\overline{B}$ 

D.  $\overline{A}B$ 

Answer: C

## Solution:



# **Question121**

To get output '1' at R, for the given logic gate circuit the input values must be:



## [10 Jan. 2019 I]

### **Options:**

A. X = 0, Y = 1

B. X = 1, Y = 1

C. X = 1, Y = 0

D. X = 0, Y = 0

**Answer: C** 

## Solution:

#### Solution:

From the given logic circuit, p = x + y  $Q = y \cdot x = y + x$ Output, R = P + QTo make output 1 P + Q must be '0' So, x = 1, y = 0

\_\_\_\_\_

# **Question122**

Figure shows a DC voltage regulator circuit, with a Zener diode of breakdown voltage = 6V. If the unregulated input voltage varies between 10 V to 16 V, then what is the maximum Zener current ?



## [12 Apr. 2019 II]

#### **Options:**

- A. 2.5 mA
- B. 1.5 mA
- C. 7.5 mA

D. 3.5 mA

#### Answer: D

### Solution:

Solution: Current in load resistance,  $i_1 = \frac{6}{4 \times 10^3} = 1.5 \times 10^{-3} \text{A} = 1.5 \text{mA}$ For V = 16 volt,  $i_s = \frac{(16-6)}{2 \times 10^3} = 5 \text{mA}$ ∴ $i_2 = i_s - i_1 = 5 - 1.5 = 3.5 \text{mA}$ 

# **Question123**

The figure represents a voltage regulator circuit using a Zener diode. The breakdown voltage of the Zener diode is 6V and the load resistance is  $R_t = 4k$ . The series resistance of the circuit is  $R_i = 1k$ . If the battery voltage V<sub>B</sub> varies from 8V to 16V, what are the minimum and maximum values of the current through Zener diode?



[10 Apr. 2019 II]

### **Options:**

- A. 0.5 mA; 6 mA
- B. 1 mA; 8.5 mA
- C. 0.5 mA; 8.5 mA

D. 1.5 mA; 8.5 mA

### Answer: C



\_\_\_\_\_

# **Question124**

The reverse breakdown voltage of a Zener diode is 5.6 V in the given circuit



The current I <sub>z</sub> through the Zener is : [8 April 2019 I]

#### **Options:**

A. 10 mA

B. 17 mA

C. 15 mA

D. 7 mA

Answer: A

## Solution:



so, current through zener diode  $= I_2 = 17 - 7 = 10 \text{mA}$ 

# **Question125**

The transfer characteristic curve of a transistor, having input and output resistance 100  $\Omega$  and 100 k  $\Omega$  respectively, is shown in the figure. The Voltage and Power gain, are respectively :





### **Options:**

A.  $2.5 \times 10^4$ ,  $2.5 \times 10^6$ 

B.  $5 \times 10^4$ ,  $5 \times 10^6$ 

C.  $5 \times 10^4$ ,  $5 \times 10^5$ 

D.  $5 \times 10^4$ ,  $2.5 \times 10^6$ 

E. None of above

### Answer: E

## Solution:

$$\begin{split} & \text{Solution:} \\ & \beta = \frac{\Delta i_c}{\Delta i_b} = \frac{200 - 100}{10 - 5} = 20 \\ & \text{Voltage gain} = \beta \frac{R_2}{R_1} = \frac{20 \times 100 \times 10^3}{100} = 20 \times 10^3 \\ & \text{Power gain} = \beta^2 \frac{R_2}{R_1} = 20^2 \left(\frac{100 \times 10^3}{100}\right) = 4 \times 10^5 \end{split}$$

# **Question126**

An npn transistor operates as a common emitter amplifier, with a power gain of 60d B. The input circuit resistance is  $100\Omega$  and the output load resistance is  $10k\Omega$ . The common emitter current gain  $\beta$  is : [10 Apr. 2019 I]

### **Options:**

A. 10<sup>2</sup>

B. 60

C.  $6 \times 10^{2}$ 

D. 10<sup>4</sup>

Answer: A

## Solution:

Power gain =  $60 = 10 \log \left(\frac{P_0}{p_i}\right)$   $\Rightarrow 6 = \log \left(\frac{P_0}{p_i}\right)$   $\Rightarrow \frac{P_0}{p_i} = 10^6$   $= \beta^2 \left(\frac{R_{out}}{R_{in}}\right)$   $\Rightarrow 10^6 = \beta^2 \left(\frac{10000}{100}\right)$  [ as  $R_{out} = 10,000\Omega R_{in} = 100\Omega$ ]  $\Rightarrow \beta = 100$ 

# **Question127**

An NPN transistor is used in common emitterconfiguration as an amplifier with 1 k &! load resistance. Signal voltage of 10mV is applied across the base-emitter. This produces a 3mA change in the collector current and  $15\frac{1}{4}$ A change in the base current of the amplifier. The input resistance and voltage gain are: [9 Apr. 2019 I]

### **Options:**

A. 0.33kΩ1.5

 $B.\ 0.67k\Omega 300$ 

C.  $0.67k\Omega 200$ 

D. 0.33kΩ300

Answer: B

## Solution:

Solution:  $\beta = \frac{\Delta l c}{\Delta l b} = \frac{3 \times 10^{-3}}{15 \times 10^{-6}} = 200$  We have  $\frac{V_0}{V_i} = \beta \frac{R^2}{R_1}$ or  $\frac{V_0}{V_i} = 200 \left(\frac{1000}{R_1}\right)$ If  $R_1 = 0.67 k\Omega \Rightarrow \frac{V_0}{V_i} = 300$ 

# **Question128**

A common emitter amplifier circuit, built using an npn transistor, is shown in the figure. Its dc current gain is 250,  $R_C = 1 \text{ k} \& !$  and  $V_{CC} = 10V$ . What is the minimum base current for  $V_{CE}$  to reach saturation?



## [8 Apr.2019 II]

### **Options:**

Α. 40μΑ

Β. 100μΑ

С. 7µА

D. 10µA

Answer: A

## Solution:

Given, 
$$\beta = 250$$
  
Voltage gain,  $\frac{V_{CC}}{V_B} = \beta \frac{R_C}{R_B}$   
 $\frac{10}{V_B} = 250 \times \frac{10^3}{R_B}$   
 $\therefore \frac{V_B}{R_B} = \frac{1}{25 \times 10^3} = 40 \mu A$ 

# **Question129**

The truth table for the circuit given in the fig. is :



### **Options:**



### Answer: C

## Solution:

A	B	(A + B)	(A+B).A	$\overline{(A+B)}.A$
0	0	0	0	1
0	1	1	0	1
1	0	1	1	0
1	1	1	1	0

# **Question130**

## The logic gate equivalent to the given logic circuit is:



[9 Apr. 2019 II]

### **Options:**

A. NAND

- B. OR
- C. NOR

D. AND

Answer: B

### Solution:

Solution:

Truth table  $\rightarrow$ The output is of OR-gate

A	B	Ā	B	$\overline{A}$ . $\overline{B}$
0	0	1	1	0
0	1	1	0	1
1	0	0	1	1
1	1	0	0	1

\_\_\_\_\_

# **Question131**

The reading of the ammeter for a silicon diode in the given circuit is :



## [2018]

#### **Options:**

A. 0

- B. 15 mA
- C. 11.5 mA

D. 13.5 mA

**Answer: C** 

## Solution:

**Solution:** Clearly from fig. given in question, Silicon diode is in forward bias.  $\therefore$  Potential barrier across diode  $\Delta V = 0.7 \text{ volts}$ Current, I =  $\frac{V - \Delta V}{R} = \frac{3 - 0.7}{200} = \frac{2.3}{200} = 11.5 \text{mA}$ 

-----

# **Question132**

## In the given circuit, the current through zener diode is:



### [Online April 16, 2018]

#### **Options:**

A. 2.5mA

B. 3.3mA

C. 5.5mA

D. 6.7mA

Answer: B

Solution:



The voltage drop across  $R_2$  is V  $_{\rm R_2}$  = V  $_{\rm Z}$  = 10V The current through  $R_2$  is

$$I_{R_2} = \frac{V_{R_2}}{R_2} = \frac{10V}{1500\Omega} = 0.667 \times 10^{-2} A$$
  
= 6.67 × 10<sup>-3</sup>A = 6.67mA  
The voltage drop across R<sub>1</sub> is  
 $V_{R_1} = 15V - V_{R_2} = 15V - 10V = 5V$ 

The current through R<sub>1</sub> is I  $_{R_1} = \frac{V_{R_1}}{R_1} = \frac{5V}{500\Omega} = 10^{-2}A = 10 \times 10^{-3}A = 10mA$ The current through the zener diode is I  $_Z = I_{R_1} - I_{R_2} = (10 - 6.67)mA = 3.3mA$ 

# **Question133**

In a common emitter configuration with suitable bias, it is given than  $R_L$  is the load resistance and  $R_{BE}$  is small signal dynamic resistance (input side). Then, voltage gain, current gain and power gain are given, respectively, by:

( $\beta$  is current gain, I <sub>B</sub>, I <sub>C</sub>, I <sub>E</sub> are respectively base, collector and emitter currents:)

[Online April 15,2018]

**Options:** 

A.  $\beta \frac{R_L}{R_{BE}}$ ,  $\frac{\Delta I_E}{\Delta I_B}$ ,  $\beta^2 \frac{R_L}{R_{BE}}$ B.  $\beta^2 \frac{R_L}{R_{BE}}$ ,  $\frac{\Delta I_C}{\Delta I_B}$ ,  $\beta \frac{R_L}{R_{BE}}$ C.  $\beta^2 \frac{R_L}{R_{BE}}$ ,  $\frac{\Delta I_C}{\Delta I_E}$ ,  $\beta^2 \frac{R_L}{R_{BE}}$ 

D. 
$$\beta \frac{R_L}{R_{BE}}$$
,  $\frac{\Delta I_C}{\Delta I_B}$ ,  $\beta^2 \frac{R_L}{R_{BE}}$ 

### Answer: D

## Solution:

$$\begin{split} \text{Solution:} \\ \text{Curent gain } \beta &= \frac{\Delta I_{C}}{I_{B}} \\ \text{Voltage gain } A_{v} &= \text{ Current gain } \times \text{Resistance gain } = \beta \frac{R_{L}}{R_{BE}} \\ \text{Power gain } A_{p} &= (\text{ Current gain })^{2} \times \text{Resistance gain } \\ &= \beta^{2} \frac{R_{L}}{R_{BE}} \end{split}$$

# **Question134**

Truth table for the given circuit will be



## [Online April 15, 2018]

### **Options:**

A.

x	у	z
0	0	1
0	1	1
1	0	1
1	1	0

В.

x	у	z
0	0	0
0	1	0
1	0	0
1	1	1

C.

	x	у	Z
	0	0	1
	0	1	1
8	1	0	1
	1	1	1

D.

x	у	z
0	0	0
0	1	1
1	0	1
1	1	1

### Answer: C

# Solution:

**Solution:** Truth table of the circuit is as follows

x	y	x	a=x.y	b = x.y	$z = \overline{a \cdot b}$
0	0	1	0	0	1
0	1	1	0	1	1
1	0	0	0	0	1
1	1	0	1	0	1

------

# Question135

What is the conductivity of a semiconductor sample having electron concentration of  $5 \times 10^{18} \text{m}^{-3}$ , hole concentration of  $5 \times 10^{19} \text{m}^{-3}$ , electron mobility of  $2.0 \text{m}^2 \text{V}^{-1} \text{s}^{-1}$  and hole mobility of  $0.01 \text{m}^2 \text{V}^{-1} \text{s}^{-1}$ ? (Take charge of electron as  $1.6 \times 10^{-19} \text{C}$ ) [Online April 8, 2017]

**Options:** 

- A.  $1.68(\Omega m)^{-1}$
- B.  $1.83(\Omega m)^{-1}$
- C.  $0.59(\Omega m)^{-1}$

D.  $1.20(\Omega - m)^{-1}$ 

Answer: A

## Solution:

```
 \begin{split} \text{Solution:} \\ \text{The conductivity of semiconductor} \\ \sigma &= e(\eta_e \mu_e + \eta_h \mu_h) \\ &= 1.6 \times 10^{-19} (5 \times 10^{18} \times 2 + 5 \times 10^{19} \times 0.01) \\ &= 1.6 \times 1.05 = 1.68 \end{split}
```

# Question136

The V-I characteristic of a diode is shown in the figure. The ratio of forward to reverse bias resistance is :



## [Online April 8, 2017]

### **Options:**

- A. 10
- B. 10<sup>-6</sup>
- $C. 10^{6}$
- D. 100

### Answer: B

## Solution:

### Solution:

Forward bias resistance  $= \frac{\Delta V}{\Delta I} = \frac{0.1}{10 \times 10^{-3}} = 10\Omega$ Reverse bias resistance  $= \frac{10}{10^{-6}} = 10^7\Omega$ Ratio of resistances  $= \frac{\text{Forward bias resistance}}{\text{Reverse bias resistance}} = 10^{-6}$ 

-----

# Question137

The current gain of a common emitter amplifier is 69. If theemitter current is 7.0 mA, collector current is : [Online April 9, 2017]

### **Options:**

- A. 9.6 mA
- B. 6.9 mA
- C. 0.69 mA
- D. 69 mA
- Answer: B

Given, current gain of CE amplifier  $\beta = 69$ ,  $I_E = 7mA$ or  $\frac{I_C}{I_B} = 69$ We know that,  $\alpha = \beta 1 + \beta = \frac{69}{70} = \frac{I_C}{I_E}$  $I_C = I_E \times \frac{69}{70} = \frac{69}{70} \times 7$ Collector current,  $I_C = 6.9mA$ 

\_\_\_\_\_

# Question138

In a common emitter amplifier circuit using an n-p-n transistor, the phase difference between the input and the output voltages will be : [Online April 2, 2017]

**Options:** 

A. 135°

B. 180°

C. 45°

D. 90°

Answer: B

### Solution:

#### Solution:

In common emitter configuration for n-p-n transistor input and output signals are 180° out of phase i.e., phase difference between output and input voltage is 180°.

\_\_\_\_\_

# **Question139**

## Identify the semiconductor devices whose characteristics are given below, in the order (i), (ii), (iii), (iv) :




## [2016]

#### **Options:**

A. Solar cell, Light dependent resistance, Zener diode, simple diode

B. Zener diode, Solar cell, simple diode, Light dependentresistance

C. Simple diode, Zener diode, Solar cell, Light dependentresistance

D. Zener diode, Simple diode, Light dependentresistance, Solar cell

#### Answer: C

## Solution:

**Solution:** Graph (p) is for a simple diode. Graph (q) is showing the V Break down used for zener diode. Graph (r) is for solar cell which shows cut-off voltage and open circuit current. Graph (s) shows the variation of resistance h and hence current with intensity of light.

\_\_\_\_\_

# **Question140**

# The temperature dependence of resistances of Cu and undoped Si in the temperature range 300-400 K, is best described by : [2016]

## **Options:**

A. Linear increase for Cu, exponential decrease of Si.

B. Linear decrease for Cu, linear decrease for Si.

C. Linear increase for Cu, linear increase for Si.

D. Linear increase for Cu, exponential increase for Si.

## Answer: A

## Solution:



# **Question141**

An experiment is performed to determine the 1-V characteristics of a Zener diode, which has a protective resistance of  $R = 100 \Omega$ , and a maximum power of dissipation rating of 1W. The minimum voltage range of the DC source in the circuit is : [Online April 9, 2016]

#### **Options:**

A. 0 - 5V

B. 0 - 24 V

C. 0 - 12 V

D. 0 - 8V

Answer: C

## Solution:

Solution: The minimum voltage range of DC source is given by  $V^2 = PR \because P = 1$  watt ,  $R = 100\Omega$  $= 1 \times 100$  $\therefore V = 10$  volt

# **Question142**

For a common emitter configuration, if  $\alpha$  and  $\beta$  have their usual meanings, the incorrect relationship between  $\alpha$  and  $\beta$  is: [2016]

**Options:** 

A. 
$$a = \frac{b}{1+b}$$
  
B. 
$$a = \frac{b^2}{1+b^2}$$
  
C. 
$$\frac{1}{a} = \frac{1}{b} + 1$$

D. None of these

#### Answer: 0

## Solution:

We know that 
$$\alpha = \frac{I_c}{I_e}$$
 and  $\beta = \frac{I_c}{I_b}$   
Also  $I_e = I_b + I_c$   
 $\therefore \alpha = \frac{I_c}{I_b + I_c} = \frac{\frac{I_c}{I_b}}{1 + \frac{I_c}{I_b}} = \frac{\beta}{1 + \beta}$ 

Option (b) and (d) are therefore incorrect.

\_\_\_\_\_

# **Question143**

A realistic graph depicting the variation of the reciprocal of input resistance in an input characteristics measurement in a common emitter transistor configuration is : [Online April 10, 2016]

**Options:** 

A.



Β.



C.







## Solution:



# **Question144**

The ratio (R) of output resistance  $r_0$ , and the input resistance  $r_i$  in measurements of input and output characteristics of a transistor is typically in the range : [Online April 10,2016]

**Options:** 

A.  $R \sim 10^2 - 10^3$ B.  $R \sim 1 - 10$ C.  $R \sim 0.1 - 1.0$ D.  $R \sim 0.1 - 0.01$ Answer: C

## Solution:

#### Solution:

For C.B. configuration  $\frac{r_i}{r_o} \cong 0.1\Omega$ For CE and CC -configuration  $\frac{r_i}{r_o} \approx 1\Omega$ 

# **Question145**

An unknown transistor needs to be identified as a npn or pnp type. A multimeter, with +ve and -ve terminals, is used to measure resistance between different terminals of transistor. If terminal 2 is the base of the transistor then which of the following is correct for a pnp transistor? [Online April 9,2016]

#### **Options:**

A. +ve terminal 2, -ve terminal 3, resistance low

B. +ve terminal 2, -ve terminal 1, resistane high

C. +ve terminal 1, -ve terminal 2, resistance high

D. +ve terminal 3, -ve terminal 2, resistance high

Answer: C

## Solution:

#### Solution:

Connecting circuit according to question, it is clear



+ve terminal 1, -ve terminal 2, resistance high.

# **Question146**

If a, b, c, d are inputs to a gate and x is its output, then, as per the following time graph, the gate is :



#### **Options:**

A. OR

B. NAND

C. NOT

D. AND

Answer: A

## Solution:

#### Solution:

In case of an 'OR' gate the input is zero when all inputs are zero. If any one input is '1', then the output is '1'.

-----

# **Question147**

## To get an output of 1 from the circuit shown in figure the input must be



# [Online April 10, 2016]

## **Options:**

- A. a = 0, b = 0, c = 1
- B. a = 1, b = 0, c = 0
- C. a = 1, b = 0, c = 1
- D. a = 0, b = 1, c = 0

#### Answer: C

## Solution:

Truth table for given logical circuit

а	Ь	(a + b)	с	Y = (a + b).c
0	0	0	0	0
0	1	1	1	1
1	0	1	1	1
1	1	1	0	0

Output of OR gate must be 1 and c = 1So, a = 1, b = 0 or a = 0, b = 1.

\_\_\_\_\_

# **Question148**

## The truth table given in fig. represents :

A	В	Y
0	0	0
0	1	1
1	0	1
1	1	1

# [Online April 9, 2016]

#### **Options:**

A. OR - Gate

B. NAND- Gate

C. AND- Gate

D. NOR- Gate

#### Answer: A

## Solution:

#### Solution:

It represents OR-Gate.

A- B-		
Α	в	A + B = Y
0	0	0
0	1	1
1	0	1
1	1	1

------

# **Question149**

A red LED emits light at 0.1 watt uniformly around it. The amplitude of the electric field of the light at a distance of 1 m from the diode is : [2015]

#### **Options:**

A. 5.48 V/m

B. 7.75 V/m

C. 1.73 V/m

D. 2.45 V/m

Answer: D

# Solution:

Solution: Using U<sub>av</sub> =  $\frac{1}{2} \varepsilon_0 E_0^2$ But U<sub>av</sub> =  $\frac{P}{4\pi r^2 \times c}$   $\therefore \frac{P}{4\pi r^2} = \frac{1}{2} \varepsilon_0 E_0^2 \times c$   $E_0^2 = \frac{2P}{4\pi r^2 \varepsilon_0 c} = \frac{2 \times 0.1 \times 9 \times 10^9}{1 \times 3 \times 10^8}$  $\therefore E_0 = \sqrt{6} = 2.45 \text{V / m}$ 

\_\_\_\_\_

# **Question150**

A 2V battery is connected across AB as shown in the figure. The value of the current supplied by the battery when in one case battery's positive terminal is connected to A and in other case when positive terminal of battery is connected to B will respectively be:



# [Online April 11, 2015]

#### **Options:**

A. 0.4 A and 0.2 A

B. 0.2 A and 0.4 A

C. 0.1 A and 0.2 A

D. 0.2 A and 0.1 A

**Answer:** A

## Solution:

#### Solution:

When positive terminal connected to A then diode  $D_1$  is forward biased, current,  $I = \frac{2}{5} = 0.4A$ 

When positive terminal connected to B then diode  $D_2$  is forward biased, current,  $I = \frac{2}{10} = 0.2A$ 

 $E_0^2 = \frac{2P}{4\pi r^2 \epsilon_0 c} = \frac{2 \times 0.1 \times 9 \times 10^9}{1 \times 3 \times 10^8}$ :  $\therefore E_0 = \sqrt{6} = 2.45 V / m$ 

\_\_\_\_\_

# **Question151**

### In an unbiased n-p junction electrons diffuse from n-region to p-region because : [Online April 10, 2015]

#### **Options:**

- A. holes in p-region attract them
- B. electrons travel across the junction due to potential difference
- C. only electrons move from n to p region and not the vice-versa
- D. electron concentration in n-region is more compared to that in p-region

#### Answer: D

## Solution:

#### Solution:

Electrons in an unbiased p-n junction, diffuse from n -region i.e. higher electron concentration to p-region i.e. low electron concentration region.

\_\_\_\_\_

# **Question152**

# The forward biased diode connection is: [2014]

## **Options:**

A.











```
D.
```



#### Answer: A

# Solution:

Solution:

P n

For forward bias, p-side must be at higher potential than n-side.  $\Delta V~=$  (+)V e

\_\_\_\_\_

# **Question153**

For LED's to emit light in visible region of electromagnetic light, it should have energy band gap in the range of: [Online April 12, 2014]

## **Options:**

A. 0.1 eV to 0.4 eV

B. 0.5 eV to 0.8 eV

C. 0.9 eV to 1.6 eV  $\,$ 

D. 1.7 eV to 3.0 eV  $\,$ 

#### Answer: D

## Solution:

Energy band gap range is given by,  $E_g = \frac{hc}{\lambda}$ For visible region  $\lambda = (4 \times 10^{-7} \sim 7 \times 10^{-7})m$   $E_g = \frac{6.6 \times 10^{-34} \times 3 \times 10^8}{7 \times 10^{-7}}$   $= \frac{19.8 \times 10^{-26}}{7 \times 10^{-7}}$   $= \frac{2.8 \times 10^{-19}}{1.6 \times 10^{-19}}$  $E_g = 1.75eV$ 

# **Question154**

A Zener diode is connected to a battery and a load as show below:



The currents, I, I  $_Z$  and I  $_L$  are respectively. [Online April 11, 2014]

#### **Options:**

A. 15 mA, 5 mA, 10 mA

B. 15 mA, 7.5 mA, 7.5 mA

C. 12.5 mA, 5 mA, 7.5 mA

D. 12.5 mA, 7.5 mA, 5 mA

Answer: D

## Solution:

Solution: Here, R =  $4k\Omega = 4 \times 10^{3}\Omega$ V<sub>i</sub> = 60VZener voltage V<sub>z</sub> = 10VR<sub>L</sub> =  $2k\Omega = 2 \times 10^{3}\Omega$ Load current, I<sub>L</sub> =  $\frac{V_{Z}}{R_{L}} = \frac{10}{2 \times 10^{3}} = 5mA$ Current through R, I =  $\frac{V_{i} - V_{Z}}{R}$ 

```
= \frac{60 - 10}{4 \times 10^{3}} = \frac{50}{4 \times 10^{3}} = 12.5 \text{mA}
Fom circuit diagram,
I = I<sub>Z</sub> + I<sub>L</sub>
\Rightarrow 12.5 = I_Z + 5
\Rightarrow I_Z = 12.5 - 5 = 7.5 \text{mA}
```

\_\_\_\_\_

# **Question155**

An n-p-n transistor has three leads A, B and C. Connecting B and C by moist fingers, A to the positive lead of an ammeter, and C to the negative lead of the ammeter, one finds large deflection. Then, A, B and C refer respectively to: [Online April 9,2014]

**Options:** 

A. Emitter, base and collector

- B. Base, emitter and collector
- C. Base, collector and emitter
- D. Collector, emitter and base

Answer: C

## Solution:

#### Solution:

In the given question, A, B and C refer base, collector and emitter respectively.

\_\_\_\_\_

# **Question156**

$$A \leftarrow 50 \Omega$$

$$B \leftarrow 50 \Omega$$

$$B \leftarrow V_{CC} - 6V$$

$$R = 10 k\Omega$$

Given: A and B are input terminals. Logic 1 = > 5 V Logic 0 = < 1 V Which logic gate operation, the above circuit does? [Online April 19, 2014]

## **Options:**

A. AND Gate

- B. OR Gate
- C. XOR Gate
- D. NOR Gate
- Answer: A

## Solution:

Solution: AND Gate

\_\_\_\_\_

# **Question157**

Identify the gate and match A, B, Y in bracket to check.



[Online April 9, 2014]

#### **Options:**

- A. AND (A = 1, B = 1, Y = 1)
- B. OR (A = 1, B = 1, Y = 0)
- C. NOT (A = 1, B = 1, Y = 1)
- D. XOR (A = 0, B = 0, Y = 0)

#### Answer: A

## Solution:



In this case output Y is equivalent to AND gate.

------

# **Question158**

Which of the following circuits correctly represents the following truth table ?

Α	в	С
0	0	0
0	1	0
1	0	1
1	1	0

# [Online April 25, 2014]

## **Options:**



















## Solution:

## Solution:

For circuit 1 A. B =  $\overline{Y + A} = C$  $\overline{Y + A} = C$ В Α 0 0 0 1 0 0 1 0 0 1 0 0 0 1 1 0 1 1 1 0

\_\_\_\_\_

# **Question159**

The I-V characteristic of an LED is [2013]

#### **Options:**





B.



C.



D.





# Solution:

Solution:

For same value of current higher value of voltage is required for higher frequency hence (a) is correct answer.

------

# **Question160**

Figure shows a circuit in which three identical diodes are used. Each diode has forward resistance of 20Omega and infinite backward

resistance. Resistors  $R_1$  =  $R_2$  =  $R_3$  = 500. Battery voltage is 6V . The current through  $R_3$  is :



[Online April 22, 2013]

#### **Options:**

A. 50 mA

B. 100 mA

C. 60 mA

D. 25 mA

Answer: A

## Solution:

#### Solution:

Here, diodes  $\rm D_1$  and  $\rm D_2$  are forward biased and  $\rm D_3$  is reverse biased. Therefore current through  $\rm R_3$ 

 $i = \frac{V}{R'} = \frac{6}{120} = \frac{1}{20}A = 50mA$ 

# Question161

A system of four gates is set up as shown. The 'truth table' corresponding to this system is :



[Online April 23, 2013]

**Options:** 

A.

A	в	Y
0	0	1
0	1	0
1	0	0
1	1	1

В.

Α	в	Y
0	0	0
0	1	0
1	0	1
1	1	0

C.

Α	В	Y
0	0	1
0	1	0
1	0	1
1	1	0

D.

	A	в	Y
	0	0	1
	0	1	1
	1	0	0
-	1	1	0

## Answer: A

# Solution:

Solution: In the given system all four gate is NOR gate Truth Table

A	B	$(y' = \overline{A + B})$	(y'' = <u>A+y'</u> )	y''' = (A + y'')	$y = \overline{y^{\prime\prime} + y^{\prime\prime\prime}}$
0	0	1	0	0	1
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

i.e.,

А	в	Y
0	0	1
0	1	0
1	0	0
1	1	1

\_\_\_\_\_

# **Question162**

Consider two npn transistors as shown in figure. If 0 Volts corresponds to false and 5 Volts correspond to true then the output at C corresponds to :



[Online April 9, 2013]

#### **Options:**

A. A NAND B

B. A OR B

C. A AND B

D. A NOR B

Answer: A

## Solution:

The output at C corresponds to A NAND B or  $\overline{A \cdot B} = C$ 

\_\_\_\_\_

# **Question163**

Which logic gate with inputs A and B performs the same operation as that performed by the following circuit?



# [Online May 7, 2012]

#### **Options:**

A. NAND gate

- B. OR gate
- C. NOR gate
- D. AND gate
- Answer: B

## Solution:

#### Solution:

When either of A or B is 1 i.e. closed then lamp will glow. In this case, Truth table

Inp	outs	Output
А	В	Y
0	0	0
0	1	1
1	0	1
1	1	1

This represents OR gate.

\_\_\_\_\_

# **Question164**

This question has Statement 1 and Statement 2. Of the four choices given after the Statements, choose the one that best describes the two Statements.

## Statement 1: A pure semiconductor has negative temperature coefficient of resistance. Statement 2: On raising the temperature, more charge carriers are released into the conduction band. [Online May 12, 2012]

#### **Options:**

A. Statement 1 is false, Statement 2 is true.

B. Statement 1 is true, Statement 2 is false.

C. Statement 1 is true, Statement 2 is true, Statement 2 is not a correct explanation of Statement 1.

D. Statement 1 is true, Statement 2 is true, Statement 2 is the correct explanation of Statement 1.

#### Answer: D

## Solution:

#### Solution:

Temperature coefficient of resistance is negative for pure semiconductor. And no. of charge carriers in conduction band increases with increase in temperature.

------

# **Question165**

## Truth table for system of four NAND gates as shown in figure is :



## [2012]

**Options:** 

A.

Α	в	Y
0	0	0
0	1	1
1	0	1
1	1	0

A	в	Y
0	0	0
0	1	0
1	0	1
1	1	1

C.

Α	в	Y
0	0	1
0	1	1
1	0	0
1	1	0

D.

A	В	Y
0	0	1
0	1	0
1	0	1
1	1	1

Answer: A

## Solution:



By expanding this Boolen expression  $Y = A \cdot \overline{B} + B \cdot \overline{A}$ Thus the truth table for this expression should be (a).

#### -----

# **Question166**

The figure shows a combination of two NOT gates and a NOR gate.



The combination is equivalent to a

# [Online May 26, 2012]

#### **Options:**

- A. NAND gate
- B. NOR gate
- C. AND gate
- D. OR gate

Answer: C

## Solution:

#### Solution:

Truth table is as shown :

A	В	Ā	B	$\overline{A} + \overline{B}$	$\overline{A+B}$
0	0	1	1	1	0
0	1	1	0	1	0
1	0	0	1	1	0
1	1	0	0	0	1

Thus the combination of two NOT gates and one NOR gate is equivalent to a AND gate.

-----

# **Question167**

# Which one of the following is the Boolean expression for NOR gate? [Online May 19, 2012]

**Options:** 

- A. Y =  $\overline{A + B}$
- B. Y =  $\overline{A \cdot B}$
- C. Y = A. B
- D. Y =  $\overline{A}$
- Answer: A

## Solution:

#### Solution: NOR gate is the combination of NOT and OR gate. Boolean expression for NOR gate is Y = A + B

-----

# **Question168**

# The output of an OR gate is connected to both the inputs of a NAND gate. The combination will serve as a: [2011 RS]

#### **Options:**

- A. NOT gate
- B. NOR gate
- C. AND gate
- D. OR gate

Answer: B

## Solution:

Solution:

When both inputs of NAND gate are jointed to form a single input, it behaves as NOT gate OR + NOT = NOR. (A + B) = N OR gate



# **Question169**

## The combination of gates shown below yields



# [2010]

#### **Options:**

A. OR gate

- B. NOT gate
- C. XOR gate
- D. NAND gate

#### Answer: A

## Solution:

The final boolean expression of these gates is,  $X = (\overline{A} \cdot \overline{B}) = \overline{A} + \overline{B} = A + B \Rightarrow OR$  gate ------

# **Question170**

A p-n junction (D) shown in the figure can act as a rectifier. An alternating current source (V) is connected in the circuit.



The current (I) in the resistor (R) can be shown by : [2009]

#### **Options:**

A.



Β.













Solution:

The given circuit will work as half wave rectifier as it conducts during the positive half cycle of input AC. Forward biased in one half cycle and reverse biased in the other half cycle].

\_\_\_\_\_

# **Question171**

The logic circuit shown below has the input waveforms 'A' and 'B' as shown. Pick out the correct output waveform.



**Options:** 

A.



Β.



C.



D.





## Solution:

Solution:

The final boolean expression

	Α	в	Y
	0	0	0
	0	1	0
	1	0	0
	1	1	1
Y	/ = hus	(A + , it is	B) : s an

# **Question172**

A working transistor with its three legs marked P, Q and R is tested using a multimeter. No conduction is found between P and Q. By connecting the common (negative) terminal of the multimeter to R and the other (positive) terminal to P or Q, some resistance is seen on the multimeter. Which of the following is true for the transistor? [2008]

#### **Options:**

- A. It is an npn transistor with R as base
- B. It is a pnp transistor with R as base
- C. It is a pnp transistor with R as emitter
- D. It is an npn transistor with R as collector

#### Answer: B

## Solution:

**Solution:** It is a p-n-p transistor with R as base.

# Question173

In the circuit below, A and B represent two inputs and C represents the output.



The circuit represents [2008]

**Options:** 

- A. NOR gate
- B. AND gate
- C. NAND gate
- D. OR gate

Answer: D

## Solution:

Solution:



The truth table for the above circuit is :

Α	в	с
1	1	1
1	0	1
0	1	1
0	0	0

when either A or B conducts, the gate conducts. It means C = A + B which is for OR gate.

#### ------

# **Question174**

If in a p-n junction diode, a square input signal of 10 V is applied as shown



Then the output signal across  $R_L$  will be [2007]

#### **Options:**

A.



В.





Answer: A

Solution:

Solution: The current will flow through  $\boldsymbol{R}_L$  when the diode is forward biased.

\_\_\_\_\_

# **Question175**

### Carbon, silicon and germanium have four valence electrons each. At room temperature which one of the following statements is most appropriate ? [2007]

#### **Options:**

A. The number of free electrons for conduction is significant only in Si and Ge but small in C.

B. The number of free conduction electrons is significant in C but small in Si and Ge.

C. The number of free conduction electrons is negligibly small in all the three.

D. The number of free electrons for conduction is significant in all the three.

#### Answer: A

## Solution:

#### Solution:

Si and Ge are semiconductors but C is an insulator. In Si and Ge at room temperature, the energy band gap is low due to which electrons in the covalent bonds gains kinetic energy and break the bond and move to conduction band. As a result, hole is created in valence band. So, the number of free electrons is significant in Si and Ge.

# **Question176**

# If the lattice constant of this semiconductor is decreased, then which of the following is correct ? [2006]

#### **Options:**

A. All E  $_{\rm c}$ , E  $_{\rm a}$ , E  $_{\rm v}$  increase

B. E  $_{\rm c}$  and E  $_{\rm v}$  increase, but E  $_{\rm a}$  decreases

C. E  $_{\rm c}$  and E  $_{\rm v}$  decrease, but E  $_{\rm q}$  increases

D. All E  $_{\rm c}$ , E  $_{\rm q}$ , E  $_{\rm v}$  decrease

#### Answer: C

## Solution:

#### Solution:

(c) A crystal structure is made up of a unit cell arranged in a particular way; which is periodically repeated in three dimensions on a lattice. The spacing between unit cells in various directions is called its lattice constants. As lattice constants increases the band-gap ( $E_g$ ), also increases which means more energy would be required by electrons to reach the conduction band from the valence band. Automatically  $E_c$  and  $E_v$  decreases.

\_\_\_\_\_

\_\_\_\_\_

# **Question177**

# A solid which is not transparent to visible light and whose conductivity increases with temperature is formed by [2006]

#### **Options:**

- A. Ionic bonding
- B. Covalent bonding
- C. Vander Waals bonding
- D. Metallic bonding

#### Answer: B

## Solution:

#### Solution:

Van der Waal's bonding is attributed to the attractive forces between molecules of a liquid. The conductivity of semiconductors (covalent bonding) and insulators (ionic bonding) increases with increase in temperature. Solid which is formed by covalent bond is not transparent to visible light and its conductivity increase with temperature.

Question178

If the ratio of the concentration of electrons to that of holes in a semiconductor is  $\frac{7}{5}$  and the ratio of currents is  $\frac{7}{4}$ , then what is the ratio of their drift velocities? [2006]

## **Options:**

- A.  $\frac{5}{8}$ B.  $\frac{4}{5}$ C.  $\frac{5}{4}$
- D.  $\frac{4}{7}$

# Answer: C

# Solution:

Relation between drift velocity and current is

 $I = nAeV_{d}$   $\frac{I_{e}}{I_{h}} = \frac{n_{e}eAv_{e}}{n_{h}eAv_{h}}$   $\Rightarrow 74 = \frac{7}{5} \times \frac{V_{e}}{v_{h}}$   $\Rightarrow \frac{V_{e}}{v_{h}} = \frac{5}{4}$ 

# Question179

The circuit has two appositively connected ideal diodes in parallel. What is the current flowing in the circuit?



D. 1.33 A

## Answer: B

# Solution:

#### Solution:

 $\rm D_2$  is forward biased.  $\rm D_1$  is reversed biased. So, it will act like an open circuit.

So effective resistance of the circuit  $R = 4 + 2 = 6\Omega$   $\therefore$   $i = \frac{E}{R} = \frac{12}{6} = 2A$ 

\_\_\_\_\_

# **Question180**

# In the following, which one of the diodes reverse biased? [2006]

**Options:** 





## Solution:

p-side connected to low potential and n-side is connected to high potential.

------

# **Question181**

In a common base mode of a transistor, the collector current is 5.488 mA for an emitter current of 5.60 mA. The value of the base current amplification factor ( $\beta$ ) will be [2006]

**Options:** 

A. 49

B. 50

C. 51

D. 48

Answer: A

## Solution:

Collector current, I<sub>C</sub> = 5.488mA, Emitter current I<sub>e</sub> = 5.6mA  $\alpha = \frac{I_c}{I_e} = \frac{5.488}{5.6},$  $\beta = \frac{\alpha}{1 - \alpha} = 49$ 

\_\_\_\_\_

# **Question182**

The electrical conductivity of a semiconductor increases when electromagnetic radiation of wavelength shorter than 2480 nm is incident on it. The band gap in (eV) for the semiconductor is [2005]

**Options:** 

A. 2.5 eV

B. 1.1 eV

C. 0.7 eV

D. 0.5 eV

Answer: D

## Solution:

Band gap = energy of photon of wavelength 2480 nm. So, Band gap, E  $_{g} = \frac{hc}{\lambda}$ 

 $= \left(\frac{6.63 \times 10^{-34} \times 3 \times 10^8}{2480 \times 10^{-9}}\right) \times \frac{1}{1.6 \times 10^{-19}} eV$ = 0.5eV

\_\_\_\_\_

# **Question183**

In a common base amplifier, the phase difference between the input signal voltage and output voltage is [2005]

**Options:** 

- А. п
- B.  $\frac{\pi}{4}$
- C.  $\frac{\pi}{2}$
- D. 0

Answer: D

## Solution:

#### Solution:

In common base amplifier circuit, input and output voltage are in the same phase. So, the phase difference between input voltage signal and output voltage signal is zero.

-----

# **Question184**

# When p-n junction diode is forward biased then [2004]

#### **Options:**

A. both the depletion region and barrier height are reduced

- B. the depletion region is widened and barrier height isreduced
- C. the depletion region is reduced and barrier height isincreased
- D. Both the depletion region and barrier height areincreased

#### **Answer:** A

## Solution:

Solution:

In forward biasing, the p type is connected to positive terminal and n type is connected with negative terminal.

So holes from p region and electron from n region are pushed towards the Junction which reduces the width of depletion layer. Also, distance between diffused holes and electrons decrease, which decrease electric field hence barrier potential.

\_\_\_\_\_

# **Question185**

# When npn transistor is used as an amplifier [2004]

#### **Options:**

- A. electrons move from collector to base
- B. holes move from emitter to base
- C. electrons move from base to collector
- D. holes move from base to emitter

#### **Answer: C**

#### Solution:

**Solution:** In npn transistor, electrons moves from emitter to base.

\_\_\_\_\_

# **Question186**

For a transistor amplifier in common emitter configuration for load impedance of  $1k\Omega(h_{fe} = 50 \text{ and } h_{oe} = 25)$  the current gain is [2004]

#### **Options:**

- A. 24.8
- B. 15.7
- C. 5.2
- D. 48.78

#### **Answer: D**

## Solution:

**Solution:** In common emitter configuration for transistor amplifier current gain  $A_{i} = \frac{-h_{fe}}{1 + b_{oe}R_{L}}$ Where  $h_{fe}$  and  $h_{oe}$  are hybrid parameters.  $\therefore A_{i} = \frac{-50}{1 + 25 \times 10^{-6} \times 1 \times 10^{3}}$  = -48.78

# **Question187**

## A strip of copper and another of germanium are cooledfrom room temperature to 80K. The resistance of [2003]

#### **Options:**

A. each of these decreases

- B. copper strip increases and that of germanium decreases
- C. copper strip decreases and that of germanium increases
- D. each of these increases

#### Answer: C

## Solution:

#### Solution:

Copper is a conductor and in conductor resistance decreases with decrease in temperature. Germanium is a semicon ductor. In semi-conductor resistance increases with decrease in temperature.

-----

# **Question188**

# The difference in the variation of resistance withtemeperature in a metal and a semiconductor arisesessentially due to the difference in the [2003]

#### **Options:**

A. crystal sturcture

- B. variation of the number of charge carriers with temperature
- C. type of bonding
- D. variation of scattering mechanism with temperature

#### Answer: B

## Solution:

#### Solution:

When the temperature increases, certain bounded electrons become free which tend to promote conductivity. Simultaneously number of collisions between electrons and positive kernels increases which decrease the relaxation time.

-----

# **Question189**

# In the middle of the depletion layer of a reverse- biasedp-n junction, the [2003]

#### **Options:**

- A. electric field is zero
- B. potential is maximum
- C. electric field is maximum
- D. potential is zero

Answer: A

## Solution:

#### Solution:

In reverse biasing the width of depletion region increases, and current flowing through diode is zero. Thus, electric field is zero at middle of depletion region.

\_\_\_\_\_

# Question190

## At absolute zero, Si acts as [2002]

#### **Options:**

A. non-metal

B. metal

C. insulator

D. none of these

Answer: C

## Solution:

#### Solution:

Pure silicon, at OK, will contain all the electrons in bounded state. The conduction band will be empty. So there will be no free electrons (in conduction band) and holes (in valence band). Therefore no electrons from valence band are able to shift to conduction band due to thermal agitation. Pure silicon will act as insulator.

\_\_\_\_\_

# **Question191**

By increasing the temperature, the specific resistance of aconductor and a semiconductor [2002]

#### **Options:**

A. increases for both
- B. decreases for both
- C. increases, decreases
- D. decreases, increases

#### Answer: C

## Solution:

Solution:

Specific resistance (resistivity) is given by  $\rho = \frac{m}{ne^2 \tau}$  where n = no. of free electrons per unit volume

and  $\tau =$  average relaxation time

For a conductor with rise in temperature n increases. Increase in temperature results increase in number of collision between free electrons due to which relaxation time T decreases. But the decrease in  $\tau$  is more dominant than increase in n resulting an increase in the value of  $\rho$ .

For a semiconductor with rise in temperature, n increases and  $\tau$  decreases. But the increase in n is more dominant than decrease in  $\tau$  resulting in a decrease in the value of  $\rho$ .

\_\_\_\_\_

**Question192** 

# The energy band gap is maximum in [2002]

#### **Options:**

A. metals

B. superconductors

C. insulators

D. semiconductors.

**Answer: C** 

Solution:

#### Solution:

In insulators, valence band is completely filled while conduction band is empty. The energy band gap is maximum in insulators.

\_\_\_\_\_

# **Question193**

### The part of a transistor which is most heavily doped to produce large number of majority carriers is [2002]

#### **Options:**

A. emmiter

- B. base
- C. collector

D. can be any of the above three.

Answer: A

# Solution:

Emitter main function is to supply the majority charge carrriers towards the collector. Therefore emitter is most heavily doped.

-----