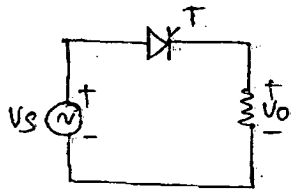


Cycloconverter


Fixed AC $\longrightarrow$ Variable AC
 $(V_s, f_s) \quad (V_o, f_o)$

$f_o < f_s \rightarrow$ step down cycloconv^r


$f_o > f_s \rightarrow$ step up cycloconv^r




AC $\longrightarrow$ DC

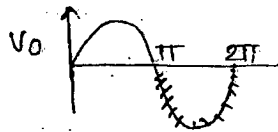

+ve rectifier

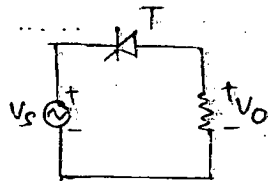


AC $\longrightarrow$ DC

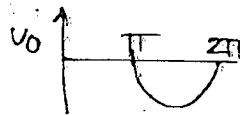

-ve rectifier


* Mid point cycloconverter $\rightarrow$

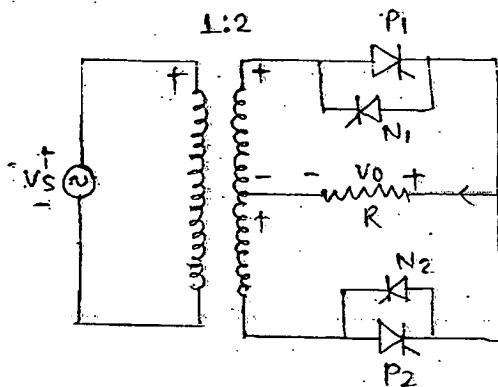

+ve, $P_1 N_2 (F)$

-ve, $P_2 N_1 (F)$


* Bridge cycloconverter $\rightarrow$

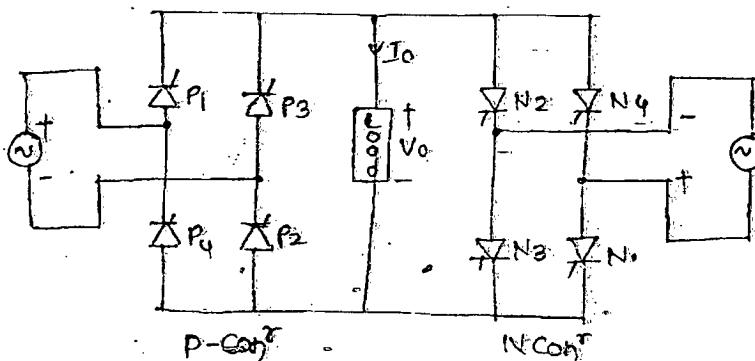

+ve $P_1 P_2, N_1 N_2 (F)$

-ve $P_3 P_4, N_3 N_4 (F)$

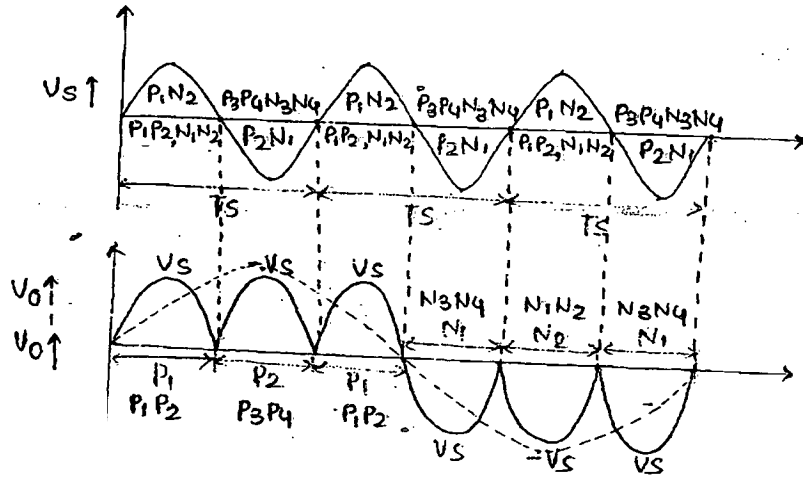Stepdown cycle [$f_0 < f_s$] $\rightarrow$ Let $f_0 = \frac{1}{3}f_s$, $T_0 = 3T_s$



$$F_0 = \frac{1}{3} F_s \quad P_1 P_2 P_1 \quad N_1 N_2 N_1$$

$$+ - + \quad - + -$$

$$F_0 = \frac{1}{4} F_s \quad P_1 P_2 P_1 P_2 \quad N_2 N_1 N_2 N_1$$

$$+ - + - \quad + - + -$$


R Load +

$$V_{or} = \frac{U_m}{\sqrt{2 \cdot \pi}} \left\{ (\pi - \alpha) + \frac{1}{2} \sin 2\alpha \right\}^{1/2}$$

RL Load $\rightarrow$

$$V_{or} = \frac{V_m}{\sqrt{2A}} \left\{ (\beta - \alpha) + \frac{1}{2} (\sin 2\alpha - \sin 2\beta) \right\}^{1/2}$$

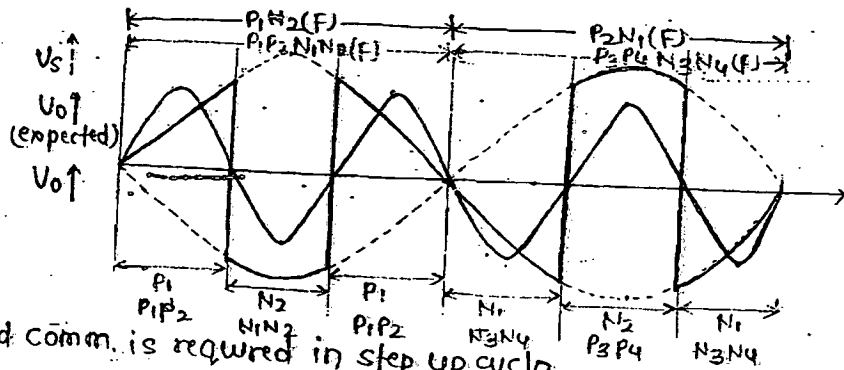
Stepup cycloconverter $\rightarrow (f_o > f_s)$ Let $f_o = 3f_s, T_s = 3T_o$



- * Forced comm. is required in step up cyclo.
- * Harmonic distortion is high in cycloconv^r therefore it operates with low PF.

Application → It is used for high power, low speed & reverseful AC drives.

* 3φ to 1φ cycloconverter →

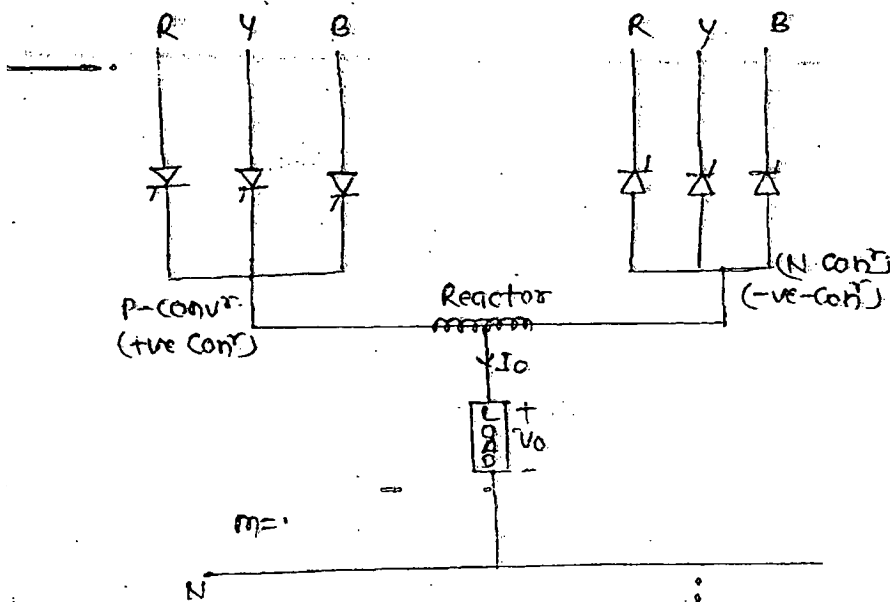


$$(1) \alpha_p + \alpha_n = 180^\circ$$

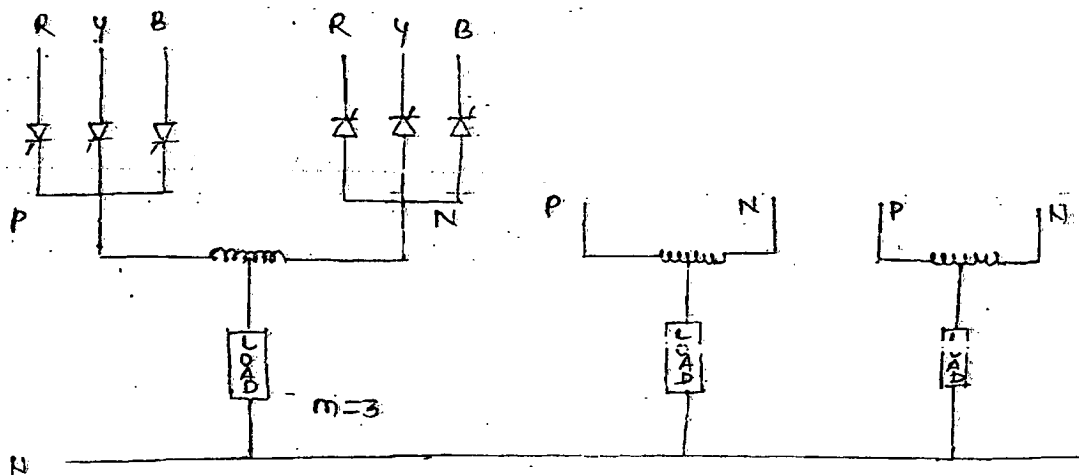(2) Reactor

$$V_{o1} = V_{ph} \cdot \frac{m}{\pi} \sin \frac{\pi}{m} \cdot \cos \alpha$$

3φ to 3φ cycloconverter → (18 thy. cycloconverter)



$$V_{o1/phase} = V_{ph} \cdot \frac{m}{\pi} \sin \frac{\pi}{m} \cdot \cos \alpha$$

If a pulse con^r is used in 3ph to 3ph. cycloconverter then we require 36 thy.

Therefore it is also known as 36 thy. cyclo.

$$V_{OL/Phase} = V_L \cdot \frac{m}{\pi} \sin \frac{\pi}{m} \cdot \cos \alpha$$