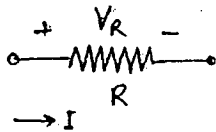


DIODE

* It is a non linear Resistor.

LINEAR RESISTOR :-




$$V \propto I$$


$$\downarrow$$

$$R$$



$$V = RI$$

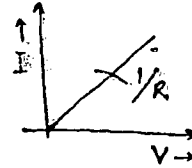

IDEAL DIODE :-

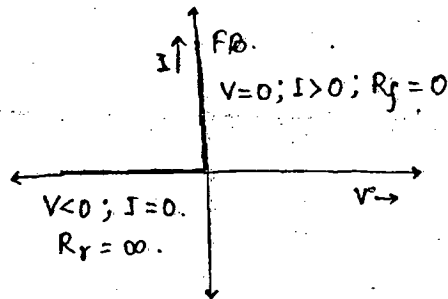

PRACTICAL DIODE

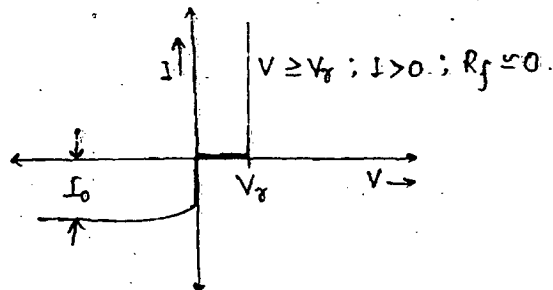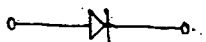

$$V_g = 0.1V \text{ to } 0.3V \text{ (Ge)}$$


$$V_g = 0.5V \text{ to } 0.7V \text{ (Si)}$$

I_0 = Reverse saturated current

$$I_0 = \mu A \text{ or } nA$$


(Ge) (Si)

PIECE WISE LINEAR MODEL

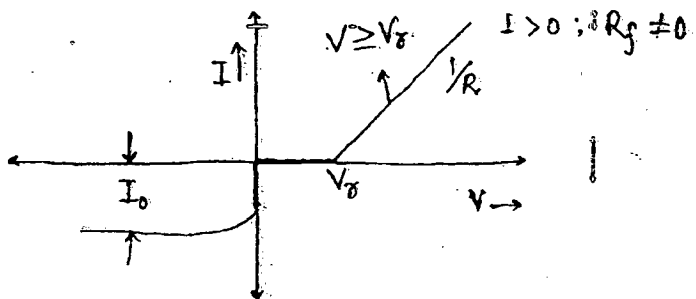


□ EQUIVALENT MODELS IN ON STATE


IDEAL

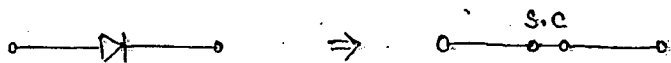

PRACTICAL

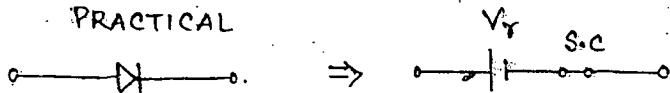


PIECE WISE LINEAR

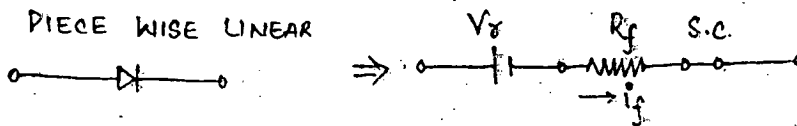

QUESTION $\Rightarrow$ The VI characteristics of a diode is defined as

$$i = \begin{cases} \frac{V - 0.7}{500} & V \geq 0.7 \\ 0 & V < 0.7 \end{cases}$$

$\therefore R_f$

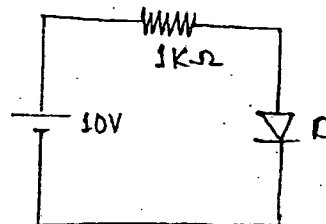


Solution $\Rightarrow$

$$\frac{V - 0.7}{500}$$

R_f



$$\Rightarrow 10 - i(1000 + 500) - 0.7 = 0$$
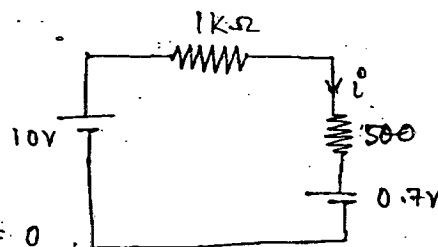
$$\Rightarrow i = \frac{10 - 0.7}{1500} = 6.2 \text{ mA}$$




$\therefore R_f$ is present
equivalent cir-
is an piece
wise linear
diode.

QUESTION $\Rightarrow$

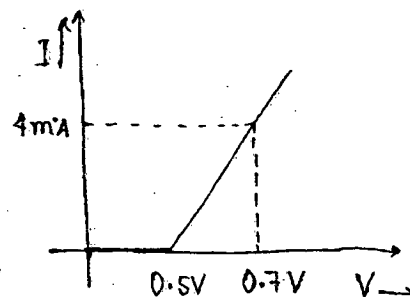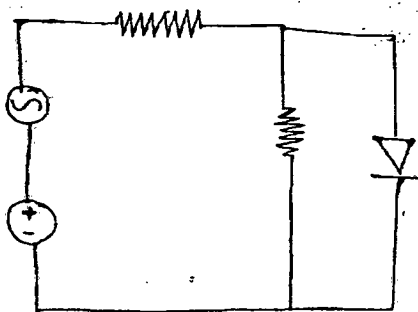
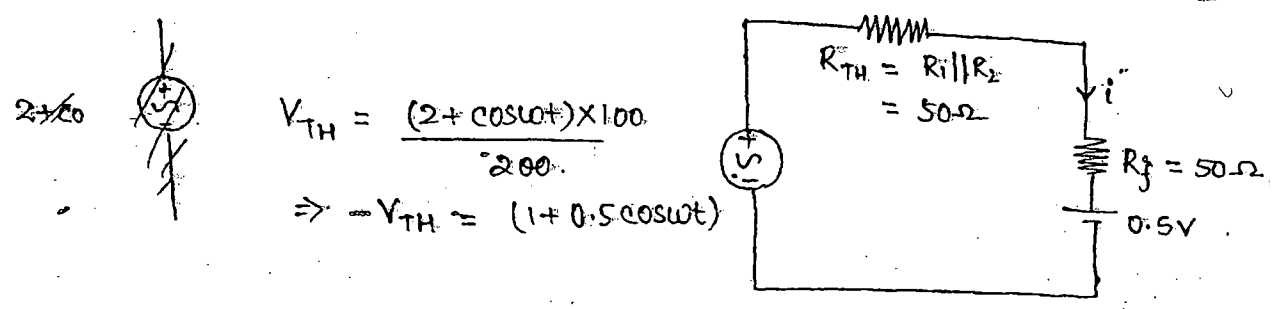
$$V_T = 0.5V, \quad R_f = \frac{\Delta V}{\Delta I} = \frac{0.7 - 0.5}{4mA - 0} = 50\Omega$$



$$i = \frac{1 + 0.5 \cos wt - 0.5}{100} = \frac{0.5(1 + \cos wt)}{1000} \times 10$$

$$\Rightarrow i = 5(1 + \cos wt) \text{ mA} = 5 + 5 \cos wt$$

↓
DC



□ V-I CHARACTERISTICS EQUATION OF DIODE.

$$I = I_0 (e^{\frac{V}{nV_T}} - 1)$$

Where ; I = Total current through diode.

I_0 = Reverse saturated current.

V = Applied voltage drop across diode.

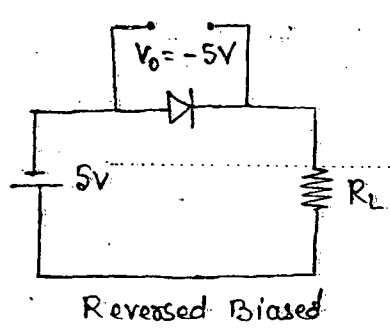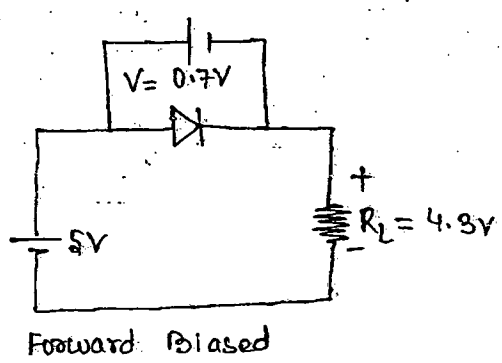

η = Idealized factor.

$\eta = 1$ (Ge) | $\eta = 1$ (Si) → Integrated electronics
 $\eta = 2$ (Si) | $\eta = 2$ (Si) → Discrete electronics.

$$V_T = \frac{KT}{q} = \frac{T}{11,600}$$

Volt eq Temp (or) Thermal Voltage

Where K = Boltzmann constant
 $= 1.38 \times 10^{-23} \text{ J/K}$

T = Temperature in Kelvin.

q = charge.

At $T = 27^\circ\text{C}$ (Room Temp) $= 300 \text{ K}$

$$q = 1.6 \times 10^{-19} \text{ C}$$

$$V_T = \frac{300}{\frac{1.6 \times 10^{-19}}{1.38 \times 10^{-23}}} \quad \text{or} \quad \frac{T}{11,600} = \frac{300}{11,600} = 26 \text{ mV (or)} \\ 0.026 \text{ V} \quad \text{or} \quad 26 \text{ mV (or)} \quad 0.026 \text{ V}$$

□ FORWARD BIASED.

$$I = I_0 (e^{V/V_T} - 1) \quad \eta = 1$$

$$\Rightarrow V \geq V_g \Rightarrow V = V_g = 0.7 \text{ V} \\ = 700 \text{ mV}$$

$$I = I_0 (e^{\frac{700 \text{ mV}}{26 \text{ mV}}} - 1)$$

$$I = \underbrace{I_0}_{\text{mA}} \cdot \underbrace{e^{V_D/V_T}}_A \text{ mA. } I_0 \text{ is neglected.}$$


REVERSED BIASED.

$$I = I_0 (e^{V/V_T} - 1)$$

$V < 0$; $V = -V$; Assume -5 V .


$$I = I_0 [e^{-5/26 \text{ mV}} - 1]$$
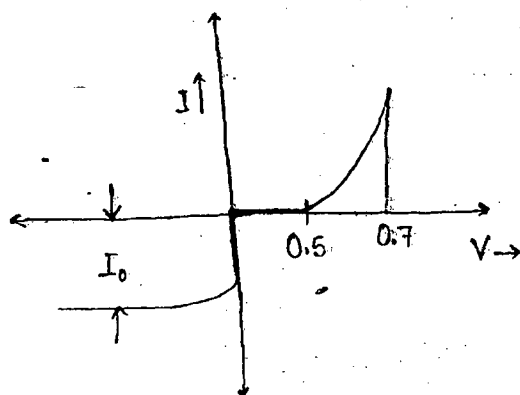
$$= I_0 [e^{\frac{1}{0}} - 1] \Rightarrow I = -I_0$$



$$V_{D \text{ cut in}} = 0.5V$$

$$V_{D \text{ active}} = 0.7V$$

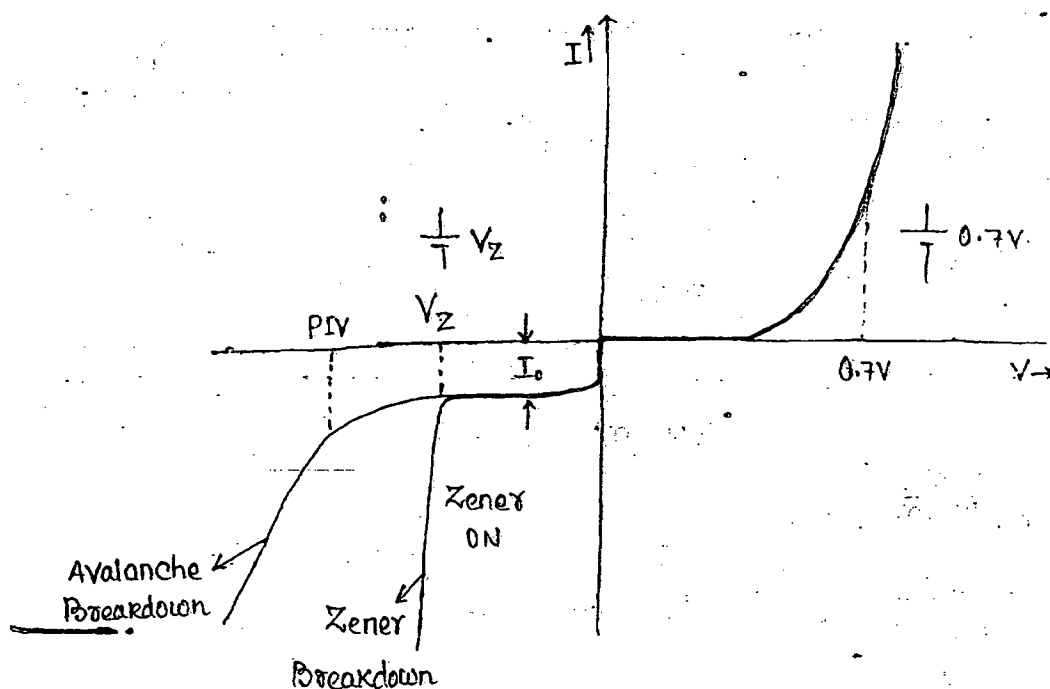

Reversed Biased $\Rightarrow$ " I_0 " increases by $7\%/^{\circ}C$ rise in temperature.

I_0 doubles for every $10^{\circ}C$ rise in temperature

$$1 + 0.07 = (1.07)^{10} = 1.96 \approx 2$$

Forward Biased $\Rightarrow I = I_0 \cdot e^{V_D/V_T}$

$V_D = V_T \ln \left(\frac{I}{I_0} \right)$ Fixed by Battery
depend on temperature.

$$\frac{dV_0}{dT} = -2.5 \text{ mV}/^\circ\text{C}$$

Ch-2

Q6, Q9 40 pA, every $10^\circ\text{C} \rightarrow$ double

$$30^\circ\text{C} = 10 \text{ pA} \times 2 = 20 \text{ pA}$$

$$40^\circ\text{C} = 20 \times 2 = 40 \text{ pA}$$

$$I_{02} = I_{01} 2^{(T_2 - T_1)/10} \rightarrow \text{Shortcut}$$


Q9. $4^\circ\text{C} \rightarrow -10 \text{ mV}$

$20^\circ\text{C} \rightarrow -50 \text{ mV}$


CLIPPERS

Clippers


1. SHUNT CLIPPER

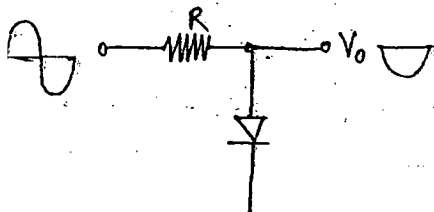


2. SERIES CLIPPER

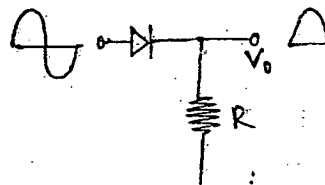

3. OUTPUT FOLLOWING INPUT DESIGN

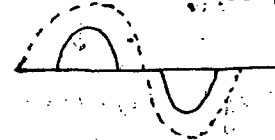


4. Two Independent Level Clipping

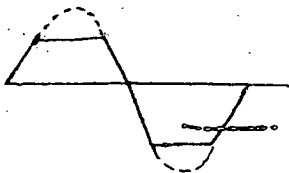

5. Attenuation

$$V_o = \frac{V_i}{A}$$

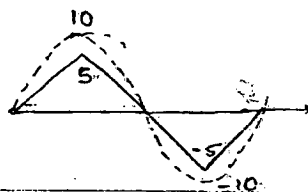


6. Single Branch Design.

7. Multi branch Design.

14/10/14

1. SHUNT CLIPPERS.

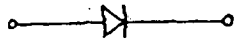

$V_A > V_K$ Diode will be ON S.C. $\rightarrow$ Forward Biased

$V_A \leq V_K$ Diode will be OFF D.C. $\rightarrow$ Reversed Biased.

Case I $\rightarrow$

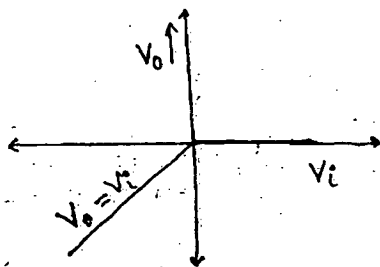
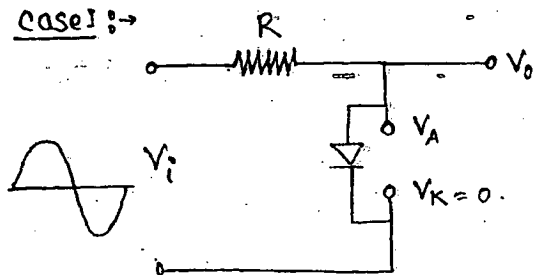


Fig: TRANSFER STUDY

Condition $\rightarrow$

$V_i < 0$ Diode OFF $\rightarrow V_o = V_i$

$V_i > 0$ Diode ON $\rightarrow V_o = 0$


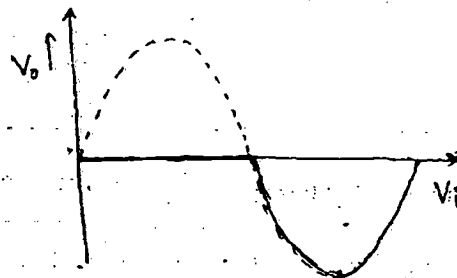


Fig: O/P CHARACTERISTICS.

Case II $\rightarrow$

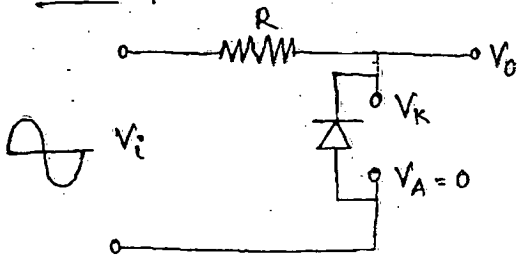

Condition $\rightarrow$

$V_i < 0$ Diode ON $\rightarrow V_o = 0$

$V_i > 0$ Diode OFF $\rightarrow V_o = V_i$

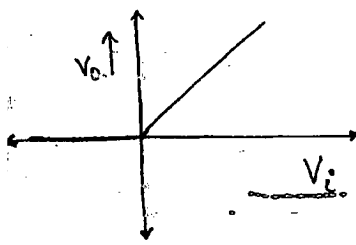


Fig:- TRANSFER STUDY


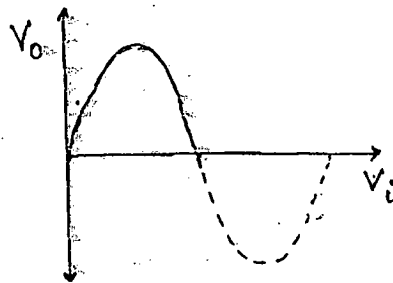


Fig:- O/P CHARACTERISTICS

NOTE:- Limiting of output comes by battery.

case III :-

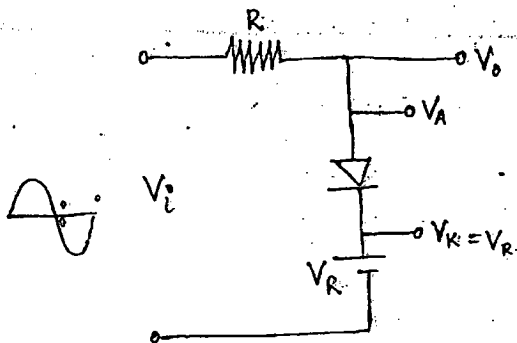

CONDITIONS :-

$V_i < V_R$ Diode OFF $V_o = V_i$

$V_i > V_R$ Diode ON $V_o = V_R$

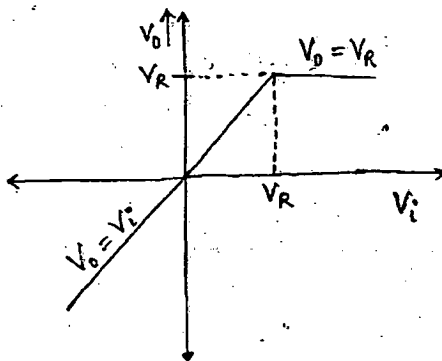


Fig:- TRANSFER STUDY


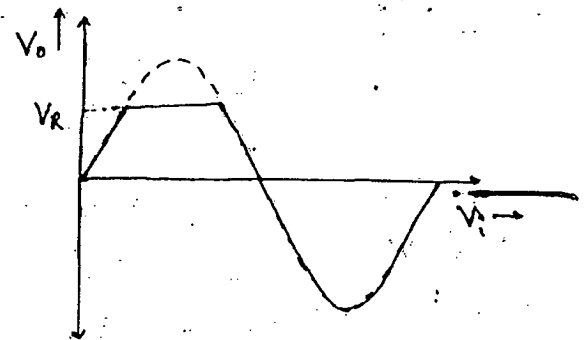


Fig:- O/P CHARACTERISTICS



case IV :-

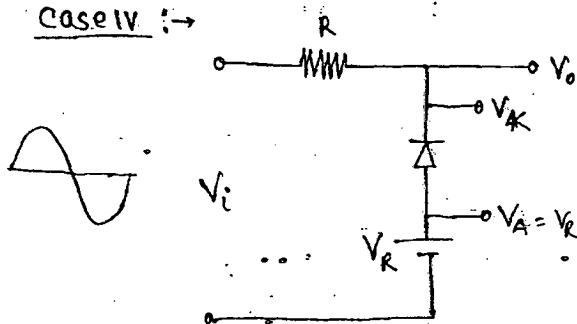


condition :-

$V_i < V_R$ Diode OFF $V_o = V_R$

$V_i > V_R$ Diode ON $V_o = V_i$

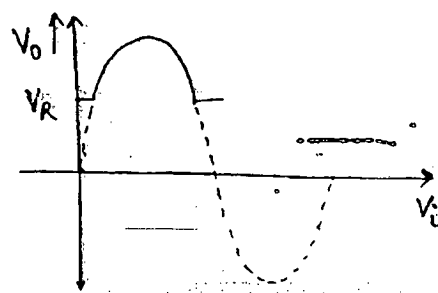
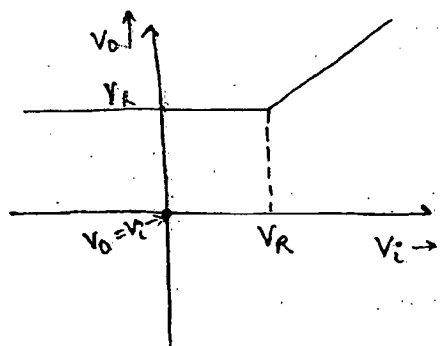


CASE - V :-

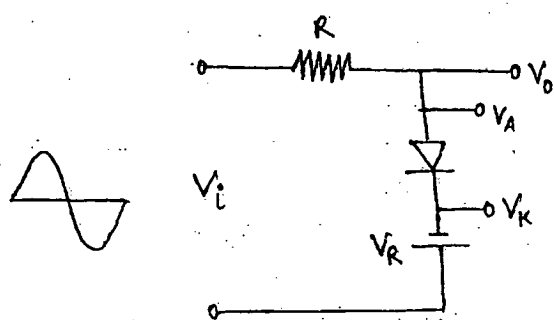


$V_i < -V_R$ Diode OFF $V_o = V_i$

$V_i > -V_R$ Diode ON $V_o = -V_R$

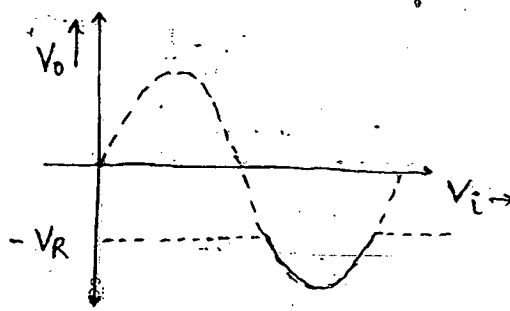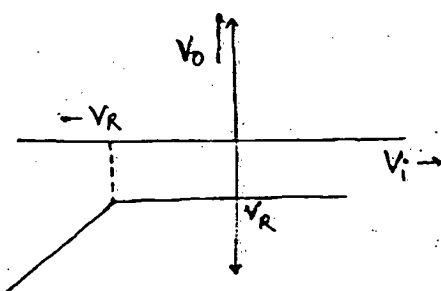


CASE - VI :-

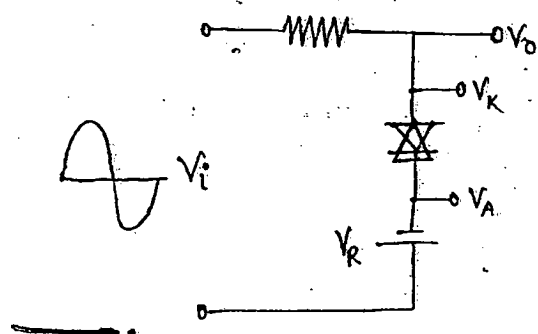

$V_i < -V_R$ Diode ON $V_o = -V_R$

$V_i > -V_R$ Diode OFF $V_o = V_i$

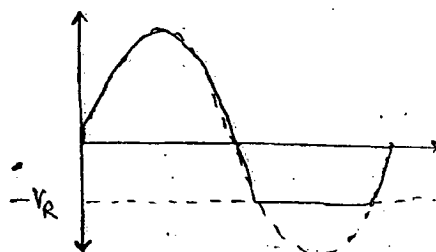


→ TECHNIQUES IN SHUNT CLIPPERS

When the diode is in downward direction the signal will be transmitted below the reference voltage.

When the diode is in upward direction the signal will be transmitted above the reference voltage.

② SERIES CLIPPER


Case I :-

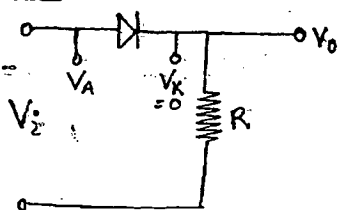


Conditions :-

$$V_i < 0 \quad \text{Diode OFF} \quad V_o = 0$$

$$V_i > 0 \quad \text{Diode ON} \quad V_o = V_i$$

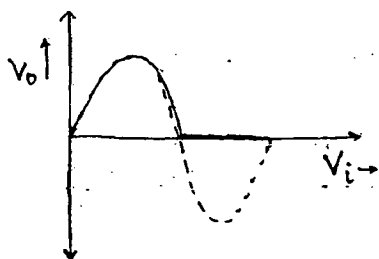

Case II :-

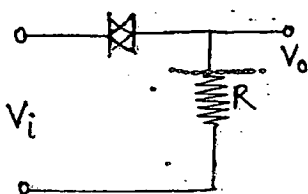

Conditions :-

$$V_i < 0 \quad \text{Diode ON} \quad V_o = V_i$$

$$V_i > 0 \quad \text{Diode OFF} \quad V_o = 0$$


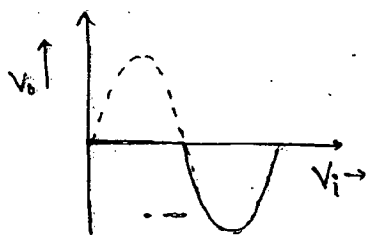



Fig:- O/p CHARACTERISTICS.

Case III :-

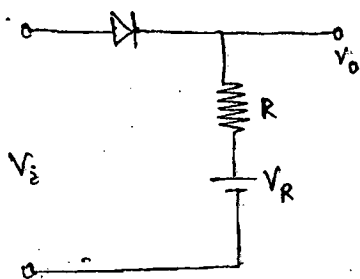


$$V_i < V_R \quad \text{Diode OFF} \quad V_o = V_R$$

$$V_i > V_R \quad \text{Diode ON} \quad V_o = V_i$$

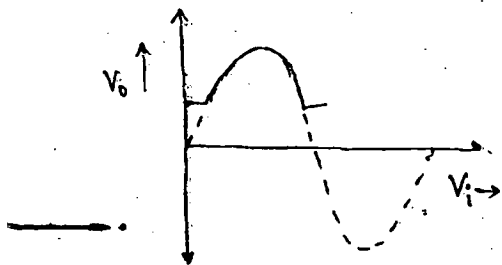


Case IV :-

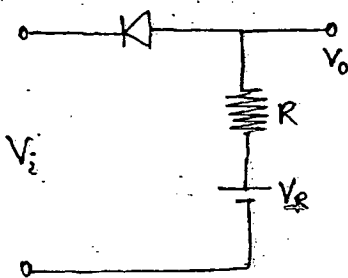


$$V_i < V_R \quad \text{Diode ON} \quad V_o = V_i$$

$$V_i > V_R \quad \text{Diode OFF} \quad V_o = V_R$$

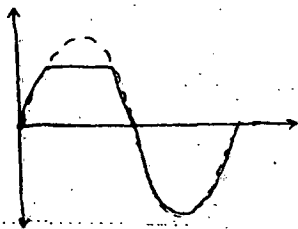


Case V :-

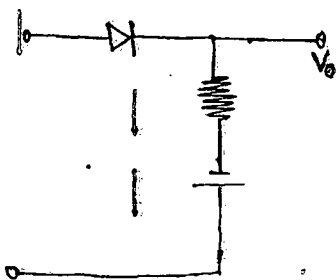


$$V_i < -V_R \quad \text{Diode OFF} \quad V_o = -V_R$$

$$V_i > -V_R \quad \text{Diode ON} \quad V_o = V_i$$

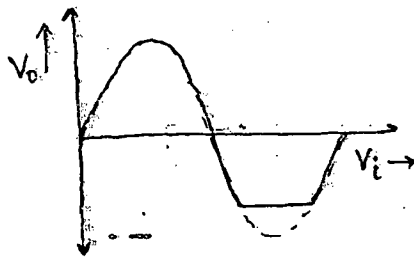


CASE VI :-

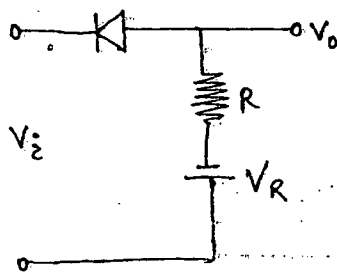

conditions :-

$V_i < -V_R$ Diode ON $V_o = V_i$

$V_i > -V_R$ Diode OFF $V_o = -V_R$

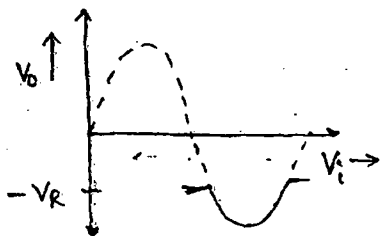


→ TECHNIQUES IN SERIES CLIPPERS.

When the diode is in forward direction to i/p s/g the s/g will be transmitted above the reference voltage

When the diode in reverse direction to the i/p s/g the s/g will be transmitted below the reference voltage

□ OUTPUT FOLLOWING INPUT DESIGN.

Case I :-

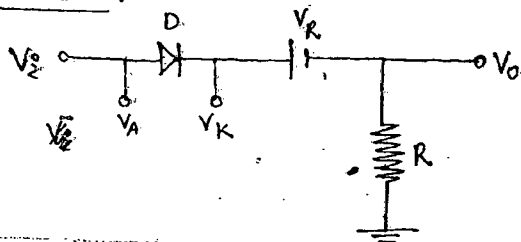

$V_i < V_R$ Diode OFF $V_o = 0$

$V_i > V_R$ Diode ON $V_o = V_i - V_R$

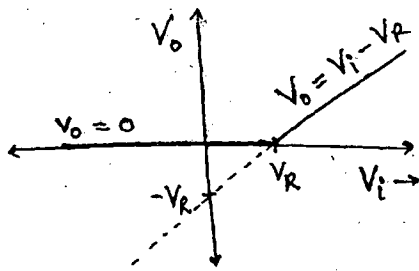


Fig:- TRANSFER STATE


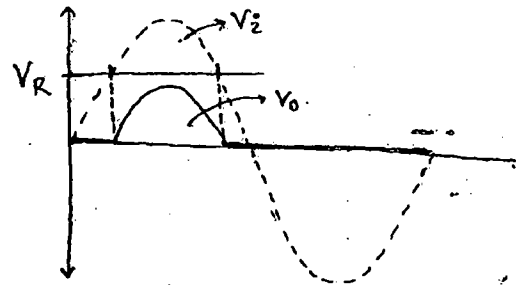


Fig:- O/P CHARACTERISTICS

Case II :-

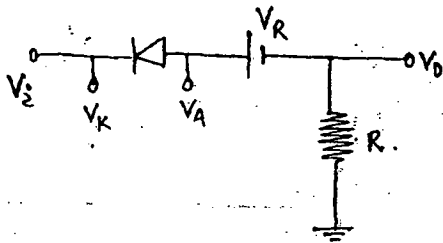

condition:-

$V_i < V_R$ Diode ON $V_o = V_i - V_R$

$V_i > V_R$ Diode OFF $V_o = 0$

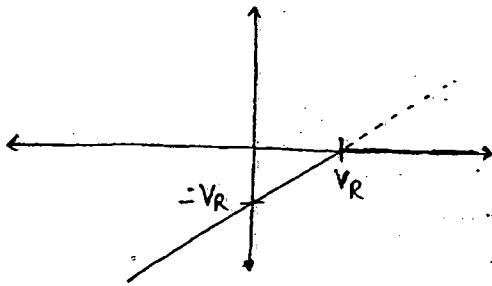


Fig:- TRANSFER STATE


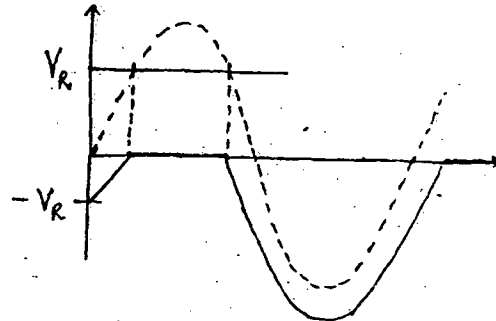


Fig:- O/P CHARACTERISTICS



Case III :-

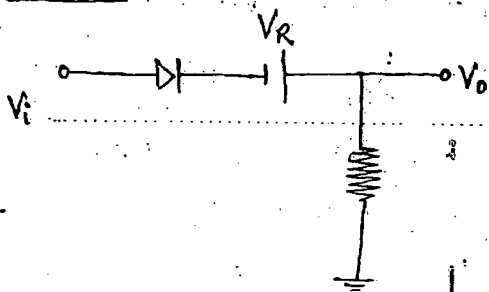


condition:-

$V_i < -V_R$ Diode OFF $V_o = 0$

$V_i > -V_R$ Diode ON $V_o = V_i + V_R$

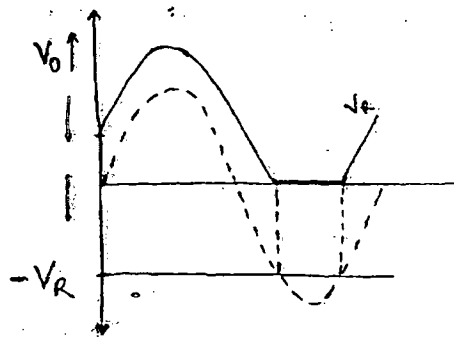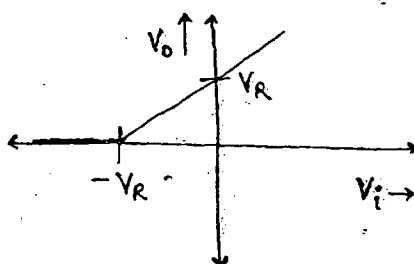



CASE-IV :-

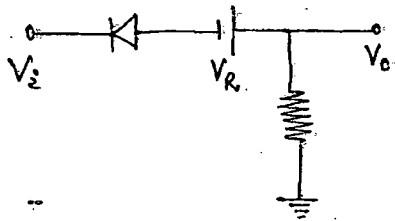

conditions :-


$$V_i < -V_R \text{ Diode ON } V_o = V_i + V_R$$
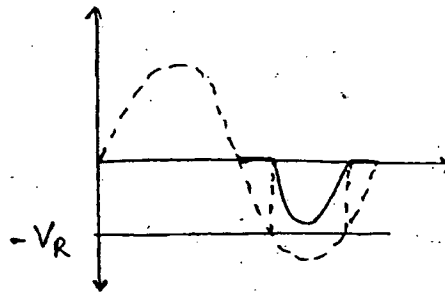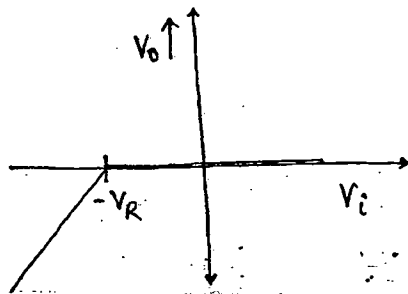
$$V_i > -V_R \text{ Diode OFF } V_o = 0$$





□ APPLICATIONS

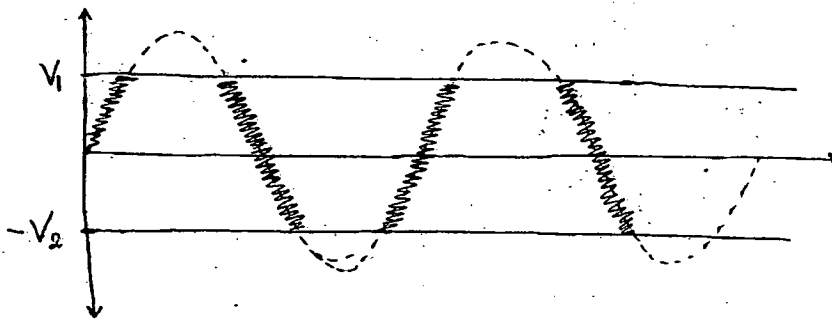Q:- Design a noise eliminator ckt with the given i/p.



Soln :-

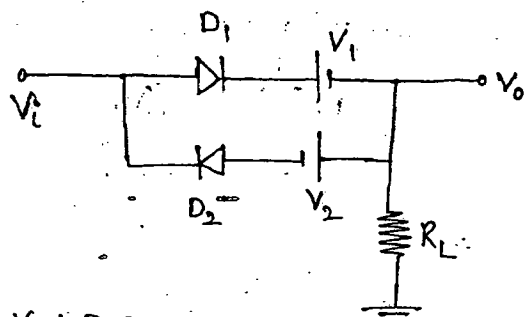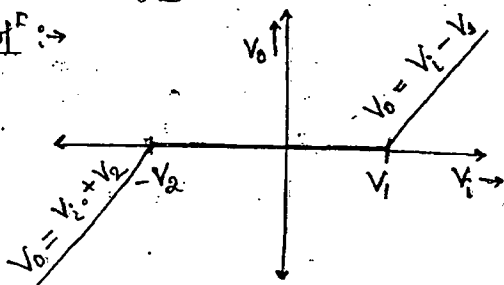


$$V_i < -V_2; D_1 \text{ OFF}, D_2 \text{ ON}; V_o = V_i + V_2$$



$$-V_2 < V_i < V_1; D_1 \text{ OFF}, D_2 \text{ OFF}; V_o = 0$$

$$V_i > V_1; D_1 \text{ ON}; D_2 \text{ OFF}; V_o = V_i - V_1$$

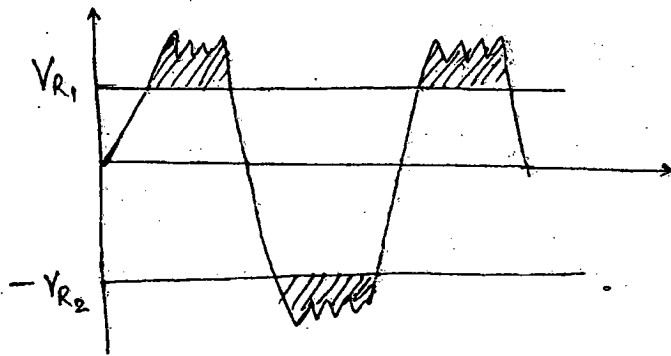Two INDEPENDENT LEVEL CLIPPING : $V_{R1}(D_1) > V_{R2}(D_2)$
Question : $\rightarrow$ Design a noise eliminator CRT with the given i/p.



Solⁿ : $\rightarrow$

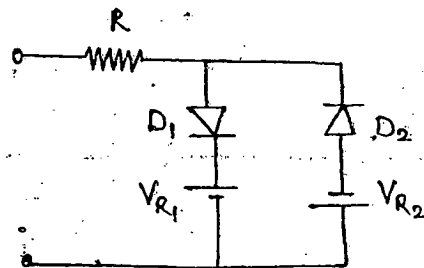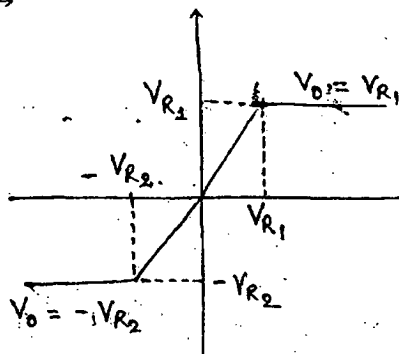


$V_i < -V_{R2}$; D_1 OFF, D_2 ON ; $V_o = -V_{R2}$

$-V_{R2} < V_i < V_{R1}$; D_1 OFF, D_2 OFF ; $V_o = V_i$

$V_i > V_{R1}$; D_1 ON, D_2 OFF ; $V_o = V_{R1}$

NOTE : $\rightarrow$

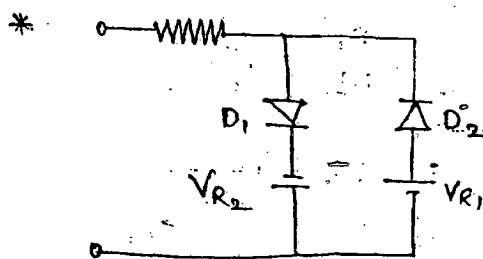




$V_{R2}(D_1) < V_{R1}(D_2)$

NOT VALID


X

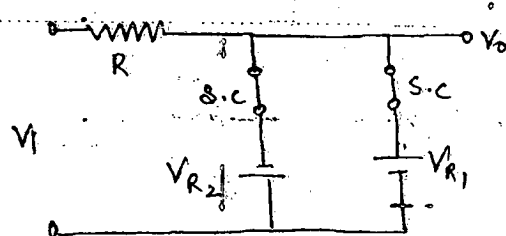$-V_{R2} < V_i < V_{R1}$, D_1 ON , D_2 ON



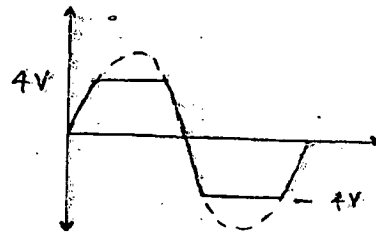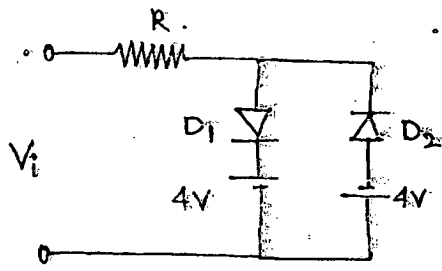



$$V_{R1} > V_{R2}$$

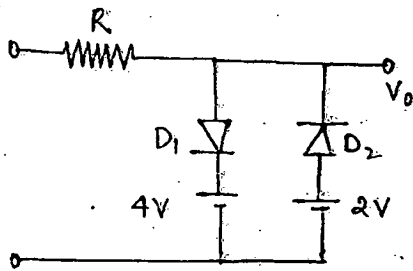

$$4V > 2V$$




$$V_{R1} > V_{R2}$$

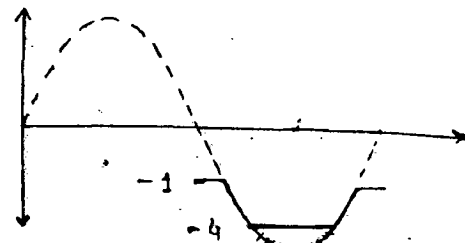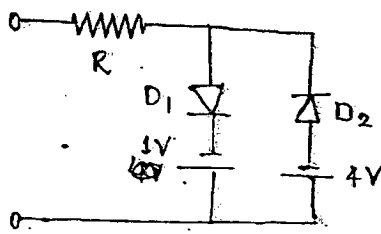

$$V_{R1} > V_{R2}$$



□ ATTENUATOR.

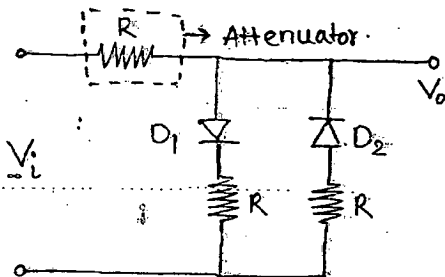





conditions :

$$V_i < 0 ; D_1 \text{ OFF } , D_2 \text{ ON } ; V_o = \frac{V_i}{2}$$
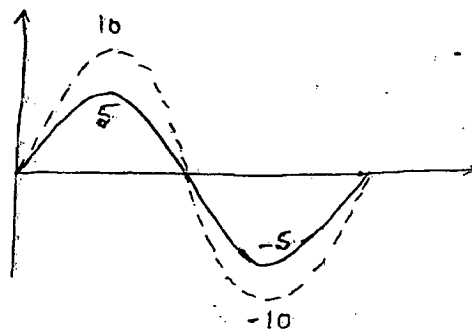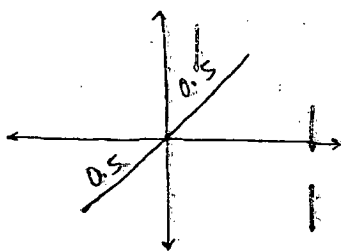
$$V_i > 0 ; D_1 \text{ ON } , D_2 \text{ OFF } ; V_o = \frac{V_i}{2}$$




□ SINGLE BRANCH DESIGN.

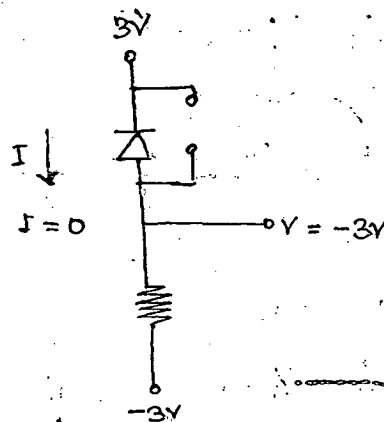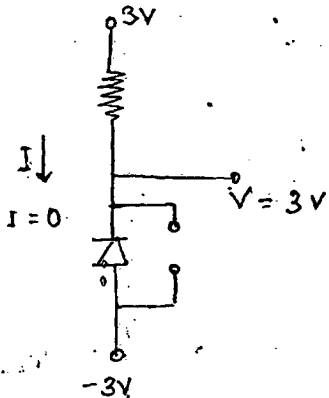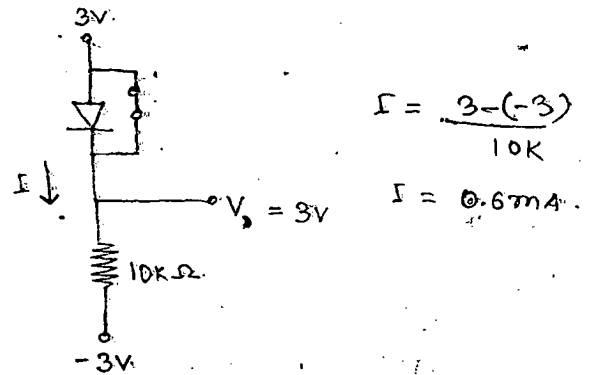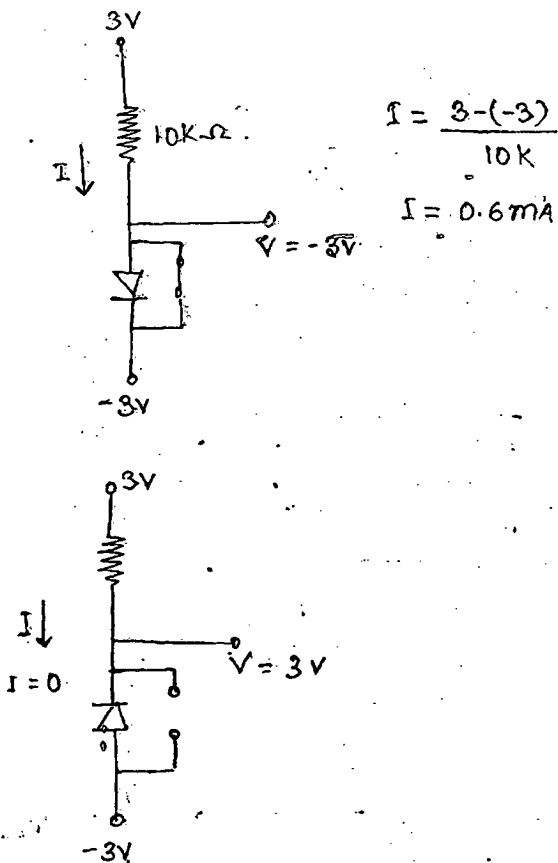


CONCLUSION :-

In any single branch circuit current will be same but voltage may be different.


□ MULTI BRANCH DESIGN.

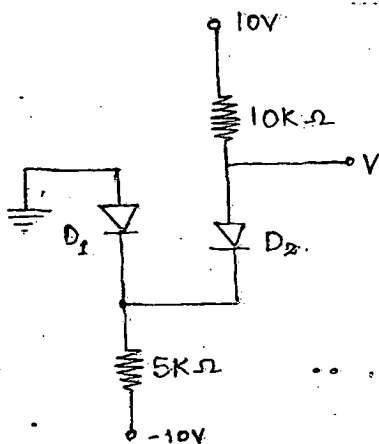

STEP-1:- Assume D_1 OFF, D_2 ON.

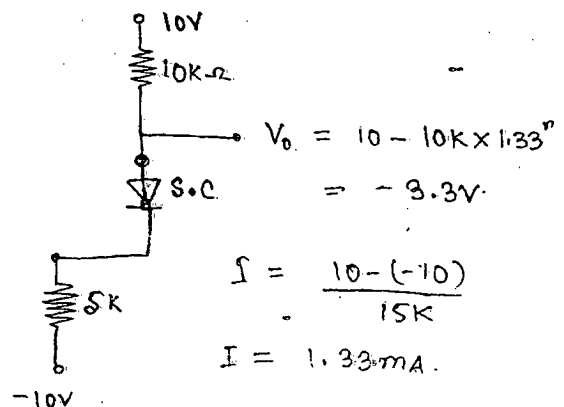


Step 2 :- Connect D_1 .

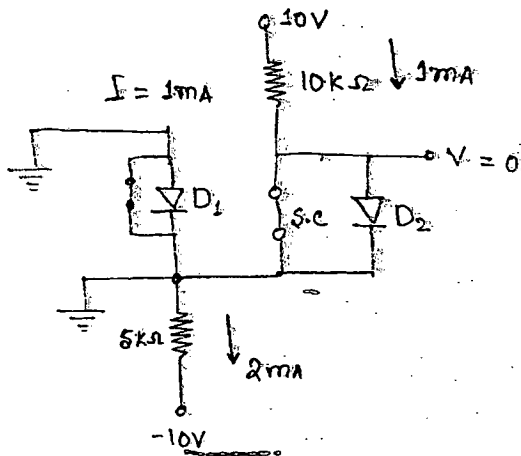

Ch-9

Q1 :-

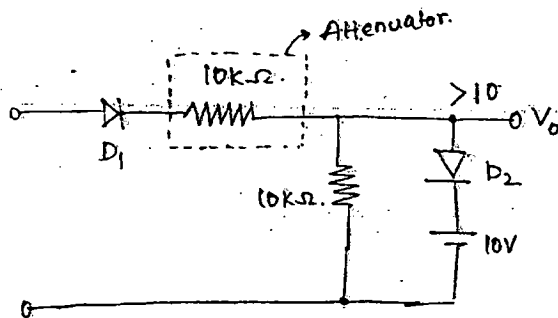

$V_i < 0 \Rightarrow D_1 \text{ OFF}, D_2 \text{ OFF}; V_o = 0$

$0 < V_i < 20; D_1 \text{ ON}, D_2 \text{ OFF}; V_o = \frac{V_i}{2}$

$V_i > 20; D_1 \text{ ON}, D_2 \text{ ON}; V_o = 10$

* Identify the Reference

Here $\rightarrow$ 2nd Reference

* Identify Slope is present or not.


Here $\rightarrow$ yes.

1st Reference = 0 $\rightarrow$ For D_1

2nd " = 10V $\rightarrow$ For D_2

$\therefore$ (C) Ans

Q7

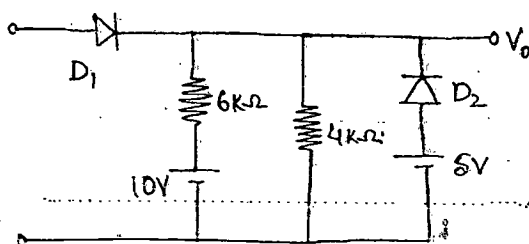


Reference for $D_1 = 10 \text{ & } 0$.

Reference for $D_2 = 5V$



Solve by multiple Branch:

Case :- Assume D_1 and D_2 OFF

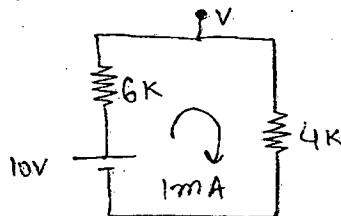


$V = 4k$

Case 2 :-

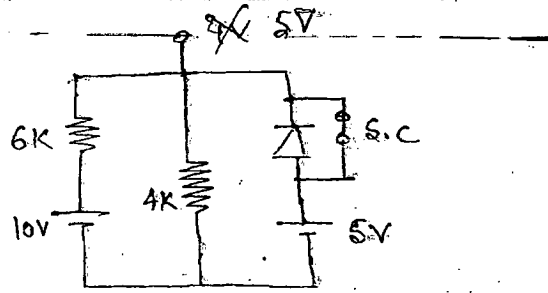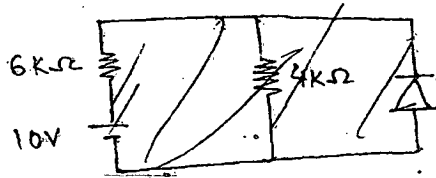


Case 3 :-

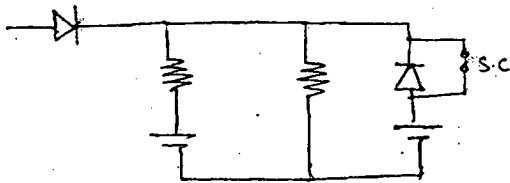


$V_i < 5V$ D_1 OFF D_2 ON $V_o = 5V$


$V_i > 5V$ D_1 ON D_2 OFF $V_o = V_i$

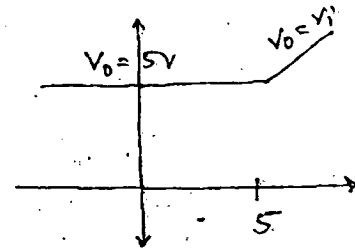


Q11.

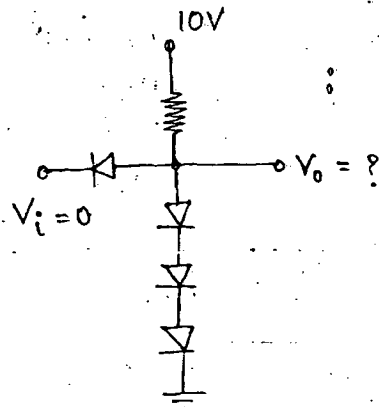

$\Rightarrow$

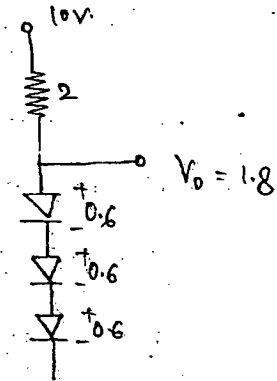

$\therefore (a)$

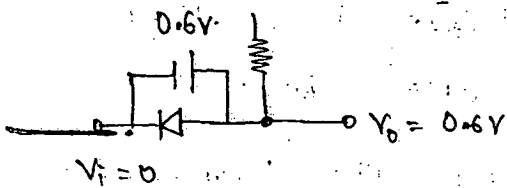

Q 13, 14, 15, 8, 12.