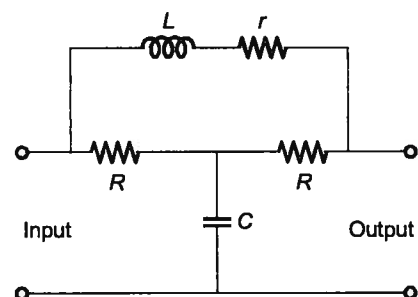





Multiple Choice Questions

Q.1 The circuit shown in the figure below is a



- (a) low pass filter (b) high pass filter
(c) band pass filter (d) band stop filter
[ESE-2000]

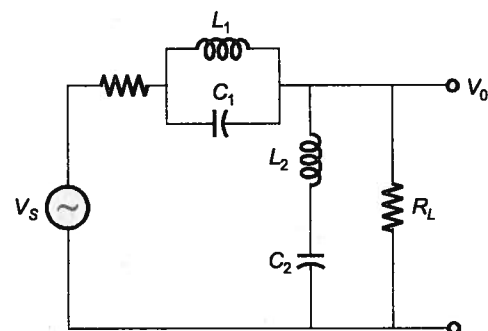Q.2 The circuit of the figure represents a




- (a) low pass filter (b) high pass filter
(c) band pass filter (d) band reject filter
[GATE-2000]

Q.3 If the numerator of a second-order transfer function $F(s)$ is a constant, then the filter is a

[ESE-2001]

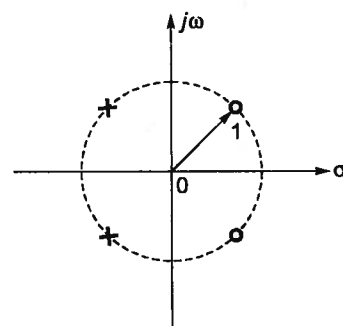Q.4 The pole-zero pattern shown in the given figure is for



- (a) a low-pass filter (b) a high-pass filter
(c) an all-pass filter (d) a band-pass filter
[ESE-2001]

Q.5 The transfer function


$$\frac{V_2(s)}{V_1(s)} = \frac{10s}{s^2 + 10s + 100}$$

- (a) low pass filter (b) band pass filter
(c) high pass filter (d) all pass filter
[ESE-2001]

Q.6 Which one of the following is the transfer function of an electrical lowpass filter using R and C elements?

- (a) $\frac{RCs}{1+RCs}$ (b) $\frac{1}{1+RCs}$
(c) $\frac{RC}{1+RCs}$ (d) $\frac{s}{1+RCs}$
[ESE-2004]


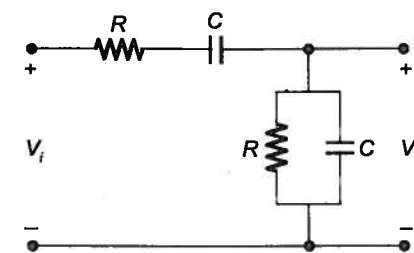
Q.7 The RC circuit shown in the figure is



- (a) a low-pass filter
(b) a high-pass filter
(c) a band-pass filter
(d) a band-reject filter
[GATE-2007]

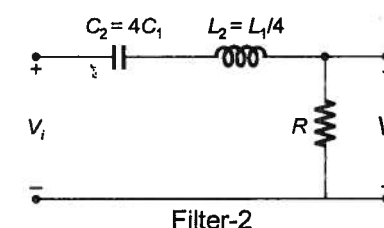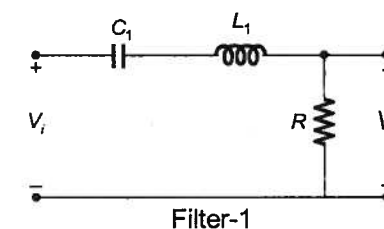
Q.8 Two series resonant filters are as shown in the figure. Let the 3-dB bandwidth of Filter 1 be B_1

and that of Filter 2 be B_2 . The value of $\frac{B_1}{B_2}$ is



- (a) 4 (b) 1
(c) 1/2 (d) 1/4
[GATE-2007]

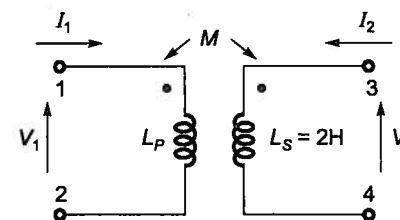
Q.9 In the transformer shown in the figure below, the inductance measured across the terminal 1 and 2 was 4 H with open terminals 3 and 4. It was 3 H when the terminal 3 and 4 were short circuited. The coefficient of coupling would be



- (a) 1
(b) 0.707
(c) 0.5
(d) indeterminate due to insufficient data
[ESE-2000]

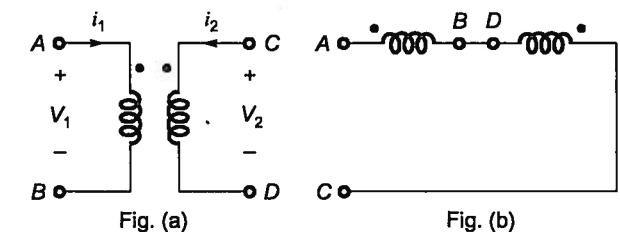Q.10 The inductance matrix of a system of two mutually coupled inductors shown in figure 1 is


$$\text{given by } L = \begin{bmatrix} 5 & +4 \\ +4 & 7 \end{bmatrix}$$



When the inductors are connected as shown in figure 2, the equivalent inductance of the system is given by


- (a) 20 H (b) 4 H
(c) 16 H (d) 8 H
[ESE-2002]

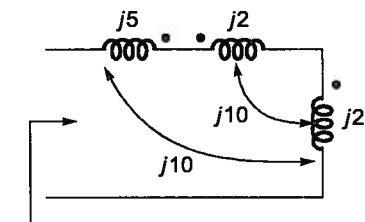Q.11 Impedance Z as shown in the given figure is



- (a) $j29 \Omega$ (b) $j9 \Omega$
(c) $j19 \Omega$ (d) $j39 \Omega$
[GATE-2005]

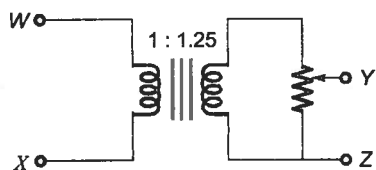Q.12 The following arrangement consists of an ideal transformer and an attenuator which attenuates by a factor of 0.8. An ac voltage $V_{WX1} = 100 \text{ V}$ is applied across WX to get an open circuit voltage V_{YZ1} across YZ . Next, an ac voltage $V_{YZ2} = 100 \text{ V}$ is applied across YZ to get an open circuit voltage V_{WX2} across WX . Then, V_{YZ1}/V_{WX1} , V_{WX2}/V_{YZ2} are respectively,




- (a) 125/100 and 80/100
 (b) 100/100 and 80/100
 (c) 100/100 and 100/100
 (d) 80/100 and 80/100

[GATE-2013]




T1. The circuit given below will act

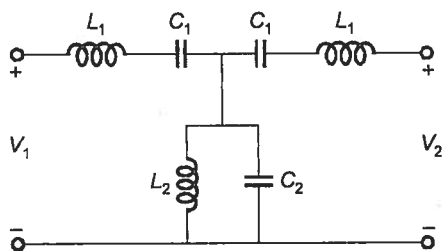

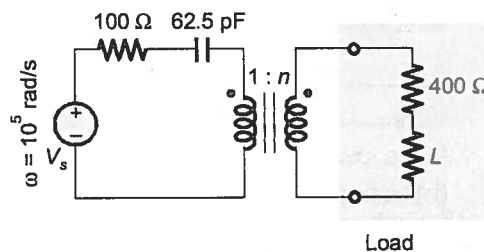- (a) Low pass filter (b) High pass filter
 (c) Band pass filter (d) Band stop filter

T2. In the circuit below, the load consists of a $400\ \Omega$ resistor and an inductor. For what value of n and L , the power transferred to the load will be maximum?



- (a) $n = 4, L = 3.2\ \text{H}$
 (b) $n = 0.5, L = 1.6\ \text{H}$
 (c) $n = 2, L = 6.4\ \text{H}$
 (d) $n = 2, L = 4.8\ \text{H}$

