
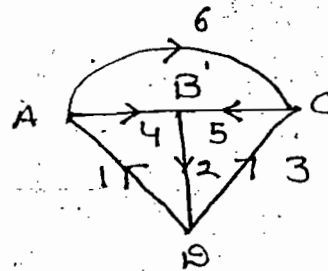


Graph Theory:-

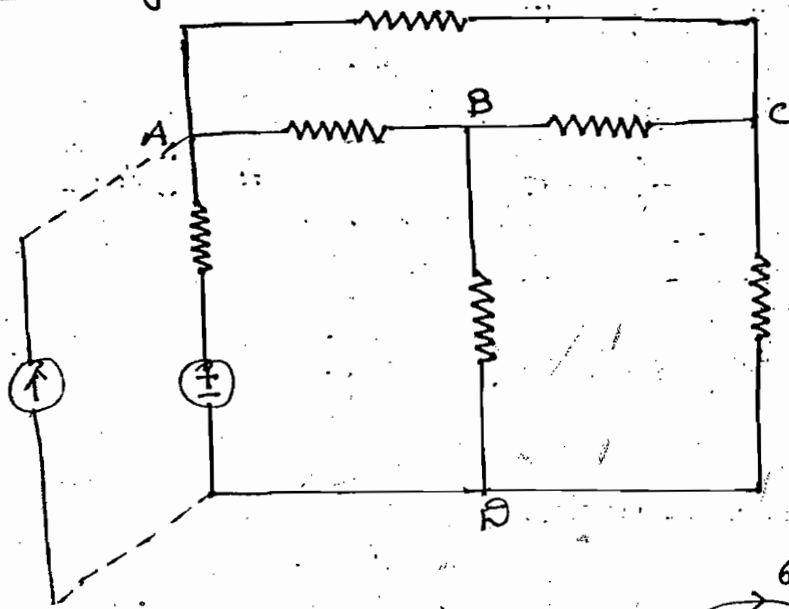

→ N/w topology is the study of the N/w properties by investigating interconnection b/w branches and nodes, it mainly concentrate on the geometry of the N/w

→ In the N/w topology any N/w is replace by graph. To develop graph of each element is replace by either straight line or arc of the semi-circle, voltage source is replace by s.c and current source is replace by o.c and graph retains all the nodes of original N/w

→

No. of branches of N/w $\geq$ No. of branch of graph.

Augmented Incidence Matrix :-

	1	2	3	4	5	6
A	-1			+1		+1
B		+1		-1	-1	
C			-1		+1	-1
D	+1	-1	+1			

$= [A_a]$

Reduced Incidence Matrix :-

	1	2	3	4	5	6
A	-1			+1		+1
B		+1		-1	-1	
C			-1		+1	-1
D	X	X	X	X	X	X

$= [A]$


D $\rightarrow$ Ref - Node or Datum Node


$\rightarrow$ All the information regarding the graph can be represent mathematically in concise form is called as Augmented incidence matrix

$\rightarrow$ For a given graph Augmented incidence matrix is unique

Tree :-

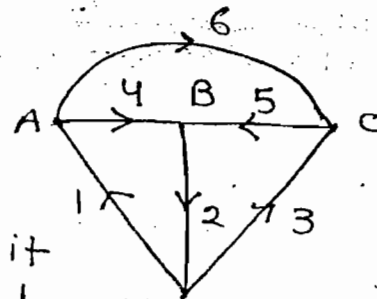$\rightarrow$ Tree is a connected sub-graph. It connects the all the nodes of the N/w but it doesn't consist of any closed path



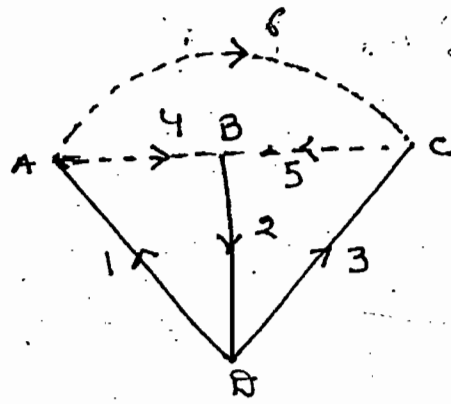

Tree $\{1, 2, 3\}$

$$\begin{aligned}\text{Total Tree Branches} &= N-1 \\ &= 4-1 = 3\end{aligned}$$

→ The set of branches which are disconnected to form a tree is called as co-tree or complementary tree

Co-Tree $\{4, 5, 6\}$

→ The branch which form a tree is called as tree branch (Twig)

→ Total no. of tree branches $= N-1$

→ The branch which is disconnected to form a tree is called as link (chord)

→ Total no. of links $(L) = b - (N-1)$

N/w where $b =$ total No. of branches of the

→ Tree is not unique

$$\text{Total no. of tree} = N^{N-2} = 4^{4-2} = 16$$


→ Total No. of possible tree $= N^{N-2}$

Note:-

→ The above formula can be applied

(a) When connection is present b/w all the node

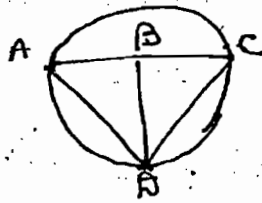(b) When no repeated branch is present b/w the node




where $A =$ Reduced incidence matrix


Total no. of node pair Voltages = $\frac{N(N-1)}{2}$

Edges = Branches

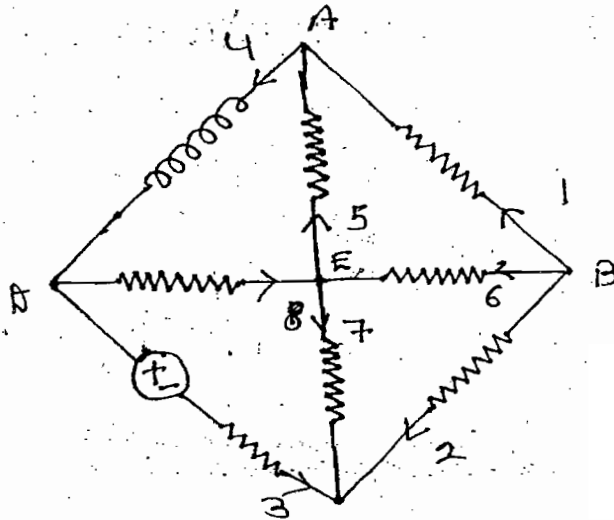ans:- Develop Tie-set matrix of the N/w shown




Develop the graph for the given N/w

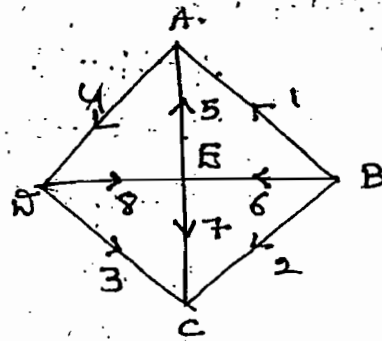

Step-(II):-

Develop a tree for the graph

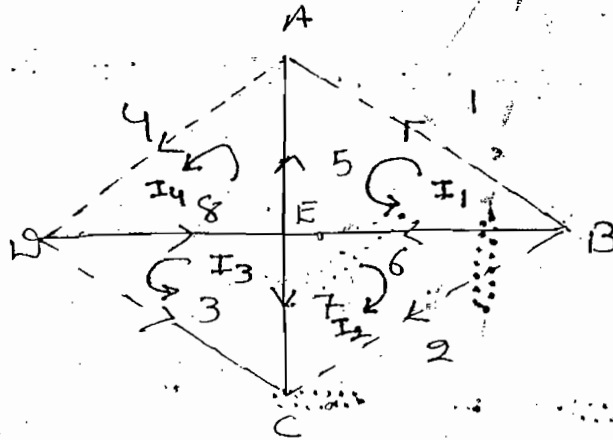

Step-(III):-

Identify total no. of basic loop / fundamental loop (f-loop) or independent loops

→ Basic loop should consist of only one link

→ Total no. of basic loop = total no. of links

i.e. $l = b - (N - 1)$

→ Basic loop direction is same as link current

direction	V_1	V_2	V_3	V_4	V_5	V_6	V_7	V_8
	1	2	3	4	5	6	7	8
I_1	+1			-	-1	-1		
I_2		+1				-1	-1	
I_3			+1				-1	-1
I_4				+1	+1			+1

= [C]

KVL Equations:-

$$V_1 - V_5 - V_6 = 0$$


$$V_2 - V_6 - V_7 = 0$$

$$V_3 - V_7 - V_8 = 0$$

$$V_4 + V_5 + V_8 = 0$$


$$[C] = [U : C_b]$$

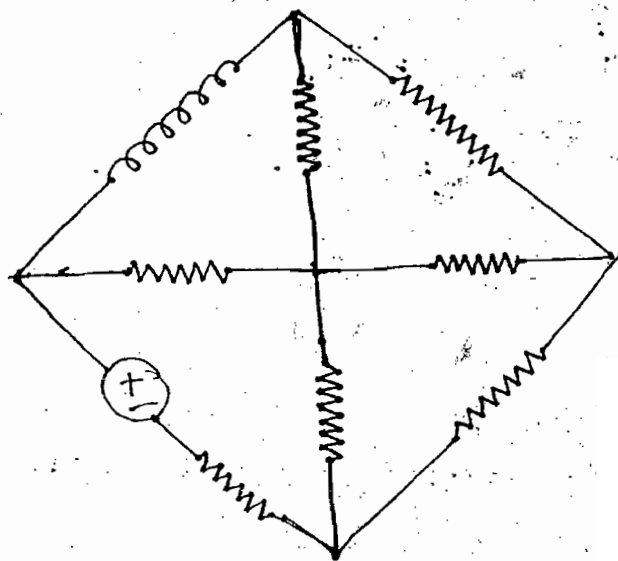ques:- Develop cut-set matrix of the N/w shown




Step-(i):-

Develop a graph for the given N/w

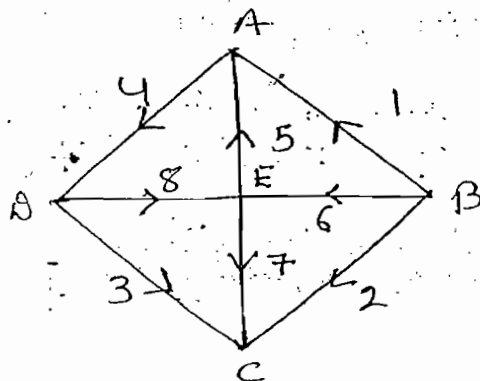

Step-(ii):-

Develop a tree for a graph

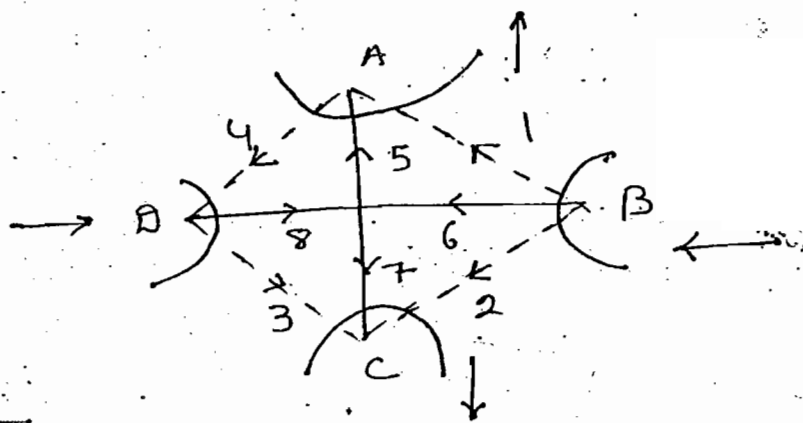

Step-(III):-

Identify total no. of basic cut-sets or fundamental cut-sets / f-cut-sets

→ Basic cut-sets should consist of only one tree branch

→ Total No. of basic cut-sets = total No. of tree branches

$$I \cdot C = N - 1$$

→ Basic cut-set direction as same as a tree branch current direction

	I_1	I_2	I_3	I_4	I_5	I_6	I_7	I_8
	1	2	3	4	5	6	7	8
A	+1			-1	+1			
B	+1	+1				+1		
C		+1	+1				+1	
D			+1	-1				+1

= [B]

KCL Equations:-

$$I_1 - I_4 + I_5 = 0$$

$$I_1 + I_2 + I_6 = 0$$

$$I_2 + I_3 + I_7 = 0$$

$$I_3 - I_4 + I_8 = 0$$

$$[B] = [B_q \quad U]$$

$$[C] = [U : C_b]$$



Tie-set


$$[B] = [B_d : U]$$



cut-set

$$\begin{aligned} [C_b] &= -[B_d]^T \\ [B_d] &= -[C_b]^T \end{aligned}$$

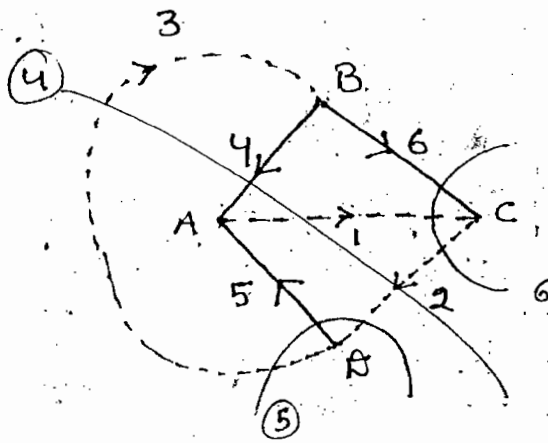ques:- Develop cut-set matrix of the graph shown



Soln:-


**

	1	2	3	4	5	6
4	-1	+1	-1	+1	..	
5		-1	+1		+1	
6	+1	-1				+1

ques:- Identify total no. of cut-sets of the graph shown

(a) 3 (b) 4

(c) 5 (d) 6

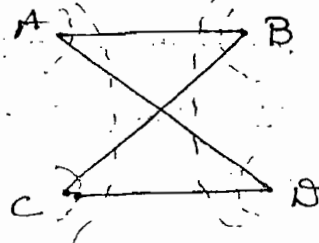



Note:-

- cut-sets may consist of one tree branch or more than one tree branch
- Basic cut-sets consist of only one tree branch

Conclusion:-

- Total no. of possible tree = N^{N-2}
- Tie-set matrix is not unique, total no. of possible tie-set matrix = N^{N-2}
- cut-set matrix is not unique, Total no. of possible cut-set matrix = N^{N-2}
- Rank of Tie-set matrix = total no. of links
i.e. $d = b - (N - 1)$
- Rank of cut-set matrix = total no. of tree branches
 $= N - 1$
- Rank of Incidence Matrix = $N - 1$

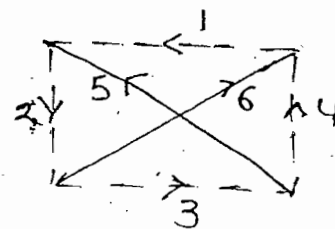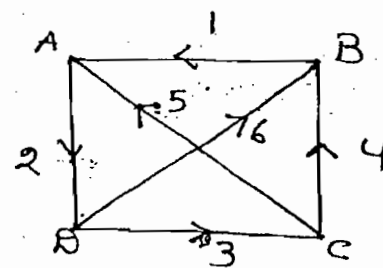- The given figure is invalid tree. Since no connection is present b/w tree branches



Quality:-

- R $\longleftrightarrow$ G
- L $\longleftrightarrow$ C
- V $\longleftrightarrow$ I
- Series $\longleftrightarrow$ Parallel
- O.C $\longleftrightarrow$ S.C
- KVL $\longleftrightarrow$ KCL

loop $\longleftrightarrow$ Node
(Mesh)


Tie-set $\longleftrightarrow$ Cut-set

Thevenin's $\longleftrightarrow$ Norton's


Foster-I form $\longleftrightarrow$ Foster-II form
(Series) (Parallel)

$$\frac{dV}{dt} \longleftrightarrow \frac{dI}{dt}$$
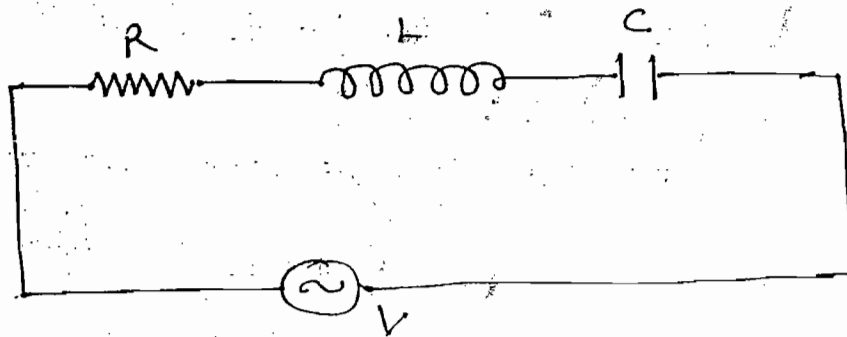
$$\int V dt \longleftrightarrow \int I dt$$



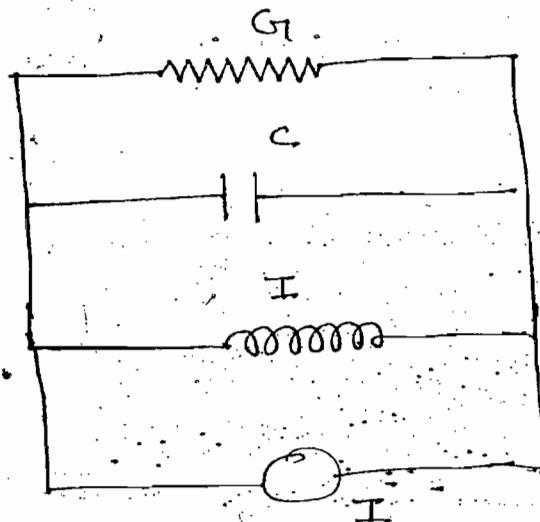
$$V = iR + L \frac{di}{dt} + \frac{1}{C} \int i dt \rightarrow \text{KVL}$$




$$I = VG + C \frac{dV}{dt} + \frac{1}{L} \int V dt \rightarrow \text{KCL}$$

Quality does not mean the equivalence but it means that mathematical representation of both N/w are identical.

Ques:- Develop dual of the N/w shown

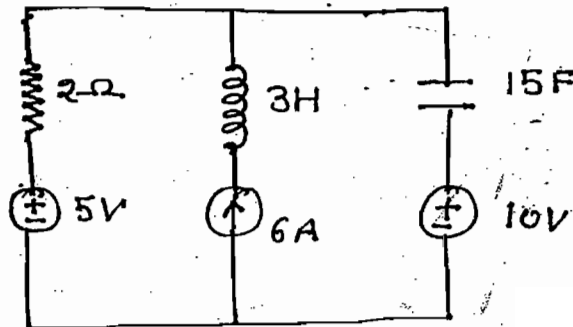

Soln:-

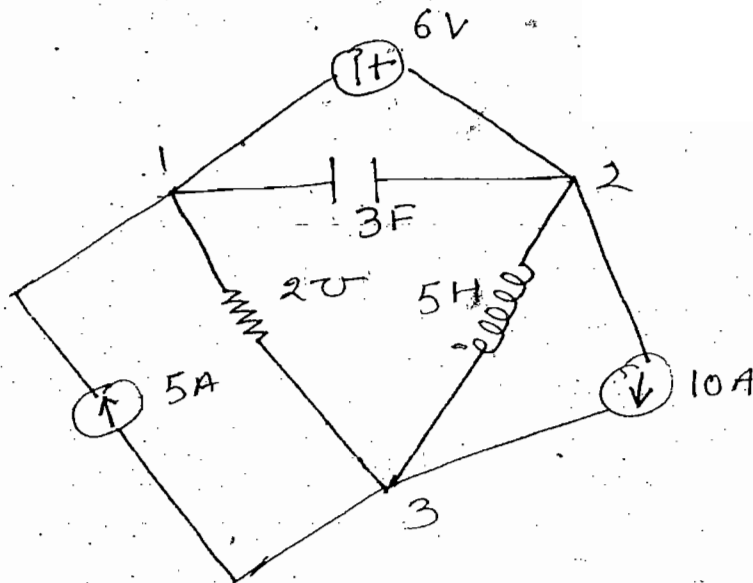

Note:-

- When voltage source circulate a current in clockwise direction arrow mark of the current source is indicated towards respective node
- When current source circulate a current in clockwise direction the sign is assign to respective node