

ELECTROSTATIC  $\mathbf{F} = \mathbf{\theta}\mathbf{E} = \mathbf{\sigma}\mathbf{A}(\mathbf{\sigma})$  $\overline{\mathbf{A}} \left( \overline{\mathbf{2}_{\mathcal{E}}} \right)$ 

## KIRCHOFF'S LAW OF CAPACITOR'S

FIRST LAW: This law is basically law of conservation of charge which states that the sum of incoming charges at a function in Equal to the sum of outgoing charges

$$\boldsymbol{q}_{_{-}} = \boldsymbol{q}_{_{1}} + \boldsymbol{q}_{_{2}} = \boldsymbol{q}_{_{3}} + \boldsymbol{q}_{_{3}}$$

SECOND LAW: IN a closed loop, the Summation of all the Potential differences must be zero.



## COMBINATION OF CAPACITOR'S ·Serief Equivalent of Capacitor's $C_2$ IN Serief— $\theta = C_1 V_1 = C_2 V_2$ $\overline{V_2}$ $\cdots$ $I_{-}$ $I_{-}$ $I_{-}$

$$\frac{\mathbf{l}}{\mathbf{C}_{equi}} = \frac{\mathbf{l}}{\mathbf{C}_{1}} + \frac{\mathbf{l}}{\mathbf{C}_{2}}$$

$$\frac{1}{C_{equi}} = \frac{1}{C_1} + \frac{1}{C_2}$$

$$\mathbf{V} = \mathbf{V}_1 = \mathbf{V}_1$$

$$\mathcal{C}_{\epsilon = 0_1 + 0_2}$$
  
 $\mathcal{C}_{\epsilon = 0_1 + C_2$ 

let Equivalent of **rallel** 
$$- \mathbf{V} = \mathbf{V}_1$$

$$m_{iv} = C_1 + C_2$$

# CAPACITOR WITH DIELEATRIC

· Capacitance of capacitor having dielectric constant (k) and (t<d):

$$C = \frac{A\varepsilon_0}{dd - t + \frac{t}{k}} \quad \begin{array}{l} t = thickness \\ k = \text{Dieletric} \\ \text{Constant} \end{array}$$



Κ

┥┥┥┽

┥┥┥┽

 $Q_1$ +

 Capacitance of Capacitor having diebctric constant (K) and (t = d):

$$C = \frac{A\varepsilon_0}{d - d + \frac{d}{k}} = \frac{kA\varepsilon_0}{d} = kC_0$$