


7

Small Signal Analysis of FET



Multiple Choice Questions

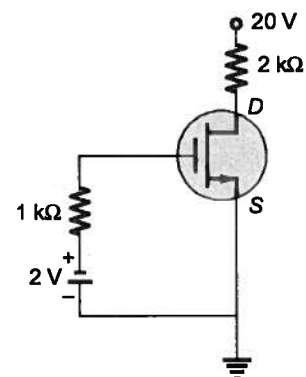
Q.1 The value of V_{GS} and V_G for the circuit shown in figure is



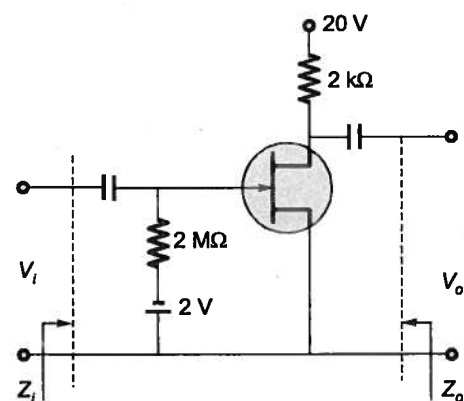- (a) $-2\text{ V}, -2\text{ V}$ (b) $2\text{ V}, -2\text{ V}$
(c) $2\text{ V}, -2\text{ V}$ (d) $-2\text{ V}, 2\text{ V}$

Common Data Questions (2 to 4):

Given: $r_d = 20\text{ k}\Omega$, $I_{DSS} = 10\text{ mA}$, $V_p = -8\text{ V}$



Q.2 Z_i and Z_o of the circuit are respectively

- (a) $2\text{ M}\Omega$ and $2\text{ k}\Omega$
(b) infinity and $2\text{ M}\Omega$
(c) $2\text{ M}\Omega$ and $20/11\text{ k}\Omega$
(d) infinity and $20/11\text{ k}\Omega$


Q.3 I_D and V_{DS} under DC conditions are respectively

- (a) 5.625 mA and 8.75 V
(b) 1.875 mA and 5 V
(c) 4.5 mA and 11 V
(d) 6.25 mA and 7.5 V

Q.4 Transconductance in milli siemens (ms) and voltage gain of the amplifier are respectively

- (a) 1.875 ms and 3.41
(b) 1.875 ms and -3.41
(c) 3.3 ms and -6
(d) 3.3 ms and 6

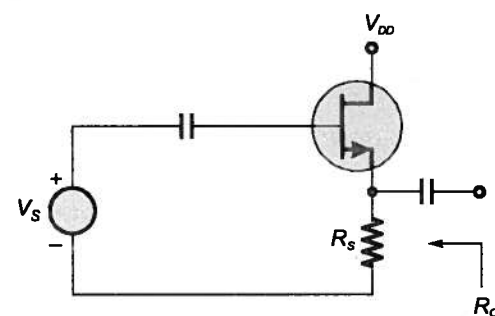Q.5 For the circuit shown below if $g_m = 3 \times 10^{-3}$ and $R_s = 3000\text{ }\Omega$, then what is the value of R_o ?




- (a) $3000\text{ }\Omega$ (b) $1000/3\text{ }\Omega$
(c) $300\text{ }\Omega$ (d) $100\text{ }\Omega$

[ESE-2006 (EE)]


Q.6 Given $g_m = 2\text{ mA/V}$; $r_d \rightarrow \infty$. The voltage gain

$$|A_v| = \left| \frac{V_o}{V_s} \right| \text{ is given by}$$

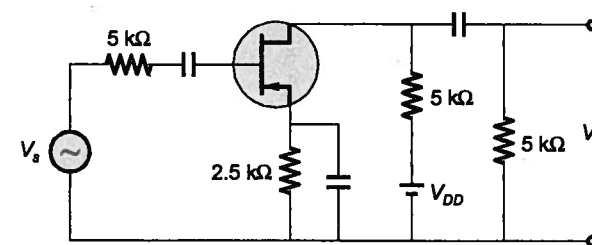


- (a) $\frac{5}{3}$ (b) 5
(c) 10 (d) $\frac{10}{3}$

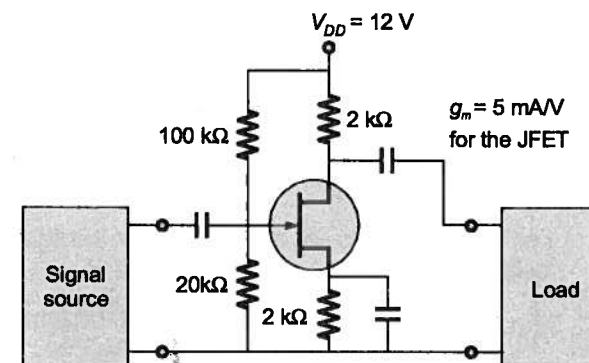Q.7 The mid-frequency input impedance of the JFET amplifier given in figure lies in the range



- (a) $100\text{--}300\text{ }\Omega$ (b) $1\text{--}3\text{ k}\Omega$
(c) $10\text{--}20\text{ k}\Omega$ (d) $100\text{--}200\text{ k}\Omega$

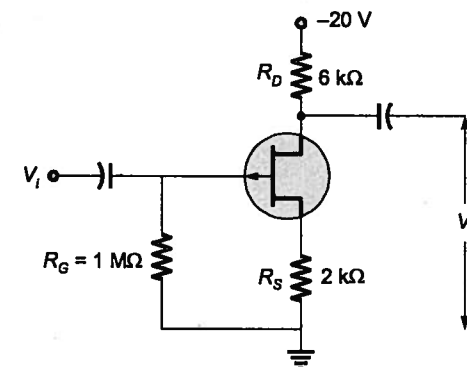Q.8 Consider a JFET amplifier shown below:





If $g_m = 4000\text{ }\mu\text{S}$ then closed loop gain of amplifier is given by

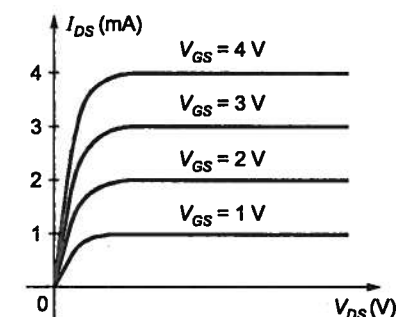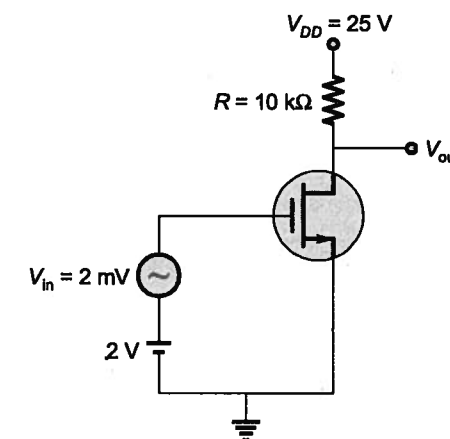- (a) 24 (b) 12
(c) 6.42 (d) 2.66

Common Data Questions (9 and 10):

Assume that that threshold voltage of the N channel MOSFET shown in figure is $+0.75\text{ V}$. The output characteristic of the MOSFET are also shown below:




Q.9 The transconductance of the MOSFET is

- (a) 0.75 ms (b) 1 ms
(c) 2 ms (d) 10 ms

Q.10 The voltage gain of the amplifier is

- (a) $+5$ (b) -7.5
(c) $+10$ (d) -10

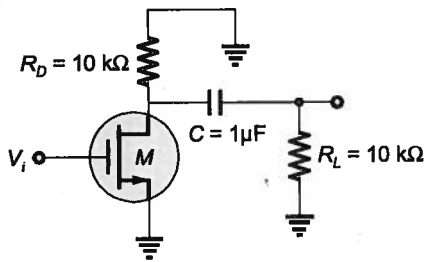Q.11 The ac schematic of an NMOS common-source stage is shown in the figure below, where part of the biasing circuits has been omitted for simplicity. For the n-channel MOSFET M, the transconductance $g_m = 1\text{ mA/V}$, and body effect and channel length modulation effect are to be neglected. The lower cut-off frequency in Hz of the circuit is approximately is




- (a) 8
(b) 32
(c) 50
(d) 200

[GATE-2013]

Numerical Data Type Questions

Q.12 In the figure shown below:

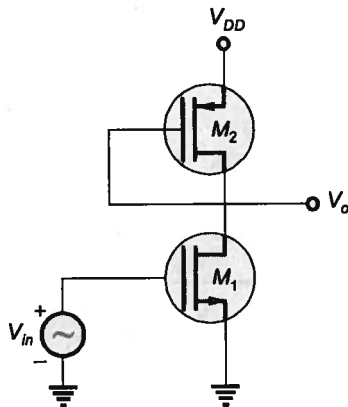


If $\mu_n = 1300 \text{ cm}^2/\text{V-sec}$; $\mu_p = 325 \text{ cm}^2/\text{V-sec}$,

then the value of the (W/L) ratio (i.e. $\frac{(W/L)_1}{(W/L)_2}$)

to make it a unity gain inverting amplifier is _____. (Assume $V_A = \infty$)

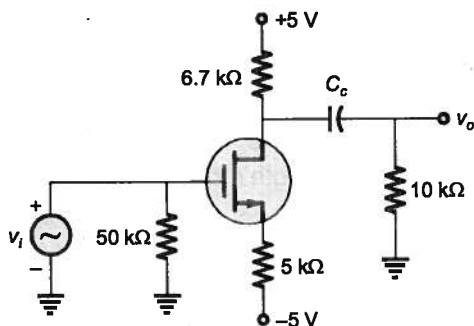
Q.13 Consider the circuit shown below. If the lower corner frequency due to coupling capacitor C_c is $f_L = 20 \text{ Hz}$, then the value of coupling capacitor C_c is ____ μF .



Q.14 Consider a circuit shown in figure below. The transistor parameters are

$$V_{TP} = -2 \text{ V}$$


$$K_p = 0.25 \text{ mA/V}^2$$

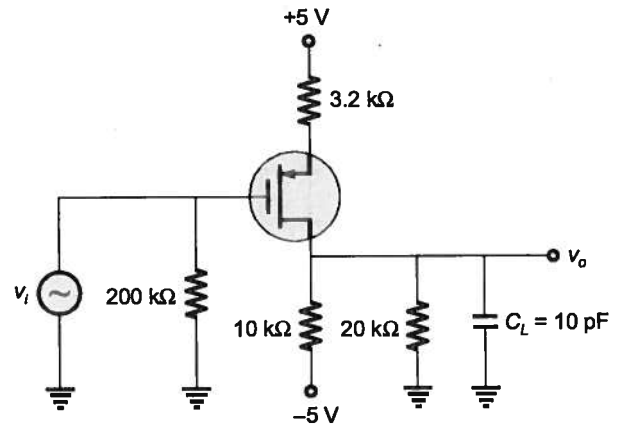

The value of 3 dB corner frequency (in MHz) due to capacitor C_L is _____.

Try Yourself

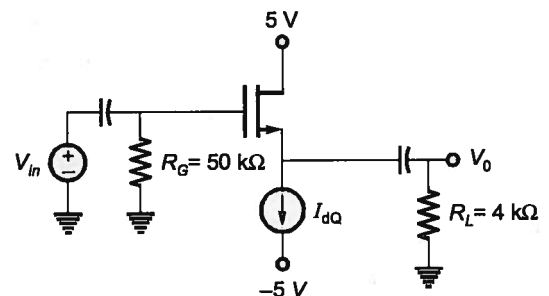T1. For the source follower circuit shown in the figure below, the transistor parameters are $V_T = 1 \text{ V}$, $\frac{1}{2} \mu_n C_{ox} = 30 \mu\text{A/V}^2$ and neglect channel length modulation. The small signal voltage gain to be $A_v = \frac{V_o}{V_i} = 0.95$. The value of $\left(\frac{W}{L}\right)$ ratio if $I_{dQ} = 4 \text{ mA}$ is



- (a) 50
(b) 47
(c) 28
(d) 36

