


CBSE Test Paper-03
Class - 12 Physics (Alternating Current)

1. Domestic power supply in India is:
 - a. 416 V 60 Hz
 - b. 110 V 60 Hz
 - c. 24 V DC
 - d. 220 V 50 Hz
2. If the current is halved in a coil then the energy stored is how much times the previous value:
 - a. $\frac{1}{2}$
 - b. $\frac{1}{4}$
 - c. 2
 - d. 4
3. If V_m and I_m are peak voltage and current, Impedance Z in an AC circuit is
 - a. $\frac{v_m}{2i_m}$
 - b. $v_m i_m$
 - c. $\frac{2v_m}{i_m}$
 - d. $\frac{v_m}{i_m}$
4. The rms current I_{rms} is related to the peak current I_o as
 - a. $I_{rms} = 0.787 I_o$
 - b. $I_{rms} = 0.9 I_o$
 - c. $I_{rms} = 0.707 I_o$
 - d. $I_{rms} = 0.5 I_o$
5. A power transmission line feeds input power at 2300 V to a step-down transformer with its primary windings having 4000 turns. Number of turns in the secondary in order to get output power at 230 V is
 - a. 325
 - b. 380
 - c. 425
 - d. 400

6. A power transmission line feeds input power at 2200V to a step-down transformer with its primary windings having 3000 turns. Find the number of turns in the secondary winding to get the power output at 220 V.
7. Is a motor starter a variable R or L?
8. The number of turns in the secondary coil of a transformer is 500 times that in primary. What power is obtained from the secondary when power fed to the primary is 10 W?
9. Mention various energy losses in a transformer.
10. An alternating voltage given by $V = 140 \sin 314t$ is connected across a pure resistor of 50Ω . Find
 - i. the frequency of the source.
 - ii. the rms current through the resistor.
11. An electric lamp having coil of negligible inductance connected in series with a capacitor and an AC source is glowing with certain brightness. How does the brightness of the lamp change on reducing the
 - i. capacitance, and
 - ii. the frequency? Justify your answer.
12. A $100\mu F$ capacitor in series with a 40Ω resistance is connected to a 110 V, 60 Hz supply.
 - a. What is the maximum current in the circuit?
 - b. What is the time lag between current maximum and voltage maximum?
13. An inductor $200\mu H$, capacitor $500\mu F$, resistor 10Ω are connected in series with a 100 V, variable frequency a.c. source.

Calculate:

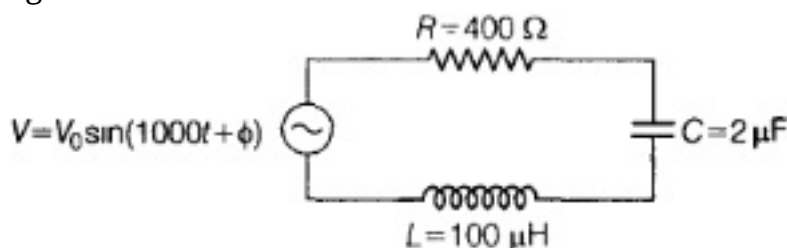- i. frequency at which the power factor of the circuit is unity
 - ii. current amplitude at this frequency
 - iii. Q-factor
14. i. Determine the value of phase difference between the current and the voltage in the given series L-C-R circuit.



-
- ii. Calculate the value of additional capacitor which may be joined suitably to the capacitor C that would make the power factor of the circuit unity.
15. A resistor of $400\ \Omega$, an inductor of $\frac{5}{\pi}$ H and a capacitor of $\frac{50}{\pi}\ \mu F$ are connected in series across a source of alternating voltage of $140 \sin 100\pi t$ V. Find the voltage (rms) across the resistor, the inductor and the capacitor. Is the algebraic sum of these voltages more than the source voltage? If yes, resolve the paradox.
(Given, $\sqrt{2} = 1.414$)..

CBSE Test Paper-03
Class - 12 Physics (Alternating Current)
Answers

1. d. 220 V 50 Hz

Explanation: In INDIA domestic power supply is at 220V and 50Hz .

2. b. $1/4$

Explanation: $E = \frac{1}{2} Li^2$

$$\frac{E_1}{E_2} = \left(\frac{i_1}{i_2} \right)^2$$

$$i_2 = \frac{i_1}{2}$$

$$\frac{E_1}{E_2} = \left(\frac{i_1}{\frac{i_1}{2}} \right)^2 = 4$$

$$E_2 = \frac{E_1}{4}$$

3. d. $\frac{v_m}{i_m}$

Explanation: Impedance refers to the overall obstruction offered by a circuit containing different components to the passage of current. Also Z has unit same as resistance.

So, drawing an analogy with the ohm's law, we get the above relation

4. c. $I_{rms} = 0.707 I_o$

Explanation: Average value of i^2 over a complete cycle is given by

$$\bar{i^2} = \frac{1}{T} \int_0^T i^2 dt$$

$$i = i_o \sin \omega t$$

$$T = \frac{2\pi}{\omega}$$

$$\bar{i^2} = \frac{\omega}{2\pi} \int_0^{2\pi/\omega} i_o^2 \sin^2 \omega t dt = \frac{\omega}{2\pi} i_o^2 \int_0^{2\pi/\omega} \frac{(1 - \cos 2\omega t)}{2} dt$$

$$\bar{i^2} = \frac{\omega}{2\pi} \frac{i_o^2}{2} \left[t - \frac{\sin 2\omega t}{2\omega} \right]_0^{2\pi/\omega} = \frac{\omega}{2\pi} \frac{i_o^2}{2} \left(\frac{2\pi}{\omega} \right)$$

$$\bar{i^2} = \frac{i_o^2}{2}$$

the root-mean-square value of the alternating current is

$$i_{rms} = \sqrt{\bar{i^2}} = \frac{i_o}{\sqrt{2}}$$

$$i_{rms} = 0.707 i_o$$

5. d. 400

Explanation: N_p = no. of turns in primary coil = 4000

N_s = no. of turns in primary coil

V_p = input voltage = 2300 V

V_s = output voltage = 230 V

$$\frac{V_s}{V_p} = \frac{N_s}{N_p}$$
$$\frac{230}{2300} = \frac{N_s}{4000}$$
$$N_s = 400$$

6. Given, input voltage (V_1) = 2200 V

Number of turns (n_1) = 3000

Output voltage (V_2) = 220 V

$$\text{As, } \frac{V_2}{V_1} = \frac{n_2}{n_1} \Rightarrow \frac{220}{2200} = \frac{n_2}{3000}$$
$$\Rightarrow n_2 = \frac{220}{2200} \times 3000$$
$$n_2 = 300$$

7. Variable R

8. If there is no loss of energy, then the output power will be 10 W.

9. For energy losses in transformer.

- Copper Losses (Winding Resistance) Core or Iron Losses
- Hysteresis Losses
- Eddy Current Losses

10. An alternating voltage given by $V = 140 \sin 315 t$, $R = 50\Omega$

Comparing it with $V = V_0 \sin \omega t$

i. Here, $\omega = 314 \text{ rad/s}$

$$\text{i.e. } 2\pi v = 314$$

$$\Rightarrow v = 314/2\pi$$

$$v = \frac{314}{2 \times 3.14}$$
$$= 50 \text{ Hz}$$

ii. As, $I_{\text{rms}} = \frac{V_{\text{rms}}}{R}$ and $V_{\text{rms}} = \frac{V_0}{\sqrt{2}}$

Here, $V_0 = 140 \text{ V}$

$$V_{\text{rms}} = \frac{140}{\sqrt{2}} \times \frac{\sqrt{2}}{\sqrt{2}} = 70\sqrt{2} \text{ V}$$

$$\therefore I_{\text{rms}} = \frac{70\sqrt{2}}{R} = \frac{70\sqrt{2}}{50} = 1.9\text{A}$$

11. When AC source is connected, the capacitor offers capacitive reactance

$$X_C = \frac{1}{\omega C} = \frac{1}{2\pi v_0 C}. \text{ The current flows in the circuit and the lamp glows.}$$

- By *reducing the capacitance*, the capacitive reactance will *increase*. So the *bulb brightness* will *decrease*.
- On reducing frequency, X_C increases so current in the circuit decrease. Therefore, the brightness of the bulb decrease.

12. Here, $C = 100\mu F = 100 \times 10^{-6} F = 10^{-4} F$, $R = 40\Omega$

$$E_v = 110\text{volt}, E_0 = \sqrt{2}, E_v = \sqrt{2} \times 110V \quad v = 60 \text{ Hz},$$

$$\omega = 2\pi v = 120\pi \text{ rad/s} \quad I_0 = ?$$

$$\text{In RC circuit as } Z = \sqrt{R^2 + X_L^2} = \sqrt{R^2 + \frac{1}{\omega^2 C^2}}$$

$$\therefore I_0 = \frac{E_0}{\sqrt{R^2 + \frac{1}{\omega^2 C^2}}} = \frac{\sqrt{2} \times 110}{\sqrt{1600 + \frac{1}{(120\pi \times 10^{-4})^2}}} \quad I_0 = 3.24 \text{ amp}$$

In RC circuit, voltage lags behind the current by phase angle ϕ

$$\text{where } \tan \phi = \frac{\frac{1}{\omega C}}{R} = \frac{1}{\omega C R} = \frac{1}{120\pi \times 10^{-4} \times 40} = 0.6628$$

$$\phi = \tan^{-1}(0.6625) = 33.5^\circ = \frac{33.5\pi}{180} \text{ rad Time lag}$$

$$= \frac{\phi}{\omega} = \frac{33.5\pi}{180 \times 120\pi} = 1.55 \times 10^{-3} \text{ sec}$$

13. i. Power factor

$$\cos \theta = \frac{R}{Z} = 1$$

$$R = Z$$

$$R = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$R^2 = R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2$$

$$\omega L = \frac{1}{\omega C}$$

$$\omega^2 = \frac{1}{LC} \text{ or } \omega = \frac{1}{\sqrt{LC}}$$

$$2\pi v = \frac{1}{\sqrt{LC}}$$

$$v = \frac{1}{2\pi\sqrt{LC}}$$

$$\omega_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$= \frac{1}{\sqrt{200 \times 10^{-6} \times 500 \times 10^{-6}}}$$


$$= 3.16 \times 10^{-3} \text{ rad s}^{-1}$$

$$\omega_0 = 3.16 \times 10^{-3} \text{ rad/s}$$

ii. The current amplitude at this frequency, $I_0 = \frac{V}{R} = \frac{100}{10} = 10A$

iii. The Q-factor, $Q = \frac{X_L}{R} = \frac{\omega_0 L}{R}$
 $= \frac{3.16 \times 10^{-3} \times 200 \times 10^{-6}}{10} = 6.32 \times 10^{-8}$

14. i.

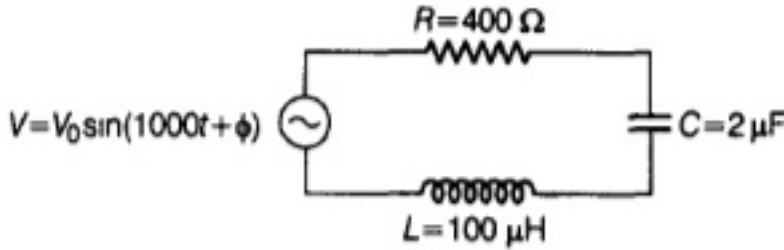

Given

$$V = V_0 \sin(1000t + \phi) \Rightarrow \omega = 1000 \text{ Hz}$$

$$R = 400 \Omega, C = 2 \mu F, L = 100 \text{ mH}$$

$$\therefore \text{Capacitive reactance, } X_c = \frac{1}{\omega C}$$

$$\Rightarrow X_C = \frac{1}{1000 \times 2 \times 10^{-6}}$$

$$\Rightarrow X_c = \frac{10^3}{2} \Rightarrow X_c = 500 \Omega$$

$$\therefore \text{Inductive reactance, } X_L = \omega L$$

$$\Rightarrow X_L = 1000 \times 100 \times 10^{-3} \Rightarrow X_L = 100 \Omega$$

$$\text{So } X_c > X_L$$

$$\Rightarrow \tan \phi \text{ is negative.}$$

Hence, the voltage lags behind the current by a phase angle ϕ .

$$\therefore \text{Phase difference, } \tan \phi = \frac{X_L - X_C}{R}$$

$$\tan \phi = \frac{100 - 500}{400} \Rightarrow \tan \phi = \frac{-400}{400}, \tan \phi = -1$$

$$\Rightarrow \tan \phi = -\tan\left(\frac{\pi}{4}\right) \Rightarrow \phi = -\frac{\pi}{4}$$

This is the required value of the phase difference between the current and the voltage in the given series L-C-R circuit.

$$\text{As, } \cos \phi < 1$$

ii. Suppose, new capacitance of the circuit is C' . Thus, to have power factor unity

$$\cos \phi' = 1 = \frac{R}{\sqrt{R^2 + (X_L - X_C')^2}}$$

$$\Rightarrow R^2 = R^2 + (X_L - X_C')^2$$

$$\Rightarrow X_L = X_C' = \frac{1}{\omega C'} \text{ or } \omega L = \frac{1}{\omega C'}$$

$$\Rightarrow \omega^2 = \frac{1}{LC'} \text{ or } (1000)^2 = \frac{1}{LC'} (\because \omega = 1000)$$

$$\Rightarrow C' = \frac{1}{L \times 10^6} = \frac{1}{100 \times 10^{-3} \times 10^6}$$

$$= \frac{10}{10^6} = \frac{1}{10^5} = 10^{-5}$$

$$\Rightarrow C' = 10^{-5} \text{F} = 10 \times 10^{-6} \text{F} = 10 \mu\text{F}$$

As, $C' > C$. Hence, we have to add an additional capacitor of capacitance

$8 \mu\text{F} (10 \mu\text{F} - 2 \mu\text{F})$ in parallel with previous capacitor.

15. It can be calculated with the help of formula of phase difference.

As applied voltage, $V = 140 \sin 100\pi t$

$$C = \frac{50}{\pi} \mu\text{F}, L = \frac{5}{\pi} \text{H}, R = 400 \Omega$$

Comparing it with $V = V_0 \sin \omega t$,

$$V_0 = 140 \text{V}, \omega = 100\pi$$

Inductive reactance, $X_L = \omega L$

$$X_L = 100\pi \times 5/\pi = 500 \Omega$$

Capacitive reactance, $X_C = \frac{1}{\omega C}$

$$X_C = \frac{1}{100\pi \times \frac{50}{\pi} \times 10^{-6}} = 200 \Omega$$

Impedance of the AC circuit,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

$$= \sqrt{400^2 + (500 - 200)^2}$$

$$Z = \sqrt{1600 + 900} = 500 \Omega$$

Maximum current in the circuit,

$$I_0 = \frac{V_0}{Z} = \frac{140}{500}$$

$$I_{\text{rms}} = \frac{I_0}{\sqrt{2}} = \frac{140}{500 \times \sqrt{2}} = 0.2 \text{A}$$

V_{rms} across resistor R, $V_{\text{rms}} = I_{\text{rms}} R$

$$V_{\text{rms}} = 0.2 \times 400 = 80 \text{V}$$

V_{rms} across inductor, $V_L = I_{\text{rms}} X_L$

$$V_L = 0.2 \times 500 = 100 \text{V}$$

V_{rms} across capacitor, $V_C = I_{\text{rms}} X_C$

$$V_C = 0.2 \times 200 = 40 \text{V}$$

Here, $V < V_R + V_L + V_C$

Because V_L and V_R are not in same phase,

$$\therefore V = \sqrt{V_R^2 + (V_L - V_C)^2}$$