


# 2

## Steady State AC Analysis



### Multiple Choice Questions

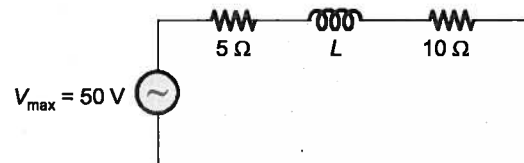- Q.1 In the circuit shown in the given figure, if the power consumed by the 5 ohm resistor is 10 W, then the power factor of the circuit is



- (a) 0.8 (b) 0.6  
(c) 0.5 (d) zero [ESE-1996]

- Q.2 A series circuit containing passive elements has the following current and applied voltage :

$$v = 200 \sin(2000t + 50^\circ)$$


$$i = 4 \cos(2000t + 13.2^\circ)$$

The circuit elements

- (a) must be resistance and capacitance  
(b) must be resistance and inductance  
(c) must be inductance, capacitance and resistance  
(d) could be either resistance and capacitance or resistance, inductance and capacitance.

[ESE-1996]

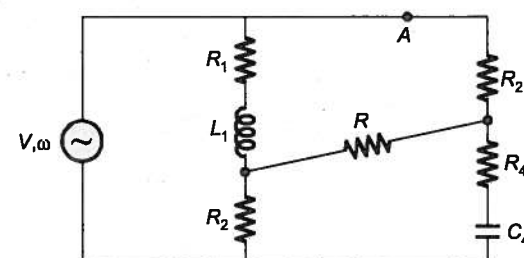
- Q.3 In the circuit shown in the figure, if the current in resistance 'R' is Nil, then



- (a)  $\frac{\omega L_1}{R_1} = \frac{1}{\omega C_4 R_4}$   
(b)  $\frac{\omega L_1}{R_1} = \omega C_4 R_4$   
(c)  $\tan^{-1} \frac{\omega L_1}{R_1} + \tan^{-1} \omega C_4 R_4 = 0$   
(d)  $\tan^{-1} \frac{\omega L_1}{R_1} + \tan^{-1} \frac{1}{\omega C_4 R_4} = 0$

[ESE-1999]

- Q.4 In the circuit shown in the figure, output  $|V_0(j\omega)|$  is

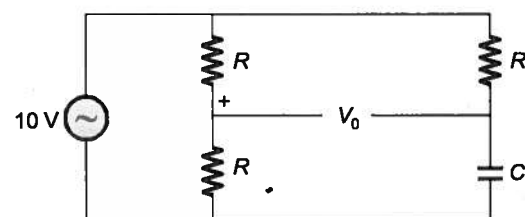

- (a) indeterminable as values of R and C are not given  
(b) 2.5 V  
(c)  $5\sqrt{2}$  V  
(d) 5 V

[ESE-1999]


- Q.5 A series LCR circuit with  $R = 10 \Omega$ ,  $|X_L| = 20 \Omega$  and  $|X_C| = 20 \Omega$  is connected across an AC supply of  $200 V_{rms}$ . The rms voltage across the capacitor is

- (a)  $200 \angle -90^\circ$  V (b)  $200 \angle 90^\circ$  V  
(c)  $400 \angle 90^\circ$  V (d)  $400 \angle -90^\circ$  V

[ESE-2000]


- Q.6 In the circuit shown in the figure below, the current supplied by the sinusoidal current source I is

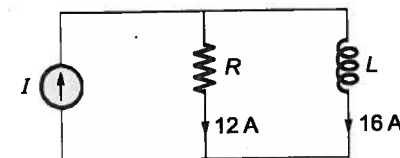- (a) 28 A  
(b) 4 A  
(c) 20 A  
(d) not determinable from the data given



[ESE-2000]

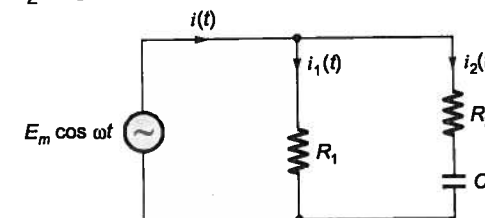- Q.7 When the angular frequency  $\omega$  in the figure is varied from 0 to  $\infty$ , the locus of the current phasor  $I_2$  is given by




- (a)
- (b)
- (c)
- (d)

[GATE-2001]

- Q.8 What is the locus of the tip of the voltage phasor across R in a series R-L-C circuit?

- (a) A parabola  
(b) An ellipse  
(c) A circle  
(d) A rectangular hyperbola [ESE-2004]

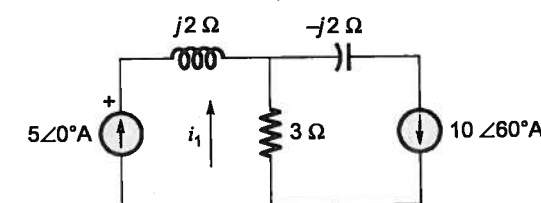- Q.9 For the circuit shown in the figure, the instantaneous current  $i_i(t)$  is



- (a)  $\frac{10\sqrt{3}}{2} \angle 90^\circ$  (b)  $\frac{10\sqrt{3}}{2} \angle -90^\circ$   
(c)  $5 \angle 60^\circ$  Amps. (d)  $5 \angle -60^\circ$  Amps.

[GATE-2005]


- Q.10 An RLC series circuit has a resistance R of  $20 \Omega$  and a current which lags behind the applied voltage by  $45^\circ$ . If the voltage across the inductor is twice the voltage across the capacitor, what is the value of inductive reactance?

- (a)  $10 \Omega$  (b)  $20 \Omega$   
(c)  $40 \Omega$  (d)  $60 \Omega$

[ESE-2005]

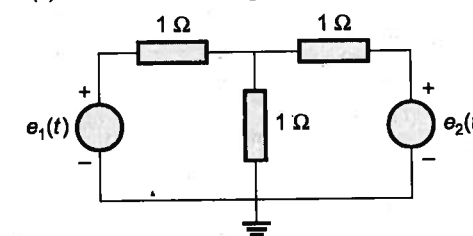- Q.11 In the circuit shown in the below figure,  $e_1(t) = \sqrt{3} \cos(\omega t + 30^\circ)$  and

$e_2(t) = \sqrt{3} \sin(\omega t + 60^\circ)$ . What is the voltage  $v(t)$  across the  $1 \Omega$  grounded resistor?



- (a)  $\{\cos \omega t\}$  V  
(b)  $\{\sin(\omega t + 30^\circ) + \cos(\omega t + 60^\circ)\}$  V  
(c)  $\{1 \angle 90^\circ\}$  V  
(d)  $\{j1\}$  V

[ESE-2006]


**Q.12 Assertion (A):** Power factor is defined as the ratio of apparent power to the average power in an a.c. circuit.

**Reason (R):** The magnitude of power factor is always less than unity.

- (a) Both A and R are true and R is the correct explanation of A.  
 (b) Both A and R are true but R is NOT the correct explanation of A.  
 (c) A is true but R is false.  
 (d) A is false but R is true.

[ESE-2008]

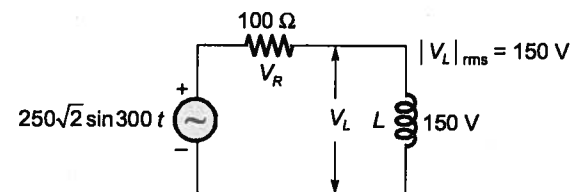**Q.13** Consider the following with respect to the circuit as shown below:




- $V_R = 100\sqrt{2} \text{ V}$
- $|I|_{\text{rms}} = 2 \text{ A}$
- $L = 0.25 \text{ H}$

Which of the above statements is/are correct?

- (a) 1 only (b) 2 and 3  
 (c) 1 and 3 (d) 1 and 2

[ESE-2009]

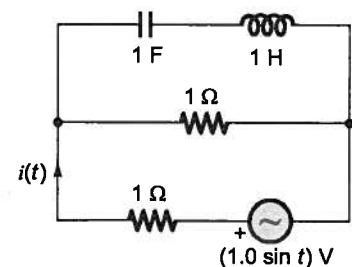
**Q.14** The r.m.s. value of the current  $i(t)$  in the circuit shown below is



- (a)  $\frac{1}{2} \text{ A}$  (b)  $\frac{1}{\sqrt{2}} \text{ A}$   
 (c)  $1 \text{ A}$  (d)  $\sqrt{2} \text{ A}$


[GATE-2011]

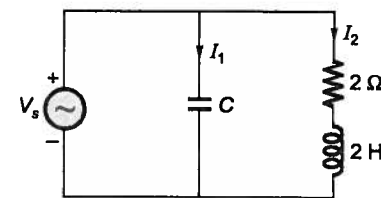**Q.15** In the network shown below  $V_s = 4 \cos 2t$ . The value of  $C$  is so chosen that the circuit impedance is maximum. Then  $I_1$  leads  $I_2$  by



- (a)  $45^\circ$  (b)  $90^\circ$   
 (c)  $0^\circ$  (d)  $135^\circ$  [ESE-2013]

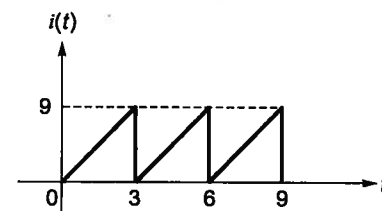**Q.16** The current waveform  $i(t)$  in a pure resistor of  $20 \Omega$  is shown in the figure.



The power dissipated in the resistor is

- (a)  $135 \text{ W}$  (b)  $270 \text{ W}$   
 (c)  $540 \text{ W}$  (d)  $14.58 \text{ W}$  [ESE-2014]


**Q.17** A  $230 \text{ V}$  rms source supplies power to two loads connected in parallel. The first load draws  $10 \text{ kW}$  at  $0.8$  leading power factor and the second one draws  $10 \text{ kVA}$  at  $0.8$  lagging power factor. The complex power delivered by the source is

- (a)  $(18 + j1.5) \text{ kVA}^*$  (b)  $(18 - j1.5) \text{ kVA}$   
 (c)  $(20 + j1.5) \text{ kVA}$  (d)  $(20 - j1.5) \text{ kVA}$

[GATE-2014]

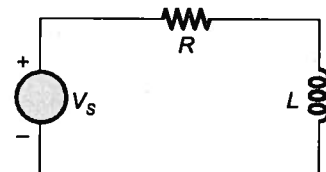**Q.18**  $V_s = 5 \cos t$  and the complex power drawn in

$P_{\text{complex}} = \frac{3}{2} + 2j$ , the value of  $R$  and  $L$  respectively will be




- (a)  $\frac{3}{2}$  and  $\frac{4}{5}$  (b)  $\frac{16}{3}$  and  $\frac{16}{5}$   
 (c)  $4$  and  $3$  (d)  $3$  and  $4$

[ESE-2015]

**Q.19** In the RLC circuit shown in the figure, the input voltage is given by

$$v_i(t) = 2 \cos(200t) + 4 \sin(500t)$$

The output voltage  $v_o(t)$  is

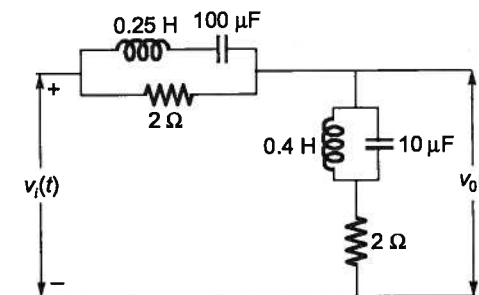

- (a)  $\cos(200t) + 2 \sin(500t)$   
 (b)  $2 \cos(200t) + 4 \sin(500t)$   
 (c)  $\sin(200t) + 2 \cos(500t)$   
 (d)  $2 \sin(200t) + 4 \cos(500t)$


[GATE-2016]



### Numerical Data Type Questions


**Q.20** A series RLC network with  $R = 45 \Omega$  and  $L = 387.5 \text{ mH}$  is connected across an ac supply of  $200 \text{ V}$  (rms) at a frequency of  $400 \text{ rad/s}$ . The impedance angle is measured to be  $36.87^\circ$ . If the power dissipated in the circuit is  $640 \text{ W}$ , then what is the value of capacitance  $C$  (in  $\mu\text{F}$ )?

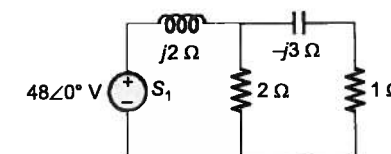**Q.21** The average power delivered to the  $1 \Omega$  resistor in the circuit shown in figure, will be \_\_\_\_\_ watts.




**Q.22** A  $0.2 \text{ H}$  inductor carries an ac current of  $0.5 \text{ A}$  (peak) at  $60 \text{ Hz}$ . A capacitor is to be connected in parallel with the inductor such that it reduces the magnitude of the current in the inductor to  $0.3 \text{ A}$ . Assuming that the total current supplied to the network does not change after adding the capacitor, what values of capacitance will be required (in  $\mu\text{F}$ )?

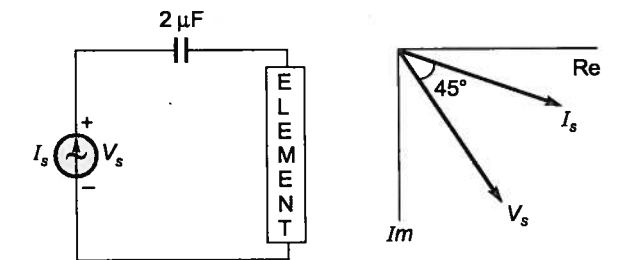**Q.23** For the following circuit, phasor diagram is given. The elements in the box is resistor then its value will be ( $\omega = 500 \text{ rad/sec}$ ) \_\_\_\_\_  $\text{k}\Omega$ .



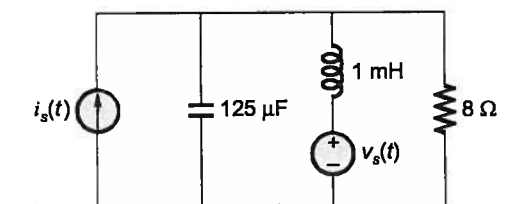
**Q.24** The voltage and current source applied to the given circuit are respectively given as  $v_s(t) = 80 \cos(8 \times 10^3 t) \text{ V}$

and  $i_s(t) = 10 \cos(2 \times 10^3 t) \text{ A}$  the average power absorbed by the  $8 \Omega$  resistor is \_\_\_\_\_ watts.



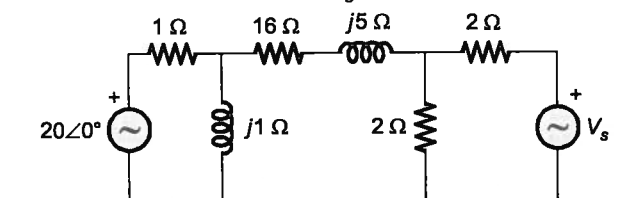
### Try Yourself

**T1.** In the circuit shown if power dissipated in  $16 \Omega$  resistor is zero then  $V_s$  is



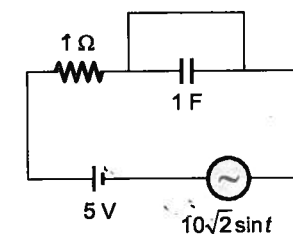**T2.** Find voltmeter reading of the circuit shown




- (a)  $5 \text{ V}$  (b)  $7.07 \text{ V}$   
 (c)  $8.66 \text{ V}$  (d)  $10 \text{ V}$

T3. The resistance of a two element circuit with an instantaneous current of  $I = 4.24 \sin(500t + 45^\circ)$  that has taken real power of 180 W at a power factor 0.8 lag is

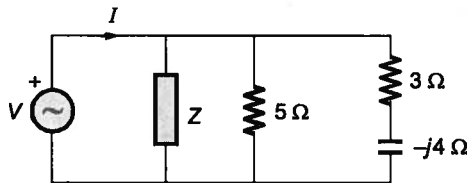
- (a)  $25 \Omega$  (b)  $15 \Omega$   
(c)  $20 \Omega$  (d)  $10 \Omega$

T4. Find  $Z$  in the parallel circuit of the network shown if  $V = 50 \angle 30^\circ$  and  $I = 27.9 \angle 57.8^\circ$




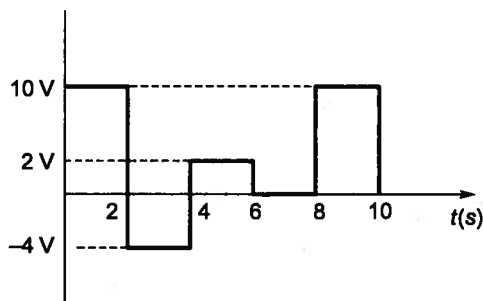- (a)  $5 \angle -30^\circ$  (b)  $6 \angle 30^\circ$   
(c)  $5 \angle 30^\circ$  (d) None

T5. Find RMS value of the following wave form



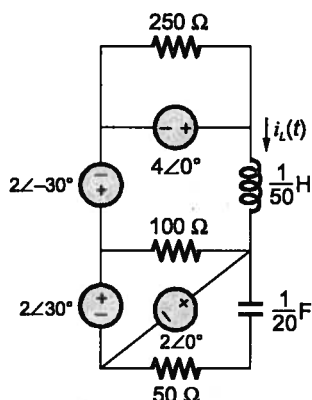T6. In the given circuit of figure, if  $\omega = 100$  rad/sec, current  $i_L(t)$  is



- (a)  $2\cos(200\pi t - 45^\circ)$   
(b)  $1.414\cos(100t + 45^\circ)$   
(c)  $1.414\cos(100t - 45^\circ)$   
(d)  $2\cos(100\pi t + 45^\circ)$

T7. The voltage across a  $20 \mu\text{F}$  capacitor is defined as follows

$$v(t) = \begin{cases} (30t^2)\text{V}, & 0 < t < 0.5\text{s} \\ 30(t-1)^2\text{V}, & 0.5\text{s} < t < 1\text{s} \\ 0, & \text{otherwise} \end{cases}$$

The waveform of current, through the capacitor is

