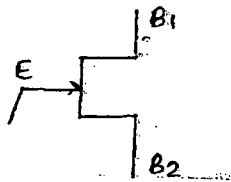



UJT



B_1 & B_2 are Base terminal
E - Emitter terminal.

UJT - unijunction transistor.


Equivalent circuit of UJT $\rightarrow$

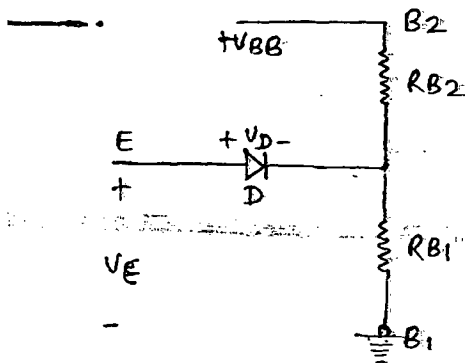

* R_{B1} & $R_{B2} \rightarrow$ High value (off state) ^{UJT}

* Diode is on then UJT on
diode is off then UJT OFF

Suppose diode is off;

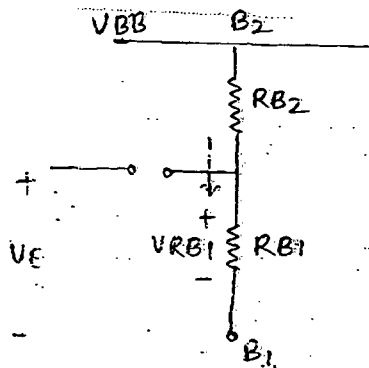

$$V_{RB1} = \left(\frac{R_{B1}}{R_{B1} + R_{B2}} \right) V_{BB}$$

$$V_{RB1} = \eta V_{BB}$$

$$\eta = \frac{R_{B1}}{R_{B1} + R_{B2}}$$

Intrinsic stand off Ratio.

η = Intrinsic stand off ratio

$$\text{Let; } V_p = V_{RB1} + V_D$$

$$V_p = \eta V_{BB} + V_D$$

($V_p \rightarrow$ Peak point voltage)

$\uparrow V_E$ & when it reaches to V_p then the UJT will turn on

$$\uparrow V_E \Rightarrow V_p, \text{ UJT} \rightarrow \text{ON}$$

* UJT exhibits -ve resistance character.

Therefore when UJT starts conducting the base resistance R_{B1} starts decreasing.


— Therefore emitter vol. starts decreasing when UJT starts conducting.

$\downarrow V_E \Rightarrow V_V, \text{ UJT} \rightarrow \text{OFF}$

$V_V = \text{Value voltage}$


* When emitter vol. starts decreasing & reaches to V_V then UJT $\rightarrow$ OFF

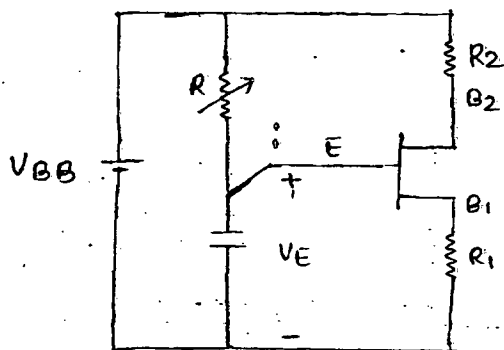* UJT working as Relaxation oscillator $\rightarrow$



UJT $\rightarrow$ OFF, $V_{B1} = 0$

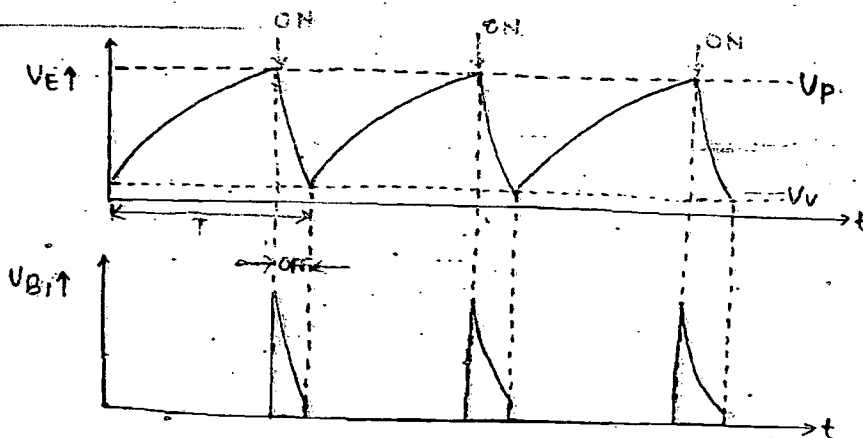UJT $\rightarrow$ OFF, base vol. will charge the capacitor.




$$T = RC \ln\left(\frac{1}{1-\eta}\right)$$


$$f = \frac{1}{RC \ln\left(\frac{1}{1-\eta}\right)}$$

* Synchronised UJT firing ckt →



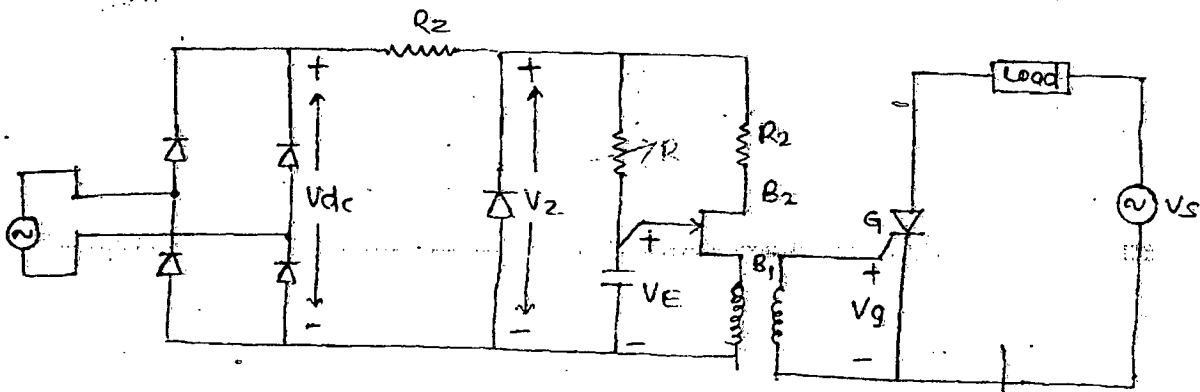
- * We must synchronise the firing ckt wrt to the main ckt power supply to match the timings of gate pulse in both the ckt.
- * Therefore we must use same power supply in both the ckt for the purpose of synchronisation.



∴ Power ckt 1- ϕ HWR

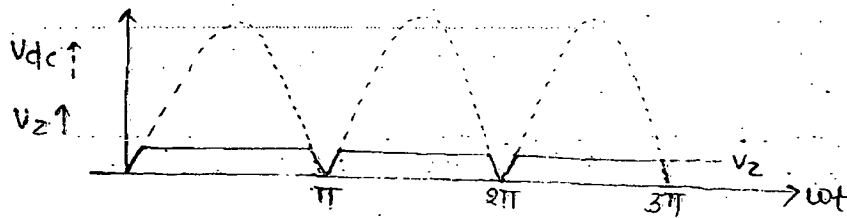

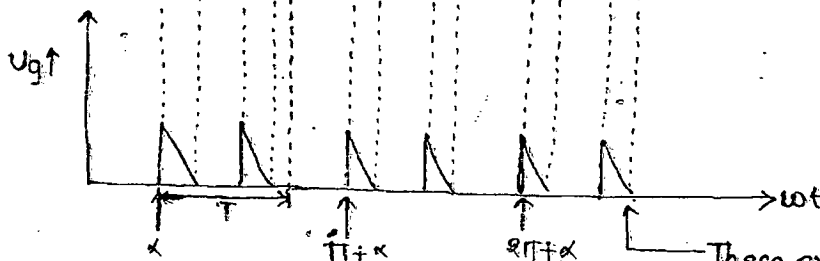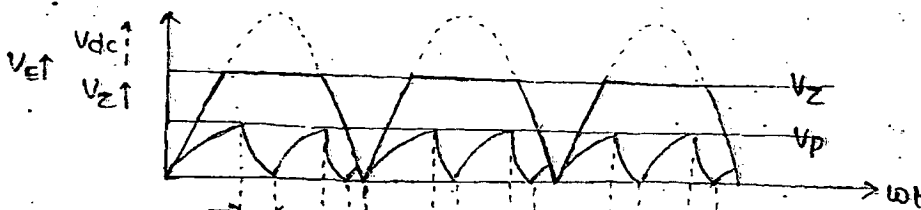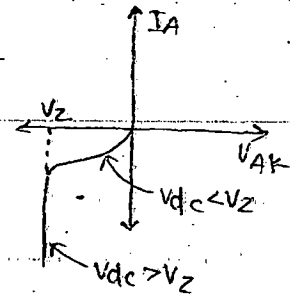(Still we are not getting the pure dc in 2 π variation)




These extra gate pulse will not effect

Protection OF Thyristor

(1) Over Current Protection → * We must connect either Fuse (or) CB in series with thy. For Oc protection.

(2) Over Voltage Protection →

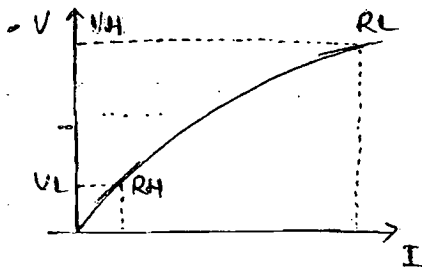

* We must connect a varistor across the thy.

* Varistor is a non-linear resistor

* All metal oxide resistor behave as non-linear resistor.

eg:- ZnO (zinc oxide)

(3) $\frac{dv}{dt}$ protection →


$$\uparrow I_c = C_j \frac{dv}{dt} \uparrow \quad \& \quad \uparrow I_c \text{ then SCR ON}$$

* At high $\frac{dv}{dt}$ the SCR may turn ON before the gate pulse is given.

* This is an accidental turn-ON.

* This unwanted turn-ON is known as False turn-ON.

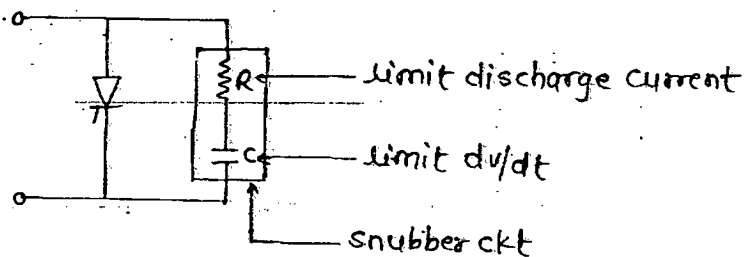* $\frac{dv}{dt}$ protection is needed to avoid the False turn ON.




* This ckt is known as Vol. snubber because of $\frac{dv}{dt}$.

Que → What is a snubber ckt?

Ans → When SCR is undergoing switching operation (ON $\rightleftharpoons$ OFF) it is subjected to high ele. stress ($\frac{dv}{dt}$ stress, $\frac{di}{dt}$ stress, overvolt etc)

* The snubber ckt will limit the ele. stress & protect the SCR during switching operations.

(iv) di/dt Protection $\rightarrow$

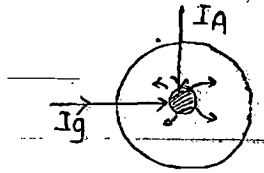

$\uparrow \frac{di_A}{dt} > \text{spread velocity of charge carriers}$

Effect of high $di/dt \rightarrow$ * If $di/dt > \text{spread velocity of charge carriers}$ then the charge density increases cumulatively in a small condⁿ area & this results in the formation of local hotspots damaging the device

* We must connect an inductor in series with SCR for di/dt protection

