

## Lecture - 5

### R-L Parallel Circuit:-

By KCL



$$I = I_R \angle 0 + I_L \angle -90^\circ$$

$$\Rightarrow \frac{V}{Z} = \frac{V}{R} - j \frac{V}{X_L}$$

$$\Rightarrow VY = VG - jVB_L$$


$$\Rightarrow \boxed{Y = G - jB_L}$$

mho    mho    mho

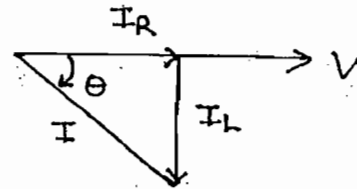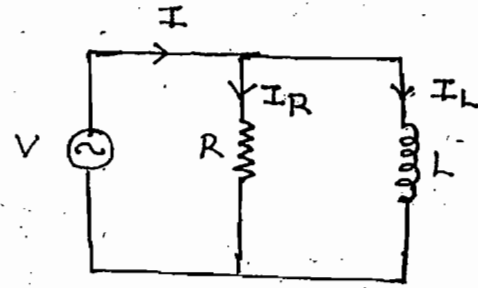


$$\boxed{I = \sqrt{I_R^2 + I_L^2}}$$
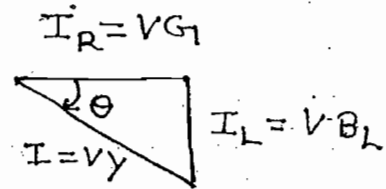
$$\theta = \tan^{-1} \left( \frac{-I_L}{I_R} \right)$$




$$\boxed{Y = \sqrt{G^2 + B_L^2}}$$
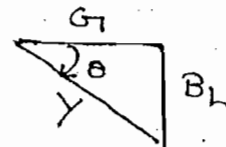
$$\theta = \tan^{-1} \left( \frac{-B_L}{G} \right)$$



$$\boxed{S = \sqrt{P^2 + Q_L^2}}$$
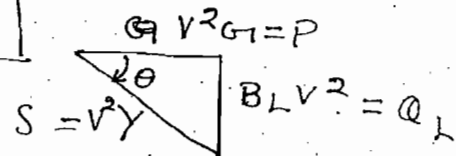
$$\theta = \tan^{-1} \left( \frac{-Q_L}{P} \right)$$



Power factor:-


$$\rightarrow \boxed{\cos \theta = \frac{I_R}{I} = \frac{G}{Y} = \frac{P}{S} = \text{Lagging}}$$

### R-C Parallel Circuit:-

By KCL

$$I = I_R \angle 0 + I_C \angle +90^\circ$$

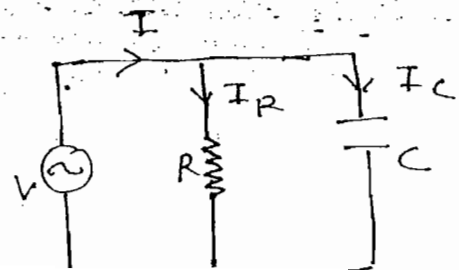
$$\Rightarrow \frac{V}{Z} = \frac{V}{R} + j \frac{V}{X_C}$$



$$\Rightarrow VY = VG_1 + jV\dot{B}_C$$


$$\Rightarrow \boxed{Y = G_1 + jB_C}$$

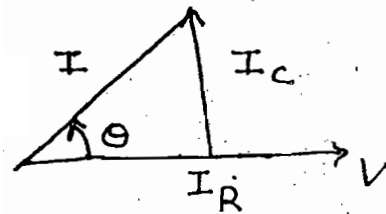$\downarrow$        $\downarrow$        $\downarrow$   
 $Mho$     $Mho$     $Mho$




$$\boxed{I = \sqrt{I_R^2 + I_C^2}}$$
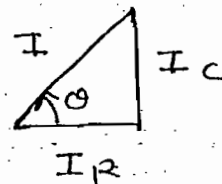
$$\boxed{\theta = \tan^{-1} \left( \frac{I_C}{I_R} \right)}$$




$$\boxed{Y = \sqrt{G_1^2 + B_C^2}}$$
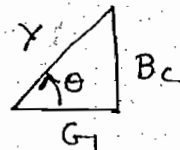
$$\boxed{\theta = \tan^{-1} \left( \frac{B_C}{G_1} \right)}$$



$$\boxed{S = \sqrt{P^2 + Q_C^2}}$$
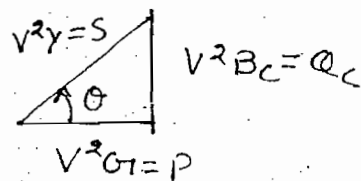
$$\boxed{\theta = \tan^{-1} \left( \frac{Q_C}{P} \right)}$$



Power Factor  $\Rightarrow$

$$\boxed{\cos \theta = \frac{I_R}{I} = \frac{G_1}{Y} = \frac{P}{S} = \text{leading}}$$

RLC Parallel Circuit:-



By KCL

$$I = I_R \angle 0^\circ + I_L \angle -90^\circ + I_C \angle +90^\circ$$

$$\Rightarrow \frac{V}{Z} = \frac{V}{R} - j \frac{V}{X_L} + j \frac{V}{X_C}$$


$$\Rightarrow VY = V [G_1 + j(B_C - B_L)]$$
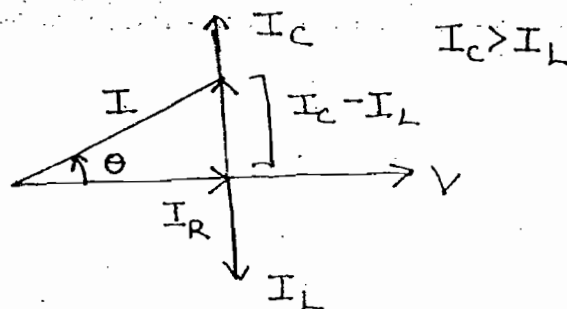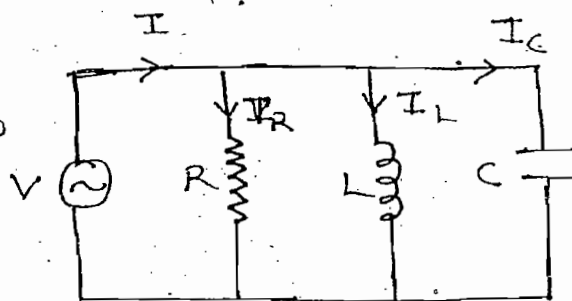
$$\Rightarrow \boxed{Y = G_1 + j(B_C - B_L)}$$




$$I = \sqrt{I_R^2 + (I_C - I_L)^2}$$
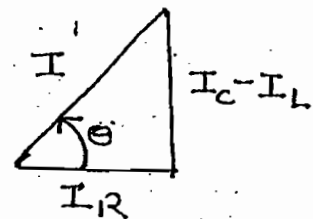
$$\theta = \tan^{-1} \left( \frac{I_C - I_L}{I_R} \right)$$



$$Y = \sqrt{G^2 + (B_C - B_L)^2}$$
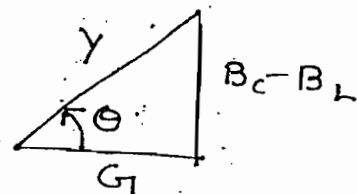
$$\theta = \tan^{-1} \left( \frac{B_C - B_L}{G} \right)$$



$$\text{Power Factor} = \cos \theta = \frac{I_R}{I} = \frac{G}{Y} = \frac{P}{S}$$

- (i)  $I_C > I_L \rightarrow$  leading  
 (ii)  $I_C < I_L \rightarrow$  lagging  
 (iv)  $I_C = I_L \rightarrow$  Unity Power factor


Note:-

When combinational elements are present then we can't directly find conductance, admittance etc. Then following procedure is used

$$I_1 = \left( \frac{V}{R_1 + jX_L} \right) \left( \frac{R_1 - jX_L}{R_1 - jX_L} \right)$$

$$\Rightarrow \frac{V}{Z_1} = V \left[ \frac{R_1}{R_1^2 + X_L^2} - j \frac{X_L}{R_1^2 + X_L^2} \right]$$

$$\Rightarrow Y_1 = G_1 - jB_L$$

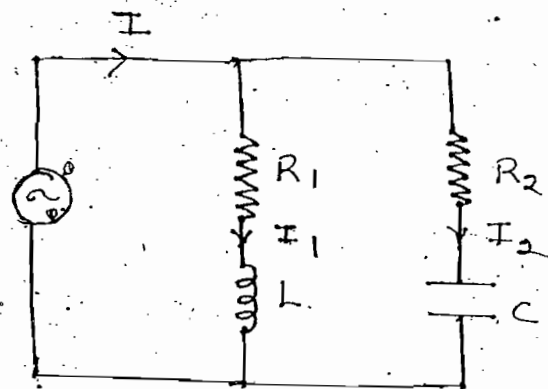

$$I_2 = \frac{V}{R_2 - jX_C} \frac{R_2 + jX_C}{R_2 + jX_C}$$

$$\Rightarrow \frac{V}{Z_2} = V \left[ \frac{R_2}{R_2^2 + X_C^2} + j \frac{X_C}{R_2^2 + X_C^2} \right]$$

$$Y_2 = G_2 + jB_c$$


$$I = I_1 + I_2$$

$$\Rightarrow VY_{eq} = VI_1 + VI_2$$

$$\Rightarrow Y_{eq} = Y_1 + Y_2$$

$$\Rightarrow Y_{eq} = (G_1 + G_2) + j(B_c - B_L)$$

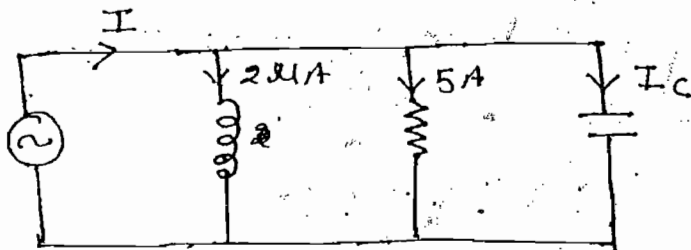ques:- Find  $I_c$  and  $I$  of the circuit shown



Soln:-

$$13 = \sqrt{5^2 + I_c^2} \Rightarrow I_c = 12A$$

$$I = \sqrt{I_R^2 + (I_c - I_L)^2}$$

$$\Rightarrow I = \sqrt{5^2 + (12 - 2mA)^2} = 13A$$

Note:-


A.C  $\rightarrow$  (KVL, KCL)  $\rightarrow$  Phasor sum

D.C  $\rightarrow$  (KVL, KCL)  $\rightarrow$  Arithmetic sum

ques:- Find capacitance of the capacitor when power factor of the circuit

is 0.8 lagging

$$V(t) = \sin t$$

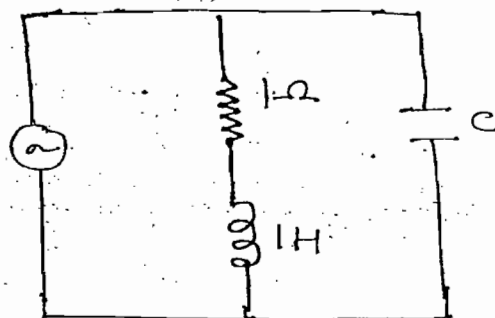

Soln:- For Branch-1

$$X_L = \omega L = 1$$

$$G_1 = \frac{R_1}{R_1^2 + X_L^2} = \frac{1}{1^2 + 1^2} = \frac{1}{2}$$

$$B_L = \frac{X_L}{R_1^2 + X_L^2} = \frac{1}{1^2 + 1^2} = \frac{1}{2}$$

$$Y_1 = G_1 - jB_L$$

$$\Rightarrow Y = \frac{1}{2} - j\frac{1}{2}$$

For Branch-2

$$Y_2 = +jB_C$$

$$Y_2 = j \frac{1}{X_C} = j\omega C \Rightarrow Y_2 = \omega C$$

$$Y_{eq} = Y_1 + Y_2$$

$$\Rightarrow Y_{eq} = \frac{1}{2} + j(C - \frac{1}{2})$$

$$\cos \theta = \frac{G}{\sqrt{G^2 + (B_C - B_L)^2}}$$

$$\Rightarrow 0.8 = \frac{\frac{1}{2}}{\sqrt{(\frac{1}{2})^2 + (C - \frac{1}{2})^2}}$$

$$\Rightarrow C = \frac{7}{8} \text{ or } \frac{1}{8}$$


Since  $B_L > B_C$

$$\frac{1}{2} > C$$

Hence,  $C = \frac{1}{8}$  Ans

ques:- Find Voltage across A and B of the circuit shown (a) 55 (b) 56 (c) 60 (d) 65

Soln:-

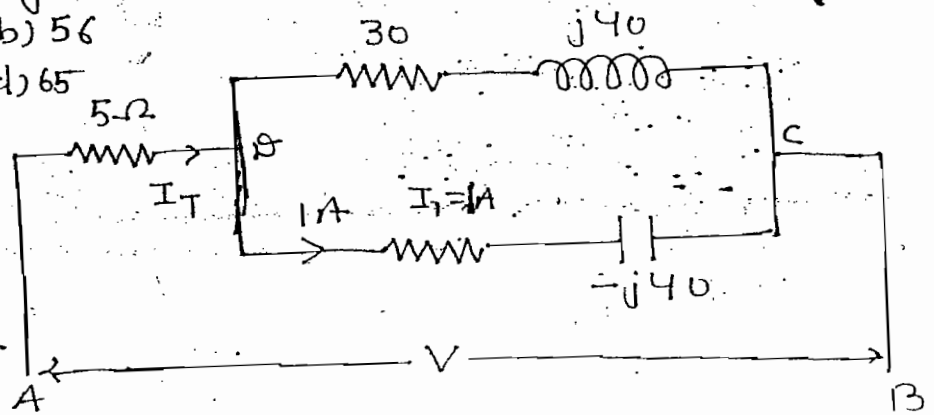

Apply current division technique.

$$I_1 = I_T \frac{30 + j40}{30 + j40 + 30 - j40} =$$

$$\Rightarrow 1 = I_T \frac{50 \angle \tan^{-1}(4/3)}{60}$$

$$\Rightarrow I_T = \frac{60}{50 \angle \tan^{-1}(4/3)} = 1.2 \angle \tan^{-1}(-4/3)$$

$$V_{AB} = I_T \times 5$$

$$\Rightarrow V_{AB} = (1.2 \times 5) \angle \tan^{-1}(-4/3)$$

$$\Rightarrow V_{AB} = 6 \angle \tan^{-1}(-4/3)$$

$$V_{BC} = (30 - j40) \angle$$

$$V_{BC} = 50 \angle \tan^{-1}(-4/3)$$

Angles are same hence they can be added

$$V_{AB} = V_{AC} = V_{AB} + V_{BC}$$

$$\Rightarrow \boxed{V_{AB} = 56 \angle \tan^{-1}(-4/3)} \quad \text{Ans}$$


Locus Diagram:-

$$X_L = 2\pi fL$$

$$X_L = 0$$

$$Z = R \Rightarrow I = \frac{V}{R}$$


$$\Rightarrow \theta = 0$$

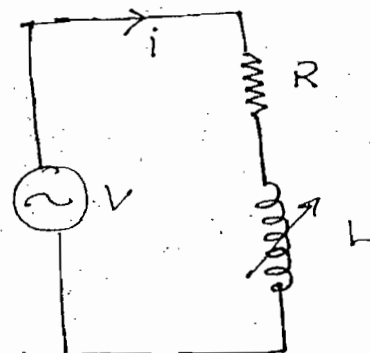

$$X_L \uparrow \quad Z \uparrow \quad I \downarrow$$

$$\theta = \tan^{-1}\left(\frac{X_L}{R}\right) \uparrow$$
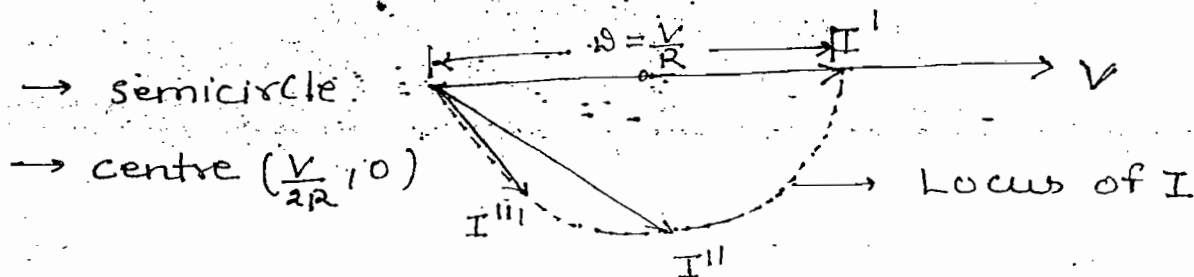
$$X_L \approx \infty \quad Z \approx \infty \quad I \approx 0$$



→ Locus diagram are useful for analysis and designing of the circuit. eg:- filters

→ With respect to practical application it is possible to develop the following locus diagram



- (i) Current locus diagram
- (ii) Voltage locus diagram
- (iii) Impedance locus diagram
- (iv) Admittance locus diagram

→ The path traced by terminous of current vectors by varying either any of the circuit elements or by varying source frequency is called as current locus

→ In the above circuit by keeping all the elements constant and by varying source frequency also same shape of the current locus diagram is obtained.

→ Develop current locus of the circuit shown

|                     |                                                                       |
|---------------------|-----------------------------------------------------------------------|
| $R=0$               | $R \uparrow$                                                          |
| $Z = X_L$           | $Z \uparrow$                                                          |
| $I = \frac{V}{X_L}$ | $I \downarrow$                                                        |
| $\theta = 90^\circ$ | $\theta = \tan^{-1} \left( \frac{X_L}{R \uparrow} \right) \downarrow$ |

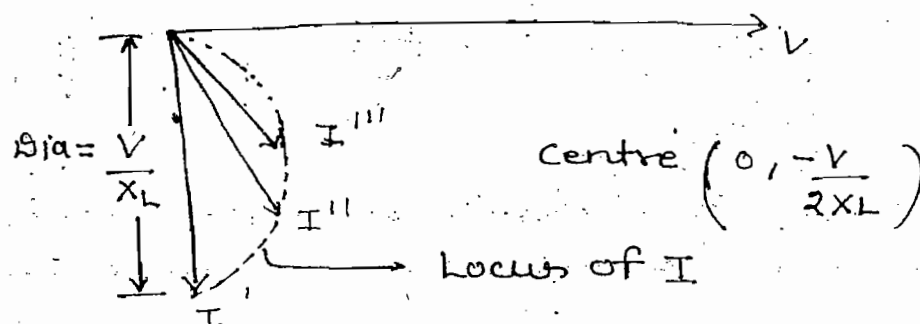
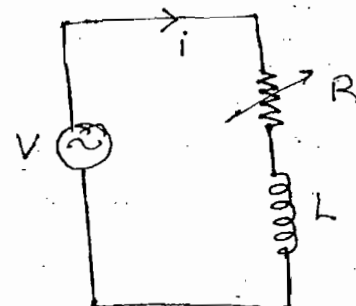


→ Diameter is always due to constant element

ques:- Develop current locus of  $I_1$  and  $I$  of the circuit shown:-

Soln:-

|                         |                         |                     |
|-------------------------|-------------------------|---------------------|
| $R_1 \simeq 0.1 \Omega$ | $R_1 \uparrow$          | $R_1 \simeq \infty$ |
| $I_1 = \frac{V}{R_1}$   | $I_1 \downarrow$        | $I_1 = 0$           |
| $\theta_1 = 0$          | $\theta_1 = 0$          | $I_2 = I$           |
| $I = I_1 + I_2$         | $I_2 = \text{Constant}$ | $I \downarrow$      |

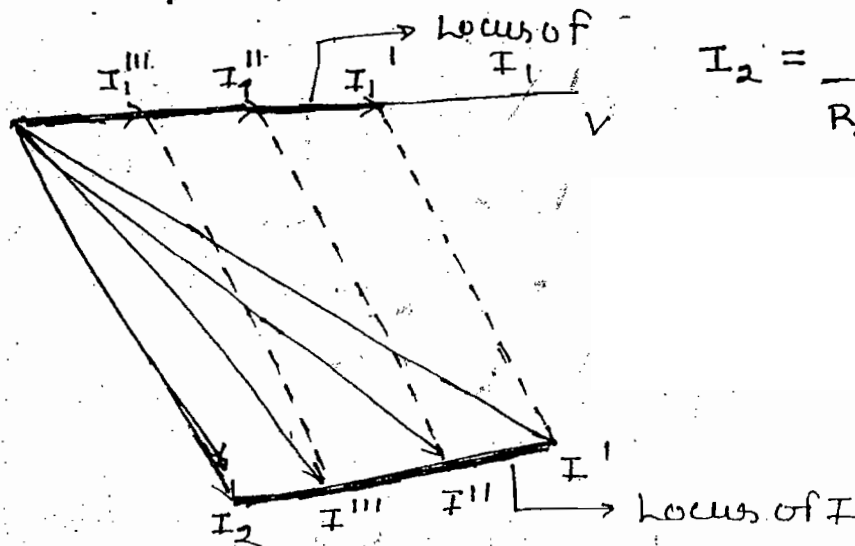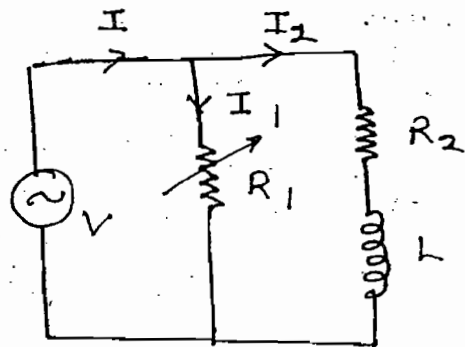

$$I_2 = \frac{V}{R_2 + jX_L}$$


Note:-

- When power factor angle is variable the shape of current locus is semi-circle
- When power factor angle is constant the shape of the current locus diagram is straight line.

ques:- Develop current locus of  $I_1$  and  $I$  of the circuit shown

Soln:-


|                           |                                                              |                     |
|---------------------------|--------------------------------------------------------------|---------------------|
| $X_C = \frac{1}{2\pi fC}$ | $X_C \uparrow$                                               | $X_C \simeq \infty$ |
| $X_C \simeq 0$            | $Z_1 = \sqrt{R_1^2 + X_C^2} \uparrow$                        | $I_1 = 0$           |
| $I_1 = \frac{V}{R_1}$     | $I_1 \downarrow$                                             | $I = I_2$           |
| $\theta_1 = 0$            | $\theta_1 = \tan^{-1}\left(\frac{-X_C}{R_1}\right) \uparrow$ |                     |
| $I = I_1 + I_2$           | $I_2 = \text{Constant}$                                      |                     |
|                           | $I_1 \downarrow$                                             |                     |

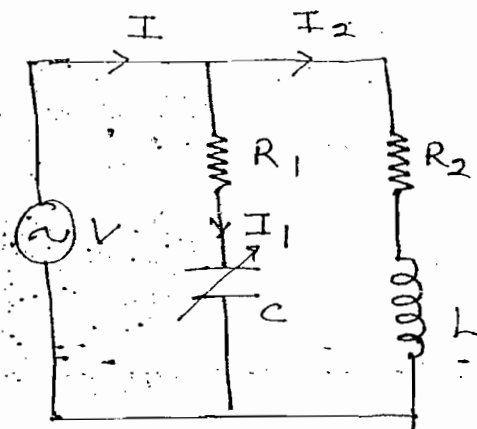


$$I_2 = \frac{V}{R_2 + jX_L}$$

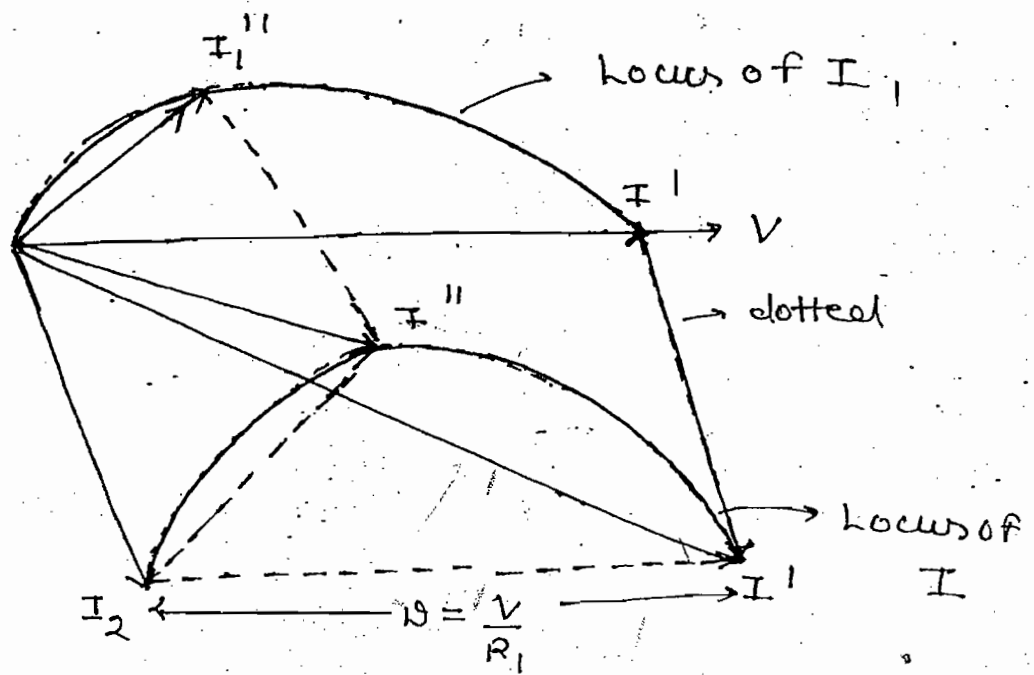Focus only angles not sign but focus on magnitude







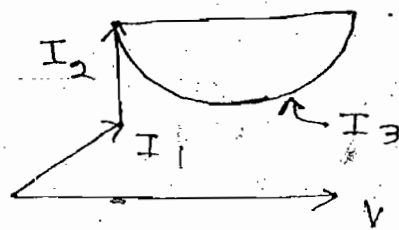
Ques:- Design a N/w for given current locus diagram



Soln:-

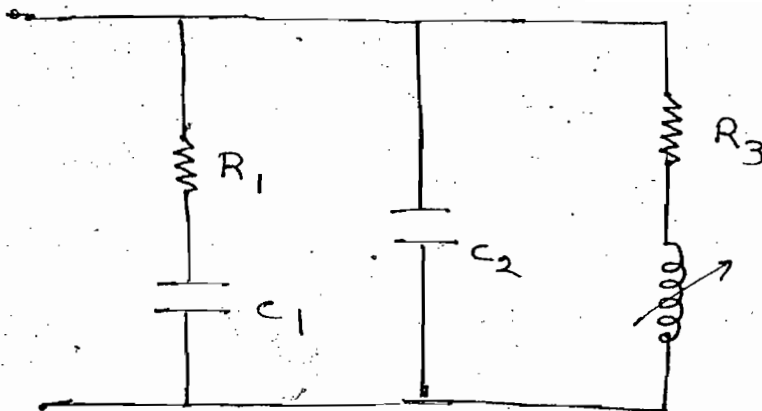

Resonance :-

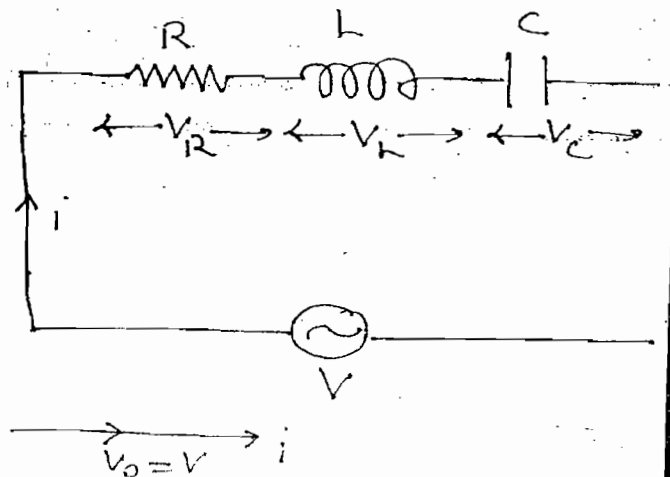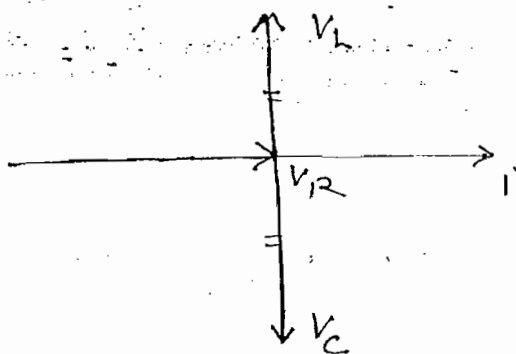

By KVL,  $V = V_R \angle 0^\circ + V_L \angle 90^\circ + V_C \angle -90^\circ$

At resonance,

$$V_L = V_C$$

$$IX_L = IX_C$$

$$\Rightarrow \omega L = \frac{1}{\omega C}$$

$$\Rightarrow \boxed{\omega_0 = \frac{1}{\sqrt{LC}}} \text{ rad/sec}$$

$$\Rightarrow \boxed{f_0 = \frac{1}{2\pi\sqrt{LC}}} \text{ Hz}$$

→ For occurrence of resonance in any circuit two energies are required. In RLC circuit inductor is having energy in the form of magnetic field capacitor is having energy in the form of electric field. When these two energies are present at particular frequency wide variations are present in the system is called as resonance.

→ The circuit is said to be resonance when source current is ~~influence~~ <sup>in phase</sup> with source voltage.

→ The frequency at which  $X_C = X_L$  is called as resonant frequency.

→ The resonant frequency indicates rate at which energy transformation is done b/w inductor and capacitor.

$$1 \rightarrow Z = R + j(X_L - X_C)$$

$$Z_{\min} = R$$

$$2 \rightarrow I_{\max} = \frac{V}{Z_{\min}} = \frac{V}{R}$$

$$3 \rightarrow \cos \theta = 1$$

$$4 \rightarrow V_R = V$$

6. Voltage across inductor or voltage across capacitor greater than source. This phenomenon is called as voltage magnification.

SECRET


- Oscillators
- Filters (BP, BE)
- Tuning circuits
- Induction heating

Variation of voltage across inductor and voltage across capacitor w.r.t frequency:-

$$X_L = 2\pi fL \quad , \quad X_C = \frac{1}{2\pi fC}$$

$$\rightarrow X = |X_L - X_C| = \infty$$

$$\Rightarrow V_C = V$$

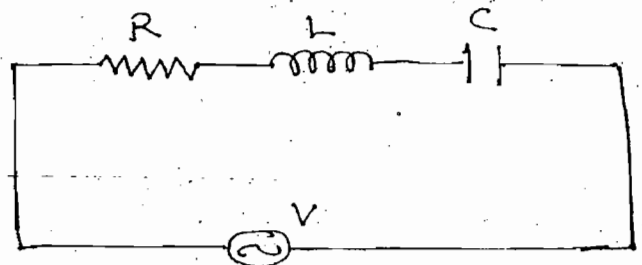

Fox indigo 7081 -

$\rightarrow f \uparrow \quad X_L \uparrow \quad X_C \downarrow \quad X = |X_L - X_C| \quad \downarrow \downarrow \quad Z \downarrow \downarrow \quad I \uparrow \uparrow \quad \boxed{V_C \uparrow}$   
 $(10\Omega) \quad (100\Omega) \quad (90\Omega)$

$\rightarrow f \uparrow \uparrow \quad X_L \uparrow \uparrow \quad X_C \downarrow \downarrow \quad Z = R + j(X_L - X_C) \uparrow \uparrow \uparrow \quad I \downarrow \downarrow \downarrow$   
(very low)  $V_C \downarrow$

$$\Rightarrow V_c = \frac{V X_c}{\sqrt{R^2 + (X_L - X_c)^2}} \Rightarrow V_c = \frac{V \frac{1}{\omega c}}{\sqrt{R^2 + (\omega L - \frac{1}{\omega c})^2}} \quad \text{--- (1)}$$

we get

$$f_c = \frac{1}{2\pi\sqrt{LC}} \sqrt{1 - \left(\frac{R_c}{2L}\right)^2}$$

For inductor:-

→  $V_L = I X_L$

→  $X_L = 2\pi f L$     &     $X_C = \frac{1}{2\pi f C}$

→  $f = 0$  ,  $X_L = 0$  ,  $X_C = \infty$      $X = |X_L - X_C| = \infty$

$Z = \infty$  ,  $I = 0$  ,     $V_L = 0$

→  $f \uparrow$      $X_L \uparrow$      $X_C \downarrow$      $X = |X_L - X_C| \downarrow \downarrow$      $Z \downarrow \downarrow$   
           (10Ω)    (100Ω)

$I \uparrow \uparrow$      $V_L \uparrow$


→  $f \uparrow \uparrow$      $X_L \uparrow \uparrow$      $X_C \downarrow \downarrow$   
                   (very low)

$Z = R + j(X_L - X_C) \uparrow \uparrow \uparrow$      $I_C \downarrow \downarrow \downarrow$      $V_L \downarrow$

→  $V_L = \frac{V X_L}{\sqrt{R^2 + (X_L - X_C)^2}} = \frac{V \omega L}{\sqrt{R^2 + (\omega L - \frac{1}{\omega C})^2}} \quad \text{--- (11)}$

Differentiate eq-(11) w.r.t  $\omega$  and equal to zero
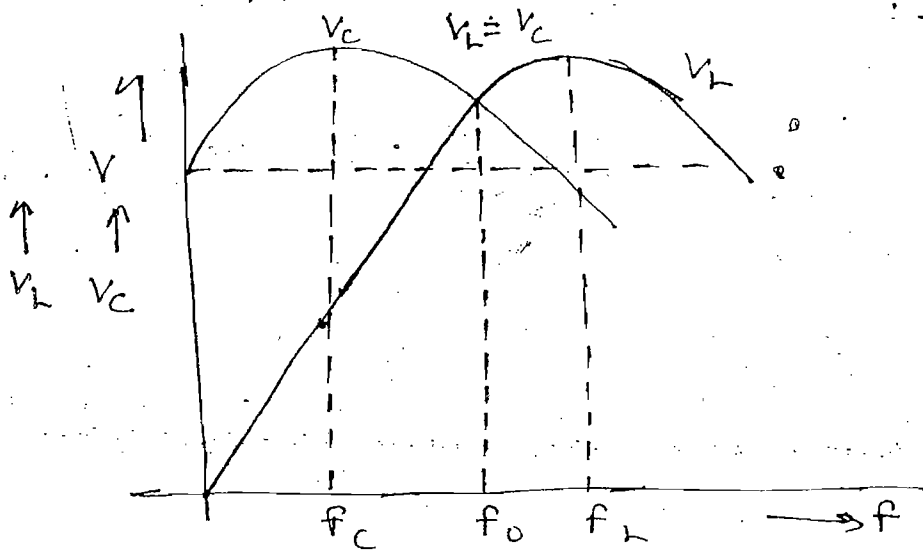
$$f_L = \frac{1}{2\pi \sqrt{LC}} \sqrt{\frac{1}{1 - \left(\frac{R^2 C}{2L}\right)}}$$



### Quality factor :-

→ Q-factor is a ratio of max. energy stored the circuit to power dissipation per cycle

$$Q =$$

$$i(t) = I_m \sin \omega t \quad \text{--- (I)}$$

$$V_c(t) = \frac{1}{C} \int i(t) dt = \frac{1}{C} \int I_m \sin \omega t dt$$

$$\Rightarrow V_c(t) = -\frac{I_m}{\omega C} \cos \omega t \quad \text{--- (II)}$$

$$W_g = \frac{1}{2} L i^2 + \frac{1}{2} C V_c^2$$

$$\Rightarrow W_g = \frac{1}{2} L (I_m \sin \omega t)^2 + \frac{1}{2} C \left( -\frac{I_m}{\omega C} \cos \omega t \right)^2$$

$$\Rightarrow W_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} C \frac{I_m^2}{\omega^2 C^2} \cos^2 \omega t$$

$$\Rightarrow W_g = \frac{1}{2} L I_m^2 \sin^2 \omega t + \frac{1}{2} L I_m^2 \cos^2 \omega t \quad \left[ \begin{array}{l} \omega^2 = \frac{1}{LC} \\ L = \frac{1}{\omega^2 C} \end{array} \right]$$

$$\Rightarrow \boxed{W_g = \frac{1}{2} L I_m^2}$$

$$\boxed{W_g = \frac{1}{2} C V_{cm}^2}$$

$$\left( \because V_{cm} = \frac{I_m}{\omega C} \right)$$

$$Q = \frac{\frac{1}{2} L I_m^2}{\left( \frac{I_m}{\sqrt{2}} \right)^2 R \frac{1}{\omega}}$$

$$I^2 R = \left( \frac{I_m}{\sqrt{2}} \right)^2 R$$

$$\Rightarrow \boxed{Q = \frac{\omega L}{R}}$$

$$\left( \omega = \frac{1}{\sqrt{LC}} \right)$$

$$\Rightarrow \boxed{Q = \frac{1}{R} \sqrt{\frac{L}{C}}}$$

$$\rightarrow \boxed{Q = \frac{\omega L}{R} = \frac{I X_L}{I R} = \frac{V_L}{V_R} = \frac{V_L}{V} \quad (V_R = V)}$$

→

$$Q = \frac{V_L \text{ or } V_C}{V}$$

$$(\because V_L = V_C)$$

→

$$Q = \frac{I^2 X_L}{I^2 R} = \frac{Q_L}{P}$$

→

$$Q = \frac{X_L \text{ or } X_C}{R}$$

$$(\because X_L = X_C)$$

→

$$Q = \frac{X_C}{R} = \frac{1}{\omega R C}$$

→

$$Q > 1, \quad X_L > R, \quad X_C > R$$

→

$$Q \propto \frac{1}{\text{Power loss } (I^2 R = P)}$$

→

$$Q \propto \frac{1}{\text{BW}}$$

Note:-

→ To obtain high efficiency circuit is designed with high Q-factor

→ To obtain wide BW circuit is designed with low Q-factor

Bandwidth:-

→ When the curve is developed b/w current and frequency then curve is called as resonance curve

 $I_m$  $\frac{I_m}{\sqrt{2}}$ 

$$\frac{1}{\sqrt{2}} = 70.7\%$$

← leading ← lagging →

 $f_1 \quad f_0 \quad f_2$ 

→ BW is the range of frequencies on either side of the resonant frequencies where the current falls from max. value to 70.7% of the max. value and it is given by

$$BW = f_2 - f_1$$

where  $f_2$  = upper cut-off frequency

$f_1$  = lower " " "

$f_1, f_2$  = 3dB points or half power frequencies

1.  $f_0 \rightarrow I_m$  ,  $Z = R$

$$f_1, f_2 \rightarrow \frac{I_m}{\sqrt{2}} \Rightarrow \boxed{Z = \sqrt{2} R}$$

2.  $f_0 \rightarrow \cos \theta = 1$

$$f_1, f_2 \rightarrow Z = R \pm jX$$

$$Z = \sqrt{R^2 + X^2} = \sqrt{2} R$$

$$\Rightarrow \boxed{X = R}$$

$$X = X_L - X_C$$

$$X_L = 2\pi f L$$

$$X_C = \frac{1}{2\pi f C}$$

$$f_1 \rightarrow X_C > X_L$$

$$X \rightarrow -ve$$

$$f_2 \rightarrow X_L > X_C$$

$$X \rightarrow +ve$$

W.r.t

$$f_1 \rightarrow Z = R - jX \quad X = R$$

$$\text{Impedance Angle} = \tan^{-1}\left(\frac{-X}{R}\right) = -45^\circ$$

$$I = \frac{V \angle 0}{Z \angle -45^\circ} = \frac{V}{Z} \angle 45^\circ$$

$$\text{Power factor angle} = 45^\circ$$

$$\Rightarrow \text{Power factor} = \cos 45^\circ = \frac{1}{\sqrt{2}} \rightarrow \text{leading}$$

W.r.t  $f_2$  :-

$$f_2 \rightarrow Z = R + jX \quad X = R$$

$$\text{Impedance angle} = \theta = \tan^{-1}\left(\frac{X}{R}\right) = +45^\circ$$

$$\text{Power factor angle} = -45^\circ$$

$$\text{Power factor} = \cos(-45^\circ) = \frac{1}{\sqrt{2}} \rightarrow \text{lagging}$$

3.  $f_1 \rightarrow X_C > X_L \quad X = R$

$$\frac{1}{\omega C} - \omega L = R \quad \text{--- (1)}$$

$$f_2 \rightarrow X_L > X_C \quad X = R$$

$$\omega_2 L - \frac{1}{\omega_2 C} = R \quad \text{--- (I)}$$

From (I) & (II)

$$\omega_1 \omega_2 = \frac{1}{LC} \quad \text{--- (III)}$$

$$\Rightarrow \omega_0^2 = \frac{1}{LC} \quad \text{--- (IV)}$$

From (III) & (IV)

$$\omega_0^2 = \omega_1 \omega_2$$

$$\Rightarrow \boxed{\begin{aligned} \omega_0 &= \sqrt{\omega_1 \omega_2} \\ f_0 &= \sqrt{f_1 f_2} \end{aligned}}$$

Add eqn (I) & (II)

$$\frac{1}{C} \left[ \frac{1}{\omega_1} - \frac{1}{\omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$\Rightarrow \frac{1}{C} \left[ \frac{\omega_2 - \omega_1}{\omega_1 \omega_2} \right] + L [\omega_2 - \omega_1] = 2R$$

$$\Rightarrow L [\omega_2 - \omega_1] + L [\omega_2 - \omega_1] = 2R$$

$$\boxed{\begin{aligned} BW &= \omega_2 - \omega_1 = \frac{R}{L} \text{ rad/sec} \\ BW &= f_2 - f_1 = \frac{R}{2\pi L} \text{ Hz} \end{aligned}}$$

$$Q = \frac{\omega_0 L}{R} \Rightarrow Q = \frac{\omega_0}{R/L}$$

$$\Rightarrow \boxed{Q = \frac{\omega_0}{\omega_2 - \omega_1} = \frac{f_0}{f_2 - f_1}}$$