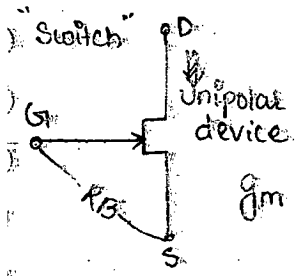


MOSFET


FET



$$(I_D)_Q = 1mA$$



$$g_m = \frac{-2 I_{DSS}}{V_p} \left[1 - \frac{(V_{GS})_Q}{V_p} \right]$$

BJT

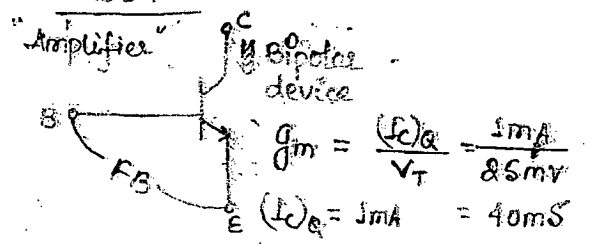


$$g_{mFET} \leq 10 g_{mBJT}$$

Ideal Switch (Inverter)

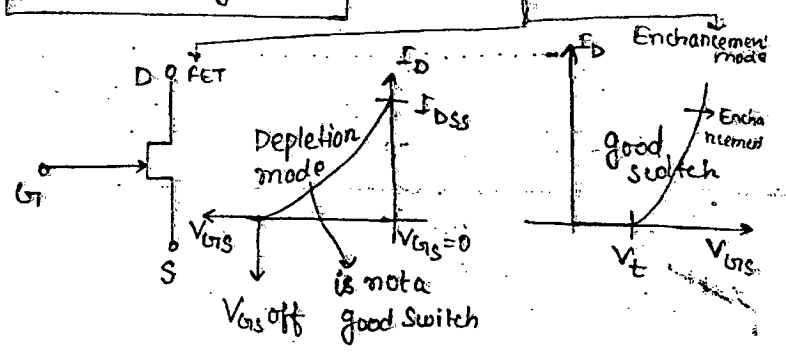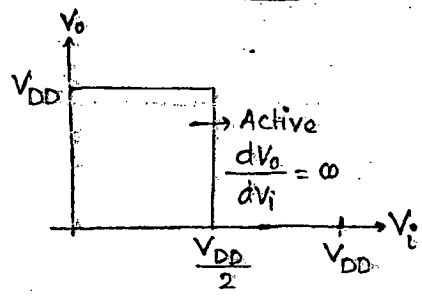



N CHANNEL ENCHANCEMENT MOSFET (NMOS)

case:

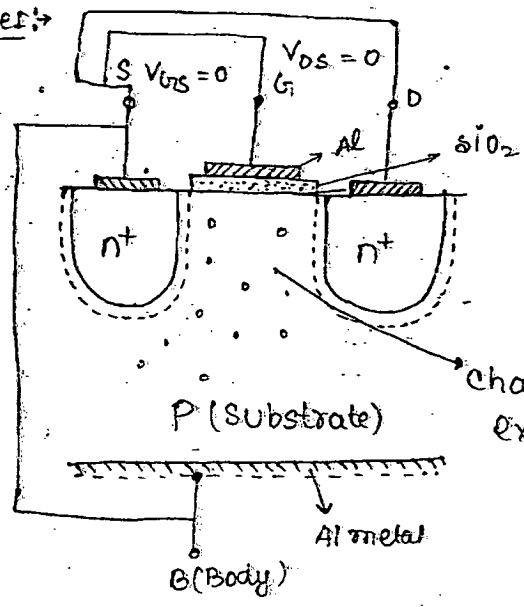

channel is not existing at $V_{GS} = 0V$
 $I_D = 0$

Case II :-

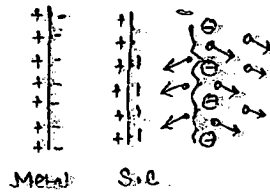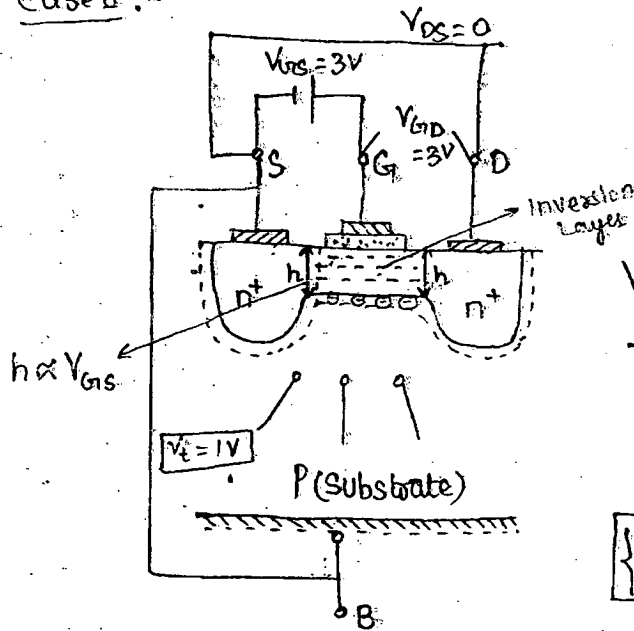

V_t = Thermal Voltage

It is the minimum V_{GS} Voltage where the conducting channel will be formed. V_t (0.5 to 1V)


$\{V_{GS} - V_t\}$ → Effective Voltage OR Over drive Voltage.

$$V_{GD} = V_{GS} - V_{DS}$$

$$= 3 - 0$$



$$= 3V$$

Case III :-

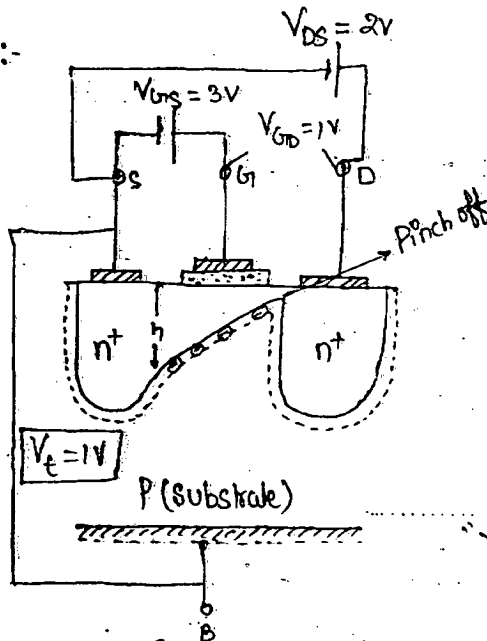

$$V_{GD} = V_{GS} - V_{DS} = 3 - 2 = 1V = V_t$$
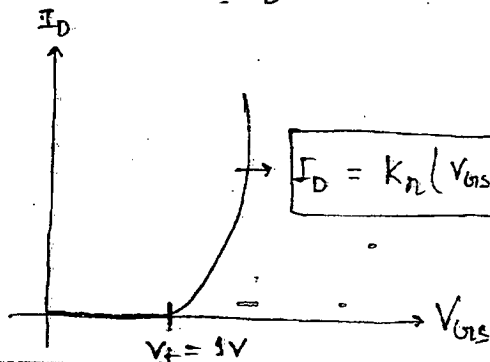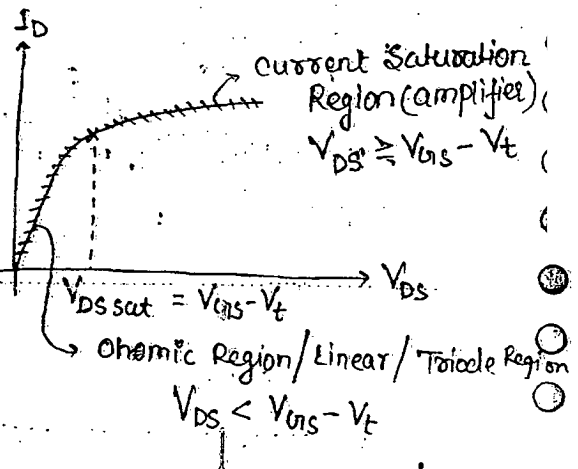
$$V_{GD} = V_{GS} - V_{DS} = 3 - 100mV \approx 3V$$



$$I_D = K_n (V_{GS} - V_t)^2 \rightarrow \text{Transfer characteristic}$$

□ V-I CHARACTERISTICS OF NMOS.



$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left\{ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right\}$$

Where, —

$\mu_n = \mu_n$ = Mobility of Electron

C_{ox} = Capacitance of oxide layer per unit area.

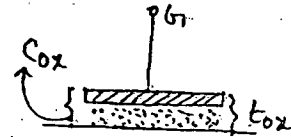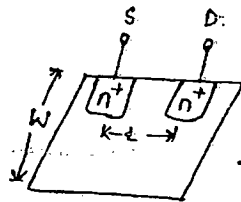$\left(\frac{W}{L} \right)$ = Aspect Ratio



$$C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$$

$$\begin{aligned} \epsilon_{ox} &= 3.9 \epsilon_0 \\ &= 3.9 \times 8.85 \times 10^{-12} \text{ F/m} \\ \epsilon_{ox} &= 3.45 \times 10^{-11} \text{ F/m} \end{aligned}$$

$\{V_{GS} - V_t\}$ = Effective voltage (or) over drive voltage.

V_{DS} = Drain to Source Voltage.

Triode Region:- $V_{DS} < V_{GS} - V_t$

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) \left\{ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right\}$$

V_{DS} (mv) Ohmic Region

$$I_D = \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t) V_{DS}$$

$$R_{DS} = \frac{V_{DS}}{I_D} = \frac{1}{\mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)}$$

Current Saturation (Amplifier)

$$V_{DS} \geq V_{GS} - V_t \quad I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2$$

K_n (Trans conductance parameter)
mA/V²

$$I_D = K_n (V_{GS} - V_t)^2 \rightarrow \text{Transfer Characteristics eq.}$$

Depletion NMOS:-

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} V_t^2 \left[\frac{V_{GS}}{V_t} - 1 \right]^2$$

$$I_D = \underbrace{\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) V_t^2}_{I_{DSS}} \left[1 - \frac{V_{GS}}{V_t} \right]^2$$

JFET



$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$$

→ Transfer Ch. eq²

$$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_t} \right]^2$$

→ Tr. Ch. eq² of NMOS depletion.

□ N-MOS

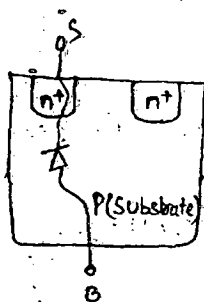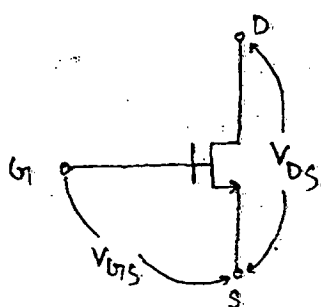

Current Saturation



$$I_D = K_n (V_{GS} - V_t)^2$$

$$K_n = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)$$

Triode Region

$$I_D = 2K_n \left\{ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right\}$$

□ P-MOS

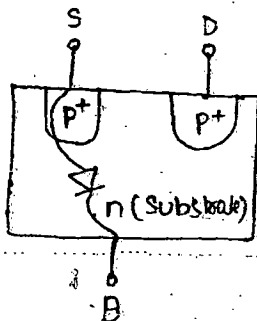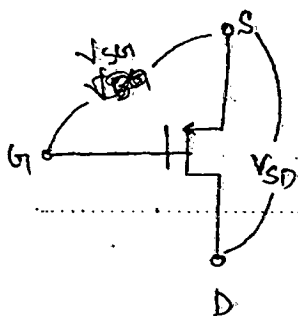

Current Saturation

$$I_D = K_p (V_{GS} - |V_t|)^2$$


Where, $K_p = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L} \right)$

Triode Region

$$I_D = 2K_p \left\{ V_{GS} - |V_t| \right\} V_{SD} - \frac{1}{2} V_{SD}^2$$

□ MOSFET BIASING

1. VOLTAGE DIVIDER BIAS

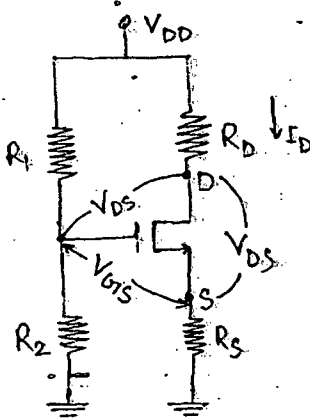

Current Saturation

$$V_{DS} > V_{GS} - V_t$$

$$V_{DS} = V_{GS} + V_{DS}$$


$$V_{DS} > V_{GS}$$

$$I_D = K_n (V_{GS} - V_t)^2$$

Assume $(I_D)_Q = 1 \text{ mA}$

$$(V_{GS})_Q = \sqrt{\frac{(I_D)_Q}{K_n}} + V_t$$

2. DRAIN TO GATE FEEDBACK BIAS

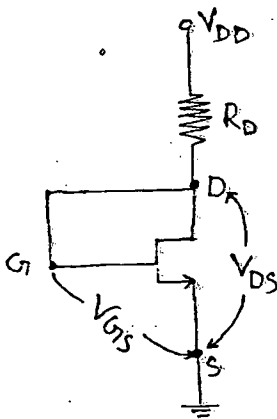

$$V_{DS} = V_{GS}$$


$$V_{DS} > V_{GS} - V_t$$

$$(V_{DS})_Q = V_{DD} - (I_D)_Q R_D$$

$$(V_{GS})_Q = V_{DD} - (I_D)_Q R_D$$

$$I_D = K_n (V_{GS} - V_t)^2$$

□ NMOS INVERTER

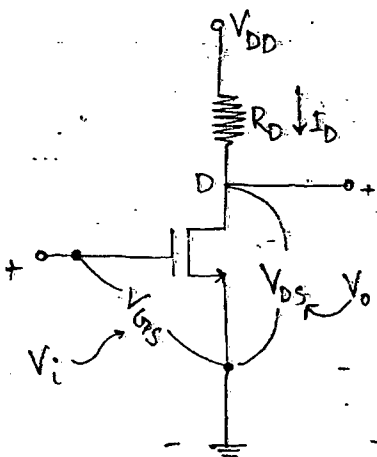

$$V_o = V_{DD} - I_D R_D$$

When $V_i < V_t$


T_{OFF} , $I_D = 0$

$$V_o = V_{DD}$$

When $V_i > V_t$

Current Saturation

$$V_o > V_i - V_t$$

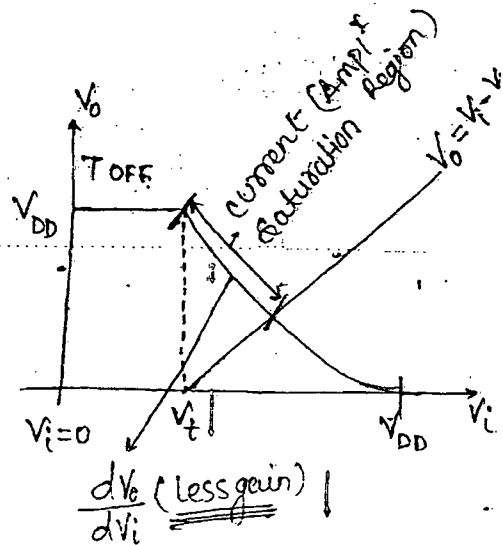

$$I_D = K_n (V_{GS} - V_t)^2$$

$$= K_n (V_i - V_t)^2$$

$$V_o = V_{DD} - K_n (V_i - V_t)^2 R_D$$

$$V_o = V_{DD} - 2K_n \left\{ (V_i - V_t) V_o - \frac{1}{2} V_o^2 \right\} R_D$$

Boundary for Triode Region.

$$V_{DS} = V_{GS} - V_t$$


$$V_o = V_i - V_t$$

When $V_o < V_i - V_t$

$$I_D = 2K_n \left\{ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right\}$$

$$I_D = 2K_n \left\{ (V_i - V_t) V_o - \frac{1}{2} V_o^2 \right\}$$

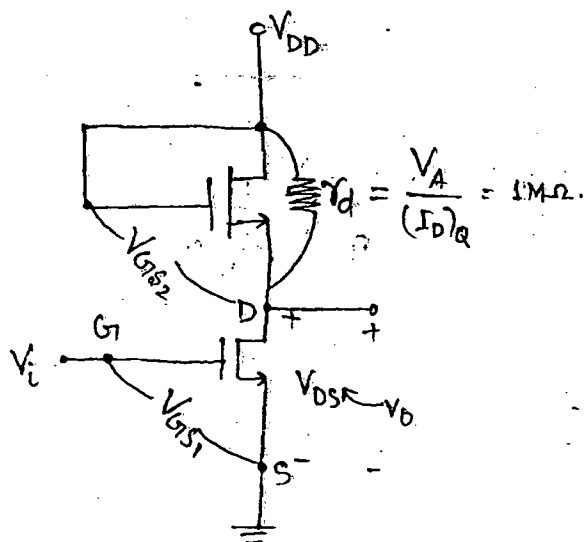□ N MOS INVERTER WITH ACTIVE LOAD (INTEGRATED)




$$A_v = -g_m R_D$$

$$= -g_m r_d$$

$$= -4 \text{ mS} \times 1 \text{ M}\Omega$$

$$= -4000$$

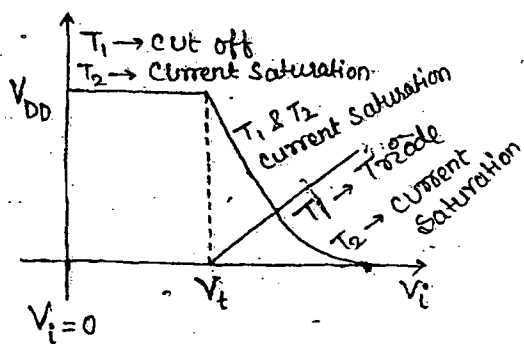


$$V_i > V_t$$

T_1 & T_2 are in current saturation

$$K_1 (V_{GS1} - V_t)^2 = K_2 (V_{GS2} - V_t)^2$$

$$K_1 (V_i - V_t)^2 = K_2 (V_{DD} - V_o - V_t)^2$$
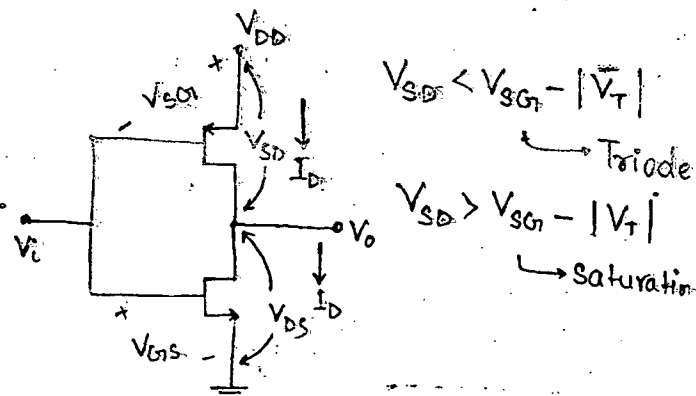
$$V_o = V_{DD} - V_t - \sqrt{\frac{K_1}{K_2}} (V_i - V_t)$$




Boundary for current saturation

$$V_{SD} = V_{SG1} - |V_T|$$

$$V_{DD} - V_0 = V_{DD} - V_{th} - |V_T|$$

$$V_0 = V_i + |V_T|$$

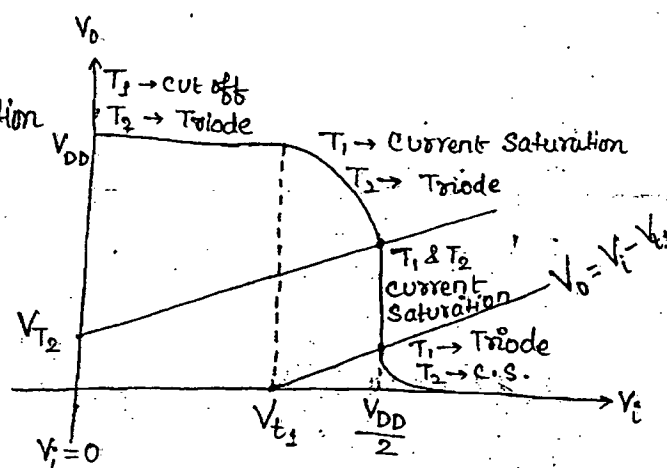

$$K_1 = K_2$$

$$V_{t_1} = V_{t_2}$$

$$V_L = \frac{V_{DD}}{2}$$

When T_1 & T_2 are current saturation

$$K_1 (V_{GS} - V_{T1})^2 = K_2 (V_{SG} - |V_{T1}|)^2$$

$$K_1 (V_i - V_{T1}) = K_2 (V_{DD} - V_i - |V_T|)$$