
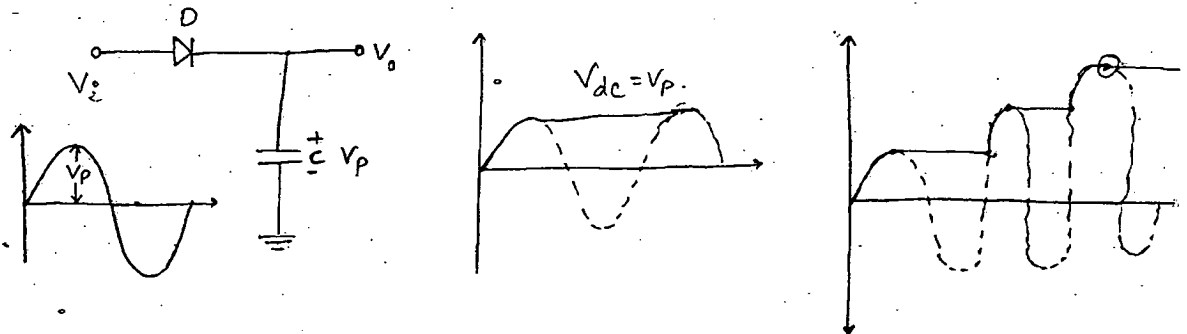


□ PEAK DETECTOR, CLAMPER AND VOLTAGE MULTIPLIER.


POSITIVE PEAK DETECTOR.

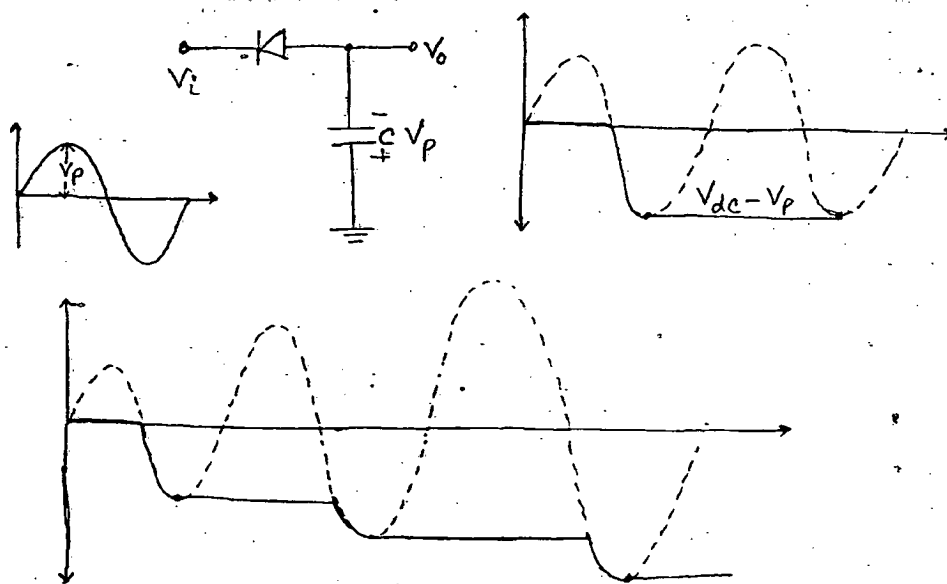


NEGATIVE PEAK DETECTOR.





CLAMPER NEGATIVE

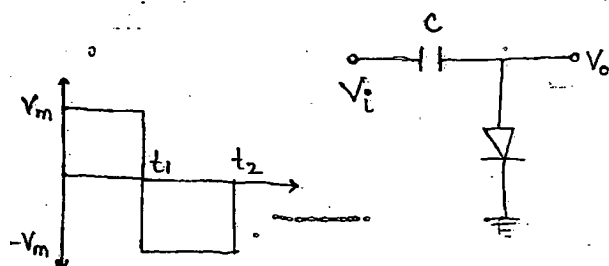

case: 0 to t_{j1}


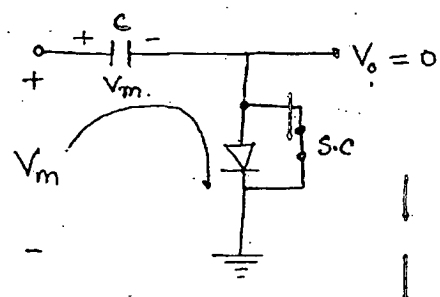


case II:- t_1 to t_2

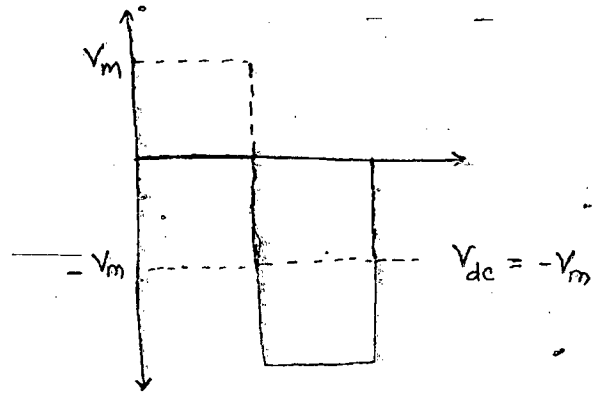
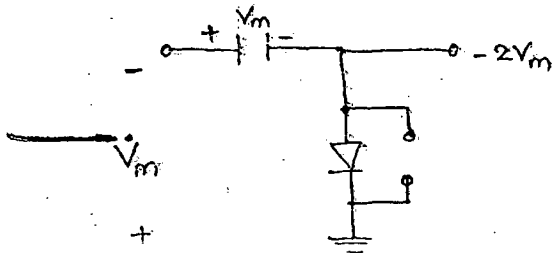


POSITIVE CLAMPER.

case I:- t_1 to t_2

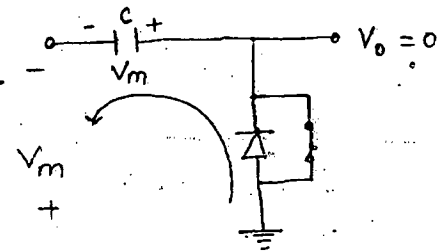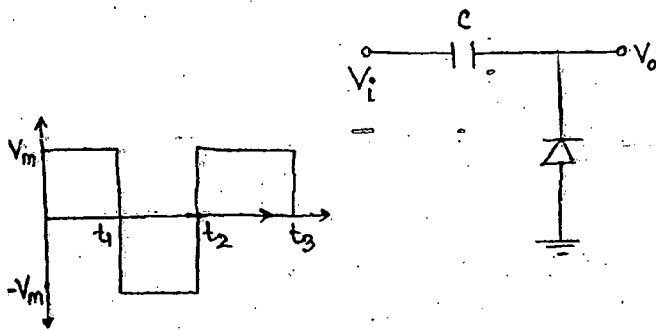

case II:- t_2 to t_3

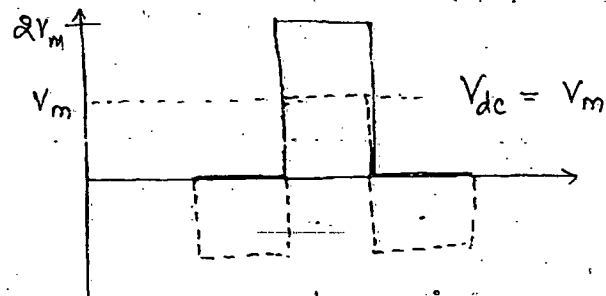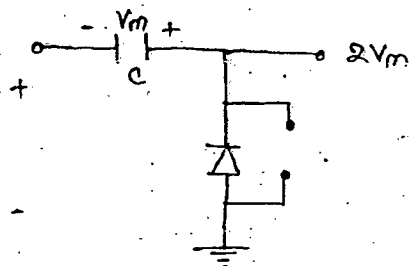


NOTE:- During 0 to t_1 capacitor will charge V_m only $\therefore$ 0 to t_1 it is neglected.


TECHNIQUES IN CLAMPERS

- * When the diode is in downward direction the total s/g will be clamped below the reference voltage.
- * When the diode is in upward direction the total s/g will be clamped above the reference voltage.


QUESTION :-

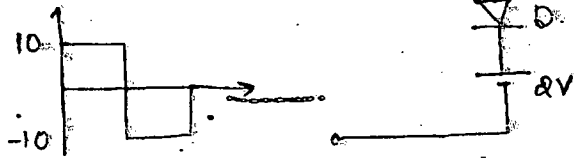


SOLUTION :-

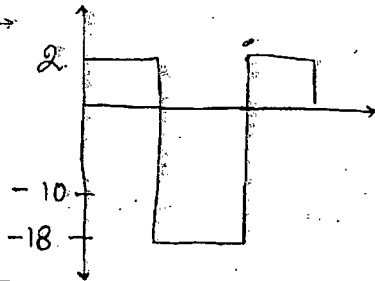

QUESTION :-


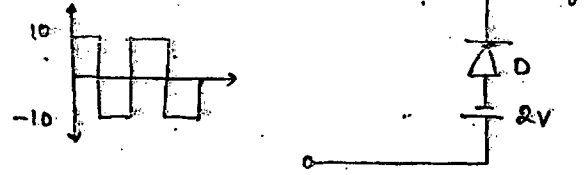


SOLUTION :-


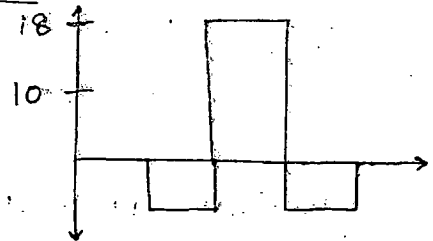


□ PRACTICAL CLAMPER DESIGN.


IDEAL CLAMPER.

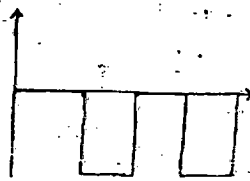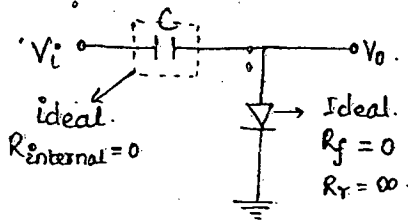

PRACTICAL CLAMPER.

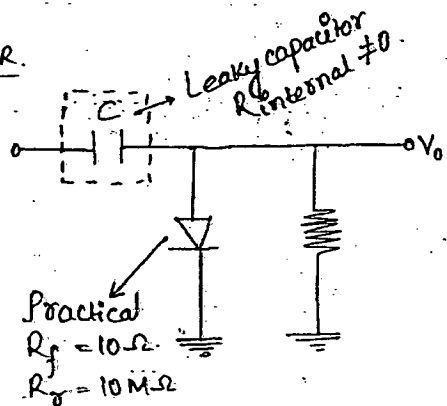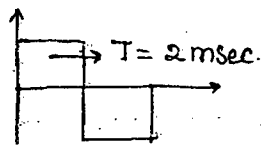


t_1 to t_2

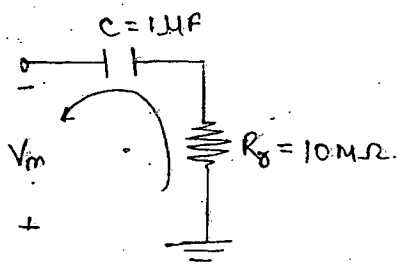

$$T_{R_r} = C \times R_r$$

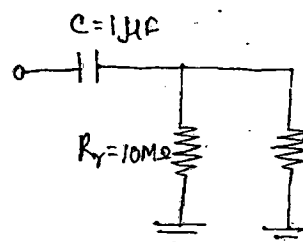
$$= 1 \mu F \times 10 \times 10^6 = 10 \text{ sec.}$$



* Geometric Mean, $\epsilon = \sqrt{ab}$

$$R = \sqrt{R_f R_r} = \sqrt{10 \times 10 \times 10^6} = 10 K\Omega.$$

t_2 to t_1

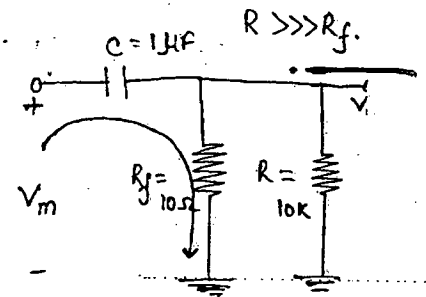

$$\text{Time constant} = C \times R_f \parallel R$$

$$= C \times R_f = 1 \mu F \times 10 \Omega$$

$$= 10 \mu \text{ sec.}$$


$$T_R = C \times R_r \parallel R$$

$$= C \times R$$

$$= 1 \mu F \times 10 \times 10^5$$


$$= 10 \text{ msec}$$

(-)VE VOLTAGE MULTIPLIER.

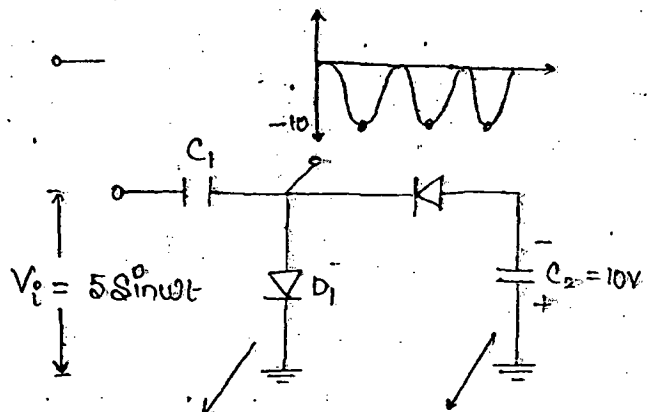

Negative clamper + Negative peak detector = Negative Voltage multiplier


POSITIVE VOLTAGE MULTIPLIER.

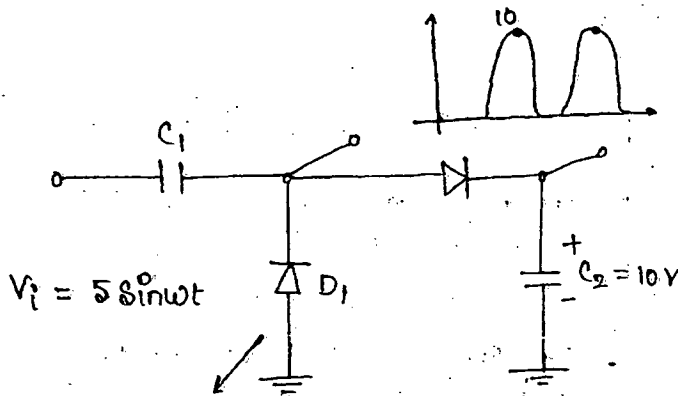


Positive clamper + Positive peak detector = Positive Voltage Multiplier

□ RECTIFIER

HALF-WAVE VOLTAGE DOUBLER


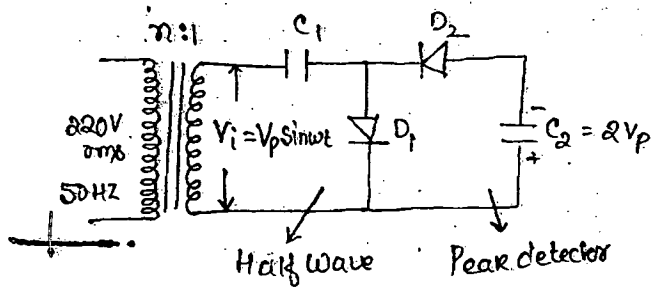


FULL WAVE VOLTAGE DOUBLER

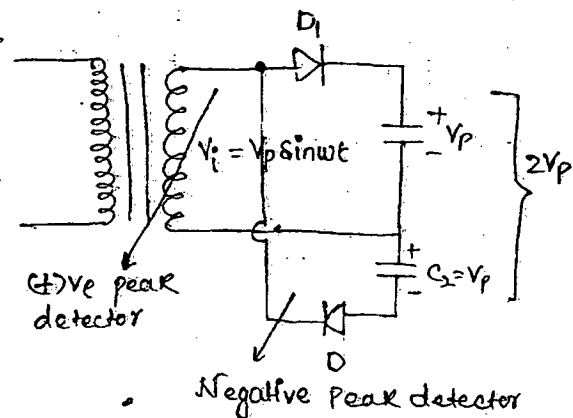


Ques: → Design a voltage multiplier crt which generates n multiples of DC.

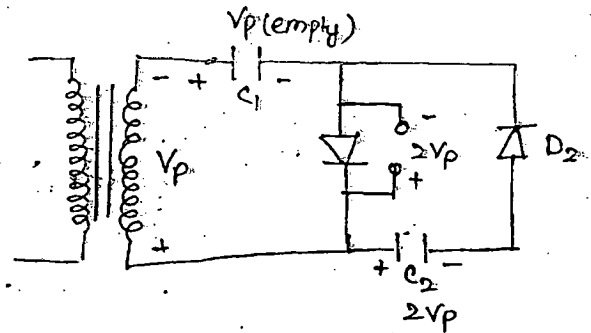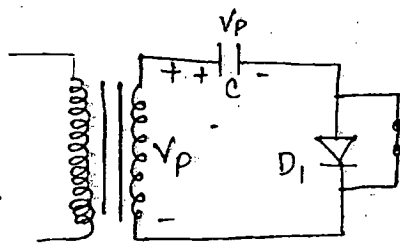
Solⁿ: → Step 1 :- 1st cycle (+)ve half Step 2 :- 1st cycle (-)ve half




Step 3 :- 2nd cycle (+)ve half

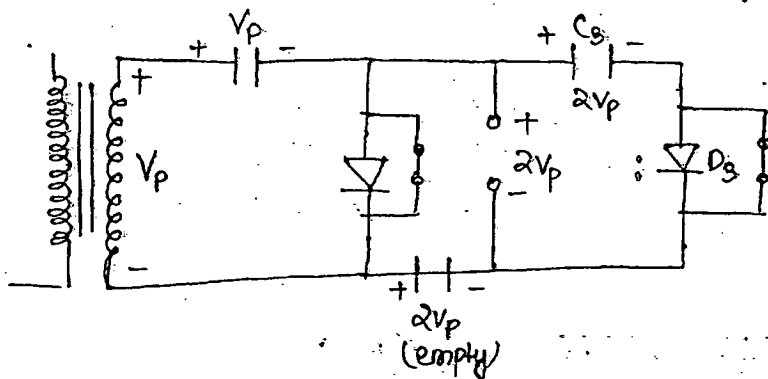

Step 4 :- 2nd cycle (-)ve half

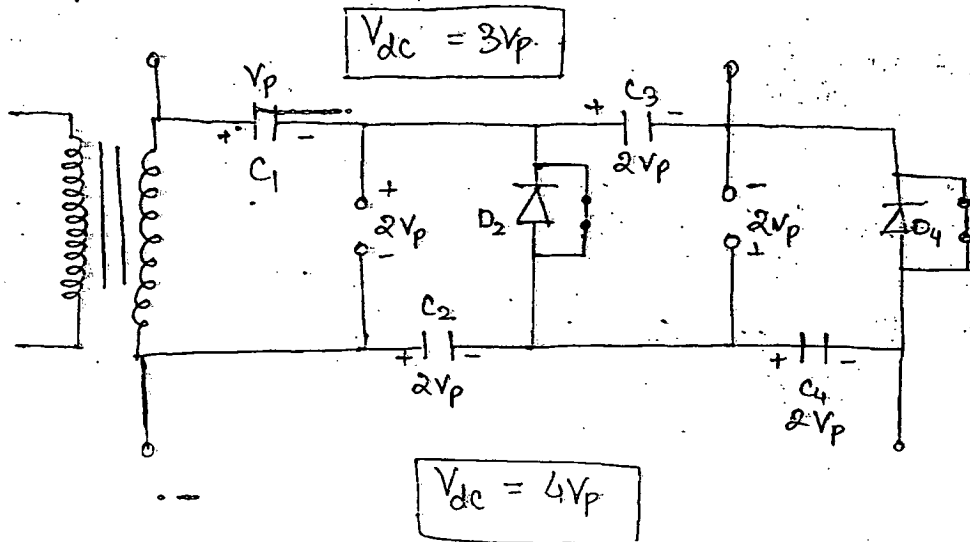

QUESTION:-

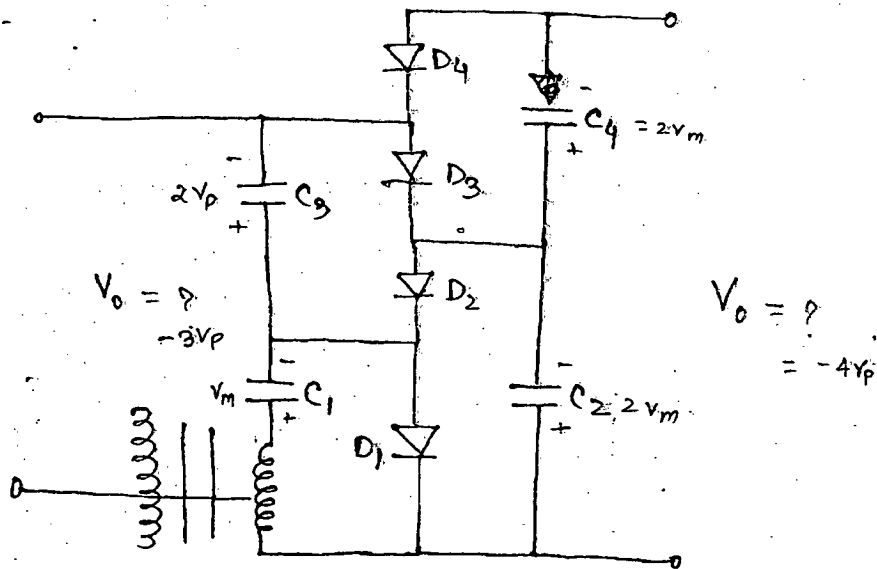


SOLUTION :->

□ DIGITAL LOGIC GATE

OR LOGIC

$$A + B = C$$


A	B	C
0	0	0
0	1	1
1	0	1
1	1	1

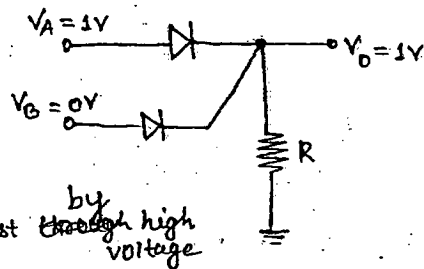


AND LOGIC

$$A \cdot B = C$$

A	B	C
0	0	0
0	1	0
1	0	0
1	1	1

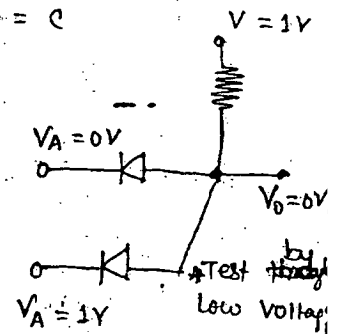


QUESTION :->

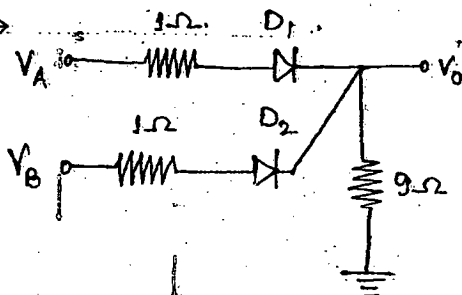


SOLUTION :->


Case I :- $V_A = 10V, V_B = 0V$

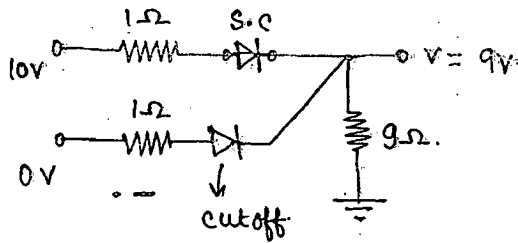


Case II :- $V_A = 10V, V_B = 5V$

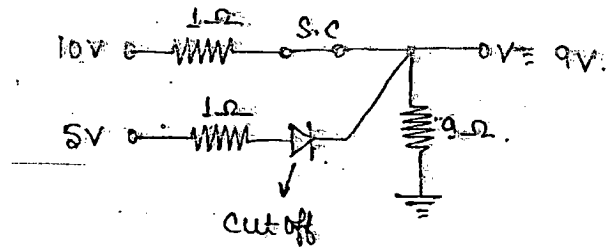

Case III :- $V_A = 10V, V_B = 10V$

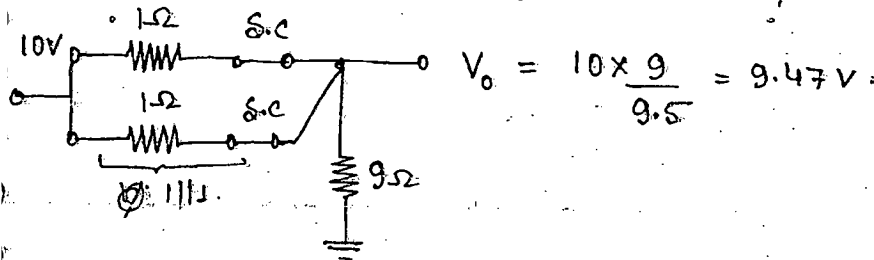


QUESTION :-

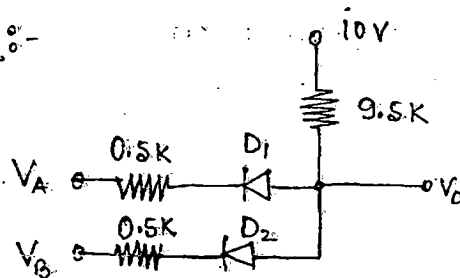


SOLUTION :-


Case I :- $V_A = 10V, V_B = 0V$

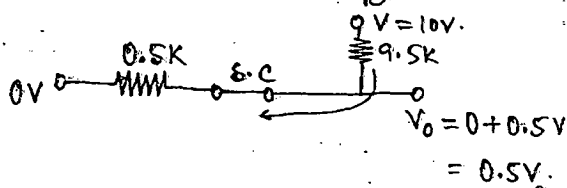

Case II :- $V_A = 10V, V_B = 5V$

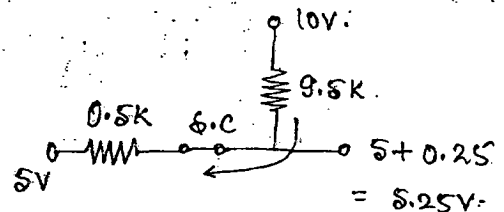



Case III :- $V_A = 0, V_B = 0$

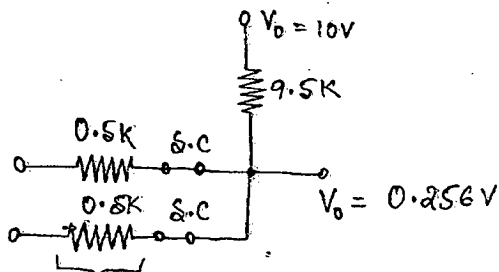


TECHNIQUES IN DIGITAL LOGIC GATE

- * For OR Logic gate we have to test with high input.
- * For AND Logic gate we have to test with low input.


□ ANALOGY GATE / SAMPLING GATE

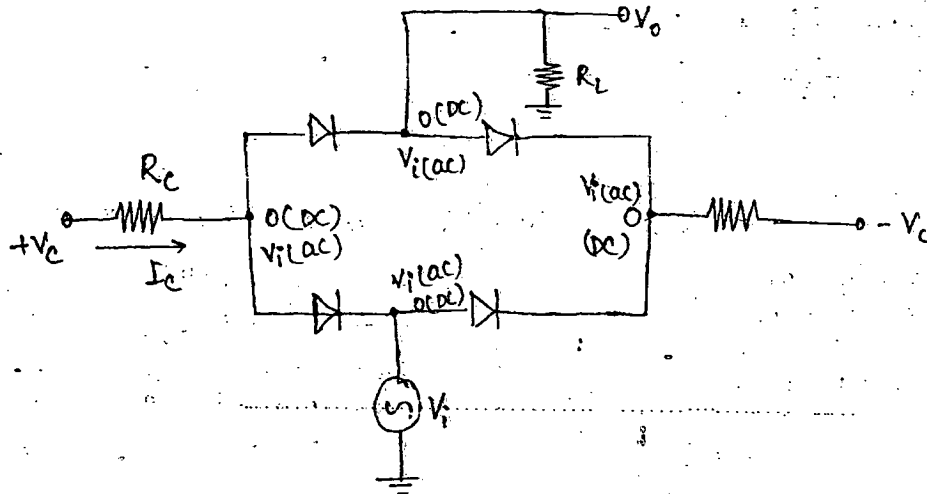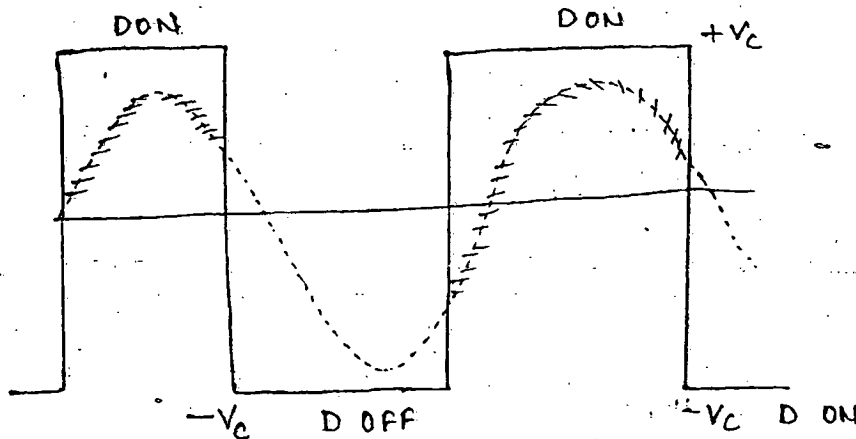


DC Analysis :-

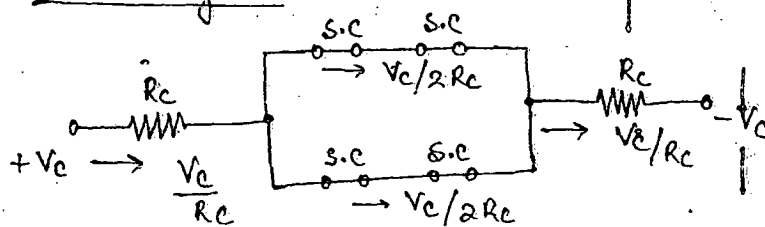

AC Analysis

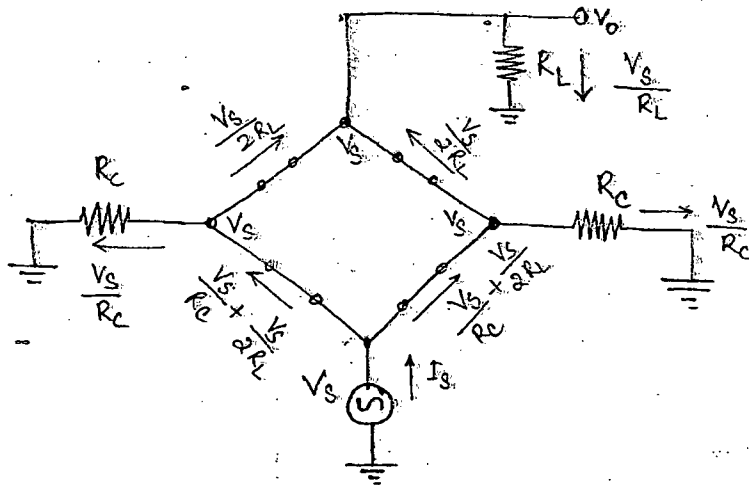

DC + AC Analysis

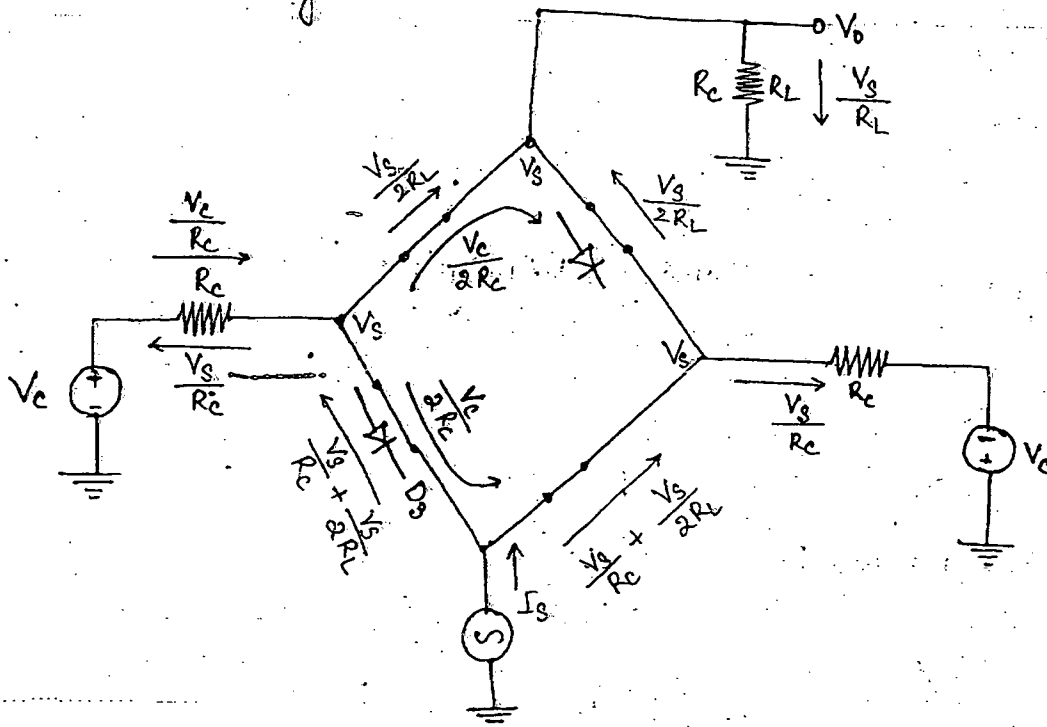

$$V_c > 2R_c \left[\frac{1}{R_c} + \frac{1}{2R_L} \right] V_s \quad \text{*condition for } D_3 \text{ switch to be "ON"}$$

$$V_c > 3V_s$$

$$\frac{V_c}{2R_c} > \frac{V_s}{R_c} + \frac{V_s}{2R_L} =$$


$$V_c > 2R_c \left[\frac{1}{R_c} + \frac{1}{2R_L} \right] V_s$$

$$R_L = R_c$$

• SMALL SIGNAL ANALYSIS OF A DIODE.

DIODE RESISTANCE

STATIC RESISTANCE

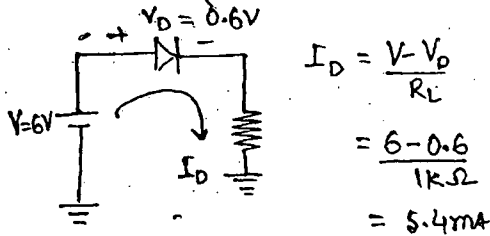


$$R_D = \frac{V_D}{I_D} \rightarrow \text{DC Resistance}$$

$$R_D = \frac{0.6V}{5.4mA}$$


$$R_D = 111\Omega$$

DYNAMIC RESISTANCE

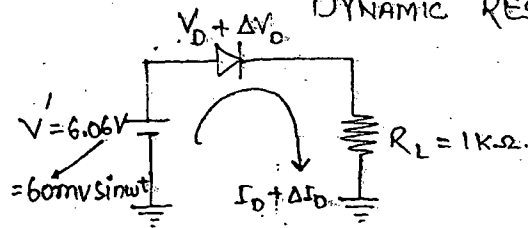

$$r_D = \frac{\Delta V_D}{\Delta I_D} \rightarrow \text{AC Resistance.}$$

Analysis of Static Resistance:-

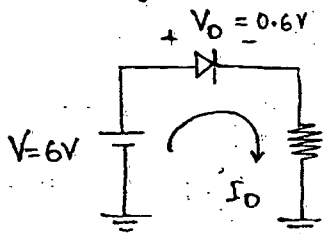

Mathematical Analysis:-


$$I_D = \frac{V - V_D}{R_L} = \frac{6 - 0.6}{1k\Omega} = 5.4mA$$

GRAPHICAL METHOD:-

$$I_D = \frac{V - V_D}{R_L}$$

$$I_D = \left(-\frac{1}{R_L} \right) V_D + \frac{V}{R_L}$$

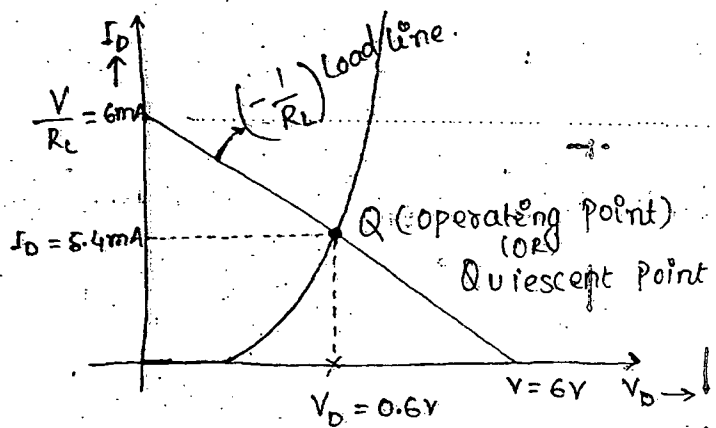
$\downarrow$ $\downarrow$ $\downarrow$
 y m $x + C$



$$R_D = \frac{V_D}{I_D} = \frac{0.6}{5.4mA} = 111\Omega$$

QUESTION :- Suppose there is a small variation in ac supply ($V_i = 60 \text{ mV sinwt}$). The DC Voltage $V = 6 \text{ V}$ changed to $V' = 6.06 \text{ V}$. Calculate new diode current I_D' and diode Voltage V_D' .

SOLUTION :-

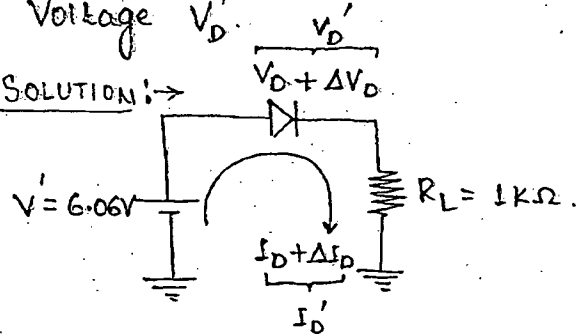

$$V' = V + \Delta V$$

$\downarrow \quad \downarrow \quad \downarrow$
 $6.06 \text{ V} \quad 6 \text{ V} \quad 0.06 \text{ V}$


$$V_D' = V_D + \Delta V_D$$

$\downarrow \quad \downarrow \quad \downarrow$
 $? \quad 0.6 \text{ V} \quad ?$

$$I_D' = I_D + \Delta I_D$$

$\downarrow \quad \downarrow \quad \downarrow$
 $? \quad 5.4 \text{ mA} \quad ?$

GRAPHICAL ANALYSIS.

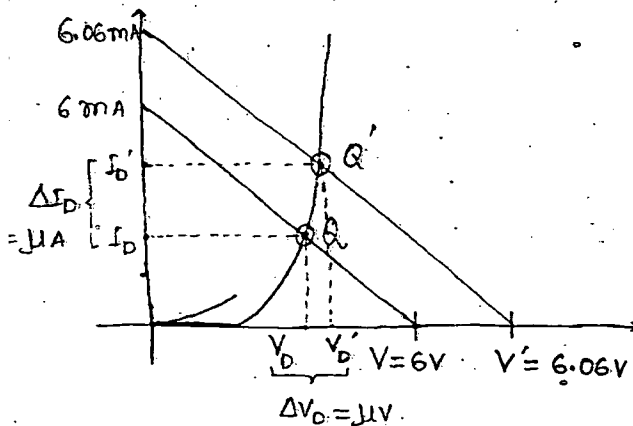

NOTE :- For Small Signal Analysis of a device (diode, BJT, FET, MOSFET). Graphical analysis is not best method because the Variation of the device will be in μA & μV . So mathematical Analysis is best.

MATHEMATICAL ANALYSIS.

$$I_D = I_0 e^{V_D/V_T}$$

(DC)

$$I_D + \Delta I_D = I_0 \cdot e^{(V_D + \Delta V_D)/V_T}$$

$$I_D + \Delta I_D = \frac{I_0 \cdot e^{V_D/V_T}}{I_D(\text{DC})} \cdot e^{\Delta V_D/V_T}$$

$$I_D + \Delta I_D = I_0 \cdot e^{\Delta V_D/V_T}$$

$$\Delta V_D = 0.06 \text{ V}$$

$$V_T = mV$$

$$e^{\Delta V_D / V_T} = e^x = 1 + x$$


$$= 1 + \frac{\Delta V_D}{V_T} \rightarrow \text{Linear.}$$

$$I_D + \Delta I_D = I_D \left[1 + \frac{\Delta V_D}{V_T} \right]$$

$$\cancel{I_D} + \Delta I_D = \cancel{I_D} + I_D \frac{\Delta V_D}{V_T}$$

$$\boxed{r_D = \frac{\Delta V_D}{\Delta I_D} = \frac{V_T}{I_{D(DC)}} = \frac{26mV}{5.4mA} = 5\Omega}$$

AC MODEL

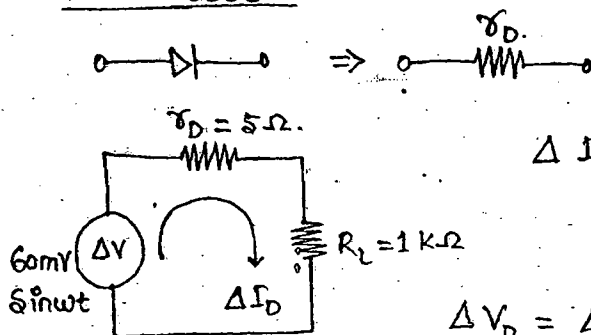


$$\Delta I_D = \frac{\Delta V}{R_L + r_D} = \frac{60mV \sin wt}{1k\Omega} = 60\mu A \sin wt$$

$$\Delta V_D = \Delta I_D + r_D = 60\mu A \sin wt \times 5\Omega$$

$$\Delta V_D = 300\mu V \sin wt$$


Ch-2
Q3.

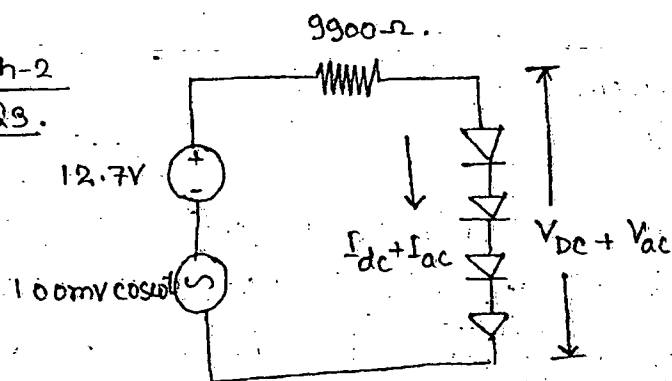

$$I_{dc} = ?$$


$$V_{ac} = ?$$

DC Model.

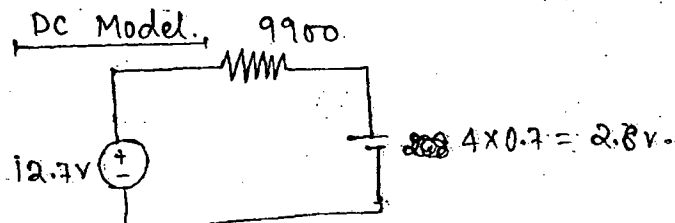

$$I_{dc} = \frac{12.7 - 2.8}{9900} = 1mA$$

AC Model.

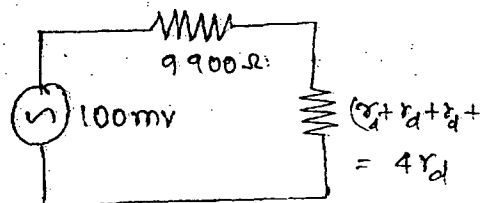


$$r_d = \frac{V_T}{I_{dc}} = \frac{25mV}{1mA} = 25\Omega$$

$$4r_d = 100 \Omega$$

$$V_{ac} = \frac{100 \text{ mV} \cos \omega t \times 100}{10,000} = 1 \text{ mV} \cos \omega t$$

□ RECTIFIER

Block Diagram.

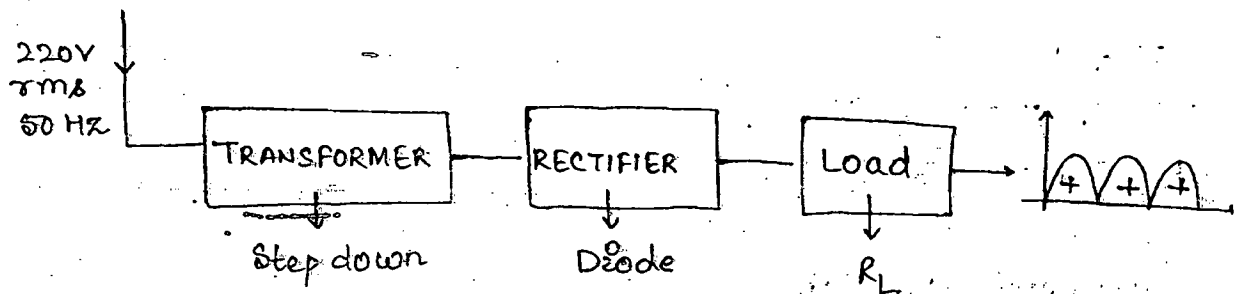

DEFINITION :- Rectifier is a circuit which convert ac to Pulsating DC.




→ PRACTICAL RECTIFIER DESIGN.

1. HALF WAVE RECTIFIER
2. FULL WAVE RECTIFIER WITH CENTRE TAPPED
3. FULL WAVE RECTIFIER WITHOUT CENTRE TAPPED (BRIDGE).

→ RECTIFIER PARAMETER.

1. Average current, I_{dc}
2. DC o/p voltage, V_{dc}
3. RMS load current, I_{rms}
4. Ripple Factor.
5. Voltage Regulation.
6. Rectification Efficiency, η .
7. Transformer utilization factor (TUF)
8. Peak Inverse Voltage (PIV)
9. Form factor
10. Peak factor.

☐ HALF WAVE RECTIFIER.

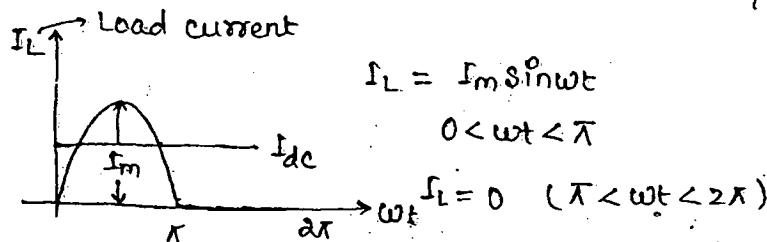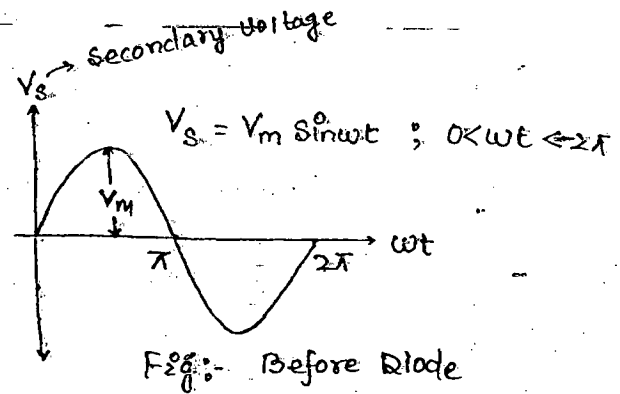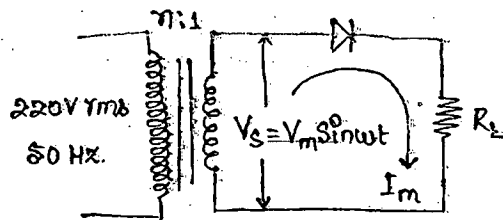

Parameter calculation:-

1. $I_{dc} = \frac{\text{Area under the curve}}{2\pi}$


$$I_{dc} = \frac{1}{2\pi} \int_0^{2\pi} I \cdot d\alpha \rightarrow \text{where } \alpha = \omega t.$$

$$1. \quad I_{dc} = \frac{1}{2\pi} \int_0^{\pi} I_m \cdot \sin \alpha \, d\alpha = \frac{I_m}{2\pi} \int_0^{\pi} \sin \alpha \, d\alpha$$

$$I_{dc} = \frac{I_m}{\pi}$$

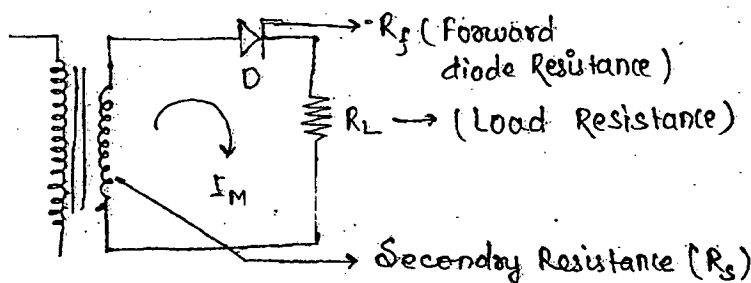2. $V_{dc} = I_{dc} \times R_L$


$$V_{dc} = \frac{I_m}{\pi} \times R_L \quad ; \quad V_{dc} = \frac{V_m}{\pi (R_f + R_s + R_L)} \cdot R_L$$



$$V_{dc} = \frac{V_m}{\pi} \cdot \frac{1}{\frac{R_f + R_s}{R_L} + 1} \quad \text{When } R_L = \infty$$

$$(V_{dc})_{NL} = \frac{V_m}{\pi}$$

3. I_{RMS} .

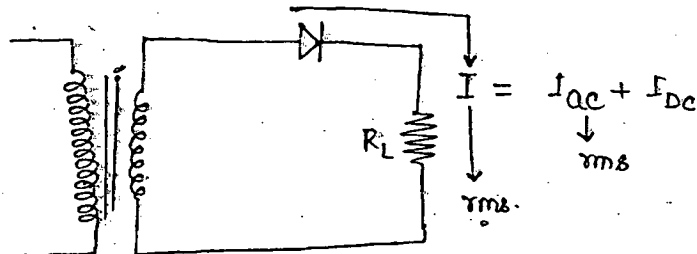

$$I_{rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I^2 d\alpha}$$


$$I_{rms} = \sqrt{\frac{I_m^2}{2\pi} \int_0^{\pi} \sin^2 \alpha d\alpha}$$

$$I_{rms} = \frac{I_m}{2} \rightarrow \text{FOR H.W.R.}$$

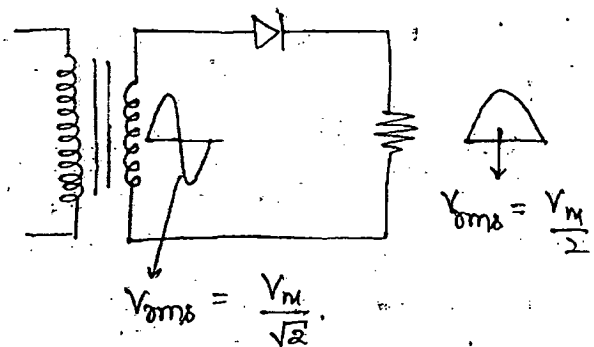4. V_{rms} .

$$V_{rms} = \frac{V_m}{\sqrt{2}} \rightarrow \text{across Load } (R_L)$$

$$V_{rms} = \frac{V_m}{\sqrt{2}} \rightarrow \text{Transformer (Secondary)}$$




14.5

5. RIPPLE FACTOR.

$$R.F = \frac{\text{RMS Value of alternating component}}{\text{Average Value}}$$

$$R.F = \frac{I_{ac rms}}{I_{dc}}$$

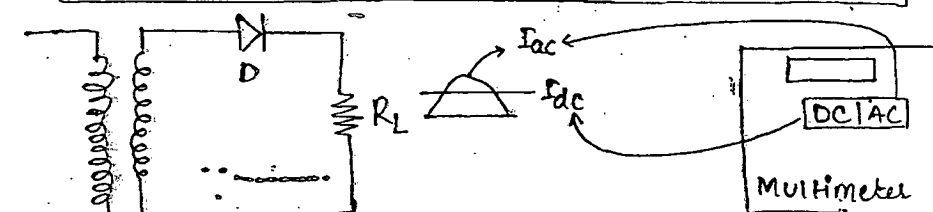

Assume

I_{ac} = Ac current ; I_{dc} = dc current.

I = Total current ; $I_{ac rms}$ = Rms value of ac current.

$$I_{ac rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} I_{ac}^2 d\alpha}$$

$$\Rightarrow I_{dc} + I_{ac} = I$$

$$\Rightarrow I_{ac} = I - I_{dc}$$

$$I_{ac rms} = \sqrt{\frac{1}{2\pi} \int_0^{2\pi} (I - I_{dc})^2 d\alpha}$$

$$I_{ac rms}^2 = \underbrace{\frac{1}{2\pi} \int_0^{2\pi} I^2 d\alpha}_{I_{rms}^2} - 2 I_{dc} \cdot \underbrace{\frac{1}{2\pi} \int_0^{2\pi} I d\alpha}_{I_{dc}} + I_{dc}^2 \underbrace{\frac{1}{2\pi} \int_0^{2\pi} d\alpha}_{=1}$$


$$I_{ac rms} = \sqrt{I_{rms}^2 - I_{dc}^2}$$

$$R.F = \frac{I_{ac rms}}{I_{dc}} = \frac{\sqrt{I_{rms}^2 - I_{dc}^2}}{I_{dc}} = \sqrt{\left(\frac{I_{rms}}{I_{dc}}\right)^2 - 1}$$

for HWR:- $I_{rms} = \frac{I_m}{2}$; $I_{dc} = \frac{I_m}{\pi}$; $R.F = \sqrt{\left(\frac{I_m/2}{I_m/\pi}\right)^2 - 1}$

$R.F = 1.21 \rightarrow$ For HWR.

6. VOLTAGE REGULATION.

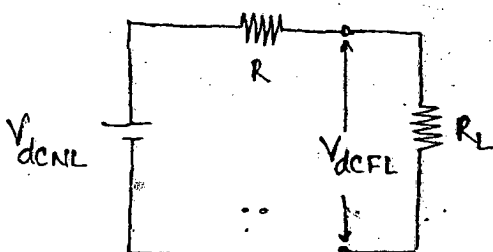

$$\% VR = \frac{V_{dcNL} - V_{dcFL}}{V_{dcFL}}$$

$$I_{dc} = \frac{I_m}{\pi} ; I_{dc} = \frac{V_m}{\pi (R_f + R_s + R_L)}$$


$$I_{dc}(R_f + R_s) + \underbrace{I_{dc} R_L}_{V_{dcFL}} = \underbrace{\frac{V_m}{\pi}}_{V_{dcNL}}$$

$$\left. \begin{array}{l} R_f = 0 \\ R_s = 0 \\ R_L = \infty \end{array} \right\} \rightarrow \text{Ideal}$$

$$\% VR = \frac{I_{dc}(R_f + R_s)}{I_{dc} R_L} ; \% V.R = \frac{R_f + R_s}{R_L}$$

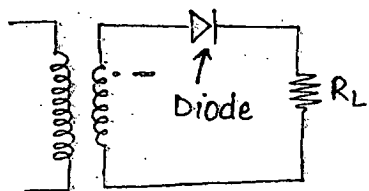7. RECTIFICATION EFFICIENCY (η) 8. T.U.F.


$$\eta = \frac{P_{d.c}}{P_{a.c}} = \frac{I_{dc}^2 R_L}{V_{rms} \times I_{rms}}$$



$$\eta = \frac{I_{dc}^2 R_L}{\left(\frac{V_m}{2}\right) \times \frac{I_m}{2}} = \frac{\left(\frac{I_m}{\pi}\right)^2 R_L}{\frac{I_m^2}{4} (R_f + R_s + R_L)}$$

$$\eta = \frac{4}{\pi^2} = 40.6\%$$


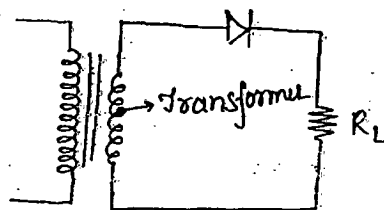
$$T.U.F = \frac{P_{d.c}}{P_{a.c}} = \frac{I_{dc}^2 R_L}{V_{rms} \times I_{rms}}$$



$$T.U.F = \frac{I_{dc}^2 R_L}{\left(\frac{V_m}{\sqrt{2}}\right) \times \frac{I_m}{2}}$$

$$T.U.F = \frac{2\sqrt{2}}{\pi^2} = 28\%$$

9. PEAK INVERSE VOLTAGE:

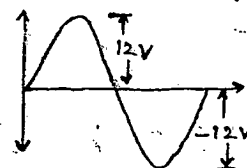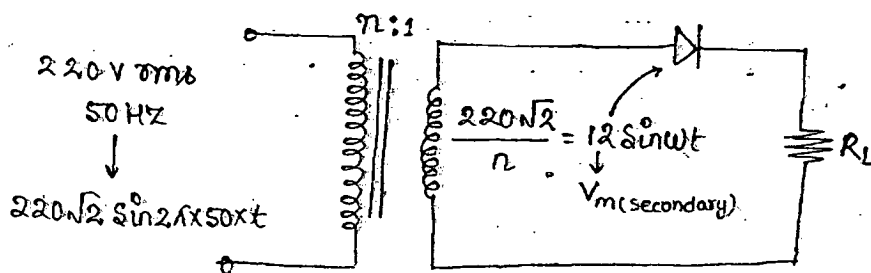

$$PIV = V_m$$

Where. V_m = Secondary V_m .

10. Form factor = $\frac{\text{Rms Value}}{\text{Average Value}}$

$$F.F = \frac{I_{rms}}{I_{dc}}$$

$$F.F = \frac{I_m/2}{I_m/\pi} = \frac{\pi}{2} = 1.57$$

FOR H.W.R.

$$I_{rms} = F.F \times I_{dc}$$

11. Peak Factor = $\frac{\text{Peak Value}}{\text{Rms Value}}$

$$P.F = \frac{I_m}{I_{rms}}$$

$$I_m = I_{rms} \times \text{Peak Factor}$$

□ FULL WAVE RECTIFIER.

→ CENTRE TAPPED.

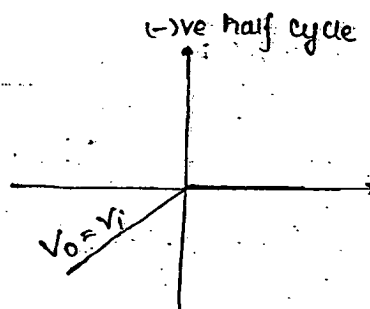
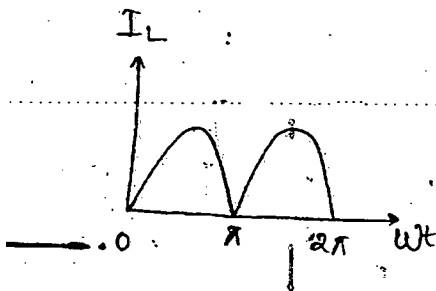
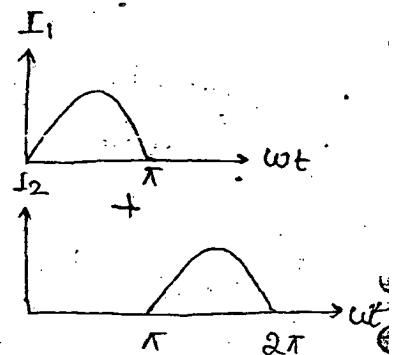
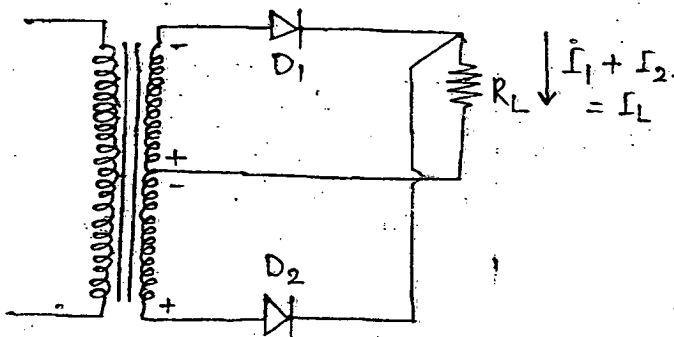


Fig:- CLIPPER

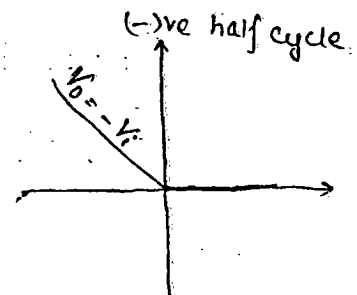


Fig:- RECTIFIER.

RECTIFIER PARAMETER

$$1. I_{dc} = \frac{2 \cdot I_m}{\pi}$$

$$2. V_{dcNL} = \frac{2 \cdot V_m}{\pi}$$

$$3. I_{rms} = \frac{I_m}{\sqrt{2}} ; V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$4. R.F = \sqrt{\frac{(I_{rms})^2}{(I_{dc})^2} - 1} = \sqrt{\left(\frac{I_m/\sqrt{2}}{2I_m/\pi}\right)^2 - 1} = 0.48$$

$$R.F = 0.48$$

5. Voltage Regulation.


$$-\frac{2I_m}{\pi} (R_f + \frac{R_s}{2}) + \frac{2I_m}{\pi} \cdot R_L = \frac{2V_m}{\pi}$$

6. Rectification Efficiency.

$$\eta = \frac{P_{DC}}{P_{ac}} = \frac{I_{dc}^2 \cdot R_L}{V_{rms} \cdot I_{rms}} = \frac{I_{dc} \cdot R_L}{I_{rms} (R_f + R_s + R_L)} = \frac{(2I_m/\pi)^2}{(I_m/\sqrt{2})^2}$$

$$\eta = \frac{8}{\pi^2} = 81.2\%$$

7. Transformer UTILIZATION FACTOR.

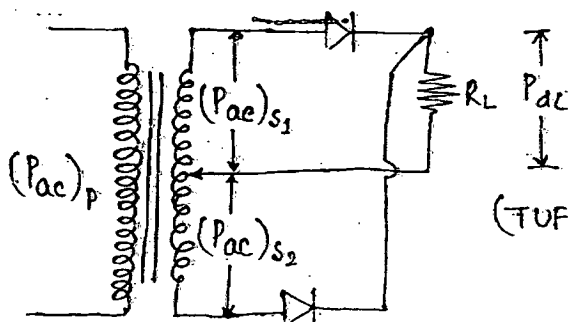

$$(T.U.F)_p = \frac{P_{DC}}{(P_{ac})_p} = \eta = 81.2\%$$

$$(T.U.F)_s = \frac{P_{DC}}{P_{ac \text{ sec one half}} + P_{ac \text{ sec other half}}}$$

$$(T.U.F)_s = \frac{I_{dc}^2 \cdot R_L}{V_{rms} \times I_{rms} + V_{rms} \times I_{rms}}$$


$$(TUF)_S = \frac{I_{dc}^2 R_L}{\frac{V_m}{\sqrt{2}} \times \frac{I_m}{2} + \frac{V_m}{\sqrt{2}} \times \frac{I_m}{2}} = 57.3\%$$

$$(TUF)_S = 57.3\%$$

$$(TUF) = \frac{(TUF)_P + (TUF)_S}{2} = \frac{81.2 + 57.3}{2}$$

$$TUF = 69.3\%$$

8. Peak Inverse Voltage (PIV)

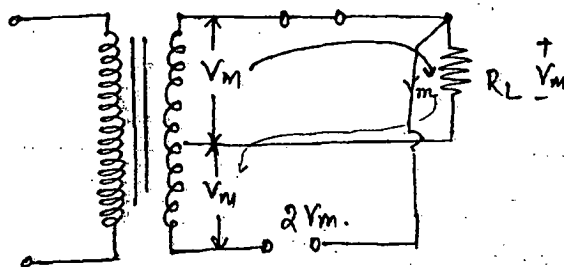


$$PIV = 2V_m$$

→ DRAWBACKS IN CENTRE TAPPED.

* The TUF is not equal to Rectification Efficiency because of centre Tapped.

* The PIV rating is high.

□ BRIDGE RECTIFIER.

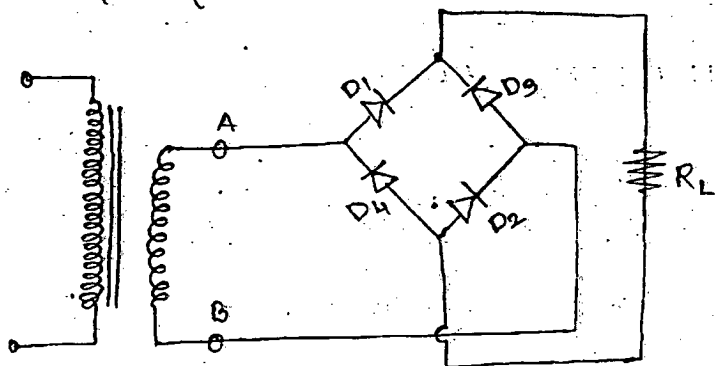

(+ve) Half cycle

Conduction path

A D_1 R_L D_2 B

D_1 and $D_2 \rightarrow ON$

D_3 and $D_4 \rightarrow OFF$


(-ve) half cycle

Conduction path

B D_3 R_L D_4 A

D_3 and $D_4 \rightarrow ON$

D_1 and $D_2 \rightarrow OFF$

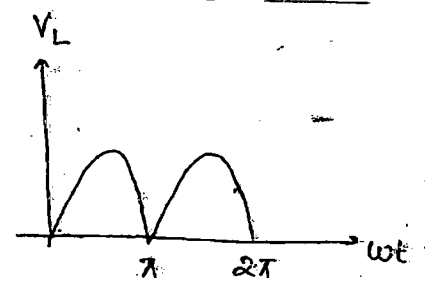

→ Common parameter as full wave Rectifier.

1. $I_{dc} = \frac{2 \cdot I_m}{\pi}$

2. $V_{dcNL} = \frac{2 \cdot V_m}{\pi}$

3. $I_{rms} = \frac{I_m}{\sqrt{2}}$; $V_{rms} = \frac{V_m}{\sqrt{2}}$

4. R.F = 0.48.

5. Rectification Efficiency, $\eta = 81.2\%$.

→ Different parameter in Bridge Rectifier.

6. % Voltage Regulation =


$$\frac{\frac{2I_m}{\pi} (R_f + \frac{R_s}{2}) + \frac{2I_m}{\pi} R_L}{\frac{2V_m}{\pi}} = \frac{2V_m}{\pi}$$

7. Transformer utilization factor (TUF)

$$TUF = \frac{(TUF)_P + (TUF)_S}{2} = \frac{81.2 + 81.2}{2} = 81.2\%$$

8. PIV = V_m .

□ FILTER.

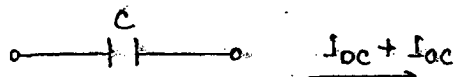
CAPACITOR $\rightarrow$ 


$$X_C \propto \frac{1}{f}$$

$$f = 0 \text{ (DC)} ; X_C \rightarrow \infty \text{ (O.C)}$$

$$f = \infty \text{ (AC)} ; X_C \rightarrow 0 \text{ (S.C)}$$

$$R.F \propto \frac{1}{R_L}$$

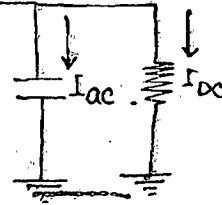

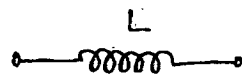
INDUCTOR $\rightarrow$ 

$$X_L \propto f$$

$$f = 0 \text{ (DC)} ; X_L \rightarrow 0 \text{ (S.C)}$$

$$f = \infty \text{ (AC)} ; X_L \rightarrow \infty \text{ (O.C)}$$

$$R.F \propto R_L$$

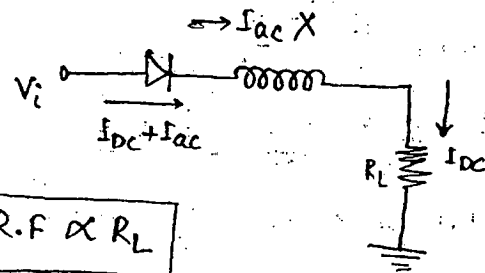


$\therefore$ Not used.

FOR ONLY.
IES-conv.

□ CAPACITANCE FILTER DESIGN (HWR).

Requirements :- V_{dc} across the $R_L = 12 \text{ V}$.

Load current $I_L = 10 \text{ mA}$

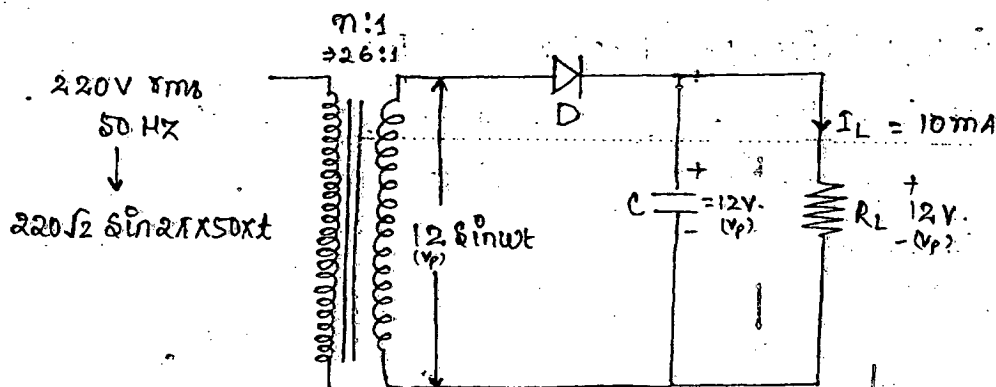

1. Turn Ratio :-


$$\frac{220\sqrt{2}}{n} = 12 \Rightarrow n = \frac{220\sqrt{2}}{12} \Rightarrow n = 26.$$

2. Voltage across the capacitor = 12V.

$$3. R_L = \frac{V_{dc}}{I_L} = \frac{12}{10\text{mA}} = 1.2\text{K}\Omega.$$

$$4. T = \frac{1}{f} = \frac{1}{50\text{Hz}} = 20\text{msec}.$$

5. Ripple waveform.

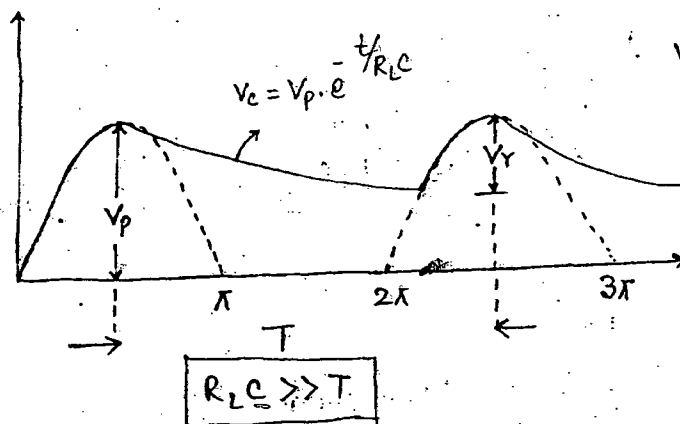


$$V_c = V_p \cdot e^{-t/R_L C}$$

$$V_c = V_p \left(1 - \frac{T}{R_L C}\right)$$

$$V_c = V_p - \frac{V_p \cdot T}{R_L \cdot C}$$

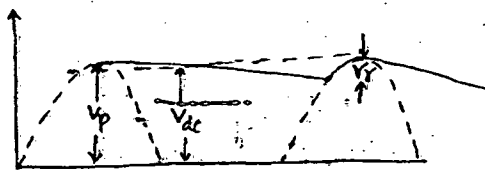
$\downarrow \quad \quad \downarrow$
 $V_{dc} \quad \quad V_r$



$$V_{dc} \approx V_p$$

$$V_r = \frac{V_p \cdot T}{R_L C} = \frac{V_r}{2} \quad (\text{Ripple to be eliminated})$$

Expression for Ripple factor :-

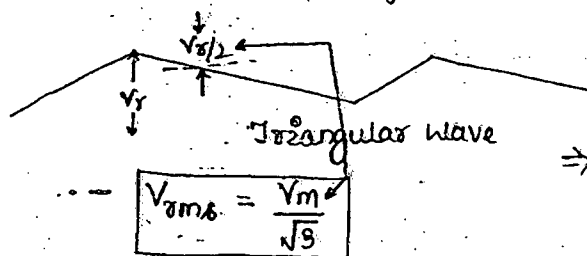


$$R.F = \frac{V_{rms}}{V_{dc}} = \frac{\frac{V_r}{2\sqrt{3}}}{V_p}$$

$$\Rightarrow R.F = \frac{V_p \cdot T}{2\sqrt{3} \cdot R_L \cdot C}$$

$$\Rightarrow R.F = \frac{1}{2\sqrt{3}} \cdot \frac{1}{R_L \cdot f \cdot C}$$

6. Conduction Time (Δt)

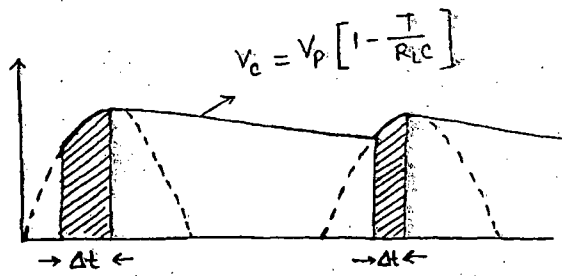

$$V_p \cos \omega \Delta t = V_p \left[1 - \frac{T}{R_L C} \right]$$

$\Delta t \rightarrow$ is very small.

$$\cos \theta = 1 - \frac{\theta^2}{2!}$$


$$\sin \theta = \theta - \frac{\theta^3}{3!}$$

$$V_p \left[1 - \frac{(\omega \Delta t)^2}{2} \right] = V_p \left[1 - \frac{T}{R_L C} \right]$$

$$(\omega \Delta t)^2 = \frac{2T}{R_L C}$$

$$\Delta t = \frac{1}{\omega} \sqrt{\frac{2T}{R_L C}}$$

7. Peak current of Diode Rating.

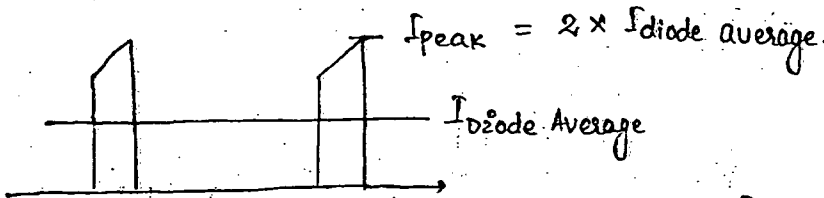

$$I_{\text{diode average}} = I_c \text{ average} + I_L$$

$$I_{\text{diode avg}} = C \frac{dv_c}{dt} + \frac{V_{dc}}{R_L}$$

$$I_c \text{ avg} \times \Delta t = C \times V_T$$

$$I_c \text{ avg} = \frac{C \times \frac{V_p}{R_L C}}{\Delta t}$$


$$I_c \text{ avg} = I_{dc} \cdot \frac{\pi}{2} \sqrt{\frac{R_L C}{2T}}$$

$$\Rightarrow I_c \text{ avg} = I_{dc} \times \frac{\pi}{2} \sqrt{\frac{R_L C}{2T}}$$

$$I_{\text{diode avg}} = I_{dc} \left[1 + \frac{\pi}{2} \sqrt{\frac{R_L C}{2T}} \right]$$

$$= 0.5$$


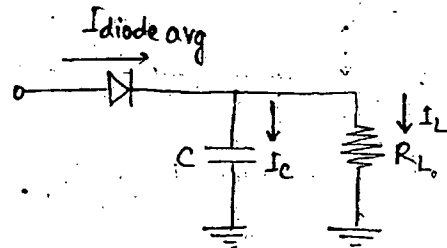
$$\text{Peak current of diode} = 2 I_{\text{diode avg}}$$



Peak current of diode $= 2 I_{dc} \left[1 + 2\pi \sqrt{\frac{R_L \cdot C}{2\pi}} \right] = 14$

8. ^{1st} PIV Rating of diode $= 2V_m$

□ FILTER DESIGN (FWR)

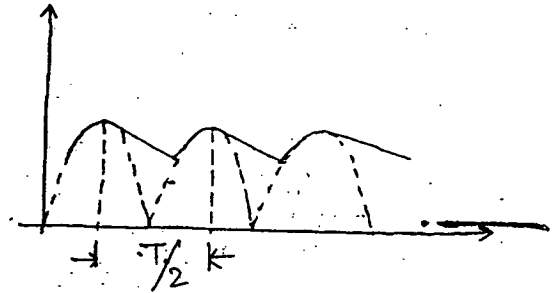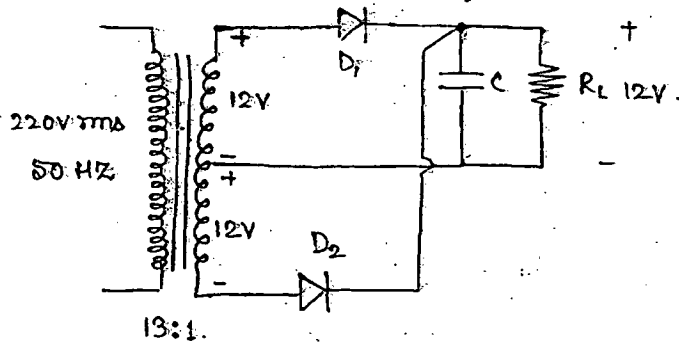


$R.F = \frac{1}{2\sqrt{3} \cdot R_L \cdot f \cdot C} \rightarrow \text{H.W.R.}$


$R.F = \frac{1}{4\sqrt{3} R_L \cdot f \cdot C} \rightarrow \text{F.W.R.}$

NOTE :- The ripple frequency of HWR $= f$


The ripple frequency of FWR and BR $= 2f$

□ ZENER DIODE AS A REGULATOR.

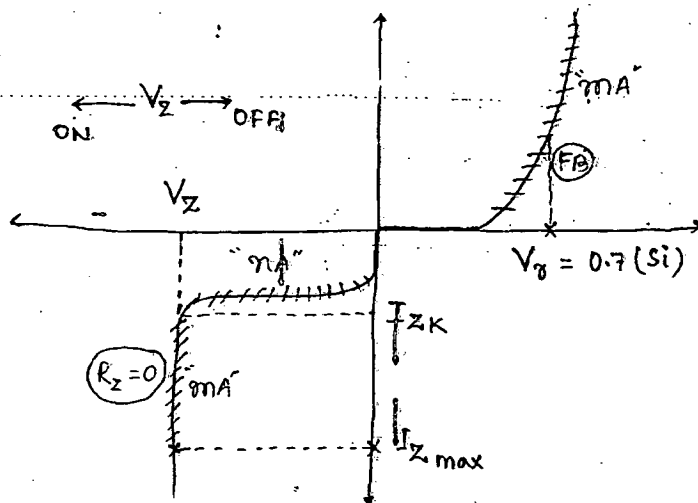

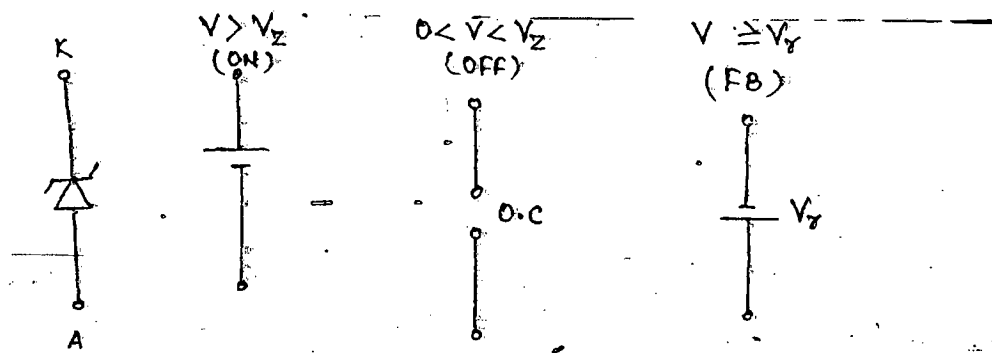

□ ZENER REGULATOR DESIGN

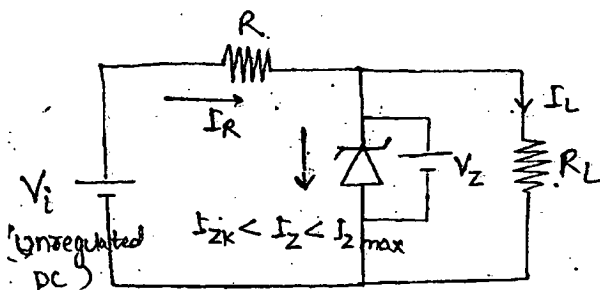


$$I_R = I_Z + I_L$$

* I_L is due Zener:
 $\therefore I_L$ does n't depend on I_R .

Design

- V_i Fixed & R_L fixed
- V_Z Variable & R_L fixed
- V_Z fixed & R_L variable
- V_Z and R_L are variable.

Cases:- V_i fixed and R_L fixed.

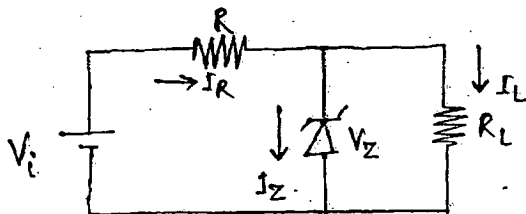


$$I_R = I_Z + I_L$$

$$I_Z = I_R - I_L$$

$$I_Z = \frac{V_i - V_Z}{R} - \frac{V_Z}{R_L}$$

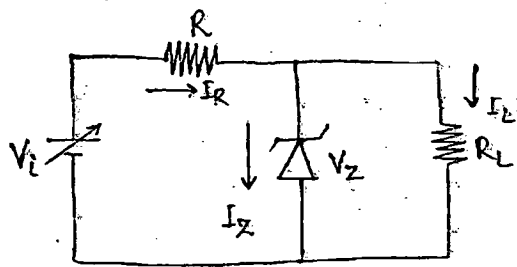Case II :- V_i is variable and R_L fixed.



$$I_R = I_Z + I_L$$

$$I_{Rmin} = I_{Zmin} + I_L$$


$$I_{Zmin} = \frac{V_{imin} - V_Z}{R} - \frac{V_Z}{R_L}$$

$$I_{Rmax} = I_{Zmax} + I_L$$

$$I_{Zmax} = I_{Rmax} - I_L$$

$$I_{Zmax} = \frac{V_{imax} - V_Z}{R} - \frac{V_Z}{R_L}$$

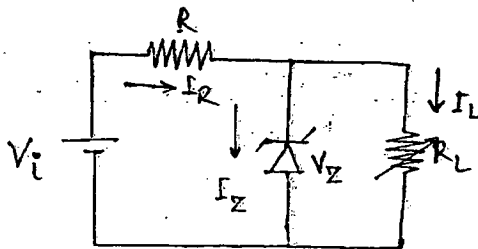Case III :- V_i is fixed and R_L is variable.



$$I_R = I_Z + I_L$$

$$I_R = I_{Zmin} + I_{Lmax}$$

$$I_{Zmin} = I_R - I_{Lmax}$$


$$I_R = I_{Zmax} + I_{Lmin}$$

$$I_{Zmax} = I_R - I_{Lmin}$$

$$I_{Zmin} = \frac{V_i - V_Z}{R} - \frac{V_Z}{R_{Lmin}}$$

$$I_{Zmax} = \frac{V_i - V_Z}{R} - \frac{V_Z}{R_{Lmax}}$$

Case IV :- V_i and R_L is variable.

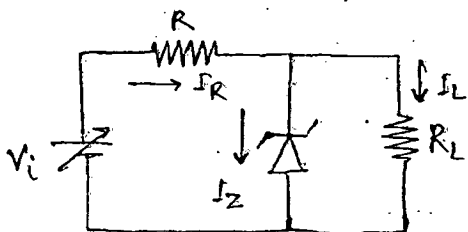

$$I_R = I_Z + I_L$$

$$I_{Rmin} \neq I_{Rmax} \quad I_{Rmin} = I_{Zmin} + I_{Lmax}$$

$$I_{Zmin} = I_{Rmin} - I_{Lmax}$$


$$I_{Rmax} = I_{Zmax} + I_{Lmin}$$

$$I_{Zmin} = \frac{V_{imin} - V_Z}{R} - \frac{V_Z}{R_{Lmin}}$$

$$I_{Zmax} = \frac{V_{imax} - V_Z}{R} - \frac{V_Z}{R_{Lmax}}$$

QUESTION :- Design a Zener diode voltage Regulator of Regulated Voltage 6V for a load current variation of 1mA to 20mA. The unregulated DC Voltage is 10V to 15V.
Zener Specification :- $I_{ZK} = 0.1\text{mA}$; $I_{Z\text{max}} = 50\text{mA}$.

SOLUTION :-

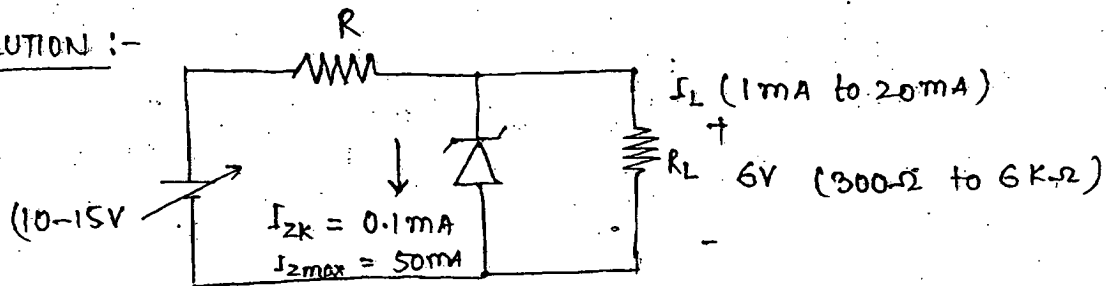

$$\Rightarrow I_{R\text{min}} - I_{L\text{max}} > I_{Z\text{min}}$$

$$\Rightarrow \frac{V_{i\text{min}} - V_Z}{R_{\text{max}}} - I_{L\text{max}} > 0.1\text{mA} \quad \Rightarrow \frac{10-6}{R_{\text{max}}} - 20\text{mA} > 0.1\text{mA}$$


$$R_{\text{max}} < 199\Omega$$

$$\Rightarrow I_{R\text{max}} - I_{L\text{min}} < I_{Z\text{max}}$$

$$\Rightarrow \frac{V_{i\text{max}} - V_Z}{R_{\text{min}}} - I_{L\text{min}} < 50\text{mA} \quad \Rightarrow \frac{15-6}{R_{\text{min}}} - 1\text{mA} < 50\text{mA}$$

$$\Rightarrow R_{\text{min}} > 176\Omega$$

□ ZENER LOAD LINE.

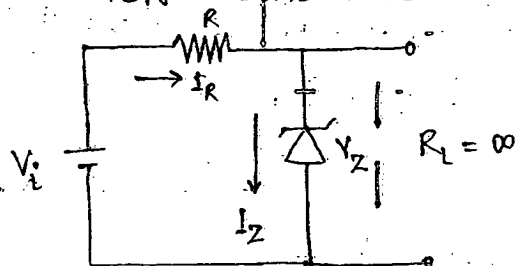


$$V_i = I_R R + V_Z$$


$$I_R = I_Z$$

$$V_i = I_Z R + V_Z$$
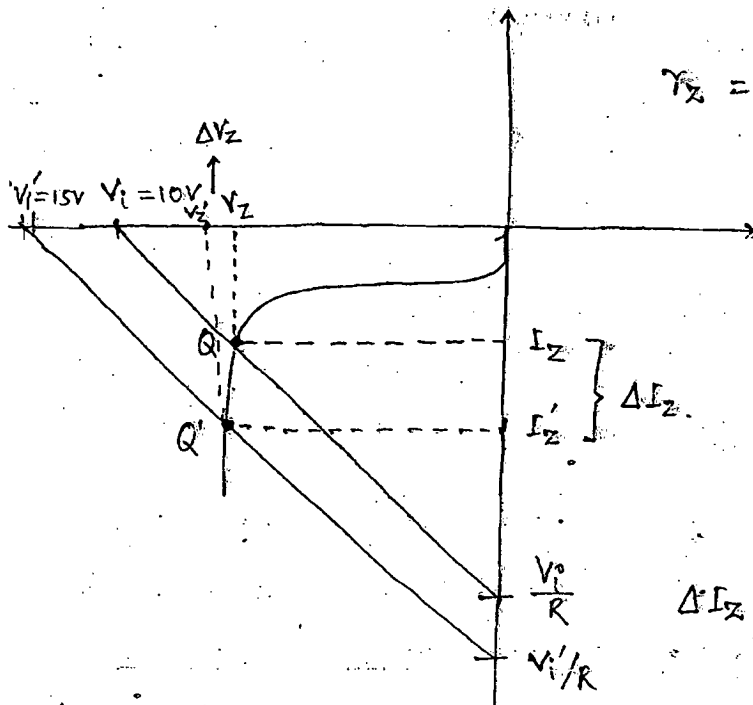
$$I_Z = \left[-\frac{1}{R} \right] V_Z + \frac{V_i}{R}$$


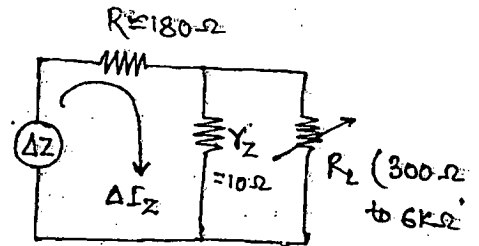
$$r_Z = \frac{\Delta V_Z}{\Delta I_Z} = 10\Omega$$



$$\Delta I_Z = \frac{\Delta V}{R + r_Z \parallel R_L} = \frac{\Delta V}{R + r_Z} = \frac{\Delta V}{R}$$

$$\Delta V_Z = \Delta I_Z \times r_Z$$

$$= \frac{\Delta V}{R} \times r_Z$$

$$\Delta V_Z = \frac{5V}{180} \times 10 = 0.27V$$

Ans: 0.27V