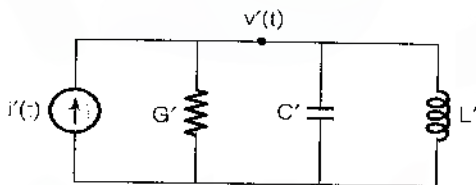


Series RLC circuit ( $N_1$ )

By applying KVL,

$$v(t) = Ri(t) + L \frac{di(t)}{dt} + \frac{1}{C} \int_0^t i(t) dt$$



Parallel RLC circuit ( $N_2$ )

By applying KCL,

$$i'(t) = v'(t) G' + C' \frac{dv'(t)}{dt} + \frac{1}{L'} \int_0^t v'(t) dt$$

- The networks  $N_1$  and  $N_2$  are called dual networks but these networks are not equivalent networks and therefore, the network  $N_1$  cannot be replaced by  $N_2$  network.
- The KVL equation for network  $N_1$  has similar format as for the KCL equation for network  $N_2$ . Therefore, if the response of the first network is known in terms of current  $i(t)$  then the response of its dual network for voltage  $v'(t)$  can be directly written without actually solving it by using necessary transformation by various elements as follows:

$N_1$	$N_2$
$v(t)$	$i(t)$
R	G
G	R
L	C
C	L
KVL	KCL