


# 4

## BJT Biasing



### Multiple Choice Questions

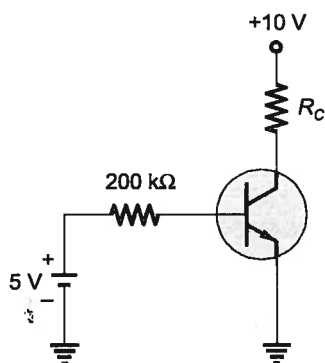**Q.1** A silicon transistor with  $V_{BE_{sat}} = 0.8 \text{ V}$ ,  $\beta_{dc} = 100$  and  $V_{CE_{sat}} = 0.2 \text{ V}$  is used in the circuit shown below:




What is the minimum value of  $R_C$  for which transistor is in saturation?

- (a)  $4286 \Omega$  (b)  $4667 \Omega$   
(c)  $5000 \Omega$  (d)  $1000 \Omega$

[ESE-2004 (EE)]

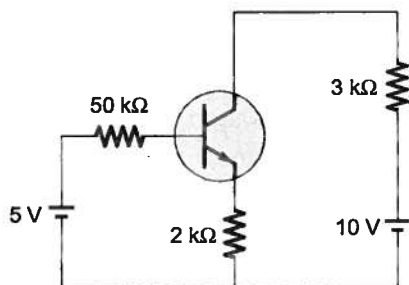
**Q.2** For the circuit shown in figure, assume  $\beta = h_{FE} = 100$ . The transistor is in



- (a) Active region and  $V_{CE} = 5 \text{ V}$   
(b) Saturation region  
(c) Active region and  $V_{CE} = 1.42 \text{ V}$   
(d) Cut-off region


[ESE-2005 (EE)]

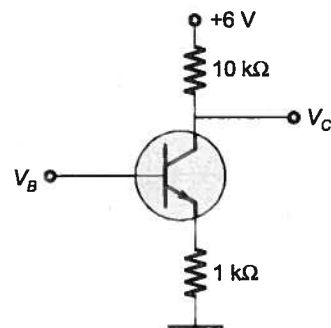**Q.3** For the transistor in circuit shown in figure  $\beta = 200$ . Determine  $V_C$  in the circuit if  $V_B = 2 \text{ V}$



- (a)  $-7 \text{ V}$  (b)  $1.5 \text{ V}$   
(c)  $2.6 \text{ V}$  (d) none

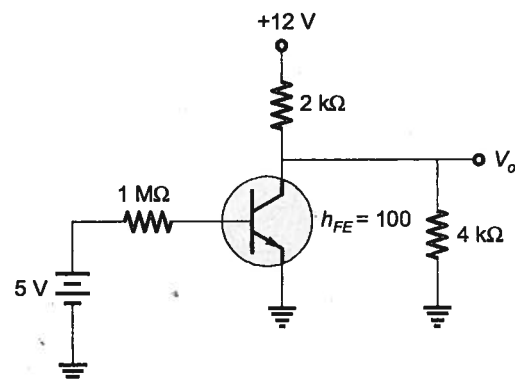**Q.4** Consider the NPN transistor circuit shown below:




What is the output voltage  $V_O$  in the above circuit?

- (a)  $0 \text{ V}$  (b)  $12 \text{ V}$   
(c)  $9 \text{ V}$  (d)  $7.5 \text{ V}$

[ESE-2004]

Q.5 Consider the following circuit:

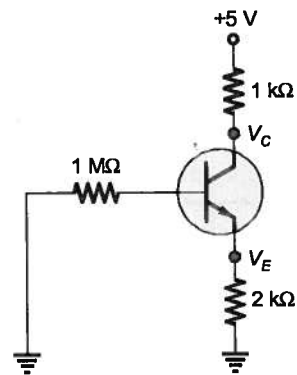


What is voltage difference between collector and emitter ( $V_{CE}$ ) in the above circuit?

- (a)  $10/3$  V (b) 0 V  
(c) 5 V (d) 3 V

[ESE-2004]


Q.6 In the circuit shown

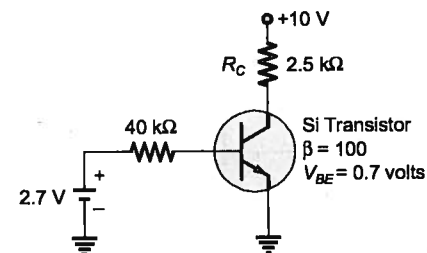

the transistor is biased at


- (a) 0 mA (b) 5 mA  
(c) 3.9 mA (d) ∞

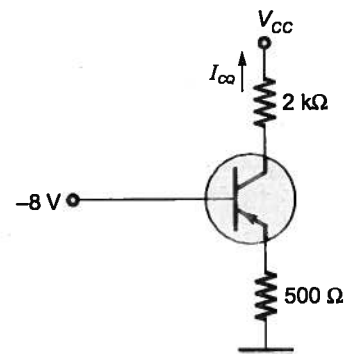Q.7 The transistor circuit shown in the figure given below is to function as an amplifier. If  $I_{CQ} = 3$  mA, what is the value of  $V_{CC}$  (approximate)?




- (a) 15 V (b) -15 V  
(c) -10 V (d) -13.5 V

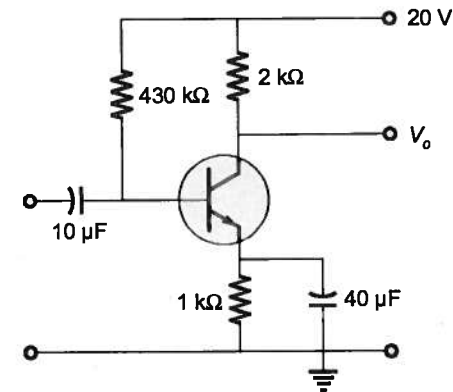Q.8 The circuit using a BJT with  $\beta = 50$  and  $V_{BE} = 0.7$  V is shown in the figure. The base current  $I_B$  and collector voltage  $V_C$  are respectively




- (a)  $43 \mu\text{A}$  and 11.4 Volts  
(b)  $40 \mu\text{A}$  and 16 Volts  
(c)  $45 \mu\text{A}$  and 11 Volts  
(d)  $50 \mu\text{A}$  and 10 Volts

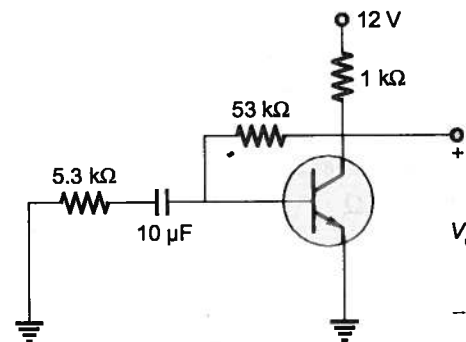Q.9 In the transistor amplifier circuit shown in the figure below, the transistor has the following parameters:  
 $\beta_{dc} = 60$ ,  $V_{BE} = 0.7$  V,  $h_{ie} \rightarrow \infty$ ,  $h_{fe} \rightarrow \infty$ .  
The capacitance  $C_C$  can be assumed to be infinite.




- (i) Find  $V_{CE}$   
(a) 3 V (b) 1.5 V  
(c) 6 V (d) 7.5 V
- (ii) If  $\beta_{dc}$  is increased by 10%, the collector-to-emitter voltage drop  
(a) increases by less than or equal to 10%  
(b) decreases by less than or equal to 10%  
(c) increases by more than 10%  
(d) decreases by more than 10%

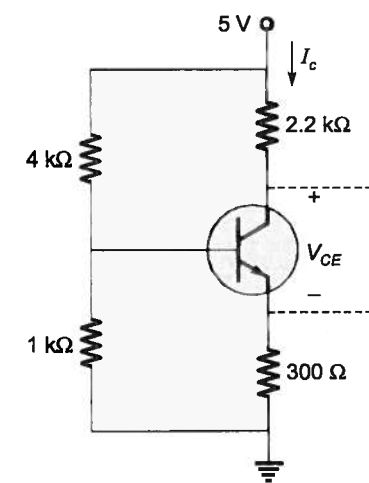Q.10 Assuming that the  $\beta$  of the transistor is extremely large and  $V_{BE} = 0.7$  V,  $I_C$  and  $V_{CE}$  in the circuit shown in the figure are



- (a)  $I_C = 1$  mA,  $V_{CE} = 4.7$  V  
(b)  $I_C = 0.5$  mA,  $V_{CE} = 3.75$  V  
(c)  $I_C = 1$  mA,  $V_{CE} = 2.5$  V  
(d)  $I_C = 0.5$  mA,  $V_{CE} = 3.9$  V

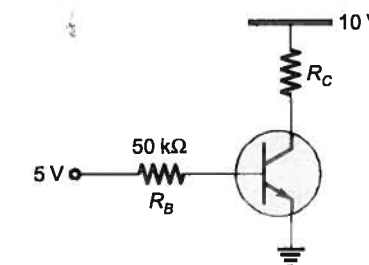
Q.11 In the circuit shown, the silicon BJT has  $\beta = 50$ . Assume  $V_{BE} = 0.7$  V and  $V_{CE(sat)} = 0.2$  V. Which one of the following statements is correct?



- (a) For  $R_C = 1$  kΩ, the BJT operates in the saturation region  
(b) For  $R_C = 3$  kΩ, the BJT operates in the saturation region  
(c) For  $R_C = 20$  kΩ, the BJT operates in the cut-off region  
(d) For  $R_C = 20$  kΩ, the BJT operates in the linear region

[GATE-2014]

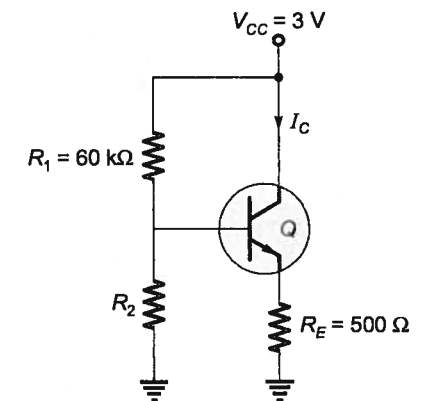
Q.12 In the circuit shown below, the silicon npn transistor Q has a very high value of  $\beta$ . The required value of  $R_2$  in kΩ to produce  $I_C = 1$  mA is



- (a) 20 (b) 30  
(c) 40 (d) 50

[GATE-2013]

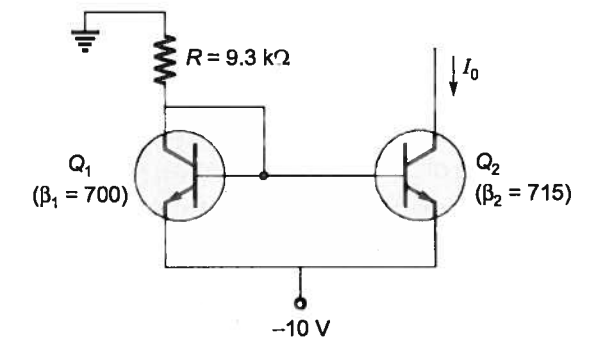
Q.13 In the silicon BJT circuit shown below, assume that the emitter area of transistor  $Q_1$  is half that of transistor  $Q_2$



The value of current  $I_O$  is approximately


- (a) 0.5 mA (b) 2 mA  
(c) 9.3 mA (d) 15 mA

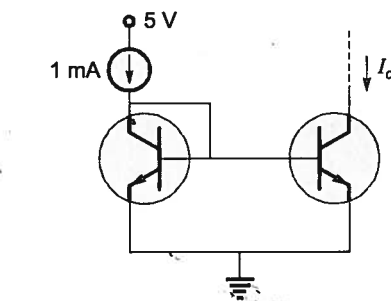Q.14 In the current mirror circuit shown below. The transistor parameters are  $V_{BE} = 0.7$  V,  $\beta = 50$  and early voltage is infinite. Assume transistor are matched




- (a) 1.04 mA (b) 1.68 mA  
(c) 962 μA (d) 432 μA

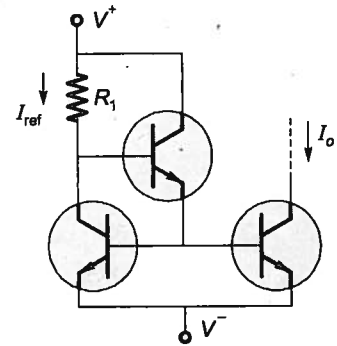**Q.15** Consider the basic three transistor current source in figure below. Assume all transistors are matched with finite gain and early voltage  $V_A = \infty$ . The expression for  $I_o$  is




- (a)  $\frac{I_{req}}{1 + \frac{2}{1 + \beta}}$  (b)  $\frac{I_{req}}{1 + \frac{1}{2 + \beta}}$   
(c)  $\frac{I_{req}}{1 + \frac{2}{\beta(1 + \beta)}}$  (d)  $\frac{I_{req}}{1 + \frac{1}{\beta(2 + \beta)}}$

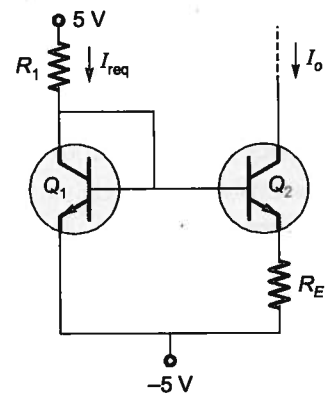**Q.16** Consider the wilder current source shown below. Both of transistor are identical and  $\beta \gg 1$  and  $V_{BE1} = 0.7$  V. The value of resistance  $R_1$  and  $R_E$  to produce  $I_{req} = 1$  mA and  $I_o = 12$   $\mu$ A is ( $V_T = 26$  mV)




- (a) 9.3 k $\Omega$ , 18.23 k $\Omega$   
(b) 9.3 k $\Omega$ , 9.58 k $\Omega$   
(c) 15.4 k $\Omega$ , 16.2 k $\Omega$   
(d) 15.4 k $\Omega$ , 34.4 k $\Omega$

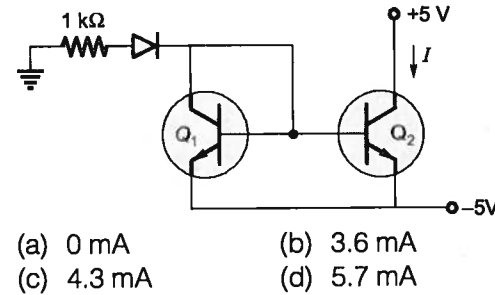**Q.17** Two perfectly matched silicon transistor are connected as shown in the figure. Assuming the  $\beta$  of the transistors to be very high and the forward voltage drop in diodes to be 0.7 V, the value of current is



- (a) 0 mA (b) 3.6 mA  
(c) 4.3 mA (d) 5.7 mA

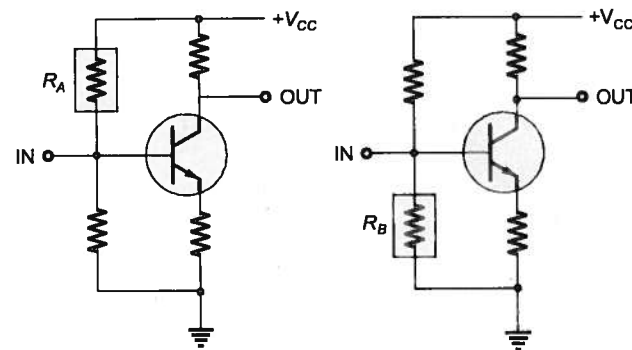**Q.18** In the following two non-linear transistor biasing circuits,



the resistors,

- (a)  $R_A$  and  $R_B$ , both have negative temperature coefficient  
(b)  $R_A$  and  $R_B$ , both have positive temperature coefficient  
(c)  $R_A$  has negative temperature coefficient and  $R_B$  has positive temperature coefficient  
(d)  $R_A$  has positive temperature coefficient and  $R_B$  has negative temperature coefficient

**Q.19** To avoid thermal runaway in the design of an analog circuit, the operating point of the BJT should be such that it satisfies the condition


- (a)  $V_{CE} = \frac{1}{2} V_{CC}$  (b)  $V_{CE} \leq \frac{1}{2} V_{CC}$   
(c)  $V_{CE} > \frac{1}{2} V_{CC}$  (d)  $V_{CE} \leq 0.78 V_{CC}$

**Q.20** The condition to be satisfied to prevent thermal runaway in a transistor amplifier where ( $P_c$  = Power dissipated at Collector,  $T_j$  = Junction temperature,  $T_A$  = Ambient temperature,  $\theta$  = Thermal resistance) is


- (a)  $\frac{\delta P_c}{\delta T_j} > \frac{1}{\theta}$  (b)  $\frac{\delta P_c}{\delta T_A} < \frac{1}{\theta}$   
(c)  $\frac{\delta P_c}{\delta T_j} < \frac{1}{\theta}$  (d)  $\frac{\delta P_c}{\delta T_A} > \frac{1}{\theta}$

## Numerical Data Type Questions

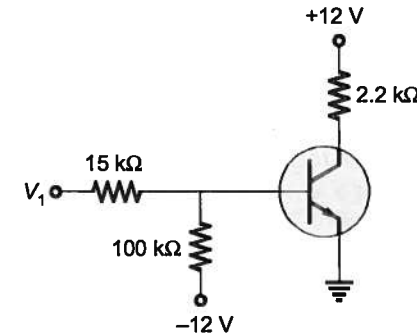**Q.21** For the transistor shown below,  $\beta = 30$  and  $V_{CEQ} = 6$  V. The value of  $V_1$  is \_\_\_\_\_ Volt.




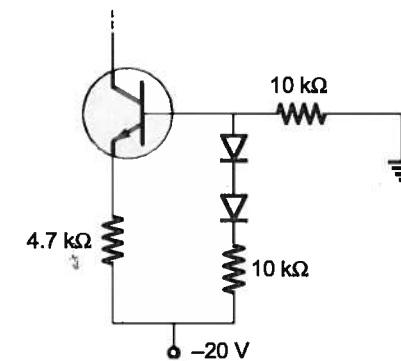**Q.22** In the bipolar current source of figure shown below, the diode voltage and transistor base-emitter voltage are equal




If base current is neglected, then collector current is \_\_\_\_\_ mA.

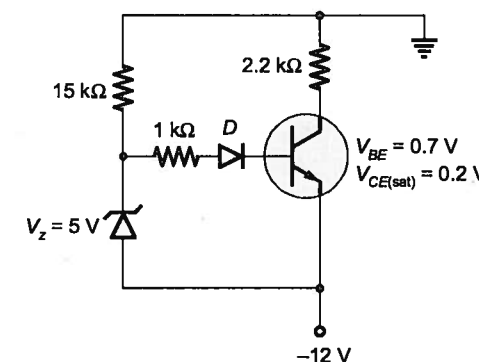**Q.23** The transistors used in the circuit shown below has  $\beta = 30$  and  $I_{CBO}$  is negligible.




If the forward voltage drop of diode is 0.7 V, then the current through collector will be \_\_\_\_\_ mA.

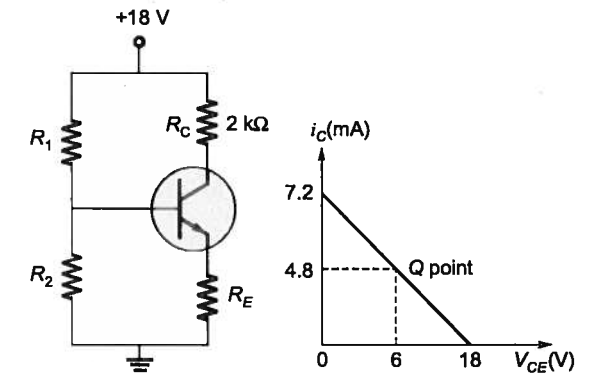**Q.24** The transistor circuit and its DC load line is shown in figure given below.




For the transistor,  $\beta = 120$ . What is the value of emitter resistance ( $R_E$ ) at Q-point (in k $\Omega$ )?

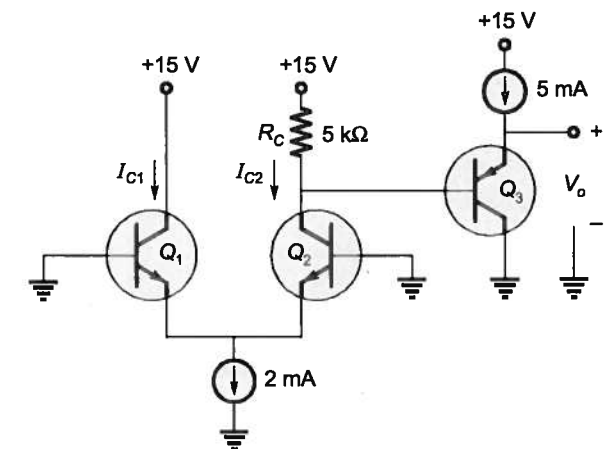**Q.25** In the circuit shown below assume that the transistors  $Q_1$  and  $Q_2$  have identical characteristics. All of the transistor operate in active region and  $\beta = 100$ . The value of output voltage  $V_o$  is \_\_\_\_\_ volts.



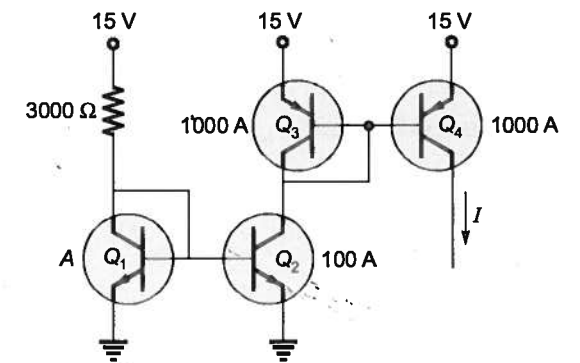
**Q.26** Consider the circuit shown in figure.




All the transistors have  $\beta = \infty$ , and  $V_{BE\text{active}} = 0.7$  for n-p-n BJT  $Q_1$  and  $Q_2$ . The transistor  $Q_1$  and  $Q_2$  are exactly same, the only difference is that cross-section area of  $Q_2 = 100$  times the cross-section area of  $Q_1$ .  $Q_3$  and  $Q_4$  are p-n-p BJT the cross-section area of  $Q_3$  is equal to cross-section area of  $Q_4$  that is equal to 1000 times the cross-section area of  $Q_1$ . The value of  $I$  is \_\_\_\_ A.



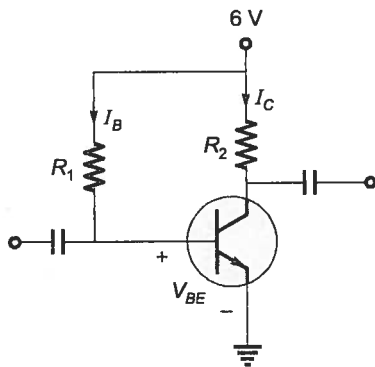- T1. In the circuit shown below,  $\beta = 150$ ,  $V_{BE} = 0.7$  V and it is operating at Q-point (3 V, 1.5 mA). If  $\beta$  increases to 200, the new operating point will be  
 (a) 2.88 V, 1.56 mA (b) 5.40 V, 3.50 mA  
 (c) 3.55 V, 4.60 mA (d) 1.06 V, 2.46 mA




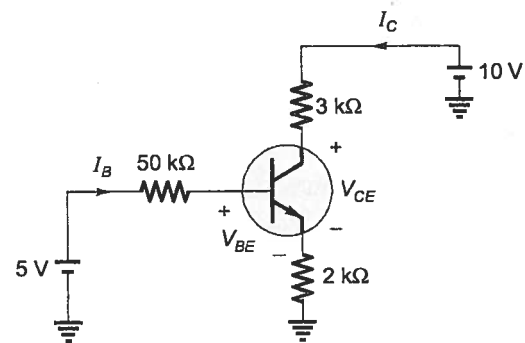- T2. In circuit shown transistor has  $\beta = 100$ .  $V_{BE(\text{sat})} = 0.8$  V and  $V_{CE(\text{sat})} = 0.2$  V. Then the region of operation



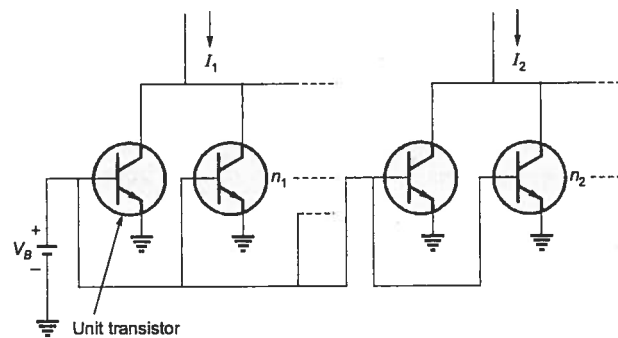- (a) active region (b) saturation region  
 (c) cut-off region (d) reverse-active region

- T3. An integrated circuit requires two current sources;  $I_1 = 0.2$  mA and  $I_2 = 0.3$  mA. Assuming that only integer multiples of a unit bipolar transistor having  $I_s = 3 \times 10^{-16}$  amp can be placed in parallel, and only a single voltage source  $V_B$  is available, the minimum number of unit transistor required for the circuit are



- |     | $n_1$ | $n_2$ |
|-----|-------|-------|
| (a) | 1     | 2     |
| (b) | 2     | 3     |
| (c) | 4     | 6     |
| (d) | 8     | 12    |

