

# 3

## Memory and I/O Interfacing



### Multiple Choice Questions

- Q.1** RAM and ROM, both are  
 (a) Sequentially accessed memory  
 (b) Randomly accessed memory  
 (c) Either (a) or (b)  
 (d) RAM: Randomly accessed, ROM sequentially accessed

- Q.2** Memory chips of four different sizes as below are available :

1. 32 K × 4
2. 32 K × 16
3. 8 K × 8
4. 16 K × 4

All the memory chips as mentioned in the above list are Read/Write memory. What minimal combination of chips alone can map full address space of 8085 microprocessor?

- (a) 1 and 2      (b) 1 only  
 (c) 2 only      (d) 4 only

[IES-2005]

- Q.3** A memory of 8 KB is designed using 2048 × 8 RAM chips. The number of chips required are

- (a) 4      (b) 6  
 (c) 8      (d) 16

- Q.4** In a 512 × 4 ROM chip, the number of address lines are

- (a) 512      (b) 4  
 (c) 9      (d) 11


- Q.5** Which of the following components are used in interfacing memory with microprocessor

- (a) Tristate buffer      (b) Encoder  
 (c) Latch      (d) All of the above

- Q.6** Ending address of an 8 KB ROM is B72E H find starting address

- (a) D72D H      (b) 972F H  
 (c) 6543 H      (d) None

 
- Q.7** Consider the 3 × 8 decoder given below



If this to be used with 8085 to generate read and write control signals then valid outputs are


- (a)  $D_0, D_1, D_2, D_3, D_4, D_5, D_6, D_7$   
 (b)  $D_0, D_1, D_2, D_4, D_5, D_6$   
 (c)  $D_1, D_2, D_5, D_6$   
 (d)  $D_0, D_3, D_4, D_7$

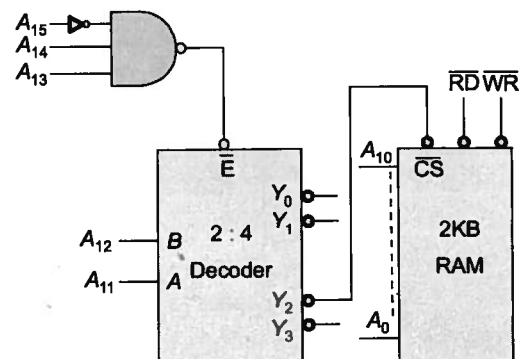- Q.8** Memory map of given interfacing logic is



- (a) 6800 H - 6FFF H  
 (b) 7800 H - 7FFF H  
 (c) 7000 H - 77FF H  
 (d) None

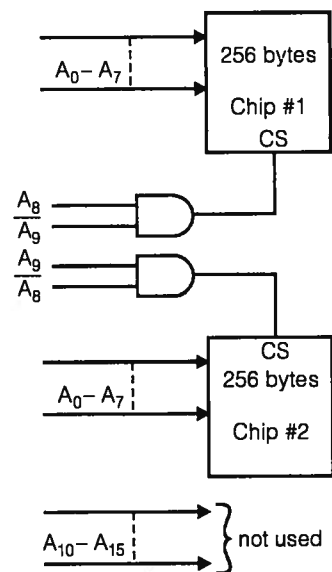
**Q.9** What memory address range is NOT represented by chip #1 and chip #2 in the figure.  $A_0$  to  $A_{15}$  in this figure are the address lines and CS means Chip select.



- (a) 0100-02FF (b) 1500-16FF  
(c) F900-FAFF (d) F800-F9FF

[GATE-2005]

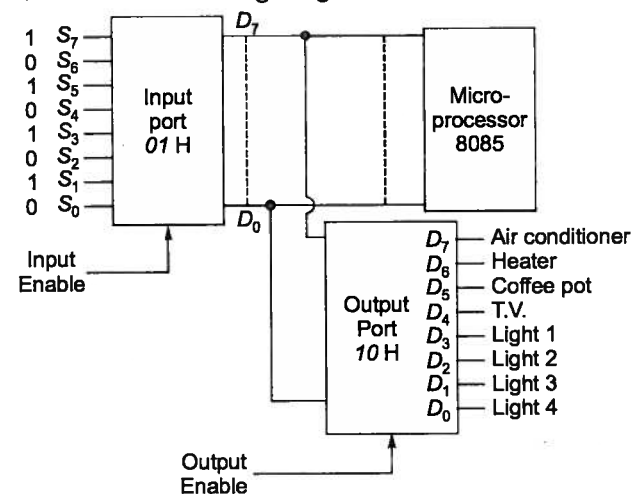**Q.10** Consider the figure given below.




The following instructions are executed.  
IN 01H  
XRI C2H  
RAL  
OUT 10H

Which of the following statements is/are true.

- (i) Air conditioner and coffee pot are ON.  
(ii) Heater and T.V. are ON.  
(iii) Only 2 Lights are ON.  
(iv) T.V. and only Light 4 are ON.  
(a) (ii) and (i) (b) (ii) only  
(c) (iii) and (iv) (d) (ii) and (iv)

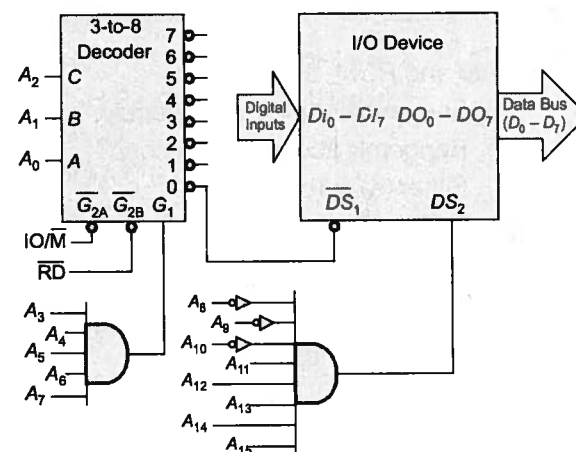**Q.11** For the 8085 microprocessor, the interfacing circuit to input 8-bit digital data ( $DI_0 - DI_7$ ) from an external device is shown in the figure. The instruction for correct data transfer is



- (a) MVI A, F8 H (b) IN F8 H  
(c) OUT F8 H (d) LDA F8F8 H

[2014 : 2 Marks, Set-2]

**Q.12** The following is not true for RS232 standards

- (a) It establishes the way data is coded  
(b) It defines signal voltage levels  
(c) Does not decide data transmission rate  
(d) It defines standard connector configurations

**Q.13** The interfacing device used to generate accurate time delay in a microcomputer system is

- (a) INTEL 8251 (b) INTEL 8253  
(c) INTEL 8257 (d) INTEL 8259

**Q.14** What is the maximum memory that can be interfaced with INTEL 8086?

- (a) 64 KB (b) 1 MB  
(c) 8 KB (d) 2 MB

## Numerical Data Type Questions

**Q.15** The internal memory of INTEL 8085 is \_\_\_\_\_ byte.

**Q.16** Maximum number of  $256 \times 4$  memory chips that can be interfaced with INTEL 8085 microprocessor are \_\_\_\_\_.

**Q.17** A read write memory chip has a capacity of 32 kb. If the memory chip is having equal number address lines and data lines, then minimum number of data lines are \_\_\_\_\_.

**Q.18** A memory system of 128 K bytes needs to be designed with RAM chips of 2 K bytes each and a decoder circuitry constructed with  $1 \times 2$  decoder chips with "enable" input. The minimum number of decoder chips required in design are \_\_\_\_\_.

**Q.19** In INTEL 8085, suppose the peripheral mapped I/O has address length of M and memory mapped I/O has address length of N. Then  $M + N =$  \_\_\_\_\_.

## Conventional Questions


**Q.20** Describe various interfacing components.

**Q.21** Design a memory of 8 KB using  $2048 \times 8$  RAM chips such that the memory map is 2000 H to 3FFF H.

**Q.22** What are the differences between memory mapped I/O and I/O mapped I/O?

**Q.23** Write an ALP to access a data byte from port address 60 H and send it to port address 70 H where a display is connected. Draw the required interfacing logic circuit.

 **Q.24** If the output of the NAND gate is connected to a memory chip  $\overline{CS}$  line then find the capacity and memory map of the memory chip.




## Try Yourself

**T1.** If a page of memory is assumed to be 256 bytes then in how many pages total memory of 8085 can be treated ?

[Ans: 256]

**T2.** A 1 Kbyte memory module has to be interfaced with an 8-bit microprocessor that has 16 address lines. The address lines  $A_0$  to  $A_9$  of the processor are connected to the corresponding address lines of the memory module. The active low chip select  $\overline{CS}$  of the memory module is connected to the  $y_5$  output of a 3 to 8 decoder with active low outputs.  $S_0$ ,  $S_1$ , and  $S_2$  are the input lines to the decoder, with  $S_2$  as the MSB. The decoder has one active low  $\overline{EN}_1$  and one active high  $EN_2$  enable lines as shown below. The address range(s) that gets mapped onto this memory module is (are)

 

- (a)  $3000_H$  to  $33FF_H$  and  $E000_H$  to  $E3FF_H$   
(b)  $1400_H$  to  $17FF_H$   
(c)  $5300_H$  to  $53FF_H$  and  $A300_H$  to  $A3FF_H$   
(d)  $5800_H$  to  $5BFF_H$  and  $D800_H$  to  $DBFF_H$

[Ans: (d)]