

Choppers

6


A chopper is a high speed on/off semiconductor switch. Chopper is a static device that converts fixed dc input voltage to a variable dc output voltage directly.

Remember:

For medium power application we use IGBT and GTO, in chopper.

Step Down Chopper

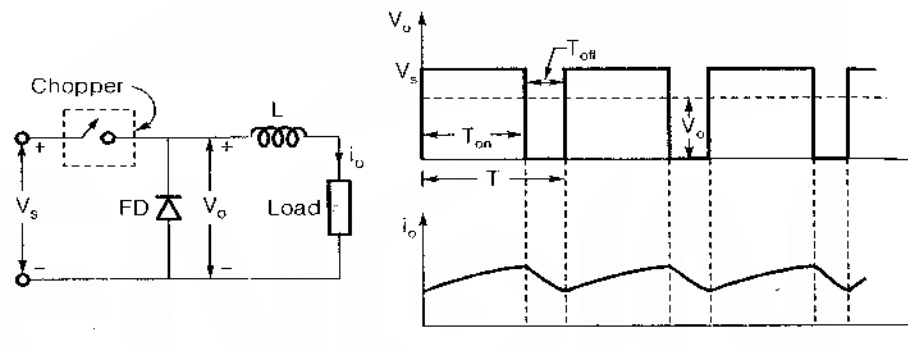Average output voltage V_o is always less than the input voltage V_s .



Duty cycle

$$\alpha = \frac{T_{ON}}{T} = \frac{T_{ON}}{T_{ON} + T_{OFF}} ; \alpha < 1$$

Average load voltage

$$V_o = \alpha V_s$$

RMS load voltage

$$V_{RMS} = \sqrt{\alpha} V_s$$

Average load current

$$I_o = \frac{V_o}{R} = \frac{\alpha V_s}{R}$$

RMS load current


$$I_{RMS} = \frac{\sqrt{\alpha} V_s}{R}$$

Note:

- Above formulae valid only for continuous conduction.
- Inductor connected in series with load is used to reduce the ripple content in output current.

Step Up Chopper

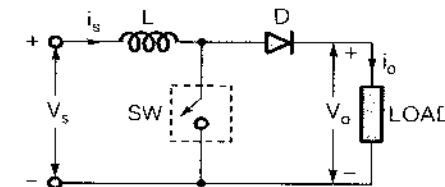Average output voltage V_o is more than input DC voltage V_s .



Average load voltage


$$V_o = \frac{1}{1 - \alpha} V_s$$

- For a basic DC to DC converter, the critical inductance of the filter circuit is given by

$$L = \frac{V_o^2 (V_s - V_o)}{2f V_s P_o}$$

where, V_o = Load voltage
 V_s = Source voltage
 P_o = Load power
 f = Chopping frequency

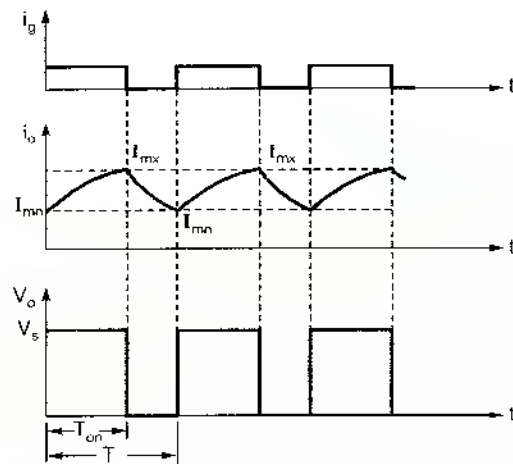Steady State Time-Domain Analysis of Type-A Chopper



□ Maximum value of current

$$I_{mx} = \frac{V_s}{R} \left[\frac{1 - e^{-T_{on}/T_a}}{1 - e^{-T/T_a}} \right] - \frac{E}{R}$$

□ Minimum value of current

$$I_{mn} = \frac{V_s}{R} \left[\frac{e^{T_{on}/T_a} - 1}{e^{T/T_a} - 1} \right] - \frac{E}{R}$$

where,

$$T_a = \frac{L}{R}$$

□ Per unit ripple current

$$\text{p.u. ripple current} = \frac{(I_{mx} - I_{mn})}{V_s/R} = \frac{(1 - e^{-\alpha T/T_a})(1 - e^{-(1-\alpha)T/T_a})}{(1 - e^{-T/T_a})}$$

Note:
The peak to peak ripple current has maximum value ΔI_{mx} when duty cycle $\alpha = 0.5$.
.....

□ For $\alpha = 0.5$

$$\Delta I_{mx} = \frac{V_s}{R} \tanh \frac{R}{4fL}$$

□ If $4fL \gg R$ then $\tanh \frac{R}{4fL} \approx \frac{R}{4fL}$

$$\Delta I_{mx} = \frac{V_s}{4fL}$$

Remember:


Higher the inductance, ripple is minimum.

□ The value of duty cycle at the limit of continuous conduction

$$\alpha' \geq \frac{T_a}{T} \ln \left[1 + \frac{E}{V_s} (e^{T/T_a} - 1) \right]$$

where, α' measures the limit of continuous conduction.

Load Current Discontinuous

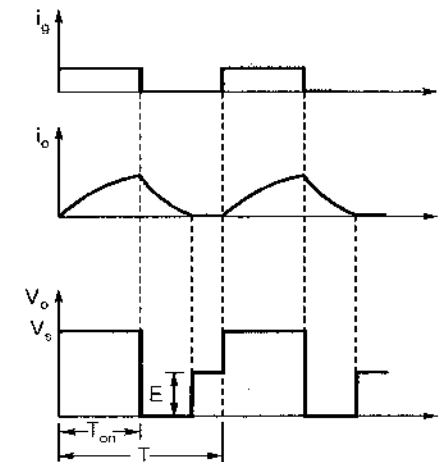

□ Minimum value of current

$$I_{mn} = 0$$

- ❑ Maximum value of current

$$I_{mx} = \frac{V_s - E}{R} (1 - e^{-T_{on}/T_a})$$

- ❑ Extinction time (t_x)

$$t_x = T_{on} + T_a \ln \left[1 + \frac{V_s - E}{E} (1 - e^{-T_{on}/T_a}) \right]$$

- ❑ Average output voltage

$$V_o = \alpha V_s + \left(1 - \frac{t_x}{T} \right) E$$

■■■■■